
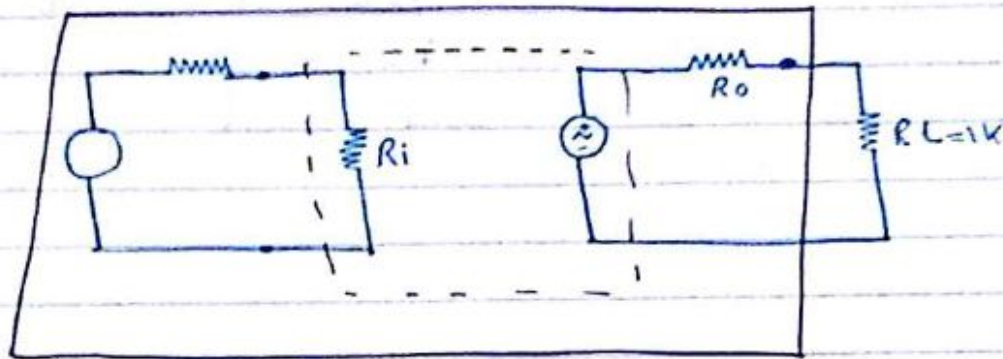


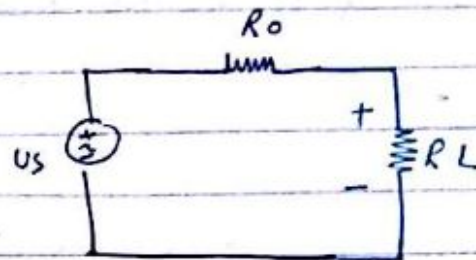* Emitter Follower \rightarrow The output voltage follows the Emitter Voltage :



Current Amplifier
Voltage buffer





The Common collector is usually designed to have a $AV=1$ with very low R_o and very high R_i .

hence, it acts as a buffer ckt without voltage gain $\approx < 1$, but with current gain, so we still get power Amplification.

even if there is R_C it's still a common collector ckt.

⇒ Common collector :->

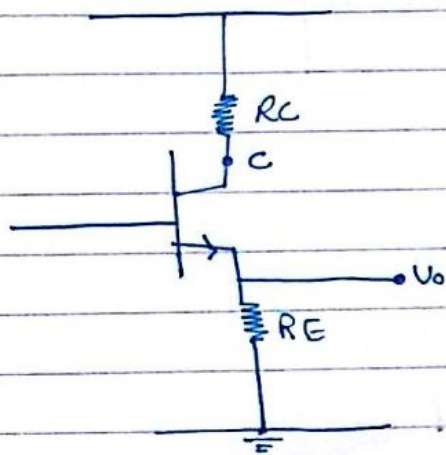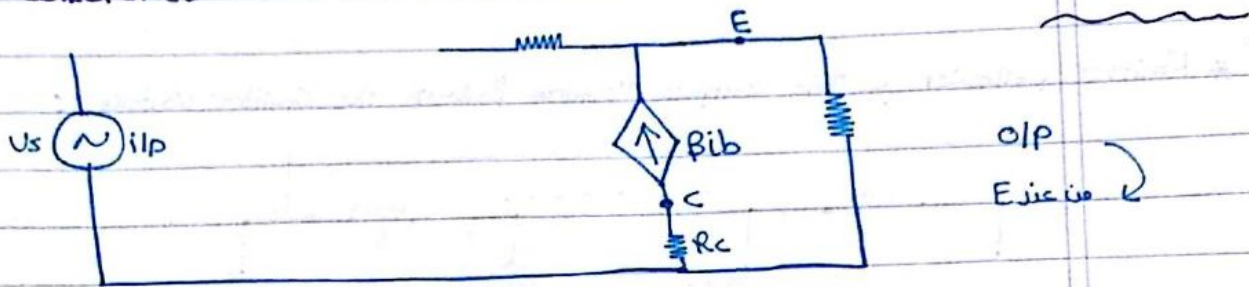


⇒ It is still a common collector ckt.

R_C لا يلا دور في β_{ib} (لا دور في)
 β_{ib} لا يلا دور في R_C *
 β_{ib} لا يلا دور في R_C *
 β_{ib} لا يلا دور في R_C *

(مبنيًا، لدارة يوجد R_C في i_{ib} مع β_{ib} و R_C)

* The common Base Amplifier :->

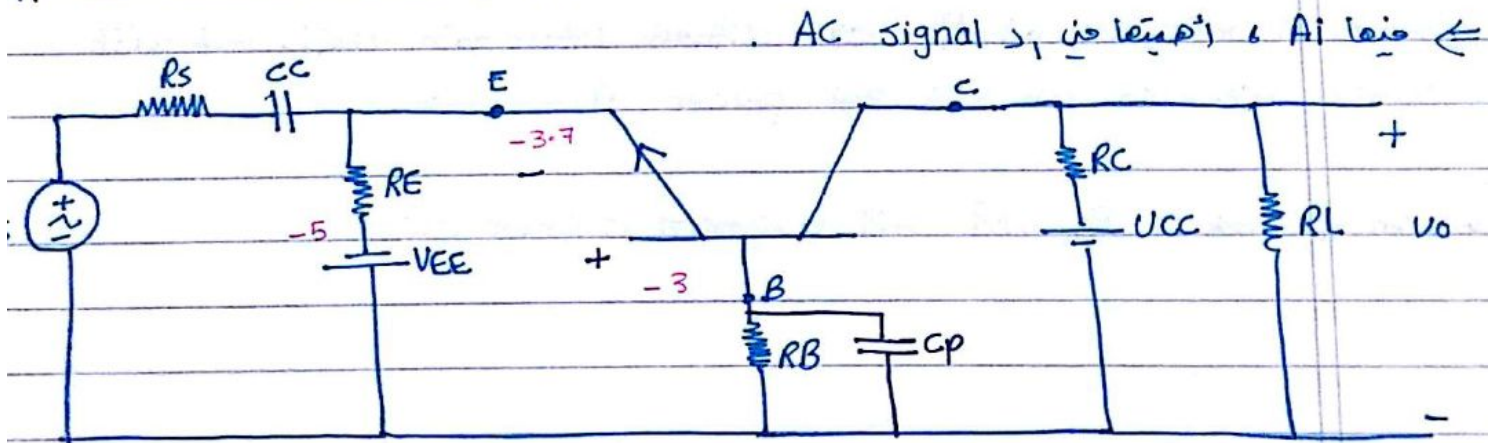


AC signal \rightarrow i_{ib} \leftarrow A_i \leftarrow

$$(-3) - (-3.7) = 0.7$$

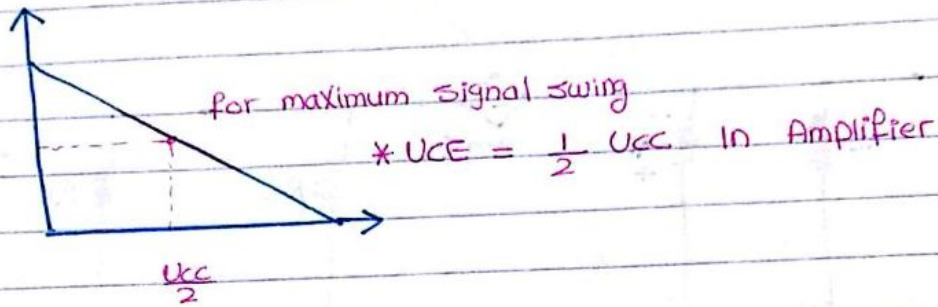(26)

* IC و VCC علاقة في IB خط علاقة في
 * VCC و RC و UCE خط علاقة في



* Coupling Capacitor (CC) → يجمع Signals 2 مع بعض

* Signal يدخل من عند E (i/p) ويخرج من عند C (o/p)


* B من موصول مع ground مباشرة حتى توصلا بتسبكتها مع
 Capacitor في حالة AC بحيز Short CKT



bypass Capacitor (Cp)

يغير اتجاه التيار (قوتلية)

Common Emitter with bypass capacitor:

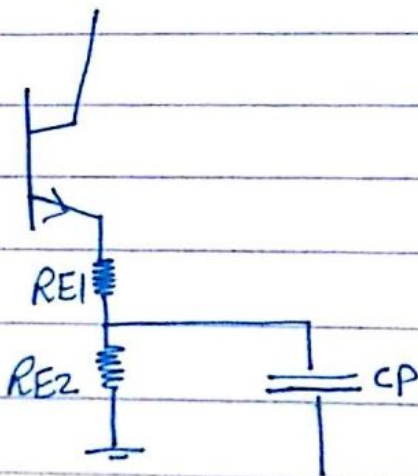


* note :- $V_{BE} \approx 0.7$

$V_{BE} \neq 0.7 = \Gamma_{\pi} I_b$

* Common Base \Rightarrow AC eq. CKT \Rightarrow r_{π} \parallel R_B

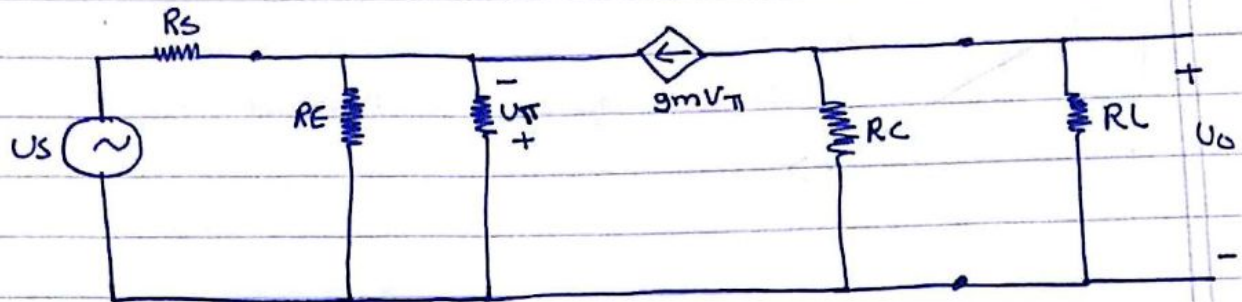* The AC eq. CKT is as shown: \Rightarrow



* It can be shown (see book) that: \Rightarrow $r_{\pi} \parallel R_B$

1] $A_V = g_m (R_C \parallel R_L)$ with Justification.

2] $A_i = \frac{I_o}{I_i} = \frac{\beta}{1+\beta} = \alpha \approx 1$ ($\alpha = 0.998 < 1$) with Justification.


3] $R_{ie} \approx \frac{r_{\pi}}{1+\beta}$ with Justification.

4] $R_o \approx r_o \parallel R_C$ " "


* Note: (In the exam):

\Rightarrow Derive, Show that, obtain \Rightarrow استنبط

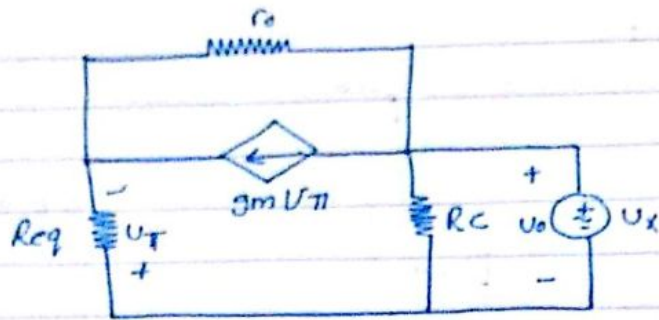\Rightarrow write down, list, mention, use \Rightarrow $\text{استخدم بدون اشتقاق}$



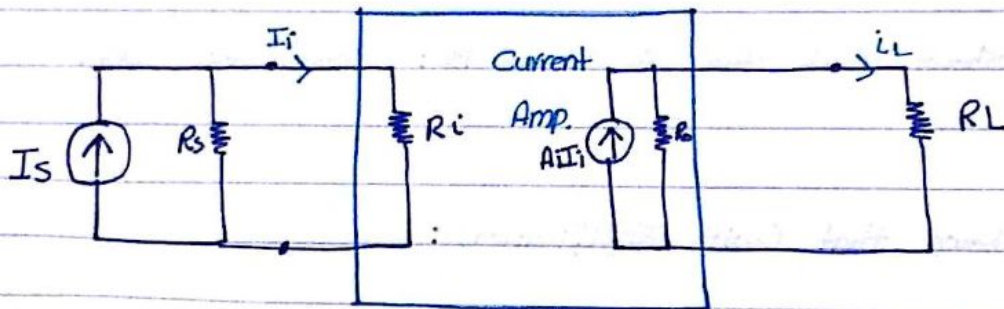* Since A_i is almost 1, R_{ie} is very low (i/p resistance) and the (o/p resistance) is very high, then the common Base Amplifier acts as a current Buffer.




$$I_i = \frac{R_s}{R_s + R_i} I_s$$

$$i_L = \frac{R_o}{R_o + R_L} (A_i I_i)$$

* The Darlington Pair :->

7/8/2017

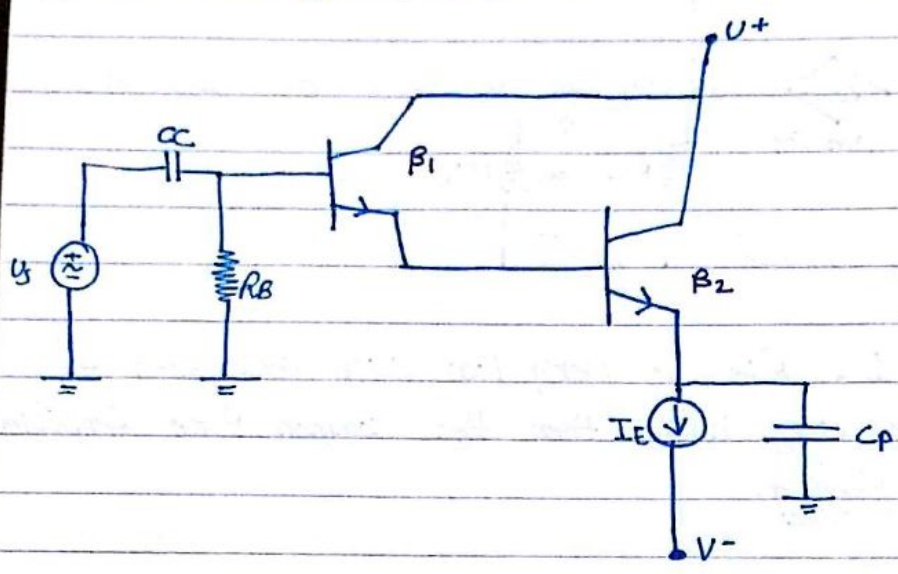

** It has Very high current gain.

=> It can be shown that the AC model is: (from book) \Rightarrow

* It can be shown that (with justification):

1] $A_i \approx \beta_1 \beta_2 \approx 10^4 \gg 1$ (Very high)

2] $R_i \approx 2\beta_1 r_{\pi 2} \Rightarrow$ considered very large.

∴ A_i Very high, why?

$A_i \approx (1 + \beta_2) \underline{i_{b2}}$

$(1 + \beta_2) \underline{i_{e1}}$


$(1 + \beta_2) (1 + \beta_1) i_{b1}$

$I_i = i_{b1}$

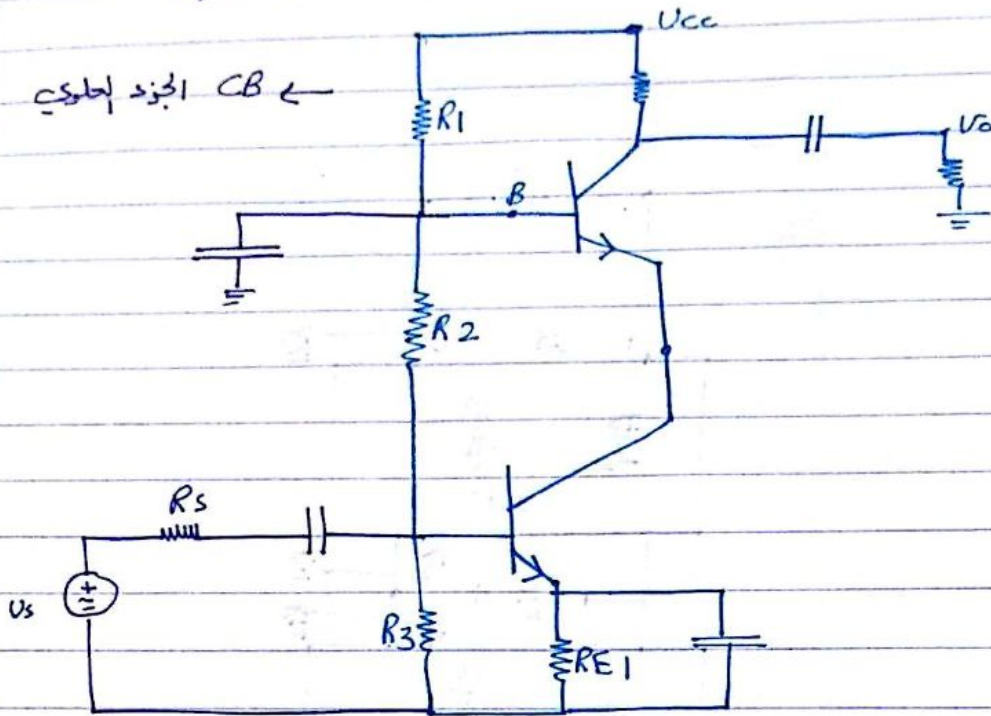(30)

* The Cascode Amplifier: \Rightarrow

\hookrightarrow It is a common Emitter (CE) stage driving a CB stage.



(Electronic CKT)

* It can be shown that the AC CKT model is (see book): \Rightarrow

* electronic CKT \rightarrow Transistors \hookrightarrow

* AC CKT \rightarrow (sources, R_i, C_i) \rightarrow CKT \rightarrow Transistors \hookrightarrow


* It can be shown that (with justification):

$$(i) AV \approx -g_m (R_C \parallel R_L) \gg -1$$

* Multi stage Amplifier \Rightarrow Darlington pair, cascode Amplifier

* Multistage Amplifier :

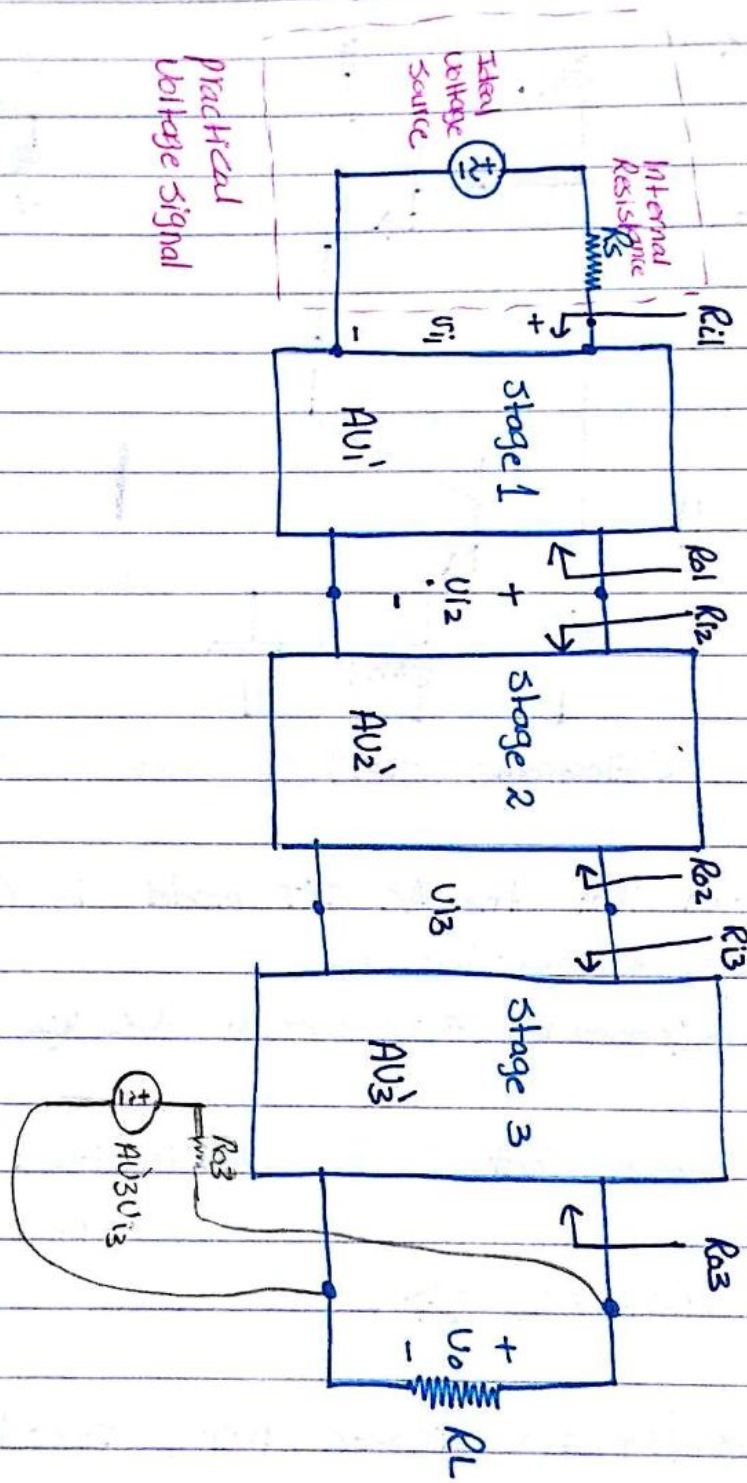↳ A multi stage Amplifier represented schematically as :



Practical
Voltage Signal

Ideal
Voltage
Source

Internal
Resistance
 R_S


$$\begin{aligned}
 * V_o &= \frac{R_L}{R_L + R_{o3}} A_{V3}' V_{i3} \\
 &\quad \downarrow \\
 &\quad \frac{R_{i3}}{R_{i3} + R_{o2}} A_{V2}' V_{i2} \\
 &\quad \quad \downarrow \\
 &\quad \quad \frac{R_{i2}}{R_{i2} + R_{o1}} A_{V1}' V_{i1} \\
 &\quad \quad \quad \downarrow \\
 &\quad \quad \quad \frac{R_{i1}}{R_{i1} + R_s} U_s
 \end{aligned}$$

$$\Rightarrow A_V = \frac{V_o}{U_s} = \frac{R_L}{R_L + R_{o3}} A_{V3}' \frac{R_{i3}}{R_{i3} + R_{o2}} A_{V2}' \frac{R_{i2}}{R_{i2} + R_{o1}} A_{V1}' \frac{R_{i1}}{R_{i1} + R_s} \quad **$$

where A_V' is the gain defined with respect to v_i and not with respect to U_s .

← Example 11

* Example :

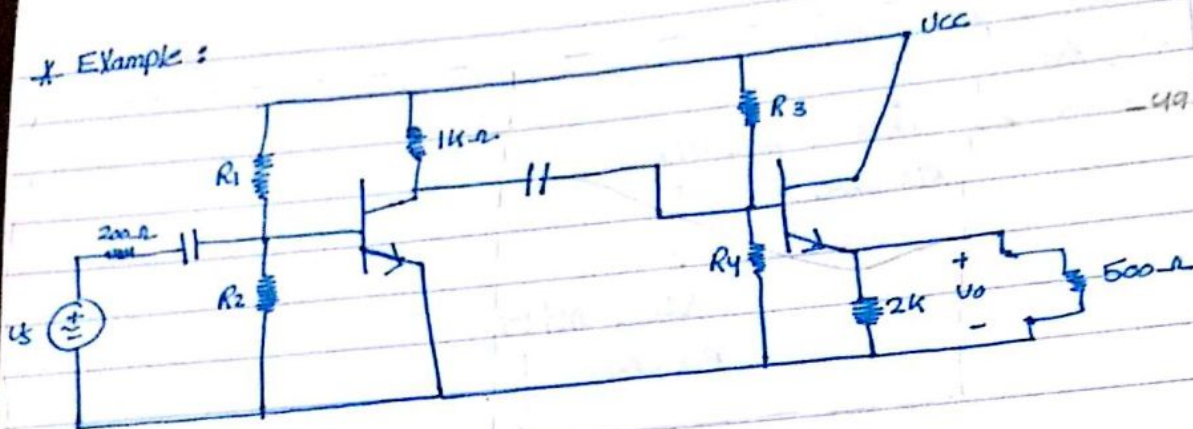

$$-49.2 \frac{500}{500 + 1000} = -16, \dots$$

→ Common Emitter ← → Common Collector ←

* Assume $R_1 \parallel R_2 = \infty \Omega$, $R_3 \parallel R_4 = \infty \Omega$, $R_{O1} = R_{O2} = \infty \Omega$
 $\beta_1 = \beta_2 = 99$, $r_{\pi 1} = r_{\pi 2} = 2k\Omega$.

* Stage 1 : 1st CE :

$$R_{i1} = \underbrace{R_1 \parallel R_2}_{\infty} \parallel \underbrace{(r_{\pi 1} + (1 + \beta_1) R_{E1})}_{R_{ib}} = r_{\pi 1} = 2k\Omega$$

$$R_{O1} = R_{C1} = 1k\Omega$$

$$A_{v1} = \frac{-\beta R_C}{r_{\pi} + (1 + \beta) R_E} = \frac{-99 \times 1k}{2k} = -49.5$$

(34)

* Stage 2: 1s CC :

$$R_{i2} = R_1 \parallel R_2 \parallel (\tau_{\pi 2} + (1+\beta)(r_{o2} \parallel R_{E2})) = 202 \text{ k}\Omega$$

2 + 100 x 2

$$A_{V2}' = \frac{(1+\beta)(R_{E2} \parallel r_{o2})}{\tau_{\pi 2} + (1+\beta)(R_{E2} \parallel r_{o2})} = \frac{200}{202} = 0.99$$

$$R_{o2} = \frac{\tau_{\pi 2} + R_S}{1+\beta} = \frac{2.2 \text{ k}}{100} = 22 \Omega$$

$$\Rightarrow A_V = \frac{V_o}{V_S} = \frac{R_L}{R_L + R_{o1}} \cdot A_{V3}' \cdot \frac{R_{i3}}{R_{i3} + R_{o2}} \cdot A_{V2}' \cdot \frac{R_{i2}}{R_{i2} + R_{o1}} \cdot A_{V1}' \cdot \frac{R_{i1}}{R_{i1} + R_S}$$

(In between = 1)

$$= \frac{500}{522} \times 0.99 \cdot \frac{2}{2+1} \times -49.5 = -31.2$$


!! قبل من AV في CE اياها

في CC يقال ان output Resistance

* DC and AC load lines =>

* consider the following CKT :

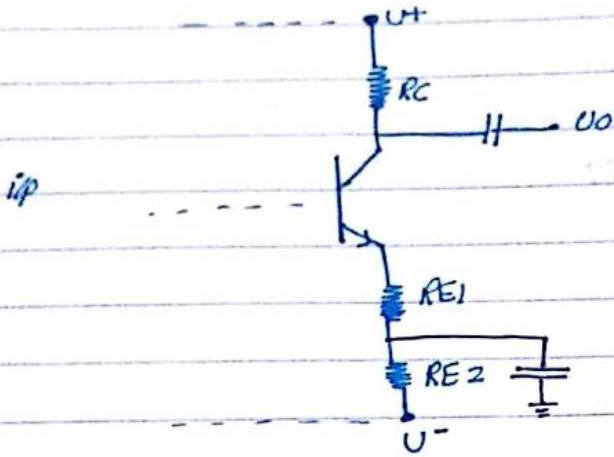
* load line إلى علاقة بـ i_c
 * Input و output i_c



* AU $RE2$ ip Uo

=> DC load line : (capacitors -> open CKT)
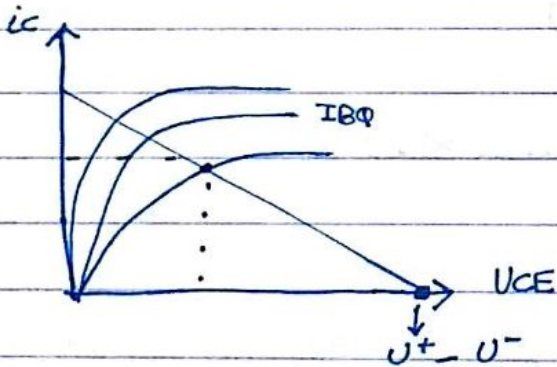
$$U^+ = R_C I_{CQ} + U_{CEQ} + (R_{E1} + R_{E2}) \frac{\beta + 1}{\beta} I_{CQ} + U^-$$





(36)

* AC load line :

$$R_c i_c + R_{E1} i_e + U_{ce} = 0$$
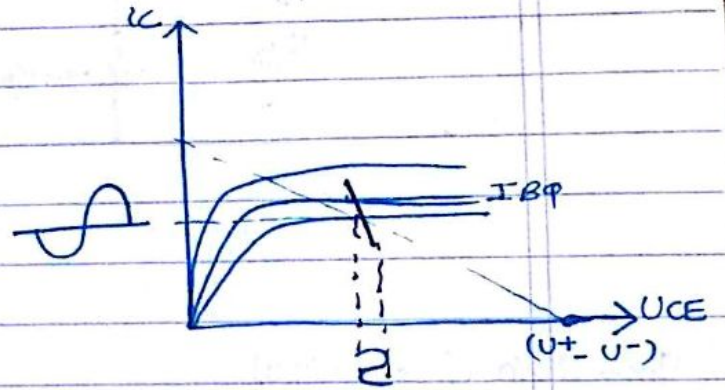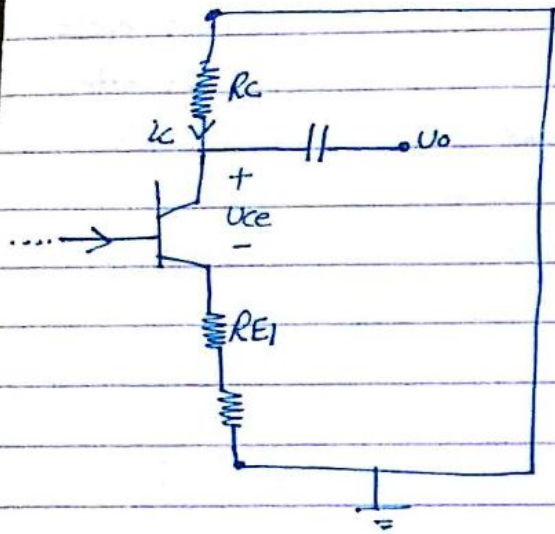
$$(R_c + \frac{B+1}{B} R_{E1}) i_c + U_{ce} = 0$$



(37)


* Ch 4 : FET Amplifier circuit.

↳ higher backing Density \rightarrow \rightarrow \rightarrow

\Rightarrow The small signal low freq. model of In-channel MOSFET :

- It can be shown that a model of N-mos transistor is :

* 10/8/2017

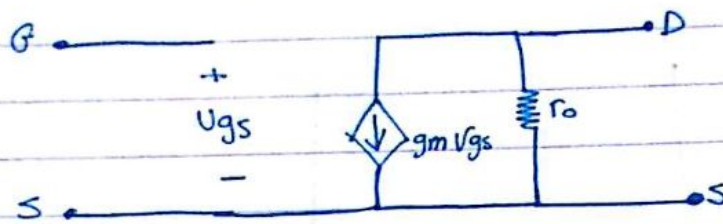

D: Drain
S: Source
G: Gate
 $I_G = 0$

$I_G = 0$ \rightarrow \rightarrow \rightarrow $g_m V_{gs}$ \rightarrow

$$g_m = 2k_n (V_{GS} - V_{TN})$$
$$= 2\sqrt{k_n I_{DQ}}$$


$$r_o = \frac{1}{\lambda I_{DQ}}$$

$$I_{DQ} = k_n (V_{GS} - V_{TN})^2 \rightarrow \text{Saturation mode.}$$

(38)


* The Common Source Amplifier :

R_{si} : Input source
 R_s : source

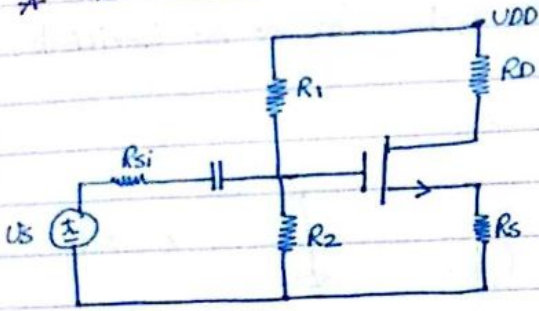

$I_D = I_S$

$i_d = i_s$

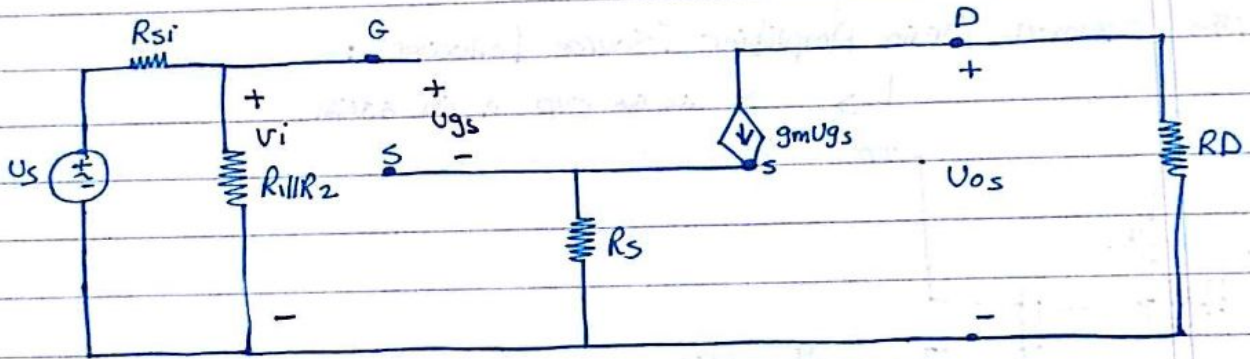

$V_o = -g_m V_{gs} R_D$

$V_i = V_{gs} + g_m V_{gs} R_s$

* $A_V = \frac{V_o}{V_s} = \frac{-g_m R_D}{1 + g_m R_s} \cdot \frac{R_1 || R_2}{R_1 || R_2 + R_{si}}$

$\Rightarrow V_{gs} = \frac{1}{1 + g_m R_s} V_i$

وہاں AV اور اس کے ساتھ ساتھ

$P_1 = 1 + g_m R_s = P_2$

$V_o = \frac{-g_m R_D}{1 + g_m R_s} V_i$

$R_1 || R_2$ کی بجائے V_i کا



بجائے V_s کا R_{si}

↓

$V_o = \frac{-g_m R_D}{1 + g_m R_s} \cdot \frac{R_1 || R_2}{R_1 || R_2 + R_{si}} V_s$ (39)

design

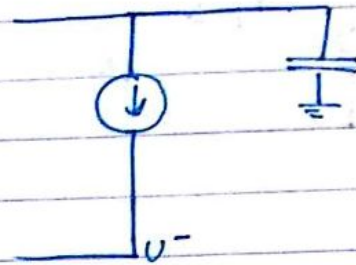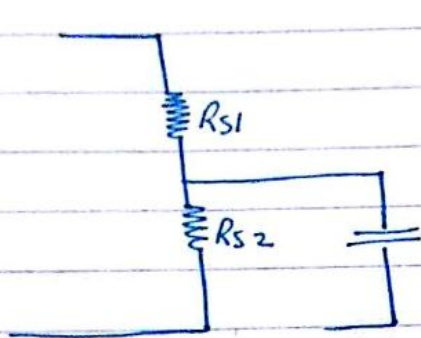
$$A_V \approx \frac{-g_m R_D}{1 + g_m R_S} \approx \frac{-R_D}{R_S} \quad \text{if } g_m R_S \gg 1 \quad \text{(has to be justified)}$$





No R_1

* The Common Drain Amplifier (Source follower) :->

↳ سابعاً في الـ O/P في الحالة الـ DC

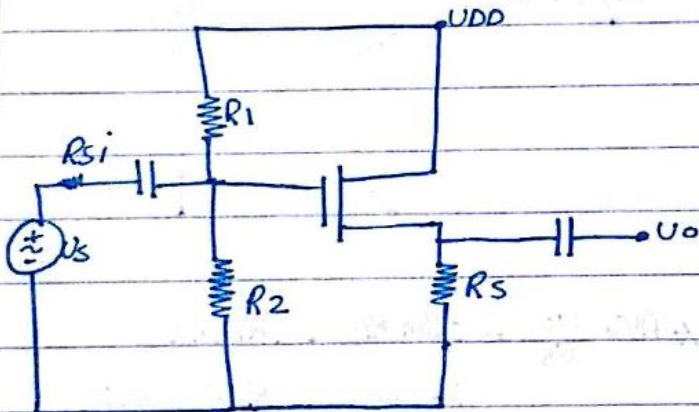

(40)

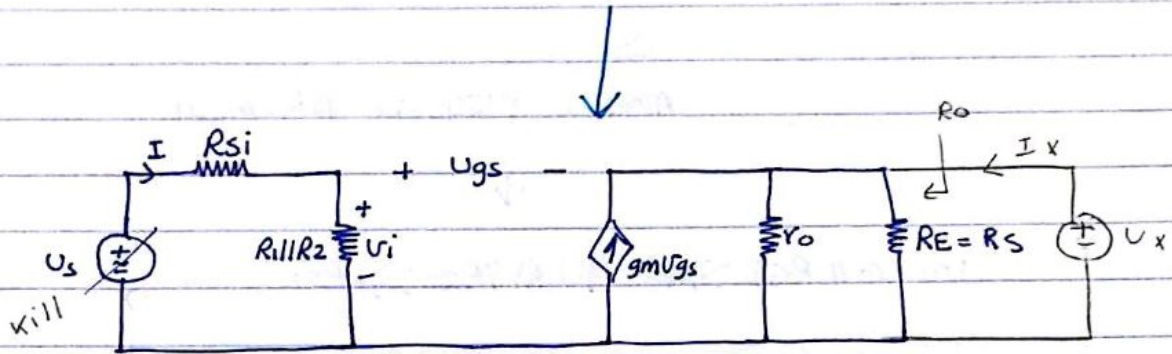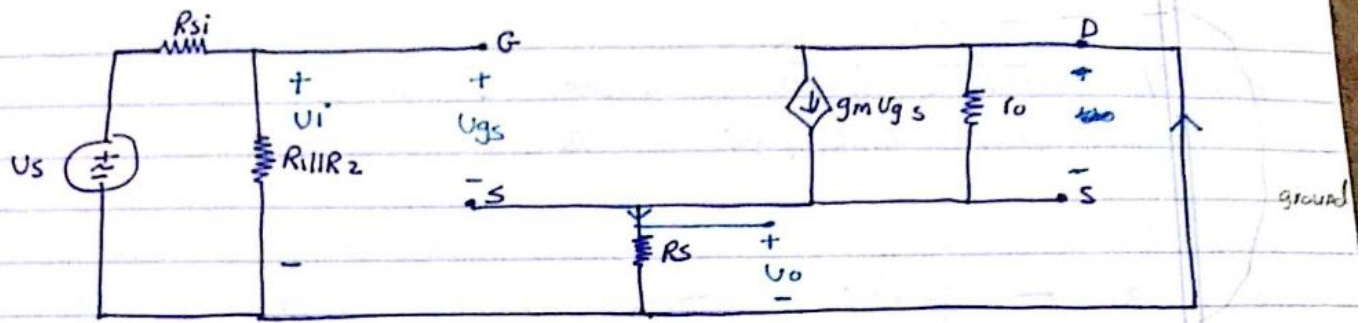

Source is killed $0 = V_i$ ←

$$V_o = g_m V_{gs} (r_o || R_E)$$

$$V_i = V_{gs} + g_m V_{gs} (r_o || R_E)$$

$$V_{gs} = \frac{1}{1 + g_m (r_o || R_E)} \cdot \underbrace{\frac{R_1 || R_2}{R_1 || R_2 + R_{si}}}_{V_i} \cdot U_s$$

$$V_o = \frac{g_m (r_o || R_E) \cdot R_1 || R_2}{1 + g_m (r_o || R_E) \cdot R_1 || R_2 + R_{si}} \cdot U_s$$

(41)

$$A_V = \frac{g_m (r_o \parallel R_E)}{1 + g_m (r_o \parallel R_E)} \cdot \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}} = \frac{V_o}{V_i}$$



$$R_1 \parallel R_2 \gg R_{Si}$$

المسألة أقل من المسألة ←



$$g_m (r_o \parallel R_E) \gg 1 \quad \& \quad R_1 \parallel R_2 \gg R_{Si}$$

$$A_V \approx 1$$

$$R_o = \frac{U_X}{I_X}$$

$$(R_{Si} I + R_1 \parallel R_2) I = 0$$

$$I = 0 \rightarrow V_i = 0$$

$$0 + V_{gs} + U_X = 0$$

$$V_{gs} = -U_X$$

(42)

$$I_X + g_m V_{gs} = \frac{V_X}{R_E \parallel r_o}$$

$$I_X = \left(g_m + \frac{1}{r_o \parallel R_E} \right) \cdot V_X$$

$$\frac{1}{R_o} = g_m + \frac{1}{r_o \parallel R_E} \rightarrow R_o = \frac{1}{g_m} \parallel (r_o \parallel R_s)$$

$\frac{1}{g_m} \rightarrow \bar{r}_{gs}$, g_m : conductance

$$R_o = \frac{1}{g_m} \parallel R_s \text{ if } r_o \gg R_s.$$

* EX: Derive A_V , R_i , R_o for:

i) The common source configuration.

ii) " " " " Drain " "


iii) " " " " Gate " "

(43)

* Ch 7: Frequency Response of Amplifiers (FR): >

13/8/2017

⇒ Typical FR of an Amplifier :

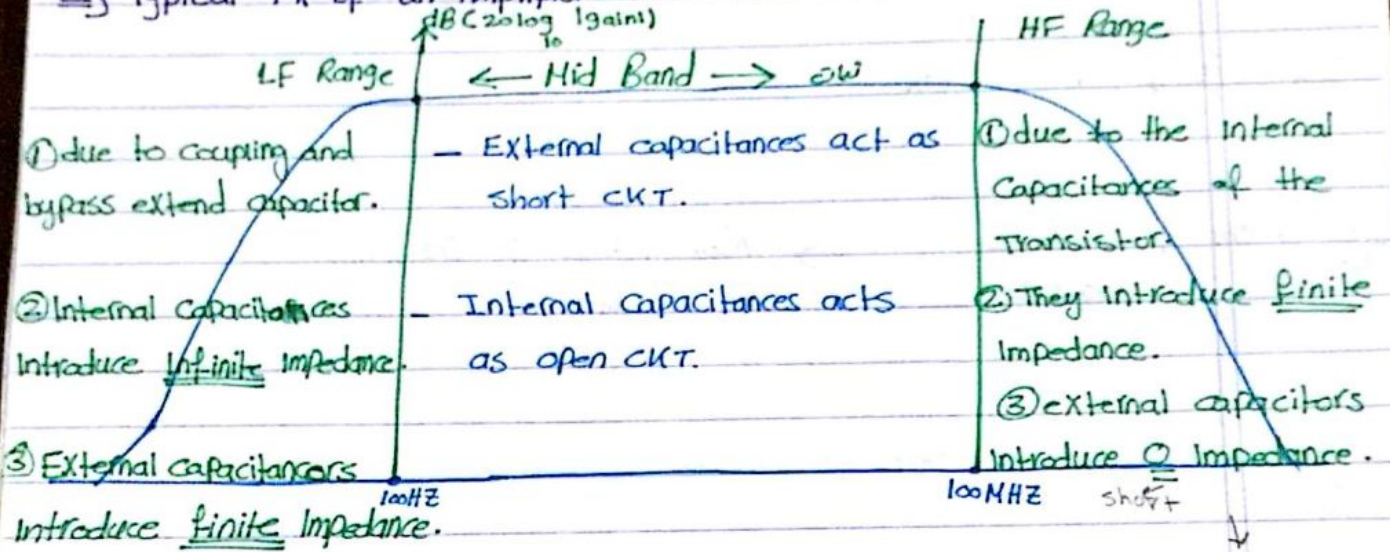


- ① due to coupling and bypass extend capacitor. — External capacitances act as short ckt.
- ② Internal capacitances introduce Infinite impedance. — Internal capacitances acts as open ckt.
- ③ External capacitances introduce finite impedance. — external capacitors introduce ∞ impedance.

↓
open ⇒ short

* Boding plot → compress information

* ...

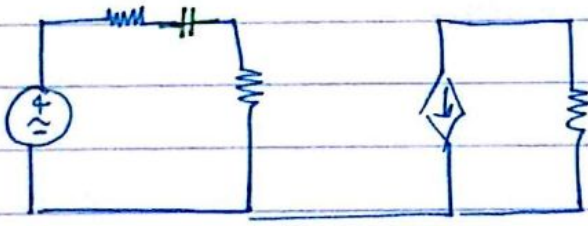* Frequency Component: Capacitors and Inductors




* Internal Impedance = pf

* External Impedance = MF

↑ p q l l s l e a i s e

$$Z = \frac{1}{\omega C} \quad (44)$$

14/8/2017

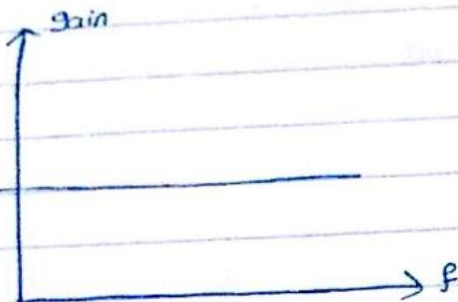


Amplifier characteristic without C & L (Ideal Amplifier)

* Coupling & by pass capacitor \rightarrow low frequency

* Internal capacitors \rightarrow High frequency

* Short and open circuit Time constant :

- given the following ckt :

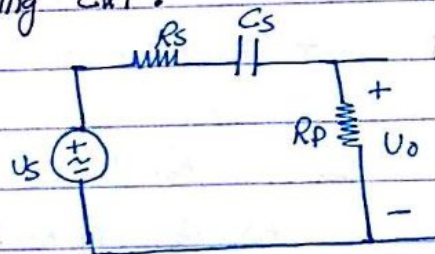

U_o Time constant *
is a first order s/c


$$\frac{U_o(s)}{U_s(s)} = \frac{R_p}{R_p + R_s + \frac{1}{sC_s}} = \frac{sR_p C_s}{1 + s(R_p + R_s)C_s} = \frac{A}{1 + Ts}$$

1 : dimension less \rightarrow Ts : dimension less \rightarrow $T = \text{Second}$, $s = \frac{1}{\text{Second}}$

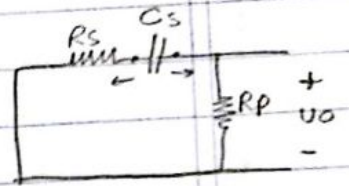(45)


* $\tau = (R_p + R_s) C_s$ known as time constant.

$R_p + R_s \rightarrow$ from CKT \rightarrow Kill $U_s \rightarrow$ short CKT
 \rightarrow calculate equ. Resistance from capacitor point of view.



* i.e. to get τ by inspection kill the independent source and obtain R_{eq} from the capacitor point of view.

* Consider now the following CKT:

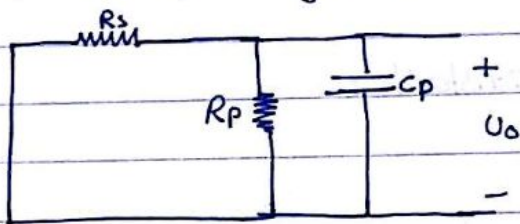


$$U_0(s) = \frac{R_p \parallel \frac{1}{sC_p}}{(R_s + R_p) \parallel \frac{1}{sC_p}} = \frac{R_p}{R_p + R_s + sR_p R_s C_p}$$

$$= \frac{R_p / (R_p + R_s)}{1 + \underbrace{((R_p R_s) / (R_p + R_s)) C_p s}_{\tau}}$$


$$\text{So, } \tau_p = (R_p \parallel R_s) C_p = \frac{R_p R_s}{R_p + R_s} C_p$$

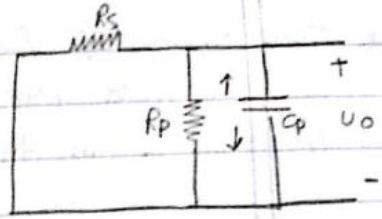(46)

* Same procedure to find τ by inspection.
 (Kill $U_s \rightarrow$ short ckt ...)



* Consider now the following CKT :

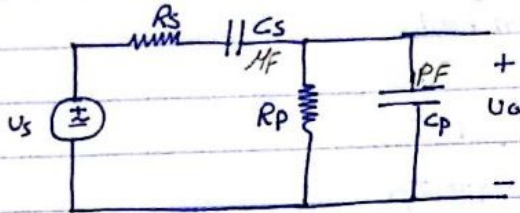

\Rightarrow Assume the two time constants are very well far apart.

* For Ranges of freq. where C_s has moderate Impedance value, C_p will have very large Impedance value, to the extent of considering it ∞ . In this case:

$$\tau_s = (R_p + R_s) C_s$$

Known as the open CKT time constant.

* إذا كان τ_1 و τ_2 متباعدان جداً
 معك يكون 2nd order system

↓
 بشكل تقريبي من خلال معرفة τ_1
 اعتبره (1st order) معبرتين
 بحيث τ_1 أقصر وأهم τ_2 لأنه
 τ فقط لل 1st order

↓
 الحالات مثل أن τ_1 واحد τ_2 \gg τ_1
 والباقي τ_2 (أو τ_1 كبير جداً)

Far apart

↓
 تقدير τ by inspection

↓
 جزر الكلام إذا كانوا جدا عن

بعض بزوج إذا لا ما

بزوج

↓
 ال Transistors التي بزوج

بزوج ✓

(47)

$$Z = 1/wC$$

* For Ranges of Frequencies where C_p has moderate Impedance value, C_s will have very small Impedance value, to the extent of considering it 0- Ω . In this case:

$$\tau_p = (R_p \parallel R_s) C_p$$

Known as the Short ckt time constant.

$$\text{So, } f_L = \frac{1}{2\pi \tau_s} \quad , \quad f_H = \frac{1}{2\pi \tau_p}$$




$$\text{Bandwidth} = f_H - f_L$$

↓
Range of Freq. with Gain of 47dB


* Time Response (p. 463 - P. 501) → غير مطلوب

* Frequency Response of BJT (p. 502).

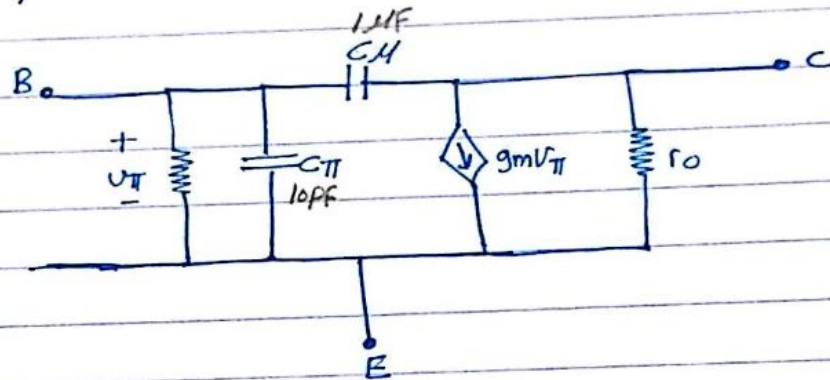⇒ It can be shown that the small signal high freq. model of npn BJT can be simplified as shown:



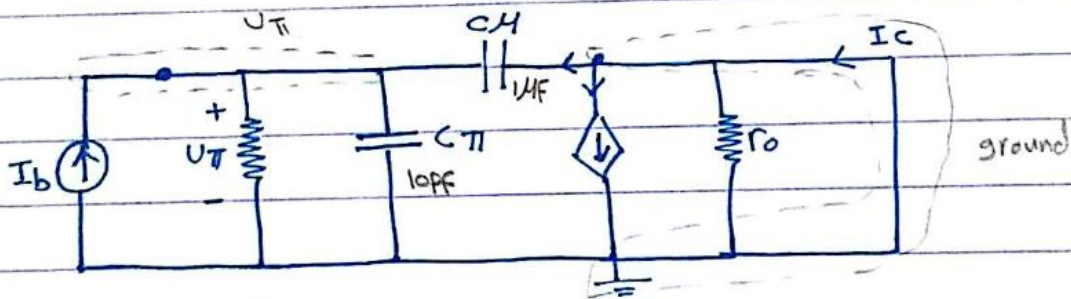* Short ckt current gain of a CE transistor Amplifier.



$$I_C = g_m V_{\pi} + j\omega (C_{\pi} - V_{\pi}) C_M = (g_m - j\omega C_M) V_{\pi}$$

$$I_b = \frac{V_{\pi}}{r_{\pi}} + j\omega C_{\pi} V_{\pi} + j\omega C_M V_{\pi}$$

$$= \left[\frac{1}{r_{\pi}} + j\omega (C_{\pi} + C_M) \right] V_{\pi} \quad (49)$$

$$A_i = \frac{I_C}{I_B} = h_{fe} = \frac{g_m - W_{CM}}{\frac{1}{r_{\pi}} + j\omega(C_{\pi} + C_M)}$$



$$\approx \frac{g_m}{\frac{1}{r_{\pi}} + j\omega(C_{\pi} + C_M)}$$

* usually $g_m \gg W_{CM}$
 50m A/V

$$2\pi \cdot 500 \times 10^6 \times 0.05 \times 10^{-12}$$

$$= \pi \times 5 \times 10^{-5}$$

$$\approx 15.7$$

$$\approx 0.157 \times 10^{-3}$$

$$\approx \frac{g_m r_{\pi}}{1 + j\omega(C_{\pi} + C_M)r_{\pi}}$$

$$1 + j\omega(C_{\pi} + C_M)r_{\pi}$$

$$\approx \frac{\beta_0}{1 + j\omega(C_{\pi} + C_M)r_{\pi}}$$

$$1 + j\omega(C_{\pi} + C_M)r_{\pi}$$

(50)