

# \* Field Effect transistor Amplifiers (FET-Amp.).

14-10-2018

\* advantage of Field Effect Transi. over BJT:-

- ① Small Size.
- ② High Input Impedance.
- ③ low power dissipation.

\* dis advantage


$$g_m \text{ (BJT)} \gg g_m \text{ (FET)} \Rightarrow A_v \text{ (BJT)} \gg A_v \text{ (FET)}$$

Types of field effect trans.

① MOS FET : Metal-oxide semiconductor FET.


↳ n-channel (NMOS FET) ↳ enhancement mode

↳ p-channel (PMOS FET) ↳ depletion mode

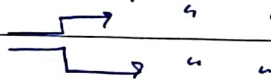


② JFET.

\* NMOSFET :

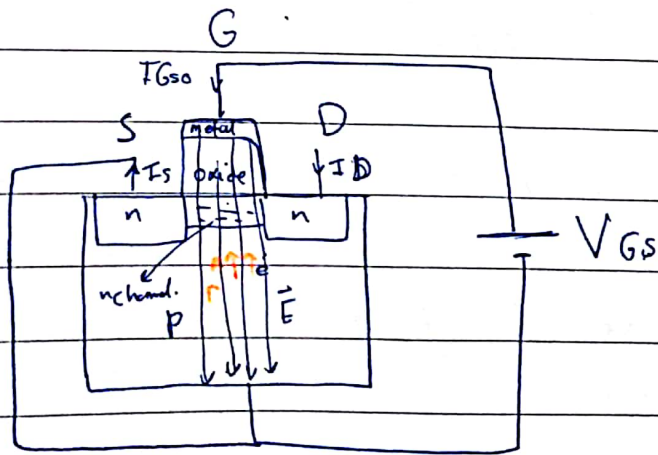


If  $V_{GS} > V_{TN} \Rightarrow n\text{-channel} \rightarrow I_D > 0.$


$I_G = 0, I_D = I_S.$

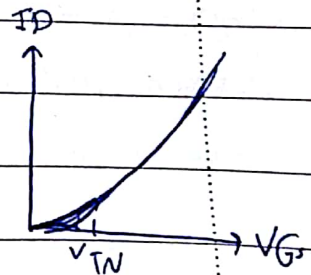

\* n-channel NMOSFET:-


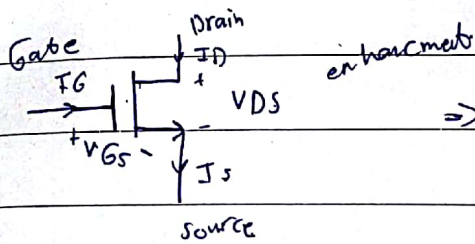


Depletion.

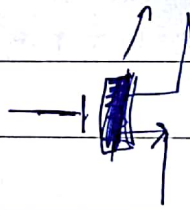

$V_{GS} \leftarrow I_B$

\* p-MosFet

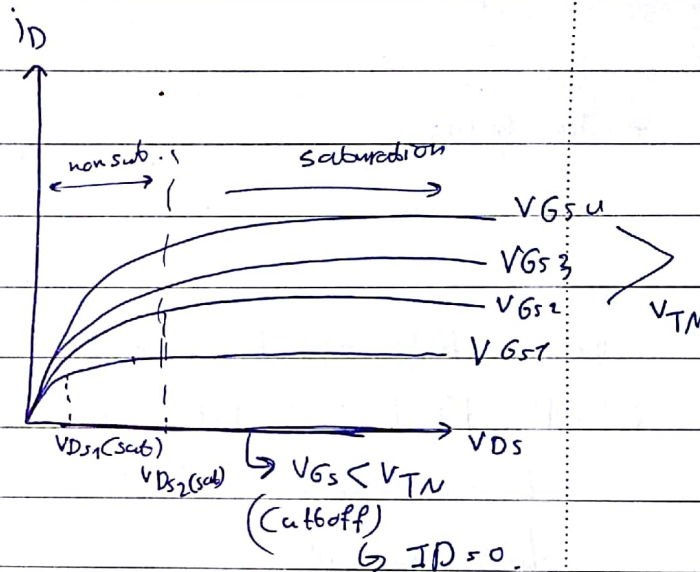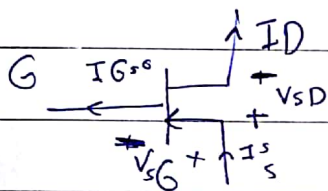

4 modes of operation.

( $V_{DS} > V_{DS(sat)}$ ).

① saturation mode  $\Rightarrow$  (Amp).

② non-saturation mode  $\Rightarrow$  (switches & logic gates).

③ cutoff.  $\Rightarrow$

\*  $V_{DS(sat)} = V_{GS} - V_{TN}$ .

\* Basic Configurations:- for (FET)

- ① Common Source. CS.
- ② common Drain CD.
- ③ common Gate CG.



\* Analysis of FET Amp.

(\*) Dc analysis  $\Rightarrow$  Q point points ( $I_{DQ}, V_{GSQ}, V_{DSQ}$ ), Dc load line ( $I_D \propto V_{DS}$ )

(\*) Ac analysis  $\Rightarrow A_v, A_i, R_i, R_o$ .

\* Dc analysis:-

\* capacitors open ckt.

\* AC sources  $\Rightarrow$  Kill all AC sources.

$\Rightarrow$  ~~N~~ NMOSFET

PMOSFET.

\* Saturation mode

\* Saturation mode.

\*  $V_{DS} > V_{DS(sat)}$

\*  $V_{SD} > V_{SD(sat)}$ .

\*  $I_D = K_n (V_{GSQ} - V_{TN})^2$

\*  $I_D = K_p (V_{SGQ} + V_{TP})^2$

\*  $V_{DS(sat)} = V_{GSQ} - V_{TN}$

$V_{SD(sat)} = V_{SGQ} + V_{TP}$ .

\* Non saturation

\* Non saturation.

$V_{DS} < V_{DS(sat)}$

$V_{SD} < V_{SD(sat)}$ .

$I_D = K_n (2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2)$

$I_D = K_p (2(V_{SG} + V_{TP})V_{SD} - V_{SD}^2)$

\*  $K_n$  or  $K_p \Rightarrow$  conduction parameter. ( $A/V^2$ ).

$V_{TN} > 0, V_{TP} < 0 \Rightarrow$  enhancement.

$V_{TP} > 0$   
 $V_{TN} < 0$  } depletion.

Finding mode of operation:-

① Assume saturation mode.

Input loop  $\Rightarrow$  find  $V_{GS} \Rightarrow$  If  $(V_{GS} < V_{TN})$  Then cutoff.

$\hookrightarrow I_D = k_n (V_{GS} - V_{TN})^2$

$\hookrightarrow$  output loop : find  $V_{DS}$ .

check If  $V_{DS} > V_{DS(sat)} \Rightarrow$  then saturation mode.

other wise:- non-saturation mode.

Input loop:-  $V_{GS}$


$I_D = k_n (2V_{GS} - V_{TN})V_{DS} - V_{DS}^2$  }  $I_D \neq V_{DS}$ .

output loop :  $I_D \propto V_{DS}$ .

21-10-2018.

NMOSFET.

Ex:-

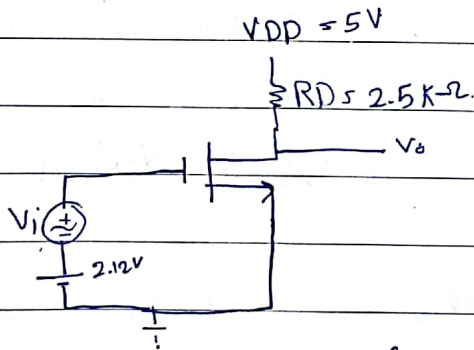


CS without  $R_s$ .

Given :  $V_{TN} = 1V$ ,  $k_n = 0.8mA/V^2$   
 $\lambda = 0.02V^{-1}$

find  $A_V = \frac{V_o}{V_i}$

\*DC analysis

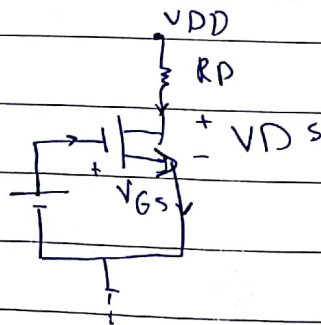

$I_D = I_S$ .



Input loop:  $\Rightarrow$

$$V_{GS} = 2.12 \text{ V} > \underline{V_{TN}} \quad \text{Not cutoff mode.}$$

$$I_{DQ} = \frac{K_n}{0.8} (V_{GS} - V_{TN})^2 = 1 \text{ mA.}$$


output loop:-

$$-V_{DD} + I_{DQ} R_D + V_{DS} = 0$$

$$V_{DS} = 2.5 \text{ V}$$

$$V_{DS} > \frac{V_{DS}(\text{sat})}{V_{GS} - V_{TN}} \quad \text{yes, saturation mode.}$$

AC analysis.

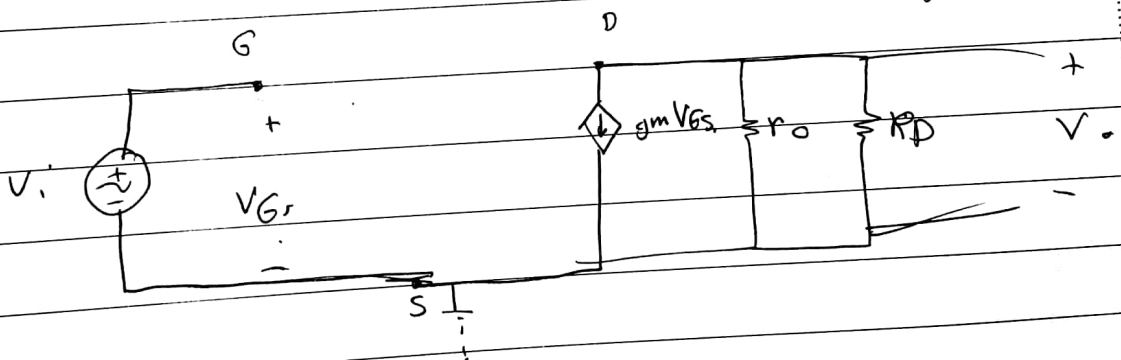


$$g_m = 2 K_n (V_{GS} - V_{TN}) = 2 \sqrt{K_n I_{DQ}} = 1.79 \text{ mA/V.}$$

$$r_o = \frac{1}{\lambda I_{DQ}} \approx 50 \text{ k}\Omega.$$


$$v_o = -g_m v_i (r_o \parallel R_D) = A_{vs} - g_m (r_o \parallel R_D) = \underline{\underline{-4.26}}$$

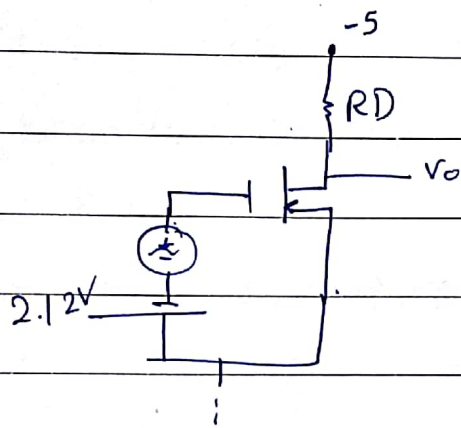Ex:- For the previous example use PMOSFET instead NMOSFET, then find  $A_v$ .




گین (gain) کا تعین

in Ac

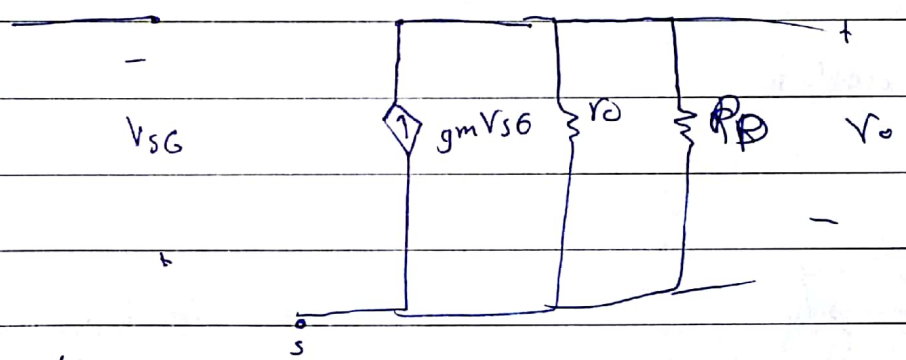

$A_{vs} = -4.26$

Ex:-

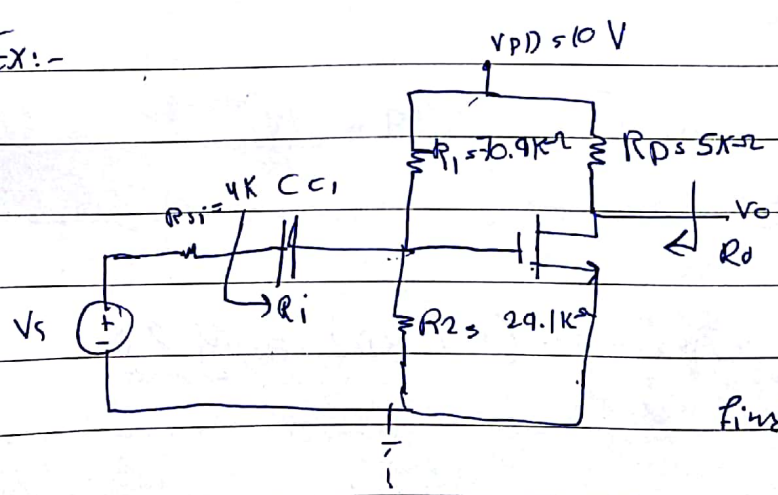


Given  $V_{TNS} = 1.5V$ ,  
 $k_n = 0.5mA/V^2$   
 $\lambda = 0.01V^{-1}$

- find @ Q-point values
- ② Dc load line.
  - ③  $A_v$
  - ④  $R_i$
  - ⑤  $R_o$



Dc analysis:-

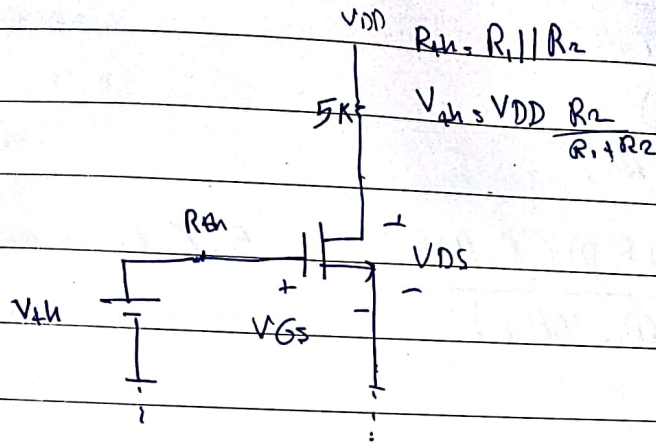

Input loop :  $V_{GS}$ .

$$V_{GS} > V_{TN} = 2.91 \text{ V}$$

outloop

$$I_{DS} K_n (V_{GS} - V_{TN})^2 = 1 \text{ mA}$$

$$V_{DS} \Rightarrow -V_{DD} + R_D I_D + V_{DS} = 0$$

$$V_{DS} = 5 \text{ V} > V_{GS} - V_{TN} \text{ yes (sat mode)}$$


① Qpoint Values

$$V_{GSQ} = 2.91, I_{DQ} = 1 \text{ mA}, V_{DSQ} = 5 \text{ V}$$

② DC load line.

$$I_{DS} = \frac{V_{DD} - V_{GS}}{R_D}$$

AC analysis:-

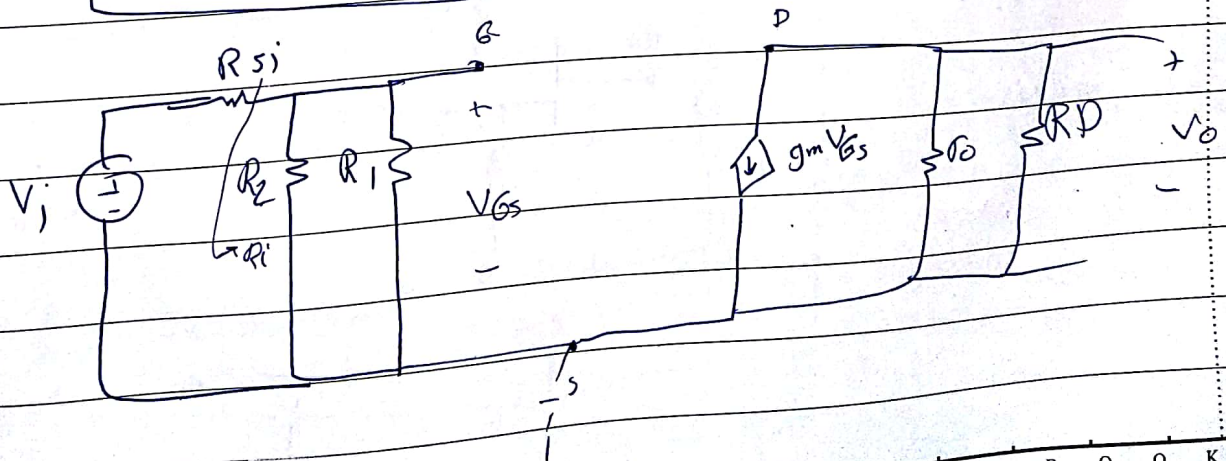

$$V_o = -g_m V_{GS} (r_o \parallel R_D)$$


$$V_{GS} = \frac{v_s (R_1 \parallel R_2)}{R_{Si} + (R_1 \parallel R_2)}$$

$$A_{vs} = \frac{-g_m (r_o \parallel R_D) (R_1 \parallel R_2)}{R_{Si} + (R_1 \parallel R_2)} = -5.62$$

④  $R_i = R_1 \parallel R_2 = 20.8 \text{ k}\Omega$

⑤  $R_o = R_D \parallel R_D = 4.76 \text{ k}\Omega$

example 1-

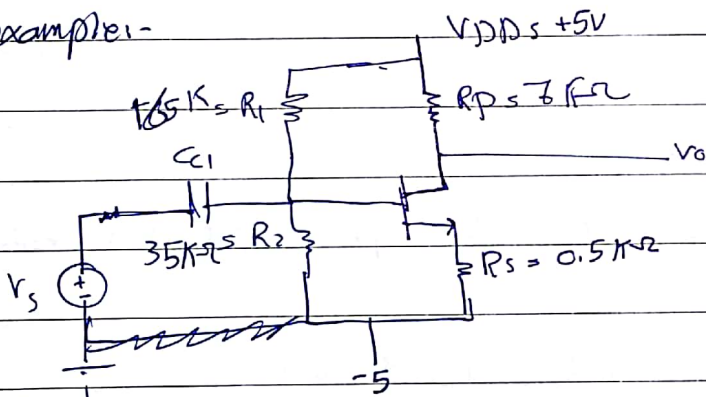


Given :-  $K_n = 1 \text{ mA/V}^2$

$\lambda = 0 \text{ V}^{-1}$


$V_{TN} = 0.8 \text{ V}$

find  $A_v = \frac{V_o}{v_s}$

DC analysis:-

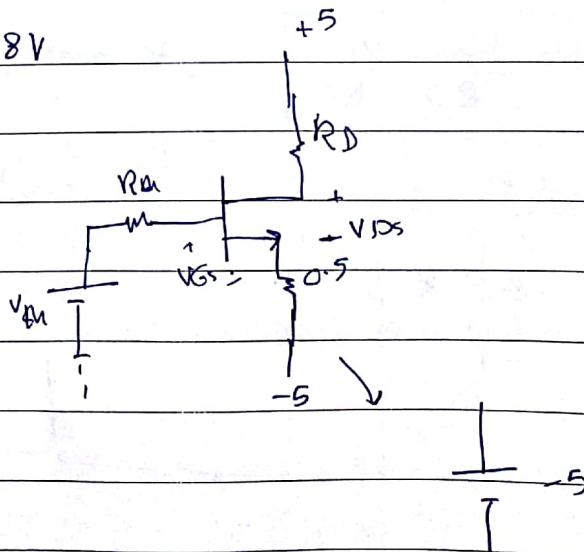



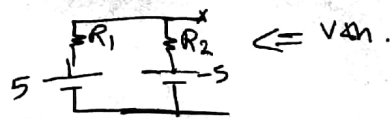

$R_{th} = R_1 // R_2 = 2.84k\Omega$

$V_{th} = \frac{V_{in} R_2}{R_1 + R_2} = \frac{5 \times 2.84}{2.84 + 5} = -3.25V$

$V_{GS} \Rightarrow$  Input loop

$-V_{th} + V_{GS} + I_{DQ} R_S - 5 = 0 \quad \text{--- (1)}$

$I_{DQ} = K_n (V_{GS} - V_{TN})^2 \quad \text{--- (2)}$

Sub (1) in (2)

$\hookrightarrow V_{GS}^2 + 0.4 V_{GS} - 2.86 = 0$

$V_{GS} = 1.5 \text{ or } -1.9V$


$V_{TN} = 0.5V$

$V_{GS} = 1.5V$

$I_{DQ} = 0.5mA$

output loop  $\Rightarrow V_{DSQ} = \square V$

Ac analysis

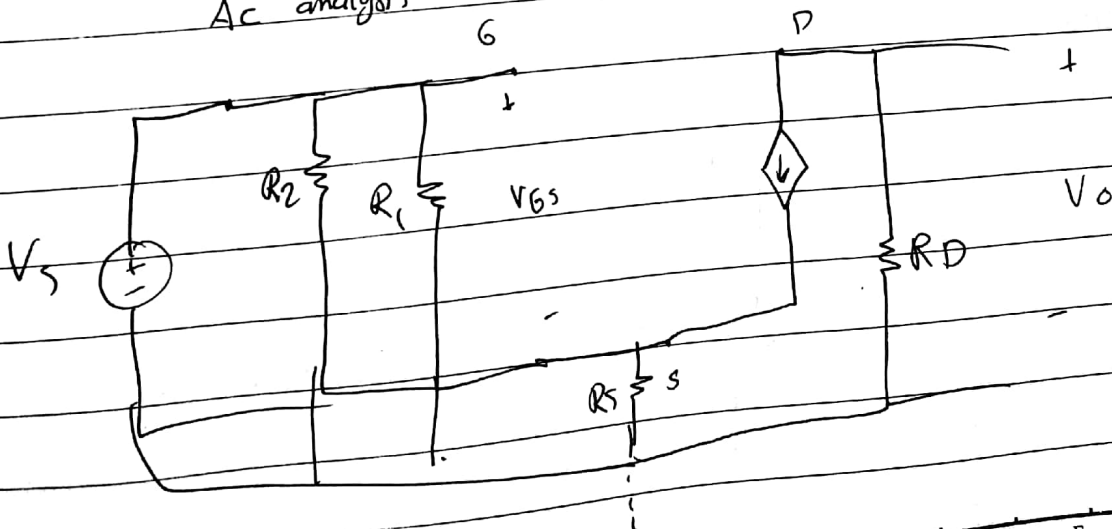

$$v_{os} = -g_m v_{GS} R_D \quad \text{--- (1)}$$

$$-v_s + v_{GS} + R_S g_m v_{GS} = 0$$

$$v_{GS} = \frac{v_s}{1 + g_m R_S}$$

~~$$\frac{v_{GS}}{v_s} = \frac{1}{1 + g_m R_S} \quad \text{--- (2)}$$~~


~~$$A_{v_s} = \frac{v_o}{v_s} = -g_m R_D$$~~

$$A_{v_s} = \frac{v_o}{v_s} = \frac{-g_m R_D}{1 + g_m R_S}$$

$$= -5.8$$

~~$g_m R_D$~~

Example:-

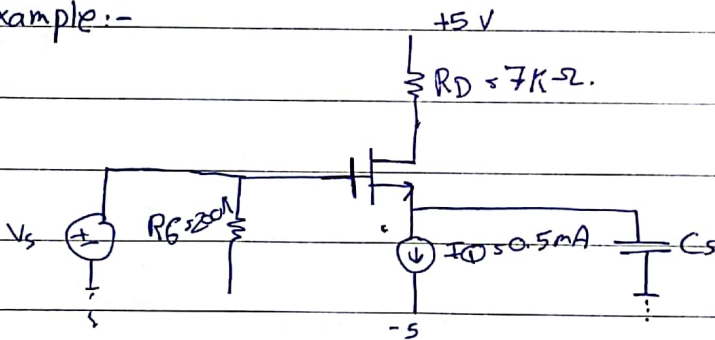

n-channel  
common source.


Given  $k_n = 1 \text{ mA/V}^2$

$V_{TN} = 0.8 \text{ V}$

$\lambda = 0$

find:  $A_{v_s} = \frac{v_o}{v_s}$

\* DC analysis:-

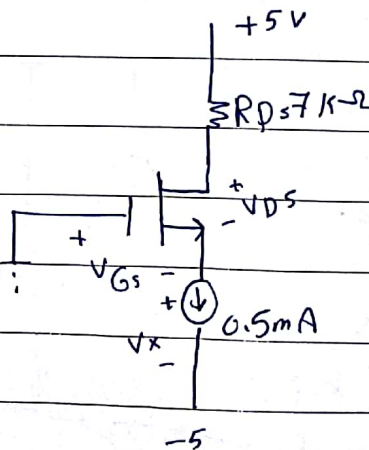

$$I_{DS} = k_n (v_{GS} - V_{TN})^2$$

$0.5 \text{ mA} = 1 \text{ mA/V}^2 (v_{GS} - 0.8)^2$

$v_{GSQ} = 1.51 \text{ V}$

$v_X$

$$\Rightarrow v_{GS} + v_X - 5 = 0$$

$$1.51 + v_X - 5 = 0$$

$$v_X = 3.49 \text{ V}$$




output loop

$$-5 + R_D I_D + V_{DS} + V_X - 5 = 0$$

$$V_{DS} = 3V$$

AC analysis:-

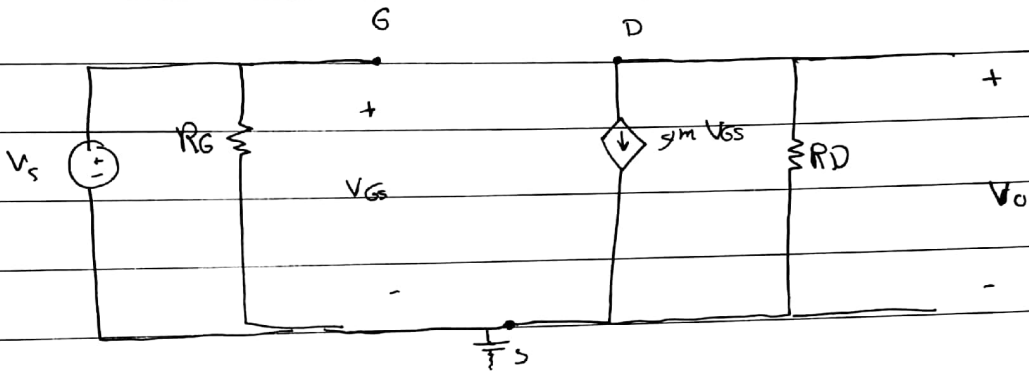

$$A_v = \frac{v_o}{v_s}$$


$$v_o = -g_m v_{GS} R_D \Rightarrow A_v = -g_m R_D = -10$$

$$v_{GS} = v_s$$

$$g_m = 2\sqrt{I_{DQ} k_n} = 1.414 \text{ mA/V}$$

$R_i = R_G$ ,  $R_o = R_D$

Example:

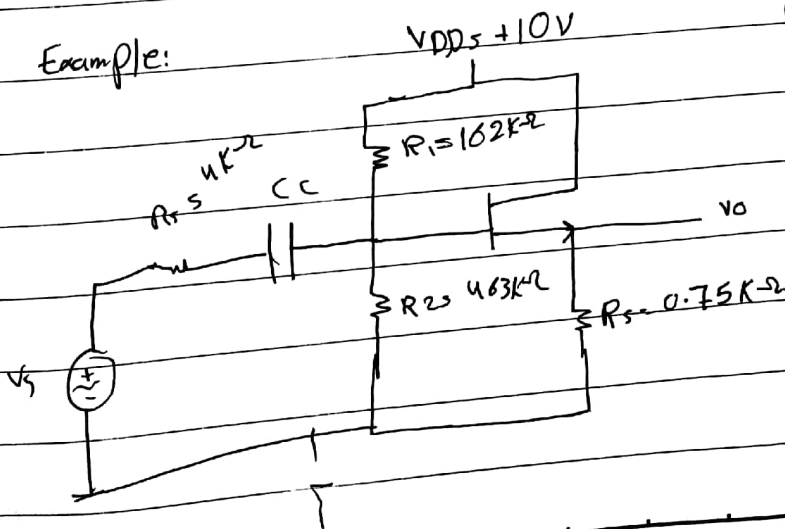

Given  $V_{TN} = 1.5V$

$$k_n = 5 \text{ mA/V}^2$$

$$\lambda = 0.01 \text{ V}^{-1}$$


find ①  $A_v$

②  $R_i$

③  $R_o$

DC

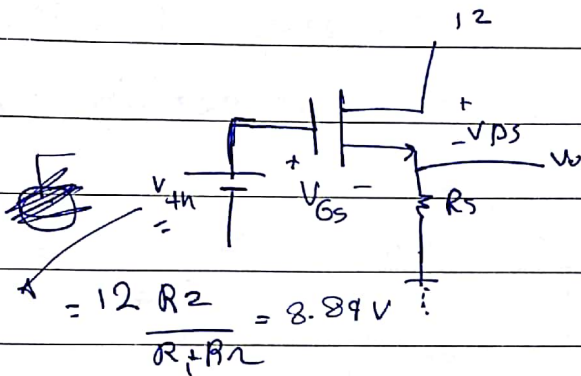$R_{th} = R_1 // R_2 = 120 \text{ k}\Omega$



Input loop  $\Rightarrow -8.89 + V_{GS} + R_S I_{D50} \dots \text{--- (1)}$

$I_{D50} = K_n (V_{GS} - V_{TN})^2 \dots \text{--- (2)}$


Solve (1) & (2)

$V_{GS}^2 - 2.67 V_{GS} - 0.713 = 0$

$V_{GS} = 2.91 \text{ V}$  OR  $-0.245 \text{ V}$

$I_{DQ} = 8 \text{ mA}$

AC analysis:-

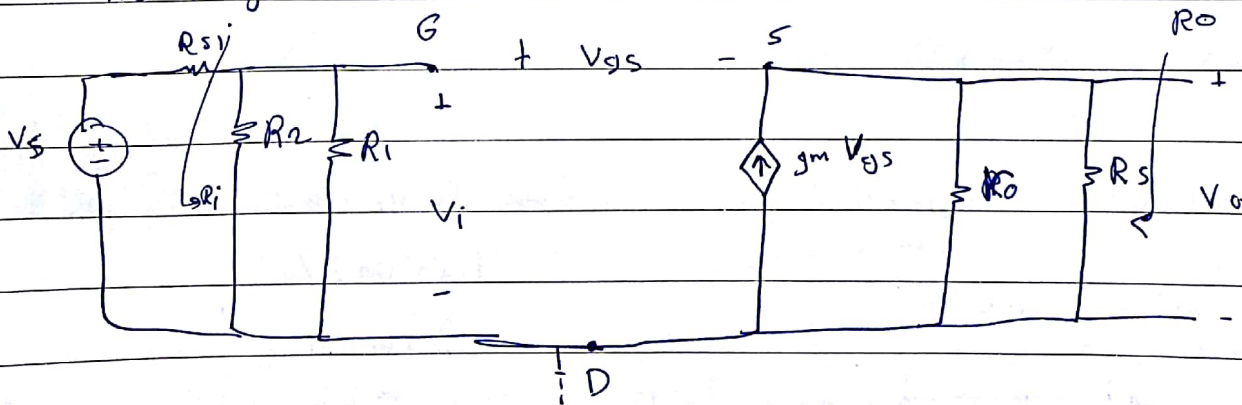

$g_m = 2\sqrt{K_n I_{DQ}} = 11.28 \text{ mA/V}$

$r_o = \frac{1}{I_{DQ}} = 12.5 \text{ k}\Omega$

$$A_{vs} \frac{V_o}{V_s} = \frac{V_o}{V_s} = g_m V_{gs} (R_o \parallel R_s)$$

$$V_{gs} = V_i - V_o$$

$$V_{gs} = V_s \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_s} \quad - V_o = ?$$

Solve ① & ②

$$A_{vs} \frac{g_m (R_o \parallel R_s) (R_1 \parallel R_2)}{[(R_1 \parallel R_2) + R_s] [1 + g_m (R_o \parallel R_s)]} = 0.86$$

$$* R_i = R_1 \parallel R_2 = 120 \text{ k}\Omega$$

$$R_o = \frac{V_x}{I_x}$$


$$\hookrightarrow \text{KCL at } S \Rightarrow I_x + g_m V_{gs} = \frac{V_x}{R_o \parallel R_s}$$

$$V_{gs} = -V_x$$

$$I_x = V_x \left[ g_m + \frac{1}{R_o \parallel R_s} \right]$$

$$R_o = \frac{V_x}{I_x} = \frac{1}{g_m + \frac{1}{R_o \parallel R_s}} = 78.8 \Omega$$

H.W  
Example: Common Gate.

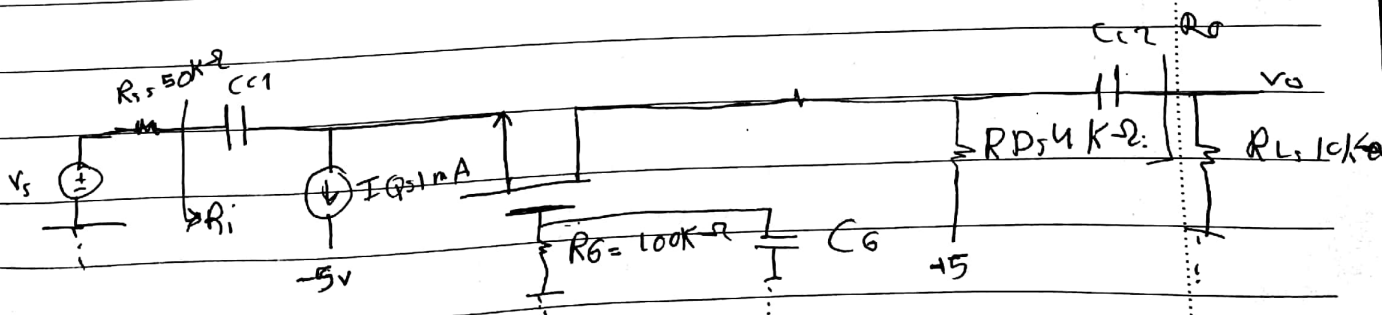



Given  $V_{TN} = 1V$

$K_n = 1mA/V^2$

$\lambda = 0$

Find ①  $A_v =$

②  $R_i =$

③  $R_o =$

DC analysis:-

$I_{DQ} = 1mA$

$V_{GSQ} = 2V$

AC analysis:-

$g_m = 2m/V$

$r_o = \infty$

$A_v = 0.06$

$R_i = 500\Omega$


$R_o = 2.96 K\Omega$

\* Frequency Response:- (Transfer function).  $T(s) = \frac{S_o(s)}{S_i(s)}$


⇒ Frequency Response for Amp. CKT:-  $A_v(f) = \frac{V_o(f)}{V_i(f)}$

In General

$|A_v(f)|_{dB} = 20 \log_{10} |A(f)|$

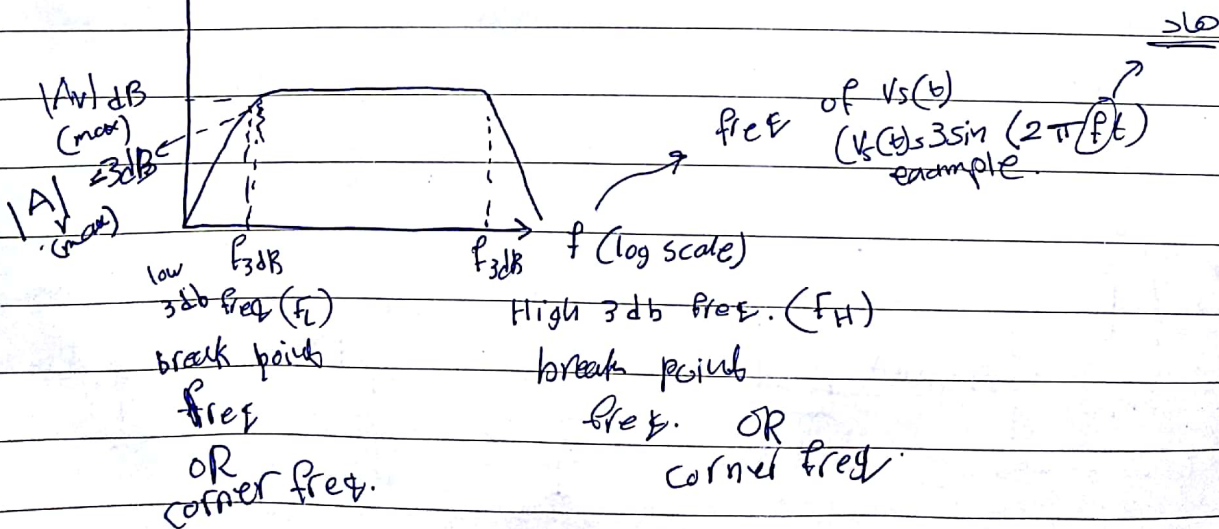

\* Voice signal power

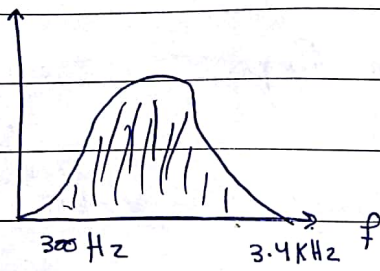

\* Band width of Amp. =  $f_H - f_L$

• implies BW of

\*  $f_L = \frac{1}{2\pi\tau_L}$  ,  $f_H = \frac{1}{2\pi\tau_H}$

↓  
Time constant

\*  $\tau_L$  low &  $\tau_C$  for low freq. Range.


&  $\tau_H$  high " " " High " "

$f_L$  &  $f_H$  are due to the capacitors in the Amp. CKT. ( $Z_s = \frac{1}{j2\pi C}$ )

\* Types of capacitor in Amp. CKT:

① Group 1, coupling capacitor & Bypass Capacitors.

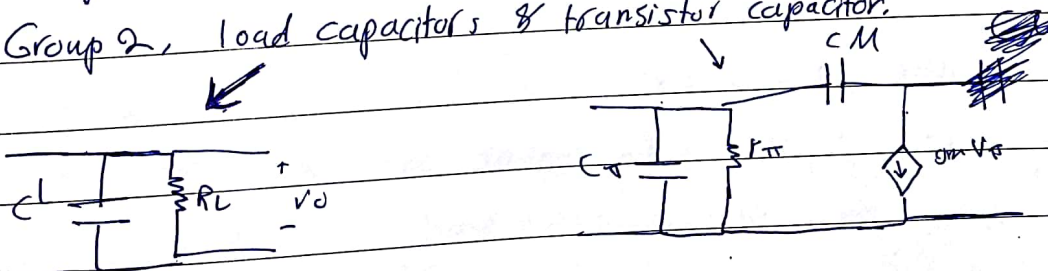② Group 2, load capacitors & transistor capacitor.



\* Values of Group 1 > values of Group 2.



\* any capacitor could be represented as open CKT, short CKT OR Impedance.

$$Z_c = \frac{1}{j2\pi f_c} \quad \text{based on freq.}$$

\* For DC ( $f=0$ ): Group 1 = open CKT, Group 2 = ~~short~~ <sup>open</sup> CKT.

\* For low freq. Rang ( $0 < f < f_L$ ):-

Group 1: Impedance. =  $\frac{1}{j2\pi f_c}$  }  $T_{\text{Low}} \approx R_{eq} \text{ Cap.}$   
 Group 2: open CKT. }  $f_L = \frac{1}{2\pi T_L}$

$$Z_c = \frac{1}{j2\pi f_c} = \frac{1}{0} = \infty$$

\* For midband freq Range ( $f_L < f < f_H$ ):-

Group 1: short CKT

Group 2: ~~short~~ open CKT.

}  $|A_v(\text{max})|$

\* For High freq Range ( $f > f_H$ ):-

Group 1: short CKT


Group 2:  $Z = \frac{1}{j2\pi f_c}$

}  $T_H$   
 $f_H = \frac{1}{2\pi T_H}$

\*  $f_L$  is due to Group 1.

\*  $f_H$  is due to Group 2.




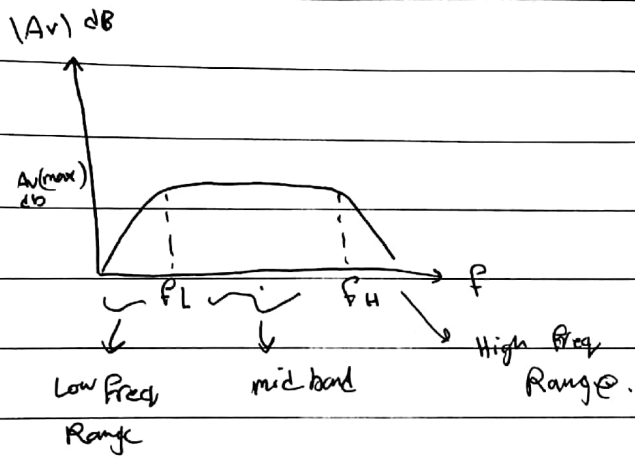

$$f_{low} = \frac{1}{2\pi C_L} \quad \text{---} \quad \text{---} \quad \text{---}$$

$$f_H = \frac{1}{2\pi C_H} \quad \text{---} \quad \text{---} \quad \text{---}$$

Ex:-

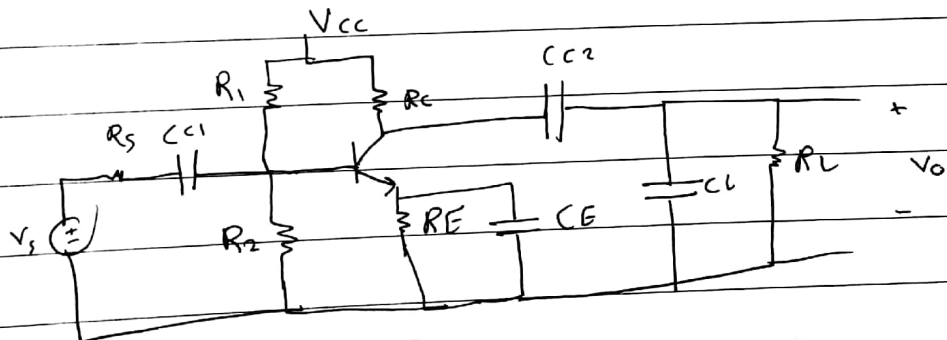


$$C_{\pi} = 5 \text{ nF}, \quad C_{\mu} = 2 \text{ pF}$$


Draw the eqn ckt :-

- ① do DC  $\rightarrow$  To find  $I_{CQ} \rightarrow r_{\pi}, g_m$
- ② in the low freq range  $\rightarrow f_L = \frac{1}{2\pi C_L} \rightarrow R_{eq} * C_{eq}$
- ③ in the mid band range  $\rightarrow |A_{v(max)}|$
- ④ in High freq. range  $\rightarrow f_H = \frac{1}{2\pi C_H} \rightarrow R_{eq} * C_{eq}$

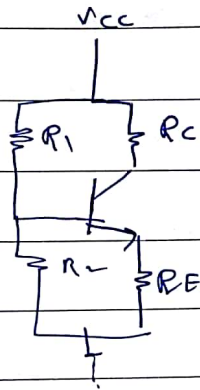
① DC ( $f = 0$  Hz)  $G_1, G_2 \Rightarrow$  open CKT.




② low freq range.

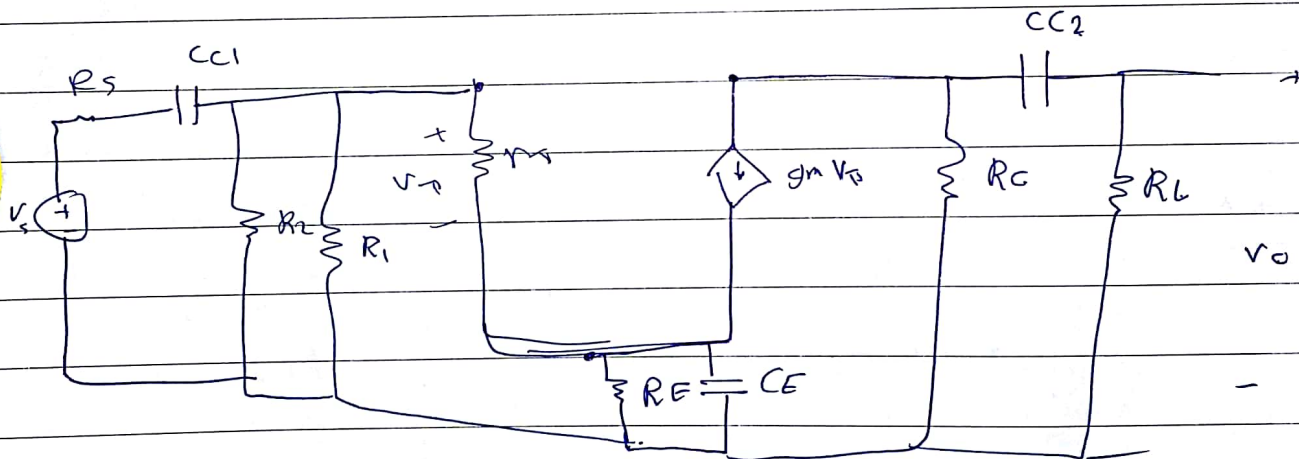

③ Mid band Freq Range.

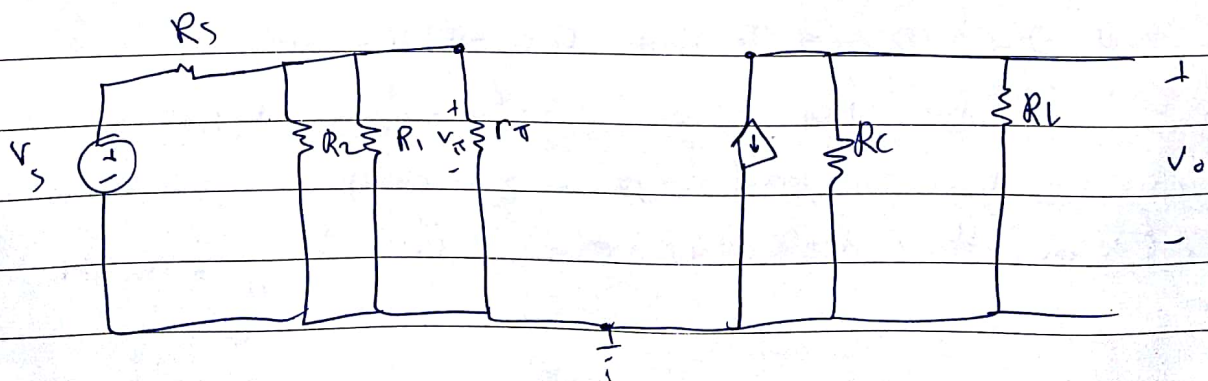


(u) High freq Range.

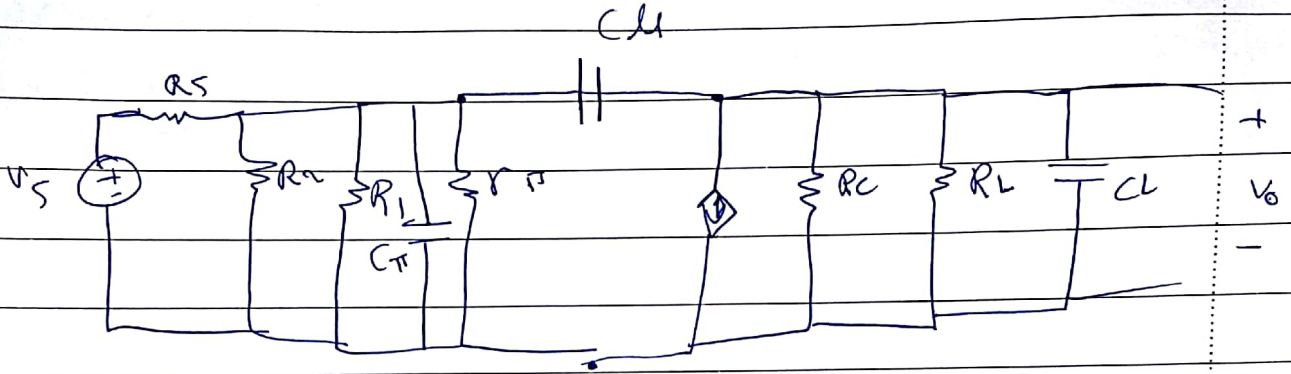

\*  $f_L = \frac{1}{2\pi T_L}$ ,  $f_H = \frac{1}{2\pi T_H}$  why? ?

Answer: Consider two special circuits :-

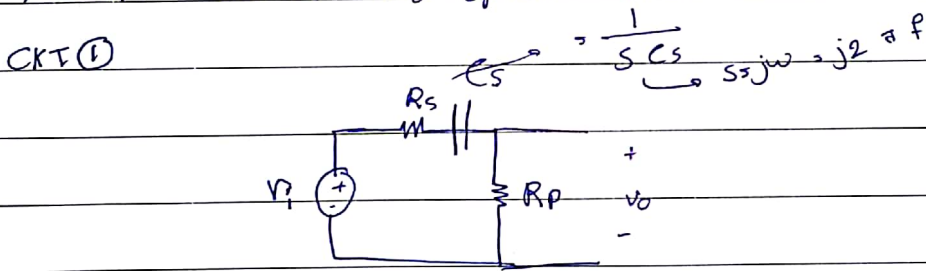

find transfer function of this circuit:-  $T_1(s) = \frac{V_o(s)}{V_i(s)}$


$$V_o(s) = V_i(s) \cdot \frac{R_p}{R_p + R_s + \frac{1}{sC_s}}$$

$$T = (R_p + R_s)C_s$$

time constant.

$$T_1(s) = \frac{R_p}{R_p + R_s} \cdot \frac{s(R_p + R_s)C_s}{1 + s(R_p + R_s)C_s} = \frac{R_p}{R_p + R_s} \cdot \frac{sT}{1 + sT}$$

circuit (2)

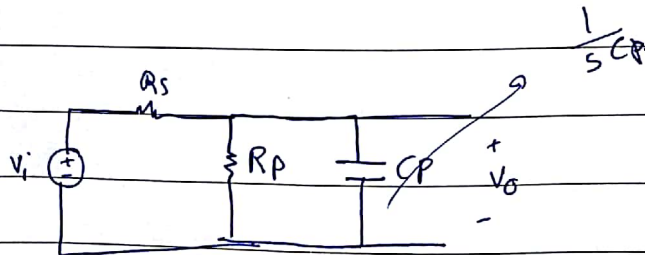



$$T_2(s) = \frac{V_o(s)}{V_i(s)}$$


$$V_o(s) = V_i(s) \frac{R_p \parallel \frac{1}{sC_p}}{R_s + R_p \parallel \frac{1}{sC_p}}$$

$$T(s) = \frac{R_p}{R_p + R_s} \cdot \frac{1}{1 + s(R_p \parallel R_s)C_p} = \frac{R_p}{R_p + R_s} \cdot \frac{1}{1 + s\tau}$$

$\tau = (R_p \parallel R_s) C_p$  time constant.


Draw  $T_1(s)$  &  $T_2(s)$

⇒ Roughly:

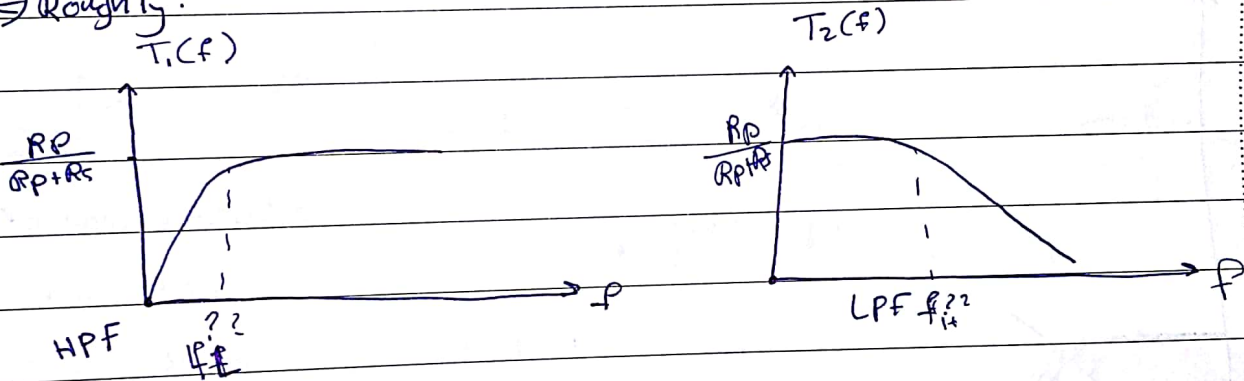

→ Use the Bode plots:-

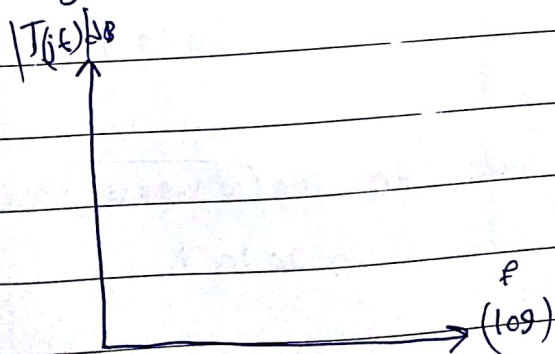Bode plots: it is a simplify Tech. used to Approximily draw the magnitude & the phase of a transfer function.




draw  $T_1(s)$  Using Bode plots.

$$T_1(s) = \frac{R_p}{R_p + R_s} \cdot \frac{s\tau}{1 + s\tau}$$


$$T_1(jf) = \frac{R_p}{R_p + R_s} \cdot \frac{j2\pi f\tau}{1 + j2\pi f\tau} \quad \begin{matrix} X = a + jb \\ |X| = \sqrt{a^2 + b^2} \end{matrix}$$

$$|T_1(jf)| = \frac{R_p}{R_p + R_s} \frac{2\pi f\tau}{\sqrt{1 + (2\pi f\tau)^2}}$$

$$20 \log |T_1(jf)| = 20 \log \left( \frac{R_p}{R_p + R_s} \right) + 20 \log (2\pi f\tau) - 20 \log (\sqrt{1 + (2\pi f\tau)^2})$$

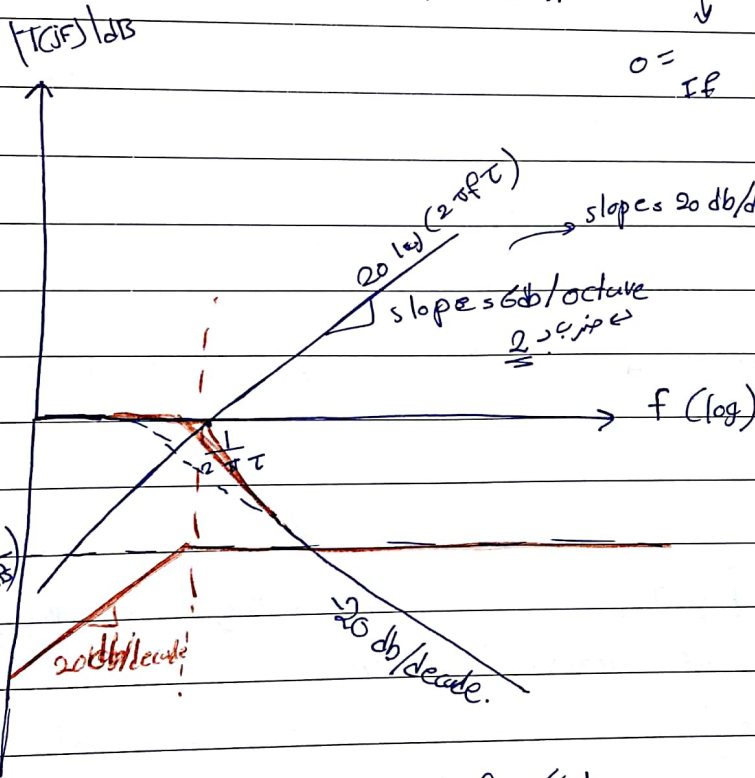

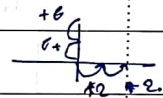0 = IF  $2\pi f\tau = 1$   
 $f = \frac{1}{2\pi\tau}$



octave =  $20 \log 2 = 6 \text{ dB}$   
 $= 20 \log 4 = 12 \text{ dB}$   
 $20 \log 8 = 18 \text{ dB}$

decade

$20 \log 10 = 20$   
 $20 \log 100 = 40$   
 $20 \log 1000 = 60$

IF  $2\pi f\tau \ll 1$

$f \ll \frac{1}{2\pi\tau}$  then  $20 \log (\sqrt{1 + (2\pi f\tau)^2}) \approx 0$   
 $\approx 20 \log 1 = 0$


IF  $2\pi f\tau \gg 1$

$f \gg \frac{1}{2\pi\tau}$  then  $20 \log \sqrt{1 + (2\pi f\tau)^2}$   
 $= 20 \log 2\pi f\tau$




$$|G(j\omega)| \approx \frac{1}{2\pi\tau_L}$$

H.W  $\Rightarrow$  USE Bode plot to Draw  $|T_2(jf)|_{dB}$

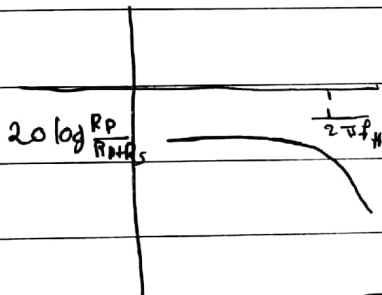


short method for Bode plot:-



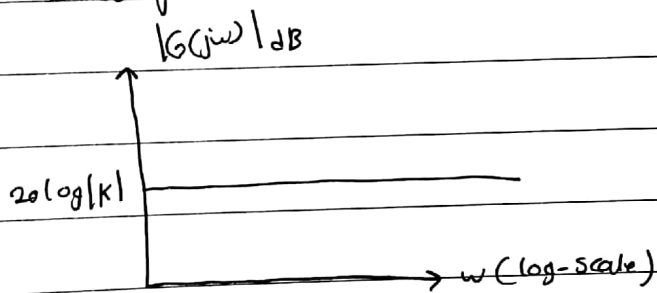
\*  $G(j\omega) \approx K \Rightarrow$   
 $\downarrow$   
 constant



\*  $G(j\omega) = j\omega$

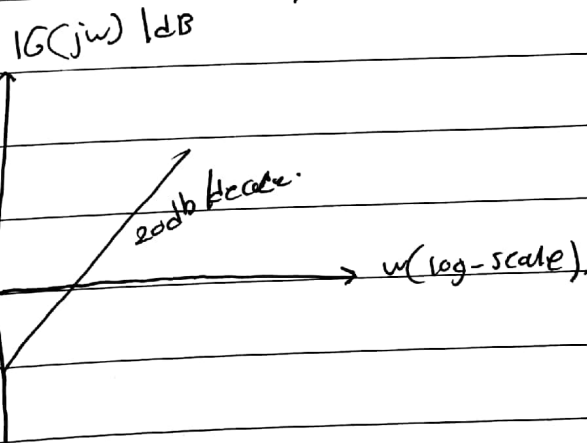




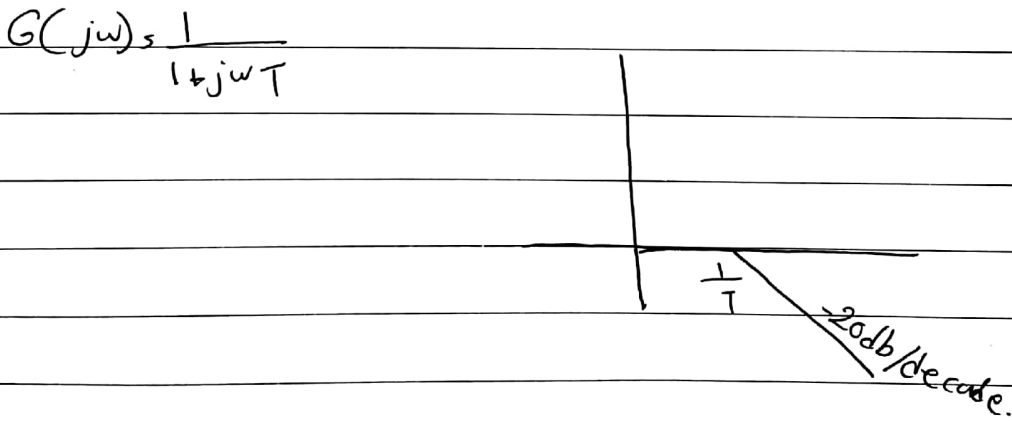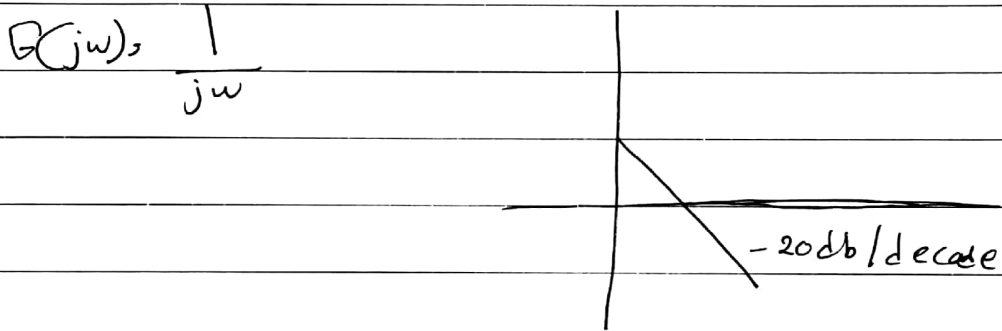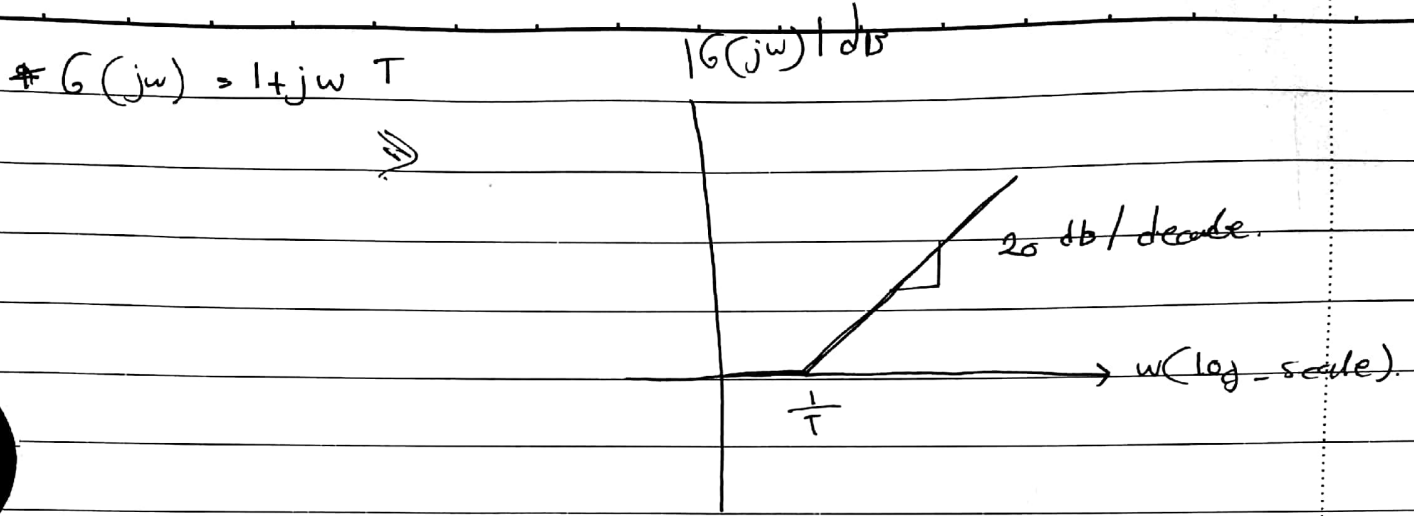


Ex:  $G(s) = \frac{100(s+2)}{s(s+40)}$  Plot  $|G(j\omega)|_{dB}$ .
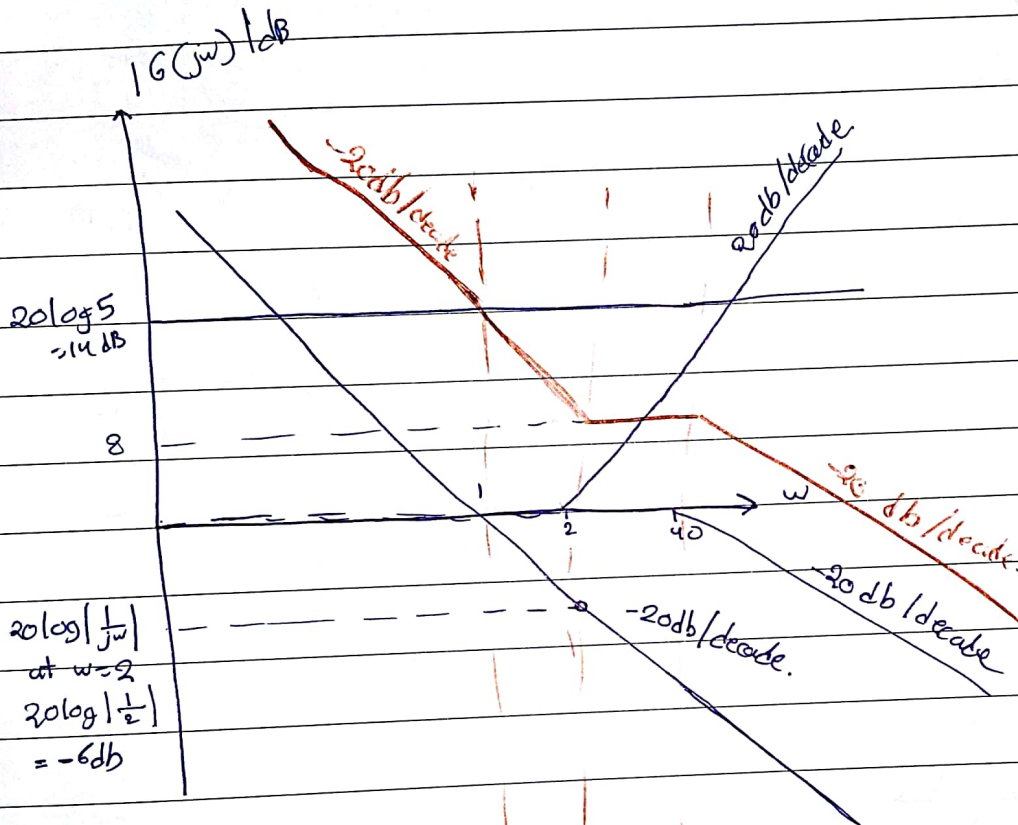
$$G(s) = \frac{100(j\omega+2)}{j\omega(j\omega+40)} = 100 \times 2 \left(\frac{1+j\omega}{2}\right) = 5 \times \left(\frac{1}{j\omega}\right) \times \left(\frac{1+j\omega}{2}\right) \times \frac{1}{\frac{1+j\omega}{40}}$$






Ex (H.W)  $\Rightarrow G(s) = \frac{1}{s^4} = \frac{1}{(j\omega)^4} = 20 \times 4 \log \left| \frac{1}{j\omega} \right| = \frac{1}{j\omega} \cdot \frac{1}{j\omega} \cdot \frac{1}{j\omega} \cdot \frac{1}{j\omega}$

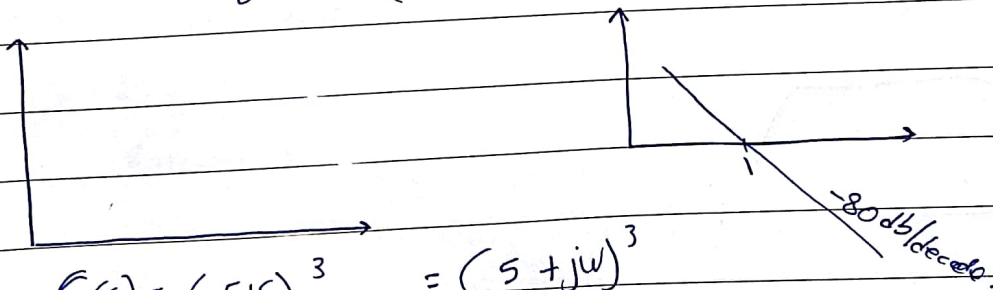

Ex:  $G(s) = (5+s)^3 = (5+j\omega)^3$   
 $= (5+j\omega)(5+j\omega)(5+j\omega)$   
 $= 5 \left(\frac{1+j\omega}{5}\right) 5 \left(\frac{1+j\omega}{5}\right) 5 \left(\frac{1+j\omega}{5}\right) = 125 \left(\frac{1+j\omega}{5}\right) \left(\frac{1+j\omega}{5}\right) \left(\frac{1+j\omega}{5}\right)$

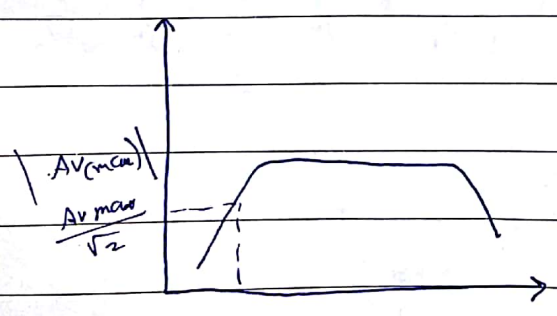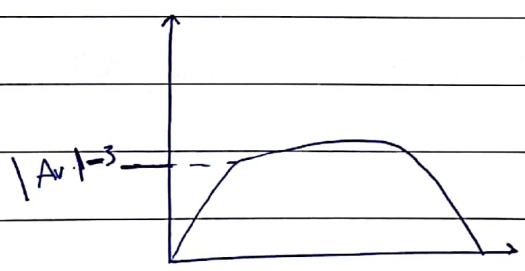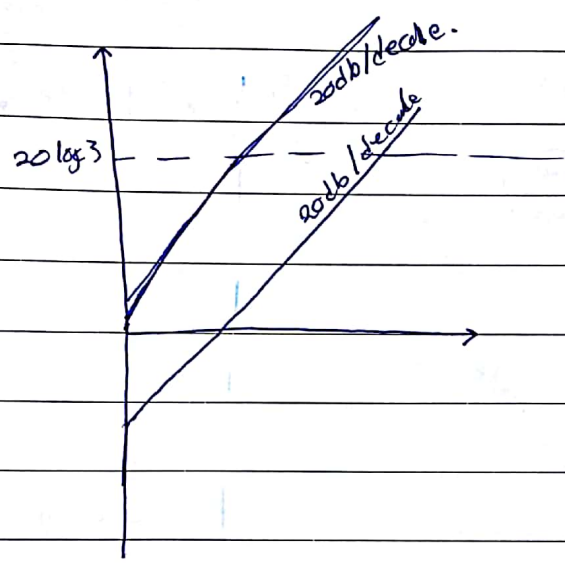
Ex:  $G(s) = -3s \Rightarrow -3(j\omega) = -3 \angle j\omega$





How to find  $T$

① from a plot.

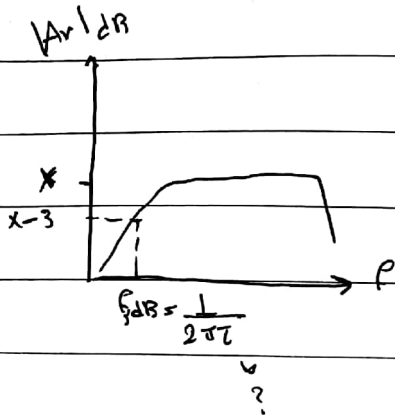

$$\text{dB } \omega; 1$$

$$\frac{x}{\sqrt{2}}$$

② from a function.

→ Simplify the function to  $T_1(s)$  or  $T_2(s)$

$$T_1(s) = K \frac{sT}{1+sT}$$

$$T_2(s) = K \frac{1}{1+sT}$$

example:-  $T(s) = \frac{5s}{3+4s}$

Find  $T = ?$

$$= \frac{5 \cdot \frac{3}{4} s}{3 (1 + \frac{4}{3} s)}$$

③ from a CKT:-

$$\Rightarrow \frac{5}{4} \frac{\frac{4}{3} s}{1 + \frac{4}{3} s}$$

Case 1:-


If there is one capacitor.

$$T = \frac{4}{3} \text{ sec.}$$

$$T = R_{eq} C_{eq}$$

↓  
R<sub>eq</sub> seen by C

\* example:


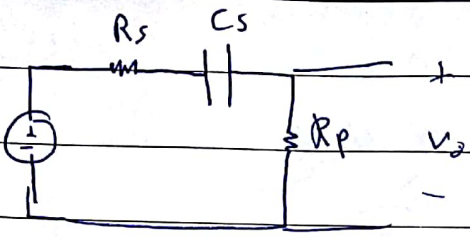


Find  $T_c$  and draw the freq. response  $|A_v|$

$$T_s \text{ Req } C_s$$

$$= (R_s + R_p) C_s$$


Zero case?  
 $\infty, \bar{i}$

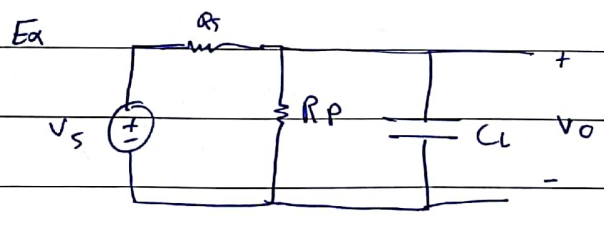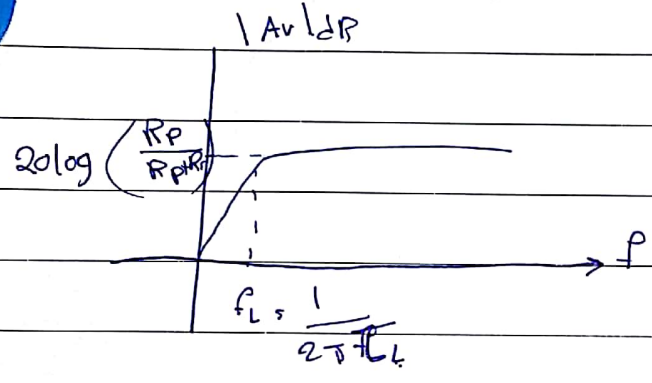


Find  $T_c$

$$T_s \text{ Req } C_L$$


$$= (R_s // R_p) C_L$$

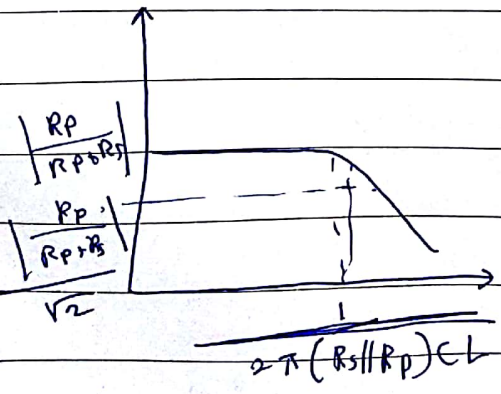

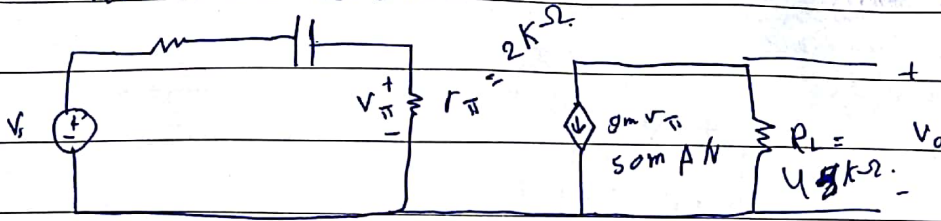example:  $R_s = 1k\Omega$   $C_c = 1\mu F$



Draw the  $|A_v(f)|_{dB}$

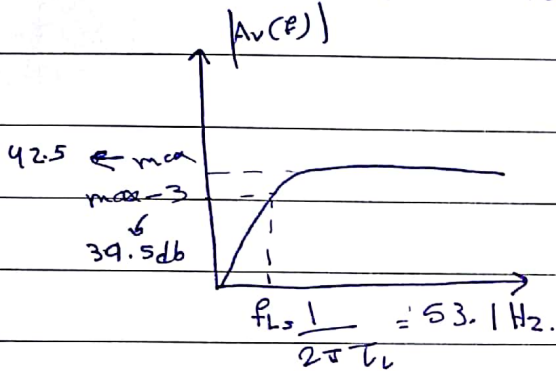

$$A_v = \frac{-g_m R_L r_\pi}{r_\pi + R_s} = -133$$

$$T_c = R_{eq} C_c$$


$$= (R_s + r_\pi) C_c$$

$$= 3k\Omega + 1\mu = 3\mu \text{ sec.}$$


$$|A_v|_{dB} = 20 \log 133$$

$$= 42.5 \text{ dB}$$

Ex: ~~2~~

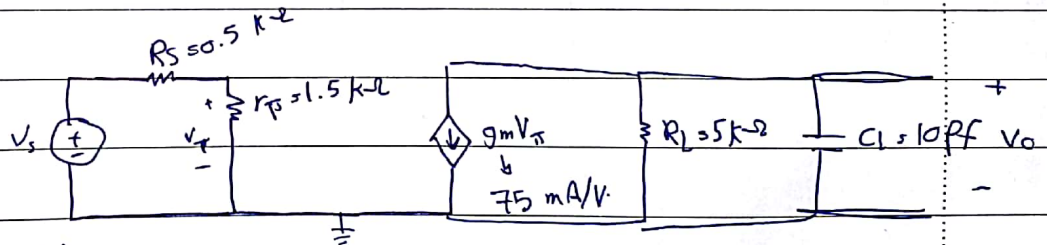

Draw  $|A_v(f)|_{dB}$

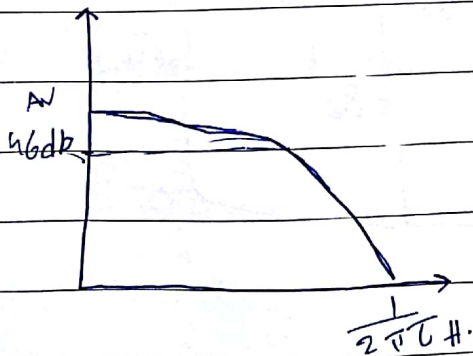

$$A_v = \frac{-g_m R_L r_\pi}{r_\pi + R_s} = -281$$

$$|A_v|_{dB} = 20 \log 281 = 49 \text{ dB}$$


~~Ex: 3~~

$$T_{H} = R_{eq} C_L = R_L C_L = 50 \text{ nsec.}$$





$f_H = 3.18 \text{ MHz}$


example:

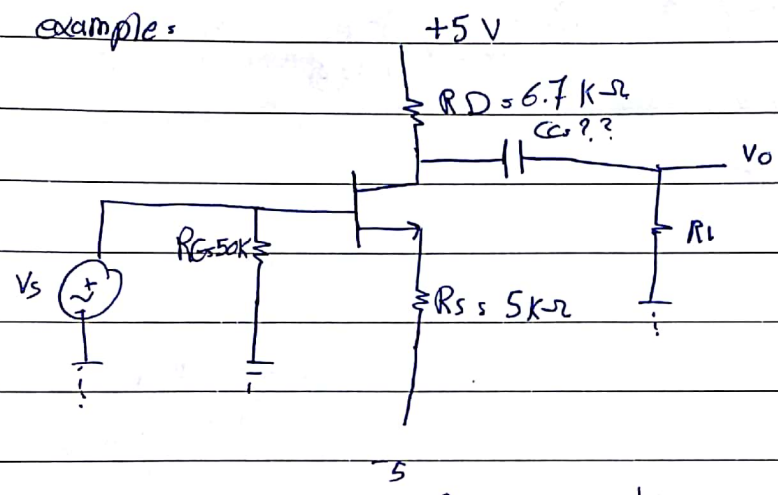

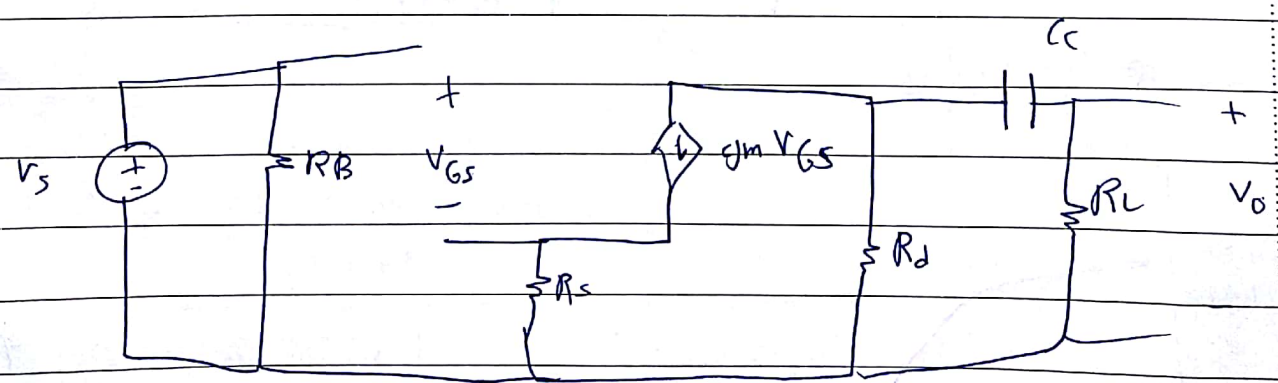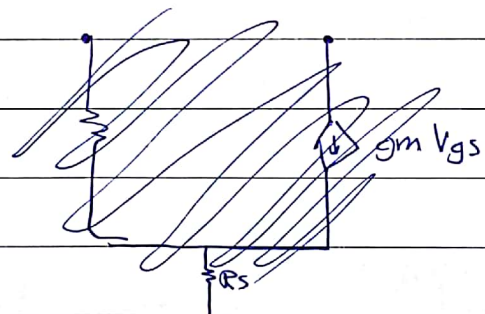find  $C_C$  such  $f_{3\text{dB}} = 20 \text{ kHz}$ .


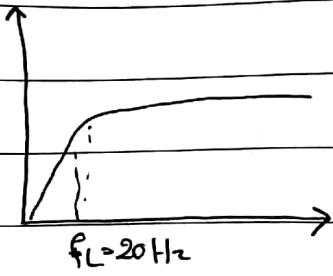
$$kcl: -g_m V_{gs} + \frac{V_{gs}}{R_s} \Rightarrow V_{gs} \left( g_m + \frac{1}{R_s} \right) \cdot \frac{296}{\dots}$$




$$20 \text{ Hz} \approx \frac{1}{2\pi \tau} \Rightarrow \tau \approx 7.96 \text{ m sec} \Rightarrow R_{eq} C_c$$

$$R_{eq} = (R_D + R_L) \parallel C_c$$

$$= 16.7 \text{ K} \parallel C_c$$

$$C_c = 0.477 \text{ } \mu\text{F}$$

short CKT.

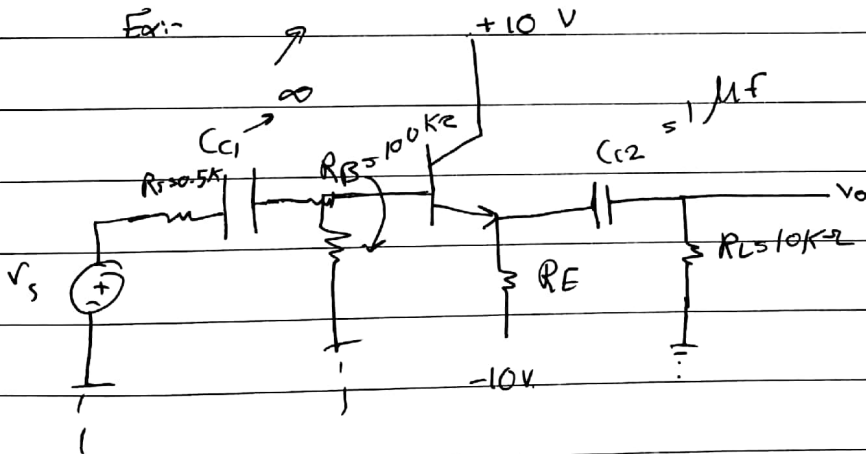


find  $f_{3dB}$ .

Answer:  $\Rightarrow 15.4 \text{ Hz}$ .

Case 2: more than one capacitor we use open CKT-short CKT time constants. (later).

↓  
If there are

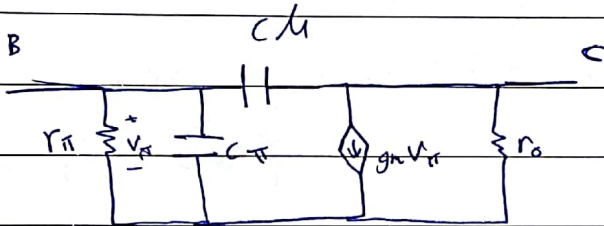\* Transistor capacitors (for bipolar junction capacitor)



\*  $C_{\pi}$  &  $C_{\mu}$  are Transistor capacitors.

\* The effect of these capacitors ~~appeared~~ can be found at High frequency.

\*  $C_{\mu} \ll C_{\pi}$ , but we cannot ignore the effect of  $C_{\mu}$  due to Miller effect.



\* The effect of  $C_{\pi}$  &  $C_{\mu}$  on short CKT current Gain.

\* Transistor is a current Amplifier because  $I_C = \beta I_B$   
 $I_O \quad I_i$

$\beta$  is called short-circuit current gain.


$$A_{is} = \frac{I_C}{I_B} = \beta$$

in DC & low & mid band frequency.

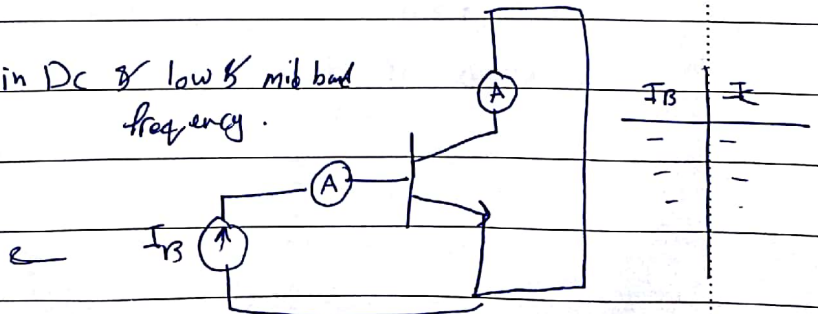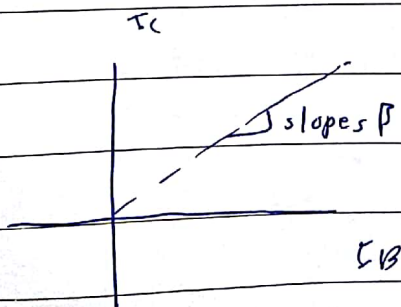



In High Frequency-

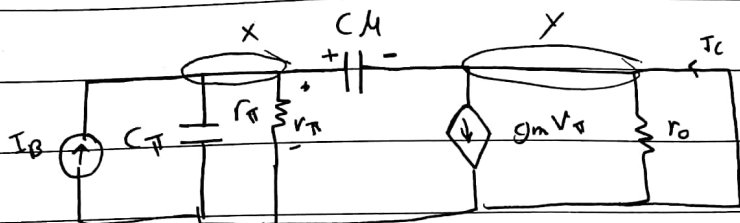

$$\text{find } A_i = \frac{i_c}{i_b}$$

Kcl at x:

$$i_b = \frac{V_\pi}{r_\pi} + \frac{V_\pi}{\frac{1}{j\omega C_\pi}} + \frac{V_\pi}{\frac{1}{j\omega C_M}} \quad \dots \text{--- (1)}$$

$$i_b = V_\pi \left[ \frac{1}{r_\pi} + j\omega(C_\pi + C_M) \right] \quad \dots \text{--- (1)}$$

Kcl at y:

$$g_m V_\pi = i_c + \frac{V_\pi}{\frac{1}{j\omega C_M}}$$

$$i_c = V_\pi (g_m - j\omega C_M) \quad \dots \text{--- (2)}$$

$$A_i = \frac{i_c}{i_b} = \frac{g_m - j\omega C_M}{\left[ \frac{1}{r_\pi} + j\omega(C_\pi + C_M) \right]}$$



Typically,  $C_M = 0.2 \text{ pF}$ ,  $g_m = 50 \text{ mA/V}$ ,  $f_{max} = 100 \text{ MHz}$

$$\omega C_M \ll g_m, \text{ so } A_i \approx \frac{i_c}{i_b} \approx \frac{\beta}{1 + j\omega r_\pi (C_\pi + C_M)}$$

$$\downarrow$$

$$f_{50\%} = \frac{1}{1.57 r_\pi (C_\pi + C_M)}$$

$|A_i|$

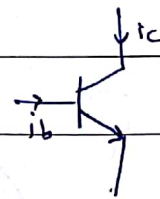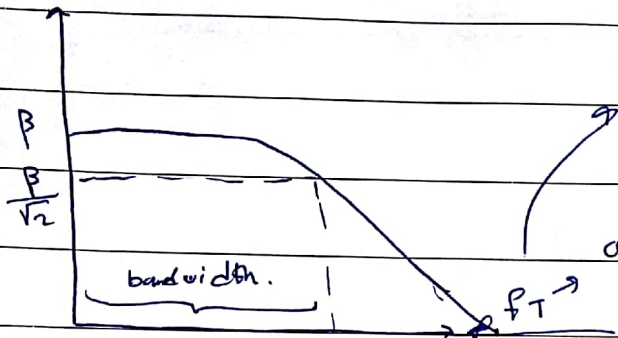

Unity gain bandwidth.  
( $I_C = I_B$ )

$f_{\beta} = \frac{1}{2\pi(r_{\pi}(C_{\pi} + C_{\mu}))}$

$f_{\beta}$  ←  
Cutoff frequency  
OR bandwidth of the transistor.

Unity gain bw ( $f_T$ ) :-

$|A_i(f_T)| = 1$

$= \left| \frac{\beta}{1 + j2\pi f_T r_{\pi}(C_{\pi} + C_{\mu})} \right| = 1$

$= \frac{\beta}{\sqrt{1 + 2\pi f_T r_{\pi}(C_{\pi} + C_{\mu})}^2} = 1$

$= \frac{\beta}{\sqrt{1 + \left(\frac{f_T}{f_{\beta}}\right)^2}} = 1$

but  $\frac{f_T}{f_{\beta}} \gg 1$

$\frac{\beta}{\frac{f_T}{f_{\beta}}} = 1 \Rightarrow \boxed{f_T = \frac{\beta}{f_{\beta}}}$

example: find the 3dB frequency of the short-circuit current gain ( $A_i$ ) of BJT  
 given  $r_{\pi} = 2.6 \text{ k}\Omega$ ,  $C_{\pi} = 2 \text{ pF}$ ,  $C_M = 0.1 \text{ pF}$ .

$$f_B = \frac{1}{2\pi r_{\pi} (C_{\pi} + C_M)} = 29.1 \text{ MHz}$$

\* Note: High frequency BJT has small sizes. because  $f_B$  High  
 it means  $C_{\pi} \rightarrow C_M$  have small values  
 $\Downarrow$   
 so small size.

Ex.: Consider BJT that has  $f_T = 500 \text{ MHz}$  and  $I_C = 1 \text{ mA}$ .  
 $\beta = 100$ ,  $C_M = 0.3 \text{ pF}$ , find  $C_{\pi}$ .

$$f_B = \frac{f_T}{\beta} = \frac{500 \text{ MHz}}{100} = 5 \text{ MHz}$$

$$f_B = \frac{1}{2\pi r_{\pi} (C_{\pi} + C_M)} = \frac{100}{\frac{V_T}{I_C}} \cdot 0.026 \Rightarrow r_{\pi} = \square$$


$\frac{g_m}{\beta}$

$$C_{\pi} = 11.9 \text{ pF}$$

\* Miller effect & Miller capacitance.

$\Rightarrow C_M \ll C_{\pi}$  but we cannot ignore  $C_M$  due to Miller effect.

$\Rightarrow$  Miller theorem

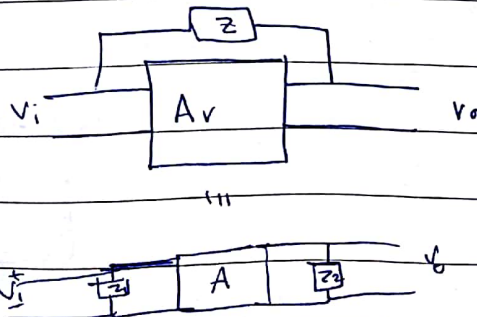




$$Z_{1s} = \frac{Z}{1 - A_v}$$

$$Z_{2s} = \frac{Z}{1 - \frac{1}{A_v}}$$


$$C_A \ll C_T$$

$$\frac{1}{j\omega C_A} \approx \infty \text{ (o.c.)}$$

\* Miller Theorem


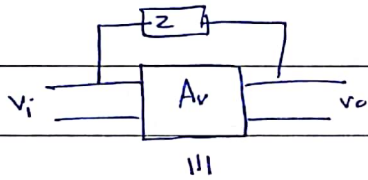

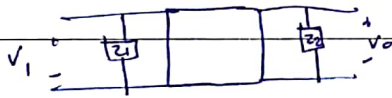
$$Z_{1s} = \frac{Z}{1 - A_{v(\text{max})}} \text{ in midband}$$



$$Z_{2s} = \frac{Z}{1 - \frac{1}{A_{v \text{ max}}}}$$

for Amp. CKTs (at High Frequency)

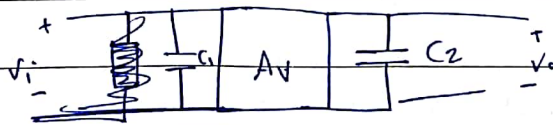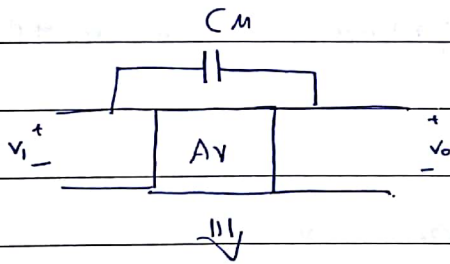


$$C_{1s} = C_M (1 - A_{v \text{ max}})$$

$$C_{2s} = C_M \left(1 - \frac{1}{A_{v \text{ max}}}\right)$$

→ small values.  
we can ignore it.

$C_1 \Rightarrow$  it's called  $C_M \Rightarrow$  Miller capacitance.

Example:-

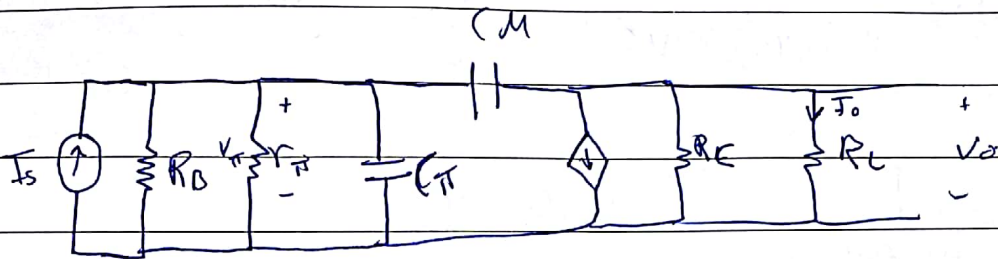

Given:  $\rightarrow R_C = R_L = 4\text{K}\Omega$ ,  $r_{\pi} = 2.6\text{K}\Omega$ ,  $R_B = 200\text{K}\Omega$ .


$g_m = 38.5\text{ m A/V}$ ,  $C_M = 0.2\text{ pF}$ ,  $C_{\pi} = 4\text{ pF}$

Find  $f_{3\text{dB}}$ :

(1) if we consider miller effect.

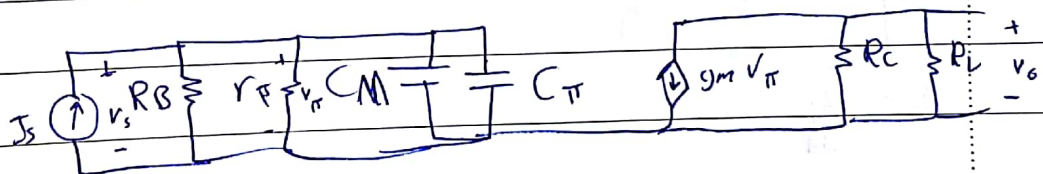(2) " " donot consider " "

$$1. f_{3\text{dB}} = \frac{1}{2\pi\tau}$$



$$C_{M_s} (1 - A_{v_{mid}})$$

$$= C_M (1 + g_m(R_C \parallel R_L))$$

$$= 15.6\text{ pF}$$

$$A_{v_{mid}} \frac{V_o}{V_s} = \frac{-g_m V_{\pi} (R_C \parallel R_L)}{V_{\pi}}$$

$$= -g_m (R_C \parallel R_L)$$


=

$$T.s \text{ Req } C_{eq} = R_{eq} (C_M + C_{\pi})$$

$$(R_B || R_{\pi}) (C_M + C_{\pi}) =$$


$$f_{3dB} = \frac{1}{2\pi (R_B || R_{\pi}) (C_M + C_{\pi})} = 3.16 \text{ MHz}$$

$$\textcircled{2} f_{3dB} = \frac{1}{2\pi (R_B || R_{\pi}) C_{\pi}} = 15.5 \text{ MHz}$$

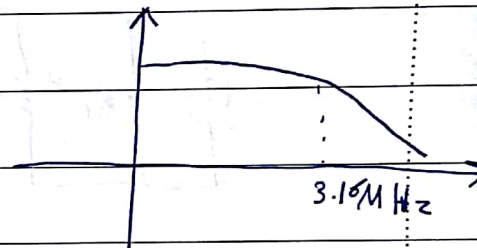

BW  $f_{3dB}$   
Miller  $\rightarrow$   $C_{\pi}$  effect.

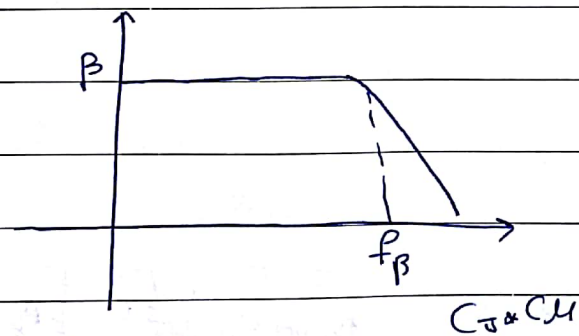
$f_{3dB}$  without Miller effect  $\approx 5 \times f_{3dB}$  (without Miller)




$$A_i = \frac{I_c}{I_B}$$

FET at High frequency:-



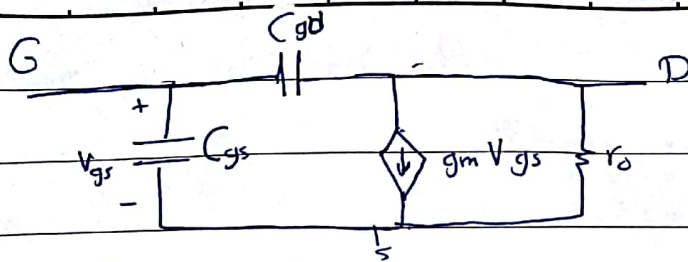


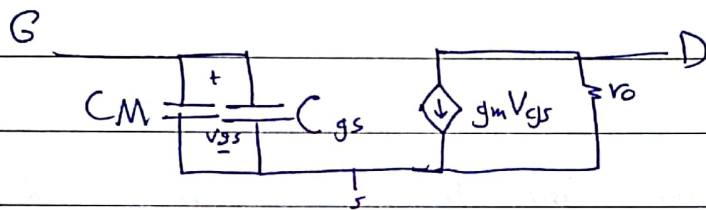$C_{gd} \ll C_{gs}$  but we cannot ignore  $C_{gd}$  due to Miller effect where:-



$$C_M = C_{gs}(1 - A_v)$$

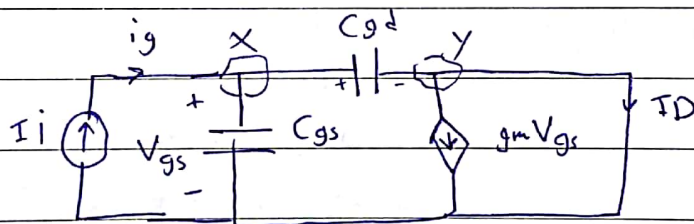\* effect of  $C_{gd}$  &  $C_{gs}$  on short-circuit current gain.



\* In DC & low  $\omega$  mid band frequenc.  $I_{G_S} = 0$

$$A_i = \frac{I_d}{I_g} = \infty$$

\* In High frequency Range

$$A_i = \frac{I_d}{I_g} =$$

KCL at X:

$$I_g = \frac{V_{gs}}{\frac{1}{j\omega C_{gs}}} + \frac{V_{gs}}{\frac{1}{j\omega C_{gd}}} = V_{gs} [j\omega (C_{gs} + C_{gd})] \quad \text{--- (1)}$$

KCL at  $y_i$ :-

$$i_d + \frac{V_{gs}}{j\omega C_{gd}} = g_m V_{gs} \quad \text{--- (2)}$$

Use (1) and (2)

$$A_i = \frac{g_m - j\omega C_{gd}}{j\omega (C_{gs} + C_{gd})}$$

Typically, at High Frequency:  $g_m \approx 1 \text{ mA/V}$ ,  $C_{gd} \approx 0.5 \text{ pF}$ ,

$$f_{H_{max}} = 100 \text{ MHz}$$



$$g_m \gg |j\omega C_{gd}|$$

So  $A_i = \frac{g_m}{j\omega (C_{gd} + C_{gs})}$

unity gain BW

$$A_i \text{ at } f_T \Rightarrow |A_i(f_T)| = 1$$

$$\frac{g_m}{2\pi f_T (C_{gd} + C_{gs})} = 1$$

$$f_T = \frac{g_m}{2\pi (C_{gd} + C_{gs})}$$

example: consider an n-channel MOSFET with parameters

$$K_n = 0.25 \text{ mA/V}^2$$

$$V_{Tn} = 1 \text{ V}, \lambda = 0, C_{gs} = 0.2 \text{ pF}, C_{gd} = 0.04 \text{ pF}$$

Assume the transistor is biased at  $V_{GS} = 3 \text{ V}$ , Find the Unity

gain  $f_u = (f_T)$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$$g_m = 2K(V_{GS} - V_{Tn}) \\ = 1 \text{ mA/V}$$

$$f_T = 663 \text{ MHz}$$

\* Finding  $T_c$ :-

- ① from plot
- ② from function
- ③ from circuit.

Case 1: one capacitor.  $T_c = R_{eq} C$


Case 2: more than one capacitor.

We use open-CKT and Short-CKT time constant.

Ex:



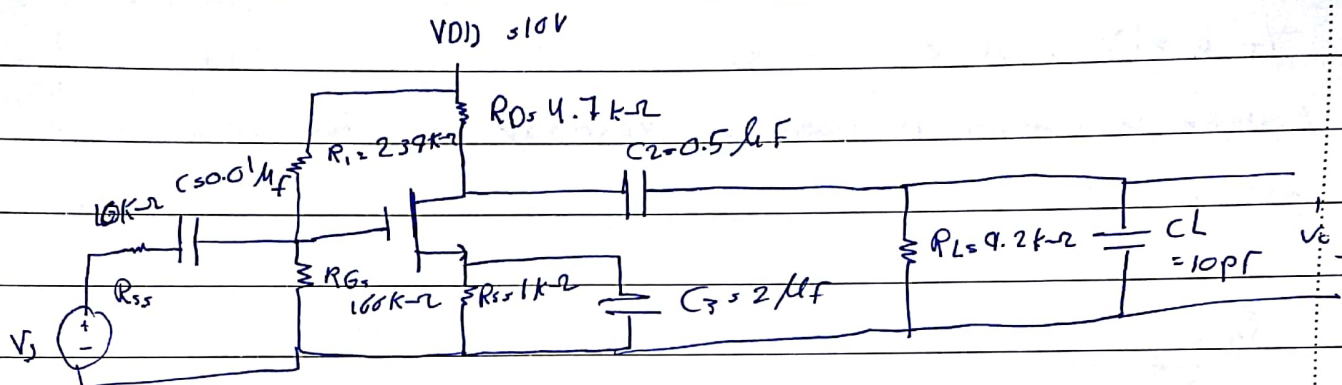Ex: Draw Frequency Response of the following Amp. CKT




Given:  $K_n = 0.4 \text{ mA/V}^2$

$V_{TN} = 1 \text{ V}$

$\lambda = 0$

$C_{gd} = 0.1 \text{ pF}$ ,  $C_{gs} = 1 \text{ pF}$

Common Source

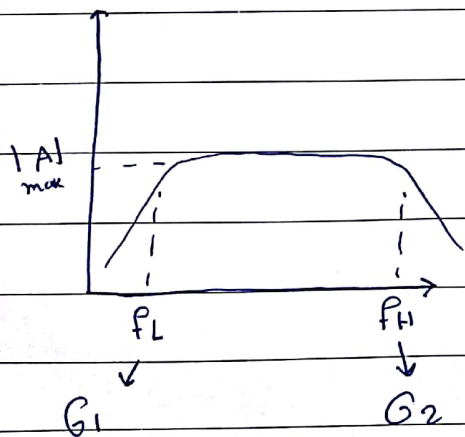

DC analysis:  $V_{GSQ} = 2.96 \text{ V}$


$I_{DQ} = 1.54 \text{ mA}$

$V_{DSQ} = 1.24 \text{ V}$

low frequency Range.

$G1 = Z_c$

$G2 = 0. C.$

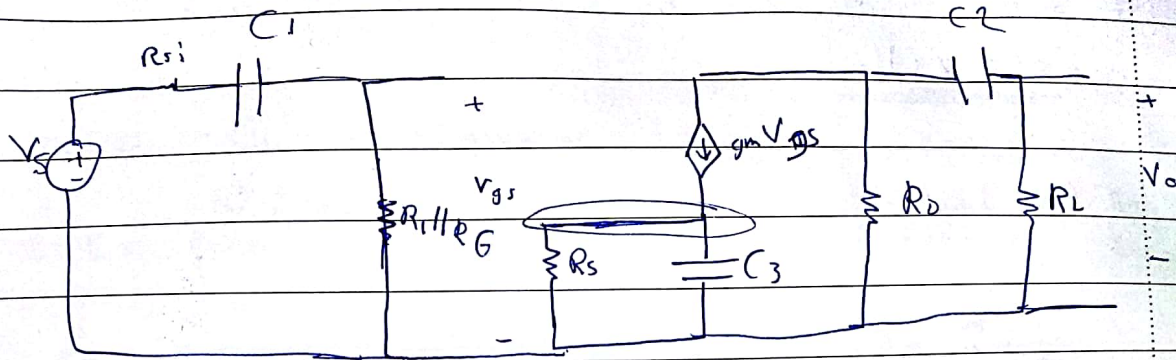

$\Rightarrow C_1$  only,  $C_2$  &  $C_3 = S.C$

$T_{1s}$  Req  $C_1$

$$\left( (R_1 \parallel R_2) + R_{si} \right) \times C_1$$

$$f_{L1} = \frac{1}{2\pi T_1} = 148.6 \text{ Hz}$$

$C_2$  only,  $C_1$  &  $C_3 = S.C$

$$T_2 = \text{Req } C_2 = (R_L + R_D) C_2$$

$$f_{L2} = \frac{1}{2\pi T_2} = 46.13 \text{ Hz}$$

$C_3$  only,  $C_1$  &  $C_2 = S.C$

$T_3$  Req  $C_3 =$

$$K_{CL} = gm V_{gs} + I_x = \frac{V_x}{R_s} \Rightarrow \frac{V_x}{I_x} = \frac{1}{gm + \frac{1}{R_s}}$$

$V_{gs} = -V_x$

$-V_x$


$$f_{L3} = \frac{1}{2\pi T_3} = 230.73 \text{ Hz}$$



$$f_L = \text{Max of } f_{L1}, f_{L2}, f_{L3}$$

$$= \underline{\underline{238.73 \text{ Hz}}}$$

at Mid band:-

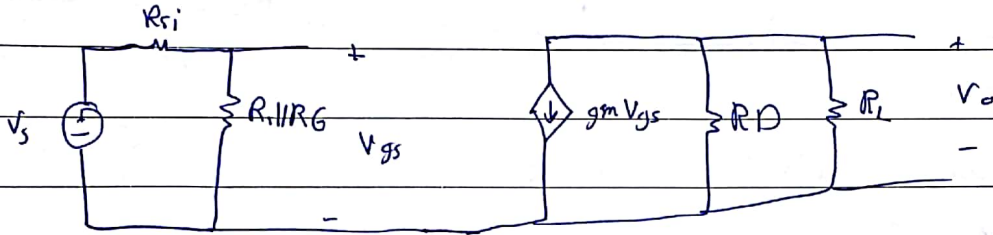

$$A_{vs} \frac{V_o}{V_s} =$$

$$V_{os} = g_m V_{gs} (R_L \parallel R_D) \quad \text{--- (1)}$$


$$V_{gs} = V_s \frac{R_i \parallel R_G}{R_i \parallel R_G + R_{si}} \quad \text{--- (2)}$$

$$A_{vs} = \frac{-g_m (R_L \parallel R_D) (R_i \parallel R_G)}{R_i \parallel R_G + R_{si}}$$

s = -2.32

\* High Frequency Range:
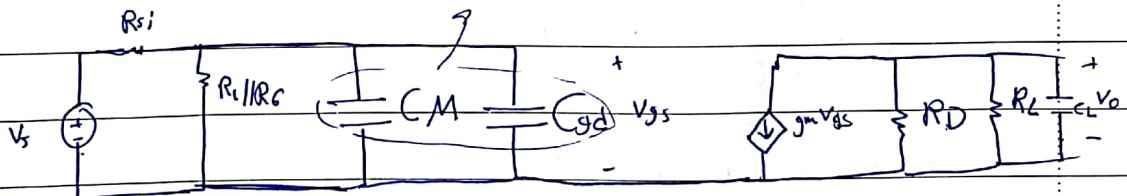
$$C_{eq} = C_M + C_{gs} = 1.33 \text{ pF}$$



$$C_M = C_{gd} (1 - A_v)$$

$$= C_{gd} [1 - (-2.32)]$$

$$C_M = 0.332 \text{ pF}$$

$C_{eq}$  only,  $C_L = \text{open}$ .

$$\tau = R_{eq} C_{eq} = R_{si} \parallel R_i \parallel R_G \quad C_{eq} = 1.2 \times 10^{-9} \text{ sec}$$

$$f_{H1} = \frac{1}{2\pi\tau} = 13.2 \text{ MHz}$$




$C_L$  only,  $\neq C_{eq}$  so.c

$$I_z = R_{eq} C_L$$



$$= R_D || R_L \quad C_L = 15 \text{ nSecond.}$$
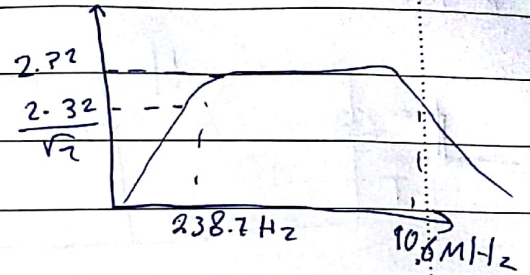
$$f_{H2} = \frac{1}{2\pi\tau_2} = 10.8 \text{ MHz}$$



So  $f_H = \text{minimum of } f_{H1} \text{ \& } f_{H2} = 10.6 \text{ MHz}$

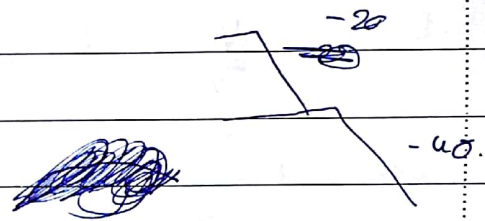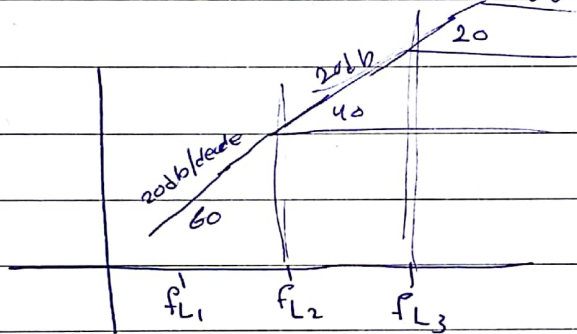
$$BW = 10.6 \text{ M} - 238.7 = 10.6 \text{ MHz}$$



\* Time Response:-


$\Rightarrow$  We consider: the time Response if input signal is an sinusoidal signal.

[Example: Square wave].

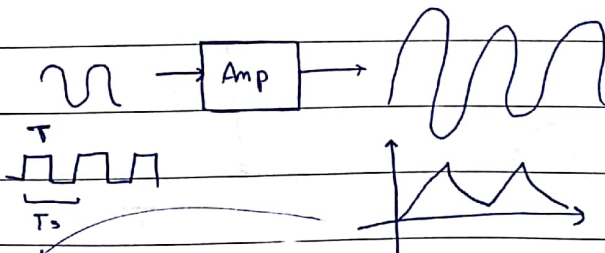

This  $\Rightarrow$  Distortion: The reason is due to coupling capacitor & load capacitors. (input CKT & output CKT).

\* Input CRT: -

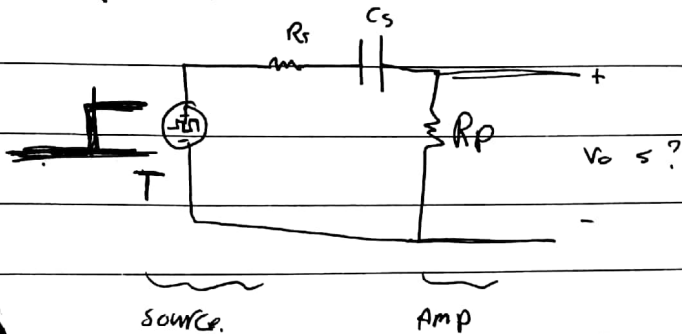

S-Domain : 
$$\frac{V_o(s)}{V_s(s)} = K \frac{sT}{1+sT}$$

where  $K = \frac{R_p}{R_p + R_s}$  ,  $T = (R_s + R_p)C_s$ .

$$V_o(s) = V_s(s) \times K \frac{sT}{1+sT}$$

if  $V_s(t) = u(t)$  then  $V_s(s) = \frac{1}{s}$

$$V_o(s) = \frac{1}{s} \times K \frac{sT}{1+sT}$$

$$V_o(s) = \frac{K T}{1+sT}$$

inverse Laplace  $\rightarrow V_o(t) = K e^{-\frac{t}{T}}$

We need  $V_o(t=T) = K$

$$K e^{-\frac{T}{T}} = K$$

So we need  $e^{-\frac{T}{T}} \approx 1$


So we need  $\frac{T}{T} \approx 0$  ,  $T \gg T$

(Rule  $T \gg 10T$ )

$\frac{1}{2} T_s \rightarrow$  period of  $V_s$

$$T_s = \frac{1}{f_s}$$

N O T S E B O O K

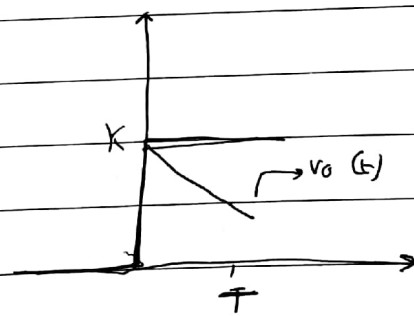

$$\tau \gg 10T$$

$$(R_s + R_p) C_s \gg 10T$$

we need  $C_s$  (coupling capacitor to be High value).