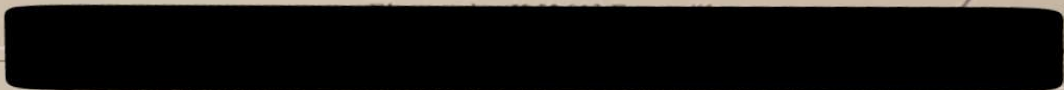


Electronics 2 1st Spring 16 Dr. Hani Jamleh

University of Jordan
Electrical Engineering Department
Engineering School



Monday, March 14, 2016 Time: 3:00 to 4:00 (60 min)

Question	Q1	Q2	Q3	Q4	Total
Total Points	3	4	5	8	20
Student's Score	3	2 2	4	6.5	15.5

Answer all the following 4 Questions clearly, fill in the blank your final answer, show details on the same sheet. Don't forget to label all plots and use the correct units per answer.

Question 1: [3-points]

The parameters of the transistor in the circuit in Figure Q.1 are $\beta = 100$, $V_A = 100$ V, and $V_T = 0.026$ V.

(a) Find the DC voltage at V_B

$V_B = -0.0346$ V

$I_{EQ} = 0.35$ mA
 $I_{BQ} = 3.47$ ~~10~~ μ A
 $I_{CQ} = 0.34$ mA
 $V_B = -I_{BQ} R_B = -0.346$

$I_E = (1 + \beta) I_{BQ}$

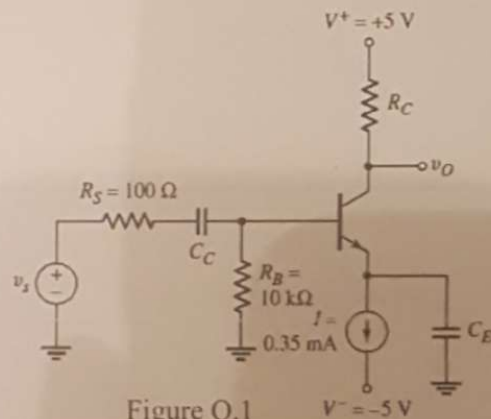


Figure Q.1

(b) Find the DC voltage at V_E

$V_E = -0.7346$ V

$V_{BE} = 0.7 = V_B - V_E$
 $V_E = V_B - 0.7 = -0.7346$

(c) Find R_C such that $V_{CEQ} = 3.5$ V.

$R_C = 6.44$ k Ω

$V_{CE} = V_C - V_E = 3.5$
 $V_C = 3.5 + V_E = 2.765$ V

$R_C = \frac{5 - 2.765}{0.347 \times 10^{-3}}$
 $= 6.44$ k Ω

Question 2: [4-points]

For the network of Figure Q.2, determine:

$r_{\pi} = 910 \Omega$

DC
 $r_{\pi} \equiv \frac{\beta V_T}{I_{ca} 0.5} = 910$

$12 = I_c R_c$
 $I_{ca} = \frac{12}{3k} = 4mA$



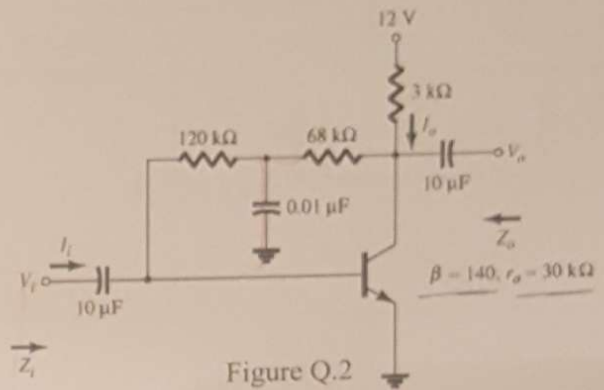


Figure Q.2

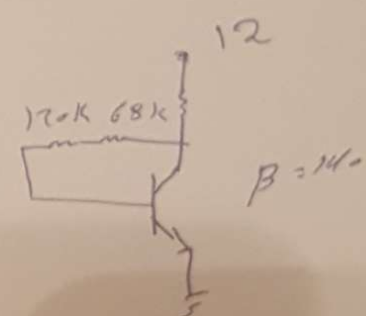

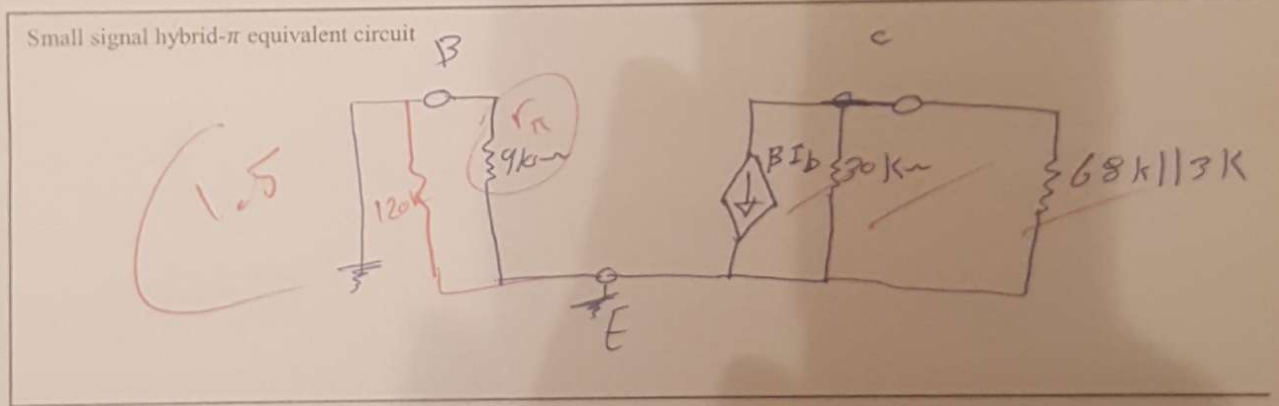Draw the small signal hybrid- π equivalent circuit in the box below.



Power Unit

Question 3: [5-points]

Consider the small signal model of amplifier circuit in Figure Q.3.


It has $I_{CQ} = 0.5\text{mA}$.

The transistor parameters are $\beta = 80$

and $V_A = 80\text{V}$.

Let $V_{BE(on)} = 0.7\text{V}$

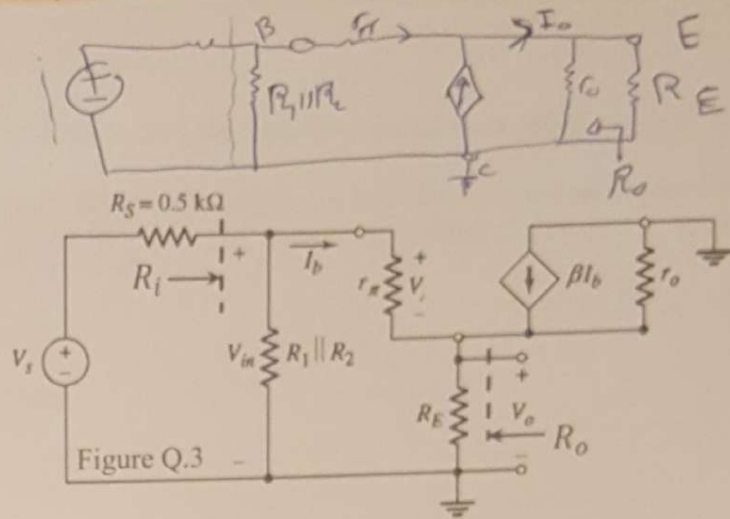- To get full credit, you need to show all your work!



In steps, show how you derive the formula for the following:

a)
$$R_i = R_1 \parallel R_2 \parallel \left[r_\pi + (1 + \beta)(r_o \parallel R_E) \right]$$

$$R_i = R_1 \parallel R_2 \parallel R_{ib}$$

$$R_{ib} = r_\pi + (1 + \beta)(r_o \parallel R_E)$$

$$I_o = I_b(1 + \beta)$$

Power Unit

b)
$$R_o = (R_E \parallel r_o) \parallel \frac{R_{ib}}{(1 + \beta)}$$

$$(R_E \parallel r_o) \parallel \frac{r_\pi \parallel R_1 \parallel R_2}{(1 + \beta)}$$

c)
$$A_{v_s} = \frac{V_o}{V_s} =$$

$$V_o = (r_o \parallel R_E)(1 + \beta) I_b$$

$$V_s = \frac{R_1 \parallel R_2 \parallel R_i}{R_s + R_1 \parallel R_2 \parallel R_i} V_{in}$$

$$\frac{R_1 \parallel R_2 \parallel R_{ib}}{R_s + R_1 \parallel R_2 \parallel R_{ib}} \cdot \frac{R_1 \parallel R_2 \parallel R_{ib}}{R_s + R_1 \parallel R_2 \parallel R_{ib}}$$

d) Briefly describe the meaning of "inverse resistance reflection rule"?

when look back into the ckt there is a factor $(1 + \beta)$ we should put in our calculation due to the dependent source

Question 4: [8-points] For the circuit in Figure Q.4, the transistor parameters are $\beta = 100$ and $V_A = \infty V$

To achieve the maximum undistorted swing in the output voltage, we need the total instantaneous C-E voltage to remain in the range $1 \leq V_{CE} \leq 8V$ and the minimum collector current is to be $i_c(\min) = 0.1mA$.

a) Write down the DC Load Line Equation:

$$I_{CQ} = \frac{V_{CEQ}}{R_C + R_E}$$

b) Write down the ac Load Line Equation:

$$i_c = \frac{-v_{ce}}{R_C \parallel R_L}$$

c) To achieve the maximum undistorted swing in the output, find the following:

$$\Delta I_C = 1.2 \text{ mA}$$

$$\Delta V_{CE} = 1.257 \text{ V}$$

$$I_{CQ} = 1.3 \text{ mA}$$

$$V_{CEQ} = 4.5$$


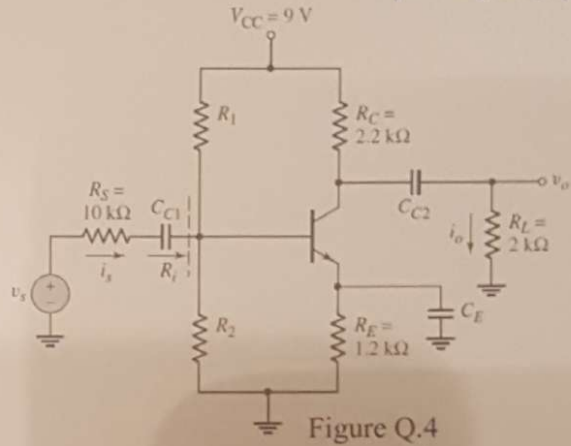


Figure Q.4

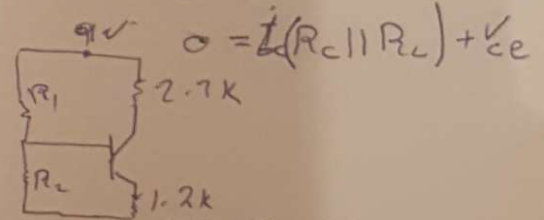

d) If the required $R_{TH} = 0.1(100 + 1)R_E$, suppose you found $I_{CQ} = 1mA$. Find R_1 and R_2

$$R_{TH} = 12.12 \text{ k}\Omega$$

$$R_1 = 50.9 \text{ k}\Omega$$

$$R_2 = 15.9 \text{ k}\Omega$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{50.9 R_2}{50.9 + R_2} = 12.12 \text{ k}\Omega$$

$$50.9 R_2 = 617.9 \text{ m}\Omega + 38.78 R_2 = 12.12 \text{ k}\Omega R_2$$

$$V_{Th} = 2.14 \text{ V} = \frac{R_2}{R_1 + R_2} \cdot 9 \text{ V} \Rightarrow R_1 = 50.9 \text{ k}\Omega$$

e) Give two reasons, why we need to use the ac load line to design a BJT amplifier?

it controls the gain & to make sure that the signal not distorted

f) How the DC load line is affected by increasing the resistor value R_1 ?

no affect

Power Unit

$$V = I_c R_c + V_{ce} + I_e R_e$$

$$I_c \approx I_e$$

$$V = V_{ce} = I_c (R_c + R_e)$$

$$I_{ca} = \frac{V}{R_c + R_e} = \frac{V_{ce}}{R_c + R_e}$$

$$0 = I_c (R_c \parallel R_e) + V_{ce}$$

$$I_c = \frac{-V_{ce}}{R_c \parallel R_e}$$

$$\Delta I_c = I_{ca} - I_c(\text{min})$$

$$\Delta I_c = \text{slope } \Delta V_{ce}$$


$$\Delta V_{ce} = V_{ceQ} - V_{ce}(\text{min})$$

$$V_{th} = I_b R_{th} + 0.7 + I_e R_e$$

$$I_{ca} = 1 \text{ mA}$$

$$I_{bQ} = 10 \mu\text{A}$$

$$V_{th} = 2.1417$$

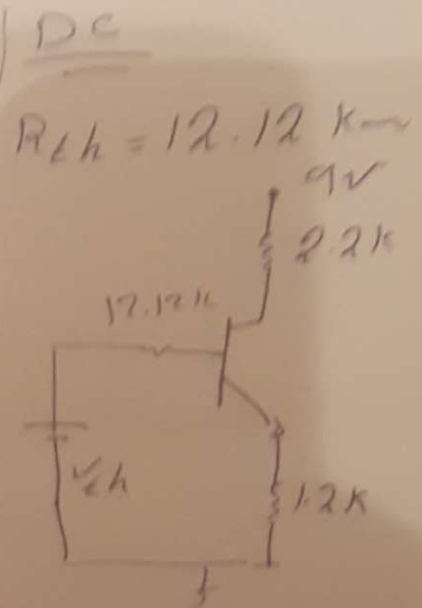

$$V_{ceQ} = 4.5 \text{ V}$$

$$I_{ca} = 1.3 \text{ mA}$$

Power Unit