

**Q1.** A particular amplifier has the Bode diagram shown in Figure 1. The unity gain bandwidth is

- a) 50 MHz      b) 150 kHz      c) 150 MHz      d) otherwise

**Q2.** A particular amplifier has the Bode diagram shown in Figure 1. The transfer function is

a)  $\frac{10^3}{1 + j \frac{f}{5 \times 10^3}}$

b)  $\frac{60}{1 + j \frac{f}{5 \times 10^7}}$

c)  $\frac{60}{1 + j \frac{f}{5 \times 10^3}}$

d)  $\frac{10^3}{1 + j \frac{f}{5 \times 10^7}}$

**Q3.** A particular amplifier has the Bode diagram shown in Figure 1. When the gain is 20 dB, then the 3 dB bandwidth is

- a) 2.5 MHz      b) 25 MHz      c) 5 MHz      d) additional information is needed

**Q4.** Consider the circuit shown in Figure 2. The midband gain is

- a)  $\frac{1}{3}$  V      b) 0.5 V      c) 0 V      d) need to know the frequency

**Q5.** Consider the circuit shown in Figure 2. The 3 dB high frequency  $f_H$  is

- a)  $\frac{1000}{6\pi}$  MHz      b)  $\frac{5000}{8\pi}$  MHz      c)  $\frac{50}{\pi}$  MHz      d) cannot decide

**Q6.** Consider the circuit shown in Figure 3 where  $v_i$  is a square wave of frequency 5 kHz. A suitable capacitance is

- a) 0.05 nF      b) 5  $\mu$ F      c) 5 nF      d) 500 nF

**Q7.** A particular amplifier has the Bode diagram shown in Figure 4. The amplifier

- a) Doesn't contain coupling and bypass capacitors      b) Must contain load capacitor  
c) Contains load, coupling, and bypass capacitors      d) Must contain bypass and coupling capacitors

**Q8.** The voltage gain of the op-amp circuit shown in Figure 3 is

- a)  $-\frac{R_2}{R_1 // R_3}$       b)  $-\frac{R_2}{R_1 + R_3}$       c)  $\frac{R_2}{R_1 // R_3}$       d)  $-\frac{R_2}{R_3}$

**Q9.** The input resistance of the standard inverting amplifier is  $R_i$ . The input resistance for the circuit shown in Figure 5 is

- a)  $R_i$       b)  $R_1 + R_2$       c)  $R_1 // R_2$       d) otherwise

**Q10.**  $v_o$  for the circuit shown in Figure 6 is

- a)  $2V_1 + 8V_2$       b)  $-2V_1 - 8V_2$       c)  $50V_2 - 20V_1$       d)  $20V_1 + 8V_2$

- Q11. For the circuit shown in Figure 7, if the saturation voltages are +10 V and -16 V, then  $V_o$  is equal to  
 a) 10 V      b) 8 V      c) -8 V      d) 5 V

- Q12. The gain of the circuit shown in Figure 8 is

- a) 1      b)  $\frac{R_2 + R_3}{R_1}$       c)  $\frac{R_1}{R_1 + R_2}$       d) 1

- Q13. The output of the circuit shown in Figure 9 is

- a)  $\frac{V_1}{R_1} (V_2 - V_1)$       b)  $\frac{R_1}{R_2} (V_2 - V_1)$       c)  $\frac{R_1}{R_2} V_2 - \frac{R_1}{R_2} V_1$       d) more information is needed

- Q14. The two capacitors in the circuit shown in Figure 10 affect the amplifier response at

- a) low frequencies      b) high frequencies      c) low and high frequencies      d) at any frequencies

- Q15. Define the frequency response. The sketch shows output of linear system with sinusoidal input signal (AC).

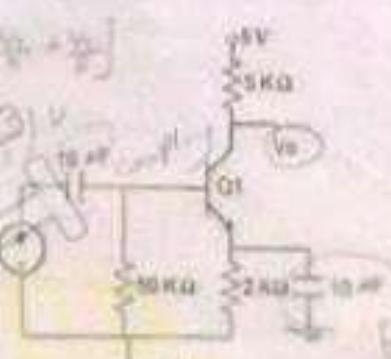
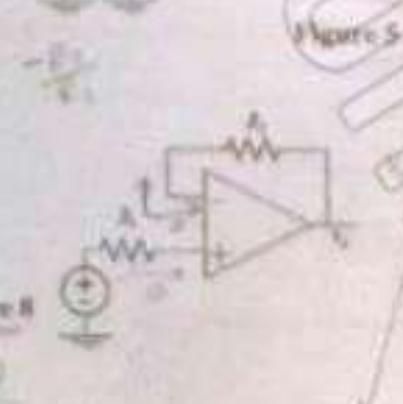
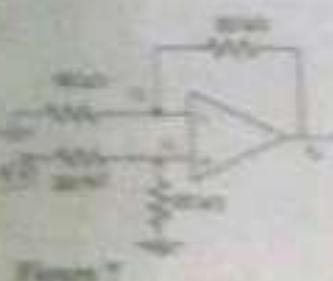
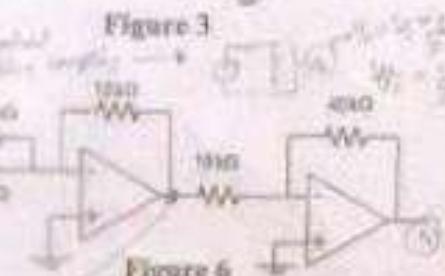
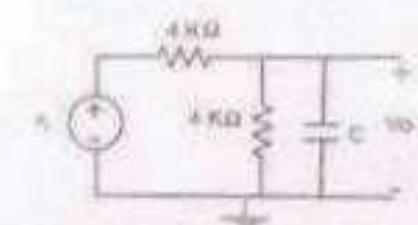
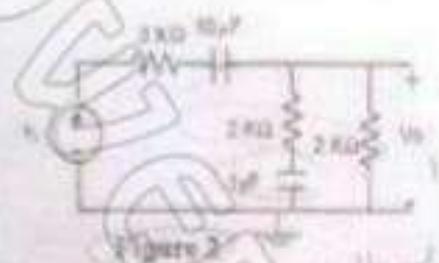
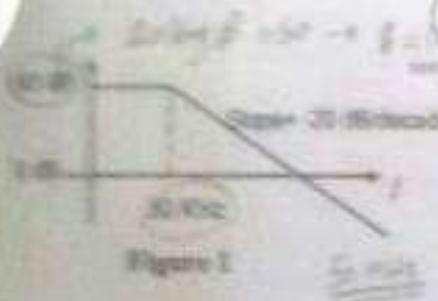


Figure 7

Figure 8

Figure 5

Figure 10

$$V_o = -g_C \left[ -100 \left( V_1 + V_2 \right) \right]$$

$$= 20V_1 + 5V_2$$

Figure 9

$$f = \frac{1}{2\pi RC} = \frac{1}{2\pi \times 10^{-9} \times 10^6} = 159\text{ Hz}$$

$$Z = \frac{1}{2\pi f C} = \frac{10^9}{2\pi \times 159 \times 10^{-9}} = 10^9 \Omega$$

$$1000 \text{ MHz} = \frac{10^9}{10^9} = 1000$$