

Amplifiers

NoteBook

Dr. Omar Ghzawi


By: Ahmad Fatafta



BJT Amplifiers:

* The use of the BJT as a linear device.

→ Consider the following ckt.

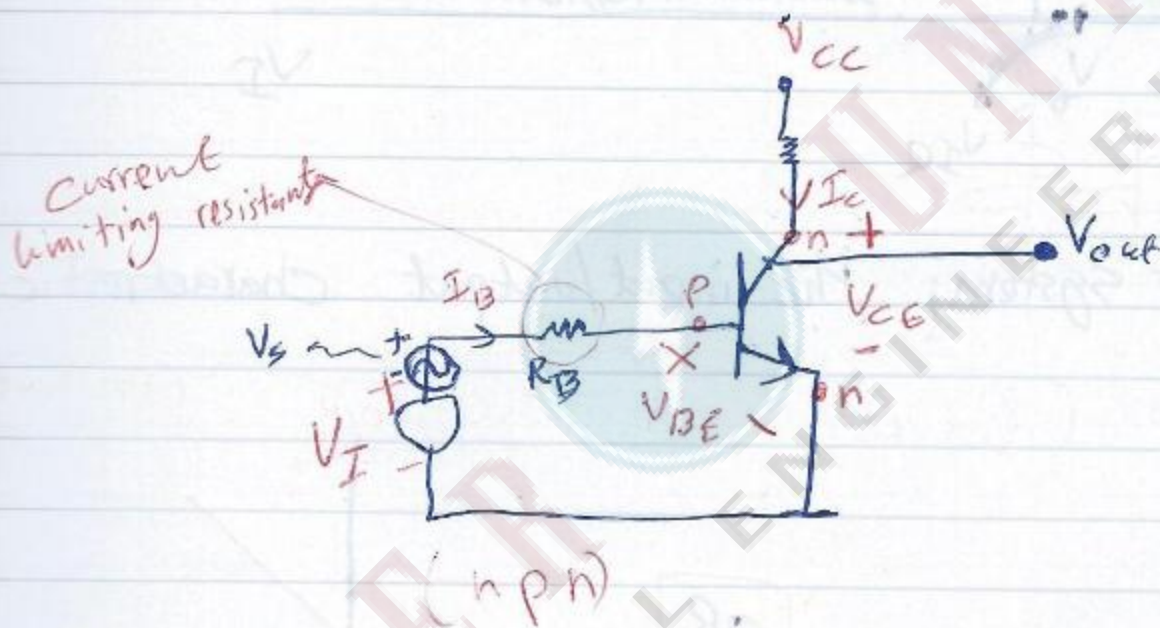

* if $V_I < V_{\frac{1}{2}}$ $\Rightarrow I_B = 0 \Rightarrow I_C = 0 \Rightarrow V_{out} = V_{CE} = V_{CC}$

* if $V_I \geq V_{\frac{1}{2}} \Rightarrow I_B = \frac{V_I - V_{\frac{1}{2}}}{R_B}$


$\Rightarrow I_C = \beta I_B$

$\Rightarrow V_o = V_{CE} = V_{CC} - R_C \cdot \beta \frac{(V_I - V_{\frac{1}{2}})}{R_B}$


Valid as long as $V_{CE} > V_{CEsat} \approx 0.2 \rightarrow 0.3$

* in all transistor ckt, we can't obtain any voltages larger than V_{CC} .

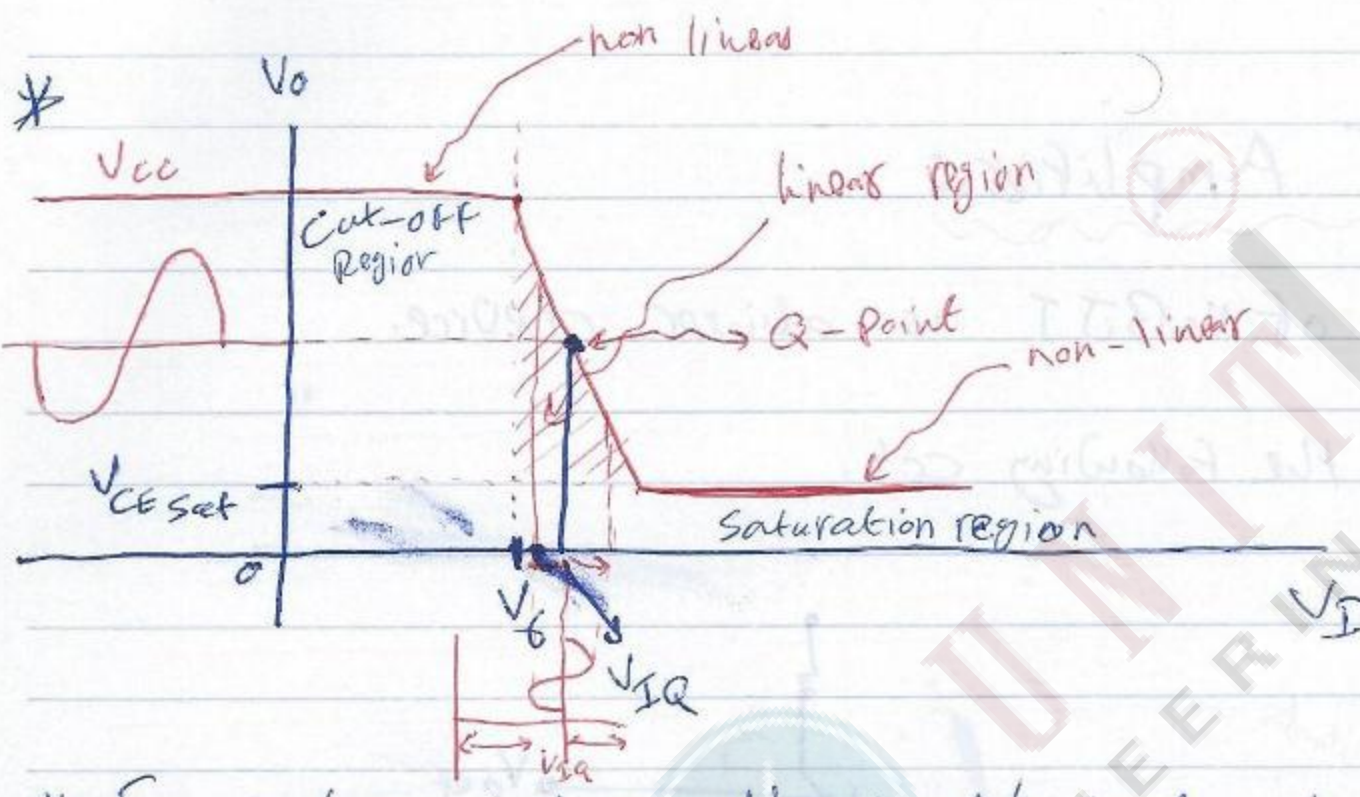* Consider $V_{CEsat} = 0.2$ in calculations.



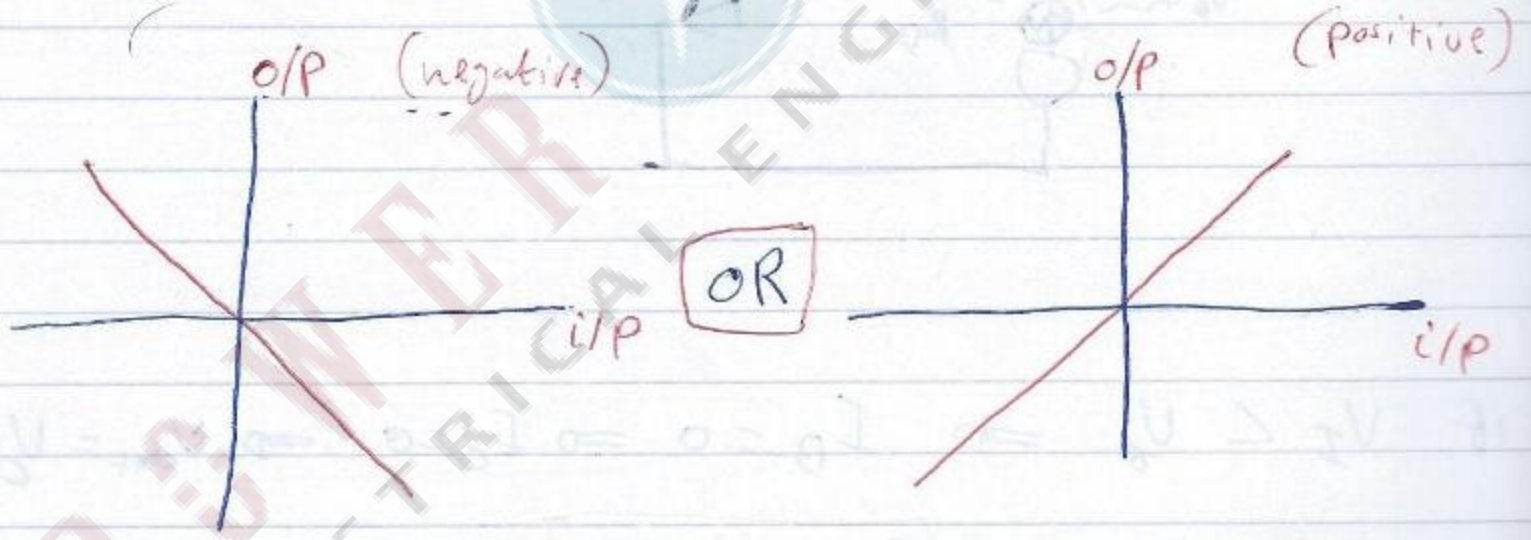* For a linear system; the input/output characteristics





*

page 3.71

* BJT Amplifier :-

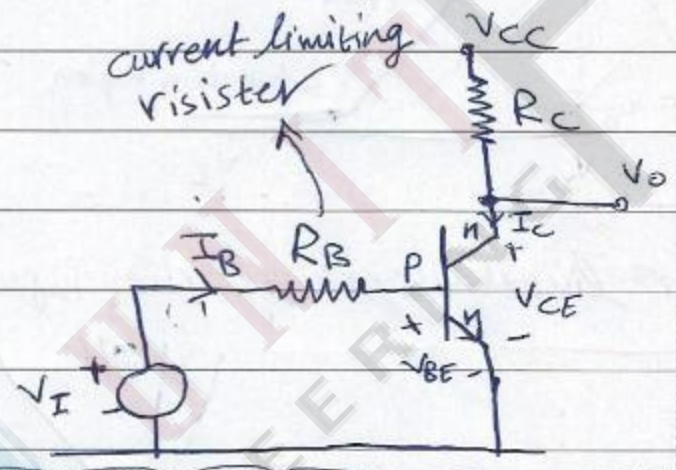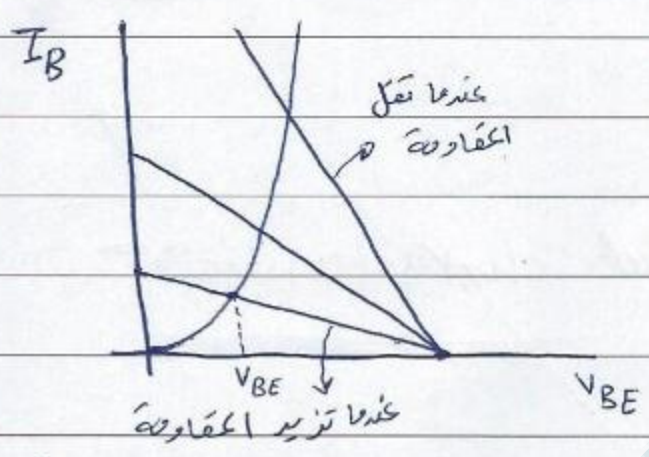The use of BJT as ~~following~~ ^{a linear} Device consider the following CKT.



* if $V_I < V_0 \rightarrow$ تيار اليبود صفر
 $I_B = 0 \Rightarrow I_C = 0 \Rightarrow V_o = V_{CE} = V_{CC}$
 Idealization

* إذا وصلنا DC source بدون مقاوة R_B يجب أن تكون قيمة قريبة من 0.7V وإذا كانت كبيرة سوف يمر تيار كبير يؤدي إلى تلف الترانزستور


* if $V_I > V_0 \Rightarrow I_B = \frac{V_I - V_0}{R_B}$

$$I_C = \beta \frac{(V_I - V_0)}{R_B} \Rightarrow V_o = V_{CE} = V_{CC} - R_C \cdot \beta \frac{(V_I - V_0)}{R_B}$$

valid as long as $V_{CE} > V_{CEsat} \approx 0.2$




* يبقى I_B يزداد ويؤدي إلى ازدياد V_{CE} إلى أنه يصل إلى قيمة V_{CE} ثابتة مع بقاء تغير I_B وتسمى هذه النقطة $V_{CEsat} \approx 0.2V$

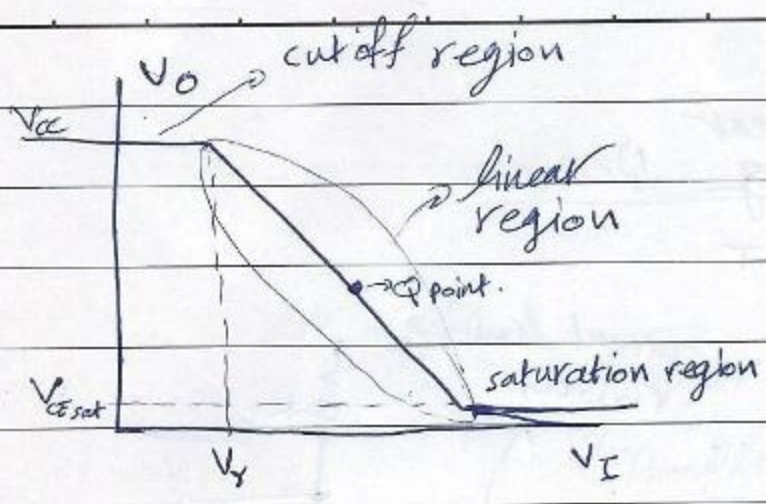* في كل دوائر الترانزستور لا يمكن أن تكون على فولت أكبر من V_{CC}



* لا يمكن ان نقول انه linear لانه لا يتغير output مع تغير input في هذه الحالات

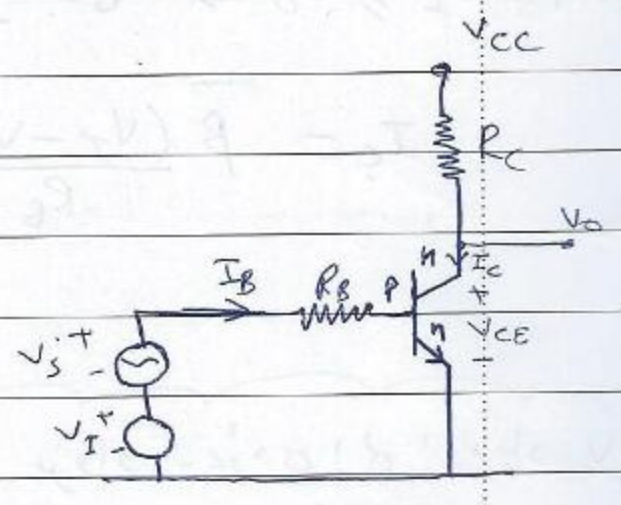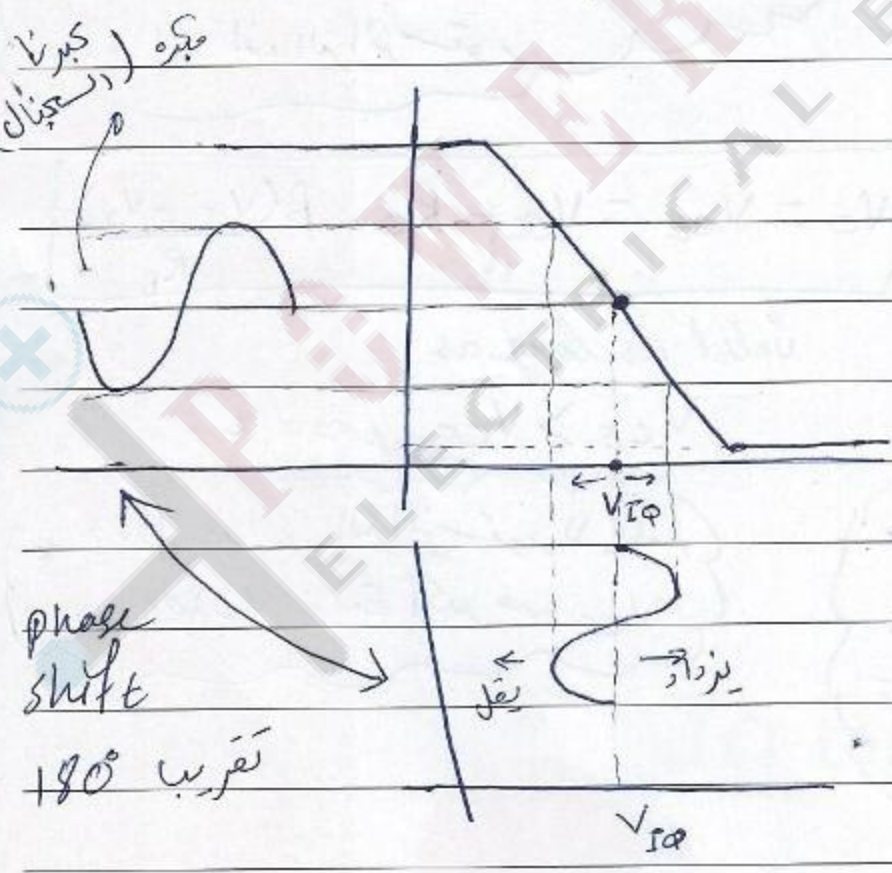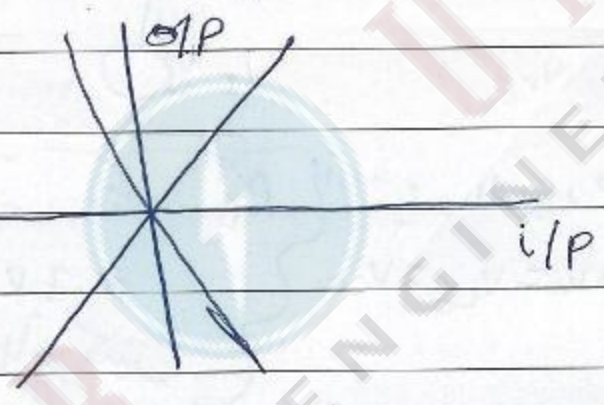* For linear system the input-output characteristic :-



* A matter of Notation :-

Convenient naming of variables together with subscripts helps in understanding and easy following of writing.

V_{DD}, I_D ; refer to dc quantities.

v_d, i, v_{gs} ; refer to ac quantities (time varying)

$v_{CE}, v_{GS}, v_{BE}, i_B$; refer to dc and ac (mixture of quantities)

So $i_B = \underbrace{I_B}_{\text{due to } V_I} + \underbrace{i_b}_{\text{due to } v_s}$

$v_{CE} = \underbrace{V_{CE}}_{\text{due to } V_I \& V_{CC}} + \underbrace{v_{ce}}_{\text{due to } v_s}$

ب) اشارة الى
قيمة الجهد

ب) اشارة الى
قيمة الجهد

* Linearization of the BJT :-

Consider

$$i_B = \frac{I_s}{\beta} e^{\frac{v_{BE}}{V_T}}$$


$$I_{BQ} + i_b = \frac{I_s}{\beta} e^{\frac{V_{BE} + v_{be}}{V_T}}$$

$$= \frac{I_s}{\beta} e^{\frac{V_{BE}}{V_T}} \cdot e^{\frac{v_{be}}{V_T}}$$

$$= I_{BQ} e^{\frac{v_{be}}{V_T}}$$

$$= I_{BQ} \left(1 + \frac{v_{be}}{V_T} + \frac{1}{2!} \left(\frac{v_{be}}{V_T} \right)^2 + \dots \right)$$

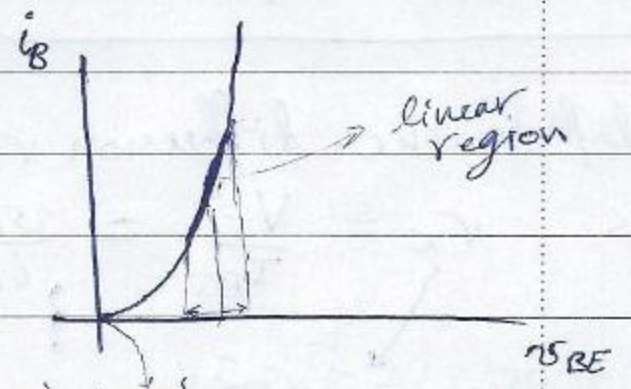في كل واحد $V_T \gg v_{be}$... neglected to get a linear model



منه
 $\frac{I_s}{\beta} e^{\frac{V_{BE}}{V_T}}$
"1 + P. value"

$$e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$$


$$e^{jx} = 1 + jx + \frac{(jx)^2}{2!} + \dots$$

$$\cos x + j \sin x = \left(1 - \frac{x^2}{2!} + \frac{x^4}{4!} - \dots \right) + j \left(x - \frac{x^3}{3!} + \dots \right)$$

* so if $v_{be} \ll V_T$ then

$$I_{BQ} + i_b = I_{BQ} \left(1 + \frac{v_{be}}{V_T} \right)$$

$$i_b = \frac{I_{BQ}}{V_T} v_{be}$$

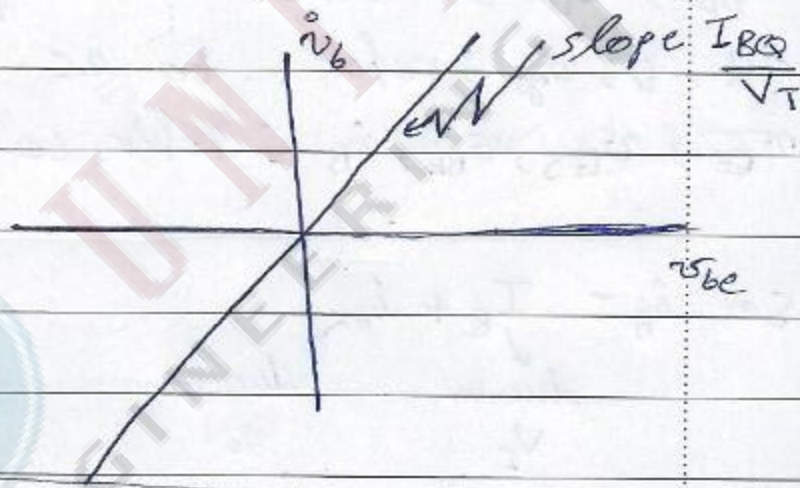

* if $v_{be} = 10 \text{ mV}$


then, the truncated exponential is 90% of the exact exponential

* Remember: $V_T = 0.026$

* define the diffusion resistance as r_π (base-emitter resistance)



$$\text{as } r_\pi = \frac{V_T}{I_{BQ}} = \frac{v_{be}}{i_b}$$

$i_b \propto v_{be}$

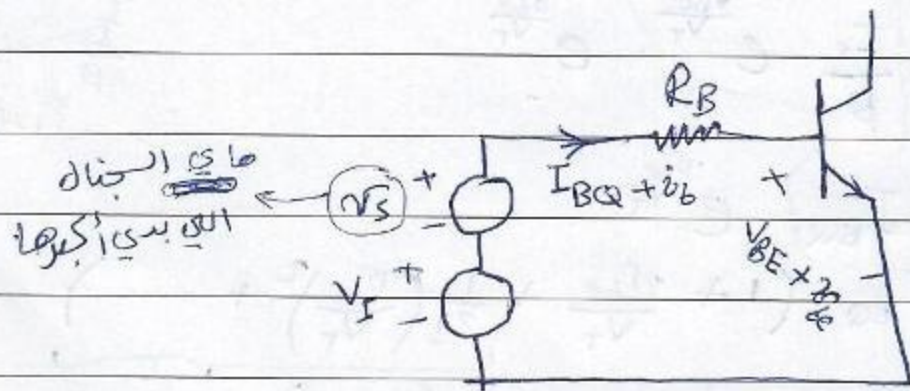

* Connections of source and resistors :-

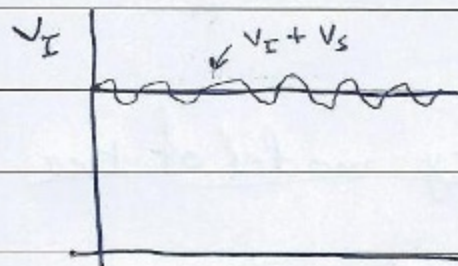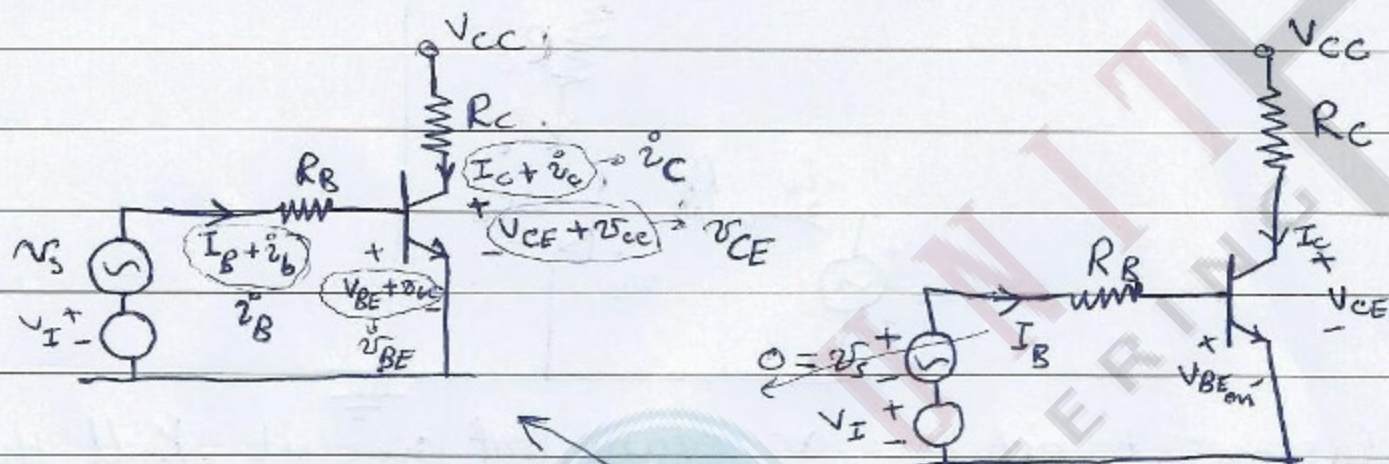Small signal Equivalent circuit
with reference to the following circuit



خطی - linear circuit ہے جس میں \$v_s\$ اور \$V_{BE}\$ کی وجہ سے قیود کا اثر ہے۔
cutoff region کے لیے \$v_s\$ کی مقدار کم ہوگی اور saturation region کے لیے زیادہ ہوگی۔

$$V_I + v_s = R_B i_B + v_{BE}$$

$$= R_B I_B + R_B i_b + V_{BE(on)} + v_{be}$$

$$V_I + v_s = R_B I_B + V_{BE(on)} + R_B i_b + v_{be}$$

$$\Rightarrow v_s = R_B i_b + v_{be}$$

consider the output circuit

$$V_{CC} = R_C i_c + v_{CE}$$

$$V_{CC} = R_C I_C + R_C i_c + V_{CE} + v_{ce}$$

$$V_{CC}^{+0} = R_C I_C + V_{CE} + R_C i_c + v_{ce}$$


$$\Rightarrow R_C i_c + v_{ce} = 0$$

$$\Rightarrow v_s = R_B i_b + v_{be}$$

$$R_C i_c + v_{ce} = 0$$

نیز در این مدار ولتاژ و جریان را می توانیم پیدا کنیم

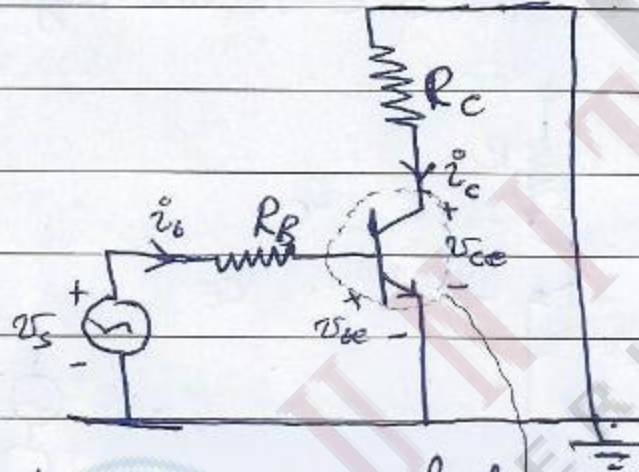v_{be} ← short circuit
 i_b ← open circuit
 DC sources // job



Conclusion: to get the ac equivalent circuit kill the independent sources:

* To get the small signal low frequency model of the


nPN BJT :-

$$v_{be} = v_{\pi} i_b$$

Using

$$\Delta i_c = \left. \frac{\partial i_c}{\partial v_{BE}} \right|_{Q\text{-point}} \Delta v_{BE}$$


$$i_c = \left. \frac{\partial i_c}{\partial v_{BE}} \right|_{Q\text{-point}} v_{be}$$

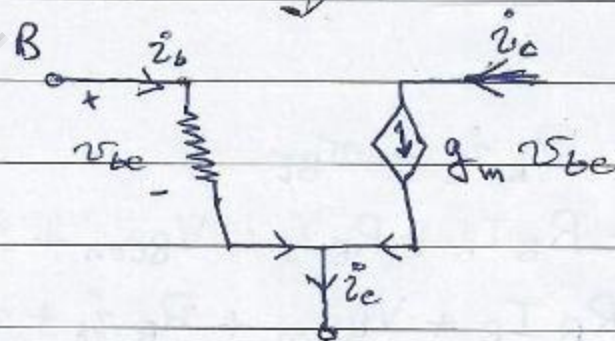

$$\frac{\partial}{\partial v_{BE}} \left(I_S e^{\frac{v_{BE}}{V_T}} \right) = \frac{1}{V_T} I_{CQ}$$

$$i_c = \frac{I_{CQ}}{V_T} v_{be}$$
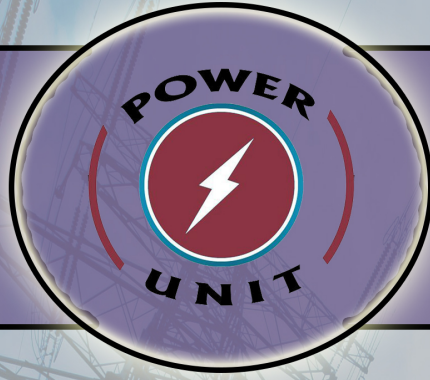
$$i_c = g_m v_{be} \quad \text{transconductance}$$



Amplifiers NoteBook

Dr. Omar Ghzawie


By . Abdalrahman alsa'ade

بأفكارنا نبدع


29-6-2014

Sunday

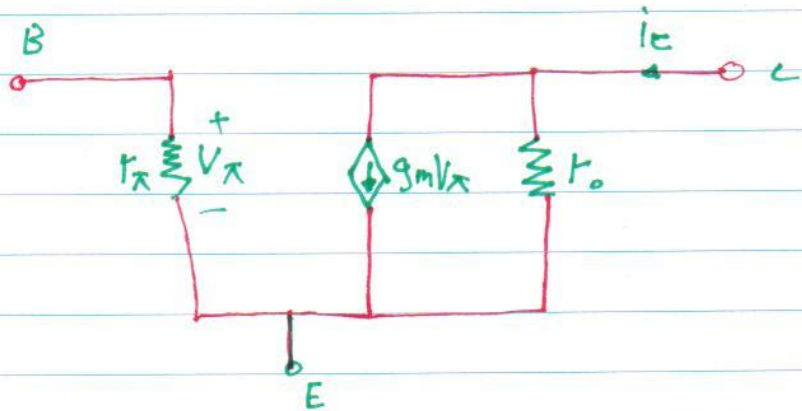V_o is known as the output resistance of the transistor this reflected on the model as shown:



* An Extended BJT model

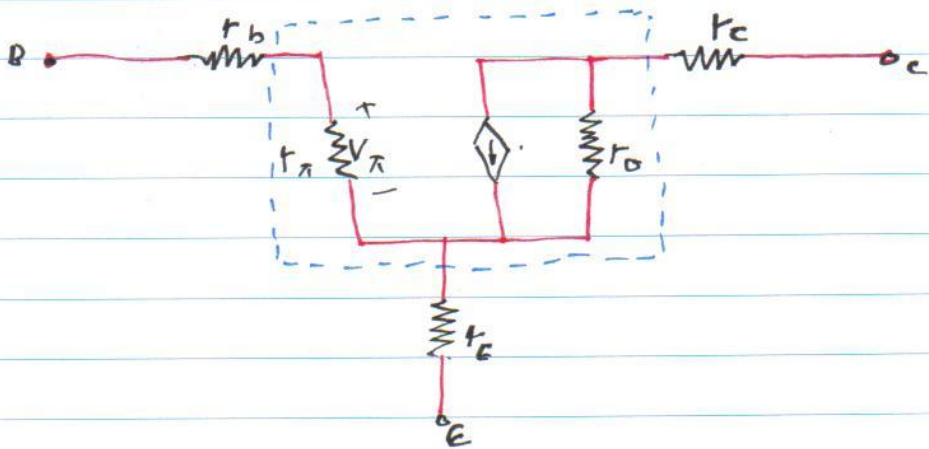

Let: $r_o = \infty$
 $r_c = r_b = r_e = 0$

30-06-2014
monday

* For a particular transistor ckt:

$$\text{given: } i_B = \underbrace{20 \times 10^{-6}}_{DC} + \underbrace{0.0008 \sin \omega t}_{AC} \text{ A}$$

$$\beta_{DC} = 100$$

Find ① I_{BQ}

② r_{π}

③ g_m

④ β_{ac}

⑤ i_b

⑥ I_{CQ}

⑦ i_c

Sol...

$$1) I_{BQ} = 20 \times 10^{-6} = 20 \mu\text{A}$$

$$2) r_{\pi} = \frac{V_T}{I_{BQ}} = \frac{V_T}{I_{CQ}/\beta_{DC}}$$

$$= \frac{25 \text{ mV}}{20 \mu\text{A}} = \frac{0.025}{20 \times 10^{-6}}$$

$$= 1.25 \text{ k}\Omega$$

problem

$$(3) I_{CQ} = \beta_{DC} \times I_{BQ}$$

$$A \quad I_{BQ} = 100 \times 20 \mu A = 2000 \mu A$$

$$= 2000 \mu A$$

$$= 2 \text{ mA}$$

$$(4) g_m = \frac{I_{CQ}}{V_T}$$

$$= \frac{2 \text{ mA}}{25 \text{ mV}} = \frac{1}{12.5}$$

$$= 0.08 \text{ A/V}$$

$$= 80 \text{ mA/V}$$

$$(5) \beta_{AC} = g_m \times r_{\pi}$$

$$= 80 \times 1.25$$


$$= 100$$

6. $i_b = 0.0008 \sin \omega t \text{ A}$

$0.8 \sin \omega t \text{ mA}$



7

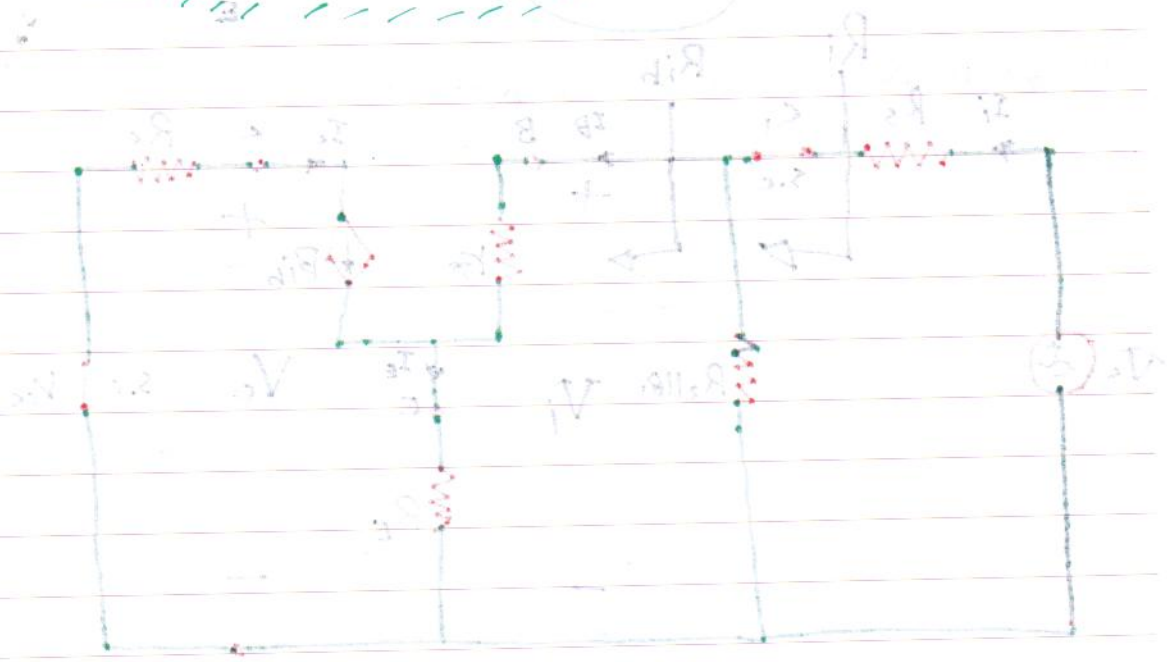$V_T = 25 \text{ mV}$
OR
 $V_T = 26 \text{ mV}$



1-07-2014

* Common Emitter *

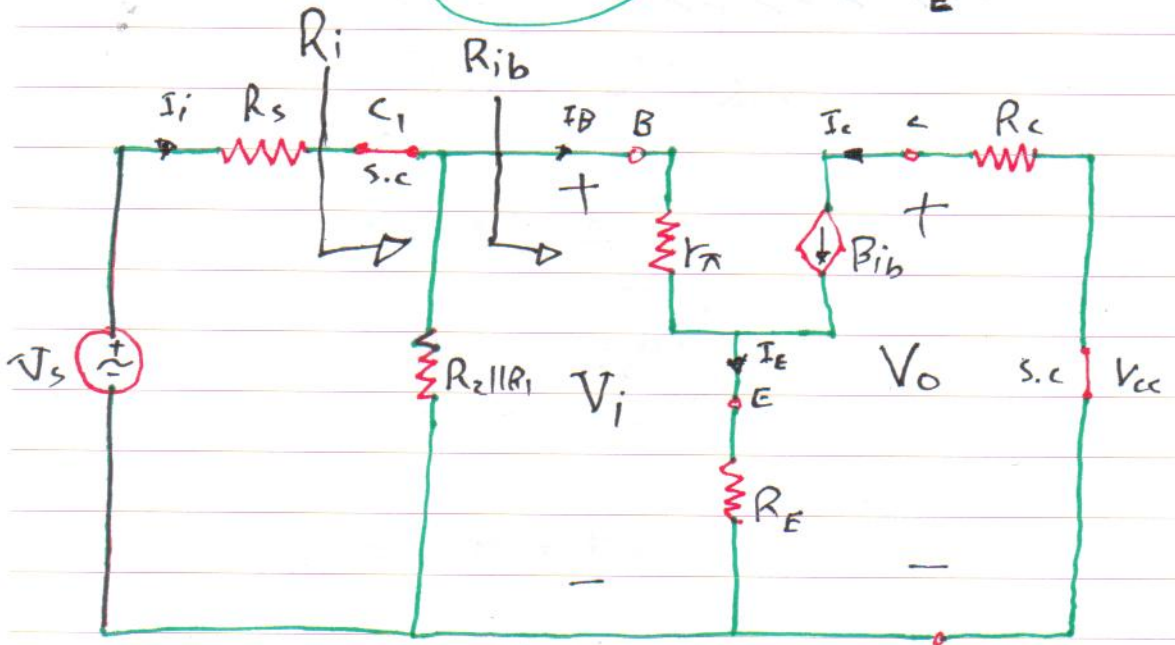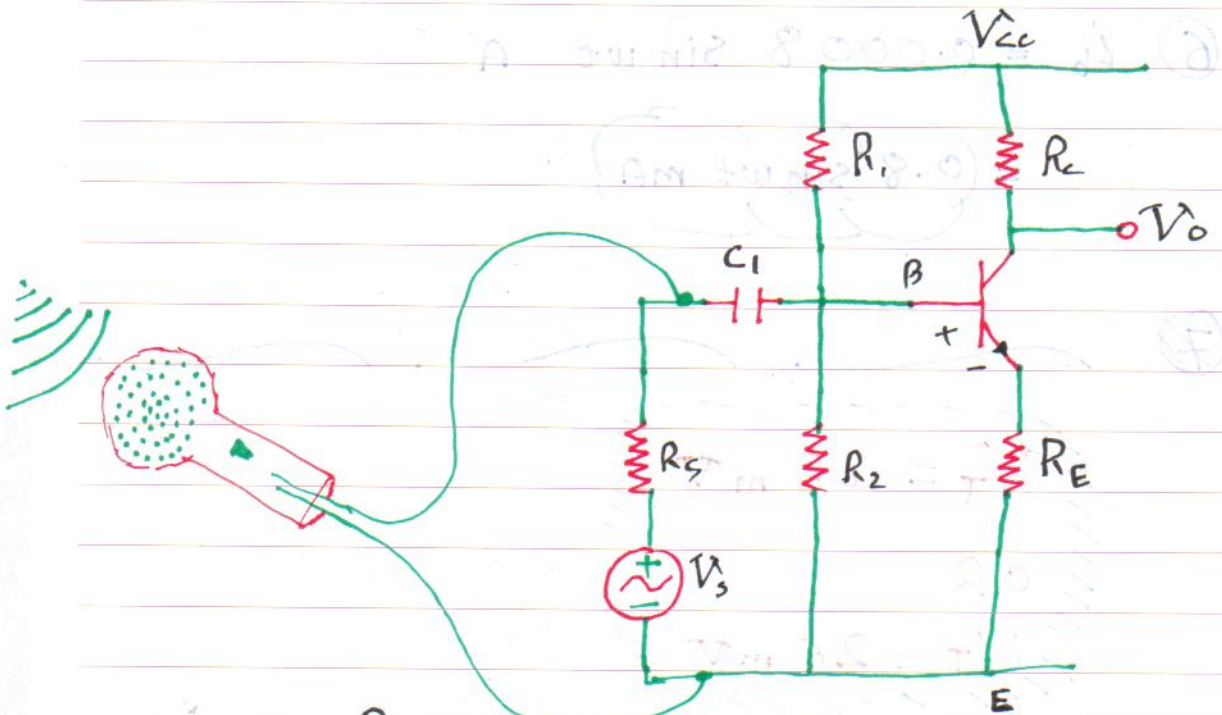

* R_i : input (R) seen by (R_s). * $V_o = -R_o i_b = -\beta V_i$ *

* R_{ib} : (R) input base

* the input resistance looking into the base (R_{ib}) is:

$$R_{ib} = \frac{V_i}{i_b} = \frac{r_{\pi} i_b + R_E (1+\beta) i_b}{i_b}$$
$$= r_{\pi} + (1+\beta) R_E$$

* the input resistance seen by (R_s) is (R_i):

$$R_i = \frac{V_i}{I_i} = \frac{R_{ib} \times i_b}{i_b + \frac{R_{ib} \times i_b}{R_1 \parallel R_2}}$$

$$= \frac{R_{ib}}{1 + \frac{R_{ib}}{R_1 \parallel R_2}}$$

$$= R_1 \parallel R_2 \parallel R_{ib}$$

2-07-2014

$$* V_o = -R_c i_c = -R_c \times \beta \times i_b$$

$$= -\beta \times R_c \times \frac{V_i}{R_{ib}}$$

$$= \frac{-\beta \times R_c}{R_{ib}} \times \frac{R_i}{R_i + R_s} \times V_s$$

$$A_v = \frac{V_o}{V_s} = \frac{-\beta \times R_c}{r_\pi + (1+\beta)R_E} \times \frac{R_i \parallel R_2 \parallel (r_\pi + (1+\beta)R_E)}{R_i \parallel R_2 \parallel (r_\pi + (1+\beta)R_E)} \frac{V_s}{V_s}$$

* if $R_i \gg R_s$:

$$A_v = \frac{-\beta R_c}{R_{ib}} = \frac{-\beta R_c}{r_\pi + (1+\beta)R_E}$$

* if $(1+\beta)R_E \gg r_\pi$:

$$A_v = \frac{-\beta R_c}{(1+\beta)R_E}$$

Since $\beta \gg 1$: $\beta \approx \beta + 1$


$$A_v = \frac{-R_c}{R_E}$$

$$|A_v| < 20$$

3-7-2014

* for (common-emitter); there are:

- 1- Current gain
- 2- Voltage gain

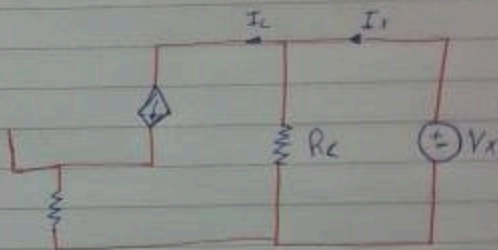

$$R_o = \frac{V_x}{I_x} = \frac{V_x}{\frac{V_x}{R_c} + \beta I_b} \quad \text{--- (1)}$$

if $I_b = \text{zero}$

$$R_o = \frac{V_x}{\frac{V_x}{R_c}} = R_c$$

$$AV = -\frac{R_c}{V_x + (1+\beta)R_e} = \frac{R_c}{R_c + R_s}$$


* For Voltage Amplifier (i/p, o/p):

" R_c " is ideally ($\infty \Omega$)

Practically its $R_c \gg R_s$

* " i_c " depends on " V_{cc} " and " i_b "

**** * Current gain * * ***

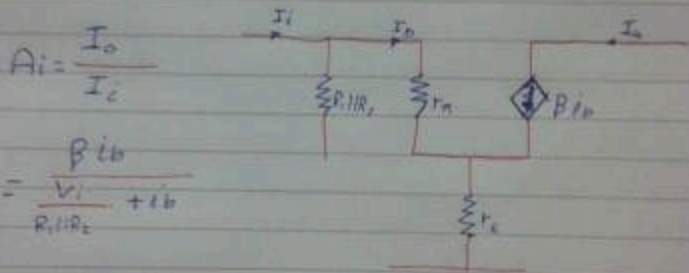


$$A_i = \frac{I_o}{I_i}$$

$$= \frac{\beta i_b}{\frac{V_i}{R_1 \parallel R_2} + i_b}$$

$$= \frac{\beta I_b}{\frac{(r_{\pi} + (1 + \beta) R_e) I_b + I_b}{R_1 \parallel R_2}}$$
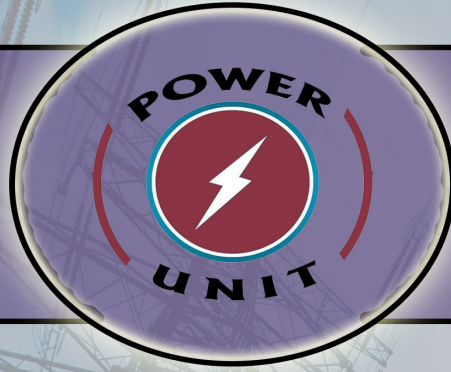
$$= \frac{\beta}{1 + \frac{r_{\pi} + (1 + \beta) R_e}{R_1 \parallel R_2}}$$



Amplifiers Notebook


Dr. Omar Alghzawi

By . Ahmad Alghzawi

بأفكارنا نبدع



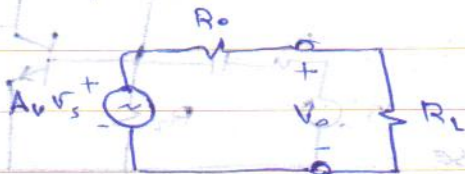* So from the load point of view, it experiences the following cct.



$$V_o = \frac{R_L}{R_o + R_L} (A_v V_s)$$

* to get maximum output, R_o should be $\ll R_L$. ideally we require $R_o = 0 \Omega$.

ex: consider the CE amplifier, based on

$A_v = -\frac{R_c}{R_E}$ Design where $R_E = 500 \Omega$ (For dc analysis)

choose R_c such that $A_v = -10$

$$R_o = 2k\Omega$$

$$R_o = R_c = 2k\Omega$$

$$\text{so } A_v = -\frac{R_c}{R_E} = -4$$


* trick

subdivide R_E into 200Ω &

300Ω (bypassed by a large

capacitance) 10's of μF

For ac analysis

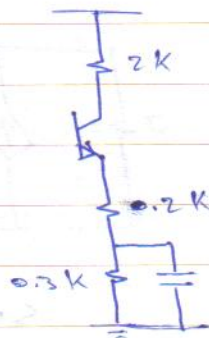


amplifiers

ex: Consider the following ckt.

* no need to calculate

↳ From scratch

it is a special case

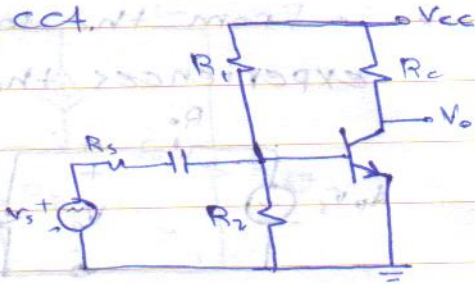

↳ about of the CE configuration, i.e. $R_E = 0$

$$R_{ib} = r_{\pi} + (1 + \beta)R_E \Big|_{R_E=0} = r_{\pi}$$

$$R_i = R_1 \parallel R_2 \parallel r_{\pi} \approx r_{\pi} \text{ generally}$$

* i.e. R_i is reduced considerably (considered a disadvantage).

$$A_v = \frac{-\beta R_c}{r_{\pi} + (1 + \beta)R_E} \frac{R_i}{R_i + R_s} \Big|_{R_E=0}$$

$$\approx \frac{-\beta R_c}{r_{\pi}} \frac{r_{\pi}}{r_{\pi} + R_s} = \frac{-g_m r_{\pi} R_c}{r_{\pi} + R_s}$$






$$= -g_m R_c \text{ provided } R_s \ll r_{\pi}$$

$$\text{So } g_m R_c > \frac{R_c}{R_E}$$

$$R_o = R_c \Big|_{R_E=0} = R_c$$

$$A_i =$$

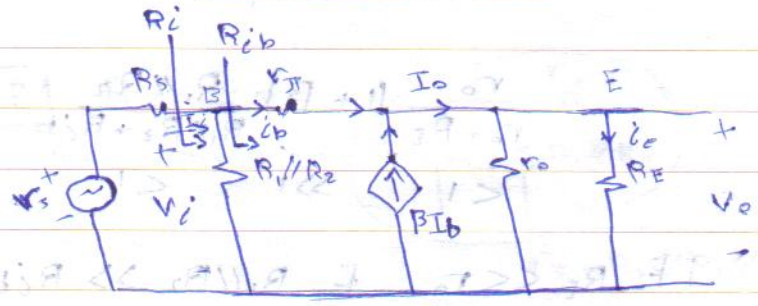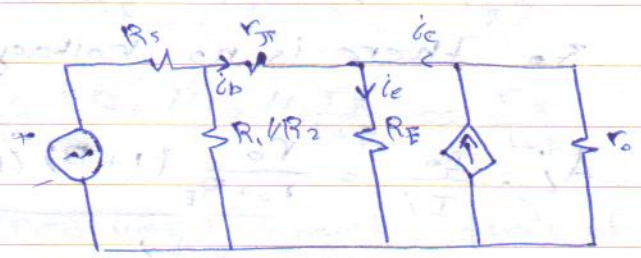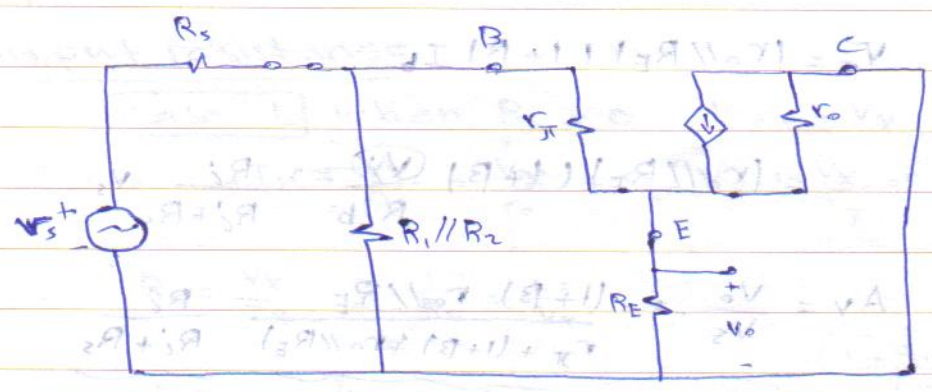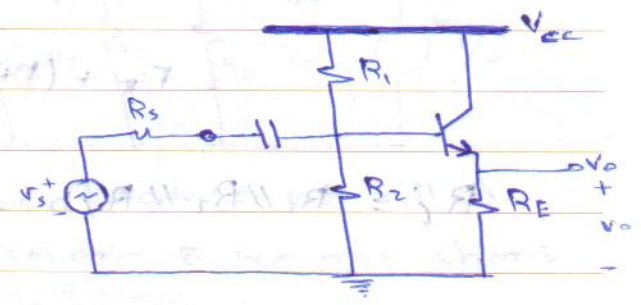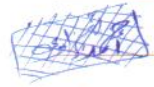* the common collector (Emitter follower) Amp.




$A_v < 1$

take the outer loop, there is voltage drop on R_s & r_{π} so $V_o < V_s$

$$-V_s + I R_s + I_b r_{\pi} + V_o = 0$$

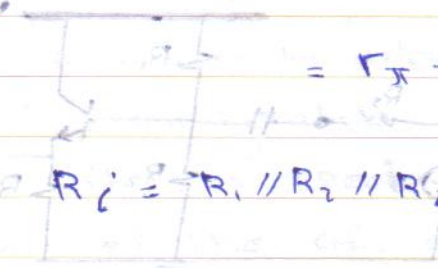
$$R_{ib} = \frac{V_o}{I_b} = \frac{r_{\pi} I_b + (1+\beta) I_b (r_o \parallel R_E)}{I_b}$$



$$= r_{\pi} + (1+\beta) (r_o \parallel R_E)$$

$$R_i = R_1 \parallel R_2 \parallel R_{ib} = \frac{R_1 \parallel R_2 (r_{\pi} + 1+\beta (r_o \parallel R_E))}{(R_1 \parallel R_2) + r_{\pi} + 1+\beta (r_o \parallel R_E)}$$
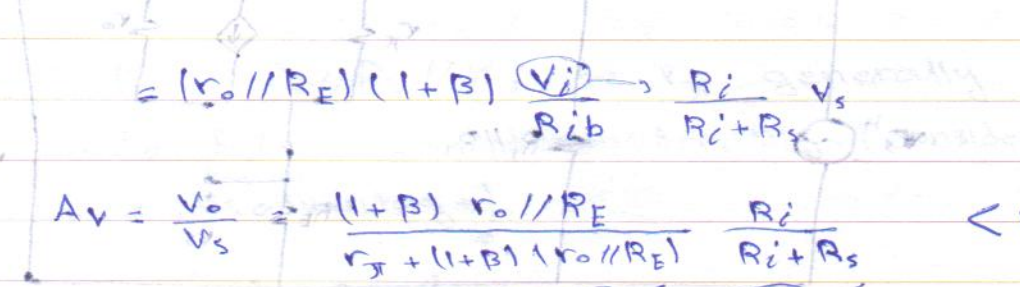
$$V_o = (r_o \parallel R_E) (1+\beta) I_b$$



$$= (r_o \parallel R_E) (1+\beta) \frac{V_i}{R_{ib}} \rightarrow \frac{R_i}{R_i + R_s} V_s$$

$$A_v = \frac{V_o}{V_s} = \frac{(1+\beta) r_o \parallel R_E}{r_{\pi} + (1+\beta) (r_o \parallel R_E)} \frac{R_i}{R_i + R_s} < 1$$


So there is no voltage gain.

$$A_i = \frac{I_o}{I_i} = \frac{r_o}{r_o + R_E} \frac{(1+\beta) I_b}{I_i} = \frac{r_o}{r_o + R_E} (1+\beta) \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{ib}} I_i$$

$$= \frac{r_o}{r_o + R_E} (1+\beta) \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{ib}} \geq 1$$

if $R_E \ll r_o$ & $R_1 \parallel R_2 \gg R_{ib}$ then

$$A_i = 1+\beta$$

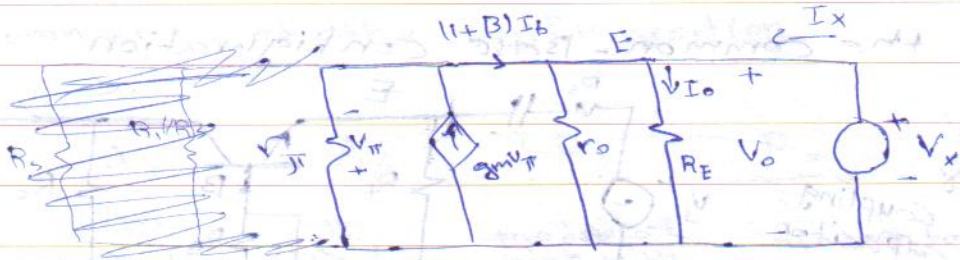

* we took out $R_1 // R_2$ because we killed the indep. voltage source & we got short ckt.

* output resistance

Case 1 when $R_s = 0$, $V_{\pi} = -V_x$

$$-I_x + \frac{V_x}{R_E} + \frac{V_x}{r_o} + g_m V_x + \frac{V_x}{r_{\pi}} = 0$$


$$R_o = \frac{V_x}{I_x} \quad \frac{1}{R_o} = \frac{I_x}{V_x}$$

$$\frac{I_x}{V_x} = \frac{1}{R_E} + \frac{1}{r_o} + \left(g_m + \frac{1}{r_{\pi}} \right) \rightarrow \frac{1 + g_m r_{\pi}}{r_{\pi}} \downarrow \frac{1 + \beta}{r_{\pi}}$$

$$R_o = \frac{V_x}{I_x} = R_E // r_o // \frac{r_{\pi}}{1 + \beta} \approx \frac{r_{\pi}}{1 + \beta}$$

* considered very small. (10's of Ω)

Case 2 $R_s \neq 0$

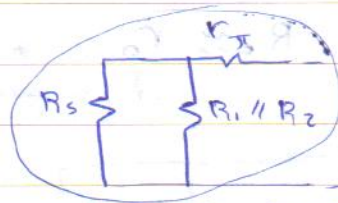

$$r_{\pi} + R_s // R_1 // R_2$$



$R_s < R_1 // R_2$

$$R_o = R_E // r_o // \frac{r_{\pi} + R_s // R_1 // R_2}{1 + \beta}$$

$$\approx \frac{r_{\pi} + R_s}{1 + \beta} \quad \text{remember this}$$



* the common-base configuration

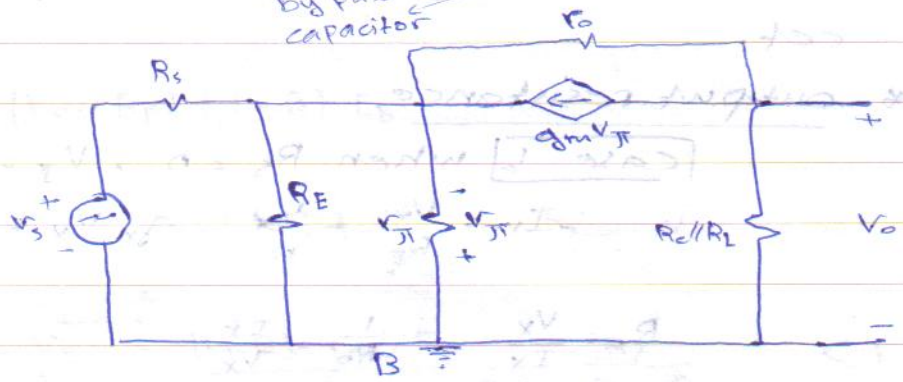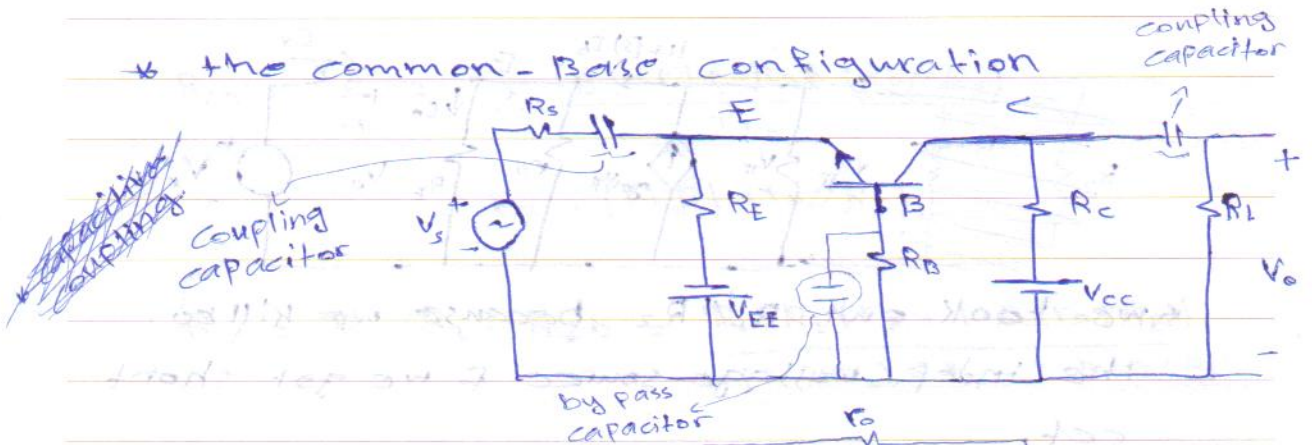

* it can be shown that

$$A_v = g_m R_C // R_L$$

$$A_i = \frac{\beta}{1 + \beta} = \alpha < 1 \quad * \text{no current gain}$$

$$R_{i_{in}} \approx \frac{r_{\pi}}{1 + \beta} \quad * \text{considered very small.}$$

$$R_{o_{out}} \approx r_o \quad * \text{considered very high.}$$

where is r_o ??

* study the book.

* summary of the configuration


	A_v	A_i	R_i	R_o
CE	yes > 1	yes > 1	moderate high with R_E	moderate
CE CC	No < 1	yes > 1	high	very small
CB	yes > 1	No < 1	very small	high

* Voltage & current buffers

* since the ~~CE~~^{CC} amp. has very high input resistance & very low output resistance & $A_v = 1$, it acts as a voltage buffer.


* " " " " CB " " " " has ~~low~~^{high} input resistance & very high output resistance & $A_i = 1$ " " " " as a current buffer.

EX: Consider the following ckt.

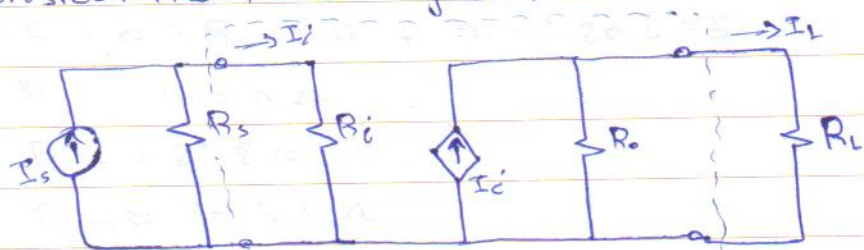

determine conditions to get max. I_L current

ex: 6.7 (P407)

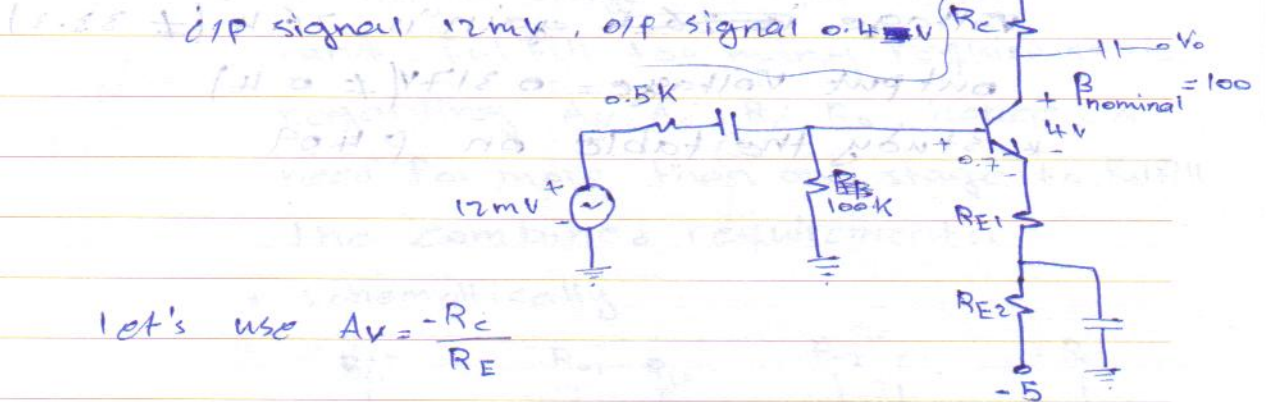

let's use $A_v = -\frac{R_c}{R_E}$

$$|A_v| = \frac{R_c}{R_E} = \frac{0.4}{0.012} = 33.3$$

since $\frac{R_c}{R_E}$ is a not very accurate gain
(~~grade~~ cradel) choose $\frac{R_c}{R_E} = 40$

let $I_E = I_C = 0.2 \text{ mA} \Rightarrow I_B = \frac{0.2}{101} \text{ mA}$

$$100 \times \frac{0.2}{101} + 0.7 + 0.2 (R_{E1} + R_{E2}) = 5$$

$$\Rightarrow R_{E1} + R_{E2} = 20.5 \text{ k}\Omega$$

$$A_v = 40 = \frac{R_c}{R_{E1}}$$

$$-5 + 0.2 R_c + 4 + 0.2 \times 20.5 = 5$$

$$R_c = 4.5 \text{ k}\Omega$$

$$R_{E1} = 238 \Omega$$


$$R_{E2} = 20.3 \text{ k}\Omega$$

choose standard values \Rightarrow 4.5 \rightarrow 10k
238 \rightarrow 240 Ω
20.3 \rightarrow 20k

* based on these values / the measured output voltage is ~~26.4~~ gain is 26.4 ($\neq 33.3$)

output voltage = 0.317V ($\neq 0.4$)

* study the table on p 409

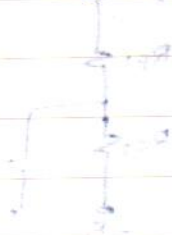

$R_1 = 100 \Omega$
 $R_2 = 100 \Omega$

$R_3 = 100 \Omega$
 $R_4 = 100 \Omega$

input voltage is a not very accurate
output voltage is a not very accurate

Let's find the output voltage

$$V_{out} = \left(\frac{R_2}{R_1 + R_2} \right) \cdot V_{in}$$

$$V_{out} = \left(\frac{100}{100 + 100} \right) \cdot 0.4$$

$$V_{out} = 0.2 \cdot 0.4$$

$$V_{out} = 0.08 \text{ V}$$

$$V_{out} = 0.08 \text{ V}$$

$$V_{out} = 0.08 \text{ V}$$

$$V_{out} = 0.08 \text{ V}$$


Let's find the output voltage

Let's find the output voltage

* multistage amplifiers

* a single stage of amplification cant fulfill too many requirements regarding A_v, A_i, R_i, R_o , hence, a need for more than one stage to fulfill the combined requirements.

* schematically

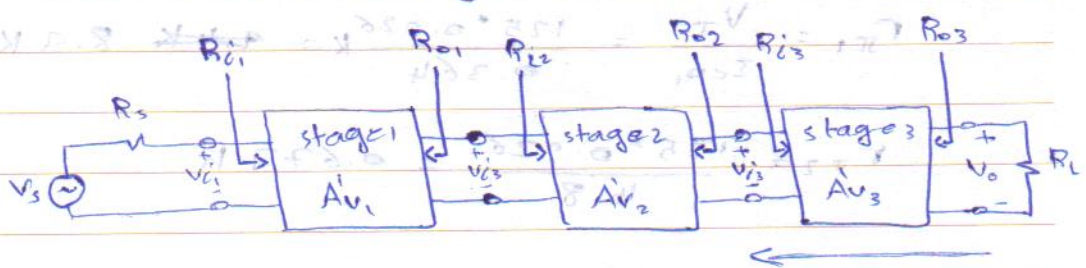

* electronics 2.


$$V_o = \frac{R_L}{R_L + R_{o3}} A_{v3} \underbrace{\frac{V_{i3}}{R_{i3}}}_{\text{* amplifiers.}}$$

* where

$$A_{v_i} \text{ is defined as } \frac{V_{o_i}}{V_{i_i}} \text{ \& not as } \frac{V_{o_i}}{V_{s_i}}$$

ghazali

Past

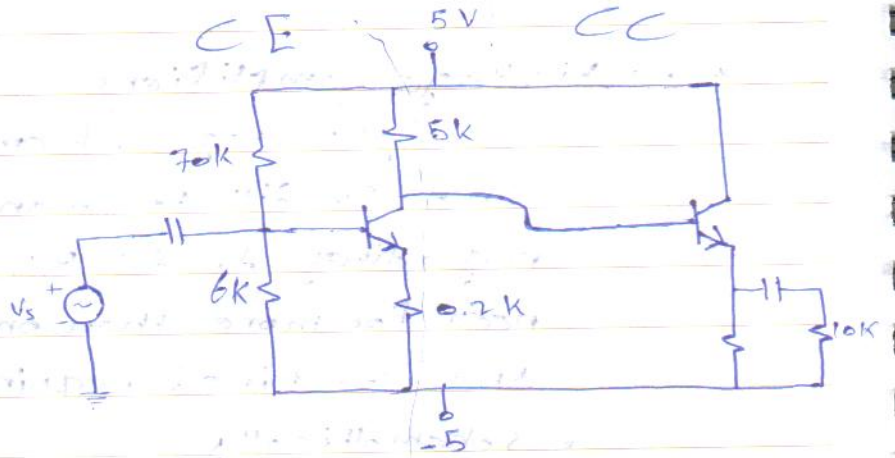


$$r_{T1} = \frac{V_{T1}}{I_{CQ1}} = \frac{125 \cdot 0.026}{0.364} \text{ k} = \cancel{4.4} \text{ k} \approx 8.9 \text{ k}$$

$$r_{T2} = \frac{125 \cdot 0.026}{4.8} = 0.677 \text{ k}$$

$$V_{CE} = \frac{P_{out}}{P_{in}}$$

$$V_{CE} = \frac{P_{out}}{P_{in}}$$



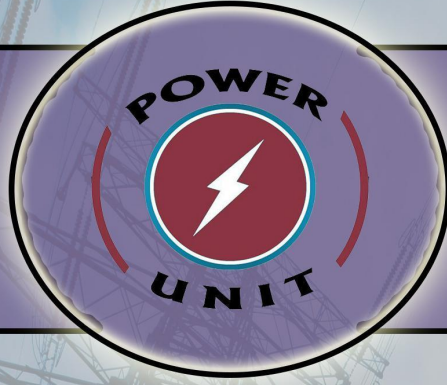

Amplifiers


NoteBook

By: Ahmad Ghzawi
Dr. Omar Ghzawi


بأفكارنا نبدع

4th & 5th Weeks

* The Darlington Pair

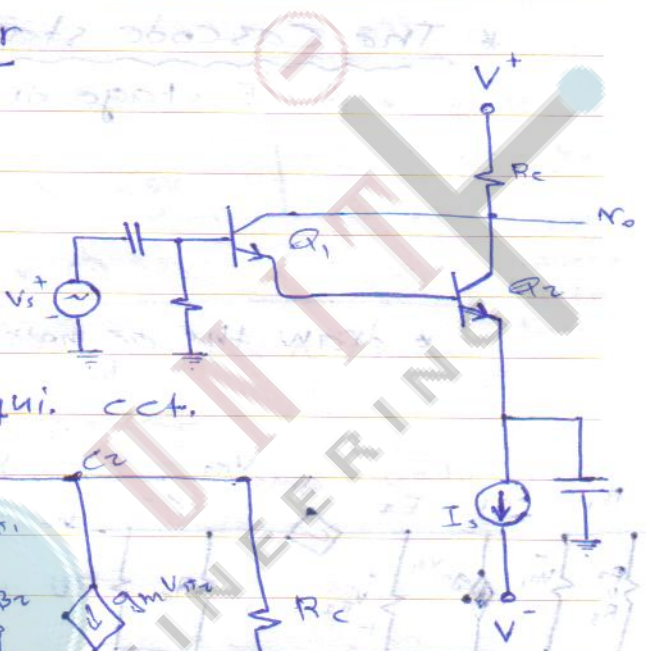

* draw the ac equi. ckt.

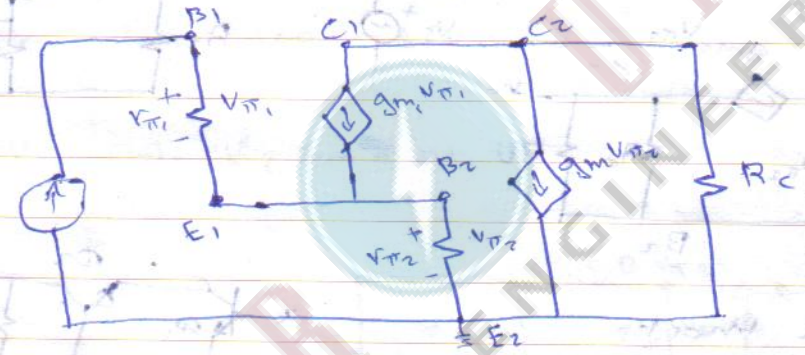

* & study the gains & resistances


$$A_v \approx \beta_1 \beta_2$$

$$R_i \approx 2\beta_1 \beta_2 r_e$$

* The Cascode stage Amplifier


* A CE stage driving a CB stage

* draw the ac model

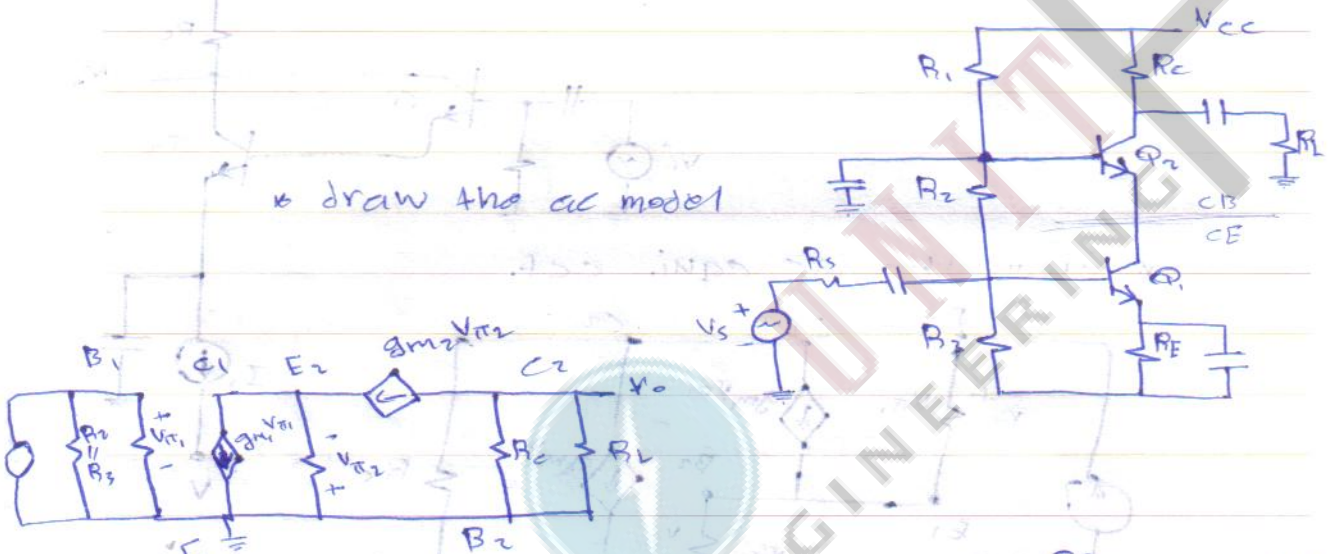

* find that

$$A_v = -g_{m1}(R_c // R_L)$$

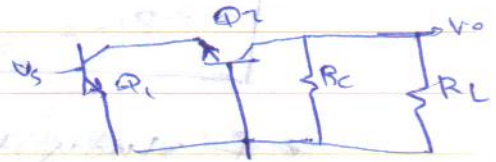


* exo past papers, for the first exam

$$-9 + 830 I_B + 0.7 = 0$$

$$I_B = 10 \mu A$$


$$I_C = 2.5 \text{ mA}$$

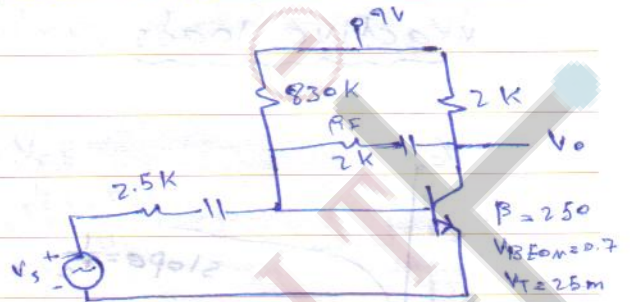

$$r_{\pi} = \frac{V_T}{I_B} = \frac{\beta V_T}{I_C} = \frac{25 \times 25 \text{ mV}}{2.5 \text{ mA}} = 2.5 \text{ k}\Omega$$

$$g_m = \frac{I_C}{V_T} = 100 \text{ mA/V} \quad \beta = r_{\pi} g_m \Rightarrow g_m = 100 \text{ mA/V}$$


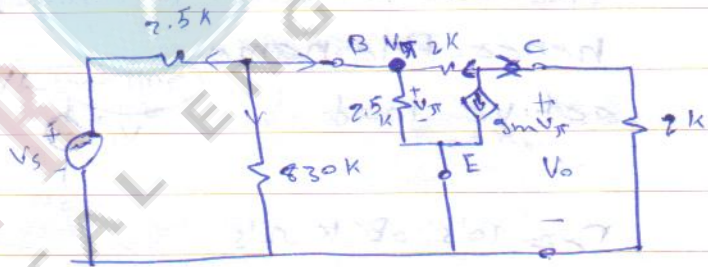
$$V_{CE} = 9 - 2\text{k} \cdot 2.5 \text{ mA} = 4 \text{ V}$$



$$\frac{V_o}{R_L} + g_m V_{\pi} + \frac{V_o - V_{\pi}}{R_F} = 0$$


$$\frac{V_{\pi} - V_{S\pi}}{2.5 \text{ k}} + \frac{V_{\pi}}{830 \text{ k}} + \frac{V_{\pi}}{2.5 \text{ k}} + \frac{V_{\pi} - V_o}{R_F} = 0$$

* active loads

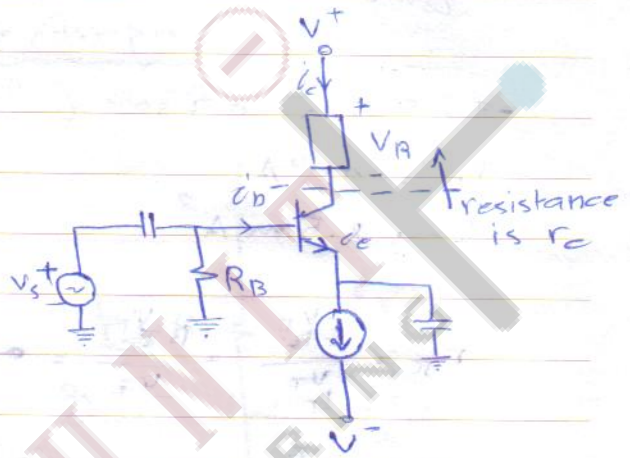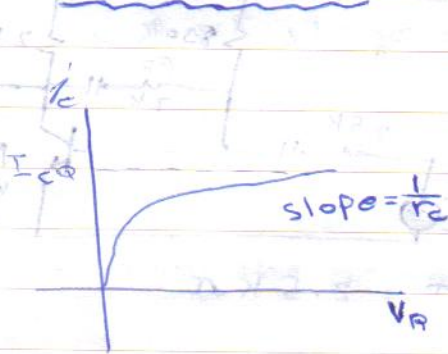

* the active load device (transistor) implements the load (collector resistance) hence the name active load

$r_c \approx 10$'s of $k\Omega$'s

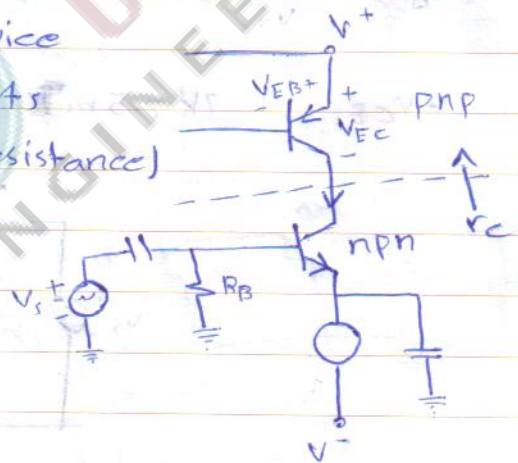

* it can be shown that $A_v = -g_m r_c$



* Consider the following ckt:

dc analysis

$$V^+ - V^- = R_C I_{CQ} + V_{CE} + (R_{E1} + R_{E2}) \left(\frac{1+B}{B} \right) I_{CQ}$$

$$I_{CQ} = - \frac{V_{CE}}{R_C + \frac{1+B}{B} (R_{E1} + R_{E2})} + \frac{V^+ - V^-}{R_C + \frac{1+B}{B} (R_{E1} + R_{E2})}$$

$$y = \text{---} \text{---} \text{---}$$

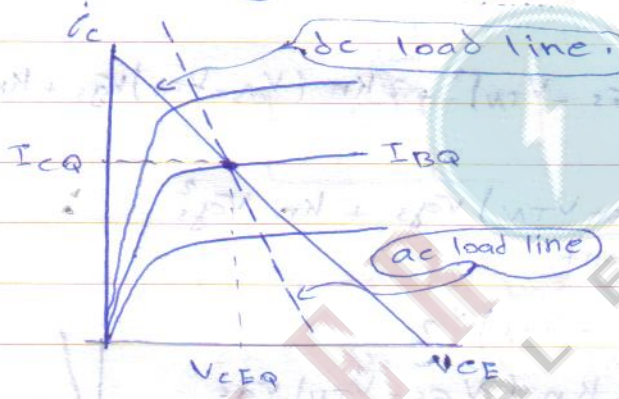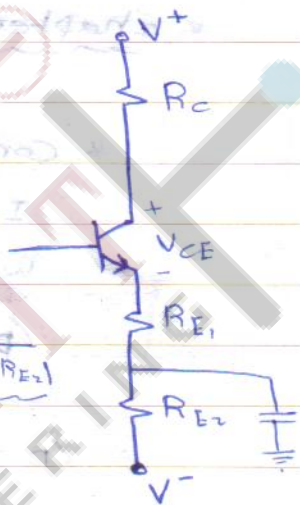

ac analysis

$$R_C i_c + V_{CE} + R_{E1} i_e = 0$$

& let $i_e = i_c$

$$i_c = - \frac{1}{R_C + R_{E1}} V_{CE}$$

Handwritten notes at the bottom of the page, including "AC load line" and "DC load line".

* chapter 4 : MOSFET Amplifiers.


* Consider the following cct.

$$I_D = k_n (V_{GS} - V_{TN})^2$$

with input signal v_i

$$i_D = k_n (V_{GS} - V_{TN})^2$$
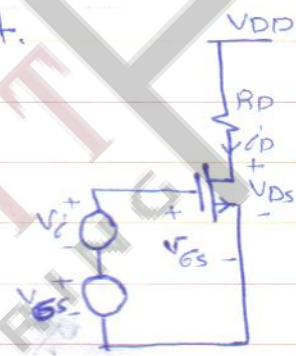
$$i_D = k_n (V_{GS} + \underbrace{v_i}_{=v_{gs}} - V_{TN})^2$$




$$I_{DQ} + i_D = k_n (V_{GS} - V_{TN})^2 + 2k_n (V_{GS} - V_{TN})v_{gs} + k_n v_{gs}^2$$

$$i_D = \underbrace{2k_n (V_{GS} - V_{TN})}_{\text{constant}} v_{gs} + k_n v_{gs}^2$$

* if $v_{gs} \ll (V_{GS} - V_{TN}) \times 2$
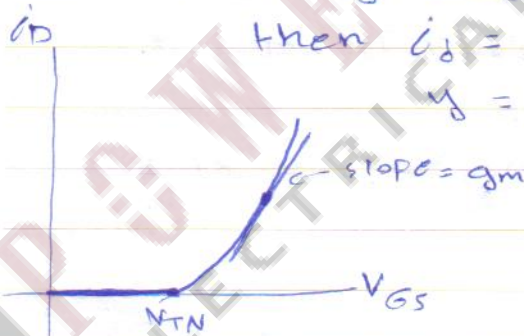
$$\text{then } i_D = 2k_n (V_{GS} - V_{TN}) v_{gs}$$





* define $g_m = \frac{i_D}{v_{gs}} = 2k_n (V_{GS} - V_{TN})$

* $g_m = \frac{\delta i_D}{\delta V_{GS}} \Big|_{V_{GSQ}}$

* it can be shown that

$$g_m = \sqrt{k_n I_{DQ}}$$

* the model so far is

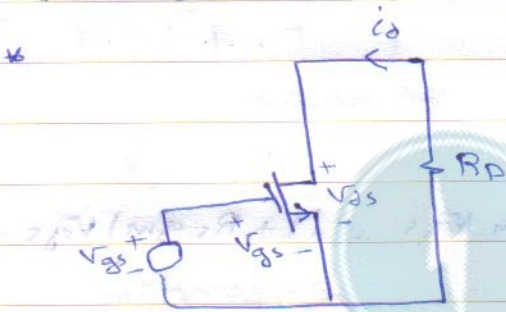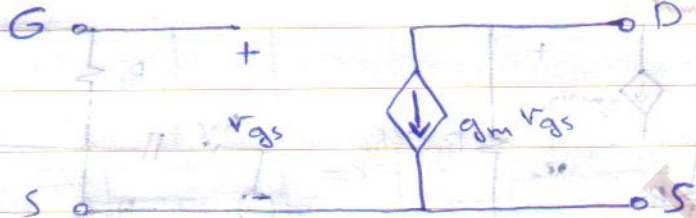


* to improve the model use


$$i_D = K_n (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$

$$\text{define } r_o = \left. \frac{\partial i_D}{\partial V_{DS}} \right|_{V_{GSQ}}$$

$$r_o = \frac{1}{\lambda I_{DQ}}$$

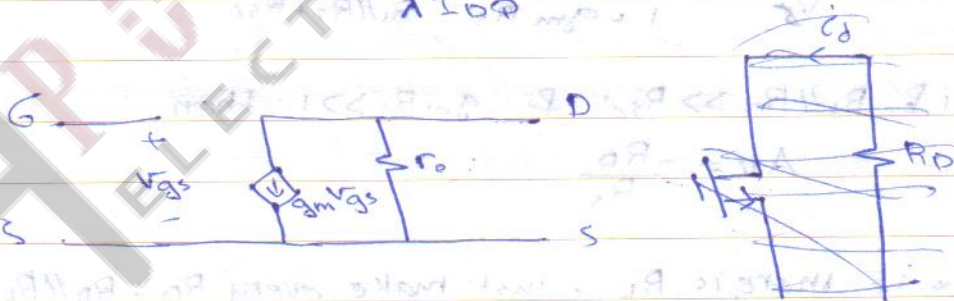

* the common source amplifier

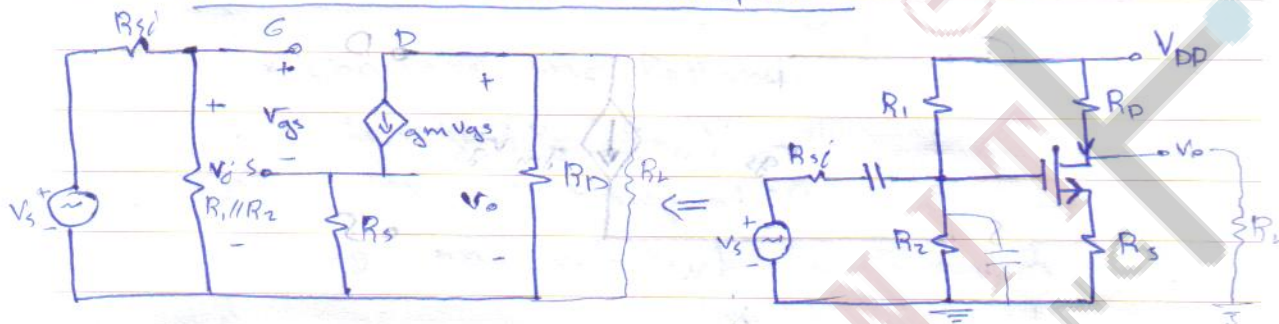

$$v_i' = \frac{R_1 // R_2}{R_1 // R_2 + R_{s1}} v_s$$

$$= v_{gs} + R_s g_m v_{gs} = (1 + R_s g_m) v_{gs}$$

$$v_{gs} = \frac{1}{1 + g_m R_s} v_i'$$

$$v_o = -g_m v_{gs} R_D$$

$$= -g_m R_D \frac{1}{1 + g_m R_s} v_i' = \frac{-g_m R_D}{1 + g_m R_s} \frac{R_1 // R_2}{R_1 // R_2 + R_{s1}} v_s$$

$$A_v = \frac{v_o}{v_s} = \frac{-g_m R_D}{1 + g_m R_s} \frac{R_1 // R_2}{R_1 // R_2 + R_{s1}}$$


* if $R_1 // R_2 \gg R_{s1}$ & $g_m R_s \gg 1$ then

$$A_v = \frac{-R_D}{R_s}$$

* if there is R_L , just make every $R_D = R_D // R_L$

* to increase the gain, we use by pass cap.
& it won't affect the dc analysis.

* the common drain amplifier

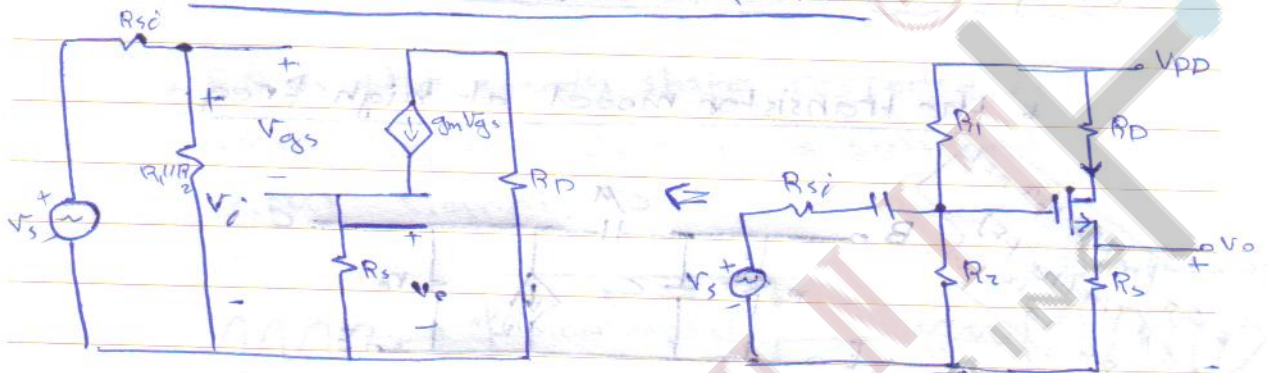

$$V_i = V_{gs} + g_m V_{gs} R_s = (1 + g_m R_s) V_{gs}$$

$$V_{gs} = \frac{1}{1 + g_m R_s} V_i \quad V_i = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{sc}} V_s$$

$$V_o = g_m V_{gs} R_s = \frac{g_m R_s}{1 + g_m R_s} V_i$$

$$\text{So } A_v = \frac{V_o}{V_s} = \frac{g_m R_s}{1 + g_m R_s} \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{sc}} < 1$$


* no voltage gain

* if \$R_L \Rightarrow R_s = R_s \parallel R_L\$


* chapter 7: Frequency response of amplifiers

* the transistor model at high freq.

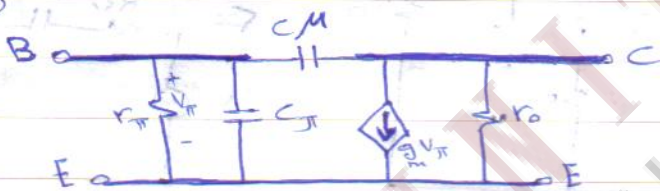* C_{π} (in the 10s pF)
 * C_M (in the pF)
 PF = 10^{-12}



* NPN BJT HF model.

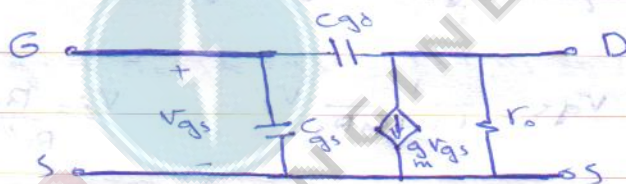


* n-MOS HF model.

* the behavior of the transistor depends on the freq. of the input signal.

* the behavior of the amplifier cct. also depends on the external capacitances (coupling & by pass capacitors)


* Definition of Frequency response (FR)

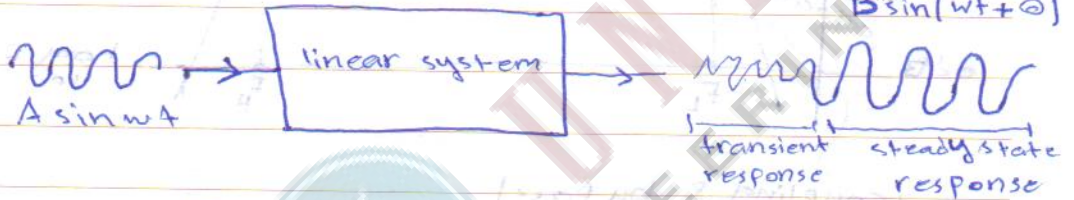* FR is the steady state response of a linear system due to a sinusoidal input signal.



* gain = $\frac{B}{A}$, phase shift = ϕ

197 * Bode plots

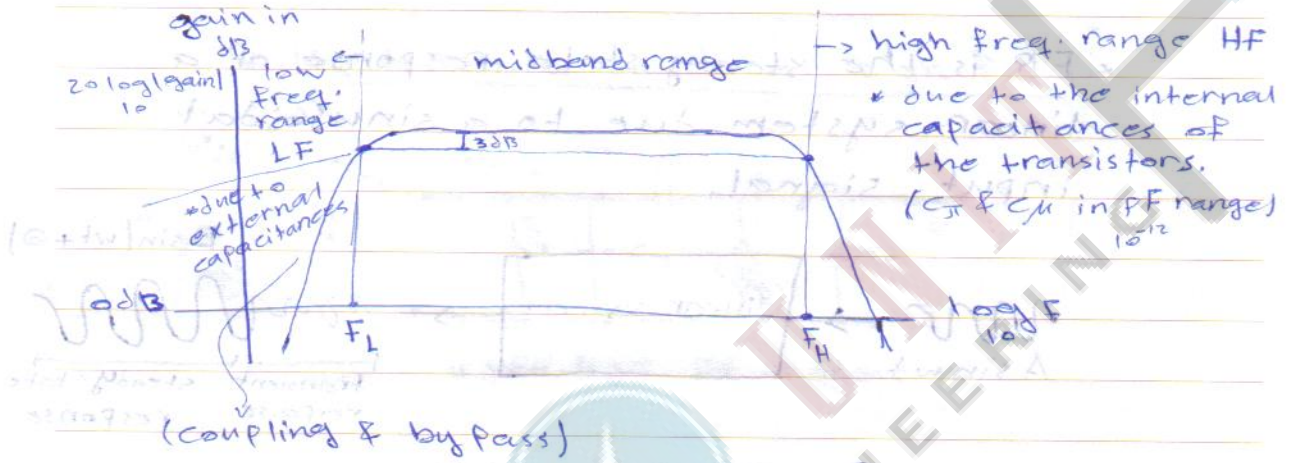

POWER ELECTRICAL ENGINEERING



Electronics II

NoteBook


Dr. Omar Ghzawi
By: Ahmad Ghzawi

بِأفكارنا نبدع

- Op-Amp circuits (ccts involving op-amps)
 - proved using the ideal model.

- the inverting amplifier
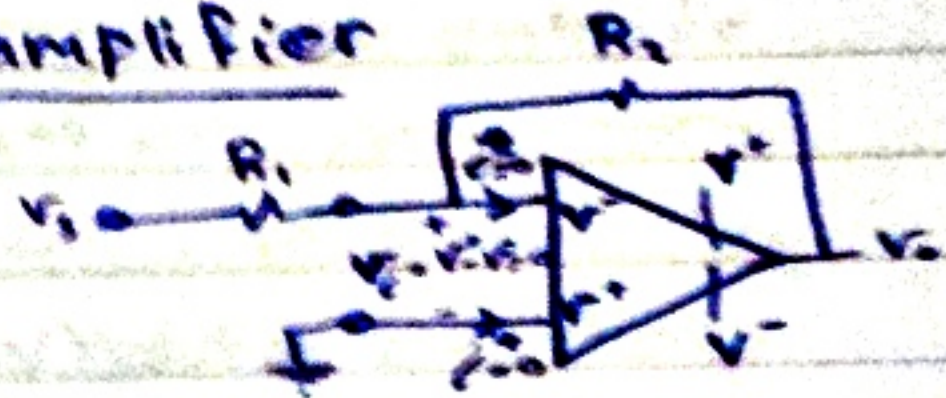
$$\frac{v_1 - v^+}{R_1} = i^- + \frac{v^- - v_o}{R_2}$$




also $v^+ = v^- = 0$

$$v^+ = 0 \Rightarrow v^- = 0 \text{ V} \quad \& \quad i^- = 0, \quad i^+ = 0$$

hence $\frac{v_1}{R_1} = -\frac{v_o}{R_2}$


generally $\frac{v_o}{v_1} = -\frac{R_2}{R_1}$

• the (-) means

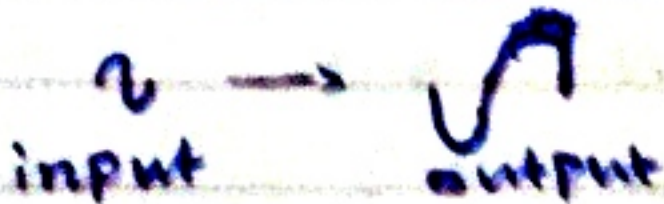

• the input resistance of this cct. is R_1 (considered a disadvantage).

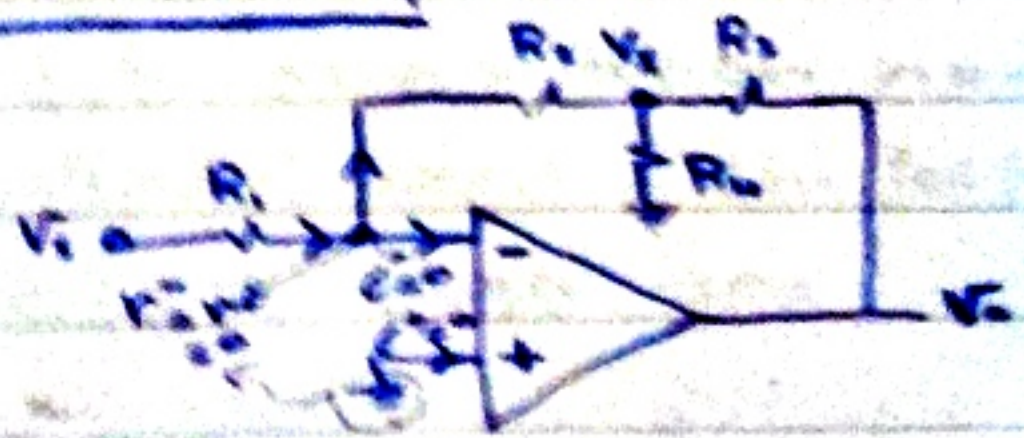• to get a high input resistance ^(R_1) for the inverting amp. together with high gain yet using a moderate R_2 resistance we use the following cct. the T-network amp.



$$v^+ = v^- = 0$$

$$v^+ = v^-$$



amplifiers

$$\frac{V_s - 0}{R_1} = \frac{0 - V_x}{R_2} \Rightarrow \frac{V_x}{V_s} = -\frac{R_2}{R_1}$$

$$-\left(\frac{0 - V_x}{R_2}\right) + \frac{V_x}{R_4} + \frac{V_x - V_o}{R_3} = 0 \Rightarrow \frac{V_o}{V_x} = R_3 \left[\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right]$$

$$= 1 + \frac{R_3}{R_2} + \frac{R_3}{R_4}$$

So $\frac{V_o}{V_s} = -\frac{R_2}{R_1} \left[1 + \frac{R_3}{R_2} + \frac{R_3}{R_4} \right]$


- * the input resistance of the amp. = ∞
- * " " of this cct. $\approx R_1$

the non-inverting amplifier

$$0 - V_s = \frac{V_s - V_o}{R_2} + 0$$

$$\frac{V_s}{R_2} + \frac{V_s}{R_1} = \frac{V_o}{R_2}$$
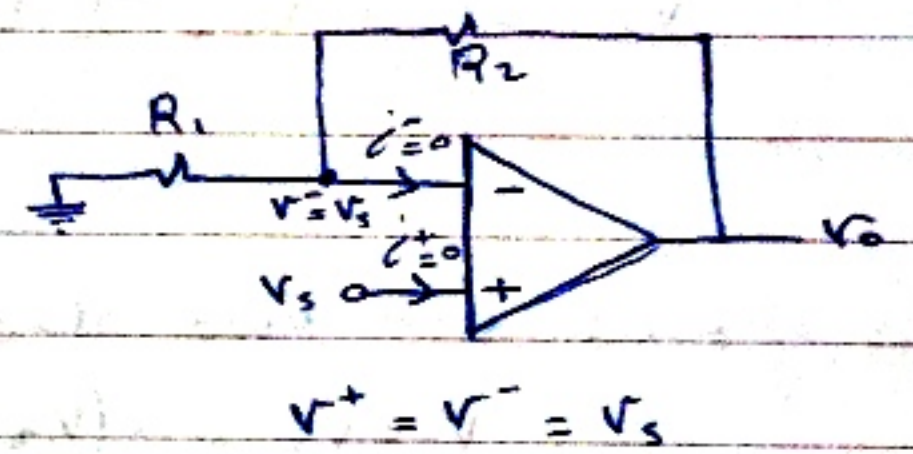
$$\frac{V_o}{V_s} = \left(1 + \frac{R_2}{R_1} \right) > 1$$




- * it can be shown that the input resistance for this cct. is very large, & the output resistance is very small.


* prove these facts.

* voltage buffers: the gain is 1 if $R_1 = \infty$ or $R_2 = 0$ or $R_1 = \infty$ & $R_2 = 0$


* determine R_i & R_o P_o

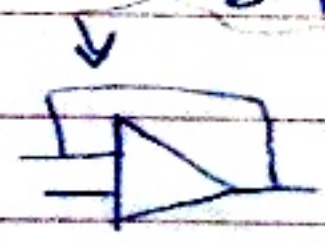

* the model

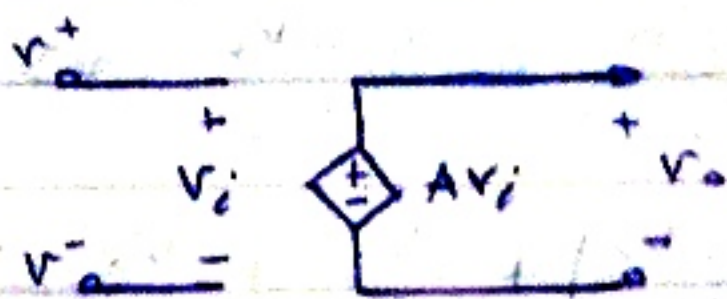


* the summing amplifier

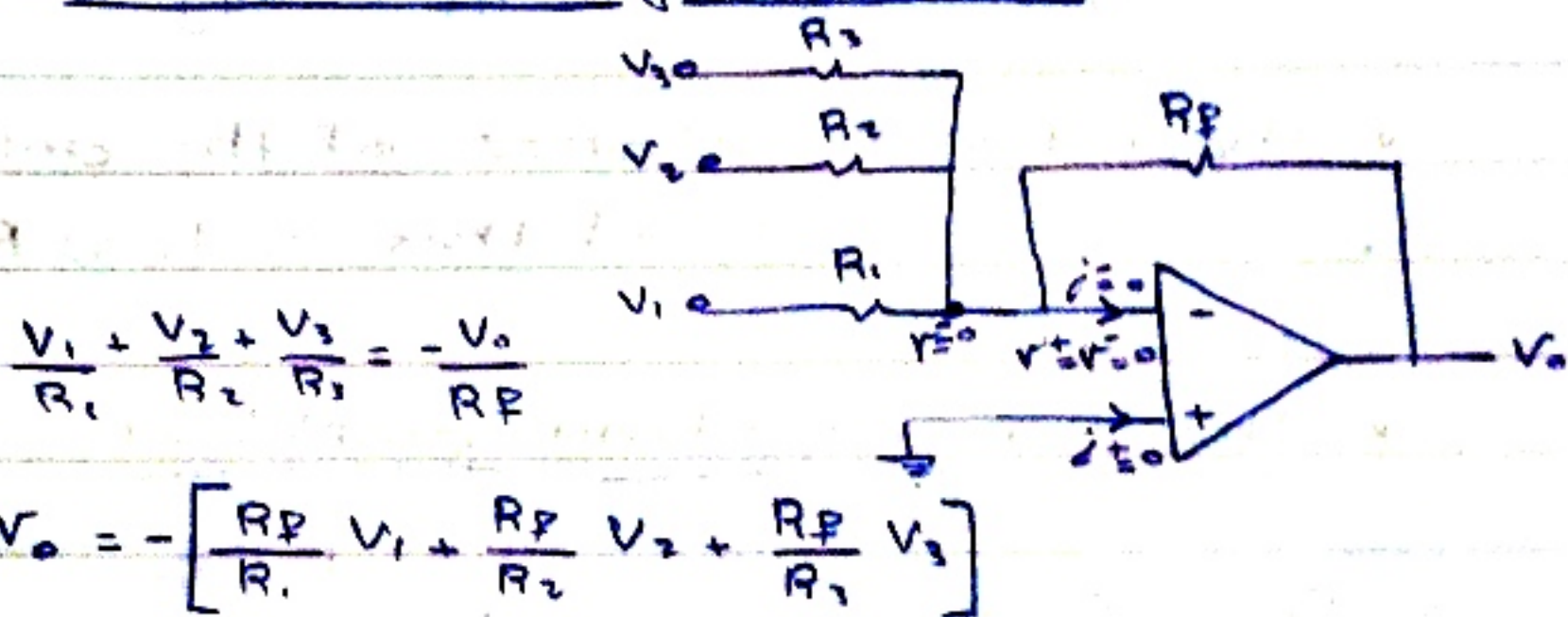


ex: use two op-amps to get $V_1 - V_2$

$$V_1 - V_2 = -(V_2 + (-V_1))$$

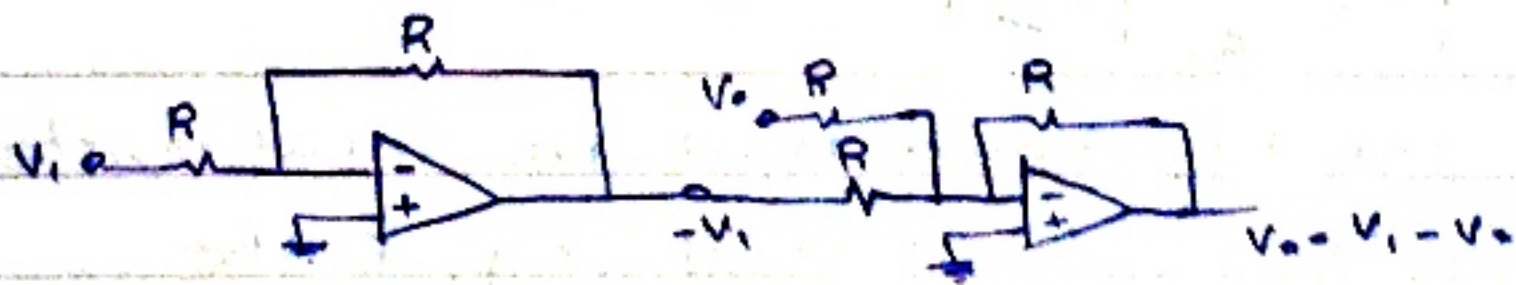

* instead of using two op-amps, we can use a single op-amp resulting in a difference amplifier.

the difference amplifier

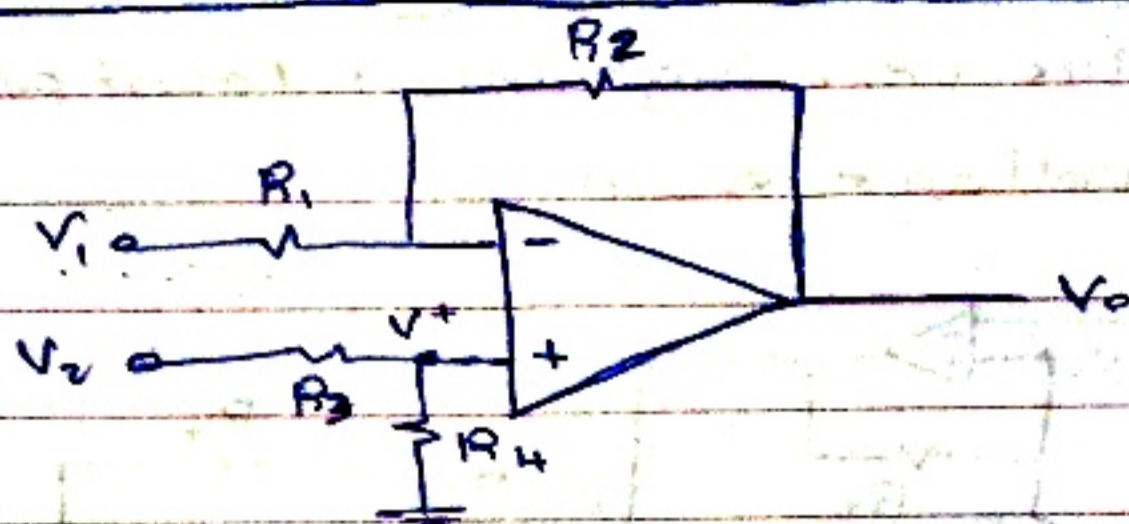

$$V^+ = \frac{R_4}{R_4 + R_3} V_2$$

using superposition

$$\text{let } V_2 = 0$$

$$V_{o1} = \frac{-R_2}{R_1} V_1$$

(V_o due to V_1)

$$\text{let } V_1 = 0$$

$$V_{o2} = \left(1 + \frac{R_2}{R_1}\right) V^+ \\ = \left(\frac{R_1 + R_2}{R_1}\right) \left(\frac{R_4}{R_4 + R_3}\right) V_2$$

$$V_o = V_{o2} + V_{o1} = \frac{R_1 + R_2}{R_1} \frac{R_4}{R_4 + R_3} V_2 - \frac{R_2}{R_1} V_1$$

$$\text{if } \frac{R_4}{R_3} = \frac{R_2}{R_1} \Rightarrow V_o = \frac{R_2}{R_1} (V_2 - V_1) = \frac{R_4}{R_3} (V_2 - V_1)$$

if a common noise signal is present, then

$$V_1' = V_1 + V_n \quad \& \quad V_2' = V_2 + V_n$$


$$\text{hence } V_o = \frac{R_2}{R_1} (V_2' - V_1') = \frac{R_2}{R_1} (V_2 + V_n - V_1 - V_n) \\ = \frac{R_2}{R_1} (V_2 - V_1)$$

i.e. the common mode noise is cancelled out.

it can be shown that the input resistance of this amp is approx $2R_1$ (with justification)

* the instrumentation amp. (IA)

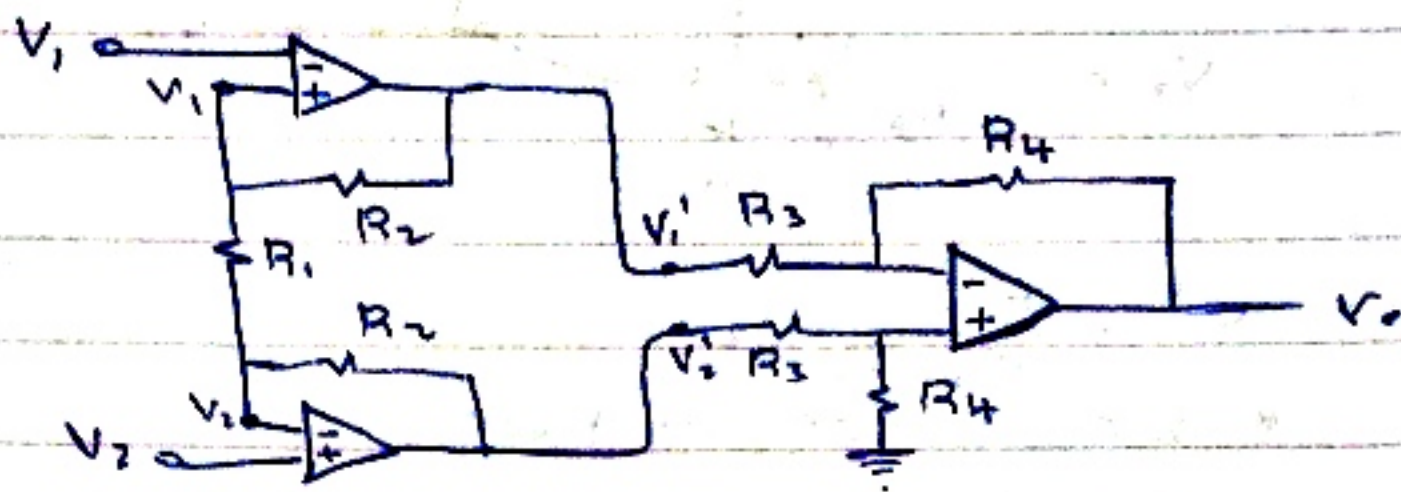* IA has very high input resistance & high voltage gain.



$$V_0 = \frac{R_4}{R_3} (V_2' - V_1')$$


$$V_2' - V_1' = i_2 (R_2 + R_1 + R_2) = (R_1 + 2R_2) \frac{|V_2 - V_1|}{R_1}$$

$$V_0 = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) (V_2 - V_1)$$

* we change R_1 to --- (gain)

13-8-2014
Wednesday
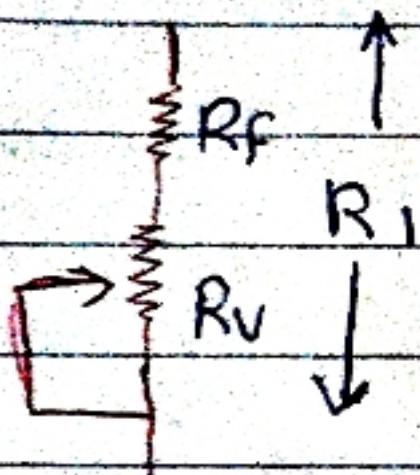
$$V_o = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) (V_2 - V_1)$$



Example 30 gain between ~~15~~ - 805
lets $\frac{R_4}{R_3} = 5$, $R_v = 50 \text{ k}\Omega$.

$$\frac{V_o}{(V_2 - V_1)} = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right)$$

$$805 = 5 \left(1 + \frac{2R_2}{R_f} \right)$$

$$80R_f = R_2 \quad \text{--- (1)}$$


$$15 = 5 \left(1 + \frac{2R_2}{50 + R_f} \right)$$

$$50 + R_f = R_2 \quad \text{--- (2)}$$

$$\text{So } R_f = \frac{50}{79} \text{ k}\Omega \quad \& \quad R_2 = 80 \left(\frac{50}{79} \right) \text{ k}\Omega \\ = 633 \text{ k}\Omega \quad = 50.6 \text{ k}\Omega$$

13-8-2014
Wednesday

Integrating circuit.

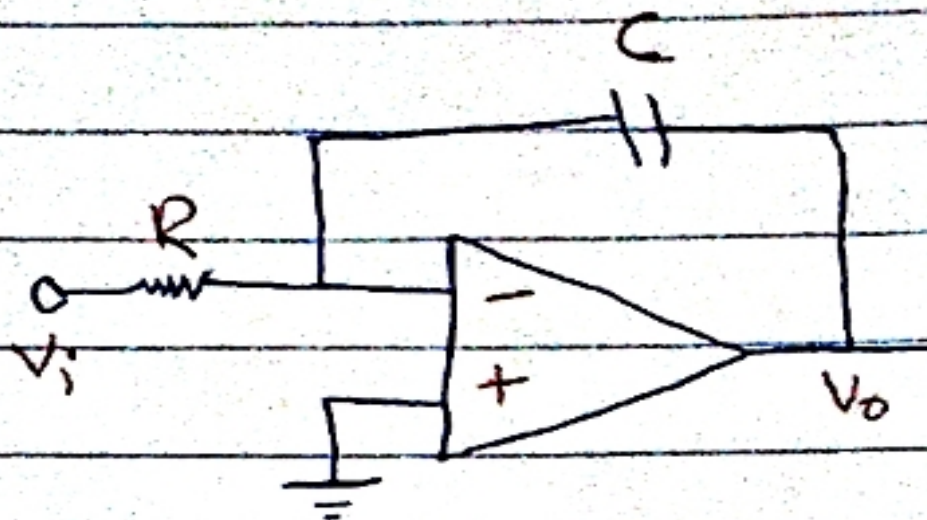


$$\frac{V_o}{V_i(s)} = \frac{-X_c}{R} = \frac{-Z_2}{Z_1} = \frac{-1}{sC} \cdot \frac{1}{R}$$

$$V_o(s) = -\frac{1}{RC} \frac{1}{s} V_i(s)$$

$$V_o(t) = \frac{1}{RC} \int V_i(t) dt$$

Basic Differentiation Circuit

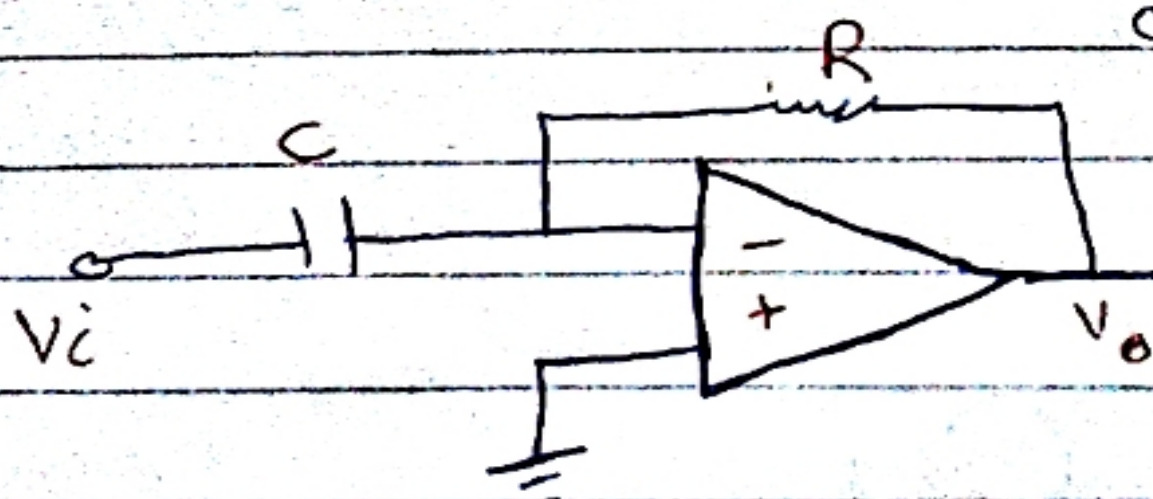

يمكن استخدام مكثف بدل من المقاومة Capacitor

ولكن غير جيد استخدامه لأنه

١- تضيق -٢- سعة عالية

٣- ضيق كبير

لذلك يتم تجنبه بل يمكن

R & C

$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)} = \frac{-R}{sC}$$

Wednesday
13-8-2014


PAGE: _____
DATE: _____

$$= -RCs$$


$$V_o(s) = -RCs V_i(s)$$

$$V_o(t) = -RC \frac{dV_i(t)}{dt}$$

Precision Rectifier

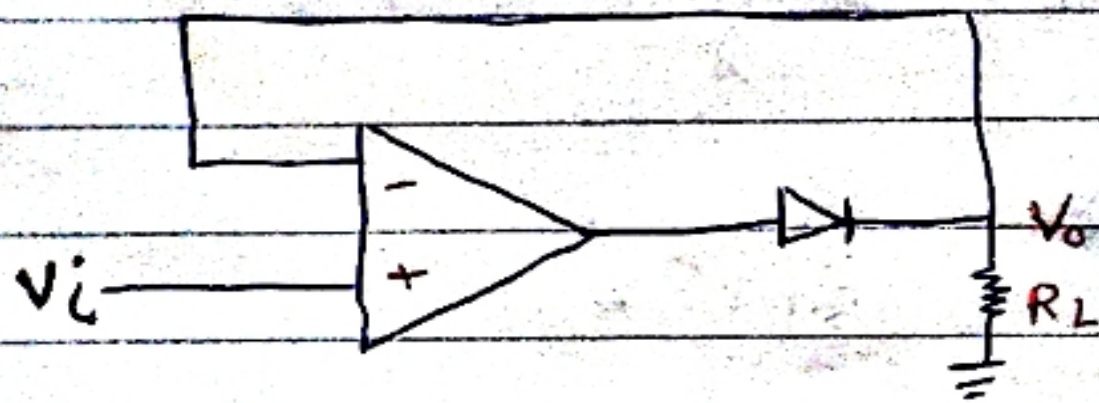

السؤال 1)
Precision Rectifier

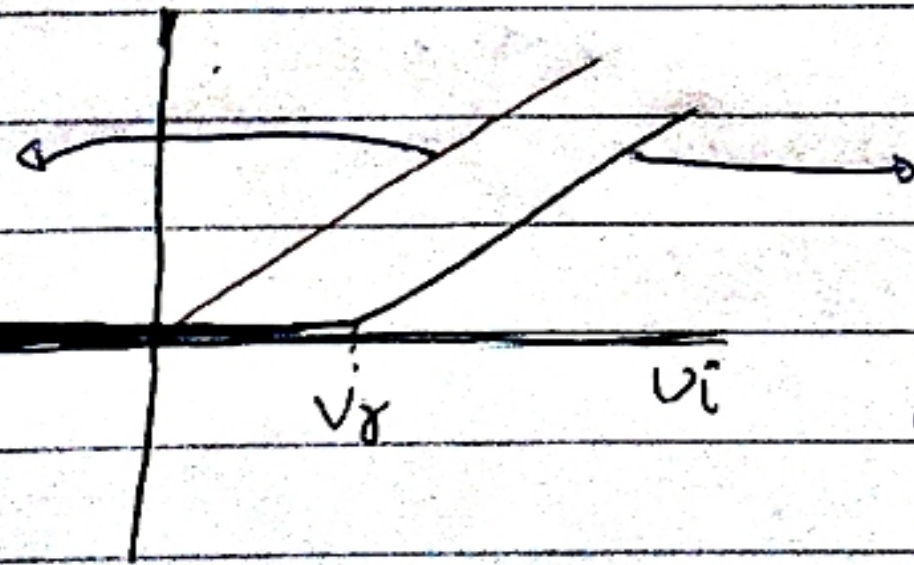

الطريقة الجديدة في
السؤال 1)
Diode

كل ما هو أقل من $V_D = V_i$
طالعاً أقل من V_D


① no waste of V_D and works even when $V_i < V_D$

السؤال 2) Diode - Precision Rectifier
(Power supply)


wednesday
13-8-2014

101 - 105
105

Square wave generator.

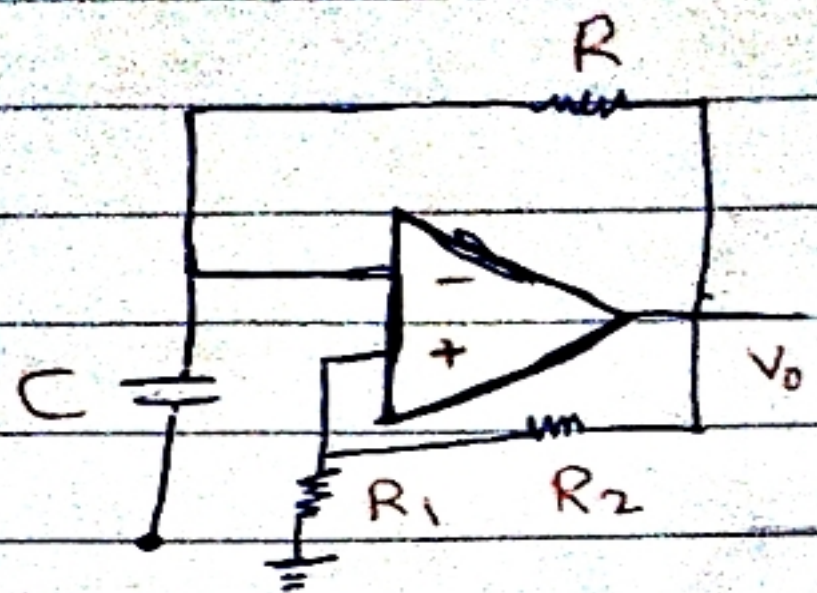

~~there is no V_i~~
there is no V_i
in this op-amp.

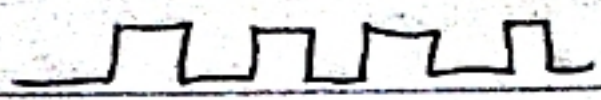generate square - wave 

$$T = 2RC \ln \frac{1+\lambda}{1-\lambda}$$

where $\lambda = \frac{R_1}{R_1 + R_2}$

The End of
The Lec.