

Amplifiers

Revision


BY: Anas Kata



* JFET or field effect Transistor.

FET



BJT

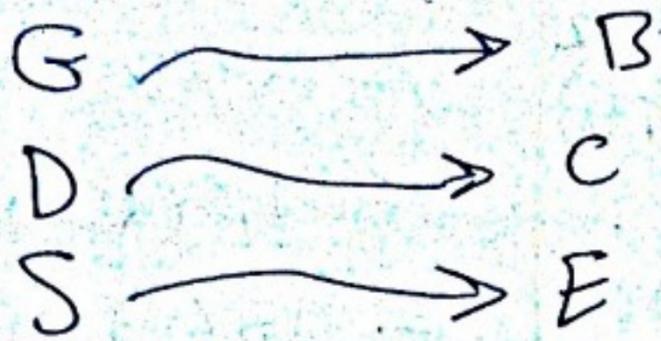

FET

BJT

N-channel

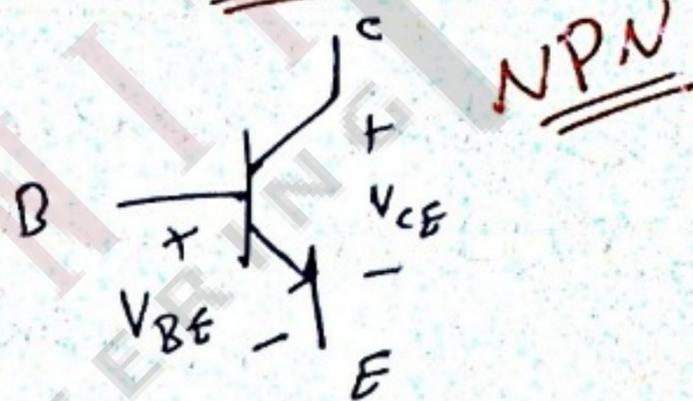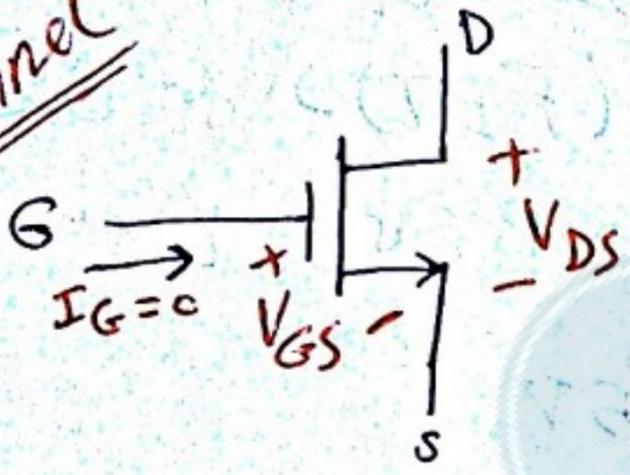

→ control by V_{GS} « Voltage »

→ control by I_B « current »

→ Work as AMP. In saturation mode

→ Work as AMP. In F.W mode

→ condition of sat. mode in FET.

→ condition of F.W mode

$$V_{DSQ} > V_{DSsat}$$

$$V_{CEQ} > V_{CEsat}$$

$$V_{DSsat} = (V_{GSQ} - V_{TN})$$

$$V_{CEsat} = 0,2 \text{ or } = 0,3$$

$V_{TN} \Rightarrow$ constant \rightarrow given

$$I_D = K_n (V_{GSQ} - V_{TN})^2$$

$$I_C = \beta I_B$$

$$g_m = 2 K_n (V_{GSQ} - V_{TN}) = \frac{dI_D}{dV_{GSQ}}$$

$$g_m = \frac{I_{CQ}}{V_T = 0,026}$$

→ $r_{\pi} = \infty \equiv$ open circuit

$$\beta = \frac{0,026}{I_B}$$

$$r_o = [\lambda I_D]^{-1} = 1/\lambda I_D$$

$$r_o = \frac{0,026}{I_C}$$

FET

$$I_G = 0$$

$$I_S = I_D = K_n (V_{GSQ} - V_{TN})^2$$

K_n :- constant \rightarrow given

$\rightarrow A_v = \underline{\text{low}}$ because g_m is low

BJT

$$I_E = I_C + I_B$$

$$= \beta I_B + I_B$$


~~$$= I_B (\beta + 1)$$~~

$$= I_B (\beta + 1)$$

$\rightarrow A_v = \text{High}$ because g_m High

بعض حالات میں FET اور BJT کی مقابله میں، فیلڈ ایف ایف (FET) کی کم گیند اور کم آؤٹ پٹ امپیڈنس کے باعث، اس کی گیند اور آؤٹ پٹ امپیڈنس کم ہوتی ہے۔


Solution of H.W :-

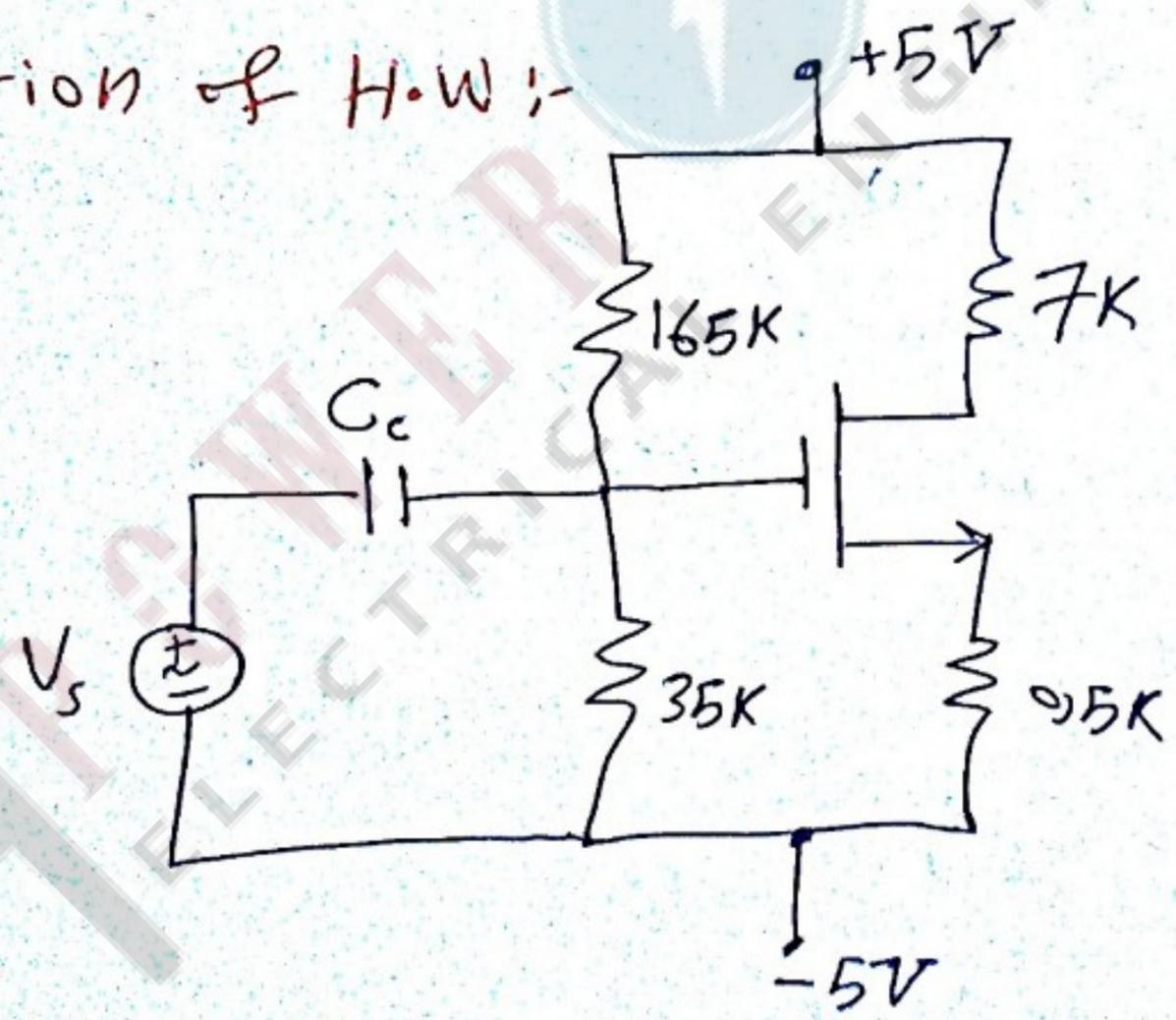

Let $V_{TN} = 0.8V$, $K_n = 1 \text{ mA/V}^2$, $\lambda = 0 \text{ V}^{-1}$
 Find A_v and Draw DC Load Line

ation :-

→ DC Analysis :-

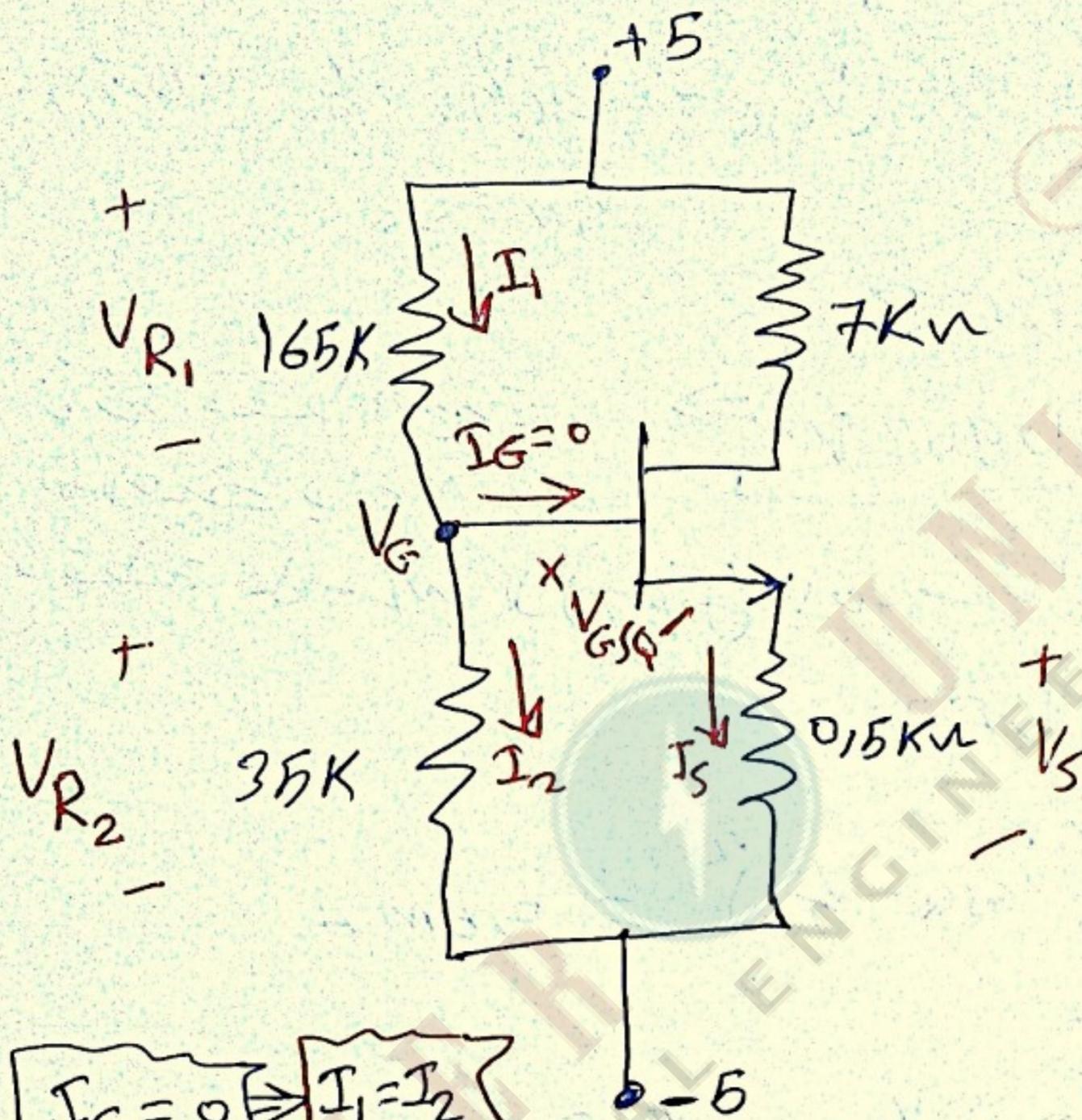

$$I_G = 0 \Rightarrow I_1 = I_2$$

$$V_{R_2} = 10 \times \frac{35 \text{ k}\Omega}{35 \text{ k}\Omega + 165 \text{ k}\Omega} = 1.75$$

انہوں نے (Voltage Division) سے V_{GSQ} کا حساب لگایا ہے ←

Voltage Div. سے V_{GSQ} کا حساب لگایا ہے ←

$$I_1 = I_2 \leftarrow I_G = 0$$

⇒ at input loop :-

$$\text{KVL :- } -V_{R_2} + V_{GSQ} + V_S = 0$$

$$\Rightarrow -1.75 + V_{GSQ} + I_S (0.15 \times 10^3) = 0$$

$$\text{but } I_S = I_D = K_n (V_{GSQ} - V_{TN})^2$$

$$\Rightarrow -1,75 + V_{GSQ} + K_n [V_{GSQ} - V_{TN}]^2 \times (0,5 \mu) = 0$$

$$\Rightarrow -1,75 + V_{GSQ} + 1 \times 10^{-3} (V_{GSQ}^2 - 2V_{GSQ}V_{TN} + V_{TN}^2) \times 0,5 \times 10^{-6} = 0$$

$$V_{TN} = 0,8$$

$$\Rightarrow \begin{cases} V_{GSQ} = 1,5 V \\ V_{GSQ} = -1,903 V \end{cases}$$

نأخذ فقط القيمة
الموجبة لأنه لا يوجد
نقطة عمل لـ (FET) لأنه سوف لا يسكن في (sat.)

نقطة عمل لـ (FET) لأنه سوف لا يسكن في (sat.)

$$\Rightarrow V_{GSQ} = 1,5 V$$

$$\Rightarrow I_{DQ} = K_n (V_{GSQ} - V_{TN})^2 = 0,5 mA$$

at out Loop :-


$$-5 + I_{DQ} R_D + V_{DSQ} + I_S R_S - 5 = 0$$

$$\rightarrow \Rightarrow V_{DSQ} = 6,25 V$$

\Rightarrow DC load line

$$-V_{DD} + I_D R_D + V_{DS} + I_S R_S = 0 \quad \text{but} \quad \boxed{I_S = I_D}$$

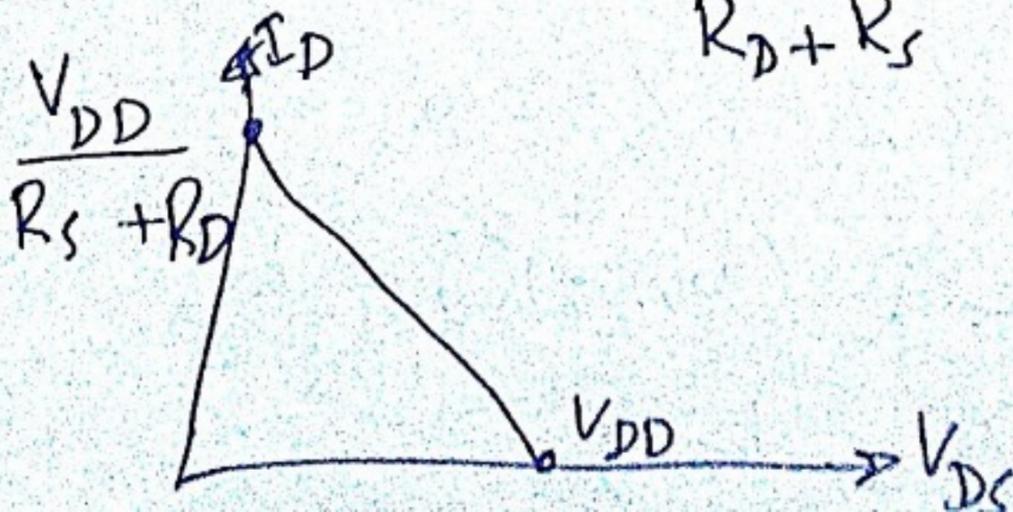
$$\Rightarrow I_D = -\frac{V_{DS}}{R_D + R_S} + \frac{V_{DD}}{R_D + R_S}$$



Frequency Response

It's the study-state output of a linear system due to a sinusoidal input.

→ In general Amplifier circuit has :-

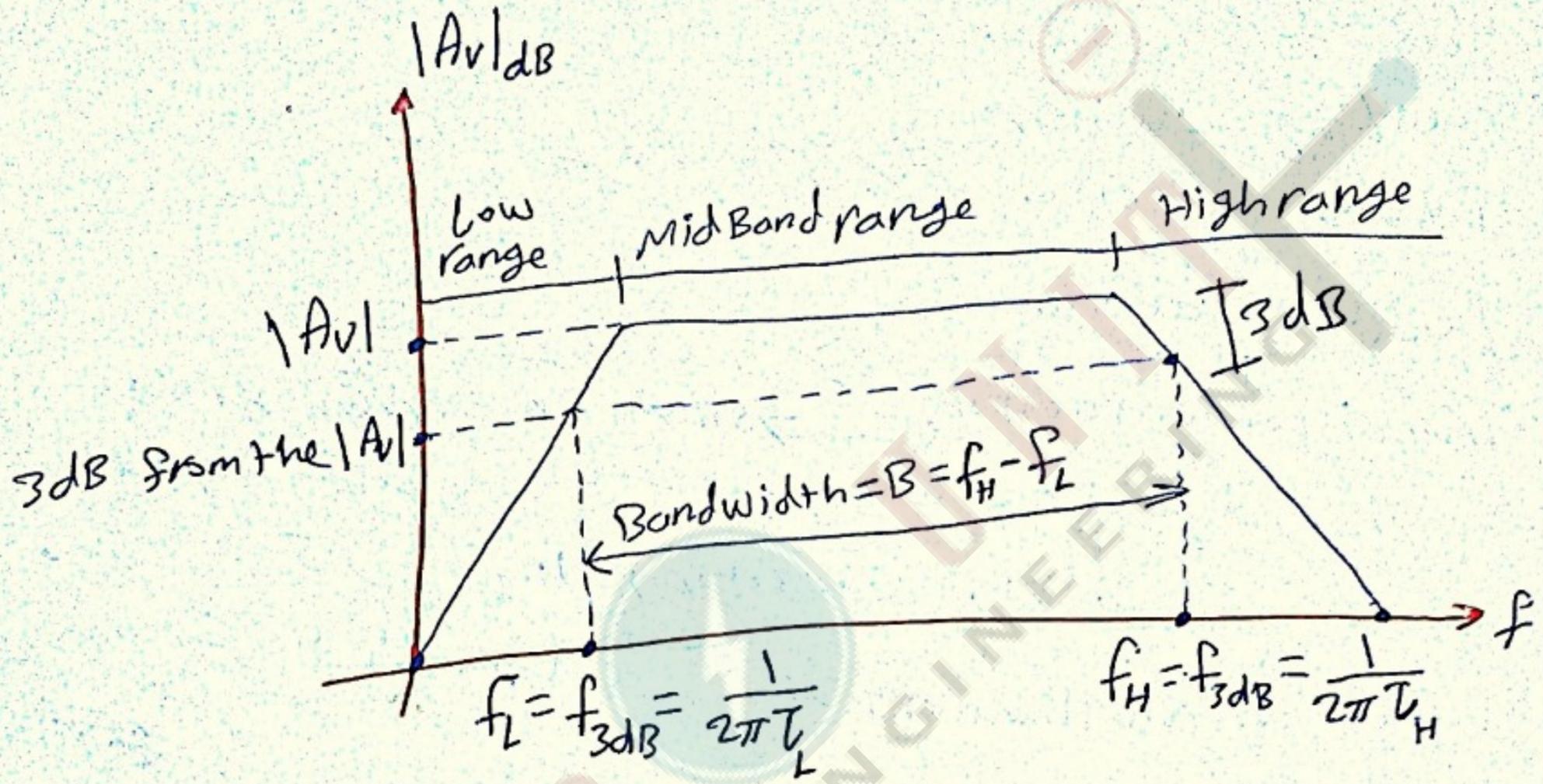

* أنا لست أعرف الطريقة الصحيحة في كتابي ومفتاحي في عن ترتيب الكتب.

وحدة Av بحدود 10³ أو 10⁴ (Unitless)

$$A_v = \frac{V_o}{V_{in}} \text{ Unitless}$$

هناك وحدة أخرى لـ (Av) وهي (dB) وللتحويل من (Unitless) لـ (dB) نستخدم العلاقة

$$dB = 20 \log_{10} (\text{Unitless})$$

$$\text{Unitless} = (10)^{dB/20}$$



$f_{3dB} = \frac{1}{2\pi\tau}$ ← انقطع منها او (f_{3dB}) ← انقطع منها او (T) كمان

* Type of capacitor are

- ① coupling capacitor } ⇒ group # 1 = G₁
 - ② By pass capacitor }
 - ③ Load capacitor } ⇒ group # 2 = G₂
 - ④ Transistor capacitor } shown in higher freq.
- * لا بالاعتقان او باي شكل راج نطلع الى قيمه او (capacitor) و بنتوف كيف وضع ال (capacitor) راج يكون و كيف بتغير مع تغير ال (freq).

- ← حالات ال (capacitor) بتغير ال (freq.)
- ① ← open circuit
 - ② ← short circuit
 - ③ ← No-chang ((have value))

$$Z_c = \frac{1}{j2\pi fC}$$

* ال بيك ابدال :-

In practical case group # 1 >> group # 2

بهاي الكانه راج بنتوف كيف ال (capacitor) راج بيكون في كل حاله من حالات ال (freq) و راج نطلع الى قيمه ال القانون

$$Z_c = \frac{1}{j2\pi fC}$$

↑ [group #1 >> group #2] ← Practical cases

freq. cases	group #1 of (C)	group #2 of (C)
at low freq عند اقل ترددات LP في (FL) $\Rightarrow f_L = \frac{1}{2\pi T_L} = f_{3dB}$	$Z_c = \frac{1}{j2\pi f c}$ F is low but c is High $\Rightarrow Z_c = \text{Have Value}$ $\Rightarrow c = \text{No change}$	$Z_c = \frac{1}{j2\pi f c}$ F is low and c is low $\Rightarrow Z_c \approx \frac{1}{0} = \infty$ $\Rightarrow c = \text{open circuit}$
at Mid Band freq. عند الترددات الوسطى LP في (First) AV	$Z_c = \frac{1}{j2\pi f c}$ f is constant but is High c is High $\Rightarrow Z_c = \frac{1}{\infty} = 0$ $\Rightarrow c = \text{short circuit}$	$Z_c = \frac{1}{j2\pi f c}$ $Z_c = \frac{1}{0} = \infty$ $\Rightarrow c = \text{open circuit}$
at High freq. عند اقل ترددات LP في (FH)	$Z_c = \frac{1}{2\pi f c}$ F is High and c is High $\Rightarrow Z_c = \frac{1}{\infty} = 0$ $\Rightarrow c = \text{short circuit}$	$Z_c = \frac{1}{2\pi f c}$ F is High but c is low $\Rightarrow Z_c = \text{Have Value}$ $\Rightarrow c = \text{No change}$
at Dc range $\Rightarrow f = 0$	$Z_c = \frac{1}{0} = \infty$ $c = \text{open circuit}$	$Z_c = \frac{1}{0} = \infty$ $\Rightarrow c = \text{open circuit}$

* بعد اتمامكم بانواع الاضمان من شرط جيبيليا LP في الحالة ان
 (group #1 >> #2) فلابد ان انتبه الى قيم او (C) المخطط واهم
 من القيمة او (High) ومن القيمة او (Low) وبعد مقارنة
 من قبل شوي

یہ ماہر کیا بتا سکتے ہیں، اس کی (freq. response) اور (T) اور (f_{3dB})

⇒ How I can find T ??


- ① find (T) by the curve
- or → ② find (T) by the Transfer function
- or → ③ find (T) by the given circuit.

Now:-


Find (T) from the curve :-

~~f_{3dB}~~ $T = \frac{1}{2\pi f}$

Ex: ①

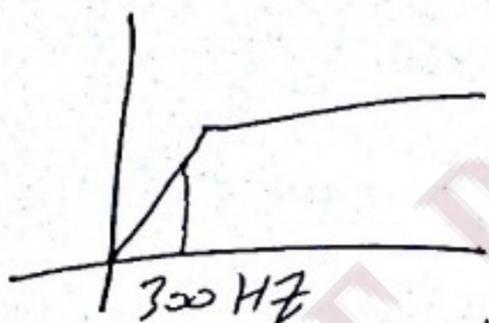


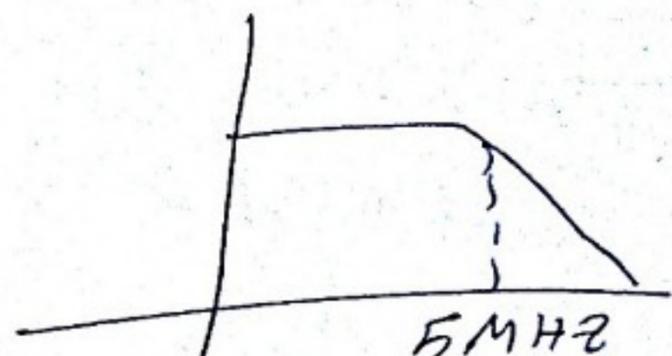② $T = \frac{1}{2\pi f} = \frac{1}{2\pi \times 300} \text{ sec}$



$T = \frac{1}{2\pi \times 5 \times 10^6} \text{ sec}$

③

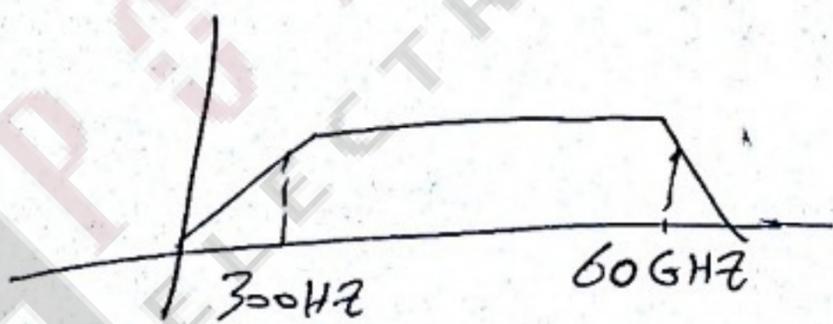

$T_1 = \frac{1}{2\pi \times 300} \text{ sec}$

$T_2 = \frac{1}{2\pi \times 60 \times 10^9} \text{ sec.}$

Answer can be

Find T from the circuit.

⇒ We have two cases so


- 1- if I have 1 capacitor in my circuit
- 2- if I have 2 capacitor " " "

→ 1 capacitor in my circuit :-


$$T = R_{eq} \times C \quad ; \quad R_{eq} = R_{th}$$

$$\Rightarrow T = R_{eq} \times C = R_{th} C$$

⇒ frequency response :-

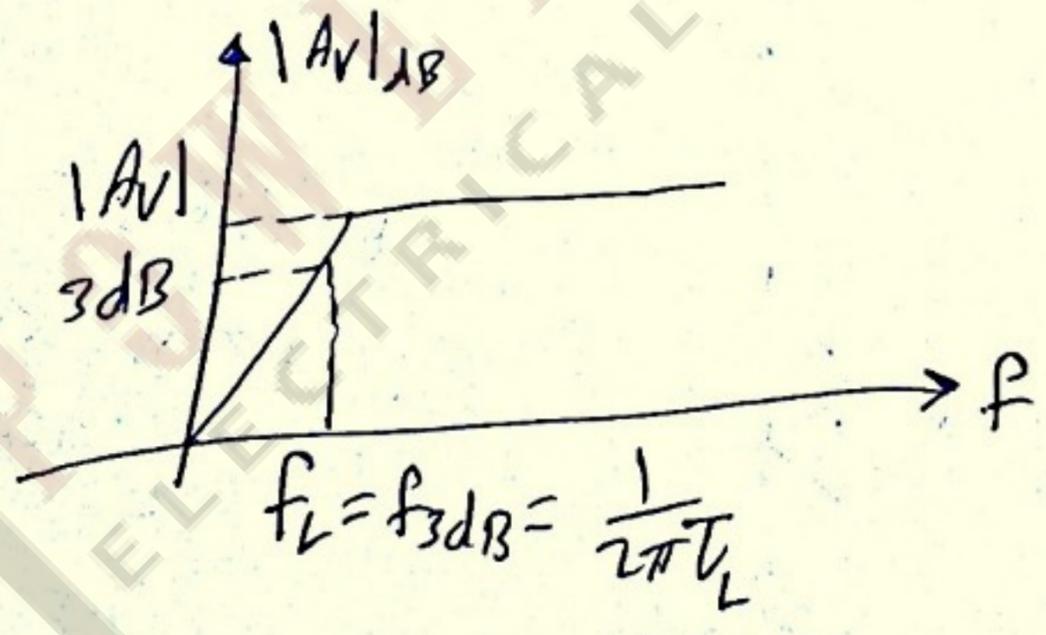


T_B

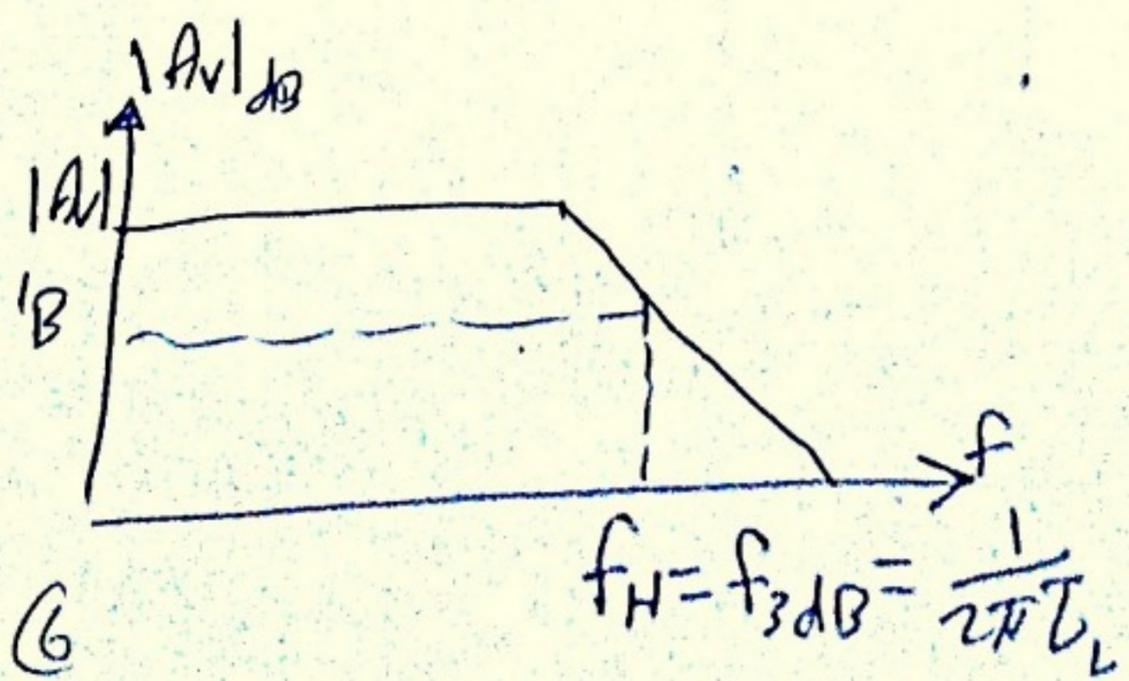

6

EX: H.W :-

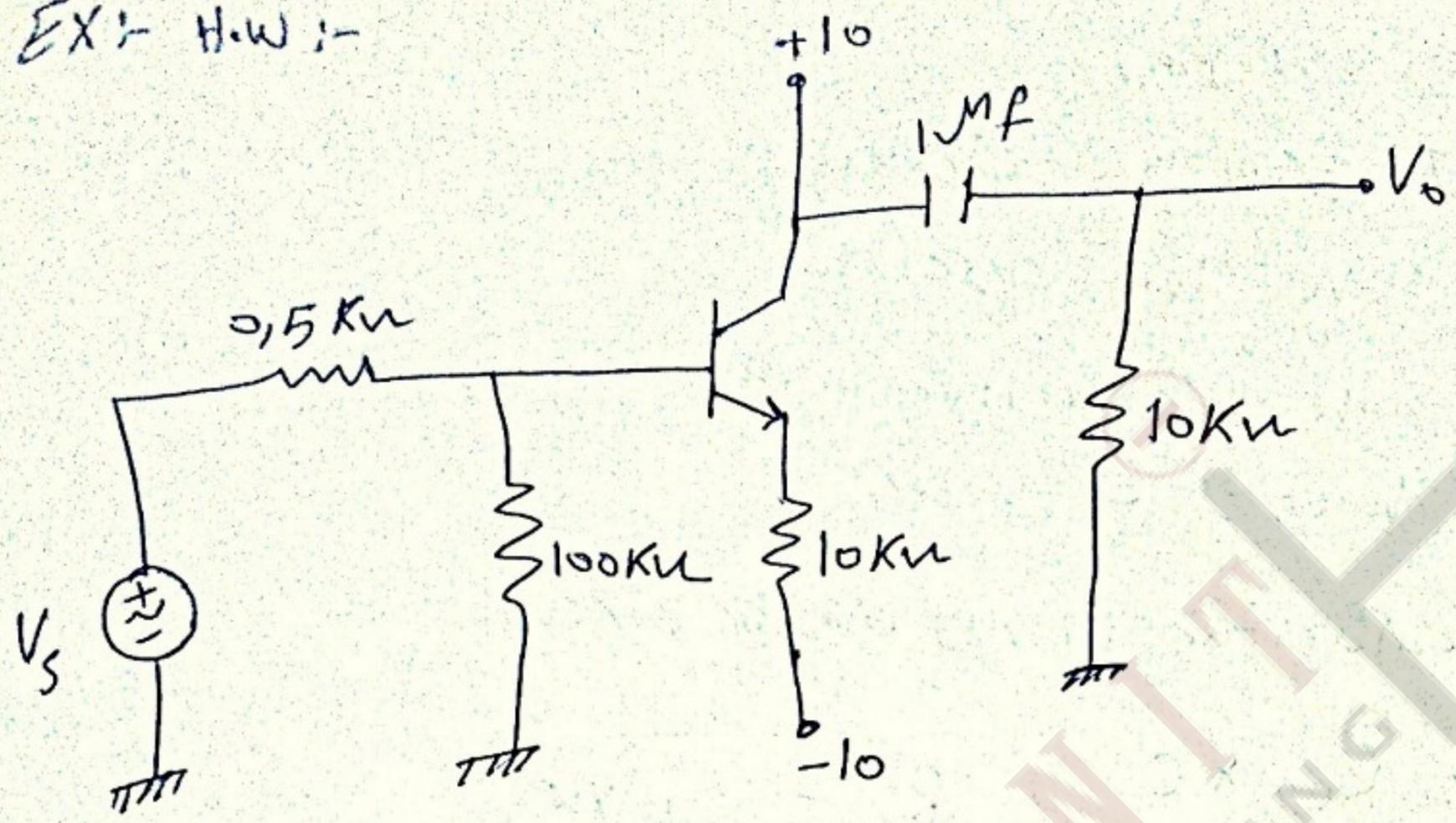


Find T and f_{3dB} .

$\beta = 100$, $V_{BE(on)} = 0.7$, $V_A = 120$.

Solution :-

→ DC Analysis :-

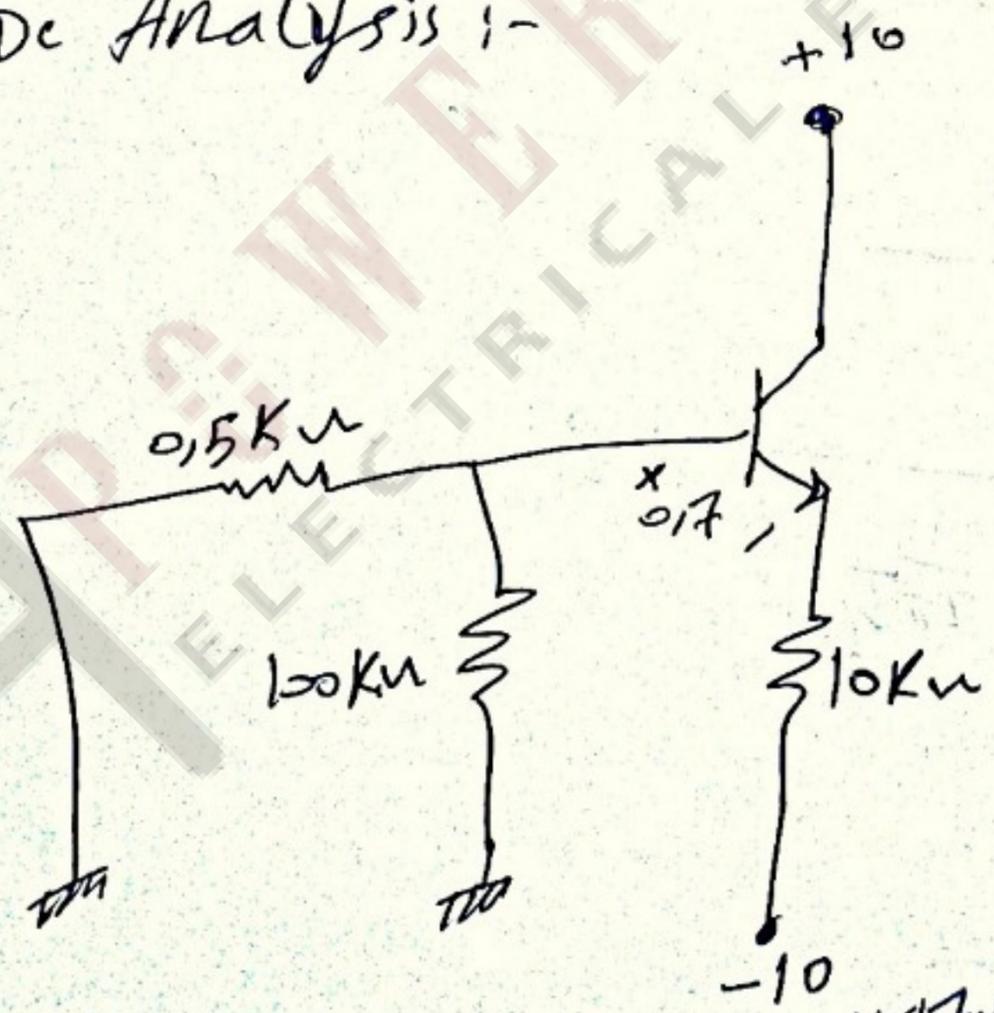

$$R_s \parallel R_B = \frac{100 \parallel 0.5k\Omega}{100} = 497.5\Omega$$

$$0.7 + I_E (10 \times 10^3) - 10 + I_B (497.5) = 0 \quad ; \quad I_E = (1 + \beta) I_B$$

$$\Rightarrow 0.7 + I_B (101)(10 \times 10^3) - 10 + I_B (497.5) = 0$$


$$\Rightarrow I_B = 9.2 \mu A \quad \Rightarrow I_C = \beta I_B = 9.2 \times 10^{-4} A$$

$$\Rightarrow r_{\pi} = \frac{0,026}{I_B} = 2825 \Omega$$

$$r_o = \frac{V_A}{I_C} = 130,435 \text{ K}\Omega$$

$$g_m = \frac{I_C}{0,026} = 0,10354 \text{ S}$$

→ AC circuit:

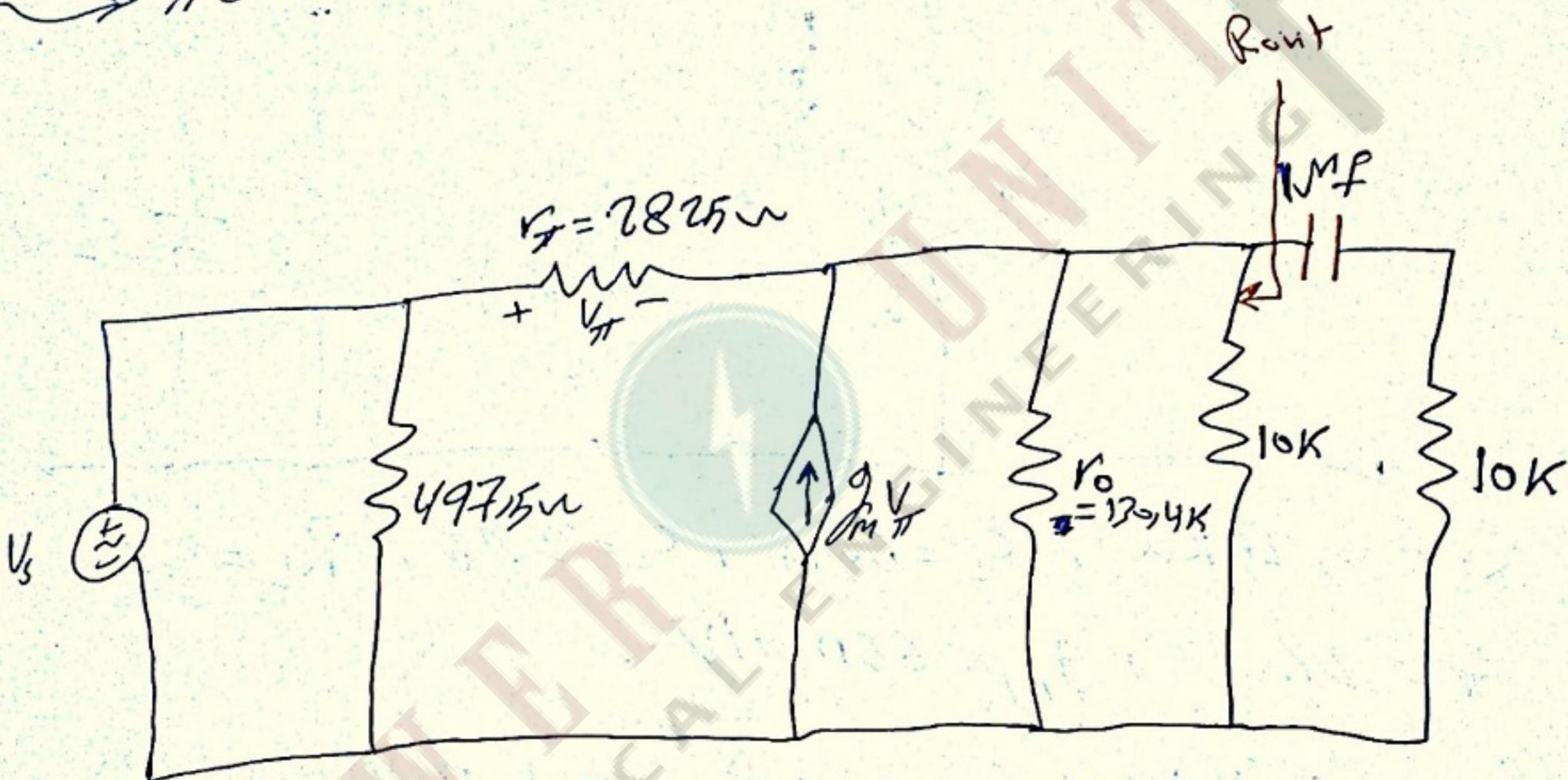

$$T = R_{th} * C \quad ; \quad R_{th} = R_{out} + R_L$$

→ This circuit is C.C Amplifier


$$\Rightarrow R_{out} = R_E \parallel r_o \parallel \left[\frac{r_{\pi} + (R_s \parallel R_B)}{1 + \beta} \right] = 32,8 \Omega$$

$$\Rightarrow R_{th} = 10032,8 \Omega$$

$$\Rightarrow T \approx 0,01 \text{ sec} \Rightarrow f_{3dB} = f_c \approx 15,9 \text{ Hz}$$

→ case 2 → 2 capacitor :-
 → so we will use open circuit test and short circuit test.

Ex:-

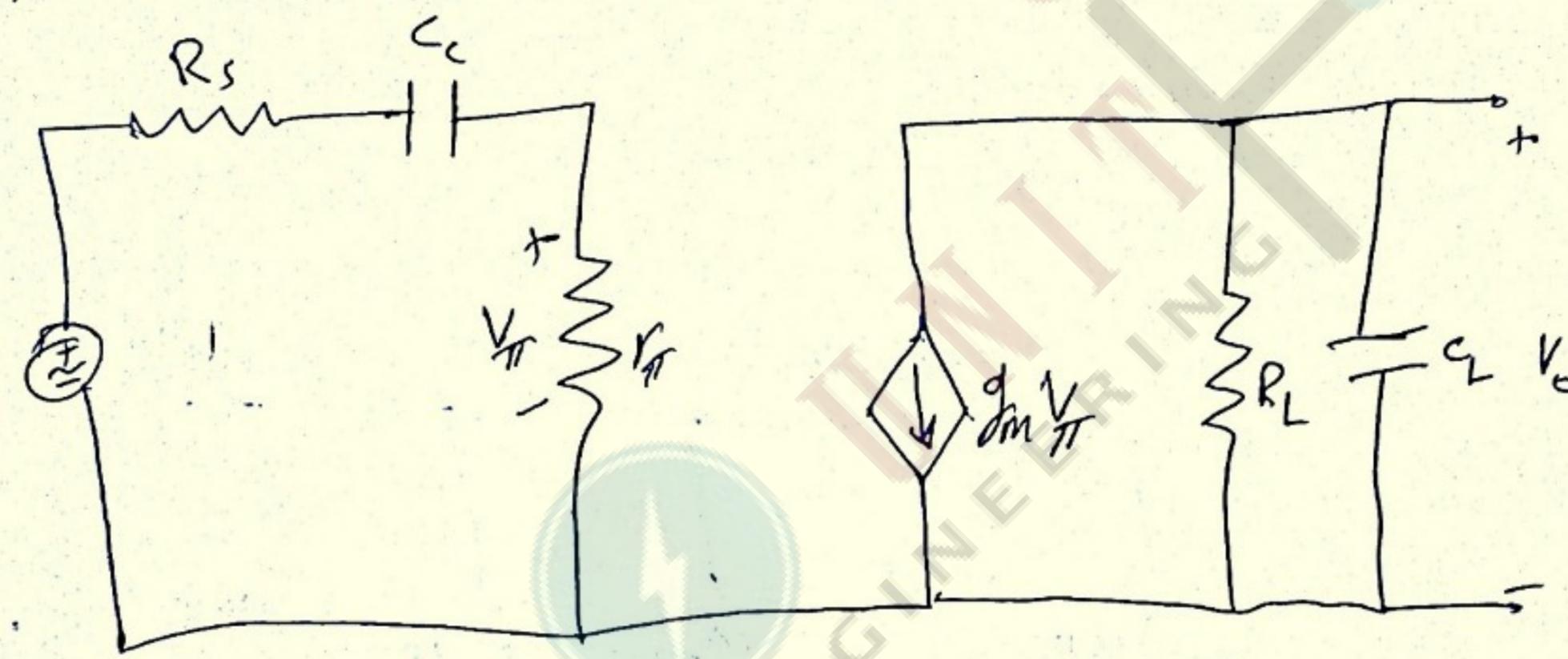

$R_s = 0, 25K\Omega$, $C_L = 50pF$, $C_c = 2\mu F$, $R_L = 4K\Omega$
 $R_D = 2K\Omega$, $g_m = 65mA/V$.

find 3dB High freq. « f_H » and 3dB low freq.

« f_L » and find A_v

solution:- $C_c \gg C_L$

→ at low freq.

$$\Rightarrow Z_c = \frac{1}{2\pi f C_c} = \text{Have Value}$$


$$Z_L = \frac{1}{2\pi f C_L} = \frac{1}{0} = \infty = \text{open circuit}$$

$$f_{3dB} = f_H = \frac{1}{2\pi f_H} = 0,796 \text{ MHz}$$

→ at Mid Band Range to find A_v :-

$Z_{cc} = \text{short circuit}$, $Z_{cl} = \text{open circuit}$

$$A_v = -g_m \frac{R_L r_{\pi}}{r_{\pi} + R_s} = -231 \Rightarrow |A_v| = 231$$

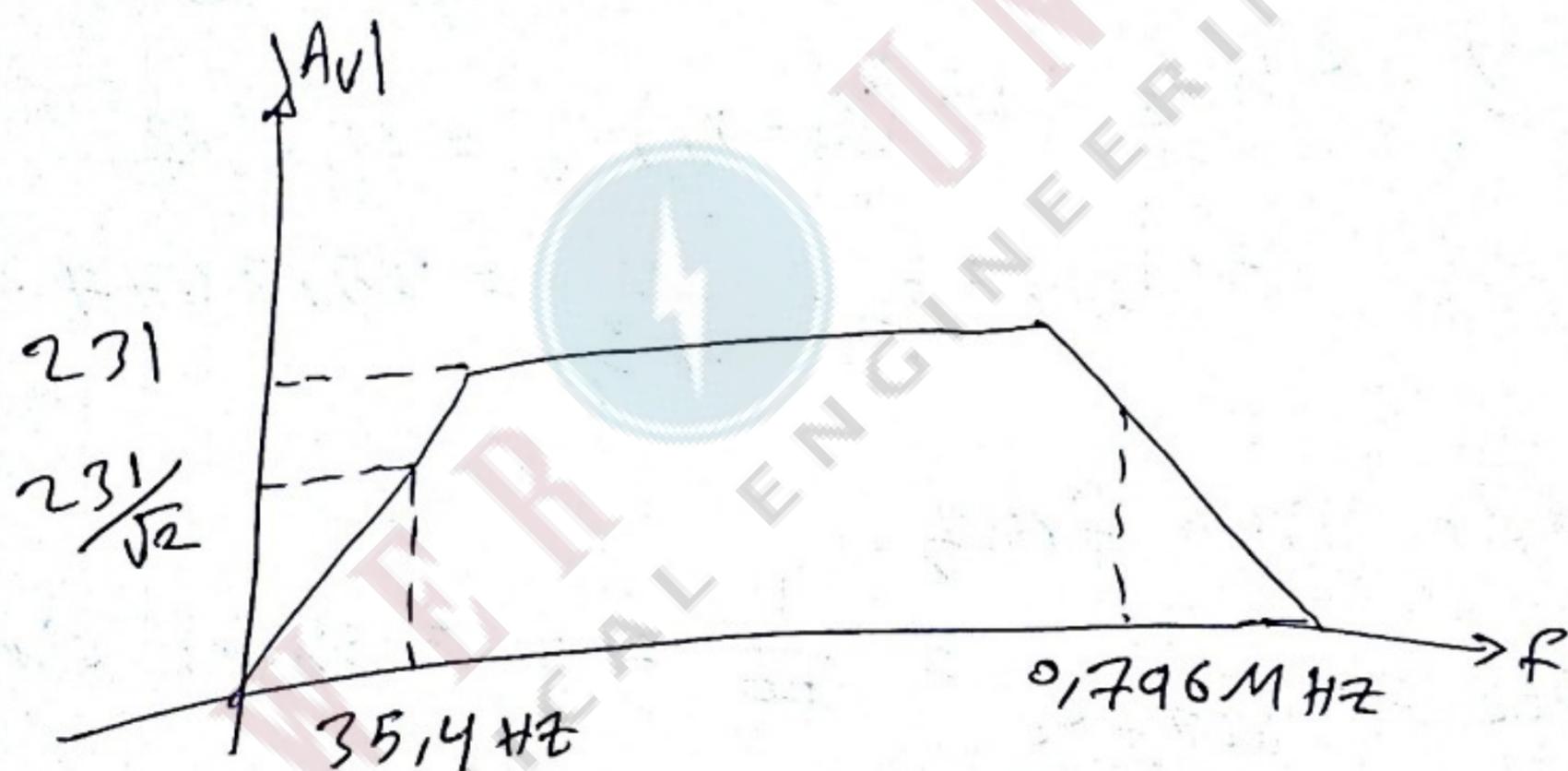


3] How I can find (T) from Transfer function $T(s)$

Transfer function $T(s)$ &

$s = j\omega = j2\pi f$:- complex frequency.

$$Z_c = \frac{1}{j2\pi f_c} = \frac{1}{j\omega_c} = \frac{1}{s_c} \text{ ~}$$

⇒ Draw the New circuit at Low freq.

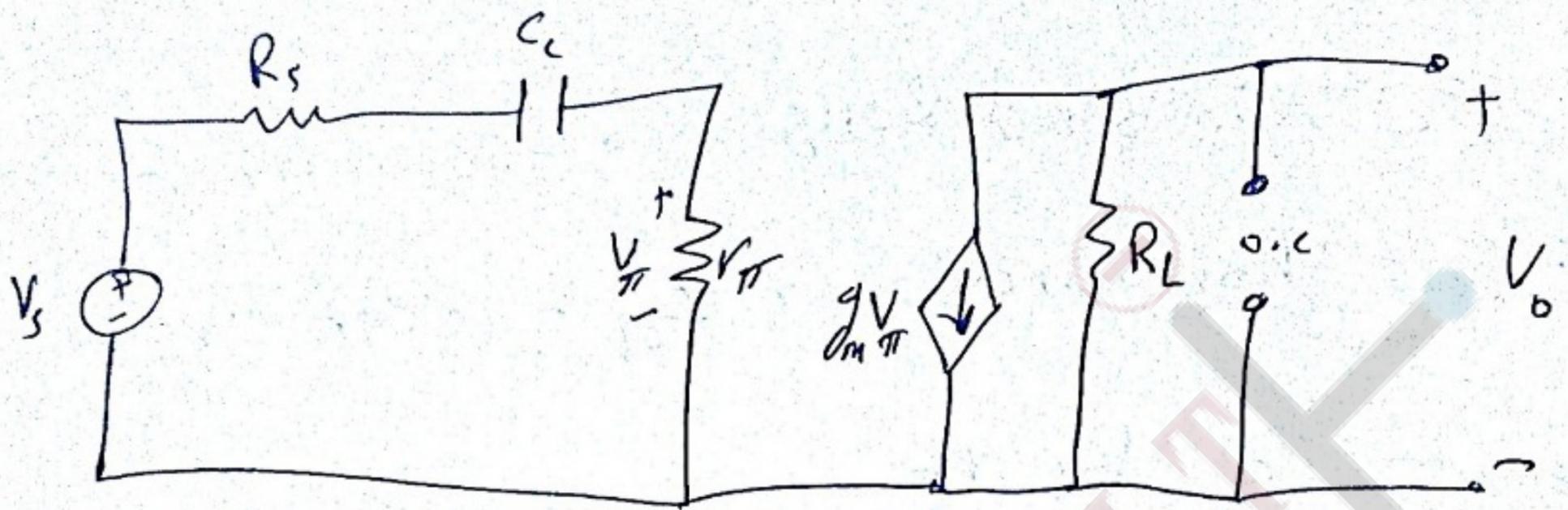

(1 capacitor) ke series (circuit) ke equivalent ←

$$\Rightarrow Z = R_{th} C_c = (R_s + R_{\pi}) C_c = 4.5 \mu F$$


$$\Rightarrow f_{3dB} = f_L = \frac{1}{2\pi T_c} = 3513677 \text{ Hz}$$

→ at High freq.

$$Z_{C_c} = \frac{1}{j2\pi f C_c} = \frac{1}{\infty} = 0 \equiv \text{short circuit}$$

$$Z_{R_L} = \frac{1}{2\pi f C_c} = \text{Have Value}$$

⇒ Draw the New circuit at High freq.

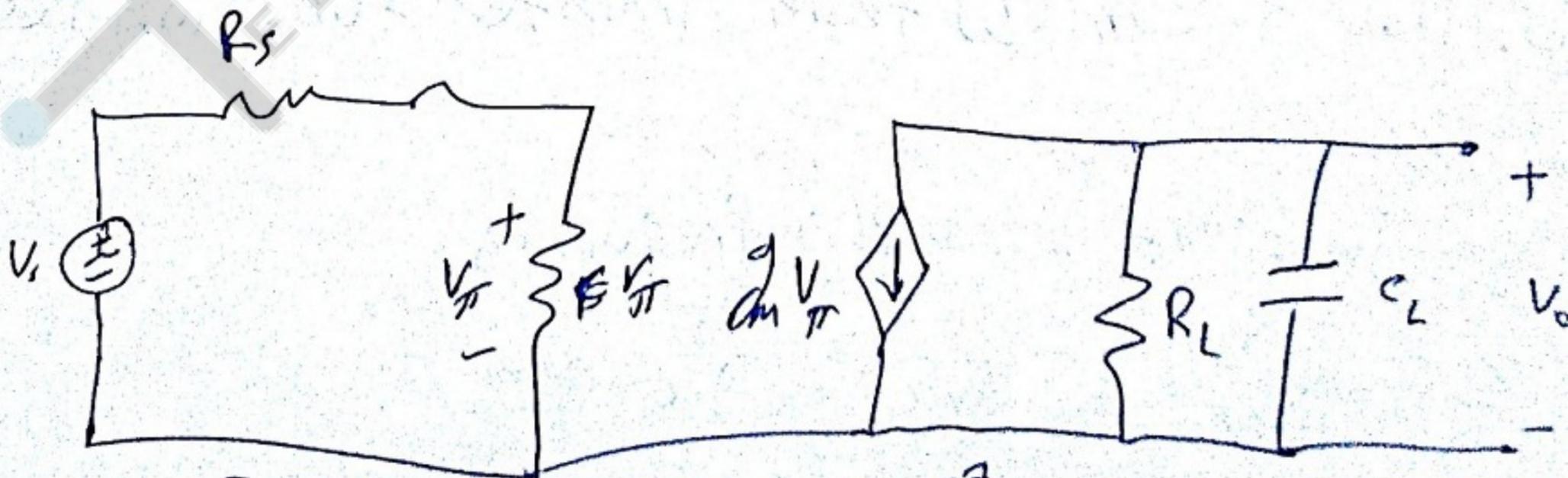

$$T = R_{th} C_c = C_c \times R_L = 2 \times 10^{-7} \text{ sec}$$


How I can draw the frequency response??

→ BY Bode Plot on


* Bode Plot :-

يجب علينا رسم المنحني (5) التالية، حفظ الامكان.

1) $G(j\omega) = G(s) = K$

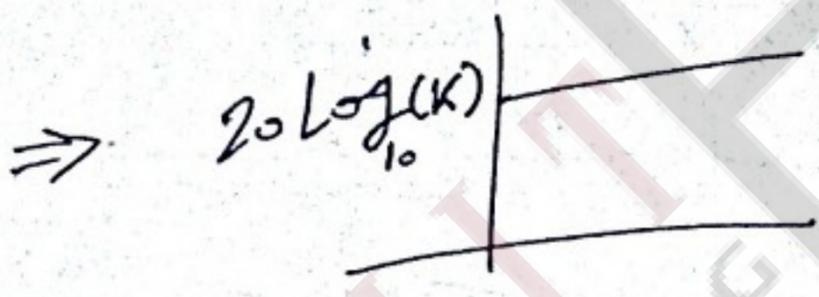


2) $G(s) = \frac{1}{s}$

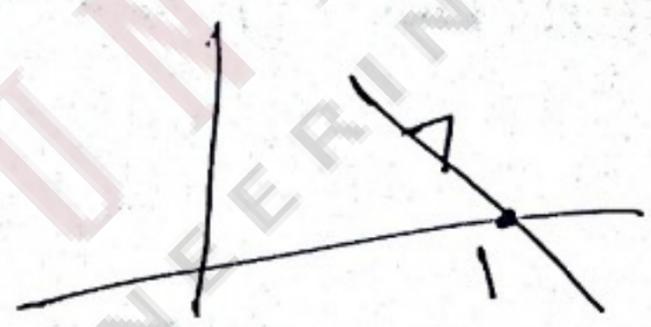


slope = -20 dB/dec
= -6 dB/octave

3) $G(s) = s$

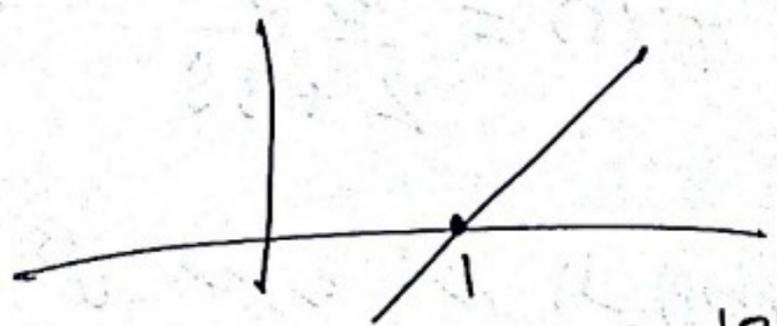

slope = 20 dB/dec

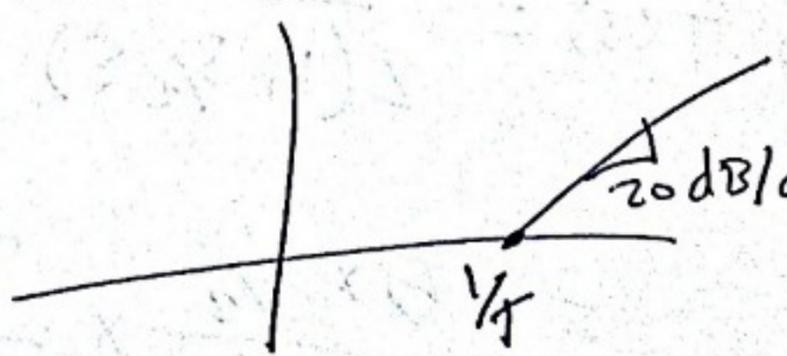4) $G(s) = 1 + sT$; $T \equiv \text{const.}$



20 dB/dec

5) $G(s) = \frac{1}{1 + sT}$



slope = -20 dB/dec

* راجع المثال الموجود بالدفتر # (12)

Time Response :-

→ In general in Amplifier ckt :- $Gain = \frac{out}{in}$


$$\Rightarrow \boxed{INPUT = Gain \times output}$$

but now we will study if $\boxed{INPUT \neq Gain \times output}$

* C_i (input) اور C_o (output) کی سیکنگ کا مطالعہ کریں

→ We will study 2 circuits :- ① In-ckt ② out-ckt

□ Input circuit :-

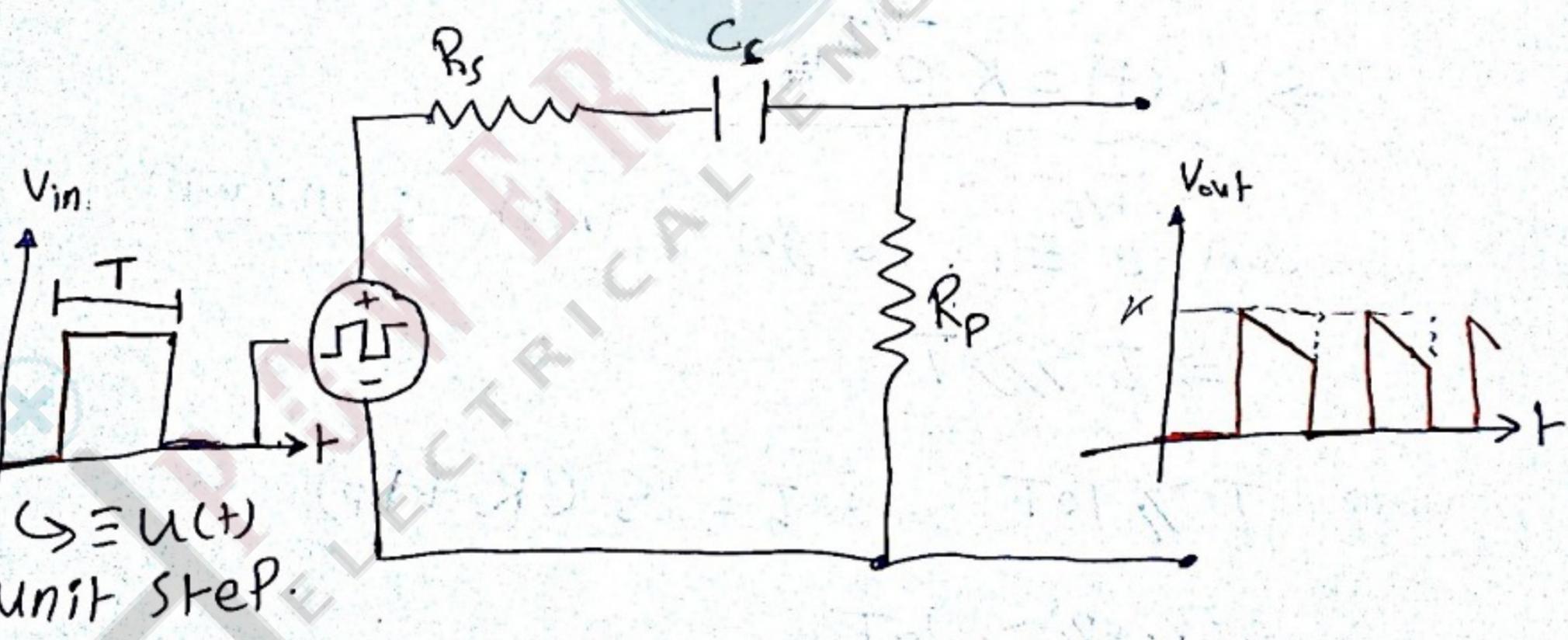

Time domain

s-domain

$$V_{in}(t) = U(t) \xrightarrow{\text{by Laplace}} V_{in}(s) = \frac{1}{s}$$

We know that from freq. response $\Rightarrow T = R_{th} C = (R_p + R_s) C_c$

and $K = |A_v| = \frac{R_p}{R_p + R_s} \Rightarrow T(s) = K \times \frac{sT}{1 + sT}$

$$\Rightarrow T(s) = \frac{V_o(s)}{V_{in}(s)} = K \frac{s\tau}{1+s\tau}$$

$$\Rightarrow V_o(s) = K \frac{s\tau}{1+s\tau} * V_{in}(s)$$

but the $V_{in}(s) = u(t) = \frac{1}{s}$

$$\Rightarrow V_o(s) = K \times \frac{s\tau}{1+s\tau} \times \frac{1}{s}$$

$$V_o(s) = K \times \frac{\tau}{1+s\tau}$$

$$\equiv K \times \frac{1}{\frac{1}{\tau} + s}$$

\Rightarrow take the INVERSE Laplace

$$\Rightarrow V_o(t) = K e^{-t/\tau}$$

we want $e^{-t/\tau} \approx 1$ to get

$$\text{Input} = \text{Gain} \times \text{output}$$

Assume $\tau \gg 10T$

$$\tau = C_s (R_s + R_p)$$

$$\Rightarrow C_s (R_s + R_p) \gg 10T$$

$$\Rightarrow C_s \gg \frac{10T}{R_s + R_p}$$

$$\Rightarrow C_c \uparrow \Rightarrow f_L \downarrow \Rightarrow B \uparrow \Rightarrow \underline{\underline{\text{good}}}$$

$$\Rightarrow T \leq \frac{T}{10}$$

$$\Rightarrow C_L (R_S \parallel R_L) \leq \frac{T}{10}$$

$$\Rightarrow C_L \leq \frac{T}{10(R_S \parallel R_L)} \quad \text{مفید}$$

$$C_L \downarrow \Rightarrow f_H \uparrow \Rightarrow B \uparrow \Rightarrow \text{good}$$

$$\Rightarrow C_C \gg C_L$$

① because we want to get large Bandwidth.

② and get good Time response. ~~and get good Time response.~~

$$G = \frac{V_o}{V_{in}}$$

* Frequency response for BJT sa

آول در (chapter) کتا نرس در (circuits) سبک نام بس
لا ریح تنصه بالترانسور نفیس.

BJT :-


→ at DC $\Rightarrow f=0$

→ current gain « short circuit current gain » = $\beta = \frac{I_C}{I_B}$

→ at low freq. and Mid band freq. sa

→ current gain « short circuit current gain » = $\beta = \frac{I_C}{I_B}$

2] output circuit i-

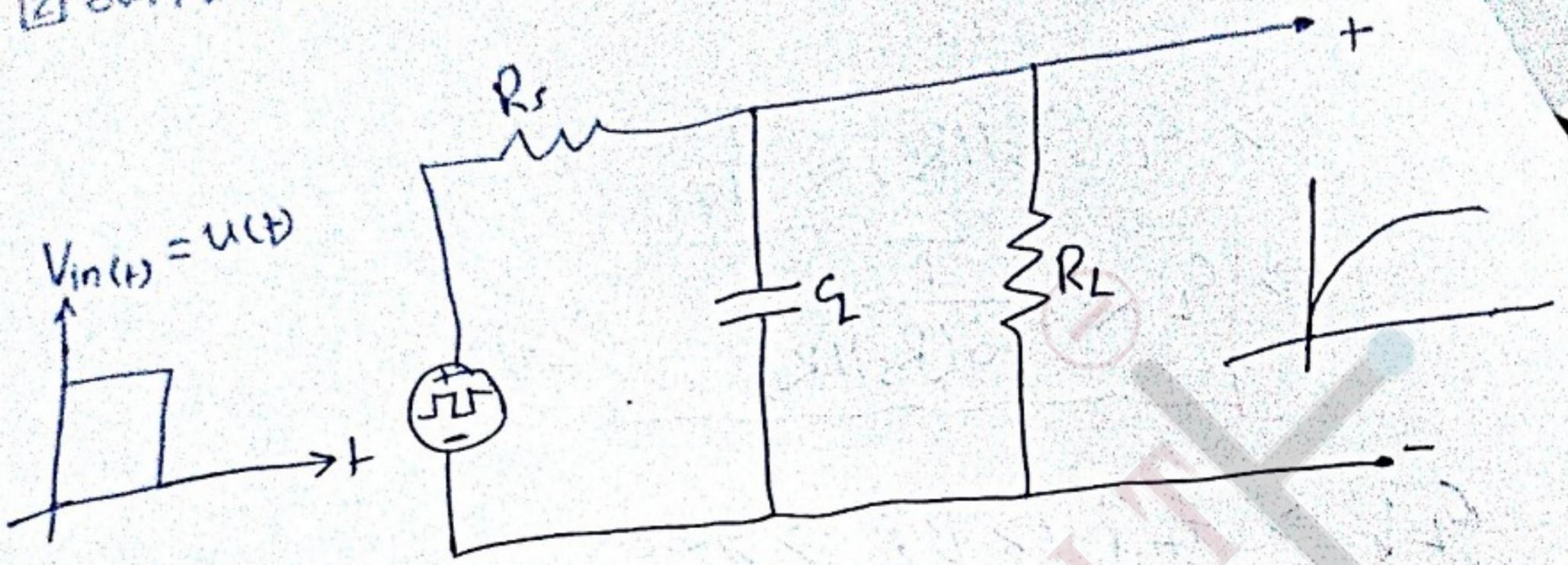

$$\frac{V_o(s)}{V_{in}(s)} = K * \frac{1}{1+s\tau} \quad \text{where } \tau = C_L (R_S \parallel R_L)$$

$u(t) \rightarrow \frac{1}{s}$

$$\Rightarrow T(s) = \frac{V_o(s)}{V_{in}(s)} = K * \frac{1}{1+s\tau}$$

$$\Rightarrow V_o(s) = V_{in}(s) * K * \frac{1}{1+s\tau} \quad \text{but } V_{in}(s) = u(t) = \frac{1}{s}$$

$$\Rightarrow V_o(s) = \frac{1}{s} * K * \frac{1}{1+s\tau}$$

by Inverse Laplace


$$\Rightarrow V_o(t) = K(1 - e^{-t/\tau})$$

we want to $e^{-t/\tau} \approx 0$ to get $V_{in} = \text{Gain} \times V_{out}$

$\tau \ll t \Rightarrow$ Assume $\tau \leq \frac{t}{10}$

but $\tau = C_L (R_S \parallel R_L)$

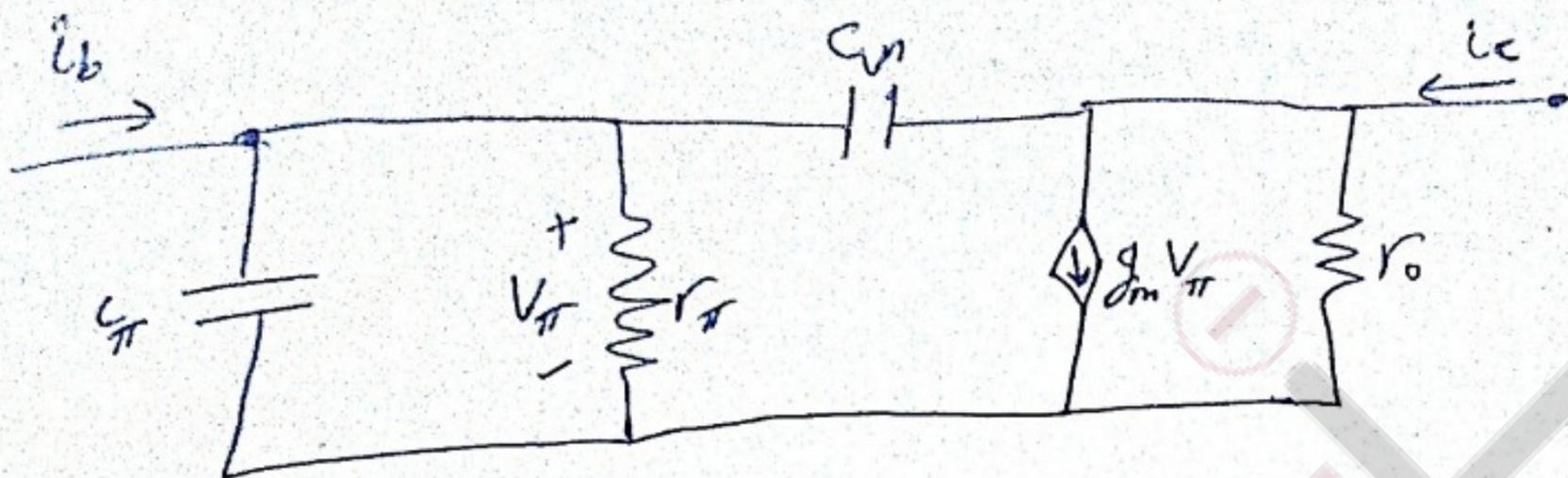at High freq. range so $\beta \neq \frac{I_c}{I_B}$



C_{π} :- Forward-biased Junction capacitor

C_{μ} :- Reverse-biased Junction capacitor

* usually $C_{\mu} \ll C_{\pi}$ so $\beta \neq \frac{I_c}{I_B}$

$$h_{fe} = A_{i.} = \frac{i_c}{i_b} \approx \frac{\beta}{1 + j\omega r_{\pi} (C_{\pi} + C_{\mu})}$$


حفظ
للإستعمال

هذا ما تعرفه في كتاب القانون الرابع الفتر أو الكتاب

$$\Rightarrow I_c = I_B \times h_{fe}$$

$$h_{fe} \equiv A_{i.}$$
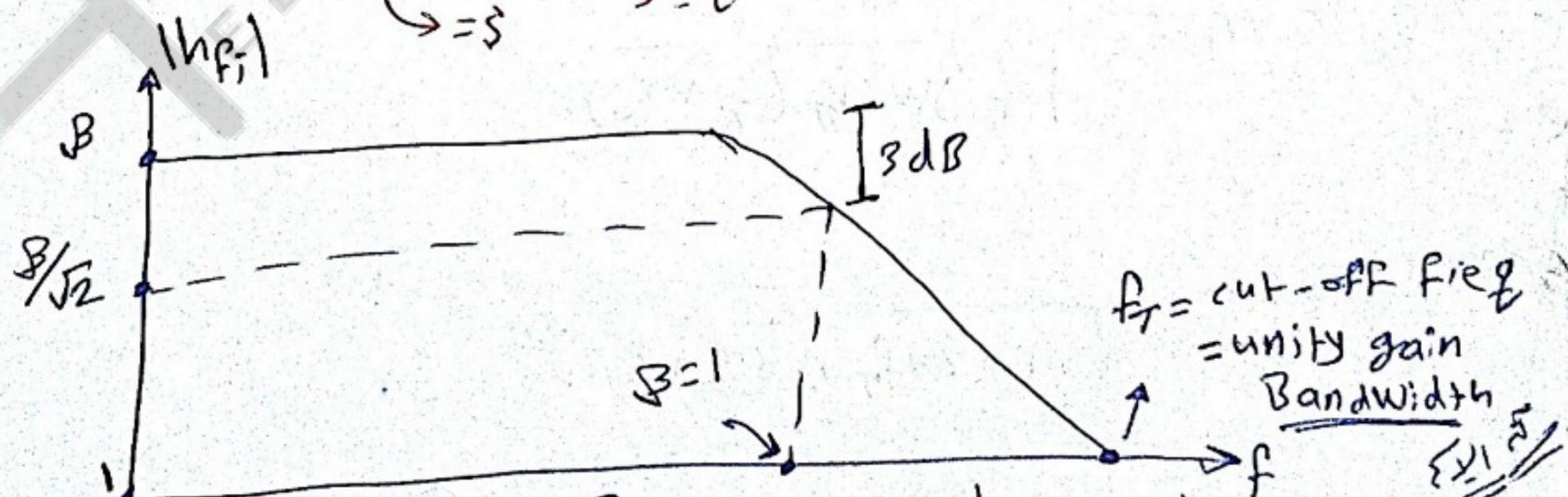
$$h_{fe} = A_{i.} = \frac{\beta}{1 + (j\omega)^2 \tau^2} \equiv T(s) = K \times \frac{1}{1 + s\tau}$$




f_T = cut-off freq
= unity gain
Bandwidth

$$f_B = f_{3dB} = f_{h_{fe}} = \frac{1}{2\pi\tau} = \frac{1}{2\pi r_{\pi} (C_{\pi} + C_{\mu})}$$

beta-cut-off freq. or the Bandwidth of Trans

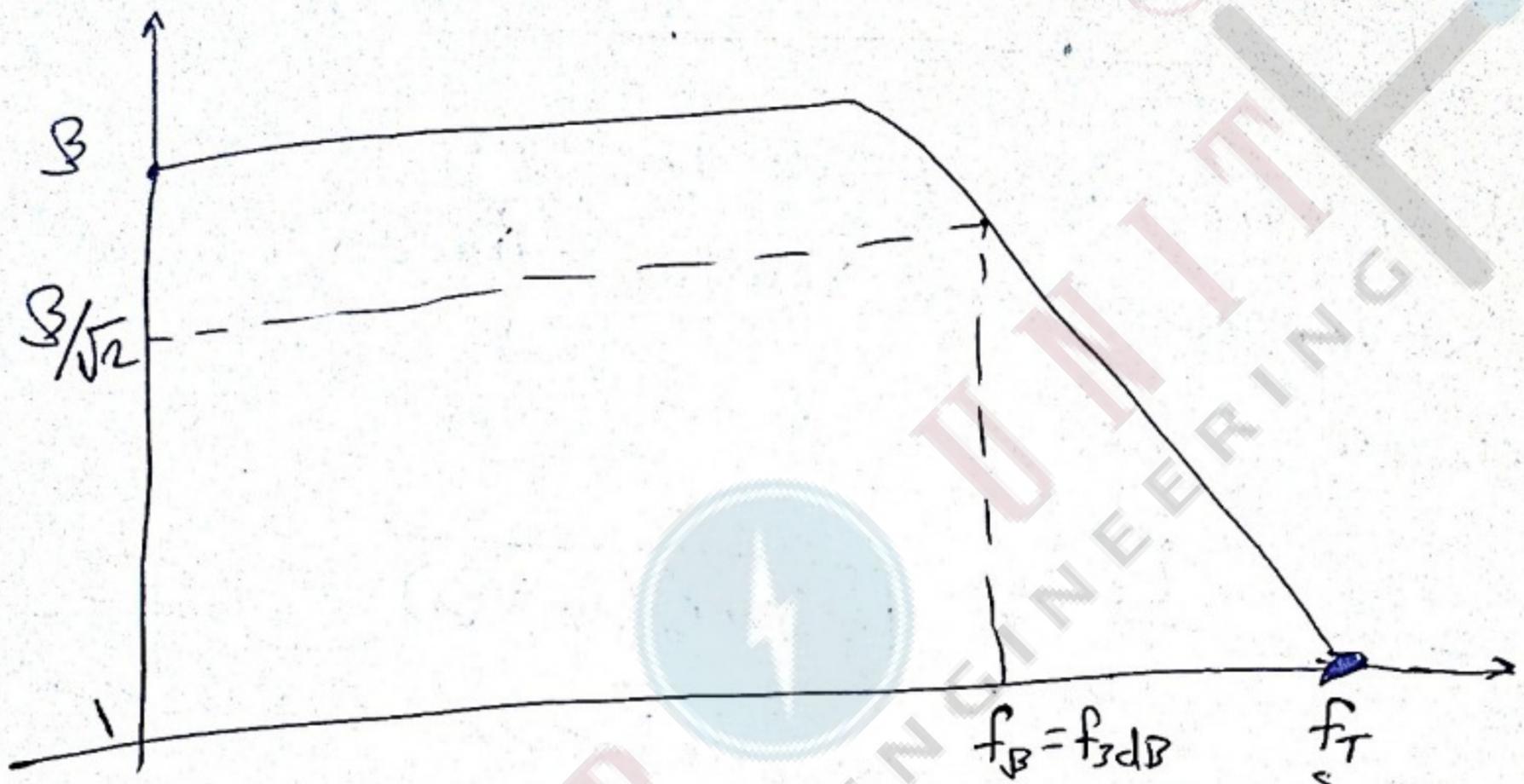إذا كان سيجب الترانزستور صغير $\leftarrow (C_{\pi} + C_M)$ راج يكون قليل
 \leftarrow راج نستخدمه في (High freq)
 \leftarrow او (Bandwidth) راج يكون واسع \leftarrow good



Bandwidth of Transistor

$$f_B = \frac{1}{2\pi\tau} = \frac{1}{2\pi r_{\pi}(C_{\pi} + C_M)}$$

cut off freq
 or
 unity gain
 Bandwidth
 $|h_{fe}(f_T)| = 1$

$$* h_{fe} = A_v = \frac{\beta}{1 + j\omega r_{\pi}(C_{\pi} + C_M)}$$

$$|h_{fe}| = \frac{\beta}{\sqrt{1 + (2\pi f_T r_{\pi}(C_{\pi} + C_M))^2}} = 1$$


$$\Rightarrow |h_{fe}| = \frac{\beta}{\sqrt{1 + (f_T/f_B)^2}} = 1$$

$$f_T \gg f_\beta \Rightarrow |h_{fe}| = \frac{\beta}{f_T/f_\beta} = 1$$


$$\Rightarrow \beta = \frac{f_T}{f_\beta} \Rightarrow f_T = \beta f_\beta$$

Miller effect « feedback effected » and Miller capacitor

EX:-

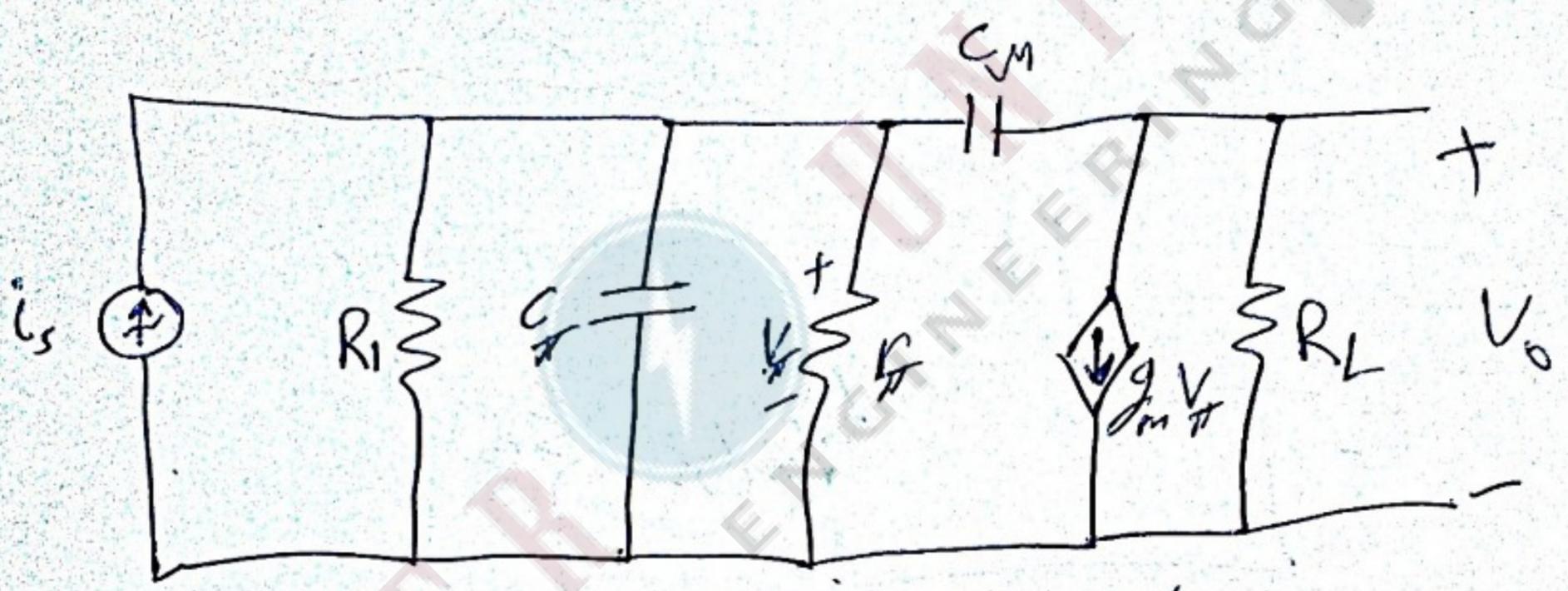

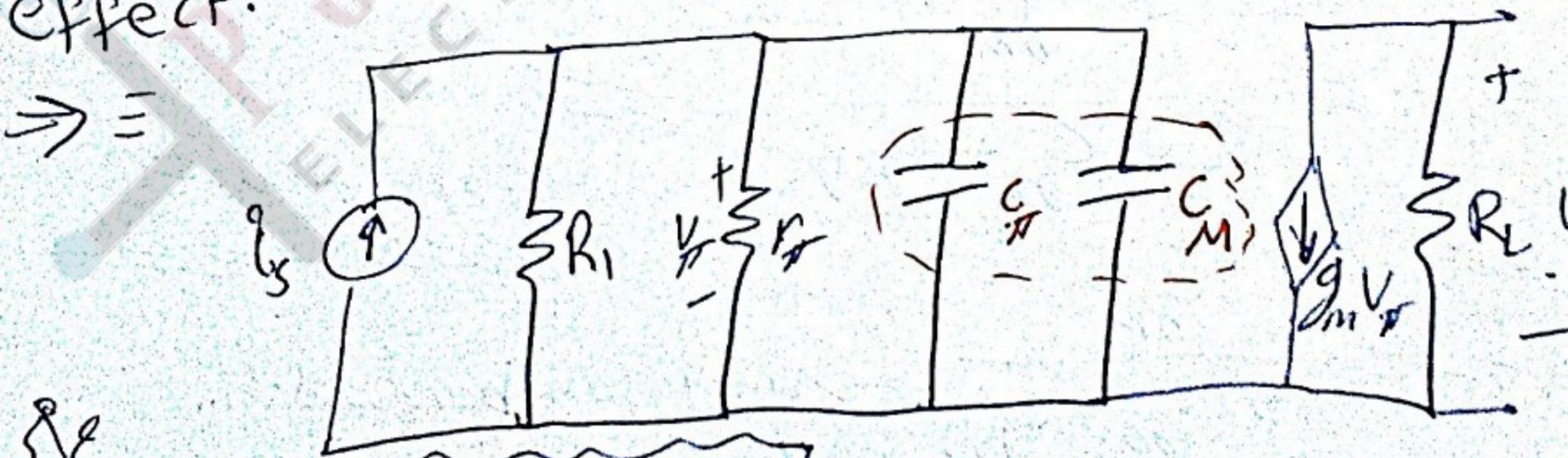~~C_M \ll C_\pi~~ but we cannot ignore C_M due to Miller effect.



Ans

$$C_M = C_M * [1 + g_m R_L] \Rightarrow \text{in general}$$

$$C_M = C_M * [1 + |V_{out}|]$$

\rightarrow let $V_\pi = 1$


* The frequency response of FET is

→ at DC → $f = 0$ $A_i = \frac{i_c}{i_g} = \infty$

→ at low freq. and midband freq

$$A_i = \frac{i_c}{i_g} = \infty$$

→ at high freq is $i_g \neq \text{Zero}$

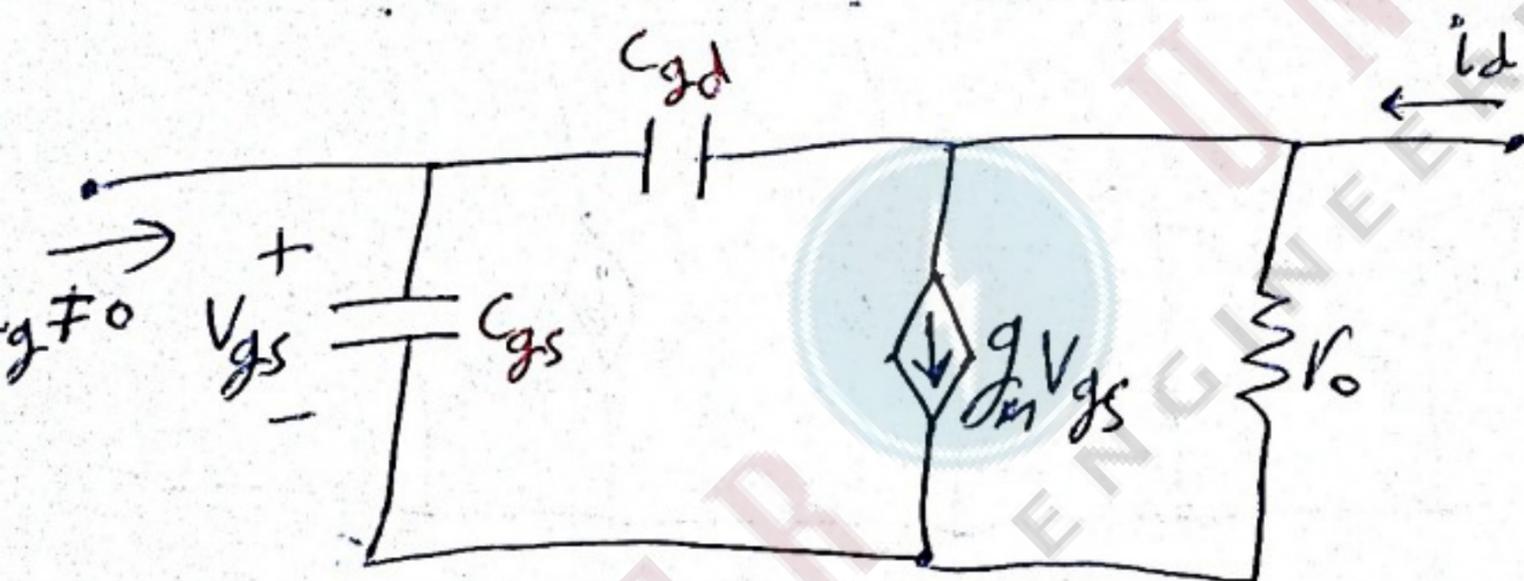

⇒ short circuit current gain $(A_i) = \frac{i_d}{i_g}$

$$A_i = \frac{g_m}{j\omega(C_{gd} + C_{gs})}$$


حفظاً

راجع الـ فتر معرفة
طريقة الاشتقاق


$$f_T = \frac{g_m}{2\pi(C_{gd} + C_{gs})}$$

→ unity gain bandwidth,

Miller effect and Miller capacitor FET

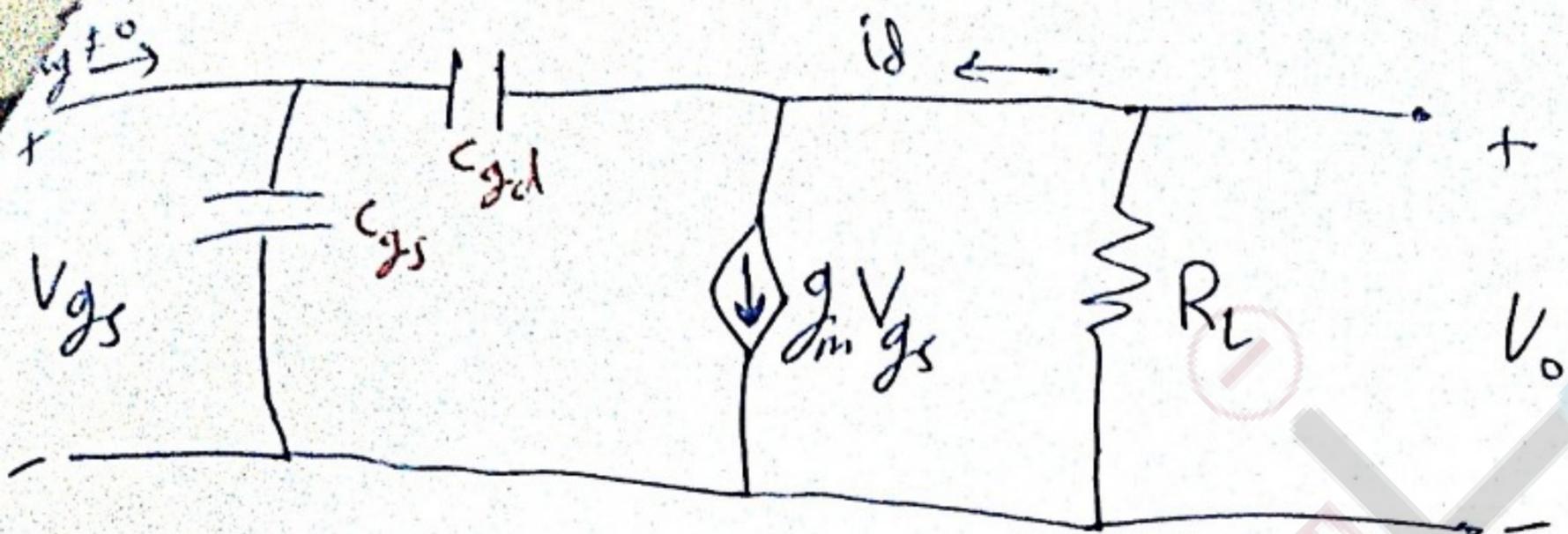

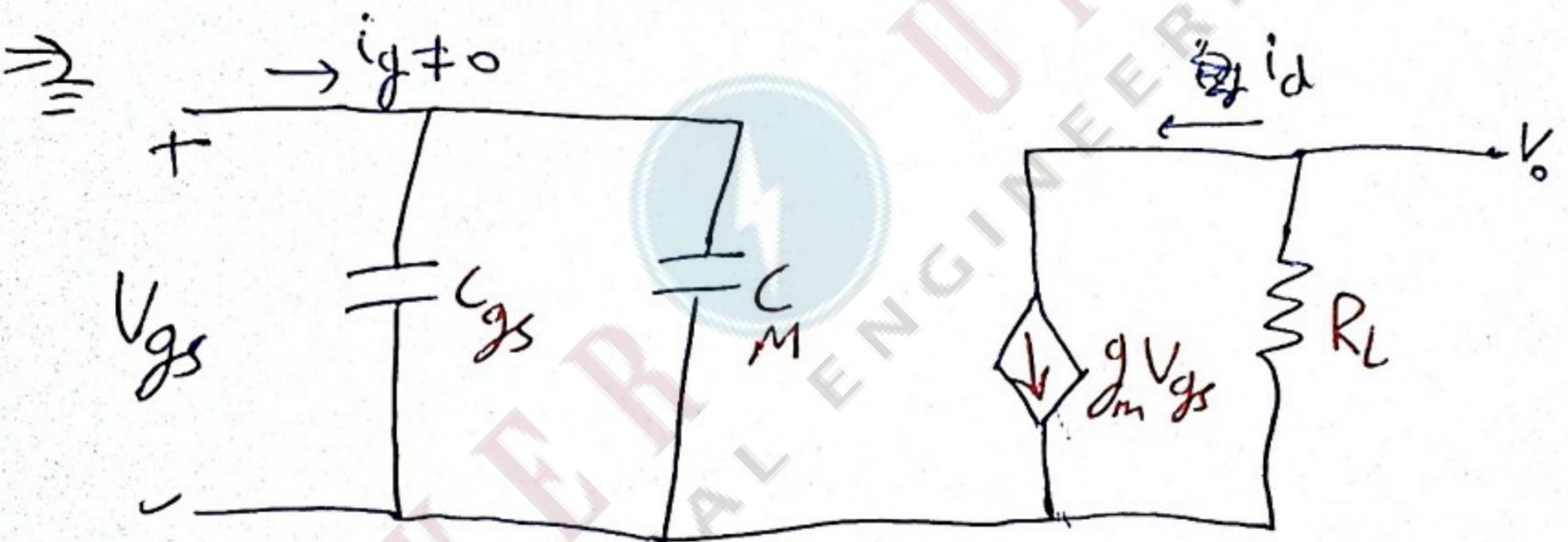$C_{gs} > C_{gd}$ but we can't ignore C_{gs} due to Miller effect.



$$C_M = C_{gd} * (1 + g_m R_L)$$

Done By \approx Anas Katz
 "Electrical Engineering"

تحت
 كذا التالى
 How do it work
 السهل

AMPLIFIER
 Final material

Mr. Kays


Voltage to current converter :-

Use Resistor (R) then you can change the Voltage to current. by ohm's law $I = \frac{V}{R}$

but the current (I) will change with R_{load}

⇒ so it's NOT solution to change from Voltage to current.

Use OP-Amp.

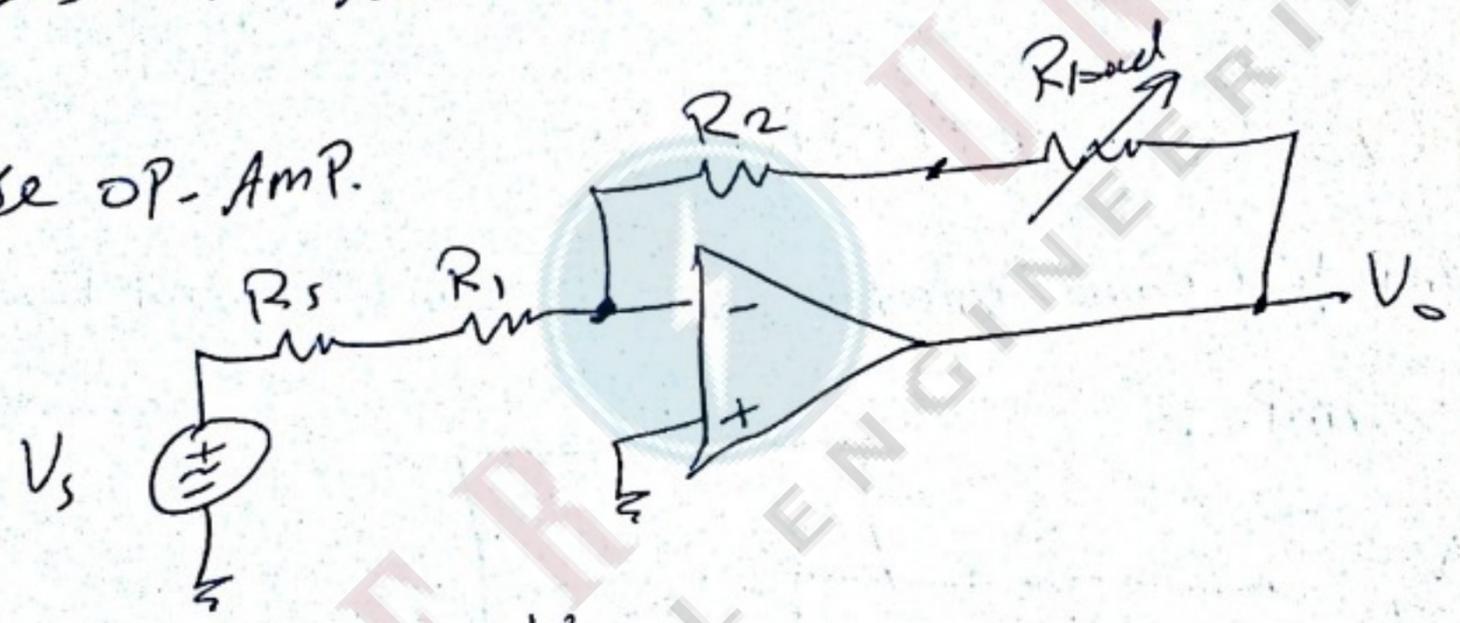


$$I_o = \frac{V_s}{R_s + R_1}$$

⇒ (I_o) will not change by changing the load ⇒ good

but the Problem:- the load can't be connected to the ground
 ⇒ solution for this problem use Transformer

Use

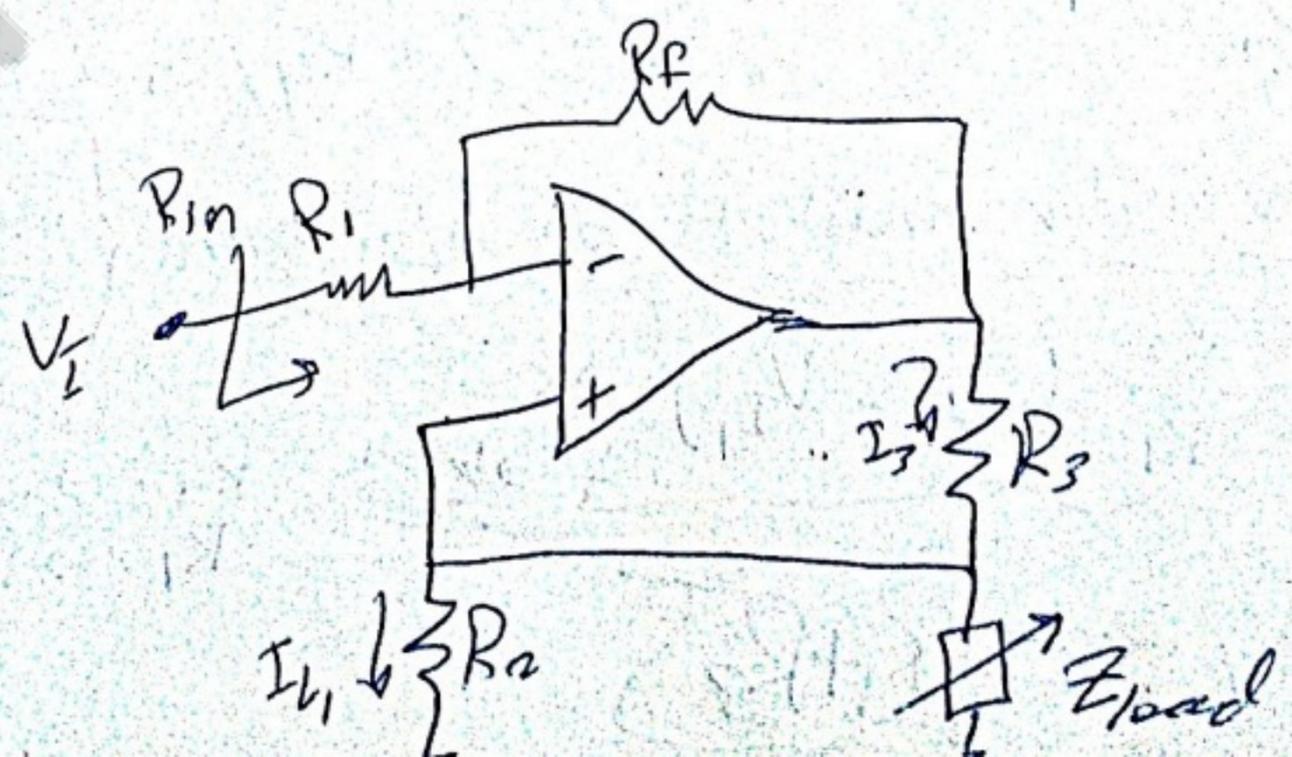

$$\Rightarrow I_L \left(\frac{R_f Z_L}{R_1 R_3} - 1 - \frac{Z_L}{R_2} \right) = V_I \left(\frac{R_f}{R_1 R_3} \right)$$

\Rightarrow by design must to be

$$\frac{R_f}{R_1 R_3} = \frac{1}{R_2}$$


$$\Rightarrow I_L = -V_I \left(\frac{R_f}{R_1 R_2} \right) \Rightarrow I_L = -\frac{V_I}{R_2} \quad \#$$

and $R_{in} = \frac{R_1 R_2}{R_2 + R_f}$

* [7] Difference Amplifier 3a

Basic OP-AMP has same function but we can't control the gain.

\Rightarrow Diff. AMP. :-

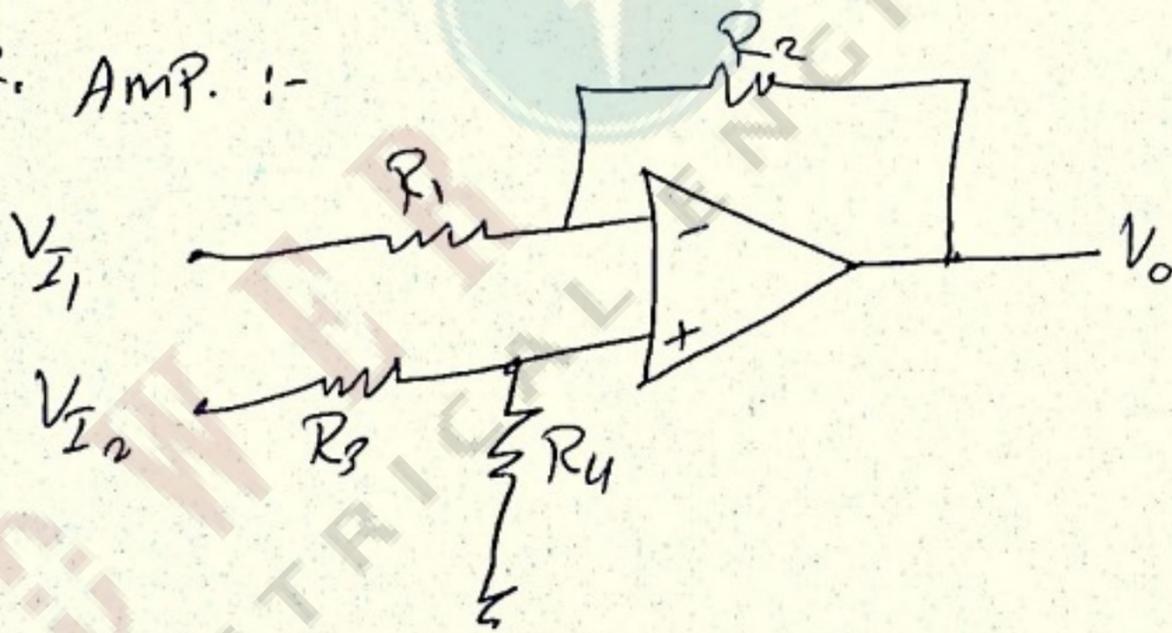

$$V_O = -\frac{R_2}{R_1} V_{I1} + \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3} \right) V_{I2}$$

\Rightarrow by design must to be the ratio

$$\frac{R_2}{R_1} = \frac{R_4}{R_3} \quad \#$$

$$\Rightarrow V_O = \frac{R_2}{R_1} (V_{I2} - V_{I1}) \quad \# \rightarrow \frac{R_2}{R_1} \rightarrow \frac{R_4}{R_3} \text{ or } \frac{R_2}{R_1} = \frac{R_4}{R_3}$$

$$\Rightarrow R_{in} = 2R_1 \quad \# = R_1 + R_3$$

⇒ For diff. Amplifier :-

$$V_o = \frac{R_2}{R_1} (V_{I_2} - V_{I_1}) \quad \text{and} \quad R_{in} = 2R_1 \quad \#$$

⇒ as we see, we have the problem :-

if $R_1 \uparrow$ then $R_{in} \uparrow$ but the gain $(\frac{R_2}{R_1}) \downarrow$


⇒ we have :- ① R_{in} Problem and ② gain $(\frac{R_2}{R_1})$ Problem

⇒ Solution for this Problem :-

① Increase (R_2) but this need the user to increase (R_4)

by the same value ⇒ ~~with~~ is Impractical.

OR ② Use the Buffer or

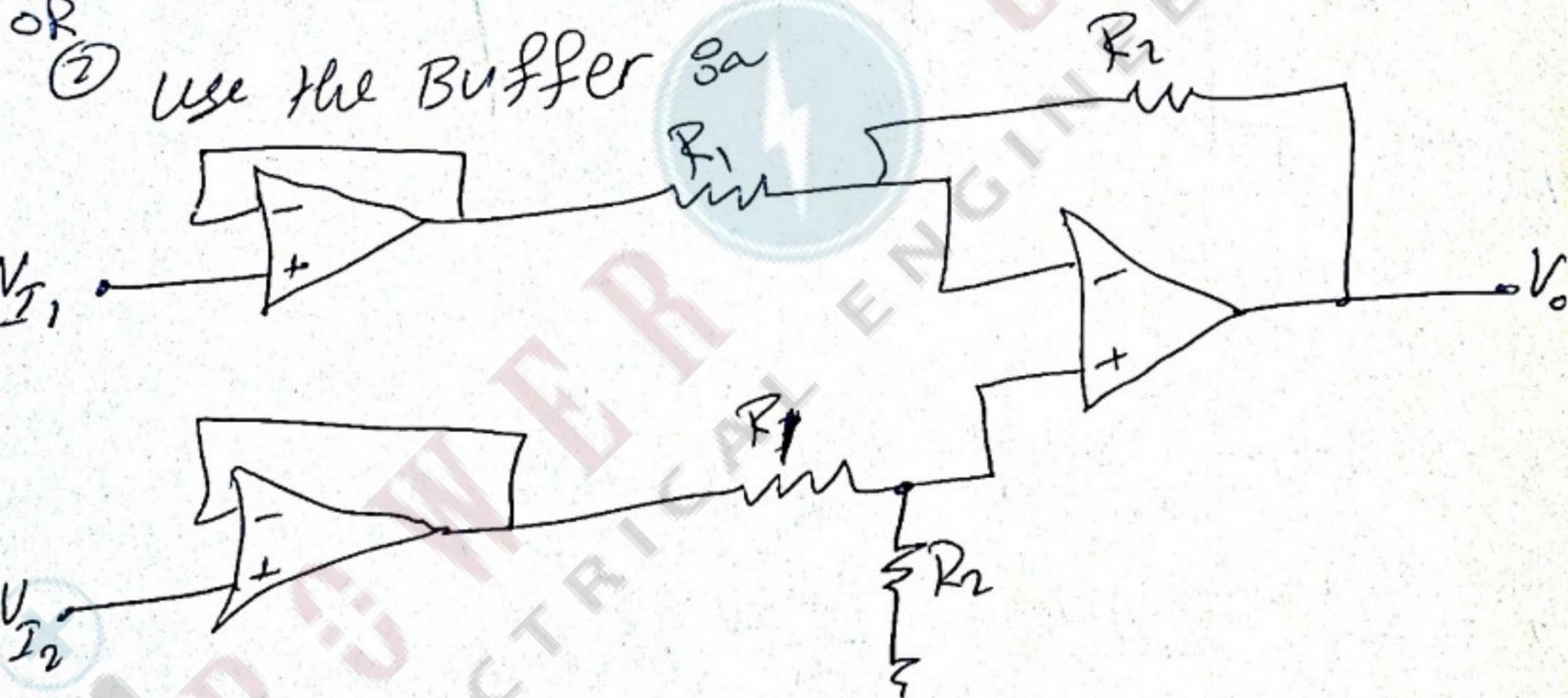


$$\Rightarrow R_{in} = \infty \quad \text{good}$$

but this solution solve the (R_{in}) Problem but it does not solve the gain $(\frac{R_2}{R_1})$ Problem

OR ③ Use (Instrumentation) Amplifier

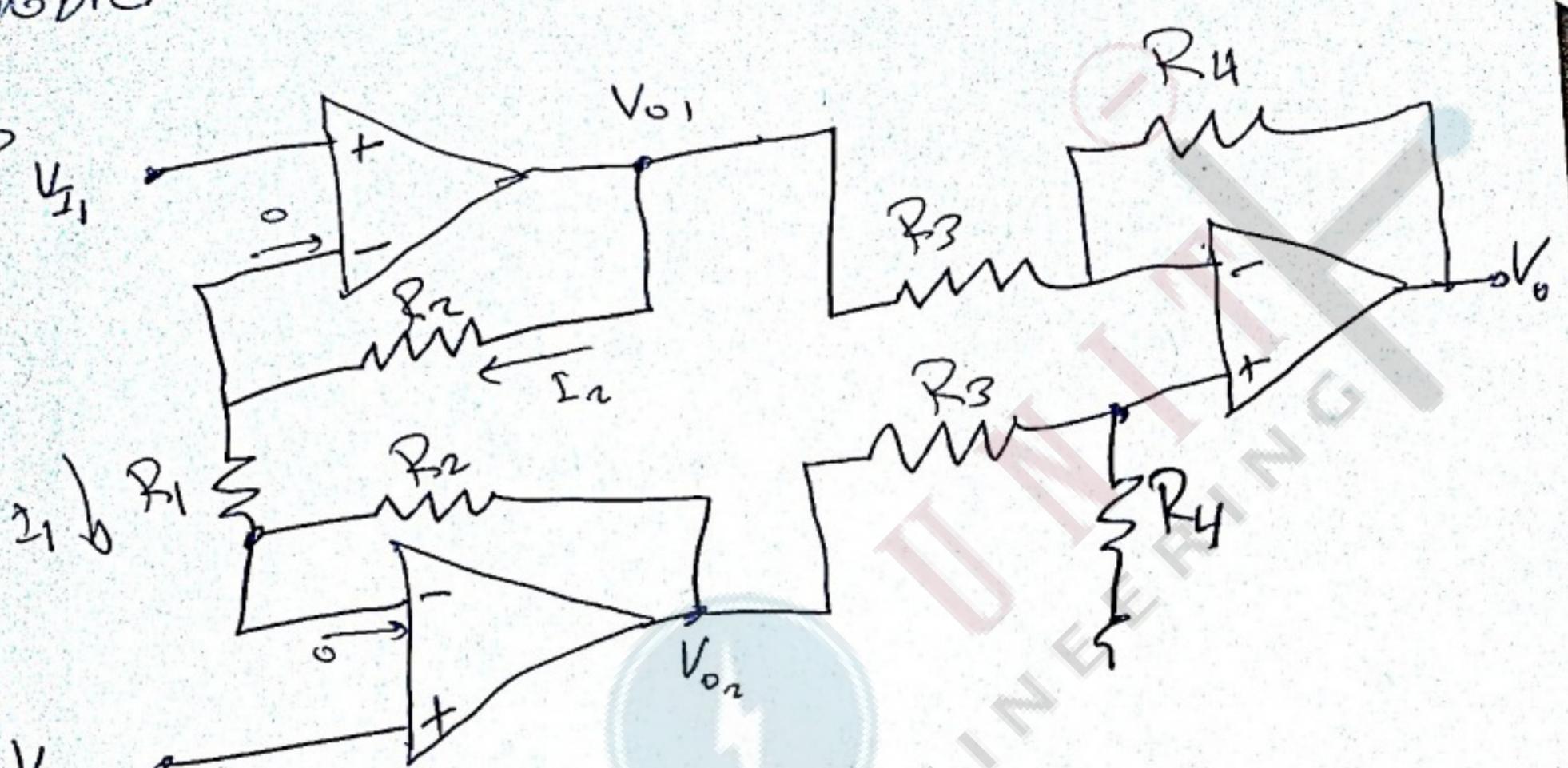\Rightarrow $\boxed{8}$ Instrumentation Amplifier \Rightarrow
 use \Rightarrow as a difference AMP. to solve (R_{in}) and gain $(\frac{R_4}{R_3})$ \rightarrow Integre
 problems.



$R_{in} = \infty$ #

$$V_{O1} = \left(1 + \frac{R_2}{R_1}\right) V_{I1} - \frac{R_2}{R_1} V_{I2}$$

$$V_{O2} = \left(1 + \frac{R_2}{R_1}\right) V_{I2} - \frac{R_2}{R_1} V_{I1}$$

$$\Rightarrow V_O = \frac{R_4}{R_3} (V_{O2} - V_{O1})$$

$$\Rightarrow V_O = \frac{R_4}{R_3} \left(1 + 2 \frac{R_2}{R_1}\right) (V_{I2} - V_{I1})$$


R_2, R_3, R_4 are constant, R_1 only variable

\Rightarrow The user can control the gain by change only (R_1) , \Rightarrow good design.

$R_{in} = \infty$

Integrator and differentiator


→ Integrator

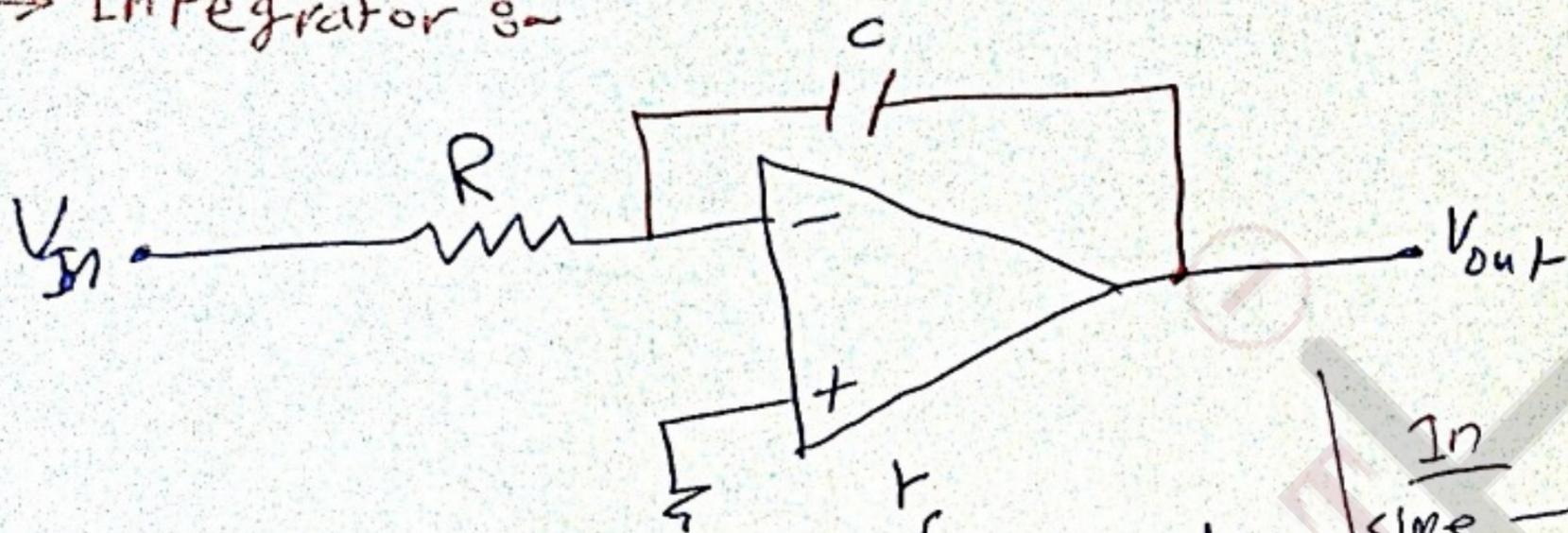

$$V_{out}(t) = V_c - \frac{1}{RC} \int_0^t V_{in}(t) \cdot dt$$

$\frac{In}{\text{sine}} \rightarrow \frac{out}{\text{sine lead } \frac{\pi}{2}}$
 $\text{square} \rightarrow \text{saw.}$

→ Differentiator

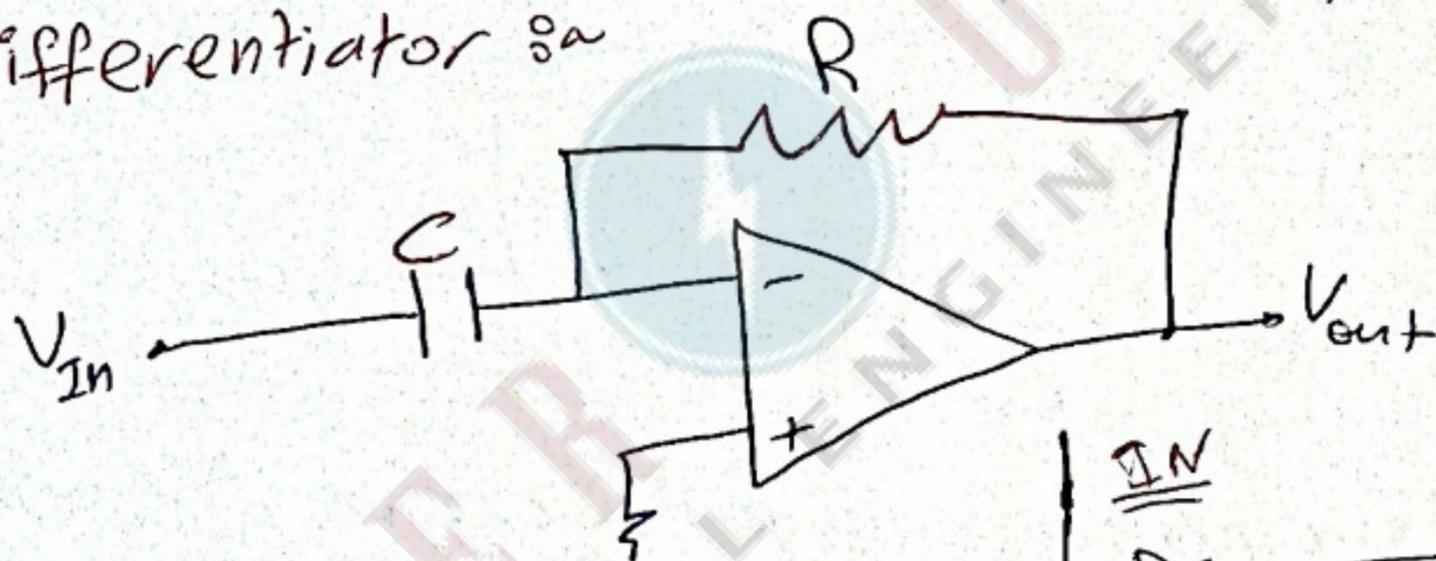


$$V_{out}(s) = -sCR V_I(s)$$

$$V_{out}(t) = -RC \frac{dV_I(t)}{dt}$$

<u>IN</u>	<u>OUT</u>
DC	Zero
SIN	SINE lead $\frac{\pi}{2}$
SQW	SQUARE

EX 1:-

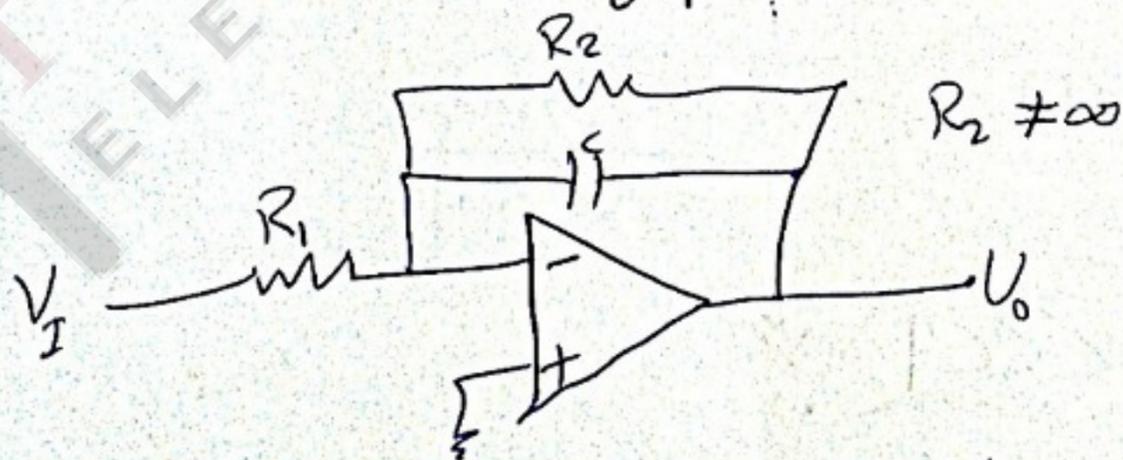

What is the condition that make this CKT an integrator

$$\Rightarrow \frac{V_O(s)}{V_I(s)} = -\frac{R_2 \parallel \frac{1}{sC}}{R_1} = -\frac{R_2 \times \frac{1}{sC}}{R_2 + \frac{1}{sC}} \cdot \frac{R_1}{R_1}$$

$$\Rightarrow = - \frac{R_2 + \frac{1}{sC}}{R_1 (R_2 + \frac{1}{sC})} \times \frac{sC}{sC}$$


$$\Rightarrow = \frac{-R_2}{R_1 (R_2 sC + 1)} \Rightarrow \frac{-1}{R_1 sC}$$

$$\Rightarrow \boxed{R_2 sC \gg 1} \#$$

this mean this work for High freq. #

Ex

How is

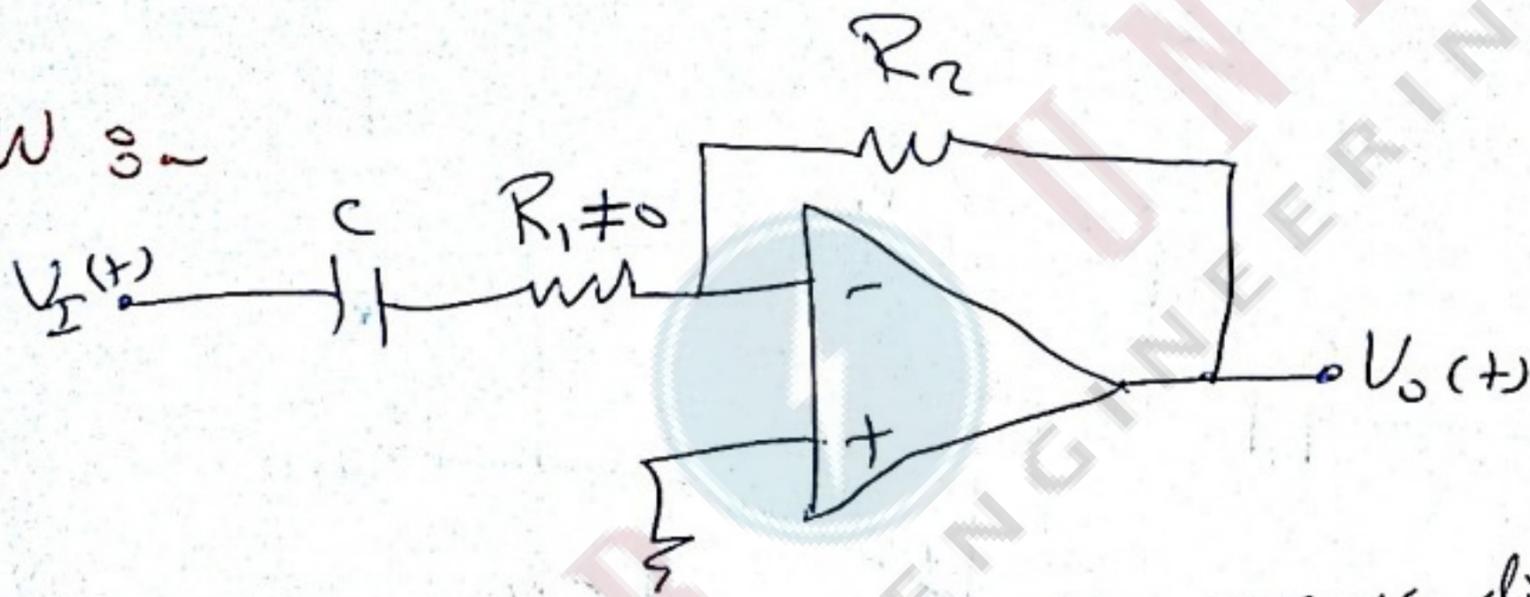

What is the condition to make this ckt as differentiator?

$$\Rightarrow \frac{V_O(s)}{V_I(s)} = - \frac{R_2}{R_1 + \frac{1}{sC}} \xrightarrow{\frac{sC}{sC}} \Rightarrow \frac{V_O(s)}{V_I(s)} = - \frac{R_2 sC}{R_1 sC + 1}$$


$$\Rightarrow V_O(s) = - \frac{R_2 sC V_I(s)}{R_1 sC + 1}$$

$$\Rightarrow \boxed{R_1 sC \ll 1} \#$$



\Rightarrow this # mean this work for low freq. #

Precision half-wave rectifier

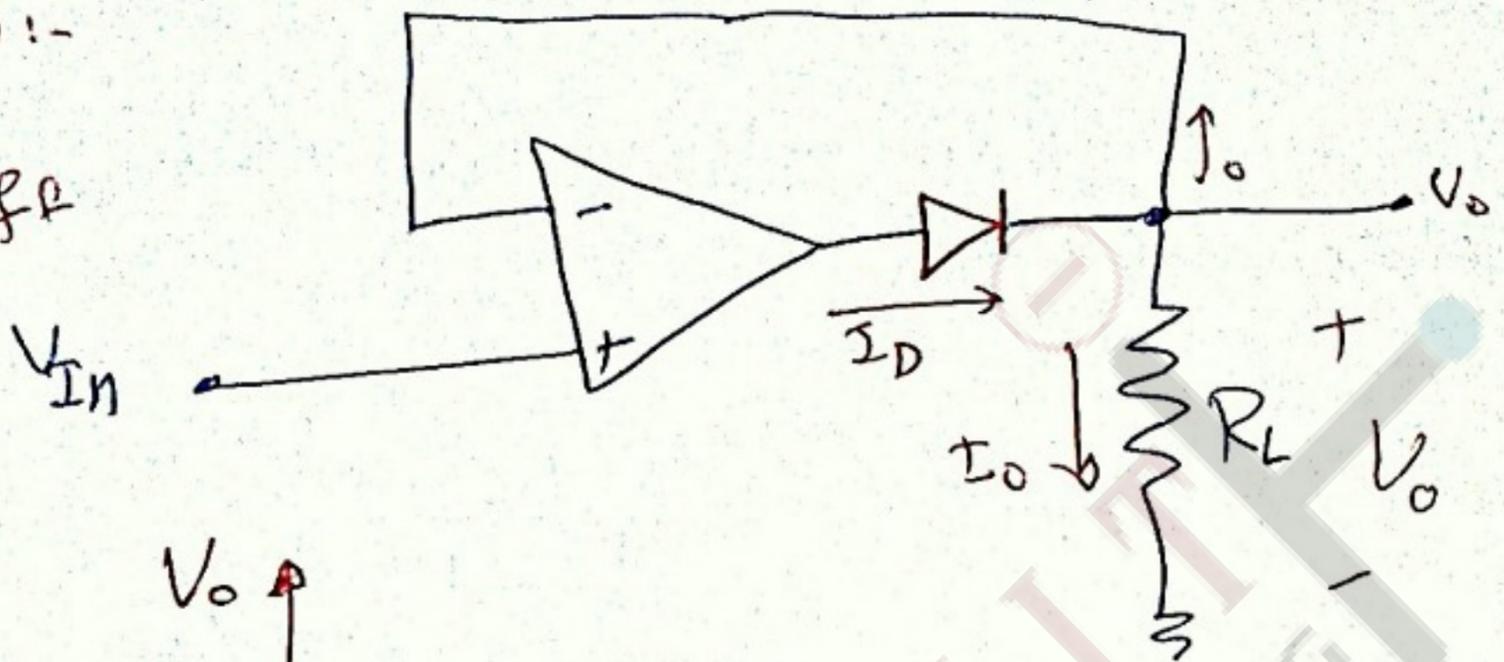- Diode on :- $V_o = V_L$
- Diode off $V_o = 0$



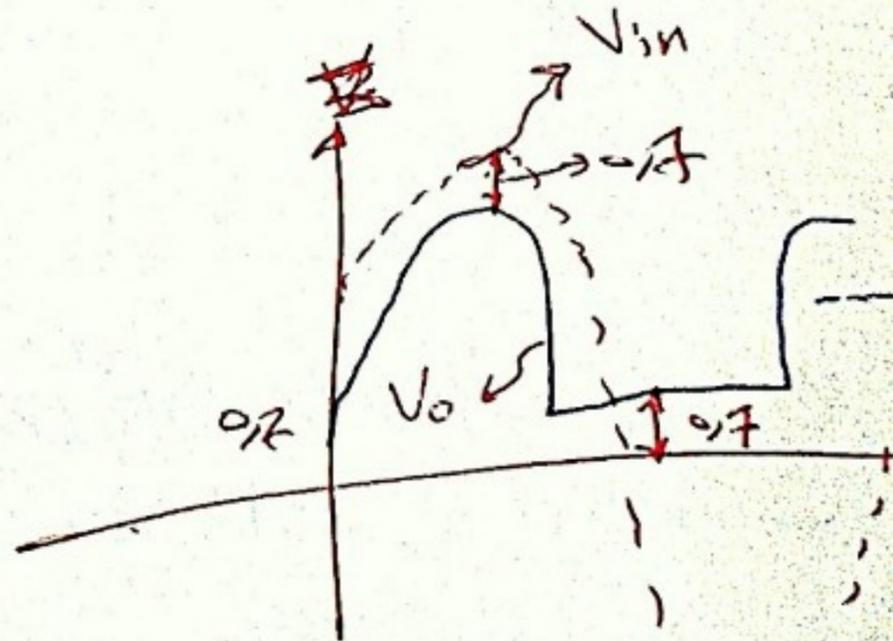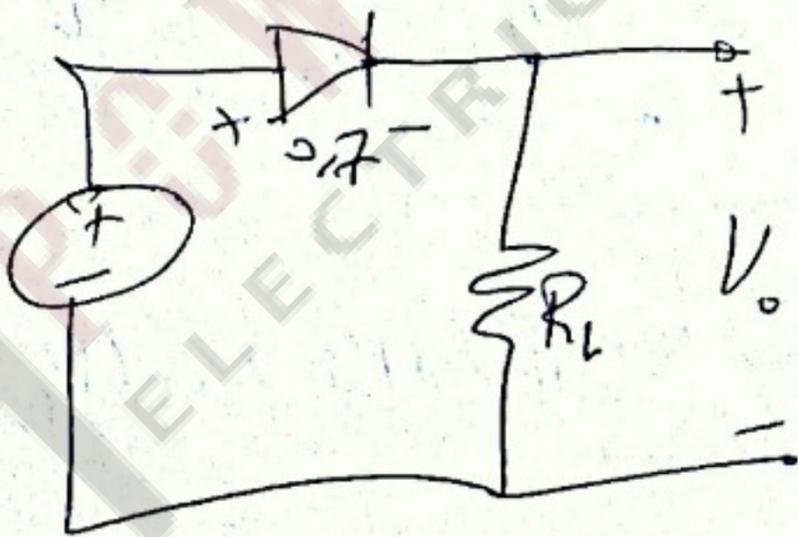Half wave → V_o [drop voltage (0.7)]
 الاستارية في إلكترونيات 1 → (electronics 1)




~~Diode on~~
~~to~~

Rectifier → drop on (إلكترونيات 1) →

Reference Voltage Source

→ In typical voltage source we have problem

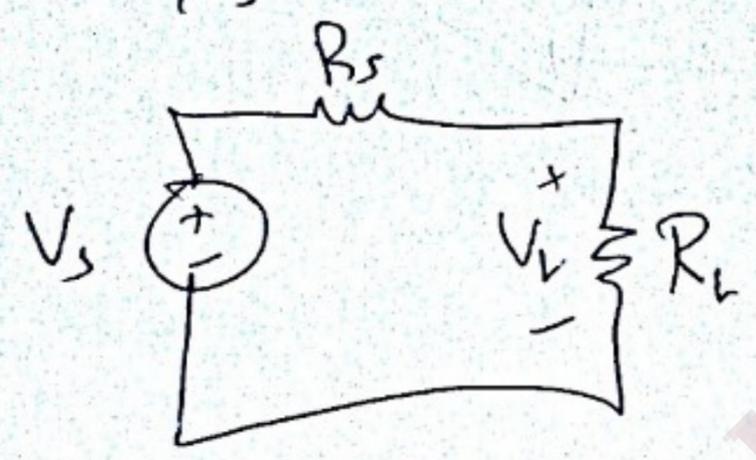- * (A) load effect $\Rightarrow V_L$ will change with change (R_L) due to R_S




$$\Rightarrow V_L = V_s \frac{R_L}{R_L + R_S}$$

\Rightarrow Load effect problem. #

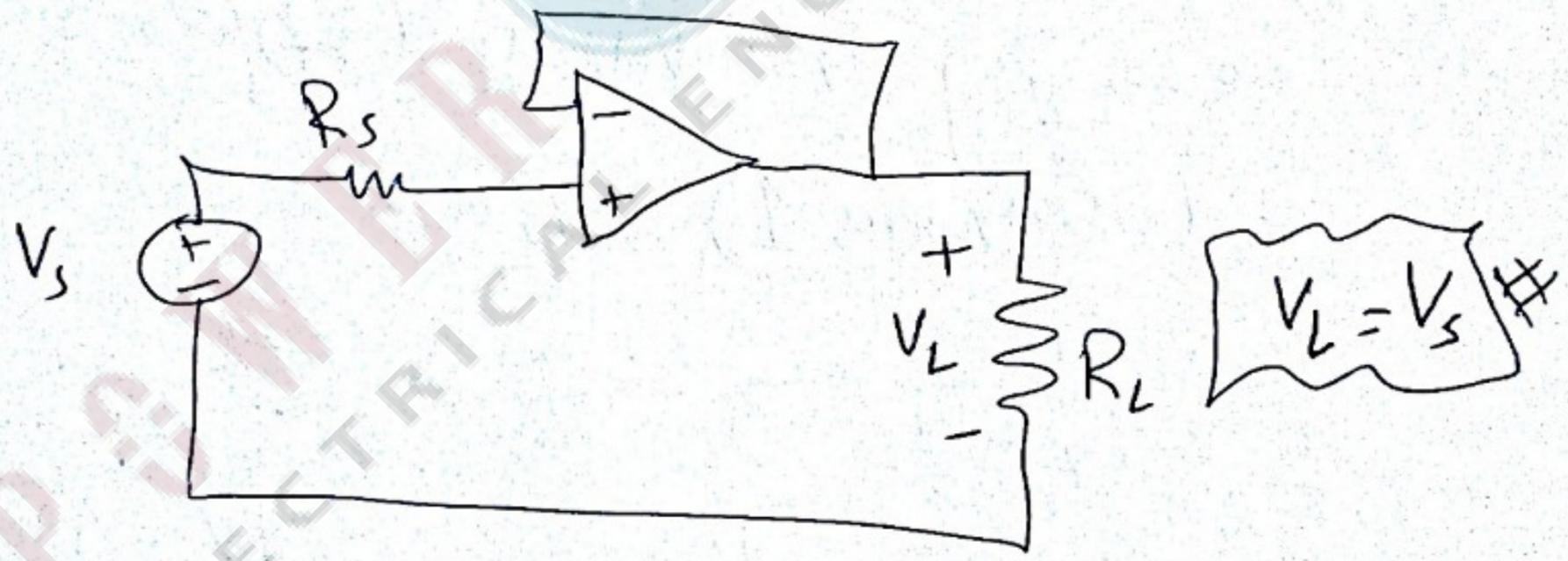* (B) (V_s) is not a fixed voltage exactly.

Solution 1



→ You can solve this problem "load effect" by using the Buffer.



but we have other problem (B) it's the (V_s) not a fixed voltage exactly.

Solution 2

→ You can use the diode. :-

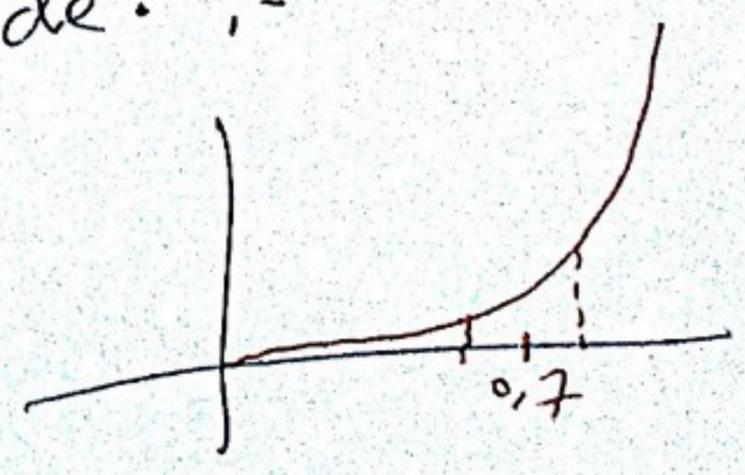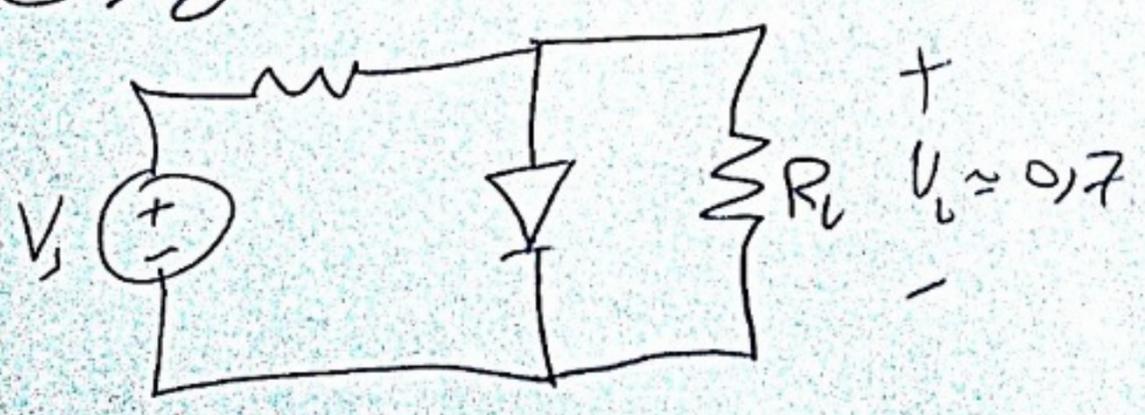


solution by using the diode we have \leq Problem

(A) $V_s \Rightarrow I_D \Rightarrow V_D$

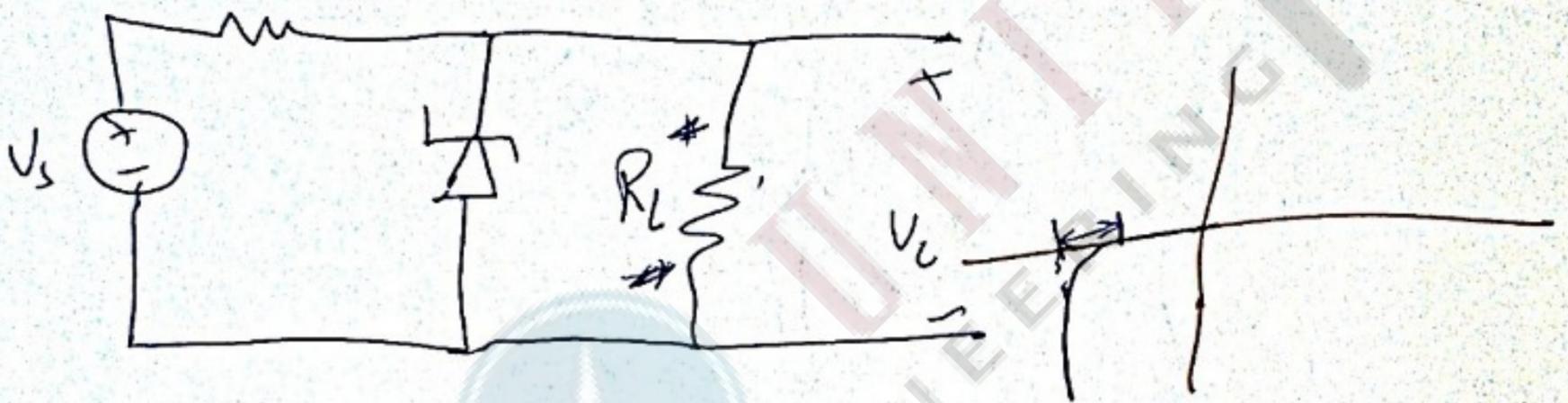(B) some time we need $V_L > 0.7$

solution (3) \rightarrow Use Zener Diode sa



Problem:-


(A) V_s, I_Z, V_o

but less than in solution 2 by the Diode.

(B) also some time we need $V_L > V_Z$

(C) we have the range of R_L max and min.


solution (4)

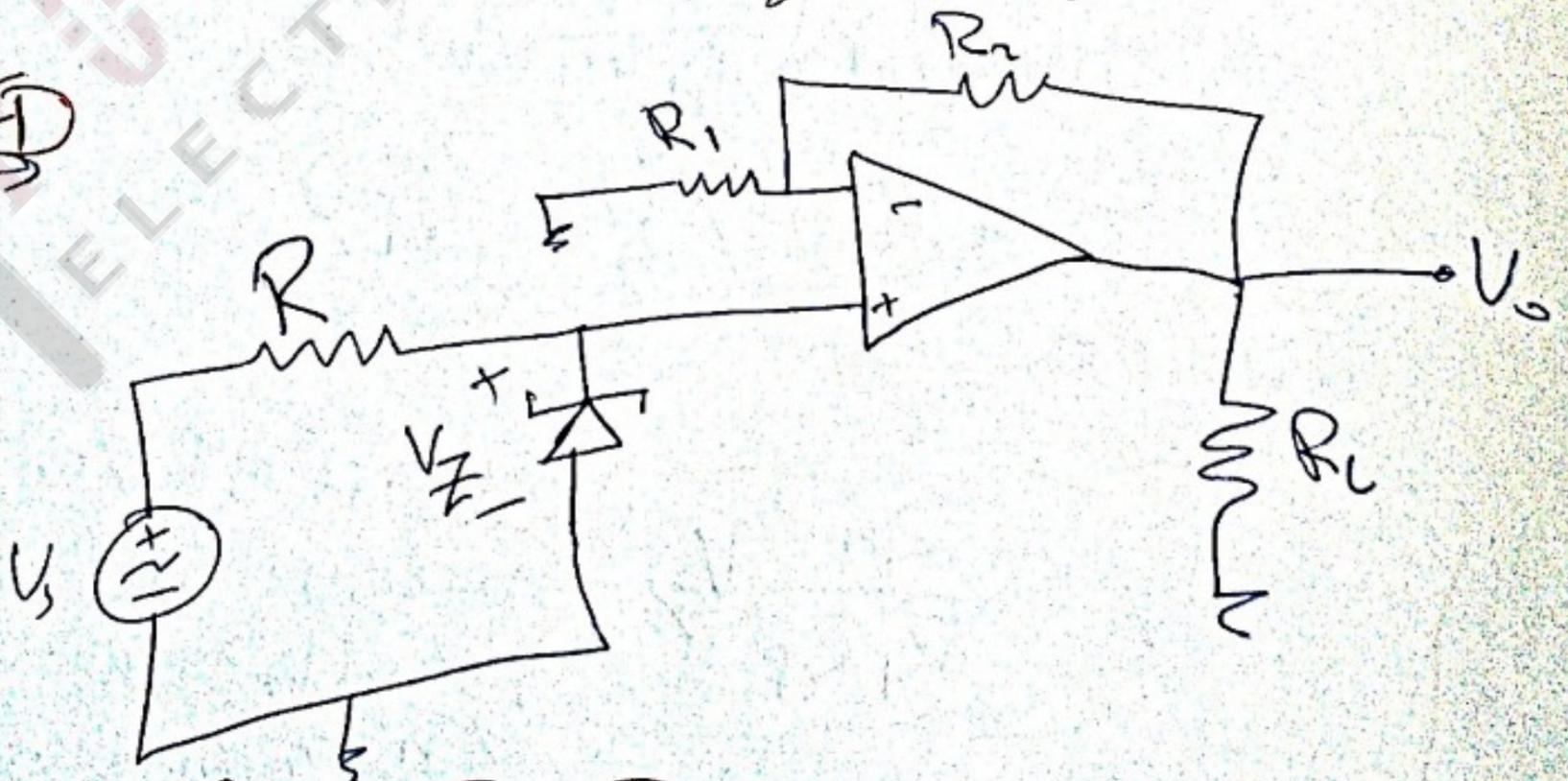

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_Z = V_L \quad \#$$

but in solution #4 only solve the Problem #B in solution #1, 2, 3

solution #5

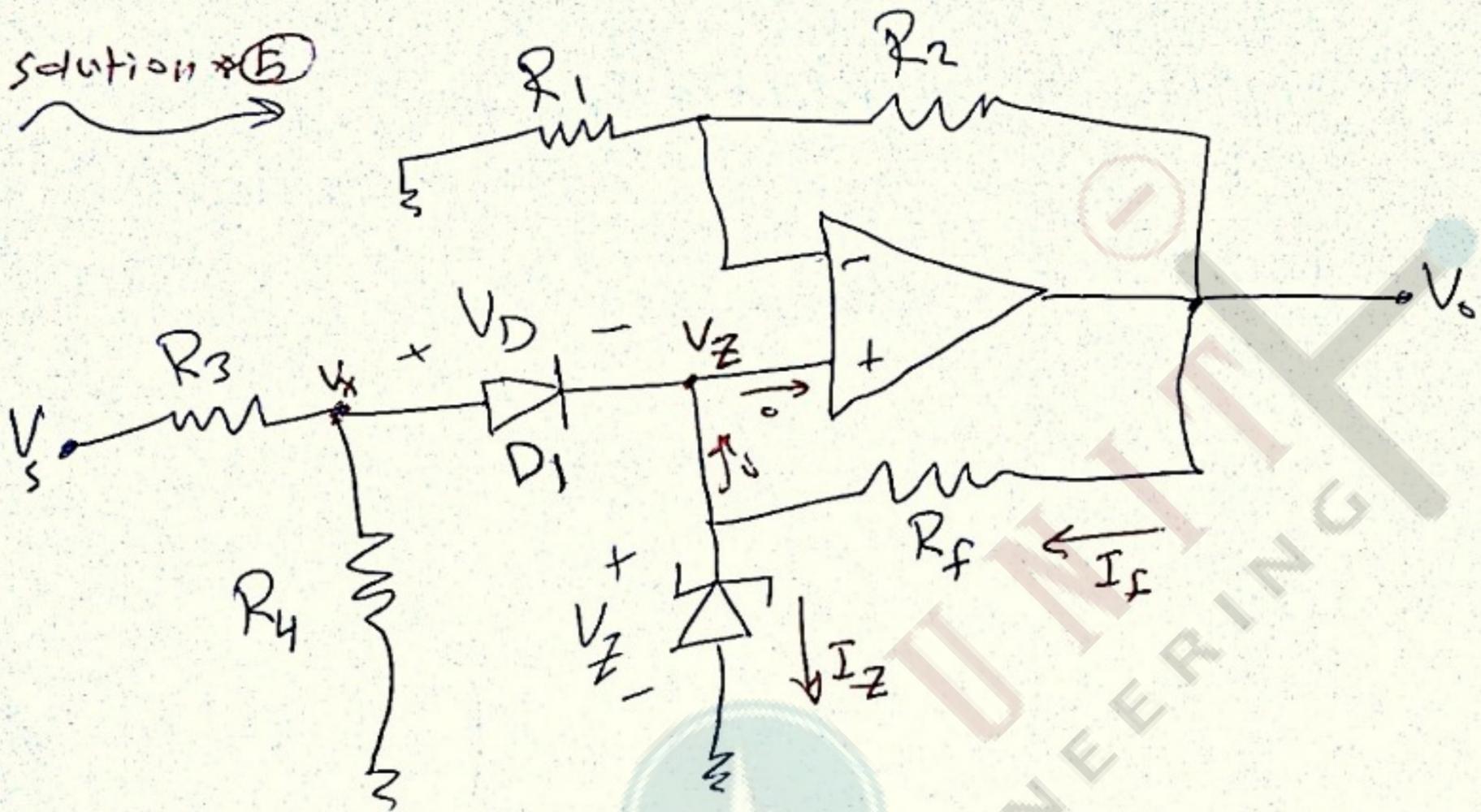

$\Rightarrow D_1$ is on if $(V_x - V_Z) > V_f$

$$V_x = V_s \times \frac{R_4}{R_3 + R_4}$$

then the voltage V_Z will be generated across Zener Diode.

\Rightarrow Increase (V_s) until D_1 is on then turn-off (V_s)

$$\Rightarrow D_1 \text{ off. } \Rightarrow V_0 = V_Z \left(1 + \frac{R_2}{R_1}\right)$$


$$\Rightarrow I_f = \frac{V_0 - V_Z}{R_f}$$

$$\Rightarrow I_f = I_Z = \frac{R_2}{R_1 R_f} V_Z$$

(V_0) is a fixed value because it's indep. on the (V_I) and you can control (V_0) .

and you can control the (V_0) by R_2 and R_1 and R_f etc.

Square - wave generator

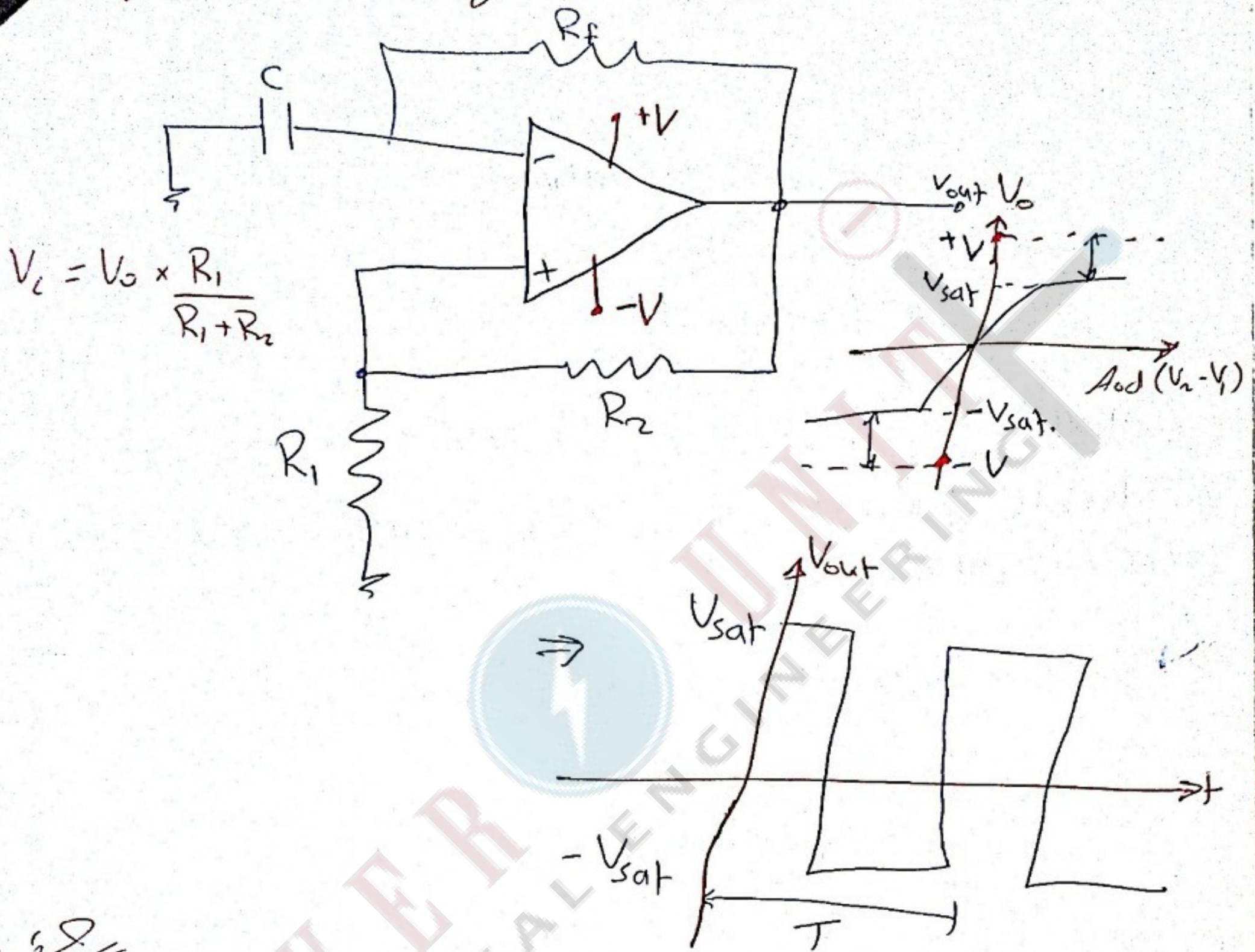

$$T = 2 R_f C \ln \left(\frac{1 + \lambda}{1 - \lambda} \right)$$

where $\lambda = \frac{R_1}{R_1 + R_2}$

$$V_0 = +V_{sat} \text{ if } V_2 > V_1$$

$$V_0 = -V_{sat} \text{ if } V_2 < V_1$$

(C) is charge if $V_0 > V_c$

(C) is discharge if $V_0 < V_c$

* feedback and stability in diodes

* Type of feedback (fb) :-

- ① Positive fb
- ② Negative fb

① +ve fb use in «oscillator».


② -ve fb use in «Stability».

Now we will study only -ve feedback.

* Advantage of -ve feedback «-ve fb» :-

① Stable gain :- \Rightarrow The gain is insensitive to the transistor parameters ($\beta, I_B, I_C, I_E, g_m, \dots$ etc.).

② -ve fb increasing the Bandwidth :-

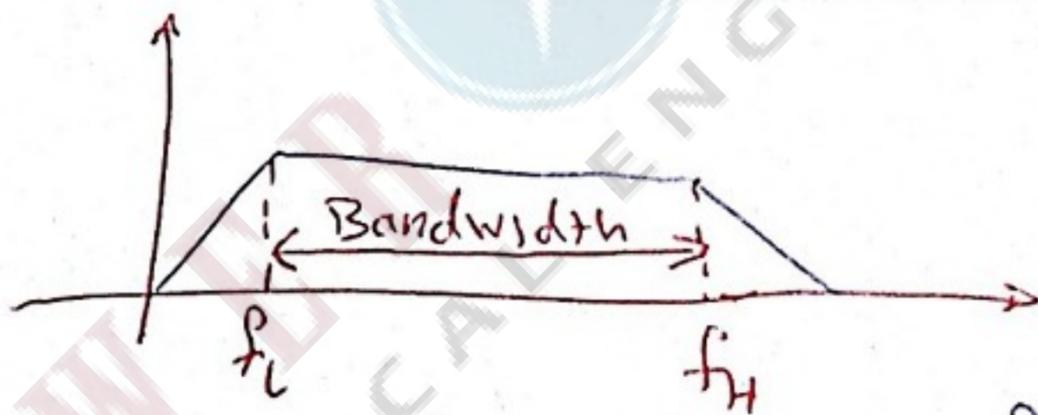

$$\text{Bandwidth} = B = f_H - f_L$$

③ -ve fb increasing the Signal to Noise Ratio :-

$$\text{SNR} = \frac{\text{Signal Power}}{\text{Noise Power}}$$


④ -ve fb ~~reduces~~ reduces the Non-linear distortion :- which occurs due to large signal

⑤ -ve fb can control & increase or decrease the input and output impedances.

advantage for -ve feedback is

① -ve f.b reduces the gain.

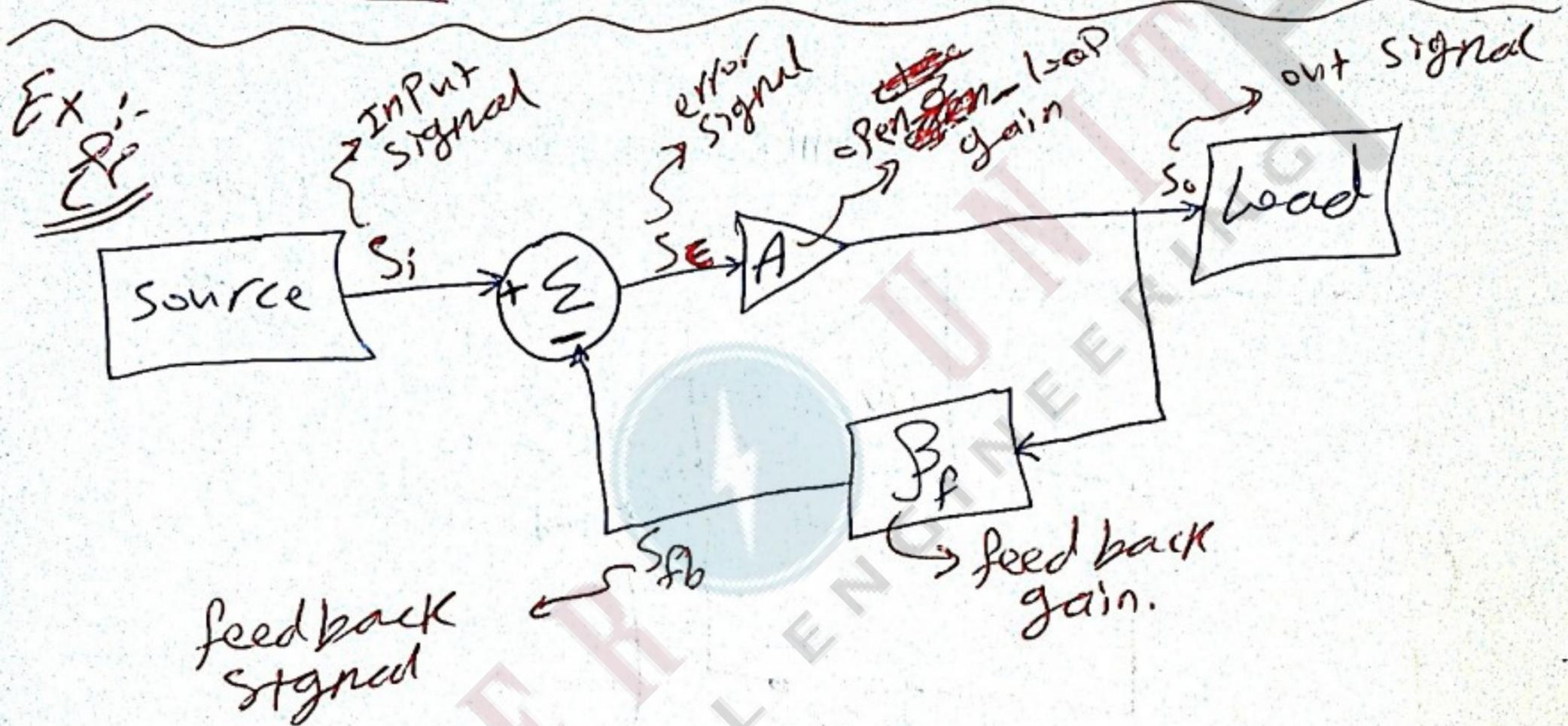② at high freq. the -ve feedback may result in unstable circuit.



$$\Rightarrow S_o = A S_e$$

$$S_e = S_i - S_{fb}$$

$$S_{fb} = \beta_f S_o$$

$$\Rightarrow S_o = A (S_i - \beta_f S_o) \Rightarrow S_o (1 + A \beta_f) = A S_i$$

$$\Rightarrow A_f = \frac{S_o}{S_i} = \frac{A}{1 + A \beta_f}$$

gain without feedback

gain with feedback

usually ~~the~~ gain $\beta_f A \gg 1 \Rightarrow A_f = \frac{1}{\beta_f} \Rightarrow$ stable gain

but the A_f is low by the value $(\frac{1}{1 + A \beta_f})$

* feedback and stability :-

* Type of feedback «fb» :- ① Positive fb
② Negative fb

① +ve fb use in «oscillator».


② -ve fb use in «stability».

Now we will study only -ve feedback.

* Advantage of -ve feedback «-ve fb» :-

① Stable gain :- \Rightarrow The gain is insensitive to the transistor parameters ($\beta, I_B, I_C, I_E, g_m, \dots$ etc.).

② -ve fb increasing the Bandwidth :-

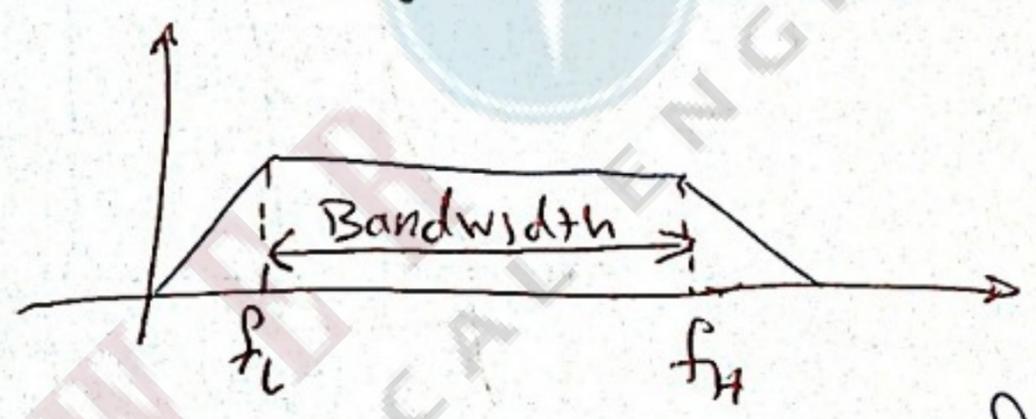

$$\text{Bandwidth} = B = f_H - f_L$$

③ -ve fb increasing the Signal to Noise ratio :-

$$\text{SNR} = \frac{\text{Signal Power}}{\text{Noise Power}}$$


④ -ve fb ~~reduces~~ reduces the Non-linear distortion :- which occurs due to large signal

⑤ -ve fb can control & increase or decrease the INPUT and output Impedances.

Advantage for -ve feedback is

① -ve f.b reduces the gain.

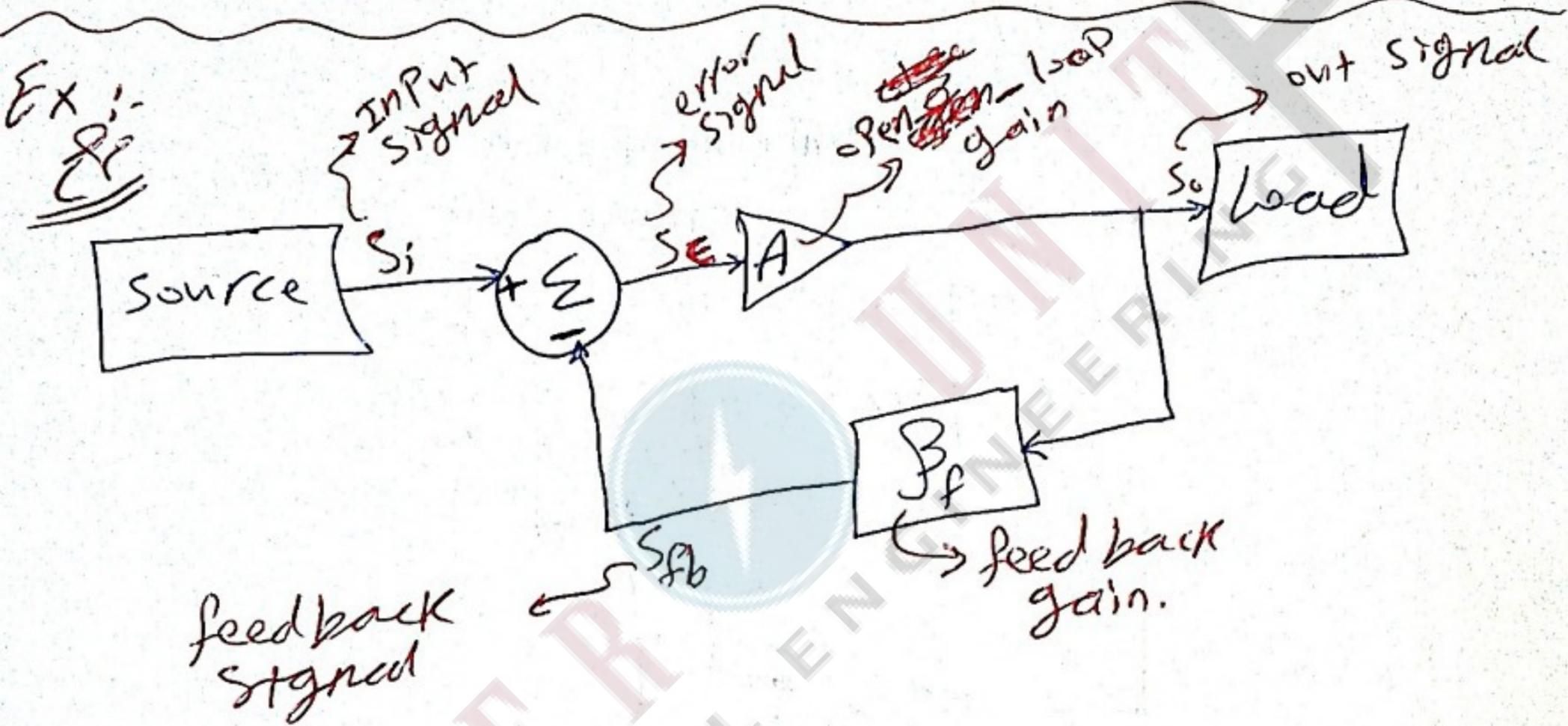② at high freq. the -ve feedback may result in unstable circuit.



$$\Rightarrow S_o = A S_e$$

$$S_e = S_i - S_{fb}$$

$$S_{fb} = \beta_f S_o$$

$$\Rightarrow S_o = A (S_i - \beta_f S_o) \Rightarrow S_o (1 + A \beta_f) = A S_i$$

$$\Rightarrow A_f = \frac{S_o}{S_i} = \frac{A}{1 + A \beta_f}$$

gain with feedback

gain without feedback

usually ~~gain~~

$$\beta_f A \gg 1 \Rightarrow A_f = \frac{1}{\beta_f} \Rightarrow \text{stable gain}$$

but the A_f is low by the value $(\frac{1}{1 + A \beta_f})$

gain \times Bandwidth = constant

* Feedback topologies (configuration) ^{في}
 ((connection between input and output))



Series - shunt

INPUT SERIES

OUTPUT SHUNT (shunt = Parallel)

Voltage gain \Rightarrow

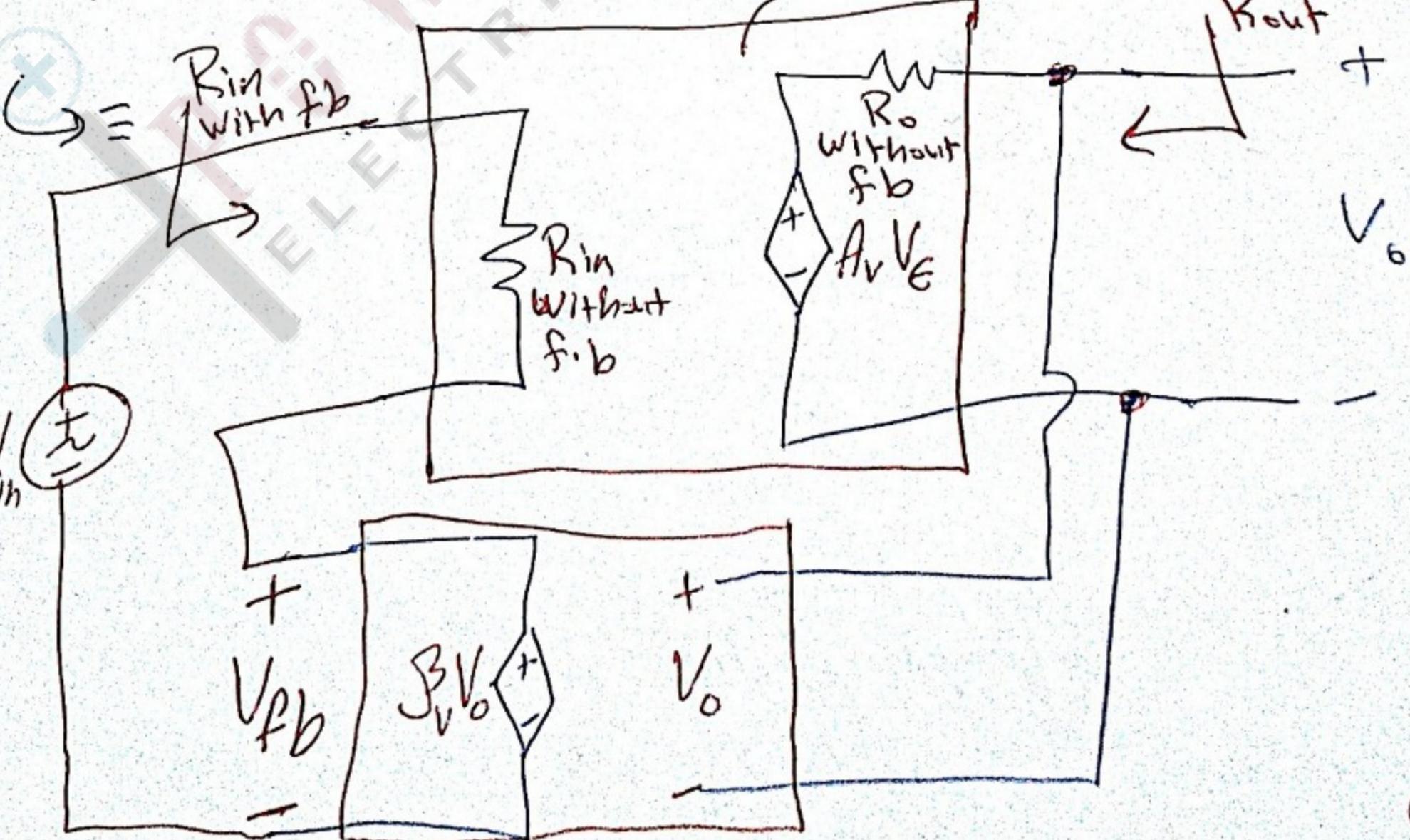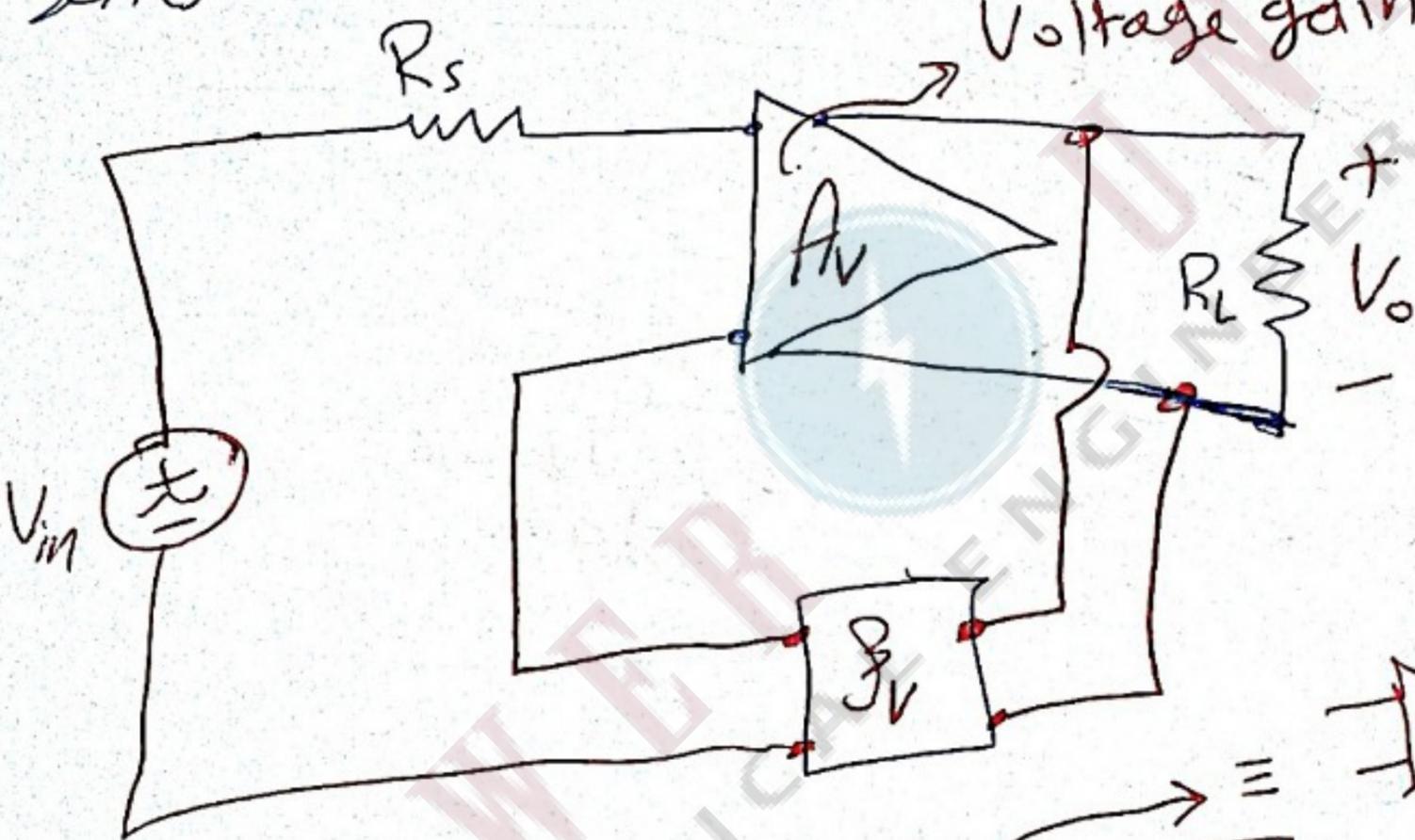لا تشارك (IN) في
 قياس عن ثغور
 واد (out) كما ان
 ثغور.



⇒ in Series - shunt β_a

① $A_{V_{fb}} = \frac{A_V}{1 + \beta_V A_V}$

where :-

$A_{V_{fb}}$:- gain with feedback

A_V :- gain without feedback.

gain ↓ decrease with fb

factor $(1 + \beta_V A_V)$

② $R_{in_{fb}} = R_{in} (1 + \beta_V A_V)$

where

$R_{in_{fb}}$:- R_{in} with feedback

R_{in} :- R_{in} without feedback.

R_{in} ↑ increase with fb


the factor = $(1 + \beta_V A_V)$

③ $R_{out_{fb}} = \frac{R_{out}}{1 + \beta_V A_V}$

R_{out} ↓ decrease with fb

the factor $(1 + \beta_V A_V)$

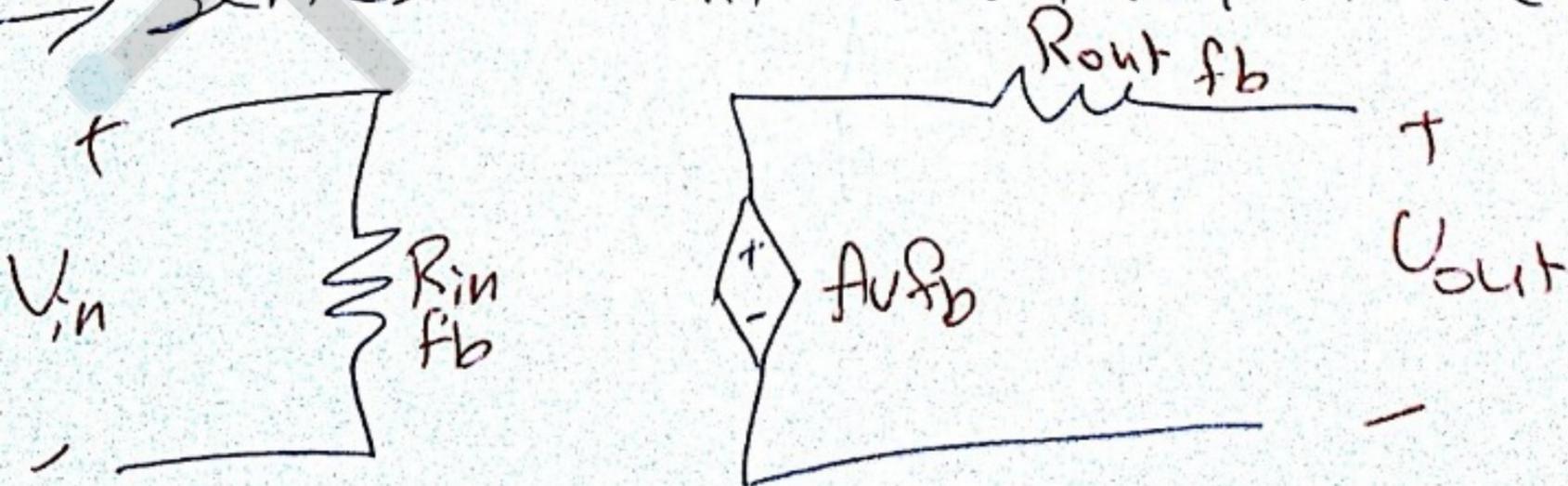⇒ Series - shunt as a two Port Network :-




where $R_{in_{fb}}$, $R_{out_{fb}}$, $A_{V_{fb}}$ as the up equation.

Shunt - series O_w

Input shunt
(Parallel)

output series

current gain $\frac{i_o}{i_s}$

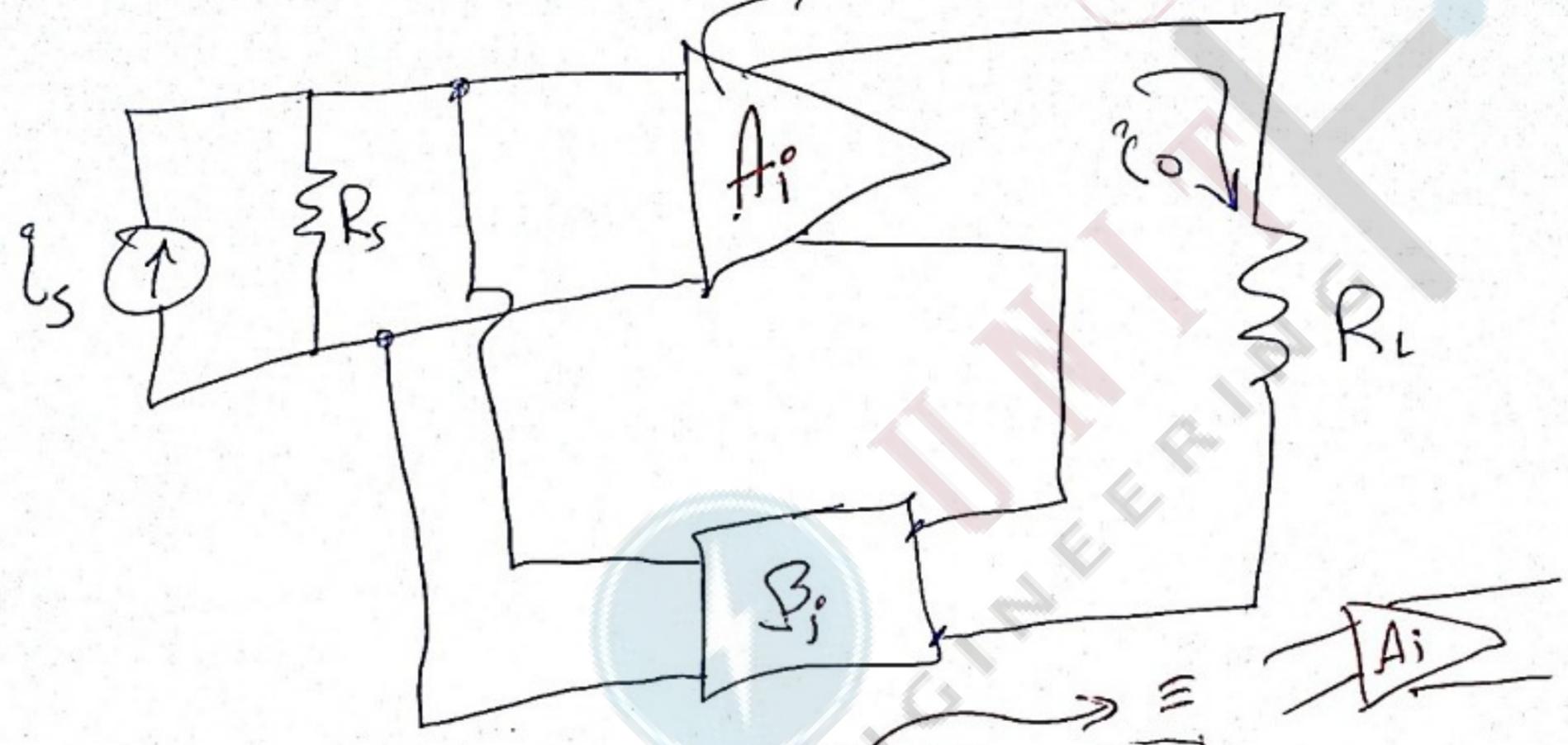

In Shunt - series

① $A_{i,fb} = \frac{A_i}{1 + \beta_i A_i}$

current gain ~~decreases~~ with feedback will decrease by the factor $1 + \beta_i A_i$


② $R_{in,fb} = \frac{R_{in}}{1 + \beta_i A_i}$

R_{in} with fb will decrease by the factor $1 + \beta_i A_i$

③ $R_{out,fb} = R_{out} (1 + \beta_i A_i)$

R_{out} with fb will increase by a factor $1 + \beta_i A_i$

⇒ Shunt-series as a two Port Network :-

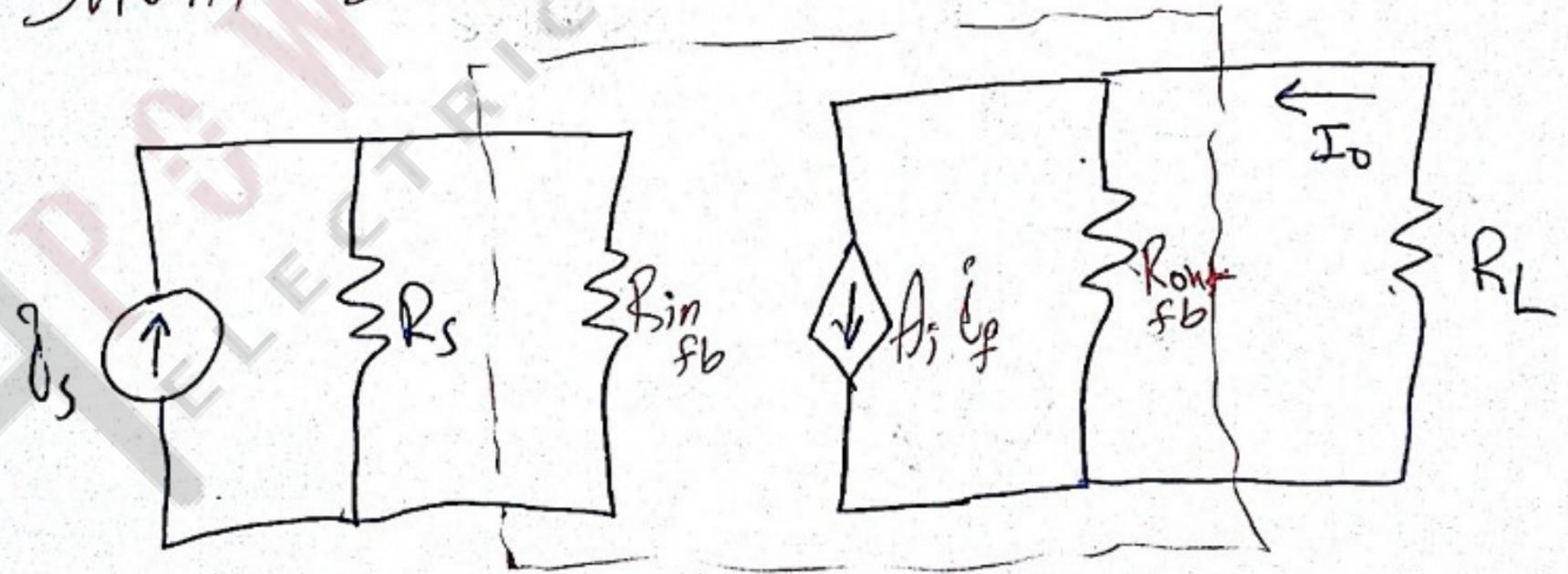

where $R_{in,fb}$, $R_{out,fb}$, $A_{i,fb}$ as the UP equation


3 Series-Series ∞ a
 output series

INPUT series

$A_g = \text{conductance gain}$
 $\equiv \left(\frac{1}{R}\right) \cdot V$
 $A = \frac{I}{V} \text{ a/y}$



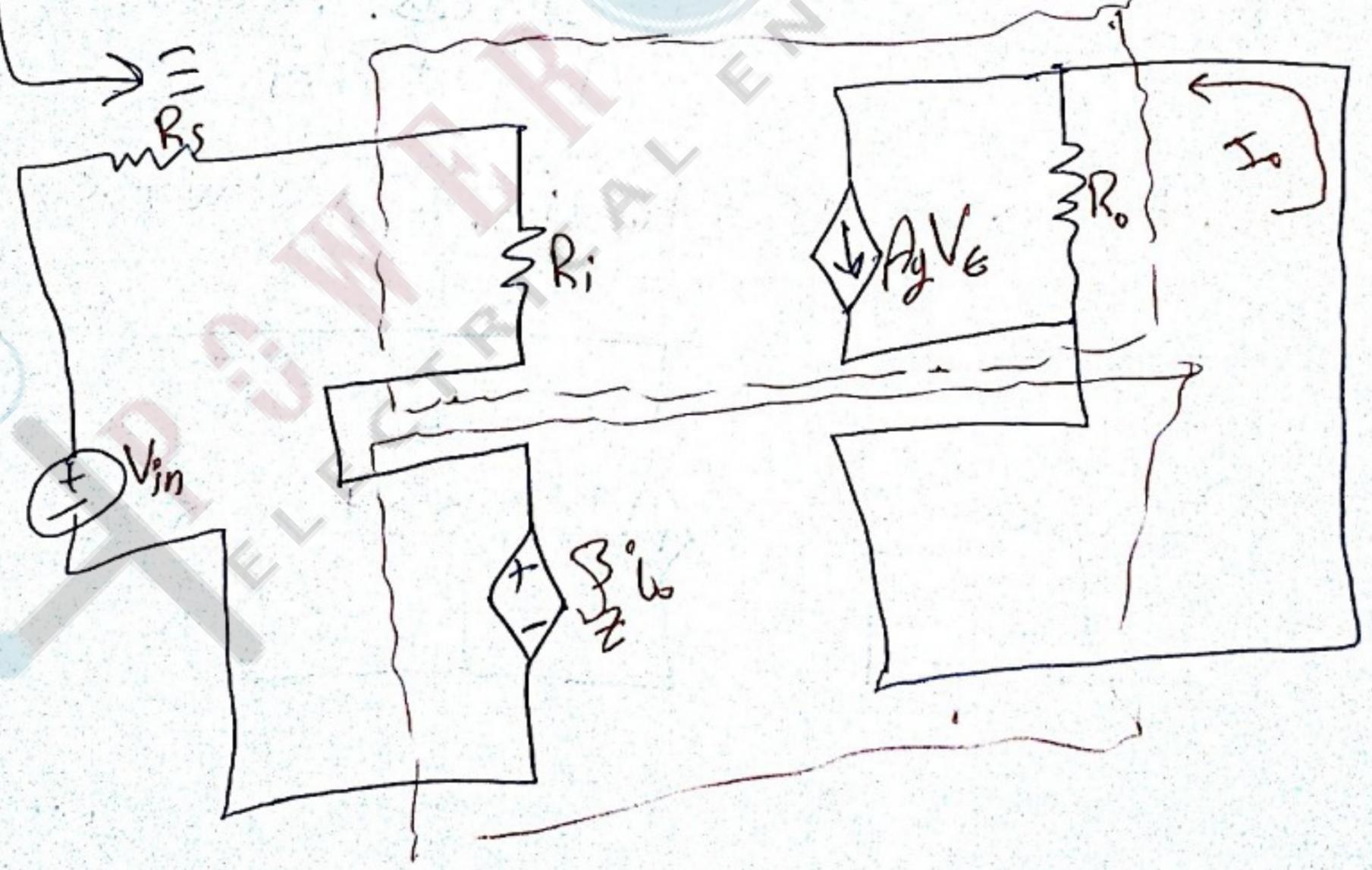$\equiv \text{Impedance gain}$
 $\equiv (R) \cdot I$
 $(A = \frac{V}{I}) \text{ a/y}$




Series - series 3~

① $A_{g_{fb}} = \frac{A_g}{1 + \beta_z A_g}$ \Rightarrow gain with feed back will decrease ~~by~~ by the factor $1 + \beta_z A_g$

② $R_{in_{fb}} = R_{in} (1 + \beta_z A_g)$ \Rightarrow R_{in} with feed back will increase \uparrow by the factor $1 + \beta_z A_g$

③ $R_{out_{fb}} = R_{out} (1 + \beta_z A_g)$ \Rightarrow R_{out} with ~~with~~ with fb will increase \uparrow by the factor $1 + \beta_z A_g$

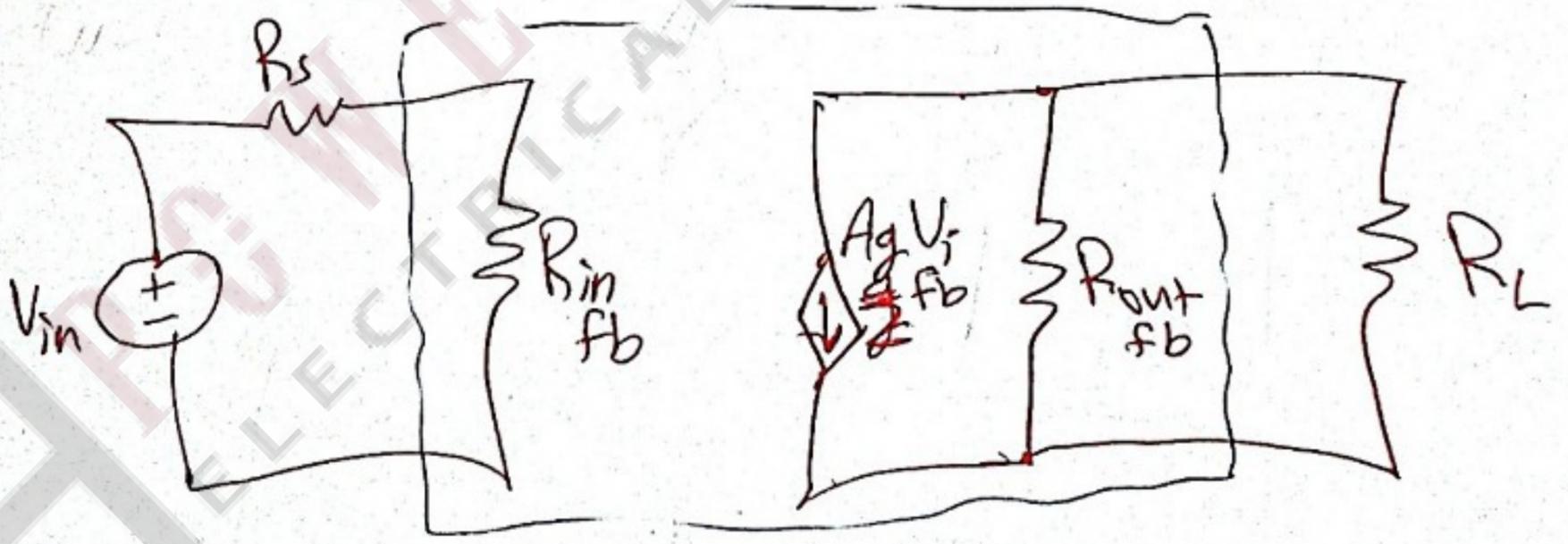\Rightarrow series - series as a two port Network :-



4] shunt - shunt \approx

INPUT shunt \equiv Parallel

output shunt \equiv Parallel

