


Circuits II


Notebook

Dr.Ghazi Alsukkar

By: Asma' Hakouz

Spring-2013

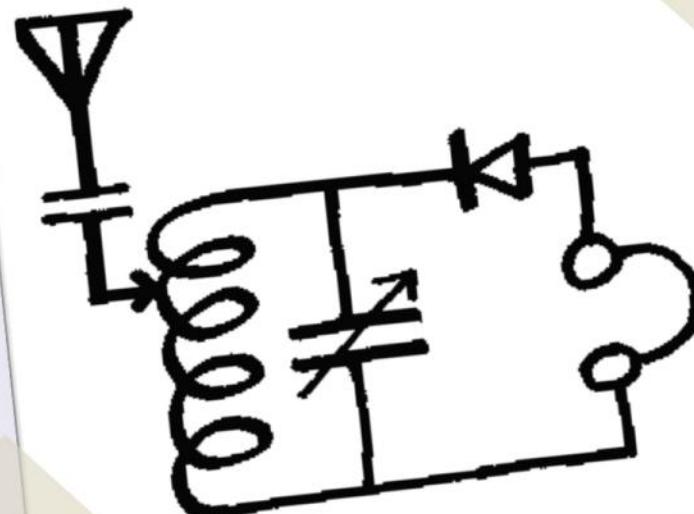

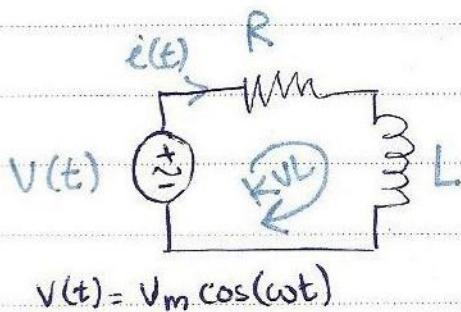

$$\text{KVL: } -V(t) + i(t)R + L \frac{di(t)}{dt} = 0 \dots \textcircled{1}$$

\rightarrow 1st order differential eqn.

$$V(t) = V_m e^{j(\omega t + \theta)}$$

$$V_r(t) = V_m \cos(\omega t + \theta)$$

+ linear CKT -

$$i(t) = I_m e^{j(\omega t + \phi)}$$

$$i_r(t) = I_m \cos(\omega t + \phi)$$

- linear CKT means that both input & output ~~variables~~ have the same form!
- $V_r(t) = \text{Re}[V(t)] \triangleq \text{Real part of } V(t) \equiv V_m \cos(\omega t + \theta)$

- Plug in 1:

$$R i(t) + L \frac{di}{dt} = V(t)$$

$$R I_m e^{j(\omega t + \phi)} + L I_m j\omega e^{j(\omega t + \phi)} = V_m e^{j(\omega t + \theta)}$$

$e^{j\omega t} \neq 0$

$$R(I_m e^{j\phi}) + j\omega L(I_m e^{j\phi}) = V_m e^{j\theta}$$

$$R I_m \angle \phi + j\omega L I_m \angle \phi = V_m \angle \theta$$

$$I_m \angle \phi (R + j\omega L) = V_m \angle \theta$$

Rectangular

$$I_m \angle \phi (\sqrt{R^2 + \omega^2 L^2} \angle \tan^{-1}(\frac{\omega L}{R})) = V_m \angle \theta$$

$$\therefore I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \dots \textcircled{2} \quad \& \quad \phi = \theta - \tan^{-1} \left(\frac{\omega L}{R} \right) \dots \textcircled{3}$$

$$\vec{I} = I_m \angle \phi$$

-from ② & ③

$$\vec{I} = \frac{V_m}{\sqrt{R^2 + w^2 L^2}} \angle \theta - \tan^{-1}\left(\frac{wL}{R}\right) \Rightarrow i(t) = \frac{V_m}{\sqrt{R^2 + w^2 L^2}} \left(\cos(wt + \theta - \tan^{-1}\left(\frac{wL}{R}\right)) \right)$$

time domain

• Phasor:-

$$i(t) = I_m \cos(wt + \phi) \Leftrightarrow \vec{I} = I_m \angle \phi \equiv I_m e^{j\phi} \equiv I_m \cos\phi + I_m \sin\phi$$

ex: a) $v_1(t) = 12 \cos(200t - 35^\circ)$

$$v_2(t) = -12 \cos(200t - 35^\circ)$$

find \vec{V}_1 & \vec{V}_2 \rightarrow the (-) sign means a phase shift by 180°

$$\vec{V}_1 = 12 \angle -35^\circ$$

$$\vec{V}_2 = -12 \angle -35^\circ \equiv 12 \angle 145^\circ$$

$(-35 + 180)$


b) $i_2(t) = 10 \sin(12t + 30^\circ)$, find \vec{I}_2 ?

first we have to transform sine to cosine:


$$i_2(t) = 10 \cos(12t + 30^\circ - 90^\circ) = 10 \cos(12t - 60^\circ)$$

$$\therefore \vec{I}_2 = 10 \angle -60^\circ$$

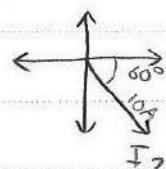* negative freq. means rotating clockwise!



1) Resistor:

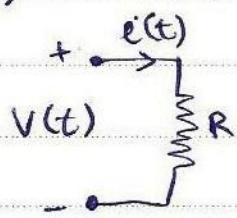

$$V(t) = i(t) \cdot R$$

$$\rightarrow V(t) = V_m \cos(wt + \theta)$$


$$\rightarrow i(t) = I_m \cos(wt + \phi)$$

$$\boxed{\vec{V} = \vec{I}R}$$


$$V_m \angle \theta = I_m R \angle \phi \dots \textcircled{1}$$

from ①:
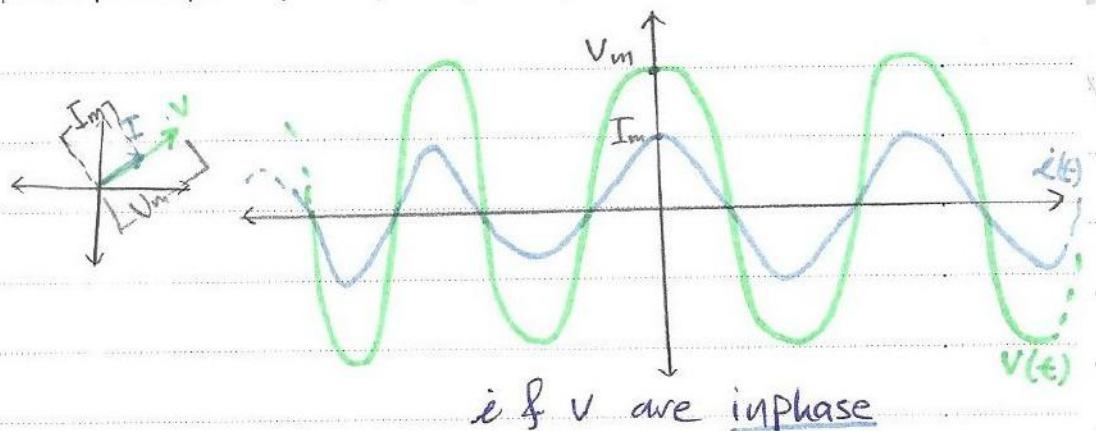
$$\phi = \theta \quad \text{and} \\ V_m = I_m \cdot R$$




2) Inductor:

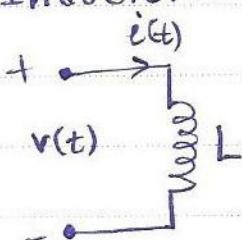


$$v(t) = L \frac{di}{dt} \Rightarrow V_m e^{j(\omega t + \theta)} = L I_m j \omega e^{j(\omega t + \phi)}$$

time
domain

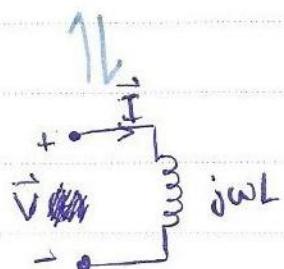
$$V_m \angle \theta = j\omega L I_m \angle \phi \\ \text{phase shift} = 90^\circ$$



$$\vec{V} = j\omega L \vec{I}$$

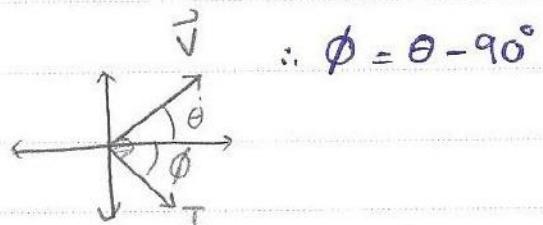



3) Capacitor:

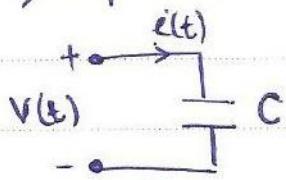

$$i(t) = C \frac{dv(t)}{dt} \Rightarrow I_m \angle \phi = j\omega c V_m \angle \theta$$

$$\therefore \phi = \theta + 90^\circ$$

$$\text{if } I_m = \omega c V_m$$

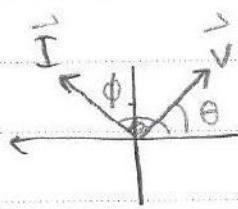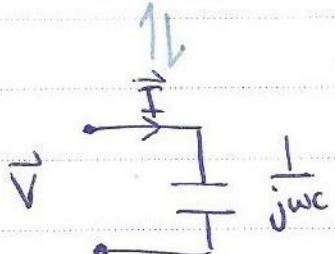

$$\vec{I} \text{ leads } \vec{V} \text{ by } 90^\circ$$

* Generalized Ohm's law:

$$\vec{V} = \vec{I} \vec{Z} \rightarrow \text{impedance } [\Omega]$$

$$\bullet \vec{Y} = \frac{1}{\vec{Z}} \rightarrow \text{admittance } \left[\frac{1}{\Omega} \equiv \text{S} \equiv \text{y} \right] \xrightarrow{\text{mho!!}}$$

7/2/2013

$$\vec{Z} = \begin{array}{c} R \\ \text{---} \\ \text{---} \\ R \end{array} \quad \begin{array}{c} L \\ \text{---} \\ \text{---} \\ j\omega L \end{array} \quad \begin{array}{c} C \\ \text{---} \\ \text{---} \\ \frac{1}{j\omega C} \end{array}$$

a) $\vec{V}_1 = \frac{\vec{V}}{\vec{Z}_1 + \vec{Z}_2} \times \vec{Z}_1 \dots \text{voltage division}$

b) $\vec{Z}_{eq} = \vec{Z}_1 + \vec{Z}_2 \text{ in series}$

c) $\vec{Z}_{eq} = \frac{\vec{Z}_1 \times \vec{Z}_2}{\vec{Z}_1 + \vec{Z}_2} \text{ in parallel}$

in general: $\vec{Z}_{eq} = \frac{1}{\sum_{i=1}^n \frac{1}{Z_i}}$ { in parallel}

& $\vec{Y}_{eq} = \vec{Y}_1 + \vec{Y}_2 + \dots + \vec{Y}_n$



\hookrightarrow better to use it in nodal analysis!

$$\vec{Z} = R + jX = \sqrt{R^2 + X^2} \angle \tan^{-1}\left(\frac{X}{R}\right)$$

R: Real part ; the resistance of the impedance $[\Omega]$.

X: Imaginary part ; the reactance $\rightarrow +ve$ inductive

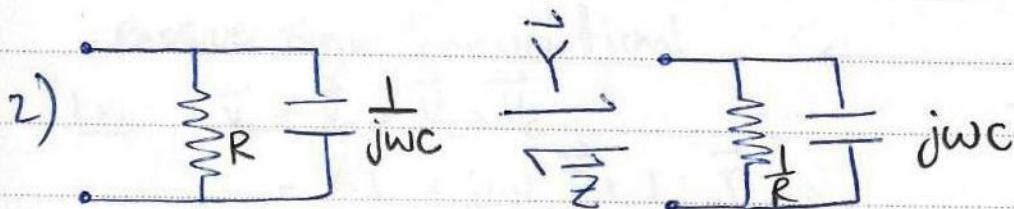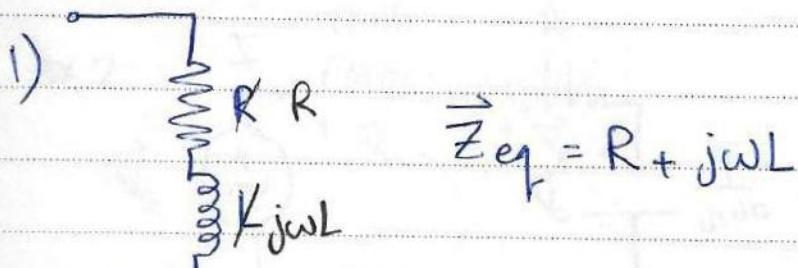$\hookrightarrow -ve$ capacitive $\frac{1}{j\omega C} = -\frac{j}{\omega C}$



$$\rightarrow \vec{Z}_{eq} = \frac{1}{\vec{Y}_{eq}} = \frac{1}{1/R + jwC} * \frac{1}{1/R - jwC}$$


$$= \frac{1/R - jwC}{(1/R)^2 + (wC)^2}$$

$$= \frac{1/R}{(1/R)^2 + (wC)^2} - j \frac{wC}{(1/R)^2 + (wC)^2}$$

$\Rightarrow \vec{Y} = G + jB$

G: conductivity ance


B: Susceptance

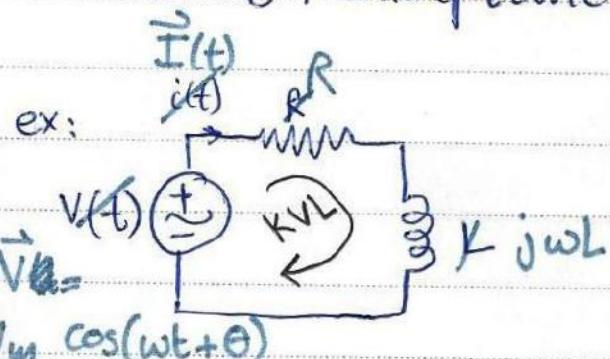

$$\text{KVL: } -\vec{V} + R\vec{I} + jwL\vec{I} = 0$$


$$(R + jwL)\vec{I} = \vec{V}$$
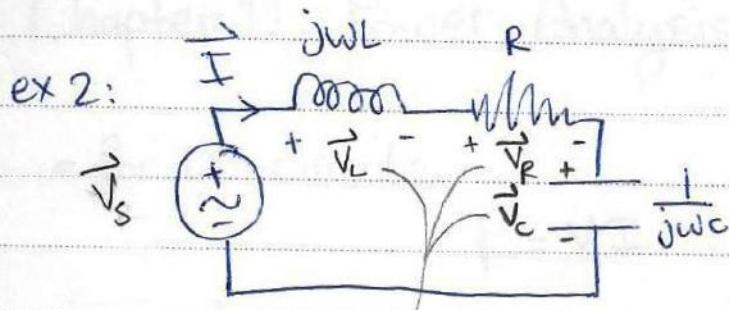
$$\vec{I} = \frac{\vec{V}_m \angle \theta}{R + jwL}$$





Passive sign convention!
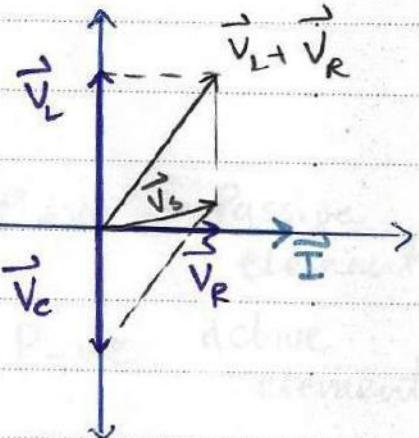
$$\text{KVL: } \vec{V}_s = \vec{V}_R + \vec{V}_L + \vec{V}_C \\ = R\vec{I} + jWL\vec{I} + \frac{1}{jWC}\vec{I}$$



* If \vec{V}_s is in phase with \vec{I} it's called a (resonant CKT) ; \vec{V}_C & \vec{V}_L cancels each other.


ex 3:

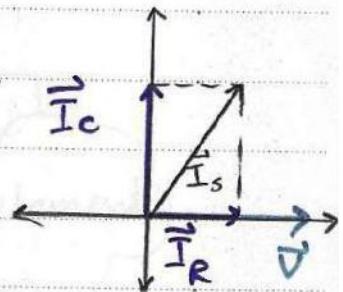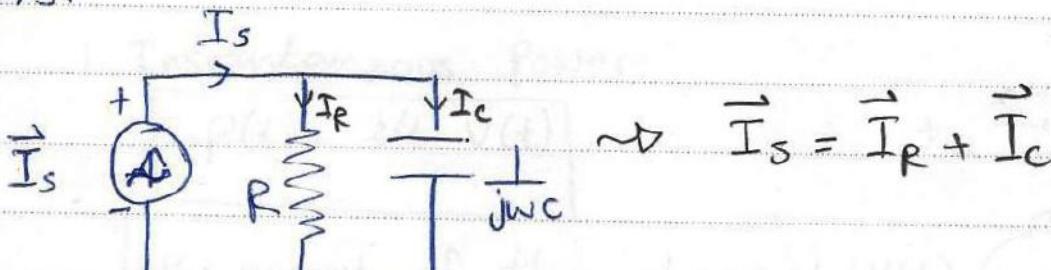


Chapter 11: Power Analysis:-

- for DC circuits :

$$P = VI$$

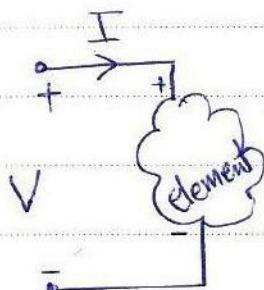

; Passive-sign convention

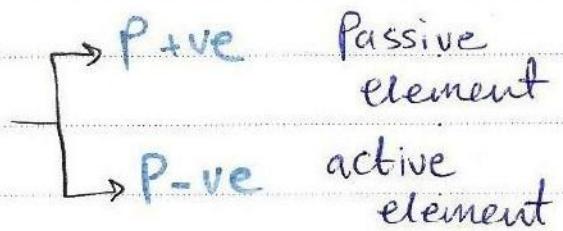



\rightarrow the element absorbs (P) amount of power; then (P) is the amount of power delivered to this element.

10/2/2013

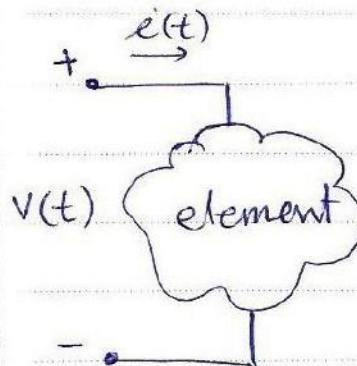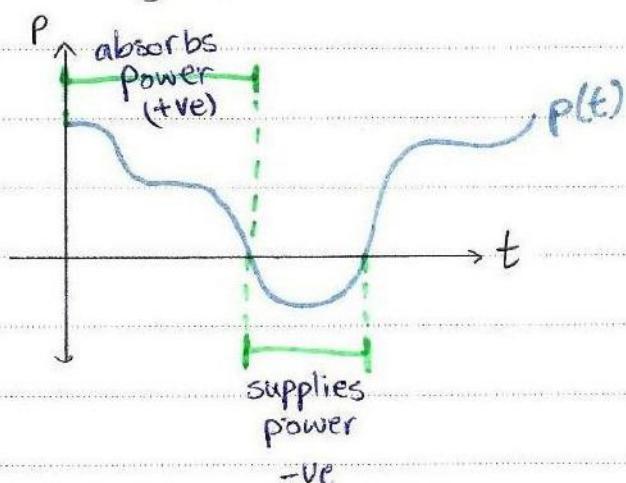1. Instantaneous Power:

$$P(t) = i(t)V(t)$$

\rightarrow the amount of the absorbed power by this element.




* P in Resistors:

$$V(t) = R \dot{e}(t) \dots *$$

$$P = \dot{e}(t) V(t)$$

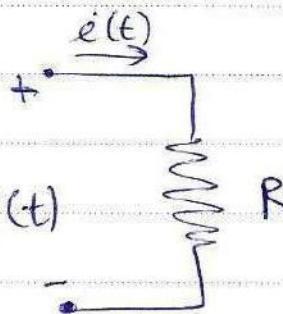$P = R \dot{e}^2(t)$
$\mathcal{F} = V^2(t)/R$




* in Inductors:

$$V(t) = L \frac{d\dot{e}(t)}{dt} \dots *$$

$P = L \dot{e}(t) \frac{d\dot{e}(t)}{dt}$

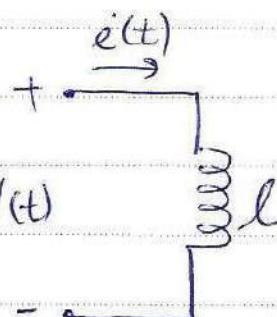$\mathcal{F} = \frac{1}{2} V(t) \int_{-\infty}^t V(\tau) d\tau$




* in Capacitors:

$$\dot{e}(t) = C \frac{dV(t)}{dt} \dots *$$

$P = C V(t) \frac{dV(t)}{dt}$

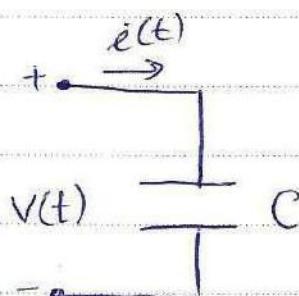
$\mathcal{F} = (1/C) \dot{e}(t) \int_{-\infty}^t \dot{e}(\tau) d\tau$




ex:- in the following circuit:

find $P_s(t)$ & prove
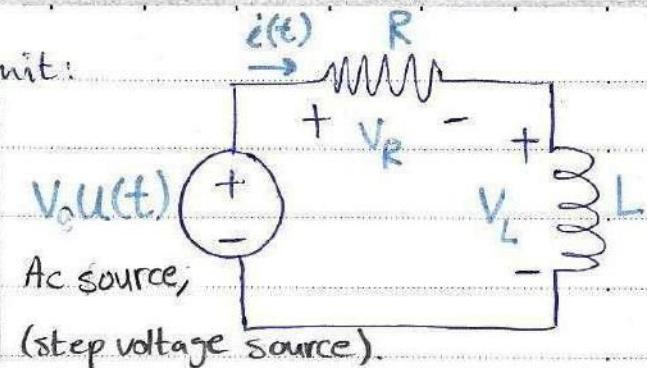
$$\text{that } P_s(t) = P_R(t) + P_L(t)$$



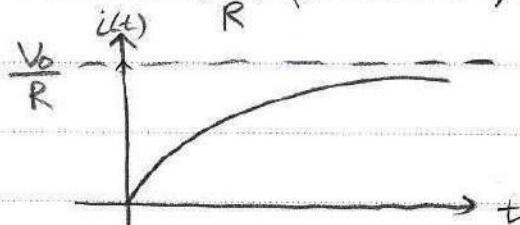
$$\text{sol: } i(t) = \frac{V_o}{R} \left(1 - e^{-\frac{R}{L}t}\right) u(t)$$



$$P_s(t) = v(t) \cdot i(t) = (V_o u(t)) \cdot \left(\frac{V_o}{R} \left(1 - e^{-\frac{R}{L}t}\right) u(t)\right)$$

$$P_s(t) = \frac{V_o^2}{R} \left(1 - e^{-\frac{R}{L}t}\right) u(t) \rightarrow u^2(t) = u(t)$$

$; \omega^2 = D$
 $1^2 = 1$

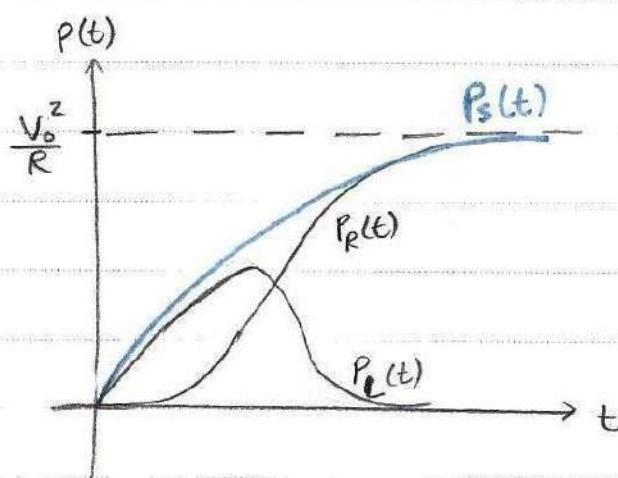

$$\rightarrow P_R(t) = i^2(t) R = \frac{V_o^2}{R^2} * R \left(1 - e^{-\frac{R}{L}t}\right)^2 u(t) \dots \textcircled{1}$$

** $\frac{du(t)}{dt} = 0$
 $t > 0$

$$\rightarrow P_L(t) \Rightarrow V_L(t) = L \frac{di(t)}{dt}$$

$$= L \left[\frac{V_o \cdot R}{L} e^{-\frac{R}{L}t} \cdot u(t) + \frac{V_o}{R} \left(1 - e^{-\frac{R}{L}t}\right) \frac{d u(t)}{dt} \right]$$

$$V_L(t) = V_o e^{-\frac{R}{L}t} \cdot u(t)$$

$$\text{cont, } P_L(t) = V_L(t) \cdot i(t)$$

$$P_L(t) = \frac{V_0^2}{R} (1 - e^{-Rt/L}) e^{-Rt/L} u(t) \quad \dots \quad (2)$$

$$(1) + (2) \Rightarrow P_R + P_L = \frac{V_0^2}{R} (1 - e^{-Rt/L})^2 u(t) + \frac{V_0^2}{R} (1 - e^{-Rt/L}) e^{-Rt/L} u(t)$$

$$= \frac{V_0^2}{R} (1 - e^{-Rt/L}) u(t) \left(1 - e^{-Rt/L} + e^{-Rt/L} \right)$$


$$P_R(t) + P_L(t) = \frac{V_0^2}{R} (1 - e^{-Rt/L}) u(t) = P_s(t) \quad \otimes$$

$$\text{ex: } \vec{V} = V_m \angle \theta$$

$$\vec{I} = I_m \angle \phi$$

find $p(t)$?!

$$V_m \cos(\omega t + \theta)$$

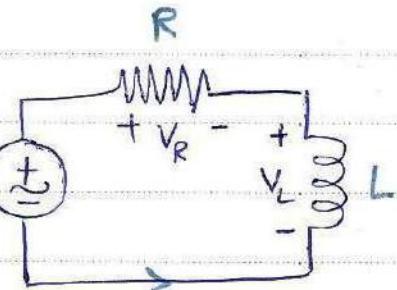

$$I_m \cos(\omega t + \phi)$$

$$\text{sol: } I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}}, \quad \phi = \theta - \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$\rightarrow p(t) = v(t) \cdot i(t)$$

$$= V_m \cos(\omega t + \theta) \cdot I_m \cos(\omega t + \phi)$$

$$** \quad \cos \alpha \cdot \cos \beta = \frac{1}{2} \cos(\alpha - \beta) + \frac{1}{2} \cos(\alpha + \beta)$$

$$\therefore p(t) = \frac{V_m I_m}{2} (\cos(\theta - \phi) + \cos(2\omega t + \theta + \phi))$$


متحف الدار

$$p(t) = \frac{1}{2} V_m I_m \cos(\theta - \phi) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta + \phi)$$


constant!

function of time

→ average Power
(DC Power)

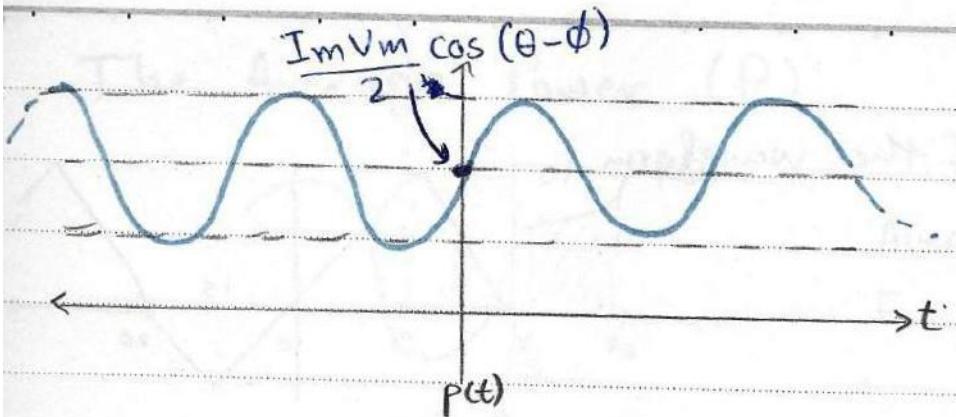

Problem 7:

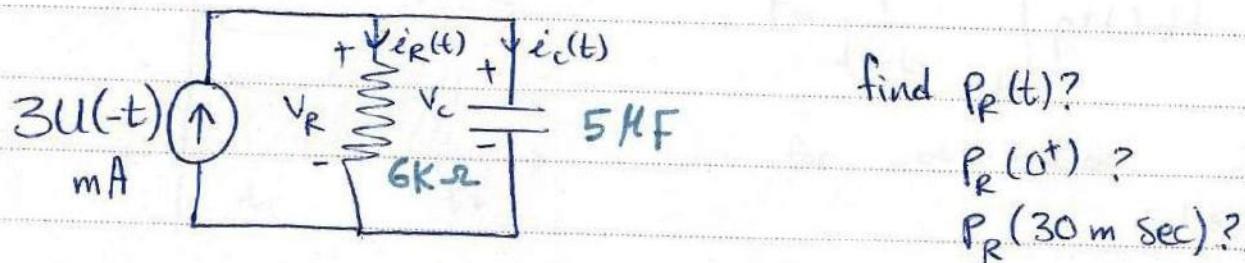


$$V_C(0^-) = V_C(0^+) = 3 \text{ mA} \cdot 6\text{k} = 18\text{V}$$

$3u(-t)$

$$i_R(0^-) = 3 \text{ mA}, \quad i_R(0^+) = \frac{18\text{V}}{6\text{k}} = 3 \text{ mA}$$

Just a coincidence

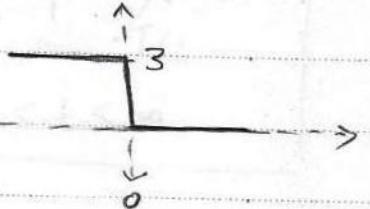

$$\therefore P_R(t) = i_R^2(t) \cdot R \quad \text{--- (1)}$$

$$i_R(t) = A e^{-t/\tau} \quad \text{--- (2)}, \quad \tau = RC = 5\mu\text{F} \cdot 6\text{k} = 0.03 \text{ sec}$$

but $i_R(0^+) = 3 \text{ mA}$ \rightarrow plug in (2) $\rightarrow A = 3 \text{ mA}$

$$\therefore i_R(t) = 3 \cdot e^{-t/0.03} \text{ mA}$$


plug in (1) ...

$$\ast P_R(t) = (3 e^{-t/0.03} \text{ mA})^2 \cdot 6\text{k}$$

$$\ast P(0^+) = (3 \cdot 10^{-3})^2 \cdot 6 \cdot 10^3 = 54 \text{ mWatt}$$


$$\ast P_R(30 \text{ m sec}) = (3 \cdot 10^{-3})^2 \cdot (e^{-30/0.03})^2 \cdot 6 \cdot 10^3 \\ = 7.308 \text{ m Watt}$$

The Average Power (P)

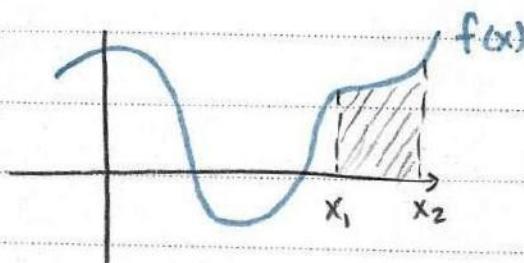


Average value of $f(x)$:
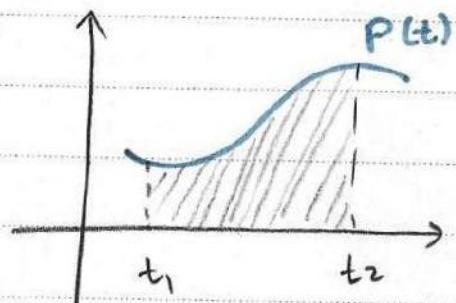
$$\bar{f} = \left(\int_{x_1}^{x_2} f(x) dx \right) / (x_2 - x_1)$$



$$P = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} p(t) dt$$

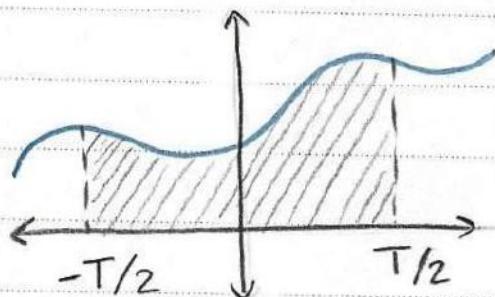for $-\infty < t < \infty$ $\bar{p} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} p(t) dt$




$$P = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} p(t) dt$$

$-\infty < t < \infty$

** For Periodic waveforms:-

$$P(t) = P(t+T) = P(t+nT), n \in \mathbb{Z} \text{ (integers)}$$

T is the period of the wave.

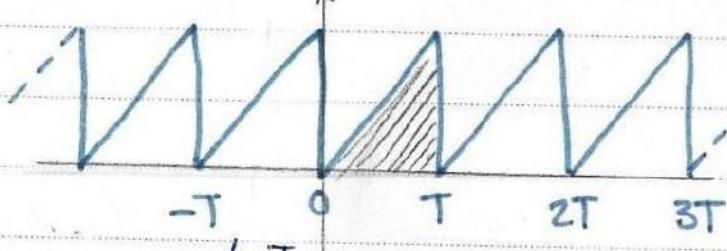

$$P = \frac{1}{T} \int_{t_x}^{t_x+T} p(t) dt$$

$$= \frac{1}{nT} \int_{t_x}^{t_x+nT} p(t) dt$$

$$= \frac{1}{T} \int_0^T p(t) dt$$

$$P = \frac{1}{T} \int_T p(t) dt$$

integrate over T

$-T/2 \rightarrow T/2$
or $0 \rightarrow T$


12 / 4 / 2013

C

ex: $v(t) = 4 \cos(\frac{\pi}{6}t)$

$$\vec{V} = 2 \angle 60^\circ \omega$$

find $p(t)$?!

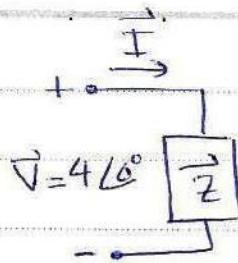

sol: $\vec{I} = \frac{4 \angle 60^\circ}{2 \angle 60^\circ} = 2 \angle -60^\circ \text{ A}$

$$P = \frac{1}{2} I_m V_m \cos(\theta - \phi)$$


$$P = 4 \times 2 \cos 60^\circ = 2 \text{ watt} \quad \text{average power / DC P}$$

$$p(t) = v(t) i(t)$$


$$i(t) \rightarrow i = 2 \cos(\frac{\pi}{6}t - 60^\circ)$$

$$p(t) = \underbrace{2}_{\text{avg } P} + \underbrace{\frac{1}{2} \times 4 \times 2}_{V_m} \cdot \underbrace{\cos(\frac{\pi}{3}t - 60^\circ)}_{i_w \sin(\theta + \phi)}$$
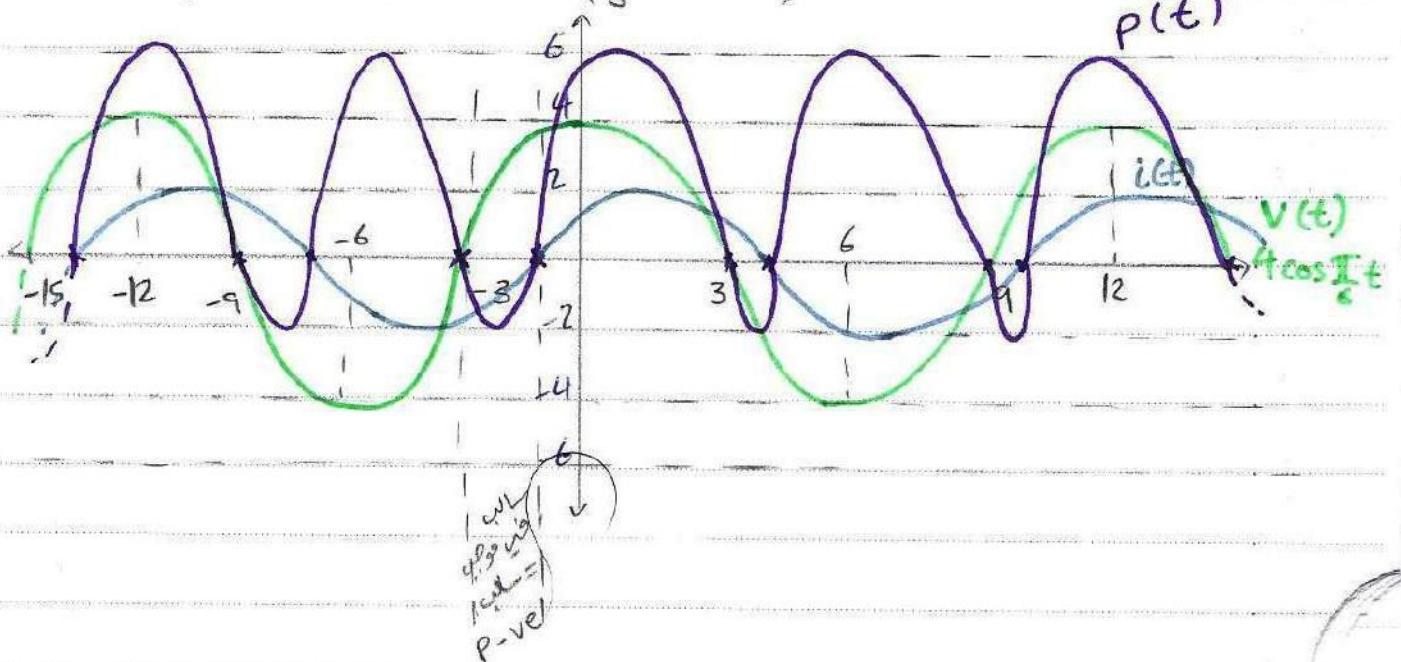
$$p(t) = 2 + 4 \cos(\frac{\pi}{3}t - 60^\circ)$$



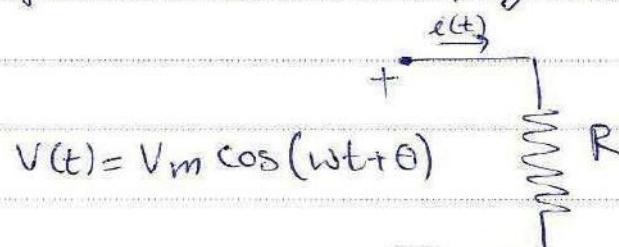
* Average power absorbed by an "Ideal Resistor":




$$i(t) = \frac{V(t)}{R} = \frac{V_m}{R} \cos(\omega t + \theta); \quad \theta = 0^\circ \quad \therefore \theta - \phi = 0^\circ$$

$$P = \frac{1}{2} V_m \left(\frac{V_m}{R} \right) \cos(0^\circ)$$
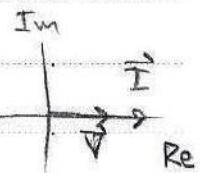
$$P_R = \frac{1}{2} \frac{V_m^2}{R} = \frac{1}{2} I_m^2 R$$



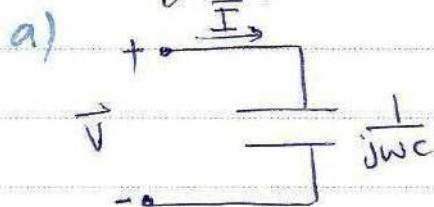* Average power absorbed by purely reactive impedance:




$$\theta - \phi = 90^\circ$$

$$P = \frac{1}{2} I_m V_m \cos(-90^\circ)$$

$$P = 0$$

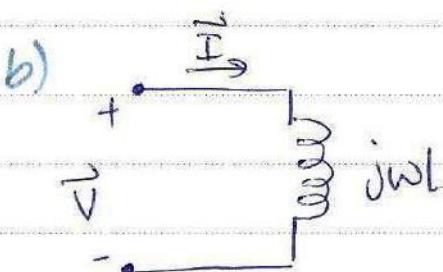capacitor doesn't consume average power (DC Power).



$$\theta - \phi = 90^\circ$$



$$P = \frac{1}{2} I_m V_m \cos(90^\circ) = 0$$

avg power.

** When $\vec{Z} = jX$ (pure reactance) : $P = 0$

** $\approx \vec{Z} = R$ (\approx resistance) : $P = \frac{1}{2} \frac{V_m^2}{R} = \frac{1}{2} I_m^2 R$

** $\approx \vec{Z} = R + jX$ next page

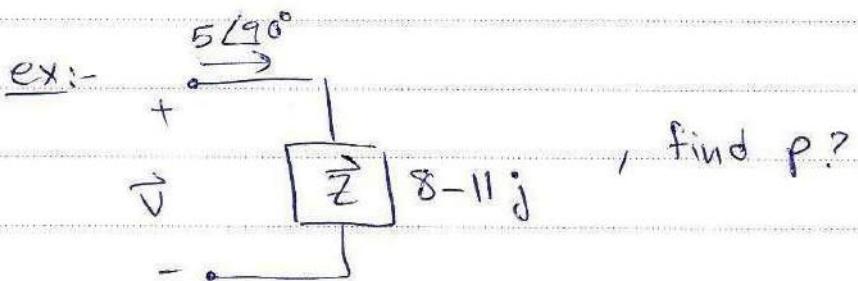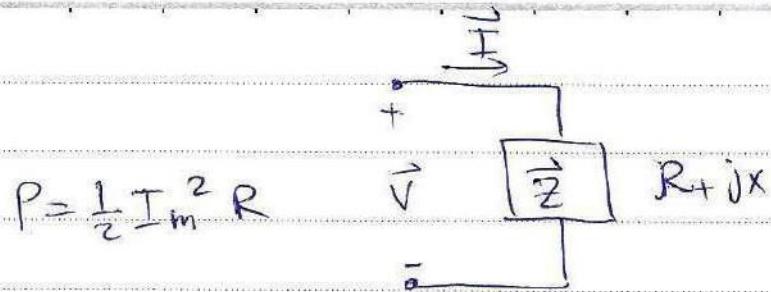

$$\text{sol: } P = \frac{1}{2} \times 5^2 \times 8 = 100 \text{ Watt}$$

another way:

$$\vec{V} = 5 \angle 90^\circ \times \left(\sqrt{8^2 + 11^2} \angle \tan^{-1} \left(\frac{11}{8} \right) \right) \quad (\vec{V} = \vec{I} \cdot \vec{Z})$$

$$P = \frac{1}{2} I_m V_m \cos(\theta - \phi)$$

$$= \frac{1}{2} 5 \times \sqrt{8^2 + 11^2} \times 5 \cos \left(-\tan^{-1} \left(\frac{11}{8} \right) + 90^\circ - 90^\circ \right)$$

$$P = 100 \text{ Watt}$$

ex:- find:

$$P_R = ?$$


$$P_L = ?$$

$$P_C = ?$$

$$P_1 = ?$$

$$P_2 = ?$$

Sol: * $P_L = P_C = 0$

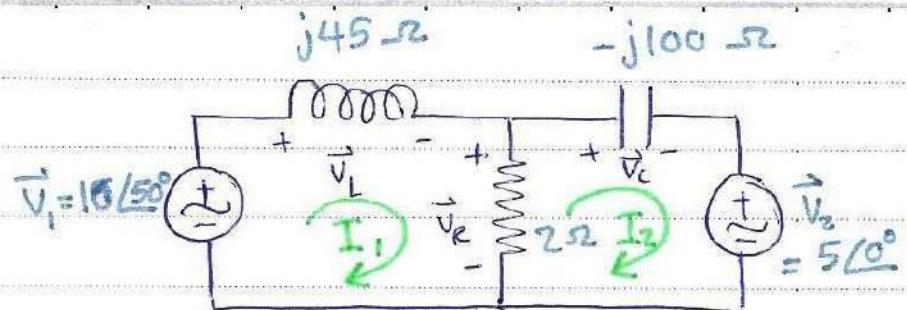

Mesh analysis

@ loop 1: $-10 \angle 50^\circ + j45 \vec{I}_1 + (\vec{I}_1 - \vec{I}_2) * 2 = 0$
 $(2 + j45) \vec{I}_1 - 2 \vec{I}_2 = 10 \angle 50^\circ \dots (1)$

@ loop 2: $(\vec{I}_2 - \vec{I}_1) * 2 - j100 \vec{I}_2 + 5 \angle 0^\circ = 0$
 $-2 \vec{I}_1 + (2 - j100) \vec{I}_2 = -5 \angle 0^\circ \dots (2)$

if we do the math; cramer, gaussian elimination, ...

$$\vec{I}_1 = 0.1724 - 0.1352j = 0.2205 \angle -37.8^\circ$$

$$\vec{I}_2 = 0.0018 - 0.0466j = 0.0466 \angle -87.78^\circ$$

$$P_R = \frac{1}{2} (\vec{I}_1 - \vec{I}_2)^2 * 2 \rightarrow \vec{I}_1 - \vec{I}_2 = 0.1706 - 0.0886j$$

$$= 0.1922 \angle -27.4^\circ$$

$$= \frac{1}{2} (0.1922)^2 * 2 = 0.0369$$

* $P_R = (36.9) \text{ mWatt}$ (absorbed)

$$* P_1 = \frac{1}{2} |\vec{I}_1| |\vec{V}_1| \cos(\theta_1 - \phi_1)$$

$$P_1 = \frac{1}{2} (0.2205) (10) \cos(50 - (-37.8)) = 42.324 \text{ Watt}$$



(supplied)

$$* P_2 = \frac{1}{2} (0.0466)(5) \cos(0 + 87.78^\circ) = 4.516 \text{ mWatt}$$

(absorbed)

Maximum Power Transfer Theorem:

DC:

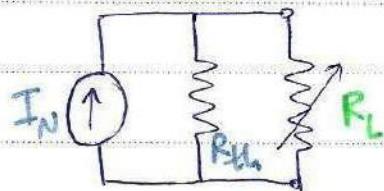
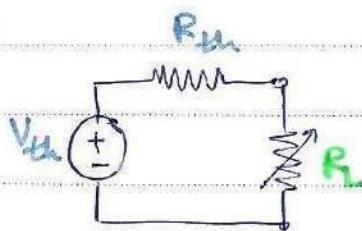


$$I_N = \frac{V_{th}}{R_{th}}$$

→ V_{th} or I_N delivers maximum power for R_L when

$$R_L = R_{th}$$

Sinusoidal Sources:

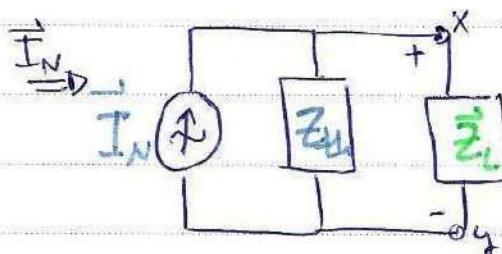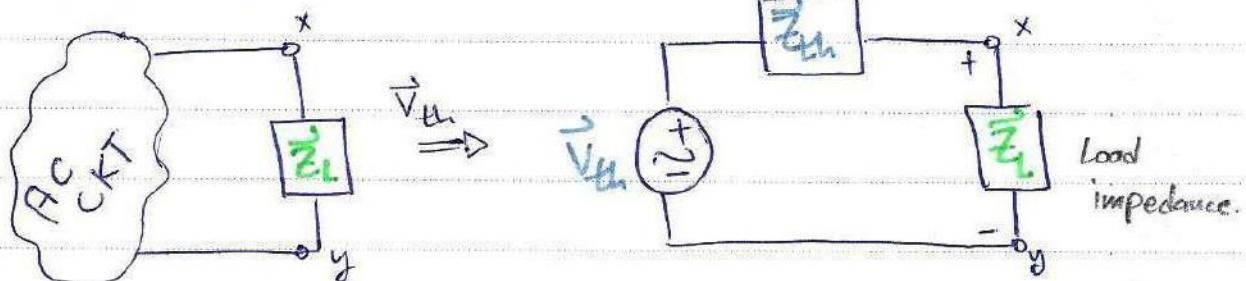


→ \vec{V}_{th} or \vec{I}_N delivers maximum average* power (P_L) to \vec{Z}_L when:

$$\vec{Z}_L = \vec{Z}_{th}^*$$

the conjugate

→ proof in the book!!

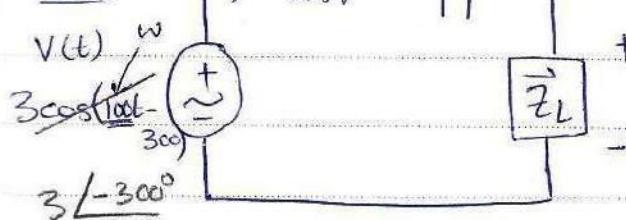ex: $\vec{I} = 500\angle 0^\circ \text{ A}$ $10\text{H} \quad \frac{1}{j1000\Omega} = -j1000$



find \vec{Z}_L that absorbs the max. power?
and find P_L max.?

sol: * $\vec{Z}_{th} = 500 - j1000$

$$\vec{Z}_L = \vec{Z}_{th}^* = 500 + j1000 \rightarrow \cancel{\text{max power}} \\ 500\Omega \quad 10H \\ (j\omega L = j1000)$$

$$* \vec{I}_L = \frac{\vec{V}_{th}}{\vec{Z}_{th}^* + \vec{Z}_{th}} = \frac{\vec{V}_{th}}{2R}$$

$$P_L = \frac{1}{2} |\vec{I}_L|^2 R$$

$$= \frac{1}{2} \left(\frac{|\vec{V}_{th}|}{2R} \right)^2 R = \frac{1}{2} \frac{|\vec{V}_{th}|^2}{4R^2} R$$

$$= \frac{|\vec{V}_{th}|^2}{8R}$$

$$P_L = \frac{3^2}{8 \times 500} \text{ watt}$$

* Non-periodic wave forms & average power:

let $i(t) = \underbrace{i_1(t)}_{\text{Periodic}} + \underbrace{i_2(t)}_{\text{non-periodic}}$

ex: $i(t) = \sin t + \sin \pi t$
 $\omega_1 = 1 \quad \omega_2 = \pi$

$$T_1 = \frac{2\pi}{1} \text{ sec} \quad T_2 = \frac{2\pi}{\pi} = 2 \text{ sec}$$


$$\frac{T_1}{T_2} = \frac{2\pi}{2} = \pi \text{ irrational} \quad \therefore i(t) \text{ is non-periodic!}$$

b/c can't be written as $\frac{a}{b}$; a & b are integers.

* A non-periodic function could be a sum of multi-periodic functions having different periods, such that no greater common period can be found.

17/2/2013

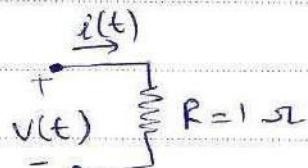ex: $i(t) = \underline{\sin(t)} + \underline{\sin(\pi t)}$
find P?



Sol: $P = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} p(t) dt \quad \dots \textcircled{1}$

$p(t) = i^2(t) R = i^2(t) ; \text{ normalized power } (R=1 \Omega)$

$$i^2(t) = [\sin t + \sin(\pi t)]^2$$

$$i^2(t) = \sin^2 t + 2\sin(t)\sin(\pi t) + \sin^2(\pi t) = p(t)$$

... plug in \textcircled{1}

$$P = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} (\sin^2 t + 2\sin(t)\sin(\pi t) + \sin^2(\pi t)) dt$$

$$= \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} \left[\frac{1}{2} - \frac{1}{2} \cos 2t \right] dt + \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} [\cos(t-\pi t) - \cos(t+\pi t)] dt + \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} \left[\frac{1}{2} - \frac{1}{2} \cos 2\pi t \right] dt$$

$$Av_1 = \frac{1}{2} + 0 \xrightarrow[\text{since it's 0}]{} \frac{(\cos 0) - 1}{2\pi} = 0$$

$$Av_2 = 0$$

$$Av_3 = \frac{1}{2}$$

$$P = \frac{1}{2} + 0 + \frac{1}{2} = 1 \text{ watt}$$

* but can we apply super position here? does $P = P_1 + P_2$?

→ In general, Super position can't be applied with power because it's not linear, but sinusoidal sources are an exception!

So, in the previous example:

$$P = P_1 + P_2 = \frac{1}{2}(I^2)(1) + \frac{1}{2}(I^2)(1) = 1 \text{ watt} *$$

* In general:

a) if

$$\begin{aligned} e(t) &= I_1 \cos(\omega_1 t + \phi_1) + I_2 \cos(\omega_2 t + \phi_2) + \dots + I_N \cos(\omega_N t + \phi_N) \\ &= \sum_{L=1}^N I_L \cos(\omega_L t + \phi_L) \quad (\text{sinusoidal}). \end{aligned}$$

$$\& \omega_1 \neq \omega_2 \neq \omega_3 \neq \dots \neq \omega_N ; \text{ since } (I_1^2 + I_2^2) \neq (I_1 + I_2)^2$$

Then

$$P = \frac{1}{2} (I_1^2 + I_2^2 + \dots + I_N^2) \cdot R$$

b) if

$$v(t) = \sum_{L=1}^N V_L \cos(\omega_L t + \phi_L) \quad \& \omega_1 \neq \omega_2 \neq \dots \neq \omega_N$$

Then

$$P = \frac{1}{2} \cdot \frac{1}{R} (V_1^2 + V_2^2 + \dots + V_N^2)$$

ex:- a) $R = 4 \Omega$

$$i(t) = \underline{2} \cos(10t) - \underline{3} \cos(20t) \text{ A , find } P_1 ?$$

$$P_1 = \frac{1}{2} * 4 * ((2)^2 + (-3)^2) = 26 \text{ watt}$$


$$b) i_2(t) = 2 \cos(10t) - 3 \cos(10t) , \omega_1 = \omega_2 !$$

$$i_2(t) = -\cos(10t)$$

$$P = \frac{1}{2} * 4 * (-1)^2 = 2 \text{ watt}$$

$$\underline{\text{ex 2:}} \quad V_s(t) = 8\sin(200t) - 6\cos(200t - 45^\circ) - 5\sin(100t) + 4$$

find P?

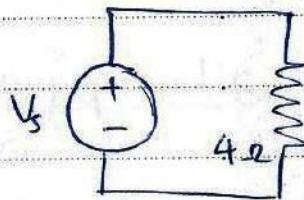



$$\underline{\text{Sol:}} \quad V_s(t) = \underbrace{8(\cos(200t - 90^\circ))}_{8/-90^\circ} - 6\cos(200t - 45^\circ) - 5\sin(100t) + 4$$

$$= 5.667 \angle 0^\circ - 5\sin(100t) + 4$$

doesn't affect P

$$P = \frac{1}{2} * \frac{1}{4} ((5.667)^2 + (-5)^2) + \frac{1}{4}(4^2) = 11.139 \text{ watt}$$

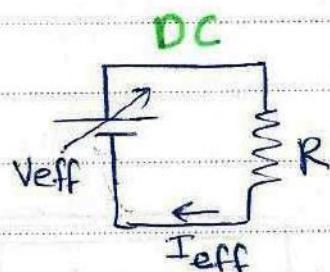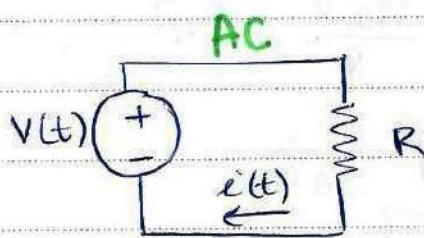Effective value of current & voltage: (r.m.s)



intuition
* if we replaced the AC source with DC source, which delivers the same amount of power (P) to the same resistance (R) then the voltage of that DC source =

$$V_{\text{eff, effective}} \equiv V_{\text{rms}}$$

$$\text{in AC: } P = \frac{1}{T} \int_0^T i^2(t) R dt = \frac{R}{T} \int_0^T i^2(t) dt \quad \dots \textcircled{1}$$

$$\text{in DC: } P = R I_{\text{eff}}^2 \quad \dots \textcircled{2}$$

but from definition: $P_{\text{AC}} = P_{\text{DC}}$

$$\therefore \frac{R}{T} \int_0^T i^2(t) dt = R I_{\text{eff}}^2$$

$$I_{\text{rms}} = I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

for any periodic source

RMS: Root-Mean-Square

* to represent an RMS value we can say:-

$$I = 5 A_{\text{rms}}$$

$$V = 6 V_{\text{rms}}$$

for V ...

$$P_{\text{AC}} = \frac{1}{T} \int_0^T \frac{V^2(t)}{R} dt$$

$$P_{\text{DC}} = \frac{V_{\text{eff}}^2}{R}$$

$$\therefore P_{\text{AC}} = P_{\text{DC}}$$

then

$$V_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt}$$

for any periodic function!

\Rightarrow RMS for sinusoidal waveforms:

$$\text{let } i(t) = I_m \cos(\omega t + \phi)$$

find I_{eff} ?

$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T (I_m \cos(\omega t + \phi))^2 dt}$$

$$= I_m \sqrt{\frac{1}{T} \int_0^T \frac{1}{2} + \frac{1}{2} \cos(2\omega t + 2\phi) dt}$$

$Au=0$

$$I_{\text{eff}} = I_m \sqrt{\frac{1}{2}} = \frac{I_m}{\sqrt{2}}$$

$$\therefore I_{\text{eff}} \approx 0.707 I_m$$

only for sinusoids!

$$V(t) = V_m \cos(\omega t + \theta)$$

$$V_{rms} = \frac{|\vec{V}|}{\sqrt{2}} = \frac{V_m}{\sqrt{2}}$$

Unit:

* $\vec{V} = (V_m \angle \theta) \rightarrow V$; peak value

Vrms $\hookrightarrow V_{rms}$; Rms value

ex: a) $\vec{V}_1 = 5 / 30^\circ \text{ V} \rightarrow V_m = 5, V_{rms} = \frac{5}{\sqrt{2}}$

b) $\vec{V}_2 = 5 / 30^\circ \text{ Vrms} \rightarrow V_{rms} = 5, V_m = 5\sqrt{2}$

RMS value & average power!

$$P_R = \frac{1}{2} I_m^2 R = \frac{1}{2} \frac{V_m^2}{R} = \frac{1}{2} V_m I_m \dots (1) \quad i(t) \quad v(t) \quad R$$

but $I_m = I_{eff} * \sqrt{2}$

$$V_m = V_{eff} * \sqrt{2}$$

plug in ①

$$P_R = I_{rms}^2 R = \frac{V_{rms}^2}{R} = I_{rms} V_{rms}$$

$$i(t) = I_m \cos(\omega t + \phi)$$

$$v(t) = V_m \cos(\omega t + \theta) \quad]-\theta = \phi \text{ in phase}$$

in general:-


$$v(t) = V_m \cos(\omega t + \theta) = \sqrt{2} I_{eff} \cos(\omega t + \phi)$$

$$i(t) = I_m \cos(\omega t + \phi) = \sqrt{2} I_{eff} \cos(\omega t + \phi)$$

$$P = \frac{1}{2} I_m V_m \cos(\theta - \phi)$$

$$= \frac{1}{2} I_{eff} V_{eff} (\sqrt{2}) \cos(\theta - \phi)$$
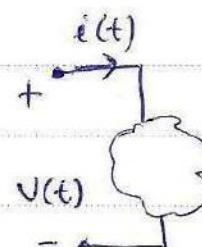
$$P = I_{eff} V_{eff} \cos(\theta - \phi)$$



⇒ rms for multi frequency waveforms:-

$$e(t) = \sum_{L=1}^N I_L \cos(\omega_L t + \theta_L) ; \omega_1 \neq \omega_2 \neq \dots \neq \omega_N$$

I_{eff} ?

$$P = \frac{1}{2} (\dot{I}_1^2 + \dot{I}_2^2 + \dots + \dot{I}_N^2) R$$

$$= \left(\frac{I_1^2}{R} + \frac{I_2^2}{R} + \dots + \frac{I_N^2}{R} \right) R$$

$$= (I_{\text{eff},1}^2 + I_{\text{eff},2}^2 + \dots + I_{\text{eff},N}^2) R$$

$$\boxed{P = I_{\text{eff total}}^2 \cdot R}$$

$$\text{where } I_{\text{eff total}}^2 = \sqrt{I_{\text{eff},1}^2 + I_{\text{eff},2}^2 + \dots + I_{\text{eff},N}^2}$$

$$v(t) = \sum_{L=1}^N V_L \cos(\omega_L t + \theta_L) ; \omega_1 \neq \omega_2 \neq \dots \neq \omega_N$$

$$V_{\text{eff}} = \sqrt{V_{\text{eff},1}^2 + V_{\text{eff},2}^2 + \dots + V_{\text{eff},N}^2}$$

$$\boxed{P = \frac{V_{\text{eff}}^2}{R}}$$

Ex: $i(t) = 6 \cos(25t) + 5 \cos^2(25t)$. A

Find I_{eff} ?

Sol: $i(t) = 6 \cos(25t) + 5\left(\frac{1}{2} + \frac{1}{2} \cos(50t)\right)$

$$= 6 \cos(25t) + \frac{5}{2} + \frac{5}{2} \cos(50t)$$


$$I_{\text{eff},1} = \frac{6}{\sqrt{2}} \quad I_{\text{eff},2} = \frac{5}{2} \quad I_{\text{eff},3} = \frac{5}{2\sqrt{2}}$$

$$I_{\text{eff}} = \sqrt{\left(\frac{6}{\sqrt{2}}\right)^2 + \left(\frac{5}{2}\right)^2 + \left(\frac{5}{2\sqrt{2}}\right)^2} = 5.232 \text{ A}_{\text{rms}}$$

* Apparent Power & Power factor:

- apparent power = $I_{\text{eff}} V_{\text{eff}}$

* unit used is : volt-Ampere [VA]

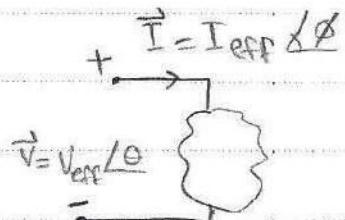

- Power factor P.F = $\frac{\text{Average Power}}{\text{Apparent Power}} = \frac{P}{V_{\text{eff}} I_{\text{eff}}}$

↳ for sinusoidal waveforms:

$$v(t) = V_m \cos(\omega t + \theta) = \sqrt{2} V_{\text{eff}} \cos(\omega t + \theta)$$

$$i(t) = I_m \cos(\omega t + \phi) = \sqrt{2} I_{\text{eff}} \cos(\omega t + \phi)$$

$$P = V_{\text{eff}} I_{\text{eff}} \cos(\theta - \phi)$$

$$\therefore \text{P.F} = \frac{P}{V_{\text{eff}} I_{\text{eff}}} = \cos(\underbrace{\theta - \phi}_{\text{P.F. angle!}})$$

for sinusoidal
 $0 \leq \text{P.F.} \leq 1$

$$\alpha = \theta - \phi = \cos^{-1}(\text{P.F.})$$

↳ can be +ve!

→ power factor \leq apparent power

P.F. = apparent power when $\cos(\theta - \phi) = 1 = \text{P.F.}$

P.F. = 1 ; unity power factor

↳ $\theta = \phi$; in-phase! ; pure resistive load.

→ for purely reactive load:

$$\theta - \phi = \pm 90^\circ \rightarrow \begin{cases} \text{capacitive - ve} \\ \text{inductive +ve} \end{cases}$$

$$\therefore P.F = \cos(\theta - \phi) = \boxed{0}$$


∴ for $\vec{Z} = R + jX$ load:

$$*\frac{\vec{Z}}{I} = \frac{\vec{V}}{I} = \frac{V_{eff} \angle \theta}{I_{eff} \angle \phi} \Rightarrow \frac{V_{eff}}{I_{eff}} = |\vec{Z}|, \theta - \phi = \angle \vec{Z}$$

a phase difference between $\vec{V} \& \vec{I}$ is the phase of \vec{Z} !

$$\boxed{P.F = \cos(\angle \vec{Z})}$$


Capacitive load

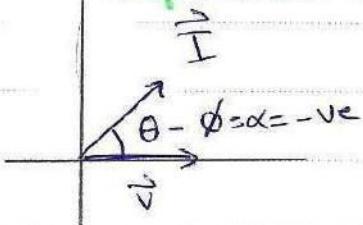

\vec{I} leads \vec{V} by α

leading P.F

Inductive load

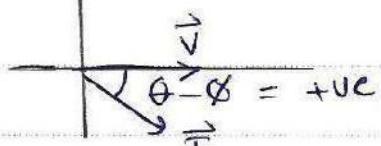

\vec{I} lags \vec{V} by α

lagging P.F

P.F $\begin{cases} 0 \rightarrow \text{purely reactive load} \\ 1 \rightarrow \text{purely resistive load} \\ \hookrightarrow \text{leading} \rightarrow \text{capacitive load} \\ \hookrightarrow \text{lagging} \rightarrow \text{inductive load} \end{cases}$

when we want to define P.F we say for example:


P.F = 0.5 leading!

ex:-

find the overall

P.F of this CKT:
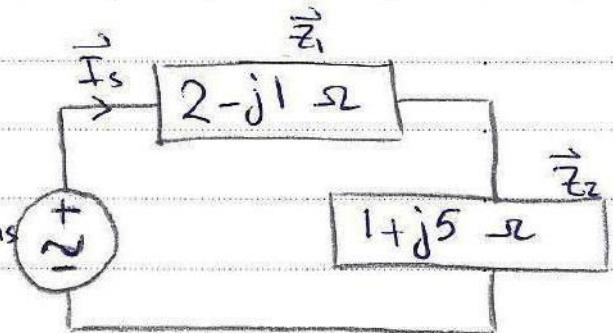
$$\vec{V}_s = 60 \angle 0^\circ V_{rms}$$



Sol: P.F = $\frac{P}{V_{eff} I_{eff}}$, $V_{eff} = 60 V_{rms}$, $I_{eff} = ?$

$$I = \frac{\vec{V}_s}{\vec{Z}_1 + \vec{Z}_2} = \frac{60 \angle 0^\circ}{(2+j1) + j(1+5)} = \frac{60 \angle 0^\circ}{3+j4} = 12 \angle -53.1^\circ A_{rms}$$

$$I_{eff} = 12 A_{rms}$$

$$z_{eq} = 3+j4; \text{inductive!}$$

$$* P.F = \cos(\theta - \phi) = \cos(0^\circ - (-53.1^\circ)) = 0.6 \text{ lagging}$$

another way:

$$P_{Z_1} = I_{eff}^2 \cdot (2) = 12^2 \times 2 = 288 \text{ watt}$$

$$P_{Z_2} = I_{eff}^2 \cdot (1) = 12^2 = 144 \text{ watt}$$

$$P_{eq} = 432 \text{ watt}$$

$$P.F = \frac{P}{V_{eff} I_{eff}} = \frac{432}{60 \times 12} = 0.6 \text{ lagging} *$$


P.42: a) find overall P.F.


b) find the avg power

Supplied by this source.

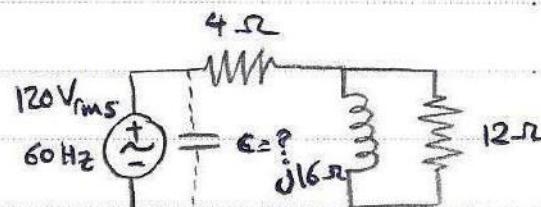c) if we add a capacitor

parallel to the R/L, find $C = ?$ such that the overall P.F becomes unity.



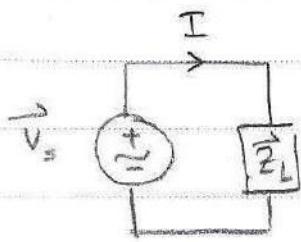

$$\vec{V}_s = 120 \angle 0^\circ$$

$$\vec{Z}_L = 4 + \left(\frac{j16 * 12}{j16 + 12} \right) = 11.68 + j5.76 \rightarrow \\ = 13.023 \angle 26.25^\circ \text{ lagging!}$$

$$I = \frac{\vec{V}_s}{\vec{Z}_L} = 9.214 \angle -26.25^\circ \text{ A rms}$$

a)

$$\text{P.F.} = \cos(\angle \vec{Z}) = \cos(26.25^\circ) = 0.8968 \text{ lagging!}$$

$$\text{b) } P = I_{\text{eff}} \cdot V_{\text{eff}} \cdot (\text{P.F.}) = (9.214)(120)(0.8968) = 991.6 \text{ watt}$$

c) P.F. = 1 ; resistive load

$$\vec{Y}_{\text{eq}} = j\omega C + \frac{1}{11.68 + j5.76}$$

$$= j\omega C + \frac{11.68 - j5.76}{(11.68)^2 + (5.76)^2}$$

$$= j\omega C + \frac{11.68}{(11.68)^2 + (5.76)^2} - \frac{j5.76}{(11.68)^2 + (5.76)^2}$$

$\text{Im}\{\vec{Y}_{\text{eq}}\} = 0$; because the load must be purely resistive.

$$\therefore \omega C - \frac{5.76}{(11.68)^2 + (5.76)^2} = 0, \omega = 2\pi(60)$$


$$C = 90.09 \mu F$$

Complex Power :-

$$\vec{I}_{\text{eff}} = I_{\text{eff}} \angle \phi$$

$$\vec{S} = \vec{I}_{\text{eff}}^* \cdot \vec{V}_{\text{eff}} \quad [\text{VA}]$$
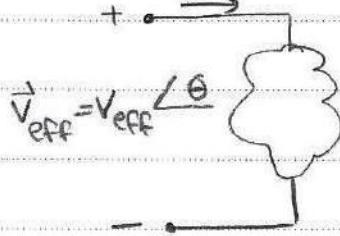
$$\vec{I}_{\text{eff}}^* = I_{\text{eff}} \angle -\phi$$



$$\begin{aligned}
 P &= \operatorname{Re}\{\vec{S}\} = \operatorname{Re}\{\vec{I}_{\text{eff}}^* \cdot \vec{V}_{\text{eff}}\} = V_{\text{eff}} I_{\text{eff}} \cos(\theta - \phi) \\
 &= \operatorname{Re}\{V_{\text{eff}} \angle \theta \cdot I_{\text{eff}} \angle -\phi\} \\
 &= \operatorname{Re}\{V_{\text{eff}} I_{\text{eff}} e^{j(\theta - \phi)}\} \\
 &= \operatorname{Re}\{V_{\text{eff}} I_{\text{eff}} \cos(\theta - \phi) + j V_{\text{eff}} I_{\text{eff}} \sin(\theta - \phi)\}
 \end{aligned}$$

Average power Reactive power
 DC Power Quadrature Power (Q)
 Real power

$$\begin{array}{l}
 \vec{S} = P + j Q \\
 [\text{VA}] \quad [\text{Watt}] \quad [\text{VAR}]
 \end{array}$$

; Volt-Ampere ; Volt-Ampere-reactive!

* Reactive Power : it's the time rate of energy & flow back & forth between the ^{power supply} source & the reactive component of the load (\vec{Z})

Imaginary part of \vec{Z}

$$P = V_{\text{eff}} I_{\text{eff}} \cos(\theta - \phi)$$

[WATT]


; measured using wattmeter.

$$Q = V_{\text{eff}} I_{\text{eff}} \sin(\theta - \phi)$$

[VAR]

; measured using VAR meter

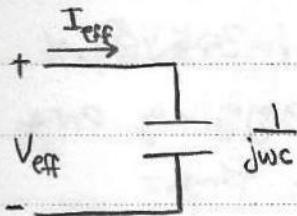- for inductive load (lagging p.f) : Q is +ve
- for capacitive load (leading p.f) : Q is -ve




$$\vec{V}_{\text{eff}} = \vec{I}_{\text{eff}} \cdot \frac{1}{jwC}$$

$$\begin{aligned}\vec{s} &= \vec{V}_{\text{eff}} \cdot \vec{I}_{\text{eff}}^* = \vec{I}_{\text{eff}} \cdot \frac{1}{jwC} \cdot \vec{I}_{\text{eff}}^* \\ &= I_{\text{eff}}^2 \cdot \frac{1}{jwC} \\ &= -j \frac{I_{\text{eff}}^2}{wC} = -j Q_c\end{aligned}$$

$$\therefore Q_c = -\frac{I_{\text{eff}}^2}{wC} \equiv -V_{\text{eff}}^2 wC$$

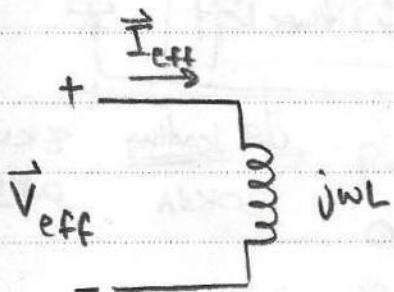* only imaginary power Q appears here, because average power absorbed by a capacitor = 0!



$$\vec{V}_{\text{eff}} = I_{\text{eff}} jwL$$

$$\begin{aligned}\vec{s} &= \vec{I}_{\text{eff}} \cdot jwL \cdot \vec{I}_{\text{eff}}^* \\ &= j I_{\text{eff}}^2 (wL) \\ &= j Q_L\end{aligned}$$

$$Q_L = wL I_{\text{eff}}^2 \equiv \frac{V_{\text{eff}}^2}{wL}$$

Spring 2011

Given the network shown below. The load $L_1 = 30 \text{ kVA}$, 0.9 p.f leading & $L_2 = 80 \text{ kWatt}$, 0.8 p.f lagging are connected in parallel & supplied from the source $V_s(t) = V_m \cos(100\pi t + \theta)$ through a line with an impedance of $0.1 + j0.1 \Omega$ as shown below.


1. Find: i) V_m, θ

2. Complex power & P.F at the source.

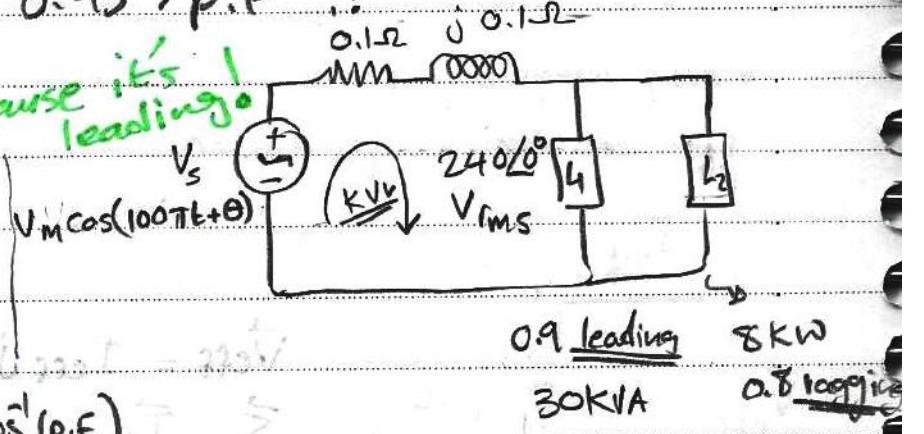3. What size capacitor should be installed in parallel with V_s to cause 0.95 p.f lagging?

Sol:-

$$\textcircled{1} \quad \vec{S}_1 = \text{apparent P} \angle -\cos^{-1} \text{P.F} \\ = 30 \angle -25.84^\circ \text{ kVA}$$



$$\vec{S}_2 = \frac{\text{Average P}}{\text{P.F}} \angle +\cos^{-1}(\text{P.F})$$

$$= 100 \angle 36.87^\circ \text{ kVA}$$

$$\vec{S}_{\text{total}} = \vec{S}_1 + \vec{S}_2 = 116.84 \angle 23.68^\circ \text{ kVA}$$

$$\vec{S}_{\text{total}} = \vec{I}_s^* \times \vec{V}$$

$$\rightarrow I_s = 487 \angle -23.68^\circ \text{ A}$$

$$V_s - V_s + (0.1 + j0.1) I_s + 240/0^\circ = 0$$

$$V_s = \frac{V_m}{V_m} \frac{1}{\theta} \angle 4.71^\circ$$

$$\textcircled{2} \quad S_s = \vec{V}_s \times \vec{I}_s^* = 148.6 \angle 28.4^\circ \text{ kVA}$$

$$\text{P.F} = \cos(\theta - \phi) = 0.88 \text{ lagging (X2+ve)}$$

③

$$C = \frac{\tan \theta_{\text{old}} - \tan \theta_{\text{new}}}{w V_{\text{rms}}^2}$$

$$\theta_{\text{old}} = \cos^{-1}(0.88) = 28.36^\circ$$

$$\theta_{\text{new}} = \cos^{-1}(0.95) = 18.19^\circ$$

$$w = 100\pi$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} = \frac{305.19}{\sqrt{2}} = 215.8$$

$$C = 1.45 \text{ nF}$$


The particulars of the composite load shown in Fig.1 are as follows:-

L₁: 10kW @ 0.8 lagging p.f.

L₂: 2kVA @ 0.707 lagging p.f.

L₃: 4kVA @ 0.866 leading p.f.

If V = 200 (0°) V rms, determine:

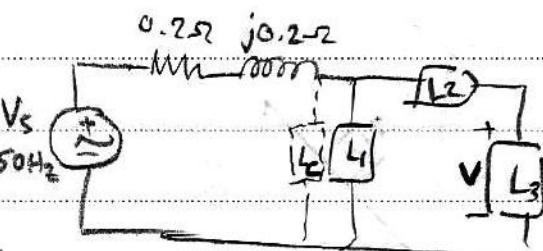

a) V_s, I₃, & p.f. source.

b) what value of C if connected to across the source will cause the source to operate @ 0.95 lagging p.f.

$$\text{p.f.}_{\text{source}} = \cos(24.56 + 1.77^\circ) = 0.897 \text{ lagging}$$

Sol:- a) $\vec{S}_1 = \frac{10 \text{ k}}{0.8} \angle \cos 0.8 = 12.5 \angle 36.87^\circ \text{ kVA}$

$$\vec{S}_2 = 2 \text{ k} \angle \cos 0.707 = 2 \angle 45^\circ \text{ kVA}$$

$$\vec{S}_3 = 4 \text{ k} \angle -\cos 0.866^\circ = 4 \angle -30^\circ \text{ kVA}$$

$$\vec{I}_3^* = \frac{\vec{S}_3}{V_3} = 20 \angle -30^\circ$$

$$\rightarrow \vec{I}_3 = 20 \angle 30^\circ$$

$$\vec{I}_3 = \vec{I}_2 !$$

$$\therefore \vec{I}_2 = \frac{\vec{S}_2}{\vec{I}_3^*} = 100 \angle 75^\circ \text{ A}$$

$$\underline{\text{KVL}} \quad V_1 = V_2 + V_3 = 245.67 \angle 23.15^\circ \text{ V}$$

$$S_{\text{total}} = \frac{(10 + 2 \times 0.707 + 4 \times 0.866)}{0.95} \angle 0^\circ$$

$$= 15.66 \angle 18.19^\circ \text{ kVA}$$

$$\vec{S}_c = S_{\text{total}} - (\vec{S}_1 + \vec{S}_2 + \vec{S}_3) = 2.03 \angle -90^\circ$$

$$= -j 2.03 \text{ kVA}$$

$$\vec{I}_c = \frac{\vec{S}_c}{V_c = V_1} = \vec{I}_c = 8.22 \angle 113.15^\circ \text{ A}$$

$$\therefore \vec{I}_1^* = \frac{\vec{S}_1}{V_1} = 50.88 \angle 13.71^\circ$$

$$\vec{I}_1 = 50.88 \angle -13.71^\circ$$

$$\text{but } I_s = I_1 + I_3 = 66.78 \angle -13.71^\circ$$


$$\vec{Z}_c = \frac{V_c}{I_c} = 29.878.09 \angle -90^\circ \text{ m}\Omega$$

$$\underline{\text{KVL}} \quad V_s + (0.2 + j0.2) I_s + V_1 = 0$$


$$\boxed{V_s = 263.49 \angle 24.56^\circ}$$

$$C = \frac{-j}{\omega (29.878.09)} = 1.068 \text{ nF}$$

* Power triangle:-

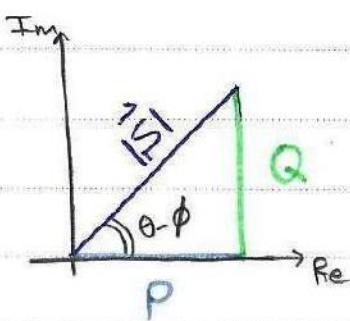

inductive load

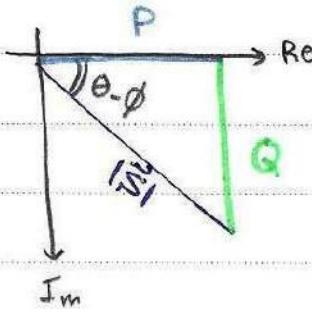

capacitive load


$$|\vec{S}| = V_{\text{eff}} I_{\text{eff}} \quad = \text{apparent power [VA]}$$

$$\therefore |\vec{S}| = \sqrt{P^2 + Q^2}$$

$$\hookrightarrow P = |\vec{S}| \cos(\theta - \phi) = V_{\text{eff}} I_{\text{eff}} \cos(\theta - \phi)$$

$$\hookrightarrow Q = |\vec{S}| \sin(\theta - \phi) = V_{\text{eff}} I_{\text{eff}} \sin(\theta - \phi)$$


I_m for a capacitive load:

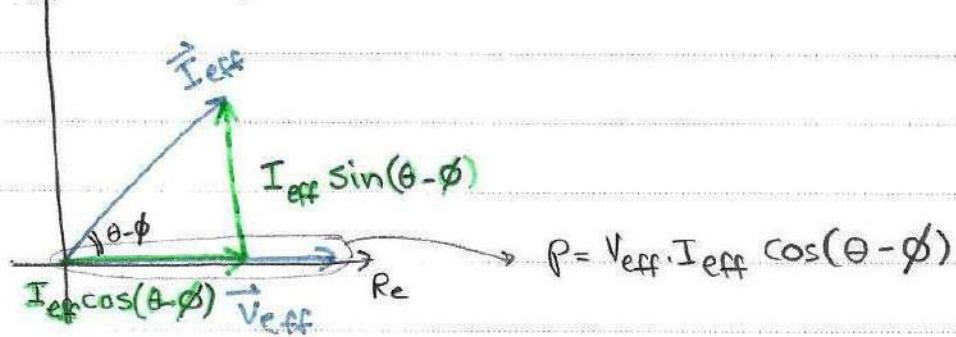

$$\vec{Z} = P + j Q$$


$\hookrightarrow 0$; pure reactive $\hookrightarrow 0$; Pure resistive

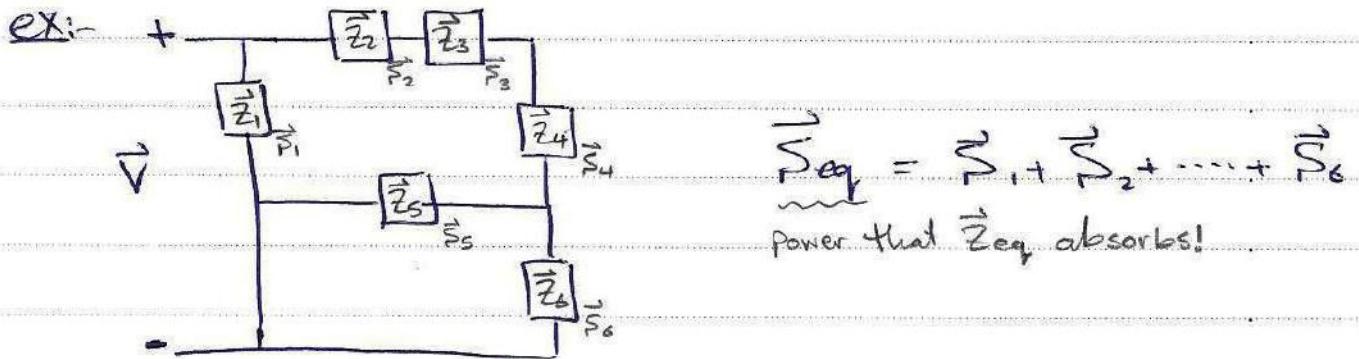$\hookrightarrow \neq 0$; \vec{Z} is complex $\hookrightarrow \neq 0$; \vec{Z} is complex.



* complex Power delivered to several interconnected loads/ impedances is "the sum of complex power delivered to each individual load!"


Proof: a) in parallel:

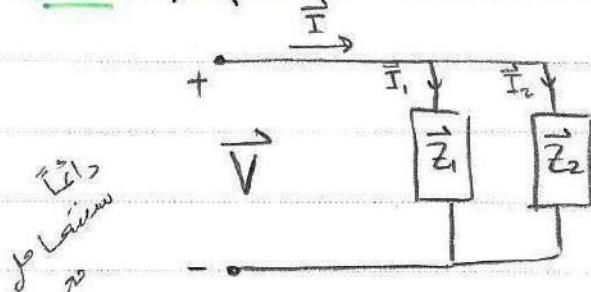

$$\begin{aligned}\vec{S} &= \vec{V} \vec{I}^* \\ &= \vec{V} (\vec{I}_1 + \vec{I}_2)^* \quad \text{KCL } (\vec{I} = \vec{I}_1 + \vec{I}_2) \\ &= \vec{V} \vec{I}_1^* + \vec{V} \vec{I}_2^* \\ \therefore \vec{S} &= \vec{S}_1 + \vec{S}_2\end{aligned}$$

effective values!

b) in series:

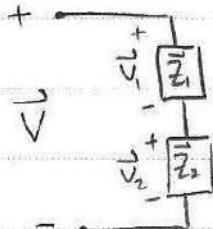


$$\begin{aligned}\vec{S} &= \vec{V}_{\text{eff}} \vec{I}^*_{\text{eff}} \\ &= (\vec{V}_1 + \vec{V}_2) \vec{I}^* \\ &= \vec{V}_1 \vec{I}^* + \vec{V}_2 \vec{I}^* \\ \therefore \vec{S} &= \vec{S}_1 + \vec{S}_2\end{aligned}$$

ex: maximum power rating = 1kW

* if $P.F = 1$ (pure resistive load)
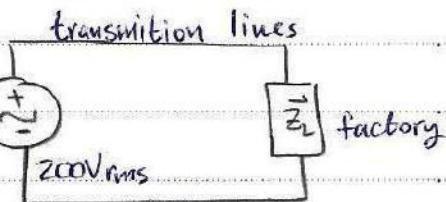
$$\text{then: } I_{\text{eff}} = \frac{1\text{k}}{(1)(200)} = 5 \text{ Arms}$$



* if the load has a lagging P.F of 0.5:


$$|I| = \frac{1\text{k}}{(0.5)(200)} = 10 \text{ Arms}$$

$$\dots I_1 (\text{P.F}=1) < I_2 (\text{P.F}=0.5)$$

it's better when P.F approaches unity (=1) because power dropped in transmission lines is given by: $P = |I|^2 R$, so increasing of I increases the power lose!

24/12/2013

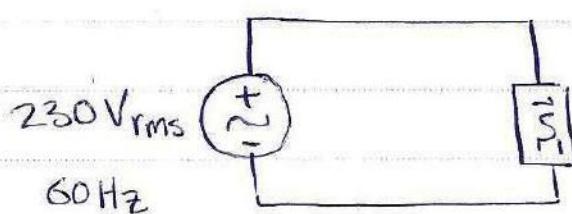ex: An induction motor operates at 50kW & lagging P.F of 0.8



$$P = 50\text{ kW}$$

$$\text{P.F}_1 = 0.8 \text{ lagging}$$

specify a suitable solution to raise the p.f to 0.95 lagging.


solt: $\text{P.F}_2 = 0.95$

solution is to put a correction load in parallel with the motor.

* we chose to put it parallel in order to maintain the voltage (230V rms) applied on \vec{Z}_1 .

* we add only an "imaginary/reactive part" load to maintain avg power (50kW) that's absorbed by the load.

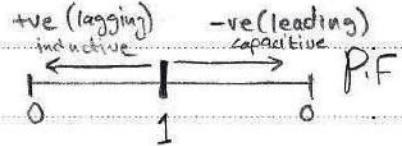+ in this case, to make P.F approaches 1 we need to add purely capacitive load!



- $\vec{S}_1 = P_1 + jQ_1$

$$\therefore P_1 = P = 50 \text{ kW}$$

$$\therefore |\vec{S}_1| = P_1 = 50 \text{ kVA}$$

$$|\vec{S}_1| = \frac{50}{0.8}$$

$$P.F_1 = \cos(\theta - \phi) = \cos \alpha_1 \Rightarrow \alpha_1 = \cos^{-1}(P.F_1) = 36.9^\circ \quad \begin{matrix} \alpha + \text{ve} \\ \text{lagging P.F} \end{matrix}$$

S_1 can be also written as:-

$$\vec{S}_1 = |\vec{S}_1| \angle \alpha_1 = \frac{50}{0.8} \angle 36.9^\circ = (50 + j37.5) \text{ kVA}$$

then, $\therefore Q_1 = (37.5) \text{ k VAR}$

- $\vec{S}_{\text{total}} = \vec{S} = \vec{S}_1 + \vec{S}_2$

$$|\vec{S}| = \frac{P}{P.F_2} = \frac{50}{0.95}$$

$$\alpha = \angle \vec{S} = \cos^{-1}(P.F_2) = \cos^{-1}(0.95) \quad (+\text{ve})$$

$$\Rightarrow \vec{S} = \frac{50}{0.95} \angle \cos^{-1}(0.95) = (50 + j16.43) \text{ kVA}$$

$$\therefore Q_{\text{tot}} = (16.43) \text{ k VAR}$$

but $\vec{S} = \vec{S}_1 + \vec{S}_2$

$$(50 + j16.43) \text{ k} = (50 + j37.5) \text{ k} + \vec{S}_2$$

$$\vec{S}_2 = -j21.07 \text{ kVA}$$

but $\vec{S}_2 = \vec{I}_2^* \vec{V}_S$ =

$$\vec{I}_2^* = -\frac{j21.07}{230} = -j91.6 \text{ Arms}$$

$$\rightarrow \vec{I}_2 = j91.6 \text{ Arms}$$

$$\therefore \vec{Z}_c = \frac{\vec{V}_s}{\vec{I}_2} = \frac{230 \angle 0^\circ}{j91.6} = \underline{-j2.51 \Omega} \\ -j/w_c$$


$$-j/w_c = -j2.51$$

$$w_c = \frac{1}{2.51}$$

$$\boxed{P.F \propto \frac{1}{\alpha}}$$

$$C = \frac{1}{2.51(2\pi \cdot 60)} = 1056 \mu F \equiv 1.056 mF$$

another: using power triangle:
way

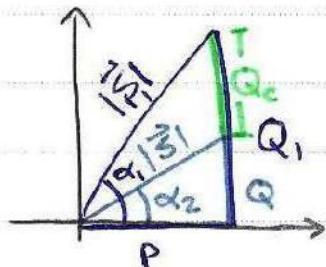

$$\vec{S}_1 = P + jQ_1$$

$$\vec{S} = P + jQ$$

$$Q_c = Q_1 - Q$$

$$\text{but } Q_1 = P \tan(\alpha_1)$$

$$\& \alpha_1 = \cos^{-1}(P.F_1)$$

$$Q = P \tan(\alpha_2)$$

$$\& \alpha_2 = \cos^{-1}(P.F_2)$$

$$\Rightarrow Q_c = Q_1 - Q$$


$$Q_c = |V_s|^2 (w_c)$$

$$\therefore C = \frac{Q_c}{|V_s|^2 \cdot w} *$$

Chapter 12: Polyphase Circuits:

* revision: double subscript notation :-


→ for voltages:

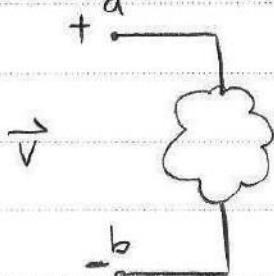


* instead of using five notations, we describe voltage difference by:

\vec{V}_{ab} ; terminal (a) is at higher Potential (+) than terminal b (-).

$$\vec{V}_{ab} = -\vec{V}_{ba}$$

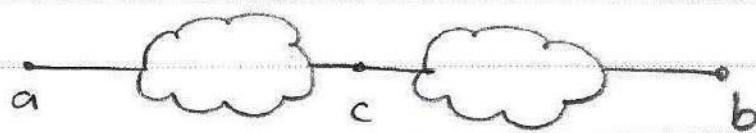
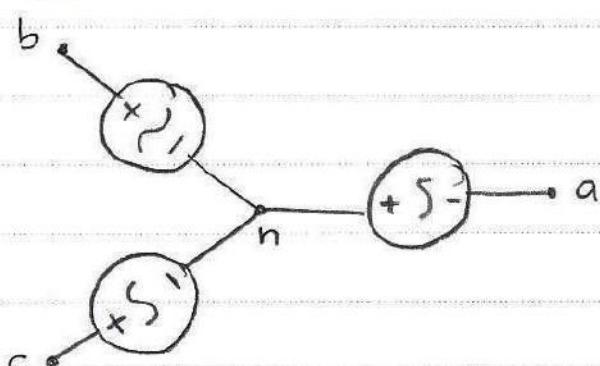
$$\vec{V}_{ab} = \vec{V}_{ac} + \vec{V}_{cb}$$




$$\vec{V}_{ab} = \vec{V}_{an} + \vec{V}_{nb} \equiv \vec{V}_{an} - \vec{V}_{bn}$$


$$\vec{V}_{ac} = \vec{V}_{an} + \vec{V}_{nc} \equiv \vec{V}_{an} - \vec{V}_{cn}$$

$$\vec{V}_{bc} = \vec{V}_{bn} + \vec{V}_{nc} \equiv \vec{V}_{bn} - \vec{V}_{cn}$$

→ for currents:

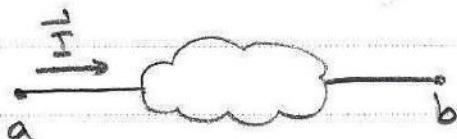

$$\vec{I}_{ab} \equiv -\vec{I}_{ba}$$

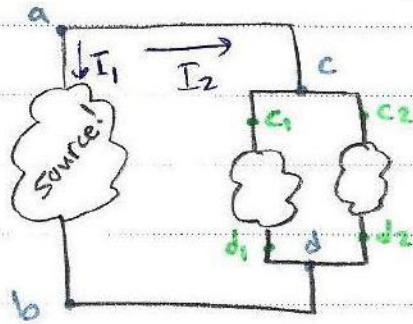

* \vec{I}_{ab} ; does it mean I_1 or I_2 ??

- we always follow the shortest/the most direct path. (I_1) elements ~~and~~ I_2


* \vec{I}_{cd} ; there's two currents which one to take?

- here we have to say \vec{I}_{c1d_1} or \vec{I}_{c2d_2} !


$$\underline{\vec{I}_{cd}} = \vec{I}_{c1d_1} + \vec{I}_{c2d_2}$$

the overall current

Poly-phase Systems:-

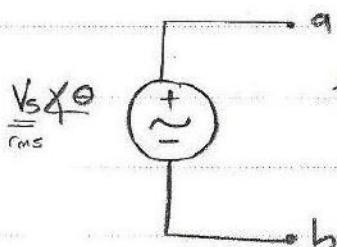


Single-phase

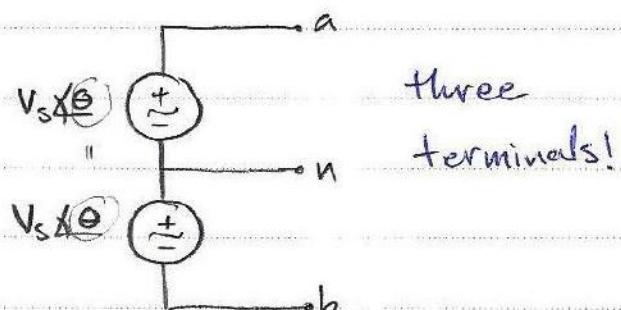

three terminals!

single-phase

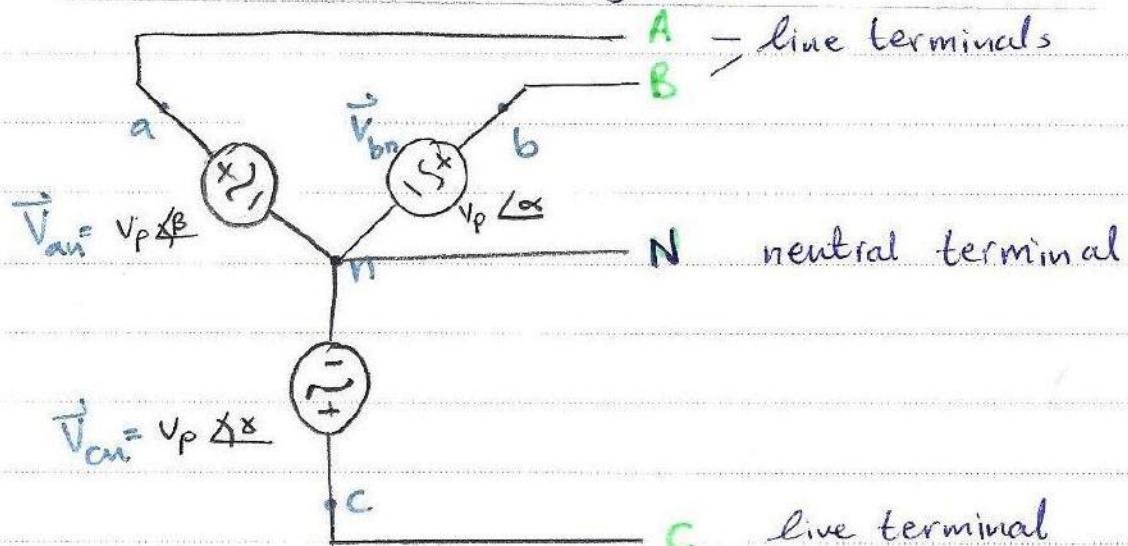

When: $\alpha \neq \delta \neq \beta$: 3-phase, 4-terminals System


$\alpha = \beta \neq \delta$: 2-phase, $\sim \sim \sim$

$\alpha = \beta = \delta$: 1-phase, $\sim \sim \sim$

* In 3 phase systems, the overall instantaneous power will be constant!

→ \vec{V}_{an} , \vec{V}_{bn} , \vec{V}_{cn} are the 'phase voltages' [V_{rms}]

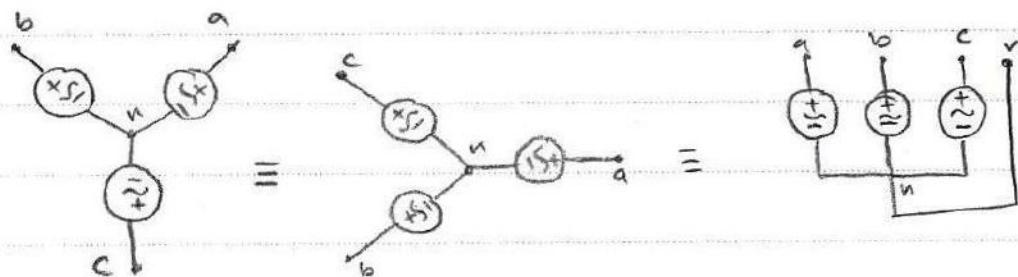→ \vec{V}_{ab} , \vec{V}_{ac} , \vec{V}_{bc} , \vec{V}_{cb} , \vec{V}_{ca} , ... are the 'line voltages' [V_{rms}]




it's called a Y-connected source!

⇒ Balanced 3-phase source:


3-phase source is balanced if:-

$$\vec{V}_{an} + \vec{V}_{bn} + \vec{V}_{cn} = 0$$

$$|\vec{V}_{an}| = |\vec{V}_{bn}| = |\vec{V}_{cn}| = V_p \text{ (rms)}$$

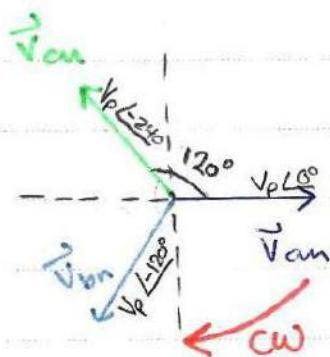

(+) sequence
(abc)

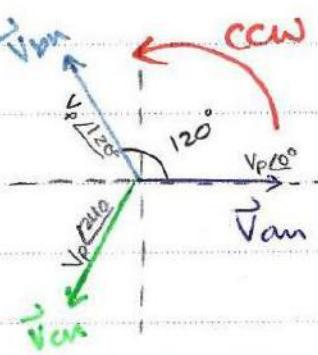


(-) sequence
(cba)

→ if \vec{V}_{an} is the reference, then $\vec{V}_{an} = V_p \angle 0^\circ$ & :

$$\text{(1)} \quad \begin{aligned} \vec{V}_{bn} &= V_p \angle 120^\circ = V_p \angle +240^\circ \quad \left\{ \begin{array}{l} (+ve\text{-phase}) \\ /abc \end{array} \right. \\ \vec{V}_{cn} &= V_p \angle -240^\circ = V_p \angle +120^\circ \end{aligned}$$
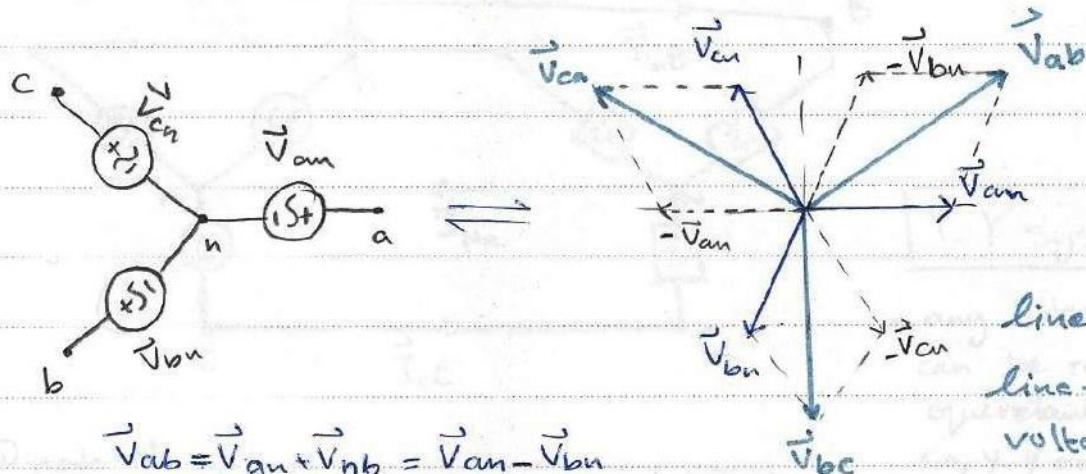
$$\text{(2)} \quad \begin{aligned} \vec{V}_{en} &= V_p \angle 240^\circ = V_p \angle -120^\circ \quad \left\{ \begin{array}{l} (-ve\text{-phase}) \\ /cba \end{array} \right. \\ \vec{V}_{bn} &= V_p \angle 120^\circ = V_p \angle -240^\circ \end{aligned}$$



$$\begin{aligned} \vec{V}_{ab} &= \vec{V}_{an} + \vec{V}_{nb} = \vec{V}_{an} - \vec{V}_{bn} \\ &= V_p \angle 0^\circ - V_p \angle 120^\circ \\ &= V_p - V_p \cos(-120^\circ) - j V_p \sin(-120^\circ) \end{aligned}$$

$$\boxed{\vec{V}_{ab} = V_p \left(1 + \frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = \sqrt{3} V_p \angle 30^\circ}$$

$\hookrightarrow V_p$: phase voltage

$\hookrightarrow V_L$: line voltage.

* line Voltages

(abc) • $\vec{V}_{ab} = \sqrt{3} V_p \angle 30^\circ$

(+) • $\vec{V}_{bc} = \sqrt{3} V_p \angle -90^\circ = \sqrt{3} \angle 30^\circ \vec{V}_{bn}$

• $\vec{V}_{ca} = \sqrt{3} V_p \angle 150^\circ = \sqrt{3} \angle 30^\circ \vec{V}_{cn}$

leads phase

voltages by 30°



(in +ve sequence)

(cba) • $\vec{V}_{ab} = \sqrt{3} V_p \angle -30^\circ = \sqrt{3} \angle -30^\circ \vec{V}_{an}$

(-) • $\vec{V}_{bc} = \sqrt{3} V_p \angle 90^\circ = \sqrt{3} \angle -30^\circ \vec{V}_{bn}$

• $\vec{V}_{ca} = \sqrt{3} V_p \angle 210^\circ = \sqrt{3} \angle -30^\circ \vec{V}_{cn}$

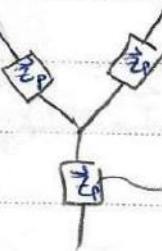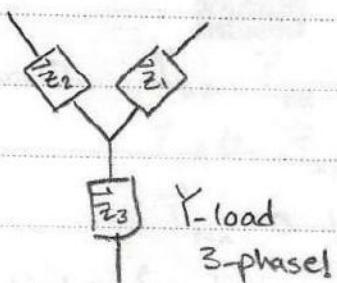
default (if it isn't mentioned) \Rightarrow +ve-sequence.



Balanced Y-load

Z_p : phase impedance
1-phase.

Balanced Y-connected System:-

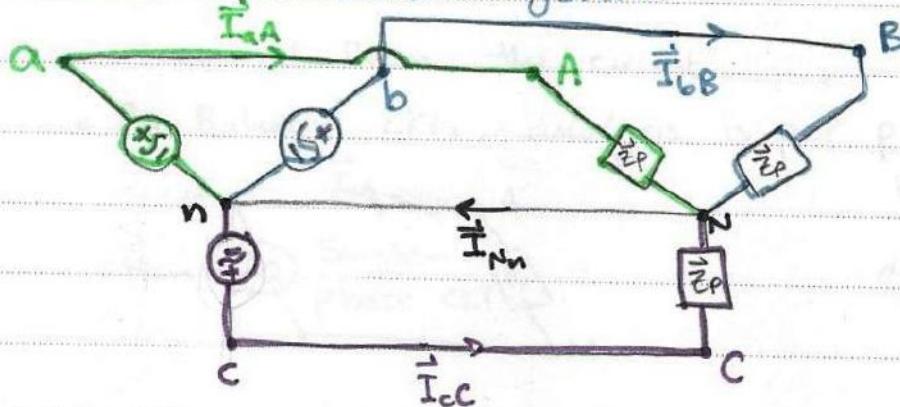


* any Balanced 3-φ system can be reduced to an equivalent Y-Y system, so, Y-Y analysis is the

...① Key to solving other 3- systems!

@ node N:

$$\vec{I}_{aA} + \vec{I}_{bb} + \vec{I}_{cc} = \vec{I}_{Nn}$$

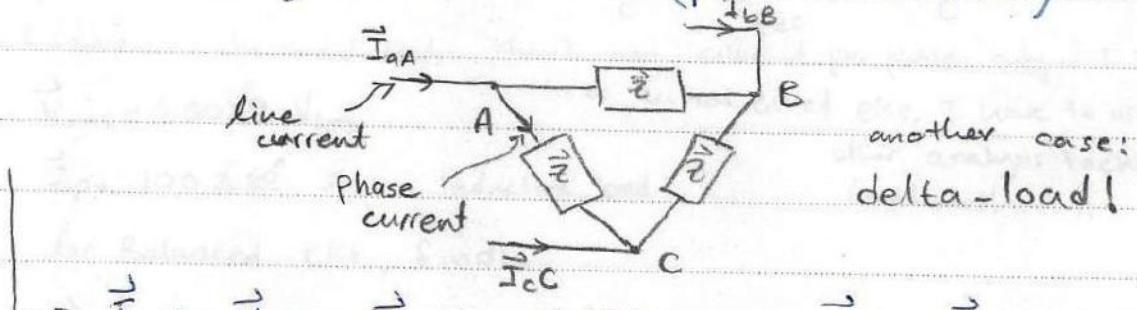- $\vec{I}_{aA}, \vec{I}_{bb}, \vec{I}_{cc}$ are called (line currents).
& in this case (transition lines has no impedance)
they are also called (phase currents).



$$\vec{I}_{aA} = \frac{\vec{V}_{AN}}{\vec{Z}_p} = \frac{\vec{V}_{an}}{\vec{Z}_p} = \frac{V_p \angle 0^\circ}{\vec{Z}_p}$$

$\vec{V}_{AN} = \vec{V}_{an}$ because it's a short ckt between a & A, n & N


$$\vec{I}_{bb} = \frac{\vec{V}_{BN}}{\vec{Z}_p} = \frac{\vec{V}_{bn}}{\vec{Z}_p} = \frac{V_p \angle -120^\circ}{\vec{Z}_p} = \frac{V_p \angle -120^\circ}{\vec{Z}_p} = \vec{I}_{aA} \angle -120^\circ$$

$$\vec{I}_{cc} = \frac{\vec{V}_{CN}}{\vec{Z}_p} = \frac{\vec{V}_{cn}}{\vec{Z}_p} = \frac{V_p \angle -240^\circ}{\vec{Z}_p} = \frac{V_p \angle -240^\circ}{\vec{Z}_p} = \vec{I}_{aA} \angle -240^\circ$$

$$\text{from } \textcircled{1}: \vec{I}_{aA} + \vec{I}_{bB} + \vec{I}_{cC} = \vec{I}_{Nn}$$

$$\vec{I}_{aA} \times^0 + \vec{I}_{aA} \times^{-120} + \vec{I}_{aA} \times^{-240} = \vec{I}_{Nn}$$

$$\therefore \vec{I}_{Nn} = 0 !$$


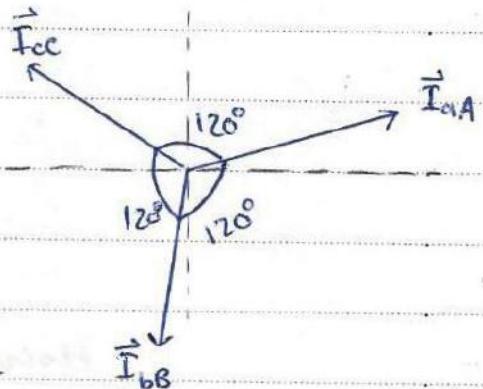


Note: for balanced loads, $I_{Nn} = 0$,

\therefore the neutral wire cord can be

removed from the circuit.

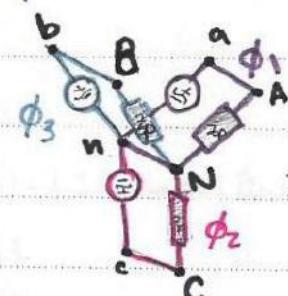
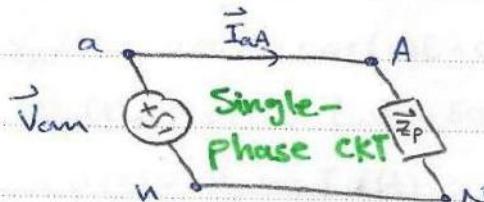
* for Balanced ckt's, analysis is per phase.



I can solve it per phase

* when $I_{Nn} \neq 0$, we have to take every ckt alone

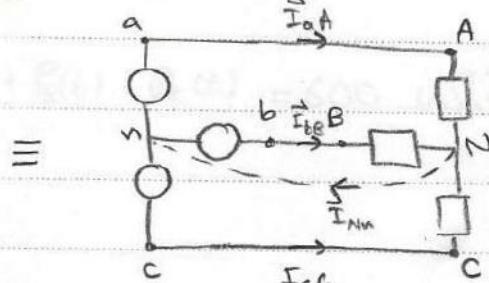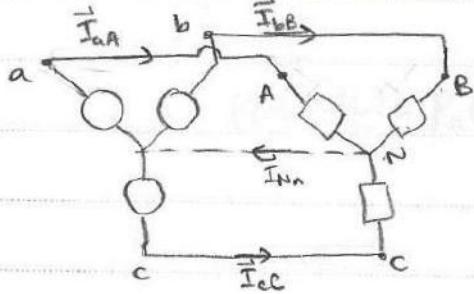and calculate $\vec{I}_{aA}, \vec{I}_{bB}, \dots$ one by one



2 loops (mesh)

* $I_{Nn}(Y)$, if I have an unbalanced load, the I can solve it per phase only if I have

$$\text{ex: } \vec{V}_{an} = 200 \times^0 \text{ V}_\text{rms}$$

$$\vec{Z}_p = 100 \times 60^\circ \Omega ; \text{ inductive load.}$$

other analysis techniques
(nodal, mesh, ...).

for Balanced ckt, find:-

$$a) \vec{I}_{aA} = \frac{\vec{V}_{an}}{\vec{Z}_p} = \frac{200 \times^0}{100 \times 60} = 2 \times^{60^\circ}$$

+ (+ve)-sequence (default)

$$\vec{V}_{bn} = 200 \times^{-120} \text{ V}_\text{rms}$$

$$b) \vec{I}_{bB} = \vec{I}_{aA} \times^{-120} = 2 \times^{-60-120} = 2 \times^{-180} \text{ A}_\text{rms}$$

$$\vec{V}_{cn} = 200 \times^{-240} \text{ V}_\text{rms}$$

$$c) \vec{I}_{cC} = \vec{I}_{aA} \times^{-240} = 2 \times^{-60-240} = 2 \times^{-300} \text{ A}_\text{rms}$$

$$d) \vec{V}_{ab} = \sqrt{3} \times^0 \vec{V}_{an} = 200\sqrt{3} \times^{30^\circ} \text{ V}_\text{rms}$$

$$f) \vec{V}_{ca} = 200\sqrt{3} \times^{-210^\circ} \text{ V}_\text{rms}$$

$$e) \vec{V}_{bc} = \sqrt{3} \times^0 \vec{V}_{bn} = 200\sqrt{3} \times^{-90^\circ} \text{ V}_\text{rms}$$

$$g) \vec{V}_{ac} = 200\sqrt{3} \times^{-150} = 200\sqrt{3} \times^{-210-180} = 200\sqrt{3} \times^{-30^\circ}$$

cont.
ii) P_{AN} :

$$P_{AN} = V_{rms} I_{rms} \cos(\theta - \phi)$$
$$= 200 + 2 \cos(0 - (-60))$$

$$P_{AN} = 200 \text{ Watt}$$

iii) P_{total} :

$$P_{total} = 3 P_{AN} = 3 \cdot 200 = 600 \text{ Watt}$$

iv) what's the instantaneous power $p(t)$ absorbed by the load?

$$V_{AN}(t) = 200\sqrt{2} \cos(\omega t + 0^\circ)$$

$$I_{AN}(t) = 2\sqrt{2} \cos(\omega t - 60^\circ)$$

$$\rightarrow P_A(t) = V_{AN}(t) I_{AN}(t) = \frac{1}{2} I_m V_m \cos(\theta - \phi) + \frac{1}{2} I_m V_m \cos(2\omega t + \theta + \phi)$$
$$= 200 + 400 \cos(2\omega t - 60^\circ) \text{ Watt}$$


$$P_B(t) = 200 + 400 \cos(2\omega t - 300^\circ)$$

$$P_C(t) = 200 + 400 \cos(2\omega t - 180^\circ)$$

$$P_{total}(t) = P_A(t) + P_B(t) + P_C(t) = 600 \text{ Watt}$$

ex:- A Balanced 3-phase, 3-wires system has a line voltage of 500 V_{rms}, two balanced Y-connected loads are present, one is a capacitive load with impedance $7-j2 \Omega$ per phase, & the other one is an inductive load with $4+j2 \Omega$ per phase, find:-

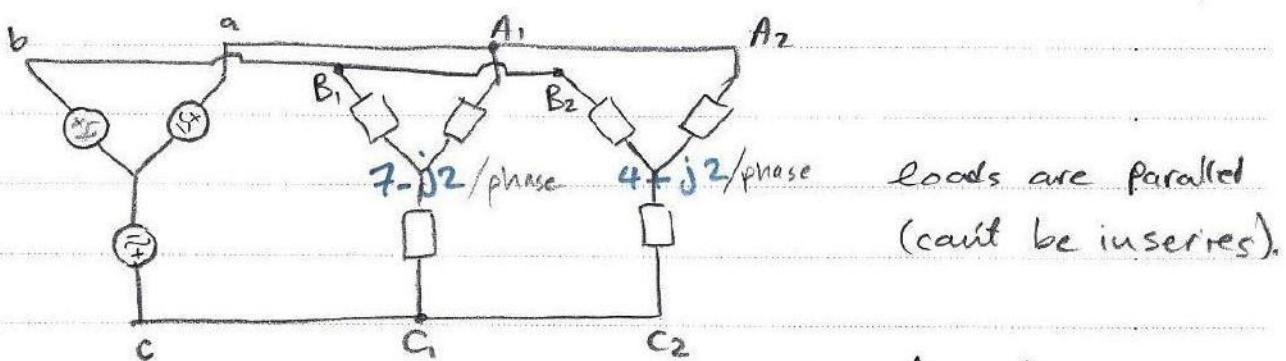1. the phase voltage.
2. the line current
3. P.F of the load.
4. the total power drawn by the load.
5. the P.F at which the source is operating.




$$V_L = 500 \text{ V}_\text{rms}$$

$$\textcircled{1} \quad V_P = V_L / \sqrt{3} = (500 / \sqrt{3}) \text{ V}_\text{rms}$$

$$V_{an} = V_P \angle 0^\circ = (500 / \sqrt{3}) \angle 0^\circ \text{ V}_\text{rms}$$

close it to be
a reference.

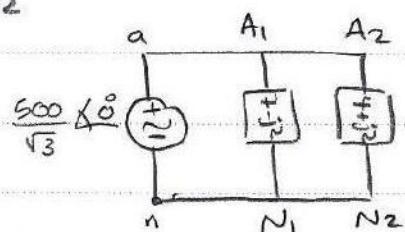

$$\textcircled{2} \quad \vec{Z}_{eq} = \vec{Z}_P = (7-j2) \parallel (4+j2) = \left(\frac{32}{11} + j \frac{6}{11} \right) \Omega$$

$$|\vec{Z}_P| = \sqrt{\frac{32^2 + 6^2}{11}} = 2.69 \Omega$$

$$\rightarrow |I_{aA_1}| = \frac{(500 / \sqrt{3})}{2.69} = 97.53 \text{ Arms}$$

inductive load

$$\text{OR} \quad \vec{I}_{aA_1} = \frac{\vec{V}_{an}}{\vec{Z}_P} = \frac{(500 / \sqrt{3}) \angle 0^\circ}{\frac{32}{11} + j \frac{6}{11}} = 97.53 \angle -10.62^\circ \text{ Arms}$$

$$\textcircled{3} \quad \text{P.F}_L = \cos(0 - (-10.62)) = 0.9828 \text{ lagging.}$$

$$④ P_{\text{Total}} = 3 * P_{\text{phase}} \quad \dots \textcircled{1}$$

$$P_p = (97.53)^2 \left(\frac{32}{11} \right) \quad \text{real part of } \vec{Z}$$

+ we take the current I
because V_p is not app-
lied only on $\text{Re } \vec{Z}$!

$$\text{Plug in } \textcircled{1} \dots P_T = 83.018 \text{ kWatt.}$$

⑤ $P.F_s = P.F_L$ "because there's zero impedance through transmission lines"


$$\therefore P.F_s = \cos(0 + 10.62^\circ) \equiv \cos(\tan^{-1}(\frac{6}{32})) \text{ lagging} \\ = 0.98285 \text{ lagging.}$$

$$\text{OR} \quad P.F = \frac{P_p}{V_1 I_1} = \frac{27.67 \text{ k}}{\left(\frac{500}{\sqrt{3}}\right)(97.53)} = 0.9828 \text{ lagging.}$$


Ex2:- 3 Balanced Y-connected loads are installed on a balanced 3-Ø, 4-wires system, load 1 draws a total power of 6 KW @ unity P.F., load 2 requires apparent Power 10 KVA

@ $P.F = 0.96$ lagging, & load 3 needs 7 kw @ $P.F = 0.85$ lagging, if the phase voltage @ loads is 135V, & each line has a resistance of 0.1Ω , while the neutral line has a resistance = 1Ω ; find:-

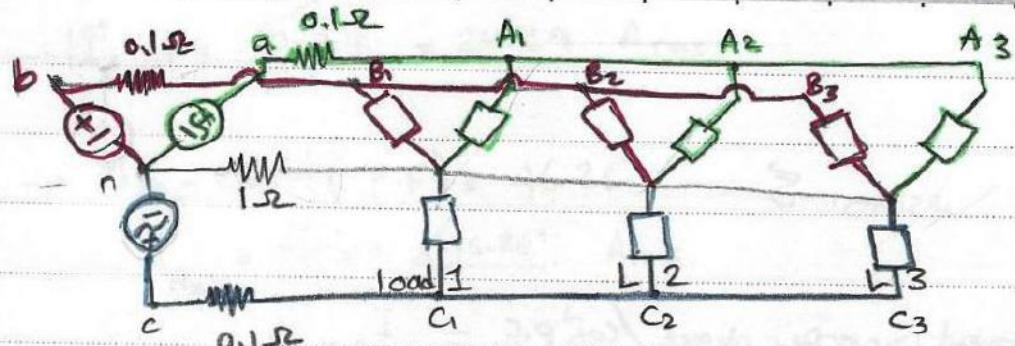- ① the total power drawn by the loads.
- ② the combined P.F of the loads.
- ③ the total power lost in the 4 lines.
- ④ the phase voltage
- ⑤ the P.F @ which the source is operating.



Pure resistive	inductive	inductive
6 KW	10 KVA	7 KW
PF = 1	PF = 0.96	PF = 0.85

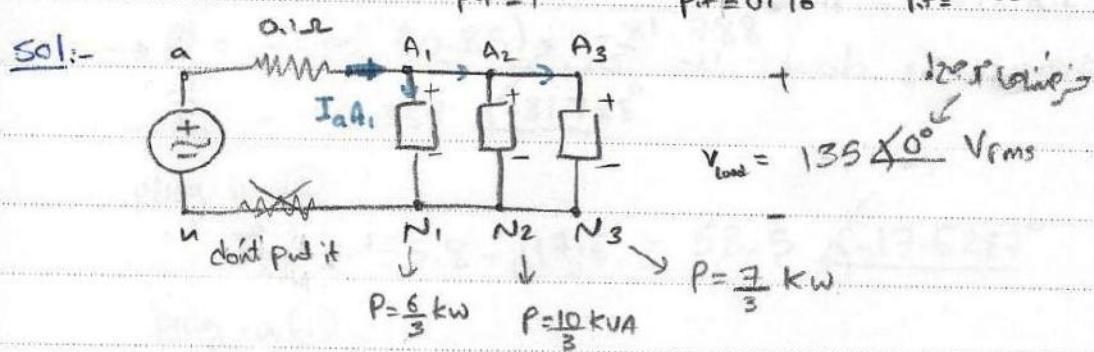

$$\textcircled{1} \quad P_{\text{total}} = 6 \text{ KW} + 10 \text{ KVA} + 0.96 + 7 \text{ KW} = 22.6 \text{ KW}$$

apparent p. = p.F = Real p.

$$\textcircled{2} \quad P_{\text{phase}} = P_p = \frac{22.6}{3} \text{ KW}$$

$$\textcircled{3} \quad \text{also } P_p = \vec{V}_{load} \cdot |I_{aA_1}| \cdot P.F_e$$

$$\therefore P.F_e = \frac{P_p}{\vec{V}_{load} \cdot |I_{aA_1}|} = \frac{22.6/3 \text{ K}}{135 \times |I_{aA_1}|} \quad \dots \textcircled{1}$$

$$\underline{\text{KCL}} \quad \vec{I}_{aA_1} = \vec{I}_{A_1N} + \vec{I}_{A_2N} + \vec{I}_{A_3N} \quad \dots \textcircled{2}$$

apparent power $\equiv V I \angle \theta \equiv \text{Real power/P.F}$

$$\Rightarrow 1) |I_{A_1N}| = \frac{6/3 \text{ K}}{V_e \times \text{P.F}} = 14.8148 \text{ Arms}$$

$$2) \phi = -\cos^{-1}(\text{P.F}) \quad , \quad \text{since } \theta = 0$$

$$= -0^\circ . 36^\circ$$

$$\vec{I}_{A_1N} = 14.8148 \angle -0^\circ \text{ Arms}$$

OR we solve it using complex power $S_i = \vec{V}_i \times \vec{I}_i^*$

already apparent

$$\rightarrow |\vec{I}_{A_2N}| = \frac{10/3}{135} K = 24.69 \text{ Arms}$$

$$\rightarrow \phi = -\cos^{-1}(P.F) = -16.26^\circ$$

$$\therefore \vec{I}_{A_2N} = 24.69 \times -16.26^\circ \text{ Arms.}$$

$$\rightarrow |\vec{I}_{A_3N}| = \frac{7/3}{135+0.85} K = 20.334 \text{ Arms}$$

$$\rightarrow \phi = -\cos^{-1}(0.85) = -31.788^\circ$$

$$\therefore \vec{I}_{A_3N} = 20.334 \times -31.788^\circ$$

plug in (2)

$$\vec{I}_{aA_1} = 55.8 - j17.6 = 58.5 \angle -17.5287^\circ$$

plug in (1)

$$P.F_e = \frac{22.6/3}{135+58.5} = 0.9535 \text{ lagging.}$$

$$(3) P_{lost} = (|\vec{I}_{aA_1}|)^2 * 3 * 0.1 = 1027.317 \text{ KWatt.}$$


$$\begin{aligned} (4) \quad \vec{V}_{bn} &= \vec{V}_S + \vec{V}_C \\ &= 0.1 * \vec{I}_{aA_1} + 135 \angle 0^\circ \\ &= 140.59 \times -0.718^\circ \end{aligned}$$

$$\begin{aligned} (5) \quad P.F_s &= \frac{1027.317/3 + (22.6/3) K}{140.5912 * 58.5183} = 0.9573 \text{ lagging.} \end{aligned}$$

first
exam

(8 marks) Q(1): Three loads are connected in parallel across 250V (rms) as shown in Fig.1. Load 1 absorbs 16kW and 28 kVA. Load 2 absorbs 10kVA at 0.6 leading PF. Load 3 absorbs 8kW at unity PF.

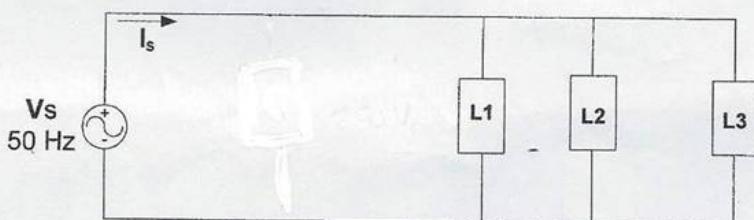- 1- Find the Impedance that is equivalent to the three parallel loads.
- 2- Find the power factor of the total load.
- 3- If the source operates at 50 Hz, find the value of the capacitor to be connected in order to improve the power factor to 0.96.



$$S_1 = 28 \angle 55^\circ 5^- \text{ kVA}$$

$$S_2 = 10 \angle -5^\circ \text{ kVA}$$

$$S_3 = 8 \angle 0^\circ \text{ kVA}$$

$$S_T = S_1 + S_2 + S_3 = 33.65 \angle 26.54^\circ \text{ kVA}$$

$$S_T = 250 \angle 0^\circ I_T^* = \underline{30.15} + j \underline{14.7} \text{ kA}$$

$$I_T = 134.2 \angle -26.5^\circ \text{ A}$$

$$\textcircled{1} \quad Z_T = \frac{V_T}{I_T} = \boxed{1.86 \angle 26.54^\circ} \text{ } \Omega$$

$$\textcircled{2} \quad P.F. = \cos 26.54^\circ = 0.89 \text{ lag}$$

$$\theta_{\text{new}} = \cos^{-1}(0.96) = 16.26^\circ$$

$$Q_{\text{new}} = 8.8 \text{ kVA}$$


$$Q_C = 14.7 - 8.8 = 5.2 \text{ kVA}$$

$$Q_C = \frac{V^2}{Z_C} \Rightarrow Z_C = 12 \Omega$$

$$Z_C = \frac{1}{2\pi f C} \Rightarrow \boxed{C = 3.14 \mu F}$$

(4 marks) Q(2): Fig.2 shows the instantaneous power $p(t)$ consumed by the load terminals, where the terminal voltage is given by $v(t) = V_m \cos(\omega t)$, then find the followings:

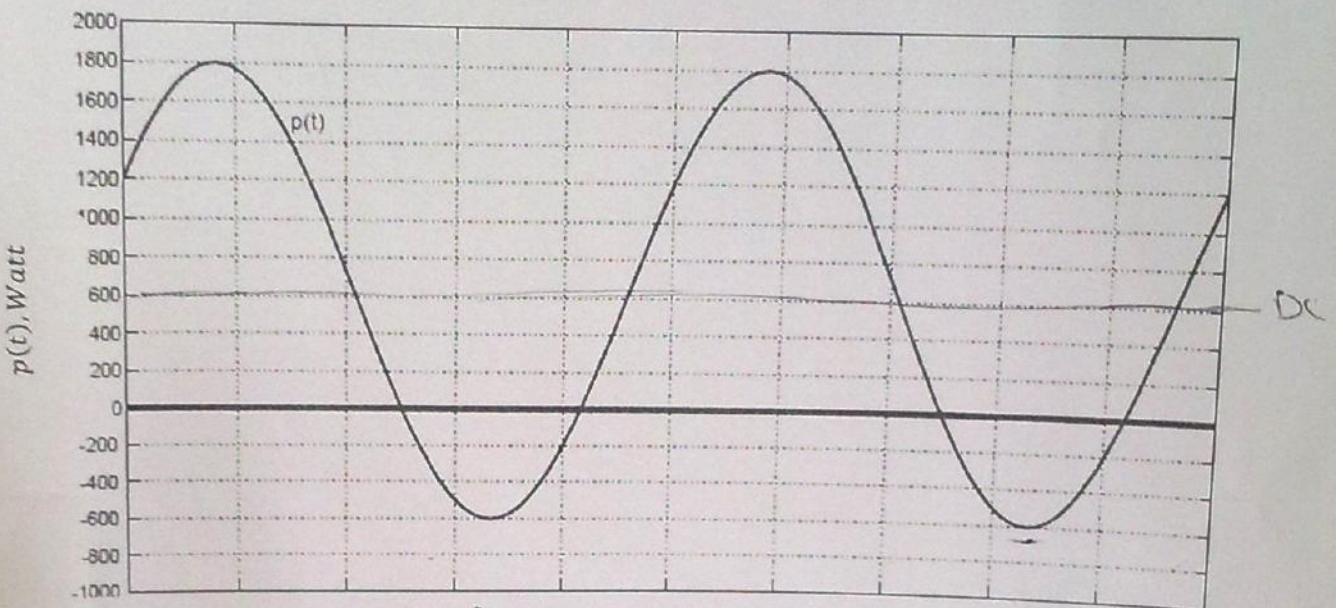- 1- PF.
- 2- The reactive power Q .
- 3- The Complex power S .



$$v(t) = V_m \cos(\omega t + \theta) \Rightarrow \theta = 0$$

Fig. 2

$$i(t) = I_m \cos(\omega t + \phi)$$

$$\Rightarrow p(t) = \frac{V_m I_m}{2} \cos(\theta - \phi) + \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi)$$

$$P = \frac{V_m I_m}{2} \cos(\theta - \phi) = 600$$

$$Q = \frac{V_m I_m}{2} \sin(\theta - \phi)$$

$$\Rightarrow p(t) = 600 + 1200 \cos(2\omega t + \theta + \phi)$$

$$PF = 1/2 \text{ lagging}$$

$$600 = 1200 \cos(\theta - \phi)$$

$$\Rightarrow \cos(0^\circ) = \cos(-60^\circ) \Rightarrow \text{from graph} \Rightarrow \theta + \phi = -60^\circ$$

$$\phi = -60^\circ \Rightarrow \theta - \phi = 60^\circ$$

$$Q = 1200 \sin(+60^\circ) = 1039.23 \text{ VAR}$$


$$Q = 1039.23 \text{ VAR}$$

$$S = (600 + j1039.23) \text{ VA}$$

$$S = 600 + j1039.23 \text{ VA}$$

(8 marks) Q(3): In the system shown in Fig.3, given $Z_Y = 20 + j8 \Omega$, and (+) phase sequence is assumed. If $I_{aA} = 20\angle-46^\circ A$ rms, and the source is operating with $PF = 0.94$ lagging, find the following:

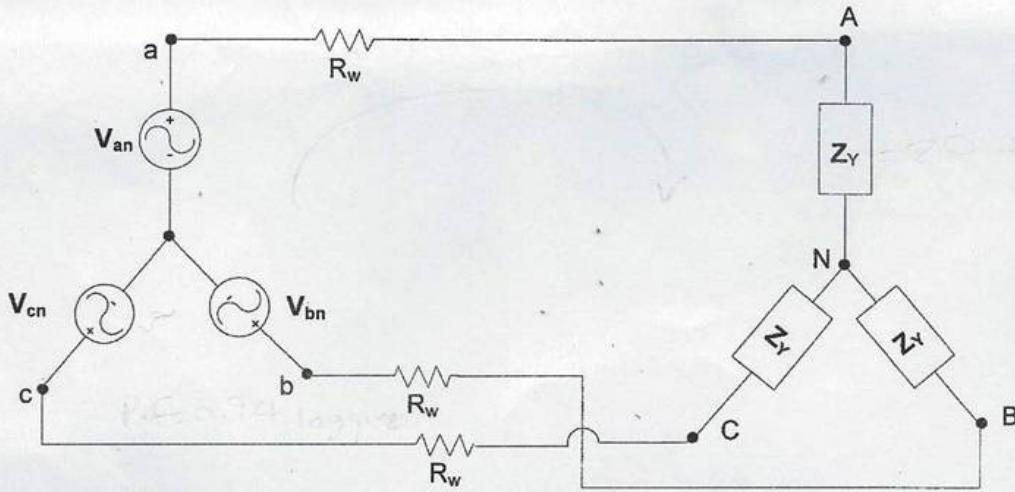- 1- R_w
- 2- The total complex power supplied by the source
- 3- V_{an} .
- 4- V_{AB} .



$$\text{① } Z_T = R_w + 20 + j8$$

$$PF = 0.94$$

$$\theta - \phi = \cos^{-1}(0.94) = 19.94^\circ$$

$$Z = a + jb = (R_w + 20) + j8$$

$$\therefore \theta - \phi \stackrel{\tan}{=} (19.94 = \tan \frac{8}{R_w + 20})$$

$$\frac{8}{R_w + 20} = \tan(19.94) = 0.362$$

$$\rightarrow R_w = \frac{8 - 20(0.362)}{0.362}$$

$$\boxed{R_w = 2.09}$$

$$\text{② } V_{an} = V_{an}^* = 2 I = (2.09 + 20 + j8) 20 \angle -46^\circ$$

$$\boxed{V_a = 469.88 \angle -26.99^\circ}$$

Fig.3

$$\text{③ } S_T = 3 \left[\frac{I \cdot Z_T}{\cos \phi} \right] = \frac{S_T \text{ (load)}}{3 (20)}$$

$$= (26.508 + j9.6) \text{ kVA}$$

$$= 26.11 / 19.94^\circ$$

$$\text{④ } V_{AN} = 2 I = (20 \angle 90^\circ) (20 \angle -46^\circ)$$

$$= \boxed{400 \angle -24^\circ}$$

$$\boxed{V_{AB} = \sqrt{3} (400 \angle -24 + 70^\circ)}$$



$$\boxed{V_{AB} = 746.18 \angle 5.8^\circ}$$

$$\boxed{R_w =}$$

5/3/2013

* Balanced Δ -connected load:

→ Y- Δ connected system:

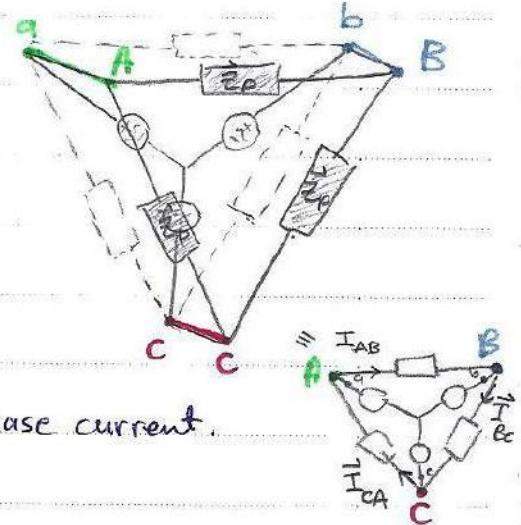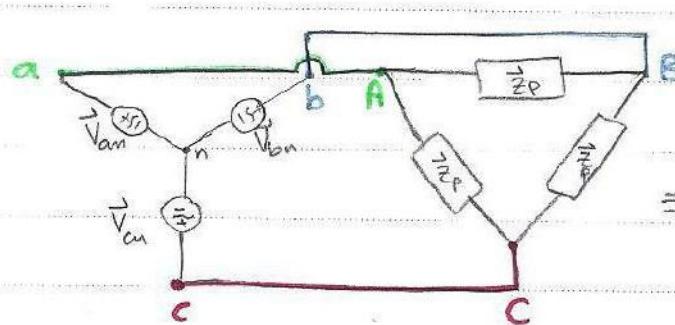

* In Δ -connected load, line current \neq phase current.

* In a balanced source:

$$V_p = |\vec{V}_{cn}| = |\vec{V}_{bn}| = |\vec{V}_{an}| \dots \text{Phase voltage}$$

$$V_L = |\vec{V}_{ab}| = |\vec{V}_{ca}| = |\vec{V}_{bc}| \dots \text{line voltage}$$

$$V_L = \sqrt{3} V_p$$

$$\vec{V}_{an} = V_p \angle 0^\circ$$

$$\vec{V}_{ab} = V_L \angle 30^\circ$$

$$\vec{V}_{bn} = V_p \angle -120^\circ$$

$$\vec{V}_{bc} = V_L \angle -90^\circ$$

$$\vec{V}_{an} = V_p \angle 120^\circ$$


$$\vec{V}_{ca} = V_L \angle -210^\circ$$

→ Phase currents: (since transmission lines has zero impedance).

$$\vec{I}_{AB} = \frac{\vec{V}_{AB}}{\vec{Z}_P} = \frac{\vec{V}_{ab}}{\vec{Z}_P} = \frac{V_L \angle 30^\circ}{|Z_P| \angle Z_P}$$

$$\vec{I}_{BC} = \frac{\vec{V}_{BC}}{\vec{Z}_P} = \frac{\vec{V}_{bc}}{\vec{Z}_P} = \frac{V_L \angle -90^\circ}{|Z_P| \angle Z_P}$$

$$\vec{I}_{CA} = \frac{\vec{V}_{CA}}{\vec{Z}_P} = \frac{\vec{V}_{ca}}{\vec{Z}_P} = \frac{V_L \angle 210^\circ}{|Z_P| \angle Z_P}$$

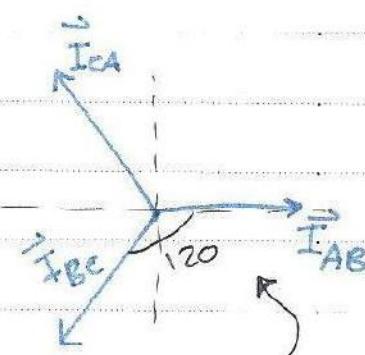

we assumed \vec{I}_{AB} to
be the reference
but that doesn't mean
that $\vec{I}_{AB} = 0$

* line currents:-

$$\vec{I}_{AA} = \vec{I}_{AB} + \vec{I}_{AC} = \vec{I}_{AB} - \vec{I}_{CA}$$

$$* \text{let } I_p = |\vec{I}_{AB}| = |\vec{I}_{BC}| = |\vec{I}_{CA}|$$


$$\therefore \vec{I}_{AA} = \sqrt{3} \vec{I}_p \times^{-30^\circ} = \vec{I}_L \times^{-30^\circ}$$

$$\vec{I}_{BB} = \vec{I}_{BC} + \vec{I}_{BA} = \vec{I}_{BC} - \vec{I}_{AB}$$

$$= \vec{I}_L \times^{-150^\circ}$$

$$\vec{I}_{CC} = \vec{I}_{CA} + \vec{I}_{CB} = \vec{I}_{CA} - \vec{I}_{BC}$$


$$= \vec{I}_L \times^{-270^\circ}$$

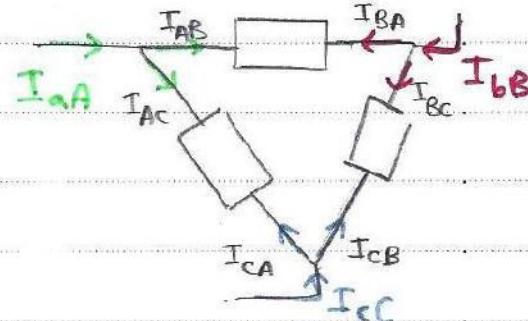

$$|I_L| = \sqrt{3} |I_p|$$

then \Rightarrow

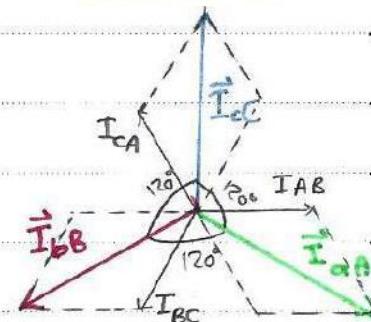$\vec{I}_{AA} = \sqrt{3} \times^{-30^\circ} \vec{I}_{AB}$
$\vec{I}_{BB} = \sqrt{3} \times^{-30^\circ} \vec{I}_{BC}$
$\vec{I}_{CC} = \sqrt{3} \times^{-30^\circ} \vec{I}_{CA}$



line currents.

ex: Determine the amplitude of the line currents in a 3-φ system with a ^{under load} _{line voltage} of $300\text{ V}_{\text{rms}}$ that supplies 1200 W to a Δ -connected load at a lagging p.f of 0.8, then find the phase impedance.

sol: I_L ? , \vec{Z}_p ?

$$|\vec{V}_{AB}| = |\vec{V}_{BC}| = |\vec{V}_{CA}| = 300\text{ V}_{\text{rms}}$$

\rightarrow the whole load absorbs 1200 W , \therefore one phase absorbs $\frac{1200}{3} = 400\text{ W}$

$$P_p = V_L \cdot I_p \cdot \text{P.F}$$

$$400 = 300 \times I_p \times 0.8$$

$$I_p = \frac{5}{3} A_{\text{rms}} = 1.667 A_{\text{rms}}$$

$$* I_L = \sqrt{3} I_p = 2.89 \text{ A}_{\text{rms}}$$

$$\vec{Z}_p = \frac{\vec{V}_{AB}}{\vec{I}_{AB}} = \frac{300 \times 0^\circ}{2.89 \times \vec{I}_{AB}} = 180 \times \vec{I}_{AB} = 180 \times 36.9^\circ$$

$$\therefore \vec{Z} = +\cos^{-1}(\text{P.F}) = \cos^{-1}(0.8) = 36.9^\circ$$


$$\vec{I}_{AB} = -\vec{Z} = -36.9^\circ \text{ S plug}$$

* Power in Y-load :

let ψ be the P.F angle

$$\therefore P_p = V_p I_p \cos(\psi)$$
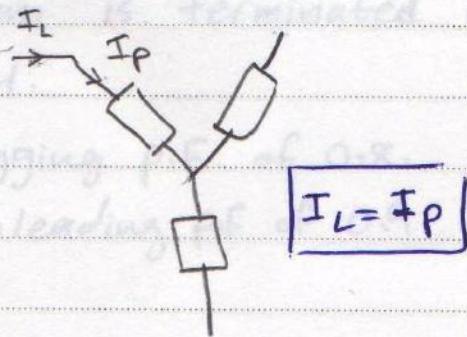
$$= \left(\frac{V_L}{\sqrt{3}} \right) I_L \cos(\psi)$$



$$\text{but... } P_{\text{total}} = 3 \times P_p$$

... in a balanced load.

$$= \sqrt{3} V_L I_L \cos(\psi)$$


* Power in Δ -load :

$$P_p = V_p I_p \cos(\psi)$$

$$\rightarrow P_p = V_L \left(\frac{I_L}{\sqrt{3}} \right) \cos(\psi)$$

$$P_{\text{total}} = 3 \times P_p$$
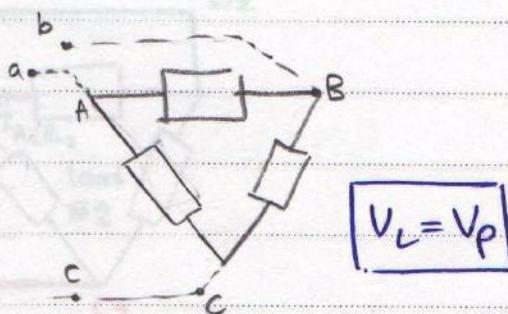
$$\rightarrow P_{\text{total}} = \sqrt{3} V_L I_L \cos(\psi)$$



for load

phase Voltage

$$\vec{V}_{AN} = V_p \angle 0^\circ$$

$$\vec{V}_{BN} = V_p \angle -120^\circ$$

$$\vec{V}_{CN} = V_p \angle -240^\circ$$

$$\vec{V}_{AB} = (\sqrt{3} \angle 30^\circ) \vec{V}_{AN}$$

$$= \sqrt{3} V_p \angle 30^\circ$$

$$\vec{V}_{BC} = (\sqrt{3} \angle 30^\circ) \vec{V}_{BN}$$

$$= \sqrt{3} V_p \angle -90^\circ$$

$$\vec{V}_{CA} = (\sqrt{3} \angle 30^\circ) \vec{V}_{CN}$$

$$= \sqrt{3} V_p \angle 240^\circ$$

line Voltages

$$I_{AA} = I_{AN} = \frac{\vec{V}_{AN}}{Z_p}$$

$$I_{BB} = I_{BN} = \frac{\vec{V}_{BN}}{Z_p}$$

$$I_{CC} = I_{CN} = \frac{\vec{V}_{CN}}{Z_p}$$

Phase current

Line current

$$\vec{V}_{AB} = \sqrt{3} V_p \angle 30^\circ$$

$$= V_{ab}$$

(if there's no $\frac{1}{2}$
in transmission lines)

$$\vec{V}_{AB}$$

$$\vec{V}_{BC}$$

$$I_{AB} = \frac{\sqrt{3} V_p}{Z_p} \angle 30^\circ$$

$$I_{BC} = \frac{\sqrt{3} V_p}{Z_p}$$

$$I_{CA} = \frac{\sqrt{3} V_p}{Z_p} \angle 240^\circ$$

$$I_{AA} = (\sqrt{3} \angle 30^\circ) \frac{\vec{V}_{AB}}{Z_p}$$

$$= (\sqrt{3} \angle 30^\circ) I_{AB}$$

$$I_{BB} = (\sqrt{3} \angle 30^\circ) I_{BC}$$

$$I_{CC} = \sqrt{3} \angle 30^\circ I_{CA}$$

For both Δ & Y

$$P_{\text{phase}} = \sqrt{3} I_L \cos(\theta - \phi)$$

7/3/2013

ex: A Balanced 3-Φ, 3-wires system is terminated with 2 Δ-connected loads in parallel.

→ load #1 draws 40K VA at lagging p.F of 0.8.

→ load #2 absorbs 24K Watt at leading p.F of 0.9


assume $\vec{V}_{ab} = 440 \angle 30^\circ$ V, find:

1. Total power drawn by the 2 loads.

2. The phase current $\vec{I}_{A_1B_1}$ for the lagging load

3. $\vec{I}_{A_2B_2}$

4. \vec{I}_{aA}

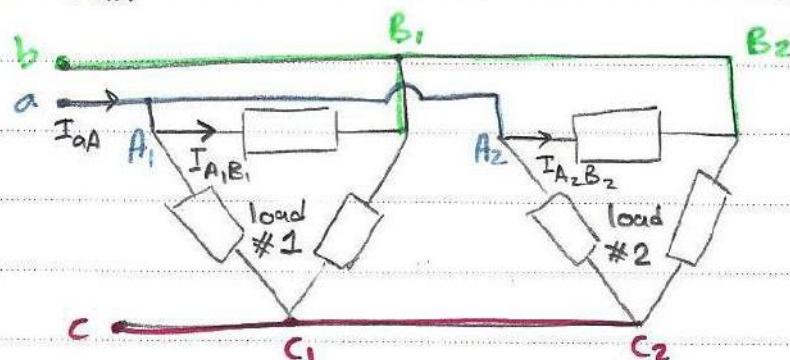

Sol:-

apparent P × p.F

$$1) P_{\text{total}} = 40 \text{ KVA} \times 0.8 + 24 \text{ K} = 56 \text{ K Watt}$$

$$2) \vec{I}_{A_1B_1} = \frac{\vec{V}_{A_1B_1}}{\vec{Z}_1} = \frac{\vec{V}_{ab}}{\vec{Z}_1} = \frac{440 \angle 30^\circ}{|Z_1| \cos^2(\text{p.F.})} = \frac{440 \angle 30^\circ}{|Z_1|}$$

$$|\vec{I}_{A_1B_1}| \rightarrow \text{Veff} \quad \text{Ieff} \quad \cos(\theta-\phi)$$

$$P_p \Rightarrow \frac{440}{40} |I_{AB}| \times \text{p.F.} = 40 \times 0.8 / 3$$

$$|I_{A_1B_1}| = \frac{(40/3) \text{ K}}{440} = 30.303 \text{ A}_{\text{rms}}$$

$$\therefore \vec{I}_{A_1B_1} = 30.303 \angle -6.87^\circ$$

$$3) \vec{I}_{A_2B_2} = \frac{\vec{V}_{ab}}{|\vec{z}_2| \cancel{-\cos^2(PF)}} = \frac{440}{|\vec{z}_2|} \cancel{\times 30 + \cos^2(0.9)} - \textcircled{1}$$

$$\rightarrow P_{P_2} \Rightarrow \frac{24}{3} K = 440 \times |\vec{I}_{A_2B_2}| \times P.F$$

$$|\vec{I}_{A_2B_2}| = 20.202 \text{ --- \textcircled{2}}$$

from \textcircled{2}: $\vec{I}_{A_2B_2} = 20.202 \angle 55.84^\circ$

$$4) \vec{I}_{aA} = \sqrt{3} \cancel{\times -30} \vec{I}_{AB}$$

$$\hookrightarrow \vec{I}_{AB} = \vec{I}_{A_1B_1} + \vec{I}_{A_2B_2}$$

$$\vec{I}_{aA} = \sqrt{3} \cancel{\times -30} (\vec{I}_{AB_1} + \vec{I}_{AB_2}) = 29.26 \cancel{\times -12.47^\circ} A$$


$Y \leftrightarrow \Delta$ transformation

$Y \rightarrow \Delta:$

$$Z_A = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2} = \frac{Z_L}{Z_2}$$

$$Z_B = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3} = \frac{Z_L}{Z_3}$$
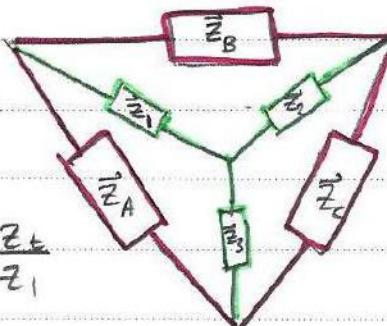
$$Z_C = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1} = \frac{Z_L}{Z_1}$$



for a balanced source:

$$Z_1 = Z_2 = Z_3 = Z_Y$$

$$Z_A = Z_B = Z_C = Z_\Delta$$

$$\text{where, } Z_Y = \vec{Z}_\Delta / 3$$


$\Delta \rightarrow Y:$

$$Z_1 = \frac{Z_A \times Z_B}{Z_A + Z_B + Z_C}$$

$$Z_2 = \frac{Z_B \times Z_C}{Z_A + Z_B + Z_C}$$

$$Z_3 = \frac{Z_A \times Z_C}{Z_A + Z_B + Z_C}$$


* Analog Wattmeter:

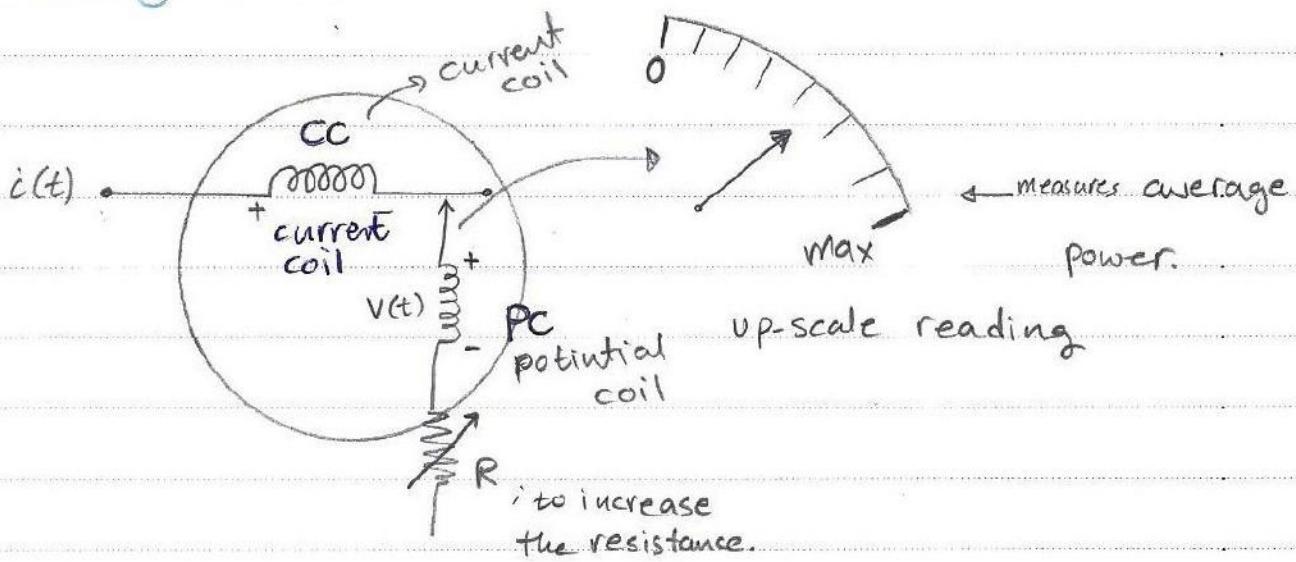



- * Current coil (CC) is made of heavy wire

- * PC is made of a fine wire, relatively light, low resistance.

- * PC has a greater number of turns.

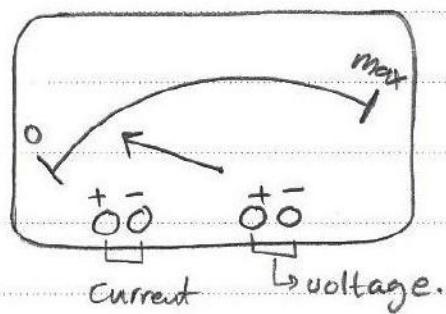

- * How to connect it with load?!

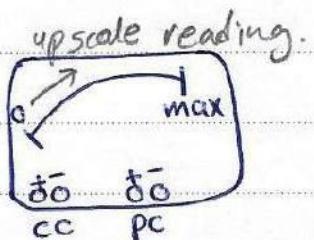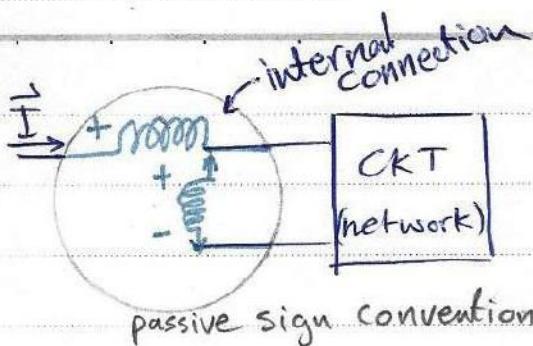


p: +ve quantity \rightarrow absorbs

-ve \leftarrow \rightarrow delivers; there will be no reading
(because it's an upscale).

(we reverse the order of PC to have a reading).

Ex:- Determine the wattmeter reading state whether or not the potential coil had to be reversed in order to obtain an upscale reading, & identify the device(s) absorbing or generating this power.

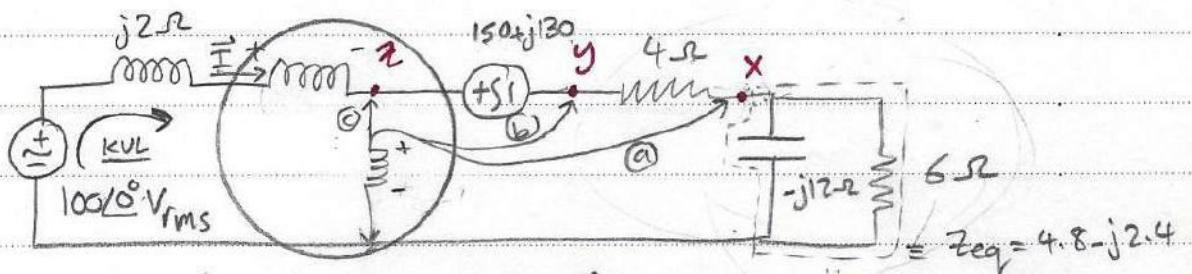The +ve terminals of the wattmeter is connected to: a) X. b) Y. c) Z.




$$\text{sol: } \vec{I} ? \text{ KVL} \quad -100\angle 0^\circ + j2\vec{I} + (150+j130) + 4\vec{I} + (4.8-j2.4)\vec{I} = 0$$

$$\vec{I} = \frac{-(150+j130)}{4+j2+4.8-j2.4} = -5-j15 = 15.81 \angle -108.43^\circ$$

a) $P_x = |\vec{I}|^2 \operatorname{Re}\{Z\} = (15.81)^2 \times 4.8 = 1200 \text{ Watt absorbs, no change to PC.}$

b) $P_y = |\vec{I}|^2 \operatorname{Re}\{4.8-2.4j+4\} = (15.81)^2 \times (6.8) = 2200 \text{ Watt absorbs.}$

$$c) P_2 = P_y + P_{\text{source}}$$

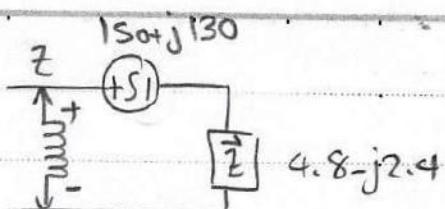

$$P_{\text{source}} = |\vec{V}_{2y}| |\vec{I}| \cos(\theta - \phi)$$


$$= 198.49 \times 15.81 \times \cos(40.914^\circ + 108.43^\circ)$$

= -2700 Watt ; delivers Power


$$P_2 = 2200 - 2700 = -500 \text{ watt} ; \text{ also delivers power}$$

\therefore PC connection has to be reversed.



Wattmeter in 3-φ system

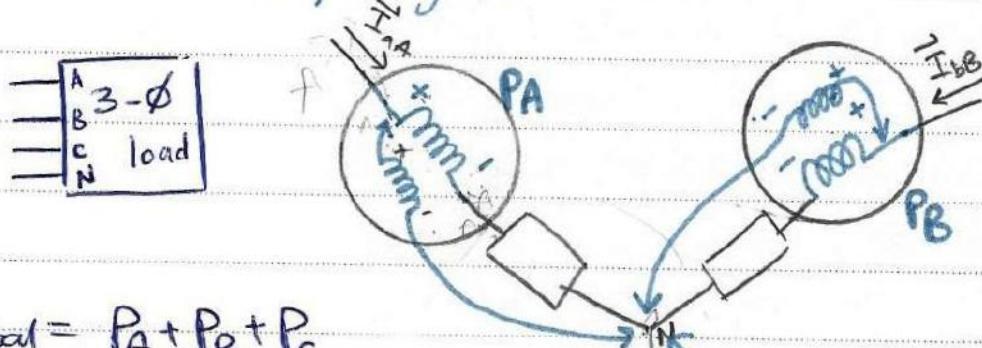

$$P_{\text{total}} = P_A + P_B + P_C$$

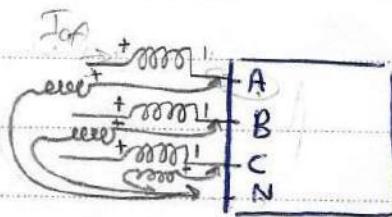

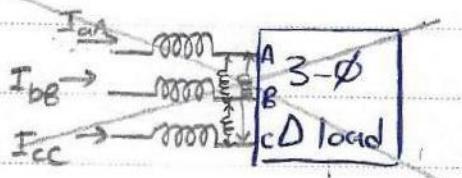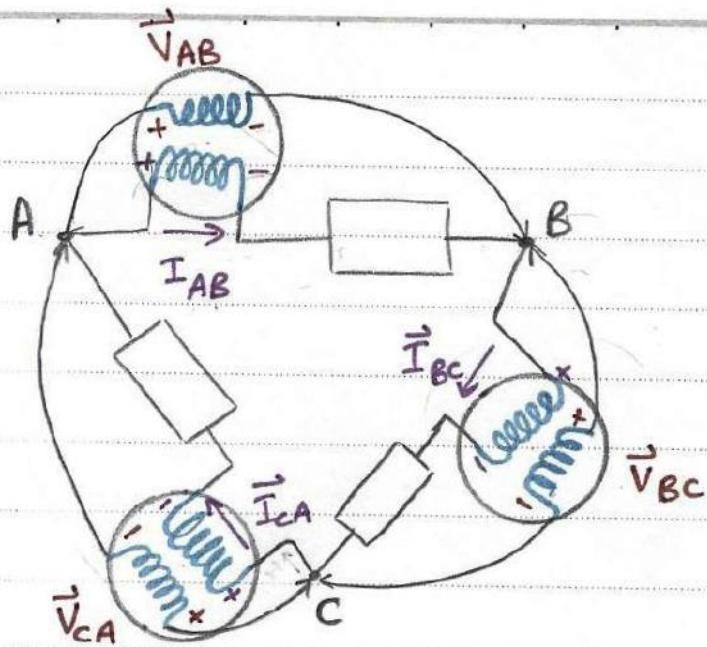
the problem↑ is that neutral label isn't always accessible.



doesn't read the right power, since

$$I_{aA} \neq I_{AB}$$

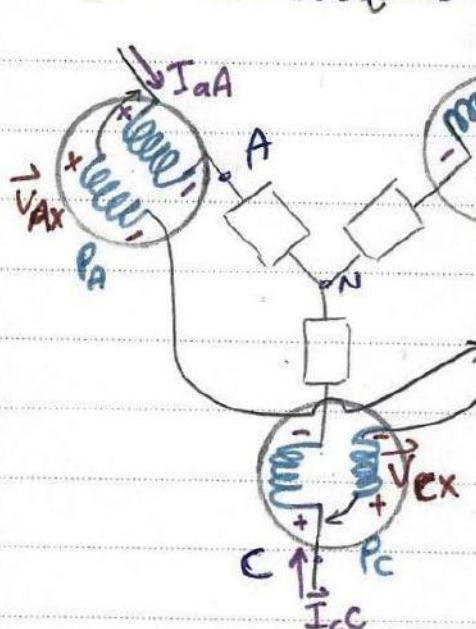problem in Δ that the phase load is not accessible.



$$P_A = \frac{1}{T} \int V_{AX}(t) i_{aA}(t) dt$$

$$P_B = \frac{1}{T} \int V_{BX}(t) i_{BB}(t) dt$$

$$P_C = \frac{1}{T} \int V_{CX}(t) i_{CC}(t) dt$$

$$P_{\text{total}} = P_A + P_B + P_C \quad \therefore \textcircled{1}$$

$$V_{AX}^{(t)} = V_{AN}^{(t)} + V_{NX}^{(t)}$$

$$V_{BX}^{(t)} = V_{BN}^{(t)} + V_{NX}^{(t)}$$

$$V_{CX}^{(t)} = V_{CN}^{(t)} + V_{NX}^{(t)}$$

in this case $P_{3\phi} \neq 3P_\phi$

$$P_{\text{total}} = \frac{1}{T} \int (V_{AX}(t) i_{aA}(t) + V_{BX}(t) i_{BB}(t) + V_{CX}(t) i_{CC}(t)) dt \quad \leftarrow V_{CX}^{(t)} = V_{CN}^{(t)} + V_{NX}^{(t)}$$

$$P_{\text{total}} = \frac{1}{T} \int_T (V_{AN}(t) i_{AA}(t) + V_{BN}(t) i_{BB}(t) + V_{CN}(t) i_{CC}(t)) dt + \frac{1}{T} \int_T V_{NX} \underbrace{(i_{AA}(t) + i_{BB}(t) + i_{CC}(t))}_{0 \text{ by KCL}} dt$$

$$\begin{aligned} P_t &= \frac{1}{T} \int_T (V_{AN}(t) i_{AA}(t) + V_{BN}(t) i_{BB}(t) + V_{CN}(t) i_{CC}(t)) dt \\ &= \frac{1}{T} \int_T V_{AN}(t) i_{AA}(t) dt + \frac{1}{T} \int_T V_{BN}(t) i_{BB}(t) dt + \frac{1}{T} \int_T V_{CN}(t) i_{CC}(t) dt \end{aligned}$$

$P_t = P_A + P_B + P_C$ same as before, so we can connect P_C with $X^{(\text{any point})}$ instead of N and still get the same readings!!

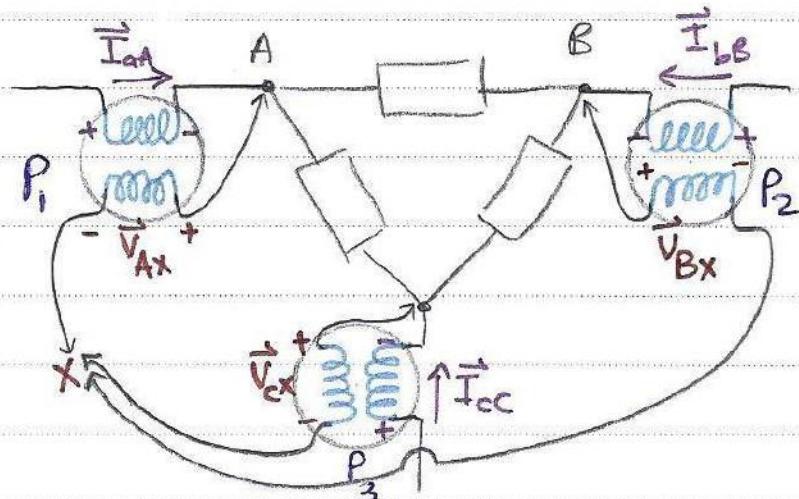



Fig. 1

$$P_{\text{total}} = P_1 + P_2 + P_3 = \frac{1}{T} \int i_{AA}(t) V_{Ax}(t) dt + \frac{1}{T} \int i_{BB}(t) V_{Bx}(t) dt \dots \textcircled{1}$$

$$+ \frac{1}{T} \int i_{CC}(t) V_{Cx}(t) dt$$

$$\begin{aligned} & \rightarrow i_{AA}(t) = i_{AB}(t) - i_{CA}(t) \\ & i_{CC}(t) = i_{CA}(t) - i_{BC}(t) \\ & i_{BB}(t) = i_{BC}(t) - i_{AB}(t) \end{aligned} \quad \left. \right\} \text{ plug them in } \textcircled{1}$$


$$\begin{aligned} P_t &= \frac{1}{T} \int i_{AB}(V_{Ax} - V_{Bx}) + i_{CA}(V_{Cx} - V_{Ax}) + i_{BC}(V_{Bx} - V_{Cx}) dt \\ &= \frac{1}{T} \int i_{AB} V_{AB} dt + \frac{1}{T} \int i_{CA} V_{CA} dt + \frac{1}{T} \int i_{BC} V_{BC} dt \\ &= P_A + P_C + P_B \text{ as before} \end{aligned}$$

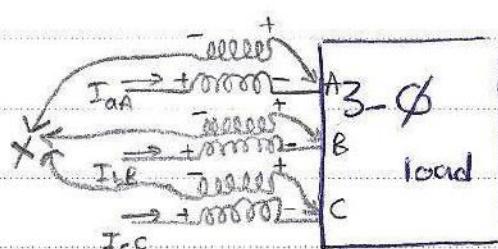

ex 1: A balanced Y-connected source is supplying an unbalanced Y-connected load.

Given $V_{ab} = 100 \angle 0^\circ$ V (rms) \leftarrow فرضي

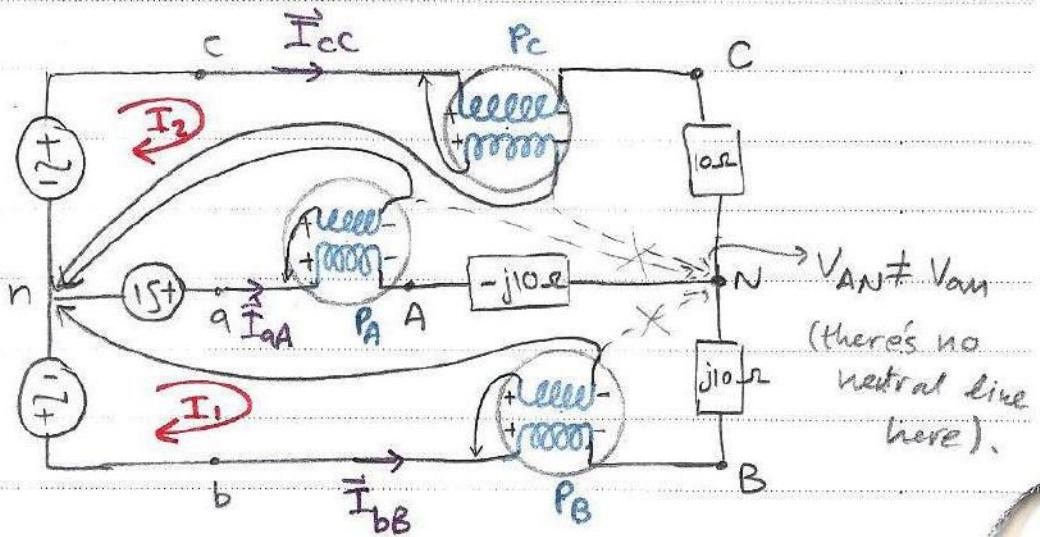- calculate the avg power absorbed by each load.



$$\text{Sol: } V_L = 100 \text{ V}$$

$$V_{ab} = 100 \angle 0^\circ \text{ V}$$

$$V_{bc} = 100 \angle -120^\circ \text{ V}$$

$$V_{ca} = 100 \angle 120^\circ \text{ V}$$

$$V_{an} = \frac{100}{\sqrt{3}} \angle -30^\circ \text{ V}$$

$$V_{bn} = 100/\sqrt{3} \angle -150^\circ \text{ V}$$

$$V_{cn} = 100/\sqrt{3} \angle -270^\circ \text{ V}$$

mesh analysis:-

@ loop 1:-

$$-V_{ab} - j10(I_1 - I_2) + j10I_1 = 0$$

$$\vec{I}_2 = \frac{100}{j10} \angle 0^\circ = 10 \angle -90^\circ \text{ Arms}$$

@ loop 2:-

$$-V_{ca} + 10I_2 - j10(I_2 - I_1) = 0$$

$$\vec{I}_1 = 18.66 - j5 \text{ Arms}$$

$$\vec{I}_{cc} = \vec{I}_2 = 10 \angle -90^\circ \text{ Arms}$$

$$\vec{I}_{bb} = -\vec{I}_1 = -18.66 + j5 \text{ Arms}$$

$$\vec{I}_{aa} = \vec{I}_1 - \vec{I}_2 = 19.318 \angle 15^\circ \text{ Arms}$$

$$P_A = |\vec{V}_{an}| |\vec{I}_{aa}| \cos(\text{ang } \vec{V}_{an} - \text{ang } \vec{I}_{aa})$$

$$= \frac{100}{\sqrt{3}} \times 19.318 \times \cos(-30 - 15^\circ) = 788.7 \text{ Watt delivered power}$$

(we used active sign convention).

$$P_B = |\vec{V}_{bn}| |\vec{I}_{bb}| \cos(\text{ang } \vec{V}_{bn} - \text{ang } \vec{I}_{bb}) = 788.7 \text{ W}$$

delivered by
the source.

$$P_c = |\vec{V}_{an}| |\vec{I}_{cc}| \cos(\text{ang } \vec{V}_{an} - \text{ang } \vec{I}_{cc})$$

= -527.35 \text{ Watt; absorbed power}

$P_{\text{total}} = P_A + P_B + P_c = 1000 \text{ Watt; delivered by the source}$

- * If a system isn't balanced we solve 3 CKTs per phase only if there's a neutral line.



- * If it's balanced I solve 1 phase and apply $\pm 120^\circ$ shift to the others. \rightarrow no N-lines reqd.

→ OR $P_{\text{total}} = |\vec{I}_{cc}|^2 \times 10 = 1000 \text{ W}$ (because $-j10 \& j10$ doesn't absorb avg power).

* The Two Wattmeter method:

in Fig 1, let X be A $\Rightarrow \vec{V}_{AX} = \vec{V}_{AA} = 0$

$$\rightarrow P_T = P_2 + P_3$$

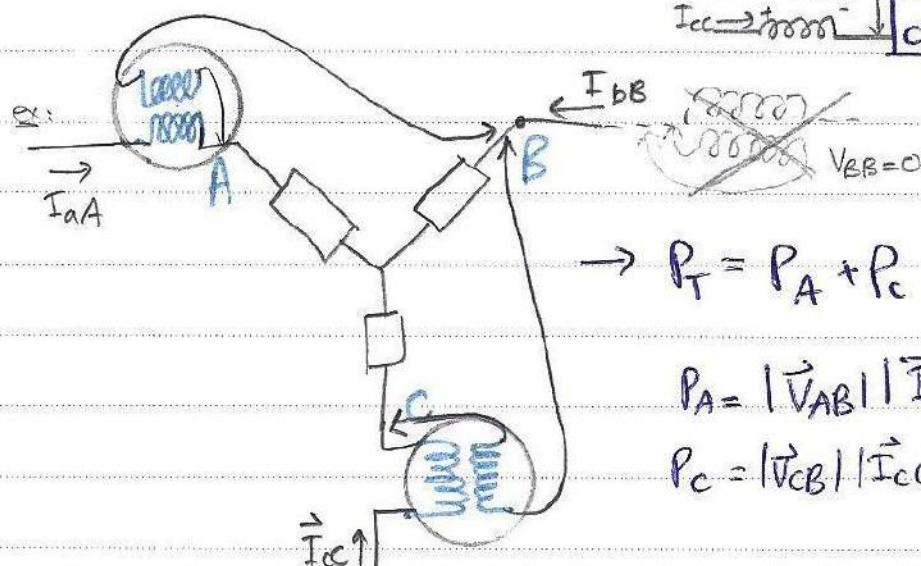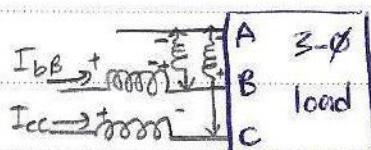


$$\rightarrow P_T = P_A + P_C$$

$$P_A = |\vec{V}_{AB}| |\vec{I}_{aa}| \cos(\text{ang } \vec{V}_{AB} - \text{ang } \vec{I}_{aa})$$

$$P_C = |\vec{V}_{CB}| |\vec{I}_{cc}| \cos(\text{ang } \vec{V}_{CB} - \text{ang } \vec{I}_{cc})$$

Return to ex1:

using 2 wattmeters:-

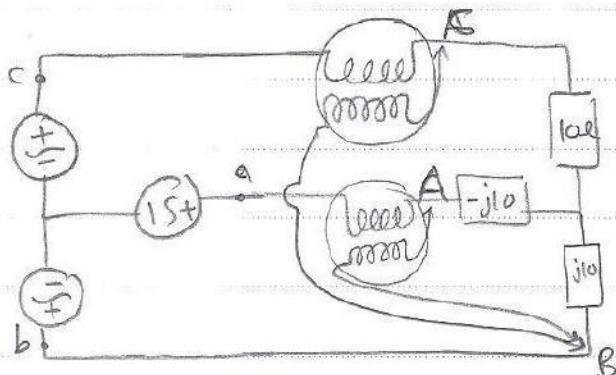

$$P_A = (19.318)(100)\cos(0 - 15^\circ)$$
$$= 1868 \text{ Watt}$$


$$P_C = (100)(10) \cos(60 + 90^\circ)$$
$$= -866 \text{ Watt}$$

$$P_T = 1000 \text{ Watt} \quad \times$$

$$V_{cb} = 100\angle 60^\circ \text{ V}$$

14 / 3 / 2013

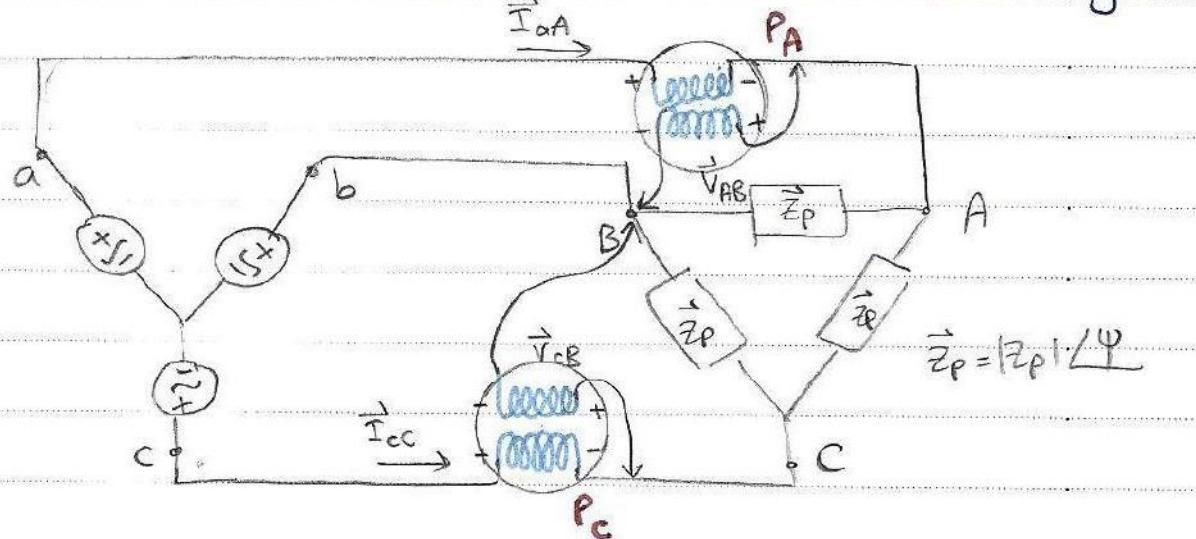* Power factor from the 'two wattmeter' readings.



$$P_{\text{total}} = P_A + P_C$$

$$\text{P.F. ?} \rightarrow \Psi ?$$

$$P_A = |\vec{V}_{AB}| |\vec{I}_{aa}| \cos(\text{ang } \vec{V}_{AB} - \text{ang } \vec{I}_{aa}) \dots \textcircled{1}$$

$$\begin{aligned} \vec{I}_{aa} &= \sqrt{3} \times -30^\circ \vec{I}_{AB} \\ &= \sqrt{3} \times -30^\circ (\vec{V}_{AB} / \vec{Z}_p) \end{aligned}$$

$$\therefore |\vec{I}_{aa}| \times \vec{I}_{aa} = \sqrt{3} \times -30^\circ |\vec{V}_{AB}| \times \vec{V}_{AB} / |Z_p| \times 0^\circ$$

$$\text{ang } \vec{I}_{aa} = -30 + \text{ang } (\vec{V}_{AB}) - \Psi$$

$$\therefore \text{ang } (\vec{V}_{AB}) - \text{ang } (\vec{I}_{aa}) = \Psi + 30$$

Plug in \textcircled{1}

$$\boxed{P_A = V_i I_i \cos(\Psi + 30)}$$

$$P_C = |\vec{V}_{CB}| |\vec{I}_{cc}| \cos(\text{ang } \vec{V}_{CB} - \text{ang } \vec{I}_{cc}) \dots \textcircled{2}$$

$$\vec{I}_{cc} = \sqrt{3} \times -30^\circ \vec{I}_{CA}$$

$$= \sqrt{3} \times -30^\circ (\vec{I}_{BC} \times -120^\circ)$$

$$= \sqrt{3} \times -30^\circ (\vec{I}_{CB} \angle -120 + 180^\circ) = \sqrt{3} \vec{I}_{CB} \times 30^\circ$$

$$\rightarrow |\vec{I}_{cc}| \times \vec{i}_{cc} = \frac{\sqrt{3} \angle 30^\circ \vec{v}_{cb}}{|\vec{Z}_p|} = \frac{\sqrt{3} \angle 30^\circ |V_{cb}|}{|\vec{Z}_p|} \delta \vec{v}_{ce}$$

plug in ② :-

$$P_c = V_L I_L \cos(\Psi - 30^\circ)$$

$$\therefore \frac{P_A}{P_c} = \frac{\cos(\Psi + 30^\circ)}{\cos(\Psi - 30^\circ)}$$

$$= \frac{\cos \Psi \cos 30^\circ - \sin \Psi \sin 30^\circ}{\cos \Psi \cos 30^\circ + \sin \Psi \sin 30^\circ} \times \left(\frac{\cos \Psi \cos 30^\circ}{\cos \Psi \cos 30^\circ} \right)$$

$$\frac{P_A}{P_c} = \frac{1 - \tan \Psi \tan 30^\circ}{1 + \tan \Psi \tan 30^\circ}$$

$$P_A + \frac{P_A}{\sqrt{3}} \tan \Psi = P_c - \frac{P_c}{\sqrt{3}} \tan \Psi$$

$$\frac{\tan \Psi}{\sqrt{3}} (P_A + P_c) = P_c - P_A$$

$$\therefore \tan \Psi = \sqrt{3} \left(\frac{P_c - P_A}{P_c + P_A} \right) \quad 4 \text{ cases!}$$

1. if $P_c = P_A \Rightarrow \tan \Psi = 0$ $\Psi = 0 \quad \left. \begin{array}{l} P.F = 1 \\ (\text{pure resistive load}) \end{array} \right.$

2. if $P_c = -P_A \Rightarrow \tan \Psi = \infty$ $\Psi = \pm 90^\circ \quad \left. \begin{array}{l} P.F = 0 \\ (\text{pure reactive load}) \end{array} \right.$

3. if $P_c > P_A \Rightarrow \tan \Psi, \Psi \text{ +ve} \rightarrow P.F \text{ lagging}$
 $(\text{inductive load}).$

4. if $P_A > P_c \Rightarrow \tan \Psi \rightarrow \Psi \text{ -ve} \rightarrow P.F \text{ leading}$
 $(\text{capacitive load}).$

$$\tan \Psi = \frac{\sqrt{3} (P_1 - P_2)}{P_1 + P_2}$$

** If we don't know which terminal is A and which is C, or the common terminal was A or C instead of B, then:

$\tan \Psi = \frac{\sqrt{3} (P_1 - P_2)}{P_1 + P_2}$, can be used to

find the magnitude of Ψ , but not its sign
then we can only determine the magnitude of the power factor without telling if it's leading or lagging.


→ to find the sign of Ψ (if p.f is leading or lagging):-

→ Add a high reactive load in parallel with the original load.

- If the reactive load is 3-φ capacitive
 - if the magnitude of Ψ decreases, then the original load is inductive (lagging p.f)
 - if the magnitude of Ψ increases, then the original load is capacitive (leading p.f)

Ex: A Balanced load is fed by a balanced source with $\vec{V}_{ab} = 230 \angle 0^\circ V_{rms}$, find:

P_1 , P_2 & P_{total} ?

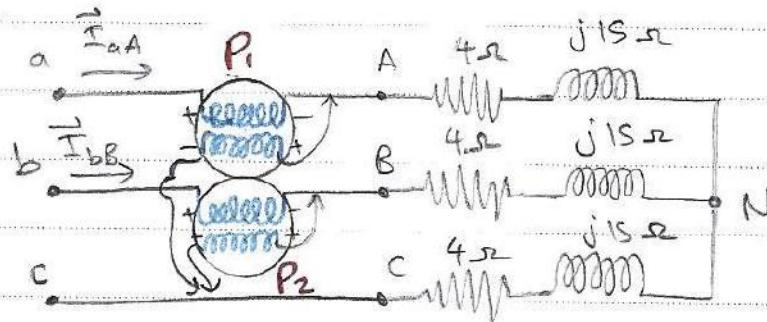

$$\bullet P_1 = |\vec{V}_{AC}| |\vec{I}_{aA}| \cos(\text{ang } \vec{V}_{AC} - \text{ang } \vec{I}_{aA}) \quad \text{...①}$$

$$\text{but } \vec{V}_{bc} = 230 \angle -120^\circ V_{rms}$$

$$\vec{V}_{ca} = 230 \angle -240^\circ V_{rms}$$

$\vec{V}_{CA} = \vec{V}_{CA}$; since there's no impedance through transmission lines.

$$\hookrightarrow \vec{V}_{AC} = 230 \angle -240 + 180^\circ = 230 \angle -60^\circ V_{rms}$$

$$\hookrightarrow \vec{I}_{aA} = \frac{\vec{V}_{AN}}{Z_P} = \frac{\vec{V}_{AN}}{4 + j15} = \frac{230 \angle -30^\circ}{4 + j15} = 8.554 \angle -105.1^\circ A_{rms}$$

Plug in ①

$$P_1 = (230)(8.554) \cos(-60 + 105.1)$$

$$= 1389 \text{ Watt}$$

$$\bullet P_2 = |\vec{V}_{BC}| |\vec{I}_{bB}| \cos(\text{ang } \vec{V}_{BC} - \text{ang } \vec{I}_{bB}) \quad \text{...②}$$

$$\hookrightarrow \vec{I}_{bB} = \vec{I}_{aA} \angle -120^\circ$$

$$= 8.554 \angle -225.1^\circ \text{ Arms}$$

$$\hookrightarrow \vec{V}_{BC} = \vec{V}_{BC} = 230 \angle -120^\circ V_{rms}$$


$$\text{Plug in ②} \quad P_2 = (230)(8.554) \cos(-120 + 225.1) = -512.5 \text{ Watt}$$

$$\therefore P_{total} = P_1 + P_2 = 876.5 \text{ Watt}$$

17/3/2013

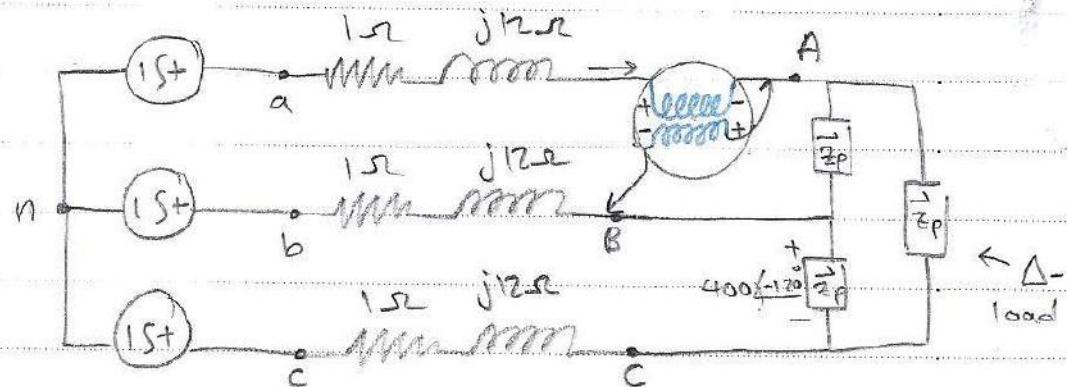Example 1: The Wattmeter reading of 3-φ balanced load is 2400 Watt & has a p.f of 0.9196 lagging. Assume +ve phase sequence, find:

- the power consumed by the load.
- the line current \vec{I}_{bb} & phase current \vec{I}_{bc} of the load.
- The voltage \vec{V}_{bn} & \vec{V}_{an}
- Calculate \vec{z}_p & total power loss of the line.
- the complex power supplied by the source.



Sol:- $\vec{V}_{AB} = 400\angle 0^\circ$

in (a) $P = 2400 \times 3$ Be careful, it's
not the same current! it's I_{ab}
not I_{AB} .

$\vec{V}_{CA} = 400\angle 120^\circ$

$\vec{V}_{AC} = 400\angle -60^\circ$

$2400 = |\vec{V}_{AB}| |\vec{I}_{ab}| \cos(\text{ang } \vec{V}_{AB} - \text{ang } \vec{I}_{ab})$ $\hat{\equiv} \text{p.f.}$

$2400 = 400 |\vec{I}_{ab}| \times 0.9196$

$|\vec{I}_{ab}| = 6.525 \text{ Arms}_{rms}$

but... $\cos(\text{ang } \vec{V}_{AB} - \text{ang } \vec{I}_{ab}) = \text{p.f.}$

$-\text{ang } \vec{I}_{ab} = \cos^{-1} 0.9196$

$\text{ang } \vec{I}_{ab} = -23.132^\circ$

$\vec{I}_{ab} = 6.525 \angle -23.132^\circ \text{ Arms}_{rms}$

$$\therefore \vec{I}_{aA} = \sqrt{3} \times 30^\circ \vec{I}_{AB}$$

$$|I_{AB}| = |I_{aA}|/\sqrt{3} = 3.767 \text{ Arms}$$

$$\text{ang } \vec{I}_{AB} = (\text{ang } I_{aA} + 30) = 6.867^\circ$$


$$\Rightarrow \vec{I}_{AB} = 3.767 \times 6.867^\circ$$

$$\begin{aligned} a) P_A &= |\vec{V}_{AB}| |\vec{I}_{AB}| \cos(\text{ang } \vec{V}_{AB} - \text{ang } \vec{I}_{AB}) \\ &= 1495.99 \text{ Watt} \end{aligned}$$

$$P_{\text{total}} = P_A \times 3 = 4487.966 \text{ Watt}; \text{ since it's balanced}$$

$$b) \vec{I}_{bB} = 6.525 \times -23.132 - 120^\circ = 6.525 \times -143.132^\circ$$

$$\vec{I}_{BC} = 3.767 \times -113.132^\circ \text{ Arms} \rightarrow (I_{aB} \angle -120)$$

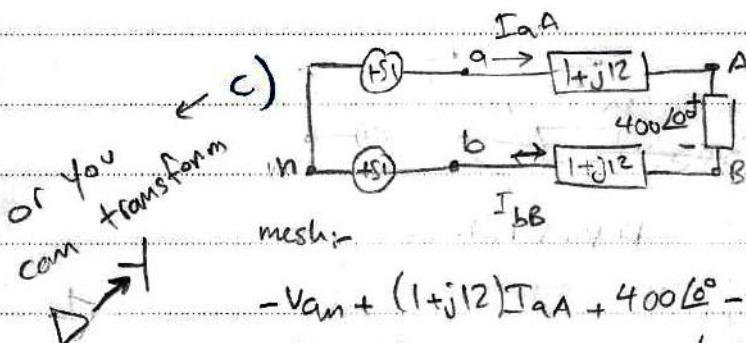

Mash 6. Waves 11.19

$$V_{an} = 241.19 \times 11.0^\circ \text{ V}_\text{rms}$$

$$-V_{an} + (1+j12)I_{aA} + 400\angle 0^\circ - (1+j12)I_{bB} + V_{bn} = 0$$

$$V_{bn} - V_{an} = -417.75 \angle 18.998^\circ \rightarrow V_{an} \angle 120^\circ - V_{an} = -417.75 \angle 18.998^\circ$$

$$d) \vec{Z}_p = \vec{V}_{AB} / \vec{I}_{AB}$$

$$= 400\angle 0^\circ / 3.767 \times 6.867^\circ = 106.185 \times -6.867^\circ$$


$$P_L = 3 \times |\vec{I}_{aA}|^2 (1) = 127.71 \text{ Watt}$$

$$e) \vec{S}_p = \vec{V}_{an} \cdot \vec{I}_{aA}^* = 1573.76 \times 17.867^\circ$$

$$\sum S_{\text{total}} = 3 \times \vec{S}_p.$$

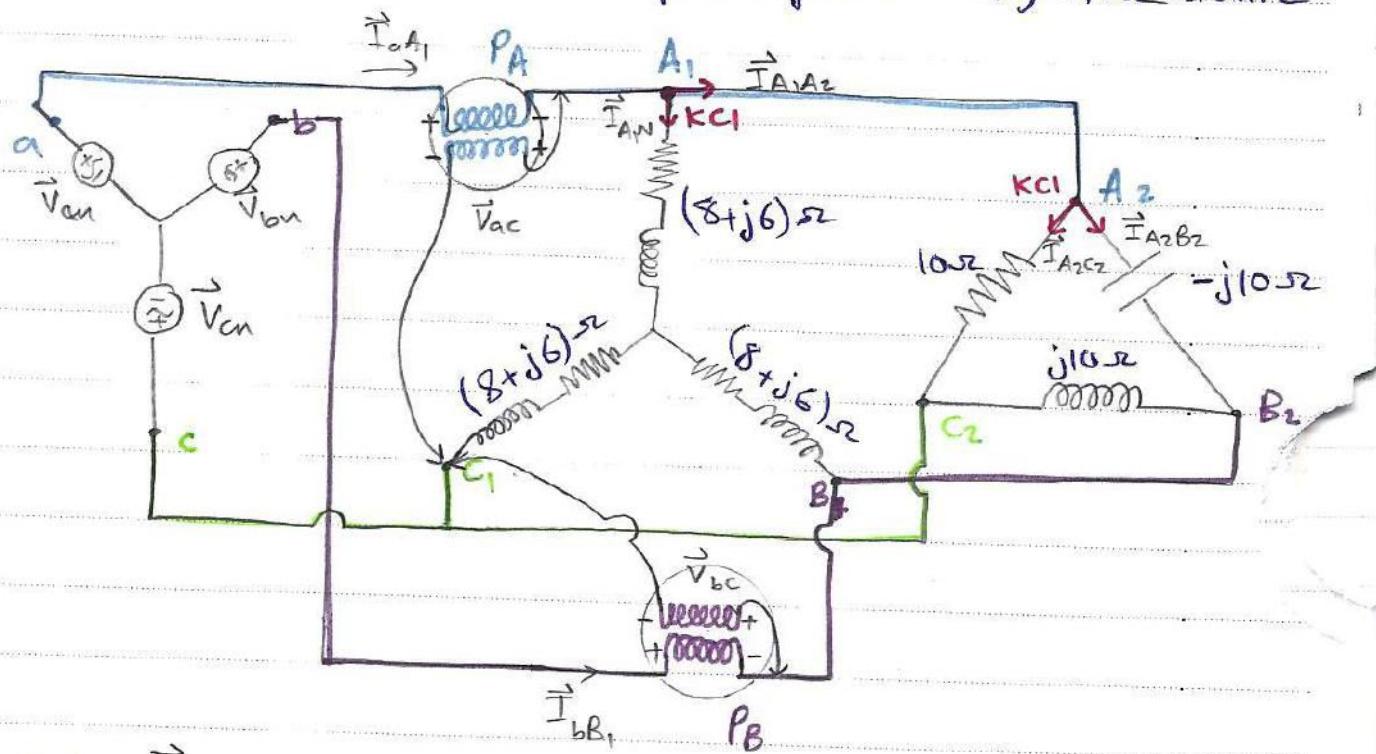example 2:- $\vec{V}_{ca} = 400 \angle -270^\circ$ V_{rms}, determine :-

- the reading of the two wattmeters P_A & P_B
- if Both wattmeters are modified to read the reactive power, Q_A , Q_B , determine their readings!
- determine the complex power by the source



$$\text{Sol:- } \vec{V}_{ca} = 400 \angle -270^\circ \text{ V}_{\text{rms}}$$

$$\vec{V}_{ab} = 400 \angle -30^\circ \text{ V}_{\text{rms}}$$

$$\vec{V}_{bc} = 400 \angle -150^\circ \text{ V}_{\text{rms}}$$

$$\text{a) } \vec{I}_{aA_1} = \vec{I}_{A_1N} + \vec{I}_{A_1A_2} \xrightarrow{\text{KCL}} \vec{I}_{A_2B_2} + \vec{I}_{A_2C_2}$$

$$\vec{I}_{A_2B_2} = \frac{\vec{V}_{A_2B_2}}{-j10} = \frac{\vec{V}_{ab}}{-j10} = \frac{400 \angle -30^\circ}{10 \angle -90^\circ} = 40 \angle 60^\circ \text{ Arms.}$$

$$\vec{I}_{B_2C_2} = \frac{\vec{V}_{bc}}{j10} = \frac{400 \angle -150^\circ}{10 \angle 90^\circ} = 40 \angle 240^\circ \text{ Arms.}$$

$$\vec{I}_{cA_2} = \frac{\vec{V}_{ca}}{10} = 40 \angle -270^\circ \text{ Arms.}$$

$$\therefore \vec{I}_{A_1 A_2} = \vec{I}_{A_2 C_2} + \vec{I}_{A_2 B_2} = 40 \angle -270^\circ + 180^\circ + 40 \angle 60^\circ \\ = 20.705 \angle -150^\circ \text{ Arms}$$

$$\vec{I}_{B_1 B_2} = \vec{I}_{B_2 C_2} + \vec{I}_{B_2 A_2} = -40 \text{ Arms}$$

$$\vec{I}_{C_1 C_2} = \vec{I}_{C_2 A_2} + \vec{I}_{C_2 B_2} = 20.705 \angle 15^\circ \text{ Arms}$$

$\hookrightarrow I_{A_1 N}$?

$$\vec{V}_{A_1 N} = \vec{V}_{an} = \frac{\vec{V}_{ab}}{\sqrt{3}} \angle -30^\circ = \frac{400}{\sqrt{3}} \angle -30 - 30^\circ = 230.94 \angle -60^\circ$$

$$\vec{I}_{A_1 N} = \frac{\vec{V}_{AN}}{8+j6} = 23.094 \angle -96.87^\circ \text{ Arms}$$

Since it's a balanced load :-

$$\vec{I}_{B_1 N} = \vec{I}_{A_1 N} \angle -120^\circ = 23.094 \angle -216.87^\circ \text{ Arms}$$

$$\vec{I}_{C_1 N} = \vec{I}_{B_1 N} \angle -120^\circ = 23.094 \angle -336.87^\circ \text{ Arms.}$$

$$\Rightarrow I_{a A_1} = I_{A_1 N} + I_{A_1 A_2} = 33.125 \angle -58.64^\circ \text{ Arms.}$$

$$I_{b B_1} = I_{B_1 N} + I_{B_1 B_2} = 60.094 \angle 165.67^\circ \text{ Arms}$$

$$I_{c C_1} = I_{C_1 N} + I_{C_1 C_2} = 43.69 \angle 19.28^\circ \text{ Arms}$$

$$a) P_A = |\vec{V}_{ac}| |\vec{I}_{a A_1}| \cos(\text{ang } \vec{V}_{ac} - \text{ang } \vec{I}_{a A_1})$$

$$= 11314.75 \text{ watt}$$

$$P_B = |\vec{V}_{bc}| |\vec{I}_{b B_1}| \cos(\text{ang } \vec{V}_{bc} - \text{ang } \vec{I}_{b B_1})$$

$$= 17485.28 \text{ watt}$$


$$b) Q_A = |\vec{V}_{ac}| |\vec{I}_{a A_1}| \sin(\text{ang } \vec{V}_{ac} - \text{ang } \vec{I}_{a A_1}) \\ = -68 \text{ VAR}$$

$$Q_B = |\vec{V}_{bc}| |\vec{I}_{b B_1}| \sin(\text{ang } \vec{V}_{bc} - \text{ang } \vec{I}_{b B_1})$$

$$= 16494.6 \text{ VAR.}$$


$$c) \vec{S}_{\text{Source}} = \boxed{(\vec{P}_A + \vec{P}_B) + j(\vec{Q}_A + \vec{Q}_B)}$$

Magnetically Coupled Circuits:

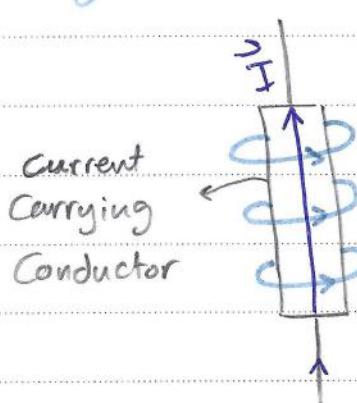


* Orested has discovered that when (I) passes through a current carrying conductor, a magnetic field is created.



* to know the direction of the magnetic field (right hand rule); thumb is in the direction of \vec{I} , other fingers with the magnetic field.

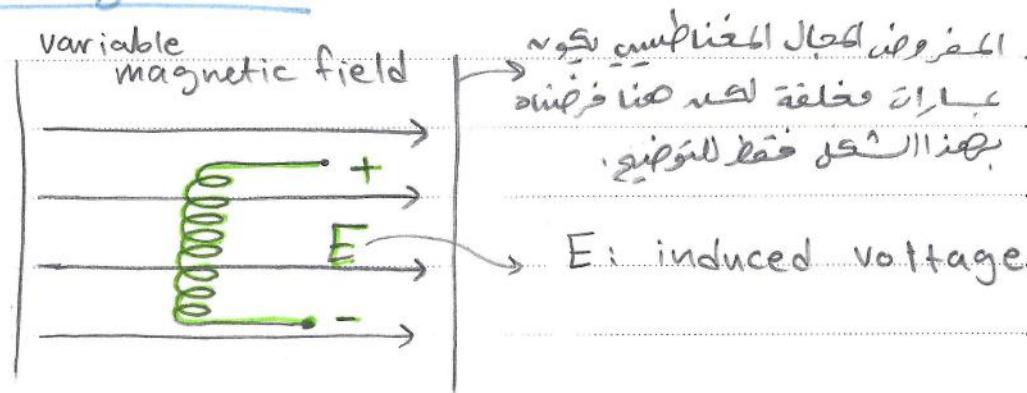- Faraday's law:

→ creating a variable Magnetic field:

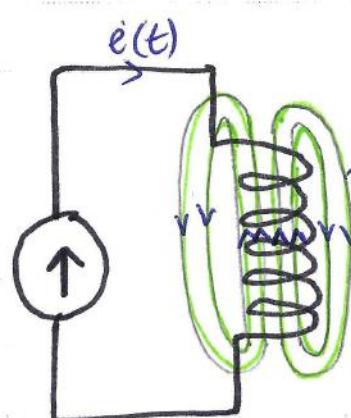

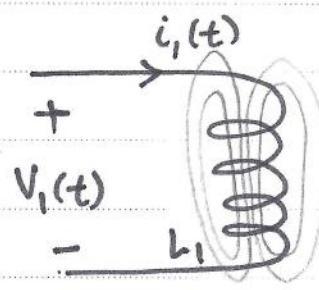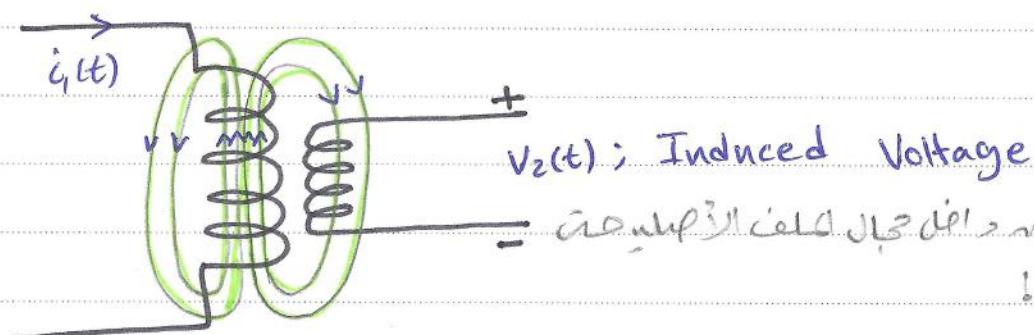
* to determine M.field direction we use the right hand rule; Thumbs with M.field while other finger with the current.



$$V_1(t) = L_1 \frac{di_1(t)}{dt}$$

L_1 is the self inductance [H]

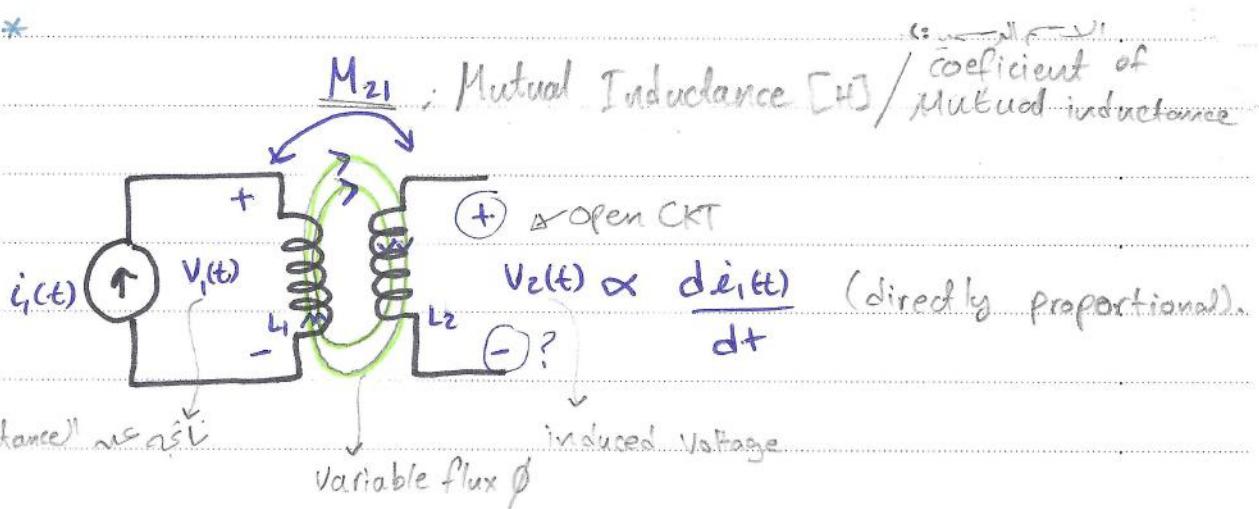
if i_1 was a DC current, $V_1 \& V_2 = 0$
& the Magnetic field will be constant!



$$V_1(t) = L_1 \frac{di_1(t)}{dt}, \quad V_2(t) = M_{21} \frac{di_1(t)}{dt}$$

Self-induced Voltage


Mutual induced Voltage

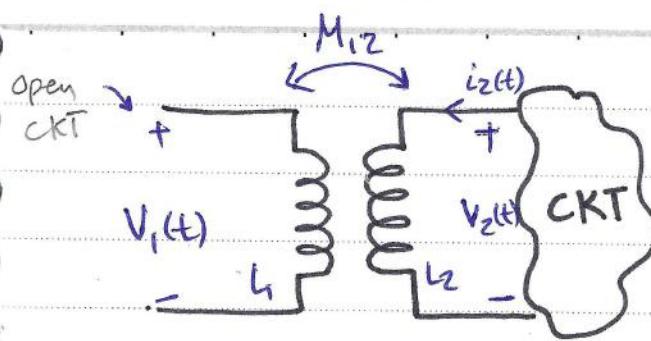

$$V_2(t) = \frac{L_2}{\text{self inductance}} \frac{di_2(t)}{dt}, \quad V_1(t) = \frac{M_{12}}{\text{Mutual inductance}} \frac{di_2(t)}{dt}$$


$\rightarrow M_{21} = M_{12} = M [H]$

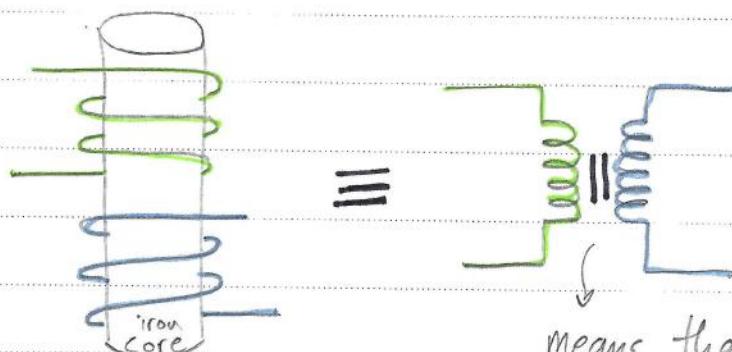* M is measured in a magnetically coupled circuit & it's not a constant for an inductor




means that they're on the same core

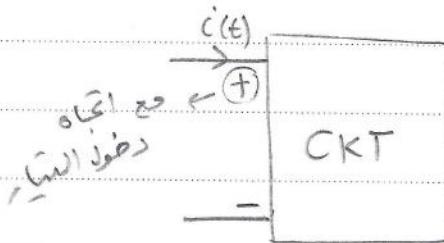* determining the induced Voltage's polarity:- (Dot convention or Mark convention).




to determine Voltage's polarity in a CKT we use "positive sign convention"

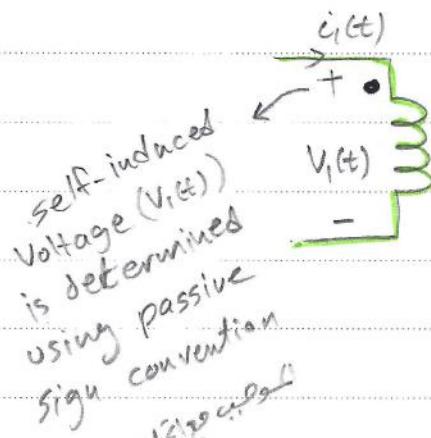but, in a magnetically coupled CKT, we use "Dot/Mark convention".





(Mutual Inductance) to determine V_2 's polarity

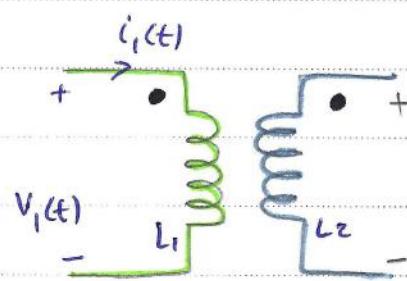we use the Dot convention; we have 4 different combinations of Dot's locations.



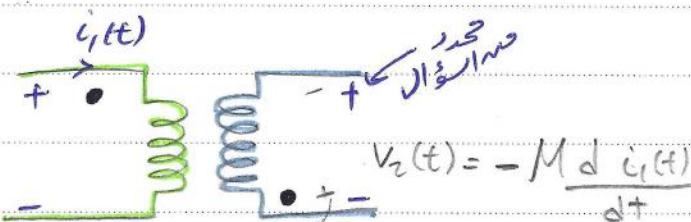
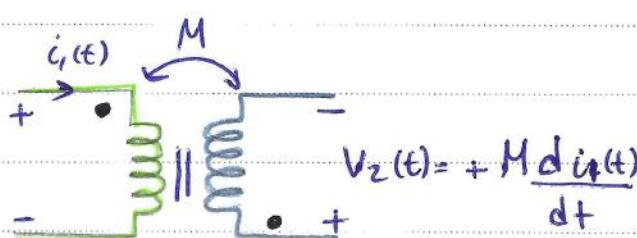
- if the current enters the dotted terminal of one coil, then it produces a true reference at the dotted terminal of the 2nd coil.





Dot convention of 1st coil


will be (-) in 2nd coil

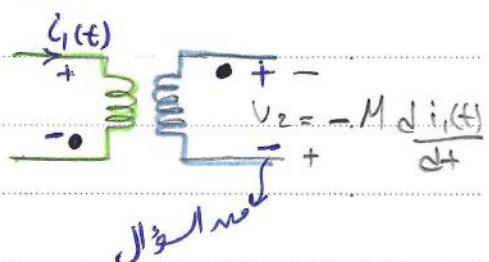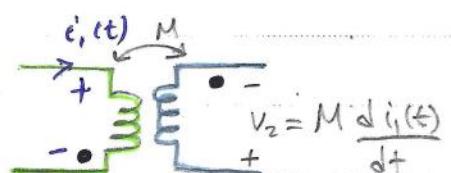- if the current enters the undotted terminal of one coil, the the voltage is truly sensed at the undotted terminal of the 2nd coil.



J31

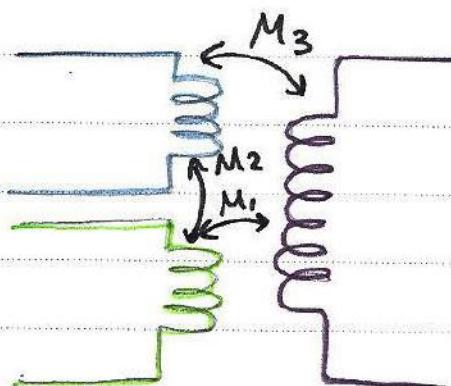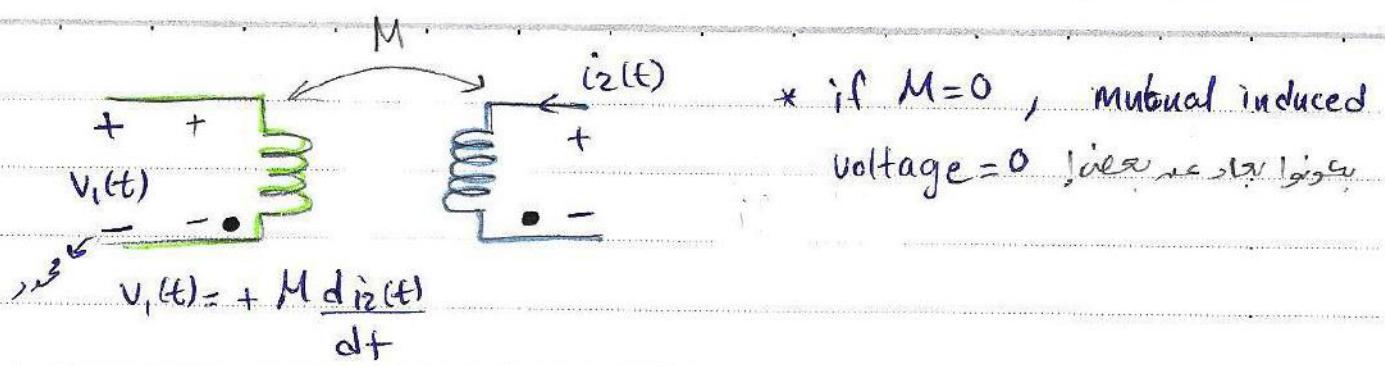

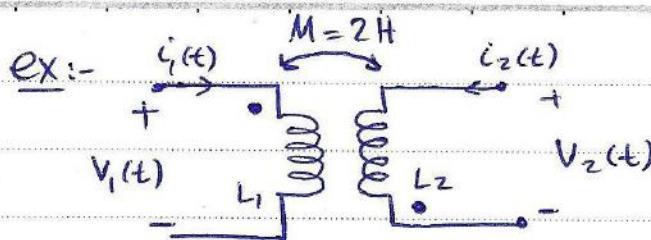


a) find $V_1(t)$ if $i_2 = 5 \sin(4\pi t) \text{ A}$, $i_1 = 0$

$$V_1(t) = -M \frac{di_2(t)}{dt} = -2 (5 \times 4\pi \cos(4\pi t)) = -40\pi \cos(4\pi t) \text{ V}$$

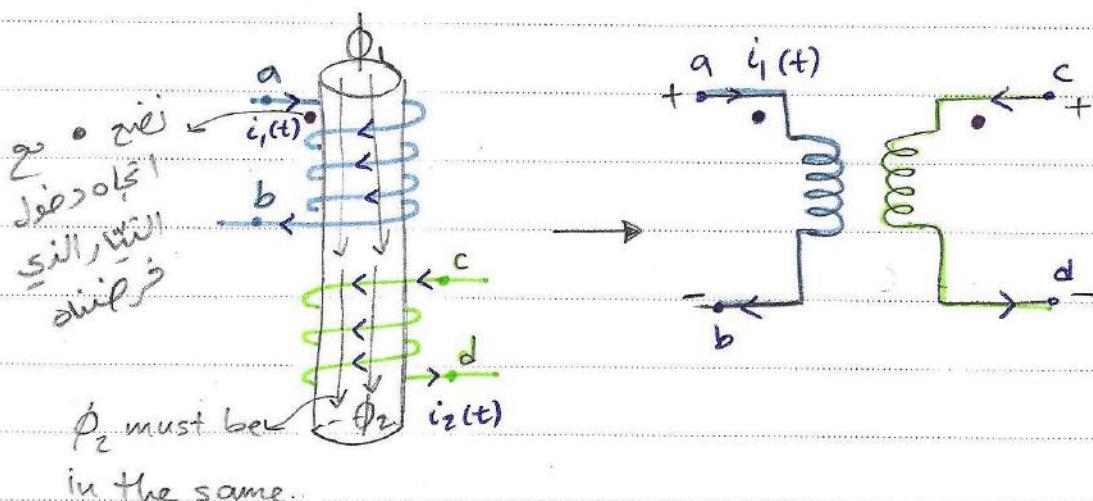
b) find $V_2(t)$ when $i_1(t) = -8e^{-t} \text{ A}$, $i_2 = 0$


$$V_2(t) = -M \frac{di_1(t)}{dt} = -2 (-8(-1)e^{-t}) = -16e^{-t} \text{ A}$$

* Physical Basics of the Dot convention:-




direction of ϕ_1

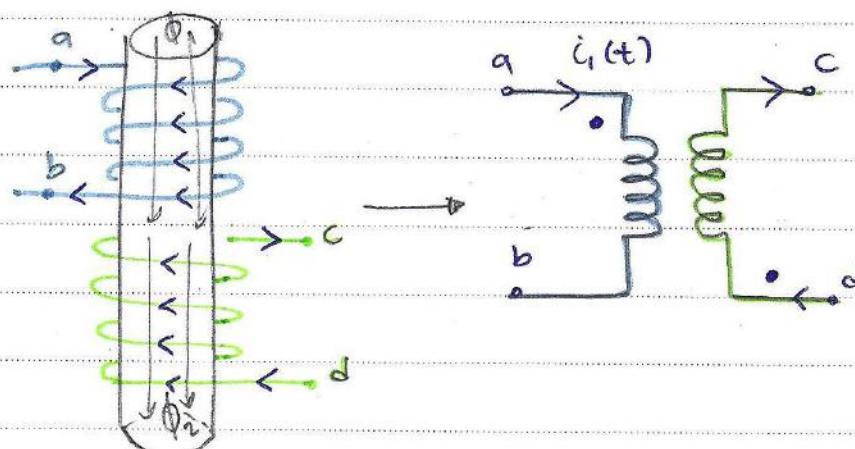

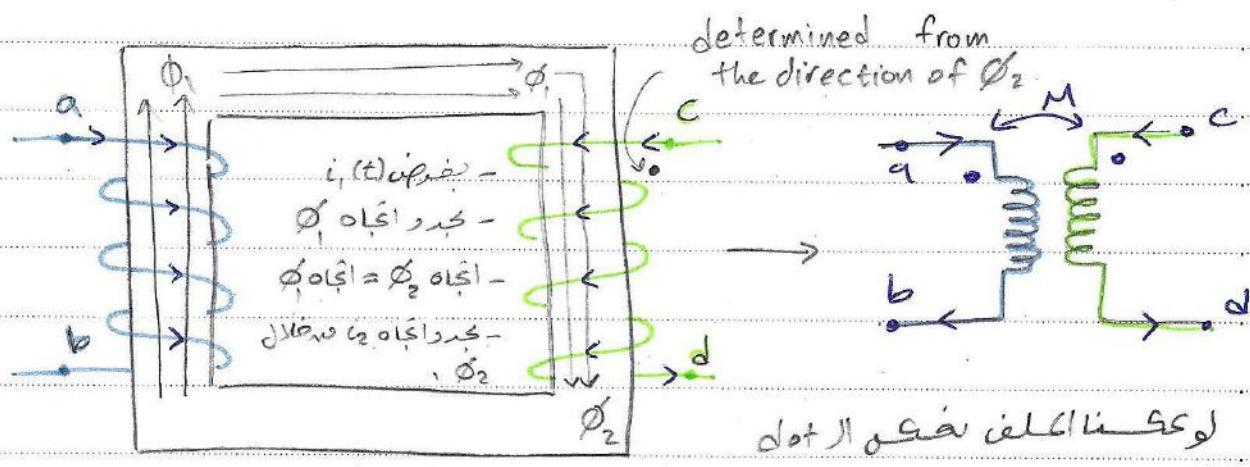

* Mutual & Self induced Voltage:-

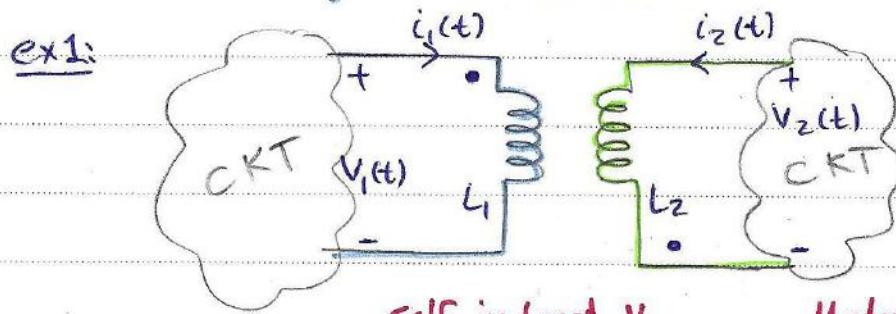


$$V_1(t) = \left(+ L_1 \frac{di_1(t)}{dt} \right) + \left(- M \frac{di_2(t)}{dt} \right)$$

determined using
passive sign convention

determined using
dot convention.

$$V_2(t) = + L_2 \frac{di_2(t)}{dt} + - M \frac{di_1(t)}{dt}$$


example In phasor domain:

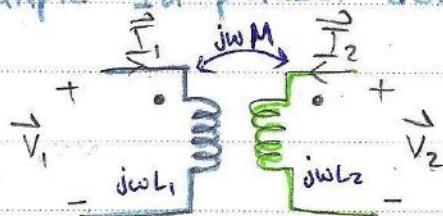

$$\vec{V}_1 = j\omega L_1 \vec{I}_1 + j\omega M \vec{I}_2$$

$$\vec{V}_2 = j\omega L_2 \vec{I}_2 + j\omega M \vec{I}_1$$


ex 2:-

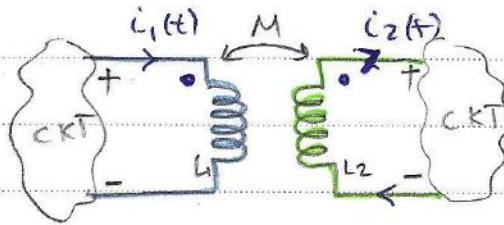

$$V_1(t) = +L_1 \frac{di_1(t)}{dt} - M \frac{di_2(t)}{dt}$$

$$V_2(t) = -L_2 \frac{di_2(t)}{dt} + M \frac{di_1(t)}{dt}$$

ex 3:-

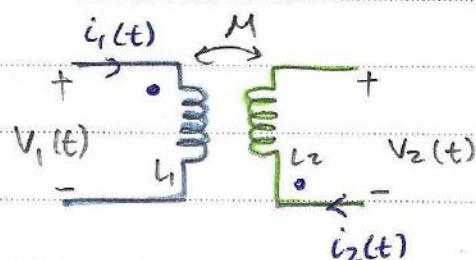


time domain $\rightarrow V_1(t) = -L_1 \frac{di_1(t)}{dt} - M \frac{di_2(t)}{dt}$

$$\hookrightarrow V_2(t) = -L_2 \frac{di_2(t)}{dt} - M \frac{di_1(t)}{dt}$$


Phasor domain $\rightarrow \vec{V}_1 = -j\omega L_1 \vec{I}_1 - j\omega M \vec{I}_2$

sinusoidal Sources $\hookrightarrow \vec{V}_2 = -j\omega L_2 \vec{I}_2 - j\omega M \vec{I}_1$

ex4:-

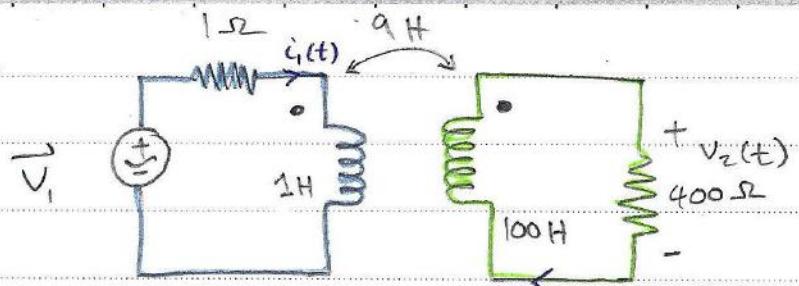
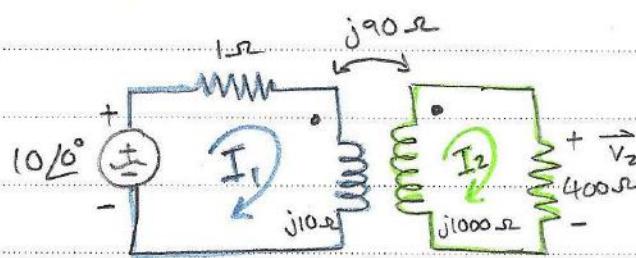
$$V_1(t) = 10 \cos(10t) \text{ V} \Rightarrow \vec{V}_1 = 10 / 0^\circ, \omega = 10 \text{ rad/sec.}$$



@ loop 1:-

$$-10 / 0^\circ + (1) \vec{I}_1 + j10 \vec{I}_1 - (j90) \vec{I}_2 = 0 \\ (1 + j10) \vec{I}_1 - j90 \vec{I}_2 = 10 / 0^\circ \dots ①$$

Self-induced Mutual-induced

$$@ \text{loop 2: } j1000 \vec{I}_2 - j90 \vec{I}_1 + 400 \vec{I}_2 = 0$$

$$-j90 \vec{I}_1 + (400 + j1000) \vec{I}_2 = 0 \dots ②$$

*Note: • في حساب \vec{I}_2 لـ loop 2، يُستخدم خطيّ self-induced $V(j10\Omega)$ لـ loop 1.

• يُستخدم terminal 2 من \vec{I}_1 في حساب \vec{I}_2 لأن \vec{I}_1 يُنافس \vec{I}_2 في الاتجاه.

الخطوة الأولى: ملحوظة على المعاوبي والمعادن، أن \vec{I}_1 و \vec{I}_2 يُنافسان بعضهما البعض.

الخطوة الثانية: ملحوظة على المعاوبي والمعادن، أن \vec{I}_1 و \vec{I}_2 يُنافسان بعضهما البعض.

الخطوة الثالثة: ملحوظة على المعاوبي والمعادن، أن \vec{I}_1 و \vec{I}_2 يُنافسان بعضهما البعض.


Solving ① & ②

$$\vec{I}_1 = (1.614 - j1.284) \text{ A} \quad \text{not in rms}$$

$$\vec{I}_2 = (0.165 + j0.0495) \text{ A}$$

$$\vec{V}_2 = 400 \vec{I}_2 = (6.6, 0.55 - j19.812) \text{ V}$$

ex5:-

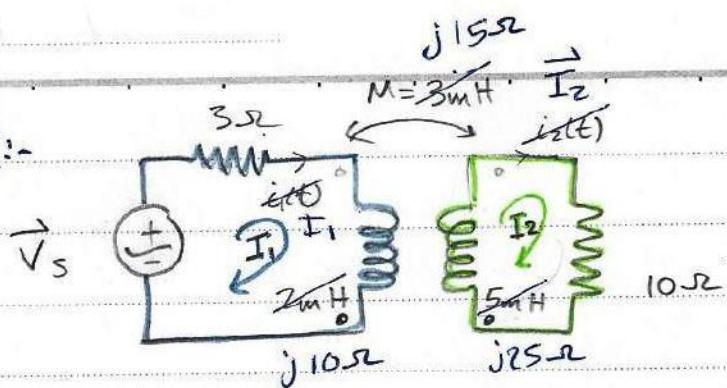ex5:-


$$\omega = 5 \text{ rad/sec.}$$

$$@ \text{loop 1: } -\vec{V}_s + 3\vec{I}_1 + j10\vec{I}_1 - j15\vec{I}_2 = 0$$

$$(3 + j10)\vec{I}_1 - j15\vec{I}_2 = \vec{V}_s \quad \dots \textcircled{1}$$

$$@ \text{loop 2: } j25\vec{I}_2 - j15\vec{I}_1 + 10\vec{I}_2 = 0$$

$$-j15\vec{I}_1 + (10 + j25)\vec{I}_2 = 0 \quad \dots \textcircled{2}$$

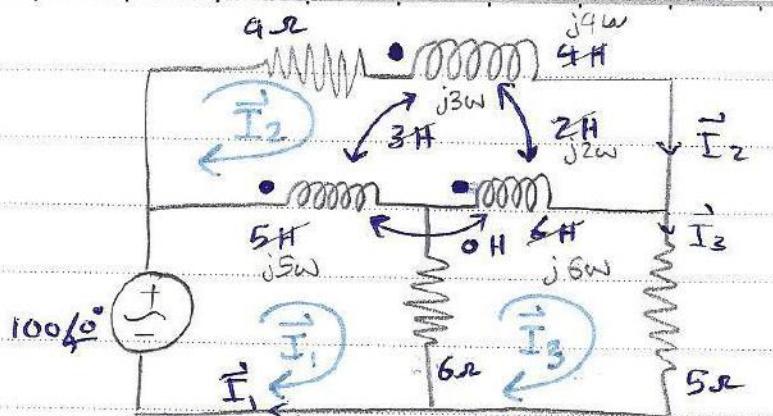Example :-Find $\vec{I}_1, \vec{I}_2, \vec{I}_3$:Sol:- @ loop 1:-

$$-100\angle 0^\circ + j5w(\vec{I}_1 - \vec{I}_2) + (j3w\vec{I}_2 + j0w(\vec{I}_3 - \vec{I}_2)) + 6(\vec{I}_1 - \vec{I}_3) = 0$$

Self-induced Mutual

$$\vec{I}_1(6 + j5w) - \vec{I}_2(j2w) - 6\vec{I}_3 = 100\angle 0^\circ \dots (1)$$

@ loop 2:-

$$4\vec{I}_2 + j4w\vec{I}_2 + j3w(\vec{I}_1 - \vec{I}_2) + j2w(\vec{I}_3 - \vec{I}_2) + j6w(\vec{I}_2 - \vec{I}_3) = 0$$

$$-j2w\vec{I}_2 + j0w(\vec{I}_1 - \vec{I}_2) + j5w(\vec{I}_2 - \vec{I}_1) - j3w\vec{I}_2 = 0$$

$$-j0w(\vec{I}_3 - \vec{I}_2) = 0$$


$$(-j5w)\vec{I}_1 + (4 + j5w)\vec{I}_2 - (j4w)\vec{I}_3 = 0 \dots (2)$$

@ loop 3:-

$$6(\vec{I}_3 - \vec{I}_1) + j6w(\vec{I}_3 - \vec{I}_2) + j2w\vec{I}_2 + j0w(\vec{I}_1 - \vec{I}_2) + 5\vec{I}_3 = 0$$

$$-6\vec{I}_1 - (j4w)\vec{I}_2 + (11 + j6w)\vec{I}_3 = 0 \dots (3)$$

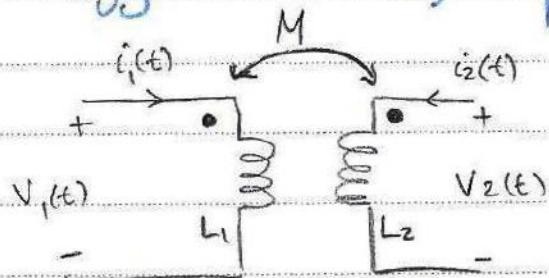
Energy stored & equality of M_{12} & M_{21} :



@ zero initial conditions.

Experiment 1:-

+ let $i_2 = 0$; open circuit.

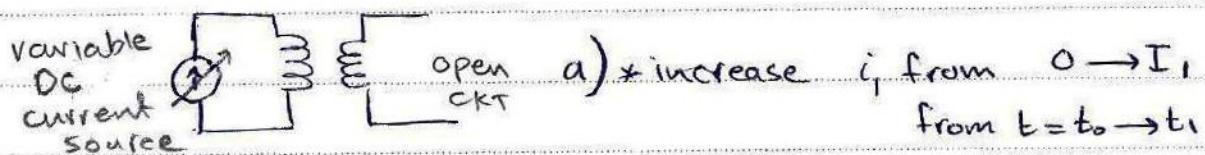

$$\text{instantaneous power} \rightarrow P_1(t) = V(t)i_1(t) = L_1 \frac{di_1(t)}{dt} + i_1(t), \quad P_2(t) = 0$$

$$\text{Energy} = \int \text{power} \cdot dt$$


$$E_{1,1} = \int_{t_0}^{t_1} L_1 \frac{di_1(t)}{dt} i_1(t) dt$$

$$= L_1 \int_0^{I_1} i_1 di_1 = \frac{1}{2} L_1 I_1^2$$

$$E_{2,1} = 0$$

b) now, hold $i_1(t) @ I_1$ &

Increase i_2 from $0 \rightarrow I_2$

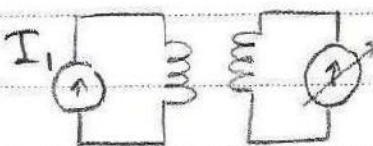

$$E'_{2,1} = \int_{t_1}^{t_2} V_2 i_2 dt = L_2 \int_0^{I_2} i_2 di_2 = \frac{1}{2} L_2 I_2^2 \leftarrow \text{self-induced}$$

$$E'_{1,1} = \int_{t_1}^{t_2} M_{12} \frac{di_2(t)}{dt} i_1 dt$$


$$= M_{12} I_1 \int_0^{I_2} di_2 = M_{12} I_1 I_2$$

$$\Rightarrow E_{T,1} = E_{1,1} + E_{2,1} + E'_{1,1} + E'_{2,1}$$

total E
stored in \rightarrow
the system

$$E_{T,1} = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M_{12} I_1 I_2 \dots \textcircled{1}$$

experiment 2:

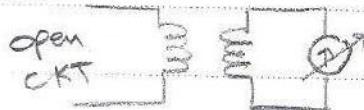

* @ $t=0$, $i_1 = i_2 = 0$ (zero initial conditions)

* increase i_2 from $0 \rightarrow I_2$
from $t=t_0 \rightarrow t_1$

$$E_{2,2} = \int_{t_0}^{t_1} V_2 i_2 dt = \frac{1}{2} L_2 I_2^2$$

$$E_{1,2} = 0$$

* now, hold i_2 @ I_2 & increase i_1 ,

from $0 \rightarrow I_1$,


from $t=t_1 \rightarrow t_2$

$$E'_{1,2} = \int_{t_1}^{t_2} V_1 i_1 dt = \frac{1}{2} L_1 I_1^2$$

$$E'_{2,2} = \int_{t_1}^{t_2} V_2 i_2 dt = M_{21} I_2 \int_{t_1}^{t_2} di_1 dt$$

Mutually-induced
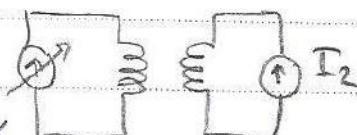
$$= M_{21} I_2 \int_0^{I_1} di_1 = M_{21} I_1 I_2$$




$$E_{T,2} = E_{1,2} + E_{2,2} + E'_{1,2} + E'_{2,2}$$

$$= 0 + \frac{1}{2} I_1^2 L_1 + \frac{1}{2} L_2 I_2^2 + M_{21} I_1 I_2 \dots \textcircled{2}$$


from \textcircled{1} & \textcircled{2}
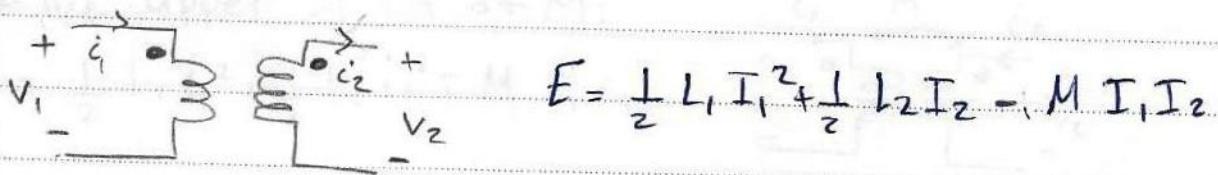
$$E_{T,1} = E_{T,2} \rightarrow \boxed{M_{21} = M_{12}} \Rightarrow$$



In general :-
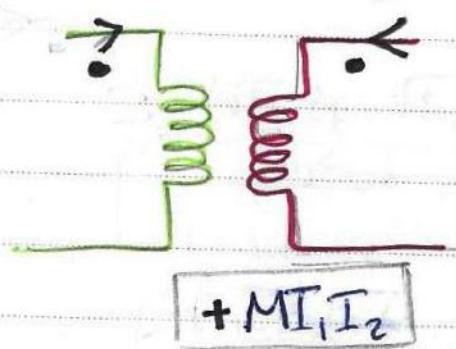
$$E_T(t) = \frac{1}{2}L_1 i_1^2(t) + \frac{1}{2}L_2 i_2^2(t) - M i_1(t) i_2(t)$$



changing the direction of one of the currents or the location of one of the dots changes $M \rightarrow -M$


~~+MI₁I₂ always positive / -MI₁I₂ always negative~~

If one current enters a dotted terminal while the other leaves a dotted \Rightarrow **then the sign of $+M$ is reversed**

$+M I_1 I_2$

* The upper limit of M :
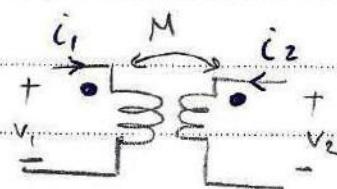
$$E_T = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2$$



- if $i_1 > 0$ & $i_2 > 0 \Rightarrow E_T +ve$

- if $i_1 < 0$ & $i_2 < 0 \Rightarrow +ve$

E_T could be -ve only if

$$E_T = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2$$

$$= \frac{1}{2} (\sqrt{L_1} i_1 - \sqrt{L_2} i_2)^2 + \underbrace{\sqrt{L_1 L_2} i_1 i_2 - M i_1 i_2}_{\text{could be small as 0}}$$

\Rightarrow to enforce it to be +ve

$$\sqrt{L_1 L_2} i_1 i_2 - M i_1 i_2 \geq 0$$

$$\boxed{\sqrt{L_1 L_2} \geq M}$$

or


$$k = \frac{M}{\sqrt{L_1 L_2}} \leq 1 \quad \dots \text{coupling coefficient.}$$

$$0 \leq \frac{M}{\sqrt{L_1 L_2}} \leq 1$$


* if $k=1 \Rightarrow M = \sqrt{L_1 L_2}$,

then, coils are said to be tightly coupled.

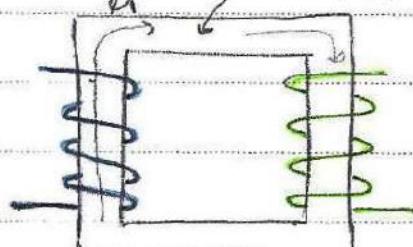loss in Φ_1 , because of the reluctance (R) ; $R\phi = \text{emf}$



$$k < 1$$

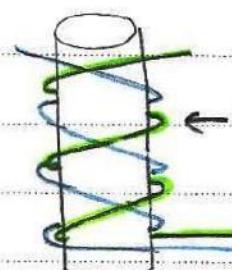


$$k \approx 1$$

$$\text{ex:- } L_1 = 0.4 \text{ H}$$

$$L_2 = 2.5 \text{ H}$$

$$k = 0.6$$

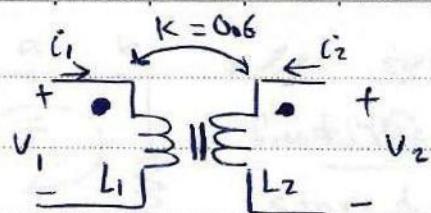

$$i_1 = 20 \cos(500t - 20^\circ) \text{ mA}$$

$$i_1 = 4 i_2$$

, find :

1) i_2 at $t=0$

2) V_1 at $t=0$

3) $W(0)$; total stored energy in the two coils.

Sol:-

1) $i_2(t) = 5 \cos(500t - 20^\circ) \text{ mA} \quad (\text{since } i_1 = 4 i_2)$

$$i_2(0) = 4.689 \text{ mA}$$

2) $V_1(t) = L_1 \frac{di_1(t)}{dt} + M \frac{di_2(t)}{dt} \quad [M = k \sqrt{L_1 L_2} = 0.6 \text{ H}]$

$$\hookrightarrow \frac{di_1(t)}{dt} = -20 \times 500 \sin(500t - 20^\circ)$$

$$\text{at } 0 = -10 \sin(-20^\circ)$$

$$\hookrightarrow \frac{di_2(t)}{dt} = -5 + 500 \sin(500t - 20^\circ) \text{ mA}$$

$$\text{at } 0 = -2.5 \sin(-20^\circ)$$

$$V_1(0) = 0.4 [-10 \sin(-20^\circ)] + 0.6 [-2.5 \sin(-20^\circ)]$$

$$= 1.881 \text{ V}$$


3) $W(0) ?$

$$W(t) = \frac{1}{2} L_1 i_1^2(t) + \frac{1}{2} L_2 i_2^2(t) + M i_1(t) i_2(t)$$

$$W(0) = (151.3) \mu \text{ Joule}$$

$$j59.52 \quad M = j10\sqrt{3} \quad S_H \quad K=0.5$$

ex 2:

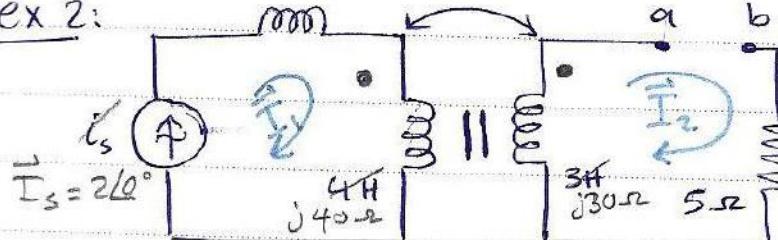

/ /

* let $i_S = 2 \cos(10t) A$,
find the total energy stored at $t=0$, if:

a) a-b is open-circuited.

b) a-b is short-circuited.

$$M = K\sqrt{L_1 L_2} = \frac{1}{2}\sqrt{3 \times 4} = \sqrt{3}$$

Sol: a) $W(t) = W_{S_H} + W_{4H}$ (mutual+self induced).

$$W(t) = \frac{1}{2}(5) i_2^2(t) + \frac{1}{2}(4) i_S^2(t) + 0 \quad ; i_2(0)=0 \text{ (open circuit)}$$

$$W(0) = \frac{1}{2}(5)(2)^2 + \frac{1}{2}(4)(2)^2 = 18 J$$

b) 1st, transform the CKT to phasor domain.

KCL :-

$$j30\vec{I}_2 - j10\sqrt{3}\vec{I}_S + 5\vec{I}_2 = 0$$

$$\Rightarrow (5+j30)\vec{I}_2 = j10\sqrt{3}(2)$$

$$\vec{I}_2 = 1.139 \times 9.462^\circ A$$

back to time domain


$$i_2(t) = 1.139 \cos(10t + 9.462^\circ) A$$

$$i_2(0) = 1.1235 A$$

$$\begin{aligned} W(0) &= \frac{1}{2} 5 i_2^2(0) + \frac{1}{2}(4) (i_S(0))^2 + \frac{1}{2}(3) (i_2(0))^2 - \sqrt{3} \times 2 \times 1.1235 \\ &= \frac{1}{2} \times 5 \times 2^2 + \frac{1}{2} \times 4 \times 2^2 + \frac{1}{2} \times 3 \times 1.1235^2 - \sqrt{3} \times 2 \times 1.1235 \end{aligned}$$


$$= 16.001 J$$

The linear Transformer:-

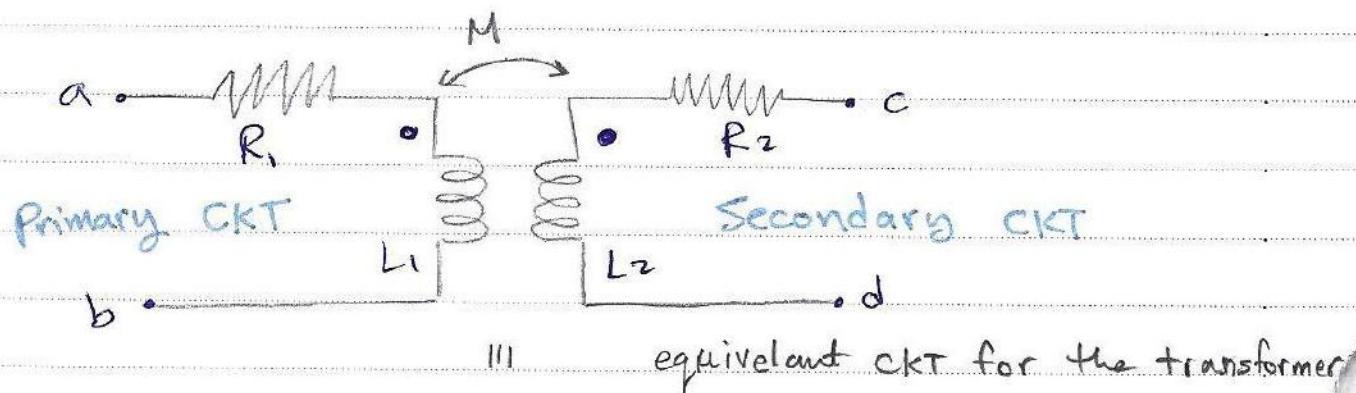

* R_1 & R_2 are the resistances of wires.

* Transformers are used as isolators.

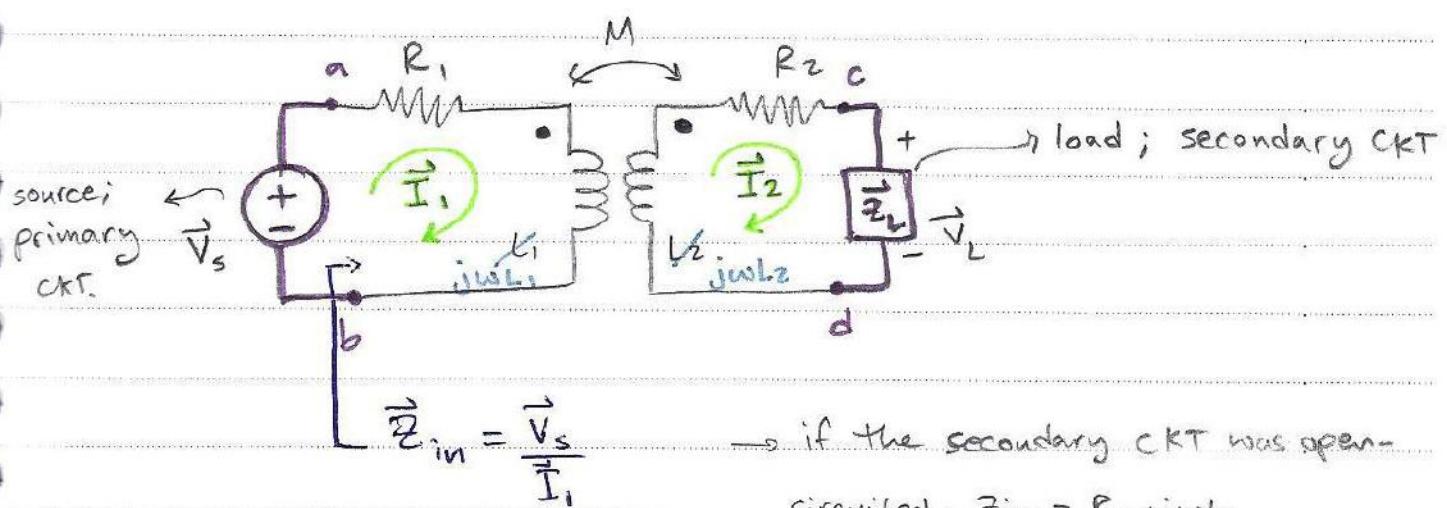

$$@ \text{loop 1: } -\vec{V}_s + (R_1 + j\omega L_1) \vec{I}_1 - j\omega M \vec{I}_2 = 0$$

$$\vec{V}_s = (R_1 + j\omega L_1) \vec{I}_1 - j\omega M \vec{I}_2 \quad \dots (1)$$

$$@ \text{loop 2: } (R_2 + j\omega L_2 + \vec{Z}_L) \vec{I}_2 - j\omega M \vec{I}_1 = 0$$


Def let $\vec{Z}_{11}'' = R_1 + j\omega L_1$

$$\vec{Z}_{22} = R_2 + j\omega L_2 + \vec{Z}_L = R_{22} + jX_{22}$$

$$R_{22} = R_2 + \operatorname{Re}\{\vec{z}_L\}$$

$$X_{22} = W_L + \operatorname{Im}\{\vec{z}_L\}$$

/ /

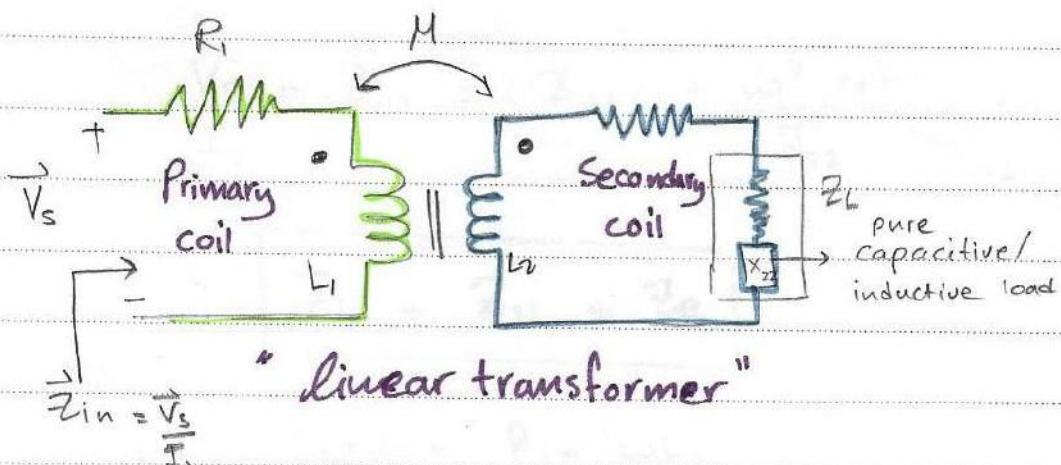

from the previous lec.

$$\vec{V}_s = (R_1 + j\omega L_1) \vec{I}_1 - j\omega M \vec{I}_2 \quad \dots \textcircled{1}$$

$$0 = (R_2 + j\omega L_2 + \vec{Z}_L) \vec{I}_2 - j\omega M \vec{I}_1 \quad \dots \textcircled{2}$$

let: $\vec{Z}_{11} = R_1 + j\omega L_1$

$$\vec{Z}_{22} = R_2 + j\omega L_2 + \vec{Z}_L = R_{22} + jX_{22}$$

$$\Rightarrow R_{22} = R_2 + Re\{\vec{Z}_L\}$$

$$X_{22} = \omega L_2 + Im\{\vec{Z}_L\}$$

Plug in \textcircled{1} & \textcircled{2}

$$\vec{V}_s = \vec{Z}_{11} \vec{I}_1 - j\omega M \vec{I}_2 \quad \dots \textcircled{3}$$

$$0 = \vec{Z}_{22} \vec{I}_2 - j\omega M \vec{I}_1 \quad \dots \textcircled{4}$$

from \textcircled{4} $I_2 = \frac{j\omega M \vec{I}_1}{\vec{Z}_{22}}$

Plug in \textcircled{3}.. $\vec{V}_s = \vec{Z}_{11} \vec{I}_1 + j\omega M \left(\frac{j\omega M \vec{I}_1}{\vec{Z}_{22}} \right)$

$$\frac{\vec{V}_s}{\vec{I}_1} = \frac{1}{\vec{Z}_{11}} \left(\vec{Z}_{11} - \frac{(j\omega M)^2}{\vec{Z}_{22}} \right) \rightarrow$$

$$\frac{V_s}{I_1} = \vec{Z}_{in} = Z_{11} + \frac{\omega^2 M^2}{\vec{Z}_{22}}$$

this equation
doesn't depend
on dots location

$$\boxed{Z_{in} = Z_{11} + Z_R}$$

$$\rightarrow \Rightarrow (-M)^2 = M^2$$

$$\rightarrow Z_{11} = R_1 + j\omega L_1$$

- $Z_R = \frac{\omega^2 M^2}{Z_{22}}$; reflected impedance

- $Z_{22} = R_2 + j\omega L_2 + \vec{Z}_L$


also $Z_{in} = \vec{Z}_{11} + \frac{\omega^2 M^2 R_{22}}{R_{22}^2 + X_{22}^2} - j \frac{\omega^2 M^2 X_{22}}{R_{22}^2 + X_{22}^2}$

ex:- let $\vec{Z}_L = 7 / 32^\circ$, $f = 50 \text{ Hz}$, $M = 800 \text{ mH}$, find:
1) the reflected impedance.

$$Z_R = \frac{\omega^2 M^2}{Z_{22}}$$

$$= \frac{(2\pi f)^2 M^2}{(R_2 + j\omega L_2 + Z_L)}$$

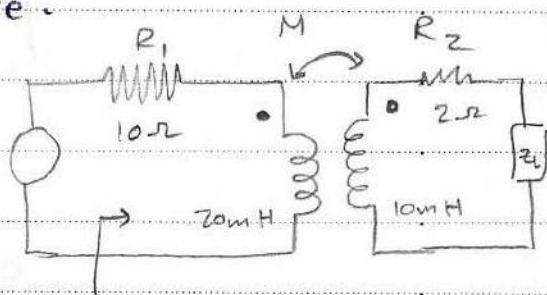
$$= 4.96 - j 3.94 \text{ k}\Omega \quad Z_{in}$$





2) $Z_{in}?$

$$Z_{in} = Z_{11} + Z_R = 10 + j 62.84 \Omega + \vec{Z}_R$$

*The T equivalent Network:

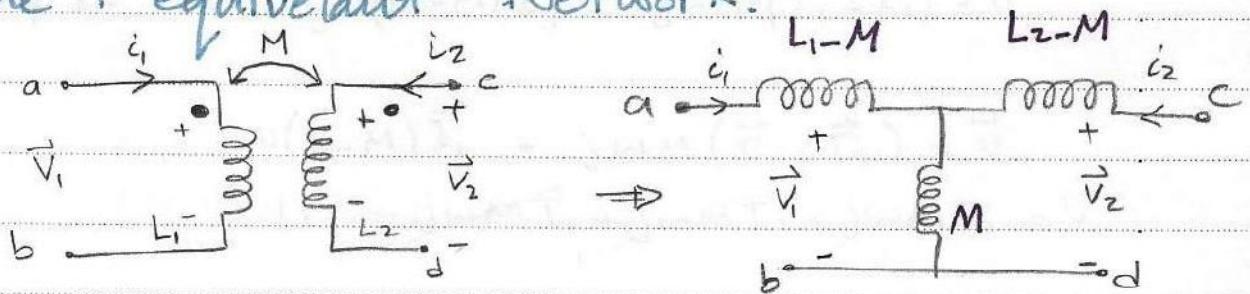

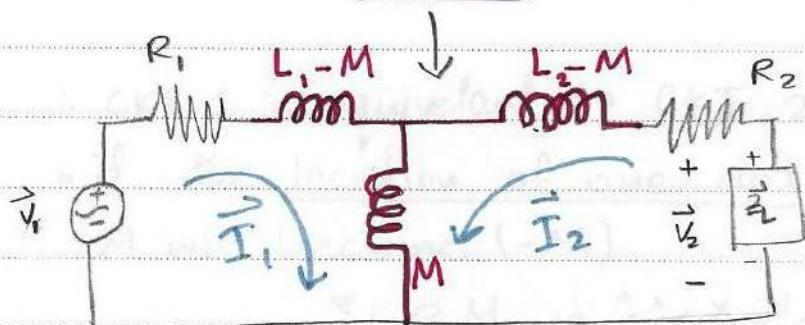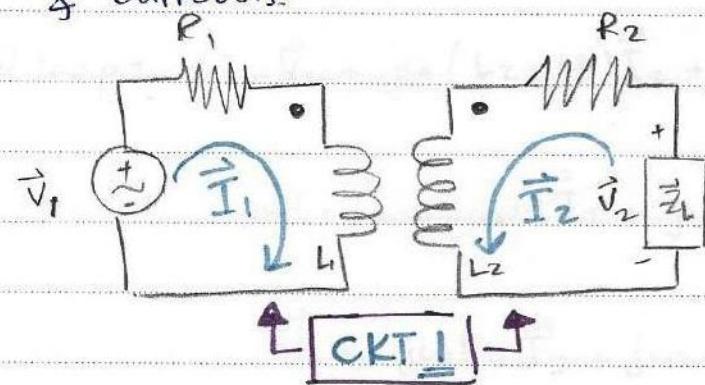→ The input voltages & currents = the output voltages & currents.



↳ CKT 2

for CKT 1: let R_1, R_2 be zero

proving that \vec{v}_1 is equal to \vec{v}_2 CKT 2.

$$\text{loop 1: } -\vec{v}_1 + j\omega L_1 \vec{I}_1 + j\omega M \vec{I}_2 = 0$$

$$j\omega L_1 \vec{I}_1 + j\omega M \vec{I}_2 = \vec{v}_1 \quad \dots \textcircled{1}$$

$$\text{loop 2: } -\vec{v}_2 + j\omega L_2 \vec{I}_2 + j\omega M \vec{I}_1 = 0$$

$$j\omega L_2 \vec{I}_2 + j\omega M \vec{I}_1 = \vec{v}_2 \quad \dots \textcircled{2}$$

for CKT 2 :-

$$\text{at loop 1:- } -\vec{V}_1 + j\omega(L_1 - M)I_1 + j\omega M(\vec{I}_1 + \vec{I}_2) = 0$$

$$j\omega(L_1 - M)\vec{I}_1 + j\omega M(\vec{I}_1 + \vec{I}_2) = \vec{V}_1$$

$$j\omega L_1 I_1 - j\omega M I_1 + j\omega M I_1 + j\omega M I_2 = \vec{V}_1$$

$$\therefore \vec{V}_1 = j\omega L_1 \vec{I}_1 + j\omega M \vec{I}_2 \text{ equal to eq(1)}$$

$$\text{at loop 2:- } -\vec{V}_2 + j\omega(L_2 - M)I_2 + j\omega M(\vec{I}_1 + \vec{I}_2) = 0$$

$$j\omega L_2 \vec{I}_2 - j\omega M \vec{I}_2 + j\omega M \vec{I}_1 + j\omega M \vec{I}_2 = \vec{V}_2$$

$$\therefore \vec{V}_2 = j\omega L_2 \vec{I}_2 + j\omega M \vec{I}_1 \text{ equal to eq(2)*}$$

\therefore CKT 1 is equivalent to CKT 2


- if the location of one dot is changed.

M will become (-M)


نحو اجهاد الـ M في قدرها ايجاد الـ M في قدرها

لـ E_{total} لـ L₁ لـ L₂ لـ M

لـ L₁ لـ L₂ لـ M

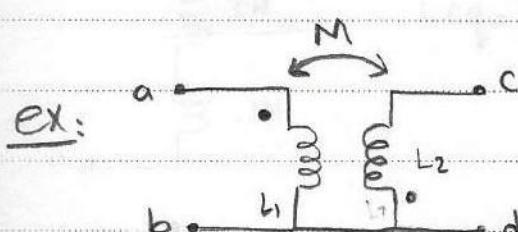

Find the equivalent

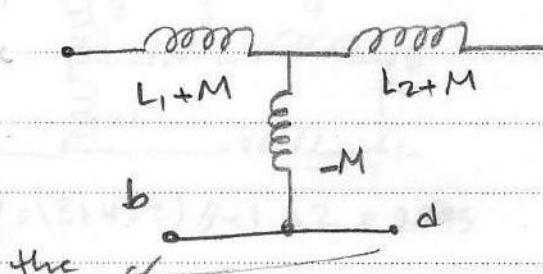




it's impossible to build this
CKT practically, but we can
deal with it mathematically

the


ex:- Find Leg seen between terminals 1 & 2 if:

- ① all terminals (A, B, C) are open.
- ② A & B are connected.
- ③ B & C are connected.
- ④ A & C are connected.

→ find the T equivalent CKT

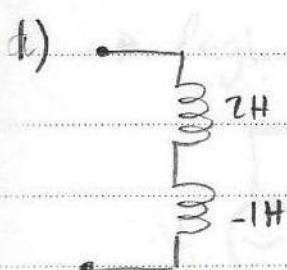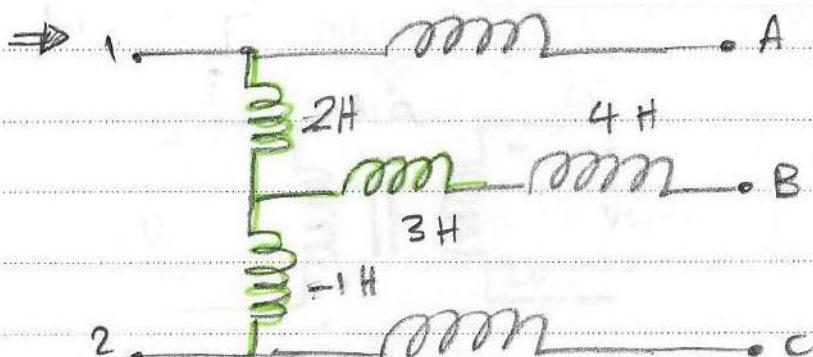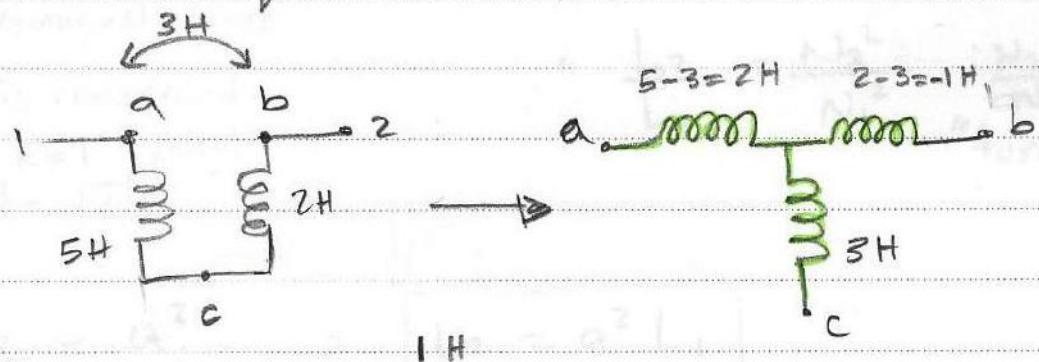


$$\text{Leg} = 2 - 1 = 1\text{H}$$

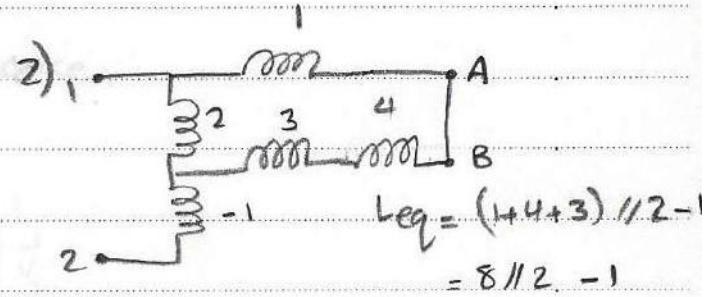


$$\text{Leg} = (1+4+3)/2 - 1 = 8/2 - 1$$

$$= 0.6\text{ H}$$

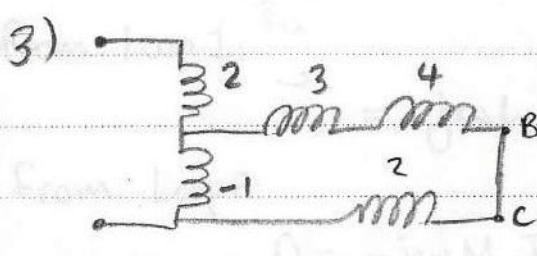

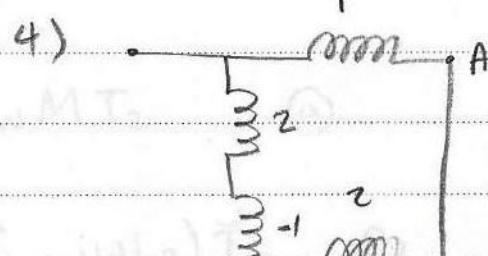
$$\text{Leg} = (3+4+2)/2 - 1 + 2 = 0.875$$



$$\text{Leg} = (2+1)/2 - 1 = 0.375\text{ H}$$

31 / 3 / 2013

The Ideal Transformer:

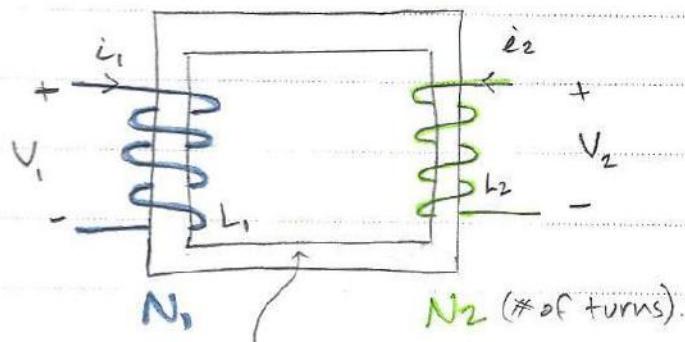

$$* L_1 = \frac{N_1^2}{R}, \quad L_2 = \frac{N_2^2}{R}$$

the same reluctance
(on the same core).

$R\phi = \text{emf...}$


ϕ is conserved

$$k=1 \text{ (unity)}$$


$$\therefore M = \sqrt{L_1 L_2}$$

$$* \frac{L_2}{L_1} = \frac{N_2^2}{N_1^2}; \quad \frac{N_2}{N_1} = a \quad \text{"turns ratio"}$$
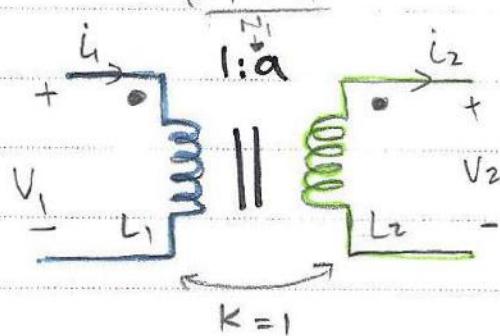
$$* \frac{L_2}{L_1} = a^2 \quad = \boxed{L_2 = a^2 L_1}$$



→ high secondary impedance:

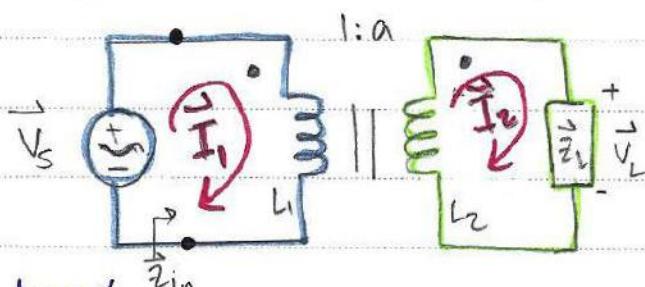

- from Loop 1:

$$\vec{V}_s = j\omega L_1 \vec{I}_1 - j\omega M \vec{I}_2 \quad \dots @$$

- from Loop 2:

$$0 = -j\omega M \vec{I}_1 + (\bar{Z}_L + j\omega L_2) \vec{I}_2 \quad \dots @$$

from (6)

$$\vec{I}_2 = \frac{j\omega M \vec{I}_1}{\vec{Z}_L + j\omega L_2} \quad \dots (1)$$

- plug (1) in (2)

$$\vec{V}_S = j\omega L_1 \vec{I}_1 + \frac{\omega^2 M^2 \vec{I}_1}{\vec{Z}_L + j\omega L_2} \quad \dots (2)$$

$$-\vec{Z}_{in} = \frac{\vec{V}_S}{\vec{I}_1} = j\omega L_1 + \frac{\omega^2 M^2}{\vec{Z}_L + j\omega L_2} \Rightarrow M^2 = L_1 L_2$$

(input impedance)

$$= j\omega L_1 + \frac{\omega^2 L_1 L_2}{\vec{Z}_L + j\omega L_2} \Rightarrow L_2 = \alpha^2 L_1$$

$$= j\omega L_1 + \frac{\omega^2 \alpha^2 L_1^2}{\vec{Z}_L + j\omega^2 L_1} \quad \dots (3)$$

$$= \frac{j\omega L_1 \vec{Z}_L - \omega^2 \alpha^2 L_1^2 + \omega^2 \alpha^2 L_1^2}{\vec{Z}_L + j\omega^2 L_1}$$

$$= \left(\frac{j\omega L_1 \vec{Z}_L}{\vec{Z}_L + j\omega^2 L_1} \right) \times \frac{j\omega L_1}{j\omega L_1}$$

$$\vec{Z}_m = \frac{\vec{Z}_L}{\frac{\vec{Z}_L}{j\omega L_1} + \alpha^2}$$

as $L_1 \rightarrow \infty$

#1:

$$\boxed{\vec{Z}_{in} = \frac{\vec{Z}_L}{\alpha^2}} \quad \dots (4)$$

- from ①

$$\frac{\vec{I}_2}{I_1} = \frac{j\omega M / j\omega L_2}{Z_L + j\omega L_2 / j\omega L_2}$$

$$= \frac{j\omega M / j\omega L_2}{\frac{Z_L}{j\omega L_2} + 1}$$

as $L_2 \rightarrow \infty$

$$\frac{\vec{I}_2}{I_1} = \frac{j\omega M}{j\omega L_2} = \frac{\sqrt{L_1 L_2}}{L_2} = \sqrt{\frac{L_1}{L_2}} = \frac{1}{a}$$

*2

$$\boxed{\frac{I_2}{I_1} = \frac{1}{a}} \rightarrow \boxed{\frac{\vec{I}_2}{I_1} = \frac{N_1}{N_2}} \rightarrow \boxed{\vec{I}_2 N_2 = \vec{I}_1 N_1}$$

also $\frac{i_2(t)}{i_1(t)} = \frac{1}{a}$

- if the dot location of one coil is changed then replace (a) with (-a) $\rightarrow \frac{I_2}{I_1} = -\frac{1}{a}$
- Voltage level adjustment:

$$\vec{V}_2 = I_2 \vec{Z}_L \rightarrow \vec{Z}_L = \frac{\vec{V}_2}{I_2}$$

$$\vec{V}_S = \vec{V}_1$$
$$\vec{Z}_{in} = \frac{\vec{V}_S}{I_1} \Rightarrow \vec{V}_1 = \vec{Z}_{in} \vec{I}_1$$

$$\therefore \vec{V}_1 = \left(\frac{\vec{Z}_L}{a^2} \right) \cdot \vec{I}_1 = \left(\frac{V_2}{I_2} \right) \cdot \vec{I}_1$$

$$\vec{V}_1 = \frac{\vec{V}_2}{a^2} \cdot a$$

→ #3: $\frac{\vec{V}_1}{\vec{V}_2} = \frac{1}{a} \rightarrow \vec{V}_2 N_1 = \vec{V}_1 N_2$

also:- $\frac{V_2(t)}{V_1(t)} = a$

* of turns for the secondary coil.

- if: $a > 1 \equiv N_2 > N_1$

$\rightarrow V_2 > V_1$: Step up transformer

- if $a < 1 \equiv N_1 > N_2$

$\rightarrow V_2 < V_1$: Step down transformer

* $\frac{\vec{V}_2}{\vec{V}_1} = a = \frac{\vec{I}_1}{\vec{I}_2}$

$$\therefore \vec{V}_2 \vec{I}_2 = \vec{V}_1 \vec{I}_1$$

- if $\vec{Z}_L = |\vec{Z}_L| \angle \theta \Rightarrow \vec{V}_2 \text{ leads (assume } \theta \text{ +ve) } \vec{I}_2$

by θ .

& \vec{V}_1 leads \vec{I}_1 by θ .


- since $\vec{Z}_{in} = \frac{\vec{Z}_L}{a^2}$ \therefore the angle to $\vec{Z}_L = \text{ang}(\vec{Z}_{in}) = \theta$

phase \Rightarrow no \vec{I}_1

$- P_2 = P_1$ for an ideal transformer.

$$|\vec{V}_2| |\vec{I}_2| \cos(\theta) = |\vec{V}_1| |\vec{I}_1| \cos \theta \quad \text{from } \vec{V}_2 \vec{I}_2 = \vec{V}_1 \vec{I}_1$$


ex:-

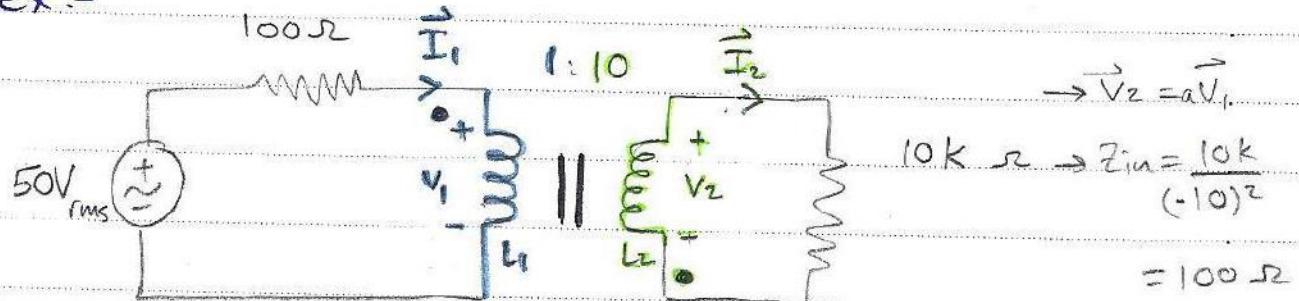

$$P = |\vec{I}_2|^2 (10k)$$

$$\text{or } P = \frac{|\vec{V}_2|^2}{10k}$$

$$Z_{in} = 100\Omega$$

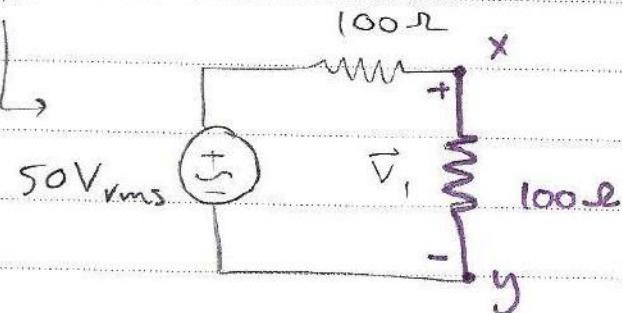

$$\vec{V}_1 = 25V_{rms} \quad (\text{voltage division})$$


$$\vec{V}_2 = a\vec{V}_1 = -10 \times 25 = -250V_{rms} \quad \text{remember:}$$

$$P = \frac{(-250)^2}{10k} = 6.25 \text{ W.att} \rightarrow \text{if } V \text{ isn't in rms} \rightarrow \text{power is multiplied by } (1/2)$$

$$\vec{I}_1 = \frac{50}{200} = \frac{1}{4} A_{rms}$$

$$\vec{I}_2 = \frac{\vec{I}_1}{a} = -\frac{1}{40} A_{rms}$$

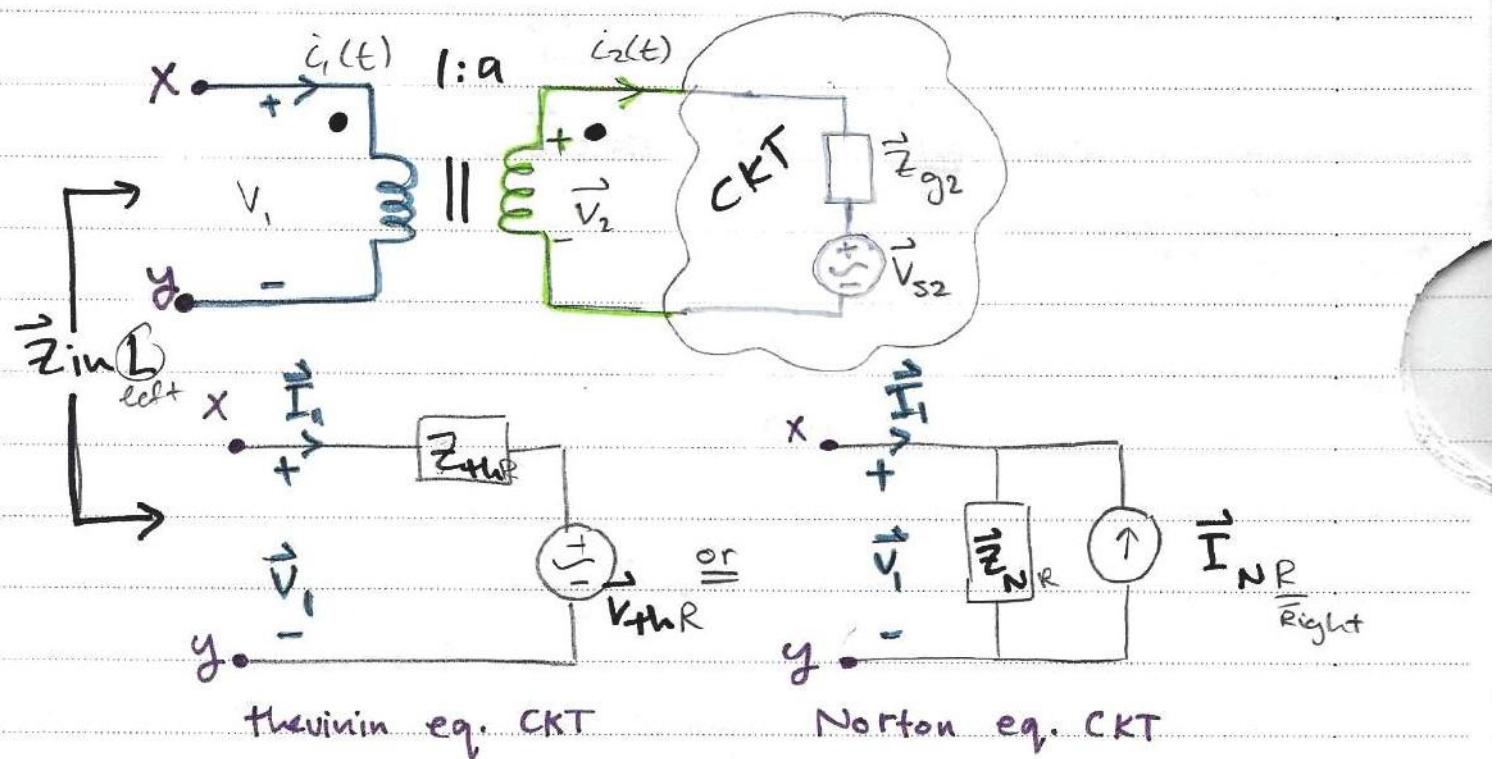- Thévenin's & Norton's equivalent CKTs for the ideal transformer:



$$* Z_{thR} = \bar{Z}_{g2} / a^2$$

$$* \bar{V}_{thR} = \bar{V}_{1,oc} \underset{\text{open CKT}}{\Rightarrow} \bar{I}_1 = 0 \\ \Rightarrow \frac{\bar{I}_1}{\bar{I}_2} = a \quad \therefore a\bar{I}_2 = 0 \rightarrow \bar{I}_2 = 0$$


$$\hookrightarrow \bar{V}_{1,oc} = \frac{\bar{V}_2}{a} = \frac{\bar{V}_{s2}}{a} = \bar{V}_{th}$$

$$* \bar{I}_{NR} = \frac{\bar{V}_{thR}}{Z_{thR}} = + \frac{\bar{V}_{s2}/a}{\bar{Z}_{g2}/a^2} = + \frac{a\bar{V}_{s2}}{\bar{Z}_{g2}}$$

another way:

$$\vec{I}_N = \vec{I}_{1, \text{S.C.}} = ?!$$

short ckt



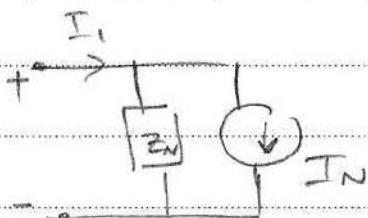


$$\vec{I}_{1, \text{S.C.}} = a \vec{I}_2 \Rightarrow \vec{I}_2 = \frac{\vec{I}_{1, \text{S.C.}}}{a} \Rightarrow V_1 = 0 \\ V_2 = 0$$

$$(\vec{I}_2 \times \vec{Z}_{g2}) + V_{S2} = 0$$

$$\therefore \vec{I}_N = \vec{I}_{\text{S.C.}} = -a \frac{\vec{V}_{S2}}{\vec{Z}_{g2}}$$

(J1, J2, V1, V2)

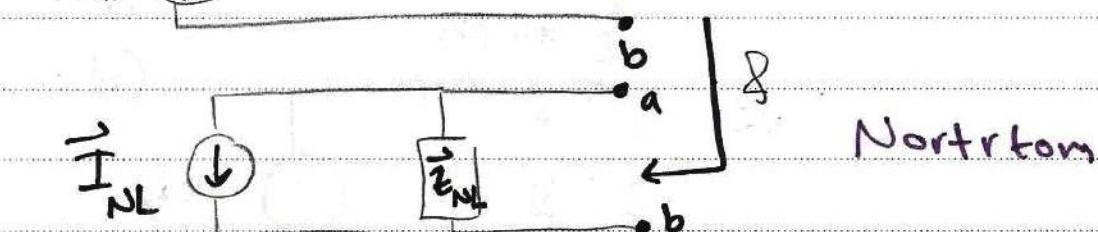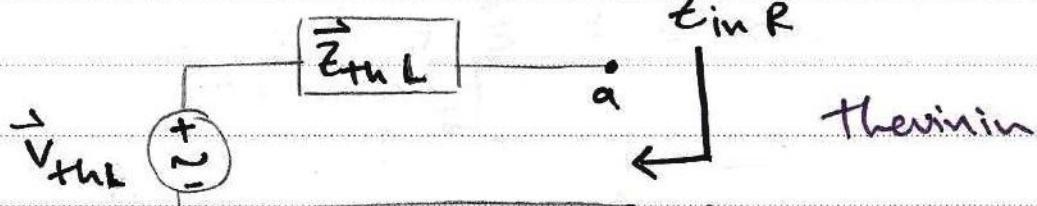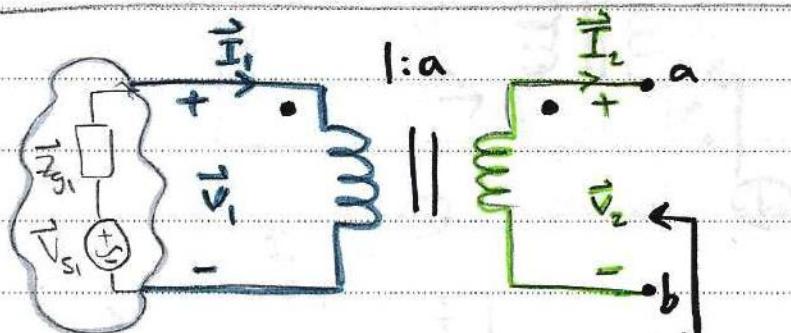

$$+ \quad \vec{Z}_{th} = a^2 \vec{Z}_{g1}$$

$$* \quad \vec{V}_{thL} = \vec{V}_{2, \text{O.C.}} = ? \quad , \quad \vec{I}_2 = 0 = \vec{I}_1$$

$$\vec{V}_1 = \vec{V}_{S1} \Rightarrow \vec{V}_{2, \text{O.C.}} = a \vec{V}_1 = a \vec{V}_{S1}$$


$$\boxed{V_{thL} = a \vec{V}_{S1}}$$

$$\vec{I}_N = -\frac{a \vec{V}_{S1}}{a^2 \vec{Z}_{g1}} = -\frac{\vec{V}_{S1}}{a \vec{Z}_{g1}}$$


* Note:

- if the dot position of one of the coils is changed, then replace (a) with (-a)


ex 2:

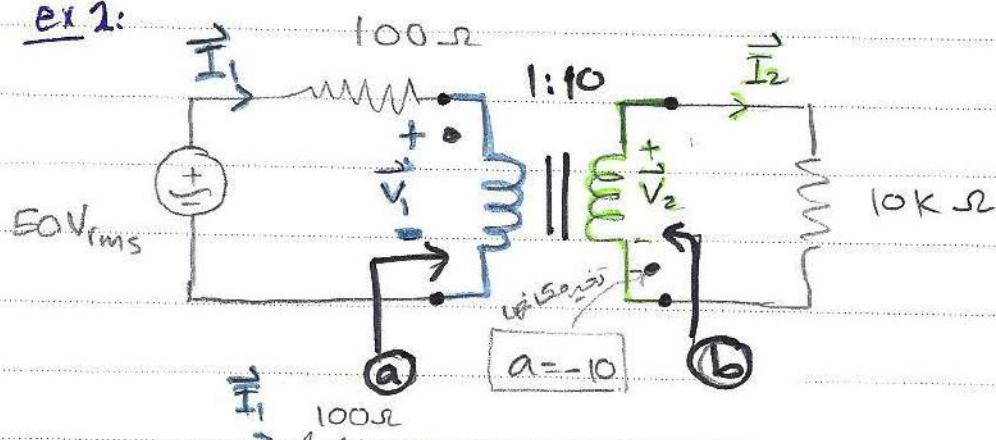


a)

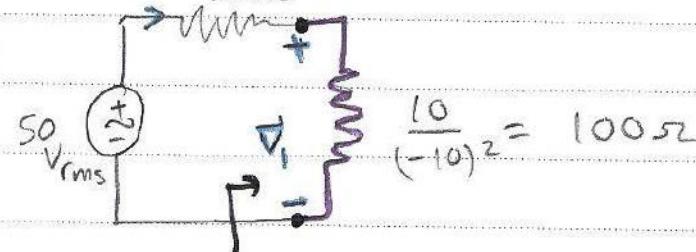


b)

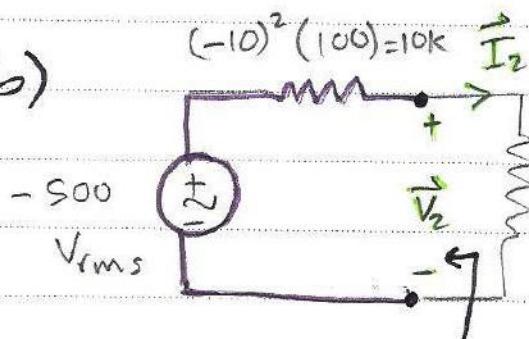

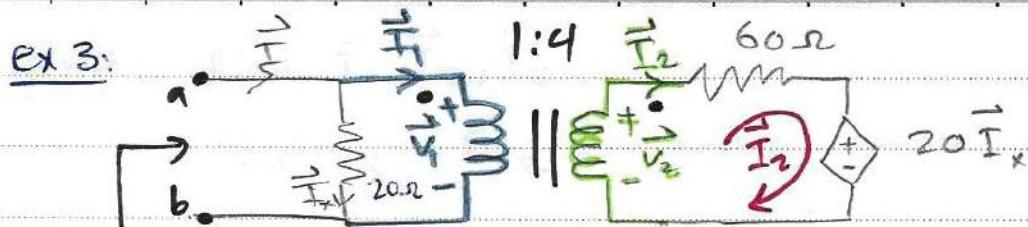

\vec{Z}_{in} - Find thevenin's eq. CKT between terminals a & b?

Sol:-

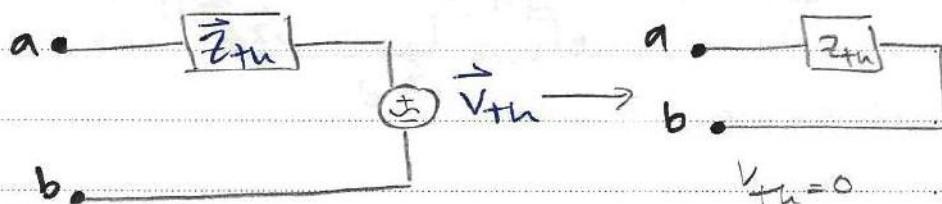

* $\vec{V}_{th} = 0$ (the source is dependant). \downarrow

* $\vec{Z}_{in} = Z_{th} = \frac{V}{I} = \frac{1}{\frac{1}{2}} = 2 \Omega$ ← test voltage (لبيان)

$$\downarrow I_x = \frac{1}{20} A = 0.05 A$$

$$\vec{V}_1 = 1 V$$

$$\vec{V}_2 = a\vec{V}_1 = 4 V \quad (a=4)$$

@ loop 2: $-V_2 + 60\vec{I}_2 + 20\vec{I}_x = 0$

$$\vec{I}_2 = \frac{V_2 - 20I_x}{60} = \frac{1}{20} = 0.05 A$$

$$\frac{\vec{I}_2}{\vec{I}_1} = \frac{1}{4} \rightarrow \vec{I}_1 = I_2 \times 4 = 0.2 A$$


KCL:

$$\vec{I} = \vec{I}_x + \vec{I}_1 = 0.05 + 0.2 = 0.25 A$$


$$\therefore Z_{th} = R_{th} = \frac{1}{0.25} \Omega = 4 \Omega$$

ex4: find $\vec{I}_1, \vec{I}_2, \vec{I}_3$

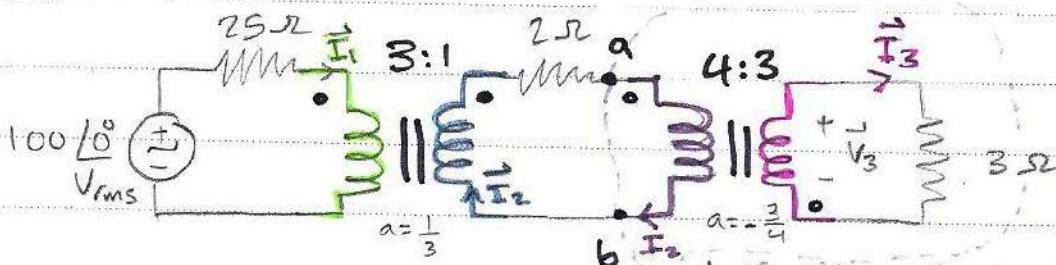$P_{25\Omega}, P_{2\Omega}, P_{3\Omega}$? $P \Rightarrow$ avg power



①

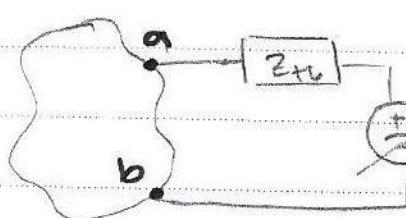


1. We first need a Z_{th} w/ $I = 0$


$I = 0$ (there's no V source)

$$\text{Z}_{th} = \frac{3}{(-\frac{3}{4})^2} = \frac{16}{3} \Omega$$

②

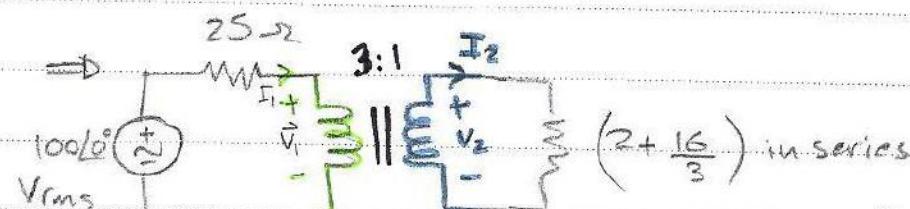
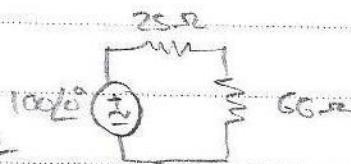
$$\text{Z}_{th} = \frac{\left(2 + \frac{16}{3}\right)}{\left(\frac{1}{3}\right)^2} = 66 \Omega$$



$$\vec{I}_1 = \frac{100 \angle 0^\circ}{25 + 66} = 1.0989 \angle 0^\circ \text{ A}_{\text{rms}}$$

$$\vec{I}_2 = \frac{\vec{I}_1}{\left(\frac{1}{3}\right)} \Rightarrow I_2 = 3\vec{I}_1 = 3.297 \angle 0^\circ \text{ Arms}$$


$$\vec{I}_3 = \frac{\vec{I}_2}{-3/4} = 4.396 \angle 180^\circ$$

$$P_{25\Omega} = \vec{I}_1^2 R_{25} = (1.0989 \angle 0^\circ)^2 \times 25 \text{ Watt}$$

$$P_{2\Omega} = \vec{I}_2^2 R_{2\Omega} = (3.297 \angle 0^\circ)^2 \times 2 \text{ Watt}$$

$$P_{3\Omega} = \vec{I}_3^2 R_{3\Omega} = (4.396 \angle 180^\circ)^2 \times 3 \text{ Watt}$$

ex:

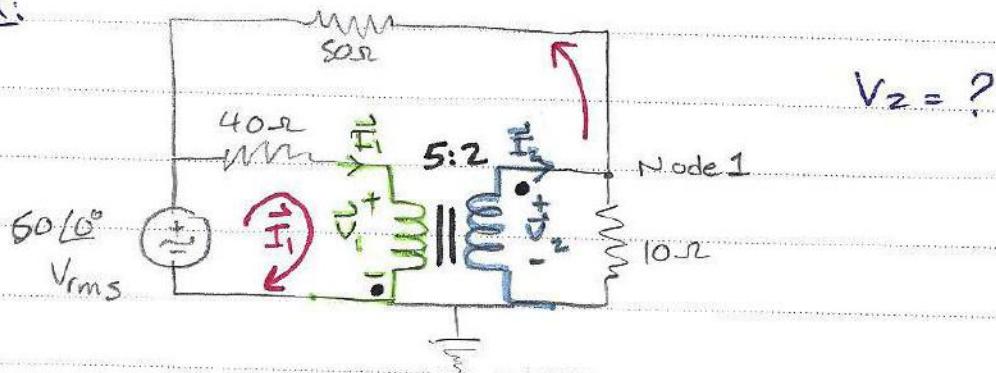

Sol: @ Node 1: $\frac{\vec{V}_2 - 60}{50} + \frac{\vec{V}_2}{10} - \vec{I}_2 = 0$

$$6\vec{V}_2 - 50\vec{I}_2 = 60 \quad \dots \textcircled{1}$$

@ Loop 1: $-60\angle 0^\circ + 40\vec{I}_1 + \vec{V}_1 = 0$

$$\vec{I}_2 = \frac{\vec{I}_1}{-2/5}, \vec{V}_2 = -2 \frac{\vec{V}_1}{5} \quad \dots \textcircled{2}$$

$$\therefore -2.5\vec{V}_2 - 16\vec{I}_2 = 60\angle 0^\circ \quad \dots \textcircled{3}$$

from $\textcircled{1}$ & $\textcircled{2}$ & $\textcircled{3}$


$$\rightarrow \vec{V}_2 = -9.235 V_{\text{rms}}, \vec{I}_2 = -2.307 A_{\text{rms}}$$

$$\rightarrow \vec{V}_1 = 23.089 V_{\text{rms}}, \vec{I}_1 = 0.92 A_{\text{rms}}$$

Summary:-

linear transformer

$$\vec{Z}_{in} = Z_{11} + Z_P$$

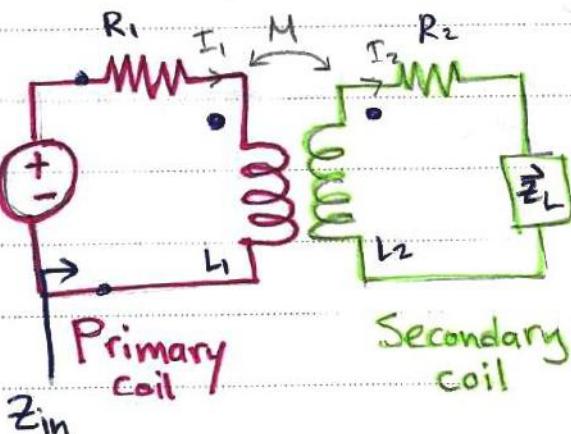



the

Reflected impedance has suffered a sign change in its reactive part, so a capacitive load will lead to an inductive contribution to the input impedance.

$$\vec{Z}_P = \frac{\omega^2 M^2}{\vec{Z}_{22}}$$

the reflected impedance.

* T equivalent Network:-

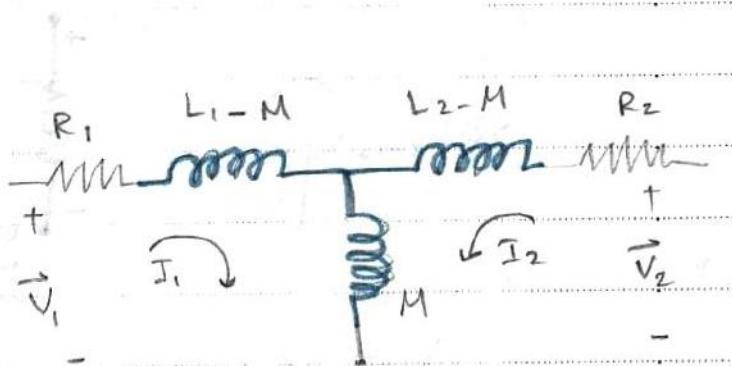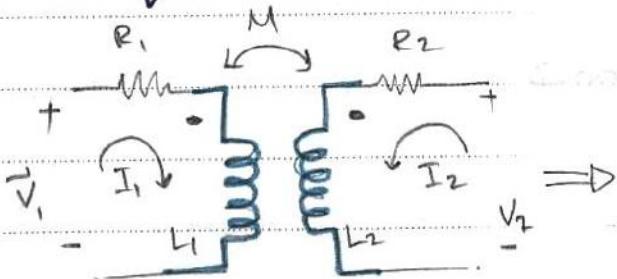


- changing one dot locations changes the sign of M.
- changing the direction of current doesn't affect the values (M , $L_2 - M$, $L_1 + M$)

Summary:-

/ /

The Ideal Transformers

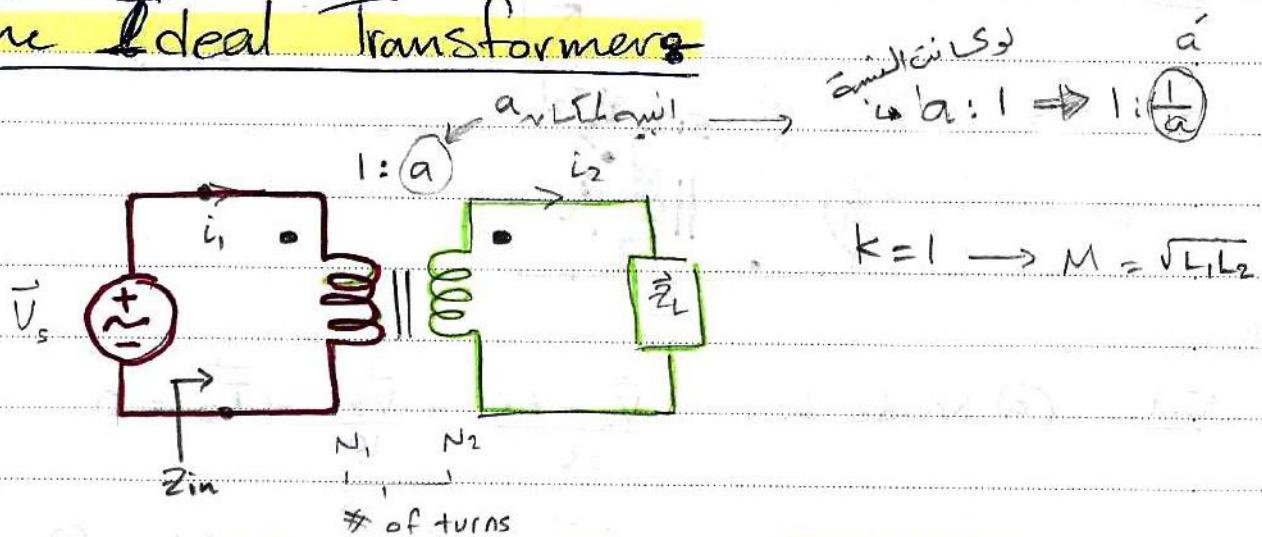

$a = \frac{N_2}{N_1}$	$\frac{L_2}{L_1} = a^2$	$\vec{V}_1 \vec{I}_1 = \vec{V}_2 \vec{I}_2$
-----------------------	-------------------------	---------------------------------------------

turns ratio a

$Z_{in} = \frac{\vec{Z}_L}{a^2}$	$\frac{I_2}{I_1} = \frac{1}{a}$	$\frac{V_2}{V_1} = a$
----------------------------------	---------------------------------	-----------------------

$\hookrightarrow I_1 N_1 = I_2 N_2 \quad \hookrightarrow V_1 N_2 = V_2 N_1$

from this relation, if the load impedance (\vec{Z}_L) is capacitive, the input impedance (Z_{in}) will also be capacitive!

* Linear \Rightarrow $\vec{V}_1 \vec{I}_1 = \vec{V}_2 \vec{I}_2$
transformer

$I_1 N_1 = I_2 N_2$	$V_1 N_2 = V_2 N_1$
---------------------	---------------------

a) change the location of one dot

$$I_1 N_1 = -I_2 N_2$$

$$V_1 N_2 = -V_2 N_1$$

b) change the direction of one current

$$I_1 N_1 = -I_2 N_2$$

$$V_1 N_2 = V_2 N_1$$

c) change the polarity of one voltage

$$I_1 N_1 = I_2 N_2$$

$$V_1 N_2 = -V_2 N_1$$

Summary : (cont.)

$a > 1$, $\therefore N_2 > N_1$

$\therefore V_2 > V_1 \longrightarrow$

Step-up transformer

$a < 1$, $N_1 > N_2$

$V_1 > V_2 \rightarrow$

Step-down transformer

$$* \text{ang}(\vec{Z}_L) = \text{ang}(\vec{Z}_{in}) = \theta$$

$$* P_2 = P_1 = |\vec{V}_2| |\vec{I}_2| \cos(\theta) = |\vec{V}_1| |\vec{I}_1| \cos(\theta)$$

$$* \text{apparent } P_1 = \text{apparent } P_2$$

* Thevenin & Norton's equivalent CKTs :-

$V_{th} = V_{oc}$! \rightarrow when I have only dependant sources


open CKT then $V_{th} = I_N = 0$ & R_{th} is calculated by applying a known I/V source

$$\text{the } R_{th} = \frac{V_{know}}{I_{calculated}} \text{ or } \frac{V_{calculated}}{I_{know}}$$

$$I_N = I_{SC}$$

short CKT $\rightarrow I_N = \frac{V_{th}}{R_{th}}$


$$R_{th} \rightarrow R_{th} = R_N$$

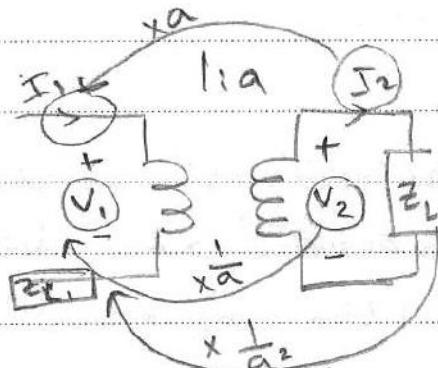

CH #14: Complex frequency (This section is taken from 5th edition (without Laplace).)

* Exponentially damped Sinusoidal Signal:
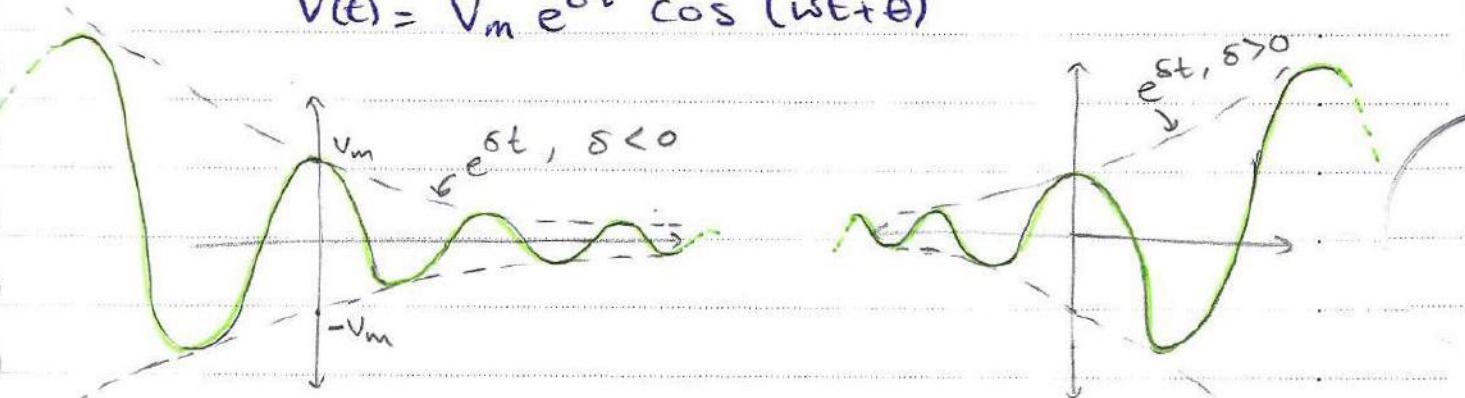
$$V(t) = V_m e^{\delta t} \cos(\omega t + \theta)$$



$$S = \delta + j\omega ; \text{ complex frequency.}$$

$\hookrightarrow \delta$: Nep er frequency (neper/sec = [Np/sec])

$\hookrightarrow \omega$: Angular \sim (rad/sec) ... real freq.

[S] = complex radian per sec.

\sim nep er \sim \sim .

$$\rightarrow V(t) = V_m e^{\delta t} \cos(\omega t + \theta) \dots \text{time domain}$$

$$\rightarrow \vec{V}(s) = V_m \times \theta , \vec{s} = \delta + j\omega \dots \text{freq. domain}$$

$$\vec{V}(t) \xleftrightarrow{\mathcal{L}} \vec{V}(\vec{s})$$

t. domain laplace transform freq. domain

- Some special cases for $(\omega \& \delta)$:

1. let $\omega = 0, \delta = 0$

$$\therefore S = 0$$

$$\rightarrow V(t) = V_m \cos(\theta) = V_0$$

constant DC Analysis

2. let $\delta = 0$

$$S = j\omega$$

$$\rightarrow V(t) = V_m \cos(\omega t + \theta)$$

$$\vec{V} = V_m \angle \theta$$

AC Analysis

(sinusoidal signal)

3. let $\omega = 0$

$$S = \delta$$

$$\rightarrow V(t) = V_m e^{\delta t}$$

transient Analysis

4. when $\delta \neq 0 \& \omega \neq 0 \rightarrow$ it's an exponentially damping sinusoidal!

- How to find Complex frequency (\vec{S})?

$$f(t) = k e^{\vec{S}t} \quad \Rightarrow \quad f(t) = k_1 e^{S_1 t} + k_2 e^{S_2 t}$$

$k \& S$ are complex $*_{ss}$.

- DC ($\omega = \delta = 0$)

$$V(t) = V_0 \Rightarrow V(t) = V_0 e^{0t}$$

$$\therefore S = 0$$

- Exponential ($\omega = 0$)

$$V(t) = V_0 e^{\delta t} \Rightarrow S = \delta$$

- Sinusoidal ($\delta = 0$)

$$V(t) = V_m \cos(\omega t + \theta)$$

from Euler's identity:

$$\cos(\alpha) = \frac{1}{2} e^{j\alpha} + \frac{1}{2} e^{-j\alpha}$$

$$\therefore V(t) = \frac{1}{2} V_m e^{j(\omega t + \theta)} + \frac{1}{2} V_m e^{-j(\omega t + \theta)}$$

$$= \underbrace{\frac{1}{2} V_m e^{j\theta}}_{K_1} e^{\underbrace{j\omega t}_{S_1}} + \underbrace{\frac{1}{2} V_m e^{-j\theta}}_{K_2} e^{\underbrace{-j\omega t}_{S_2}}$$

$$\overline{S}_1 = j\omega$$

$$\overline{S}_2 = -j\omega = \overline{S}_1^*$$

$$k_1 = k_2^*$$

$$\therefore V(t) = k_1 e^{\overline{S}_1 t} + k_2 e^{\overline{S}_2 t}$$

where

$$\overline{S}_1 = \overline{S}_2^*$$

$$k_1 = k_2^*$$

$$V(t) = k e^{\overline{S} t} + k^* e^{\overline{S}^* t}$$

$; \quad S = j\omega$
 $k = \frac{1}{2} V_m e^{j\theta}$

• Exponentially damped sinusoids: $(\omega \neq 0, \delta \neq 0)$

$$V(t) = V_m e^{\delta t} \cos(\omega t + \theta)$$

$$= \frac{1}{2} V_m e^{\delta t} \left[e^{j(\omega t + \theta)} + e^{-j(\omega t + \theta)} \right]_{(S-j\omega)t}$$

$$= \underbrace{\frac{1}{2} V_m e^{j\theta}}_{k_F} e^{\underbrace{(\delta + j\omega)t}_{S_1}} + \underbrace{\frac{1}{2} V_m e^{-j\theta}}_{k_2} e^{\underbrace{-(\delta + j\omega)t}_{S_2}}$$

$$= k_1 e^{\overline{S}_1 t} + k_2 e^{\overline{S}_2 t}$$

$$V(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

$$; \vec{s}_1 = s + j\omega = \vec{s}_2^*$$

$$\vec{k}_1 = \frac{1}{2} V_m e^{j\theta} = \vec{k}_2^*$$

ex: find the complex frequency (s) for:-

$$\textcircled{1} \quad i(t) = 160$$

$$s = 0 \quad (\text{DC})$$

$$\textcircled{2} \quad V(t) = 5 e^{-2t}$$

$$s = -2 \quad (\text{exponential})$$

$$\textcircled{3} \quad i(t) = 2 \sin(500t)$$

$$s_1 = j500, \quad s_2 = -j500$$

$$s = j500$$

$$\textcircled{4} \quad V(t) = 4 e^{-3t} \sin(6t + 10^\circ)$$

$$s_1 = -3 + j6$$

$$s_2 = -3 - j6 \quad \quad \quad s = -3 + j6$$

ex2: if $s_1 = j10, k_1 = 6 - j8, V(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$
find $V(t) = ?$

$$k_2 = 6 + j8, \quad s_2 = -j10, \quad s = 0$$

$$V(t) = \frac{1}{2} V_m e^{j\theta} e^{j\omega t} + \frac{1}{2} e^{-j\theta} e^{-j\omega t}$$

$$V(t) = V_m \cos(\omega t + \theta), \quad \omega = 10$$

$$k_1 = \frac{1}{2} V_m e^{j\theta}$$

$$6 - j8 = \frac{1}{2} V_m e^{j\theta}; \quad \theta = -53.13^\circ = -\tan^{-1}\left(\frac{8}{6}\right)$$

$$V_m = 10 \times 2 = 20V$$

$$\therefore V(t) = 20 \cos(10t - 53.13^\circ)$$

ex8: find S ?

$$i(t) = (2e^{-100t} + e^{-200t}) \sin(200t)$$

Sol: $i(t) = 2e^{-100t} \sin(200t) + e^{-200t} \sin(200t)$



$$S_1 = ?$$



$$S_2 = ?$$

$$S_1 = -100 + j200$$

$$S_2 = -200 + j200$$

Frequency response representation:

$$V(t) = V_m e^{\delta t} \cos(\omega t + \theta) \quad \text{exponentially damped.}$$

$$S = \delta + j\omega$$

$$\hookrightarrow V(t) = \operatorname{Re} \{ V_m e^{\delta t} e^{j(\omega t + \theta)} \}$$

$$= \operatorname{Re} \{ V_m e^{\delta t} [\cos(\omega t + \theta) + j \sin(\omega t + \theta)] \}$$

$$= \operatorname{Re} \{ V_m e^{j\theta} e^{(\delta + j\omega)t} \}$$

$$= \operatorname{Re} \{ V_m e^{j\theta} \underbrace{e^{\delta t}}_{\text{phasor}} \}$$

$$= \operatorname{Re} \{ V_m \underbrace{e^{j\theta}}_{\vec{V}} e^{\delta t} \}, \quad \vec{V} = V_m e^{j\theta} = V_m \angle \theta$$

$$V(t) = \operatorname{Re} \{ \vec{V} e^{\delta t} \}$$

* when $i(t) = I_m \cos(\omega t + \phi)$

$$\vec{I} = I_m \angle \phi$$

$$i(t) = \operatorname{Re} \{ I_m e^{j\phi} e^{j\omega t} \}$$

$$= \operatorname{Re} \{ \vec{I} e^{j\omega t} \}$$


* Since we are dealing with linear circuits,

* input & output must take the same form

e.g: exponentially damped input gives exponentially damped output!

\therefore forced ^{output} response has the same form of the forcing function.

input

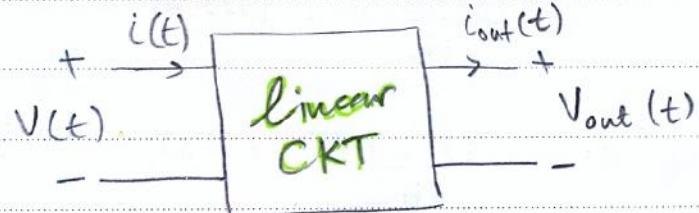

$$V(t) = \underline{V_m} e^{\underline{\delta t}} \cos(\underline{\omega t + \theta})$$


only
 V_m, θ may change
 $\omega \& \delta$ must stay the same.

$$\rightarrow V_{out}(t) = V_o e^{\delta t} \cos(\omega t + \theta_o)$$

$$i(t) = I_m e^{\delta t} \cos(\omega t + \phi)$$

$$\rightarrow i_{out}(t) = I_o e^{\delta t} \cos(\omega t + \phi_o)$$

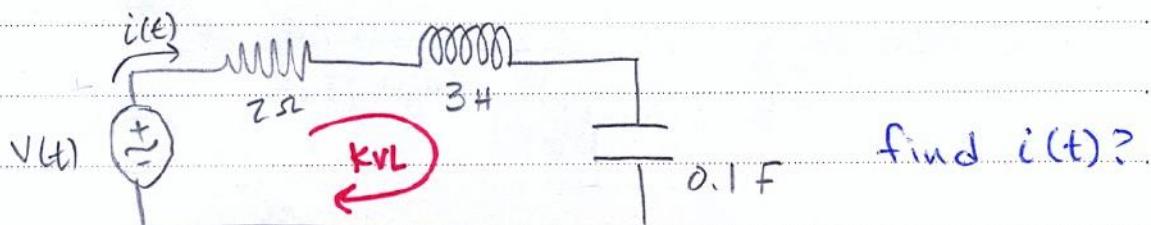ex1:- $V(t) = 60 e^{-2t} \cos(4t + 10^\circ) \text{ V}$



Sol:- Since it's a linear CKT...

$$i(t) = I_m e^{-2t} \cos(4t + \phi) \dots @, \quad S = -2 + j4$$

I need I_m & ϕ

$$\Rightarrow V(t) = \operatorname{Re} \{ 60 e^{j10^\circ} e^{(-2+j4)t} \}$$

$$= \operatorname{Re} \{ \vec{V} e^{st} \} \quad \vec{V} = 60 \times 10^\circ, s = -2+j4$$

it's the same for $i(t)$

$$\Rightarrow i(t) = \operatorname{Re} \{ I_m e^{j\phi} e^{st} \}$$

$$= \operatorname{Re} \{ \vec{I} e^{st} \} \quad \vec{I} = I_m \times 0^\circ, s = -2+j4$$

KVL

$$V(t) = R i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt$$

$$V(t) = 2i(t) + 3 \frac{di(t)}{dt} + 10 \int i(t) dt$$

$$\operatorname{Re} \{ \vec{V} e^{st} \} = 2 \operatorname{Re} \{ \vec{I} e^{st} \} + 3 \operatorname{Re} \{ \vec{I} e^{st} \} + 10 \operatorname{Re} \{ \vec{I} e^{st} \}$$

$$\operatorname{Re} \{ 60 \times 10^\circ e^{st} \} = \operatorname{Re} \{ 2 \vec{I} e^{st} + 3 s \vec{I} e^{st} + \frac{10}{s} \vec{I} e^{st} \}$$

since $e^{st} \neq 0$


$$60 \times 10^\circ = 2 \vec{I} + 3 s \vec{I} + \frac{10}{s} \vec{I}$$

$$60 \times 10^\circ = \vec{I} \left(2 + 3s + \frac{10}{s} \right)$$

$$\therefore \vec{I} = \frac{60 \times 10^\circ}{2 + 3(-2+j4) + \frac{10}{(-2+j4)}} = \frac{5.37 \times -106.6^\circ}{\operatorname{Im}} \quad \phi$$

plug in ②
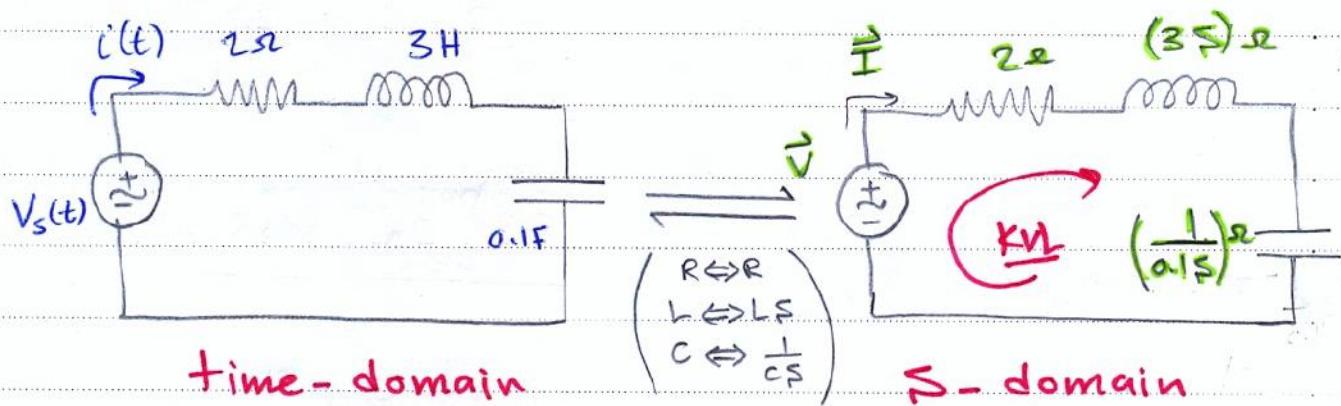
$$i(t) = 5.37 e^{-2t} \cos(4t - 106.6^\circ)$$



$$\underline{\text{KL}}: \vec{V} + 2\vec{I} + 3s\vec{I} + \frac{1}{0.1s}\vec{I} = 0$$

- impedance & admittance with respect to s !
 $\vec{Z}(s)$, $\vec{Y}(s)$ (they aren't phasors) they don't have time domain representation

- Resistor:

$V(t)$

$i(t) \quad R$

$\vec{V} \quad \vec{I}$

$V(t) = R \cdot i(t)$

$\text{Re}\{\vec{V} e^{st}\} = R \cdot \text{Re}\{\vec{I} e^{st}\}$

$\vec{Z}_f = R$

- Inductor:

$V(t)$

$i(t) \quad L$

$\vec{V} \quad \vec{I} \quad (Ls)\Omega$


$V(t) = L \frac{di(t)}{dt}$

$\Rightarrow \vec{Z}_L = sL$

$$\text{Re}\{\vec{V} e^{st}\} = L \text{Re}\{s\vec{I} e^{st}\}$$

$$\vec{V} = (sL)\vec{I}$$

- Capacitor :

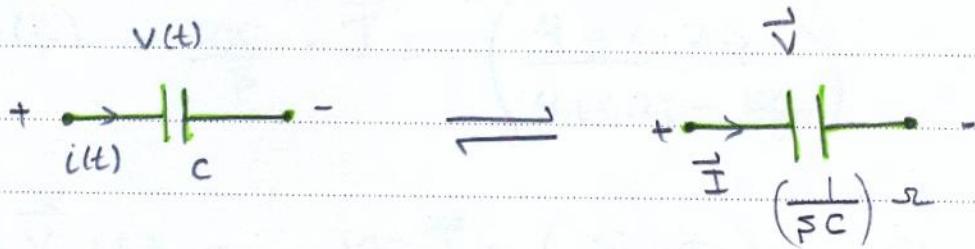

$$i(t) = C \frac{dV(t)}{dt}$$

$$\operatorname{Re}\{\vec{I} e^{st}\} = C \cdot \operatorname{Re}\{s\vec{V} e^{st}\}$$

$$\vec{I} = sC \vec{V}$$

$$\vec{V} = \left(\frac{1}{sC}\right) \vec{I}$$

$$\therefore \vec{Z}_C = \frac{1}{sC}$$

- Now, we can apply any type of analysis (mesh, Nodal, ...) over these CKTs.


Ex:-

Find $\vec{V}_1(s), \vec{V}_2(s)$:
(we'll solve with respect to s).

Sol:- $V_2(s) = \vec{I}_1 (0.2s)$

current division $\rightarrow \vec{I}_1 = \vec{I}_S \cdot \frac{\frac{100}{s}}{\frac{100}{s} + 4 + 0.2s}$
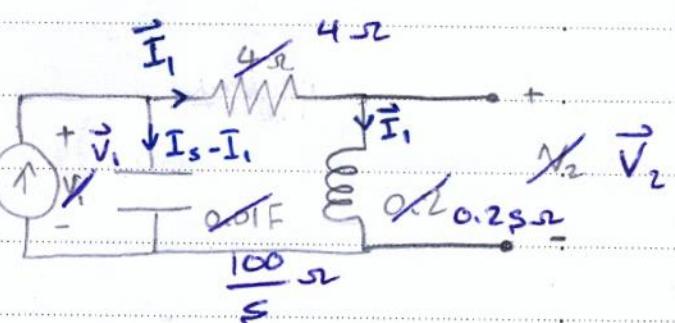
$$\rightarrow \vec{V}_2(s) = \frac{100s \vec{I}_S}{s^2 + 20s + 500} \quad \text{①}$$



$$\vec{V}_1(s) = \frac{100}{s} \cdot \vec{I}_s \left(\frac{4 + 0.2s}{4 + 0.2s + \frac{100}{s}} \right)$$

$$\rightarrow \vec{V}_1(s) = \frac{100 \vec{I}_s (s + 20)}{s^2 + 20s + 500} \quad \dots \textcircled{2}$$

→ now, let $i_s(t) = 3 e^{-st} \cos(10t + 18) A$
& $s = -5 + j10$

$$\vec{I}_s = 3 \angle 18^\circ A$$

from ① & ②

$$\rightarrow \vec{V}_1(-5 + j10) = 13.094 + j9.03 = 15.9 / 34.59^\circ V$$

$$v_1(t) = 15.9 e^{-st} \cos(10t + 34.59^\circ) V$$

$$\rightarrow \vec{V}_2(-5 + j10) = -4.55 + j8.75 = 9.86 \angle 117.5^\circ V$$

$$v_2(t) = 9.86 e^{-st} \cos(10t + 117.5^\circ) V$$

• Sketch!

step 1. • Response as a function of ω :

Section 9.5

Response function

$$\text{e.g.: } \vec{Z}(s) = \frac{\vec{V}(s)}{\vec{I}(s)} \quad \begin{matrix} \text{Input} \\ \text{Output} \end{matrix}$$

$$\vec{Y}(s) = \frac{\vec{I}(s)}{\vec{V}(s)}$$

$$\text{or } \frac{\vec{V}_i(s)}{\vec{V}_o(s)} = H(s) \quad \text{"transfer function"}$$

$$H_v(s) = \frac{\vec{V}_i(s)}{\vec{V}_o(s)}$$


transfer functions.

$$H_i(s) = \frac{\vec{I}_i(s)}{\vec{I}_o(s)}$$

* Sketch $H(j\omega)$, assume $\delta=0$

let $\vec{H}(s) = \frac{\vec{I}}{\vec{V}_s}$... ①, transfer func.
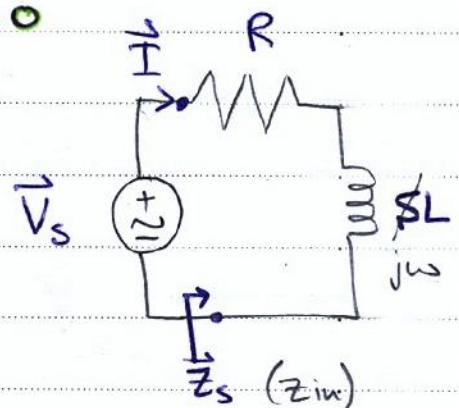
$$\vec{I} = \frac{\vec{V}}{\vec{Z}_s} = \frac{\vec{V}_s}{R+j\omega L}$$





Plug in ①

$$\vec{H}(s) = \frac{1}{R+j\omega L} \quad \leftarrow \text{Notice, it's the input admittance! } \vec{Y}_{in}$$

$$\boxed{\vec{Y}(j\omega) = \frac{1}{R+j\omega L}}$$

$$\boxed{|\vec{Y}(j\omega)| = \frac{1}{\sqrt{R^2 + \omega^2 L^2}}, \quad \text{Ang}(\vec{Y}(j\omega)) = -\tan^{-1}\left(\frac{\omega L}{R}\right)}$$

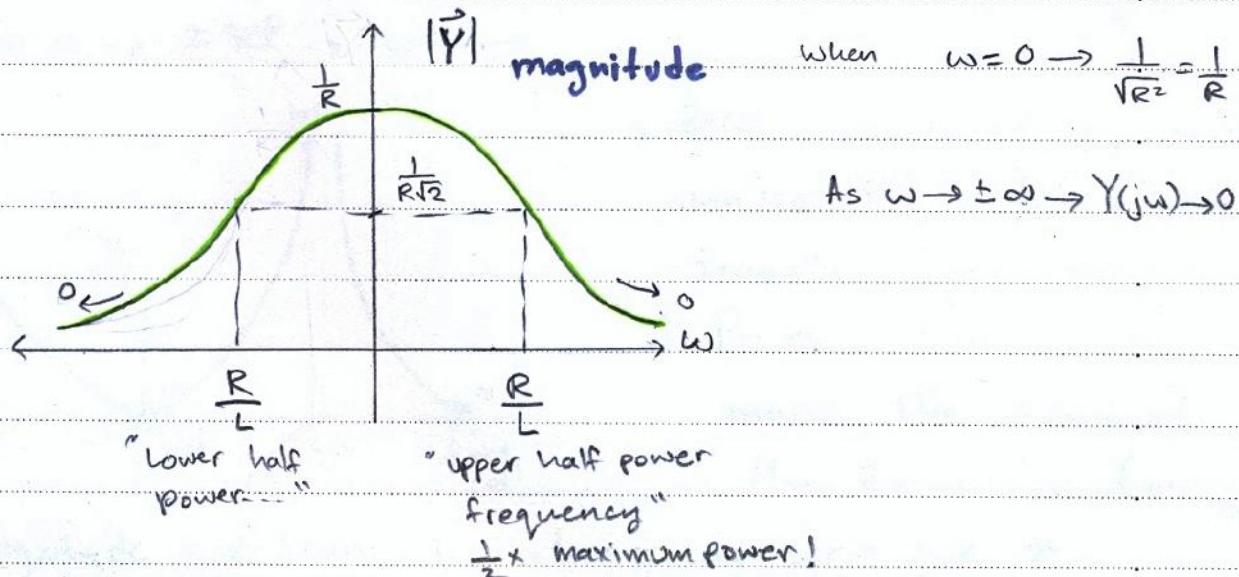

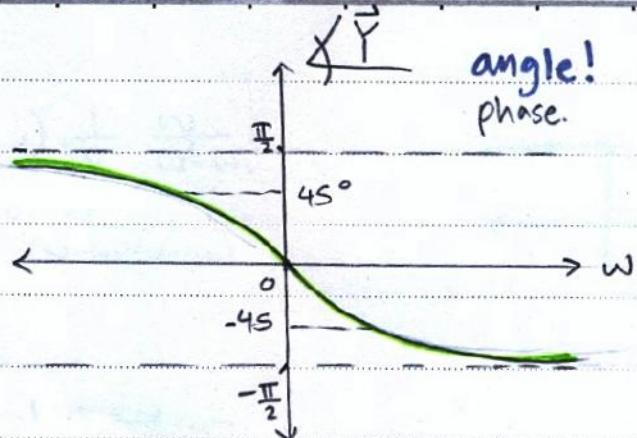


$$\text{at } \omega=0 \rightarrow \vec{Y} = 0^\circ$$

$$\text{at } \omega=\infty \rightarrow \vec{Y} = \frac{\pi}{2}$$

$$\omega = -\infty \rightarrow \vec{Y} = -\frac{\pi}{2}$$

ex:

Sketch $\frac{V}{I_s}$!

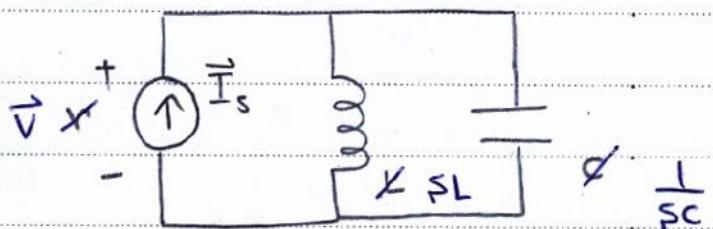

Sol:

$$\vec{V} = \vec{I}_s \left(j\omega L \right) \left(\frac{1}{j\omega C} \right)$$


$$\begin{aligned} \vec{Z}_{in} &= \frac{\vec{V}}{\vec{I}_s} = \frac{L/C}{j(\omega L - j \frac{1}{\omega C})} = -j \frac{1}{C} \frac{\omega}{\omega^2 - \frac{1}{LC}} \\ &= -j \frac{1}{C} \frac{\omega}{\omega^2 - \omega_0^2} \end{aligned}$$

$$\text{mag.} \rightarrow |\vec{Z}| = \sqrt{\left(\frac{1}{C} \frac{\omega}{\omega^2 - \omega_0^2}\right)^2} \quad \begin{matrix} \leftarrow \text{since the real part = 0.} \\ \omega_0 = \frac{1}{\sqrt{LC}} \end{matrix}$$

Phase $\rightarrow \pm 90^\circ \rightarrow (\omega)$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

resonance freq.

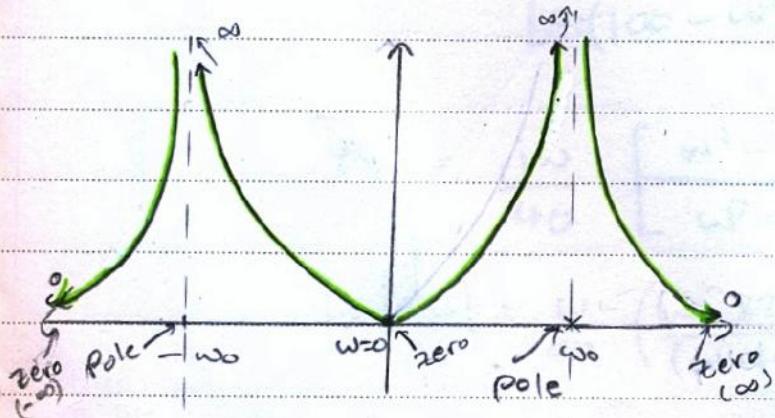

- **Zeros:** values of ω , which make the value of the transfer func. = 0.


- **Poles:** values of ω , which make the value of the transfer func. $\pm \infty$.

• magnitude spectrum is always an even func. of ω .

$$\vec{Z} = -j \frac{1}{C} \frac{\omega}{\omega^2 - \omega_0^2}$$

$$= -j \frac{1}{C} \frac{\omega}{(\omega - \omega_0)(\omega + \omega_0)}$$

↓

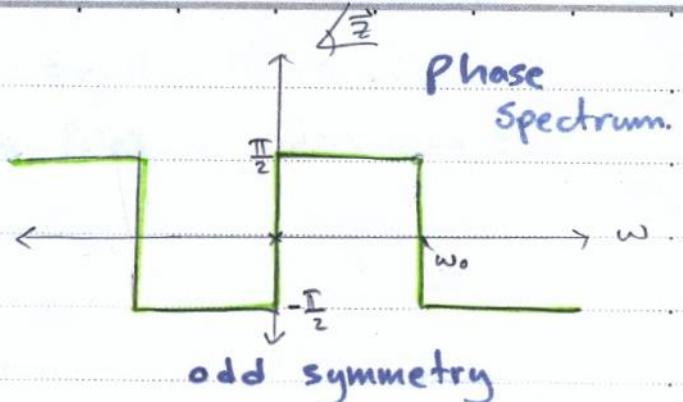

* critical points:-


@ $\omega = 0 \Rightarrow \pm \infty$ (zeros)

@ $\omega = \omega_0, -\omega_0$ (Poles)

sketching طريقة اول

الخطوة انجام

ex:

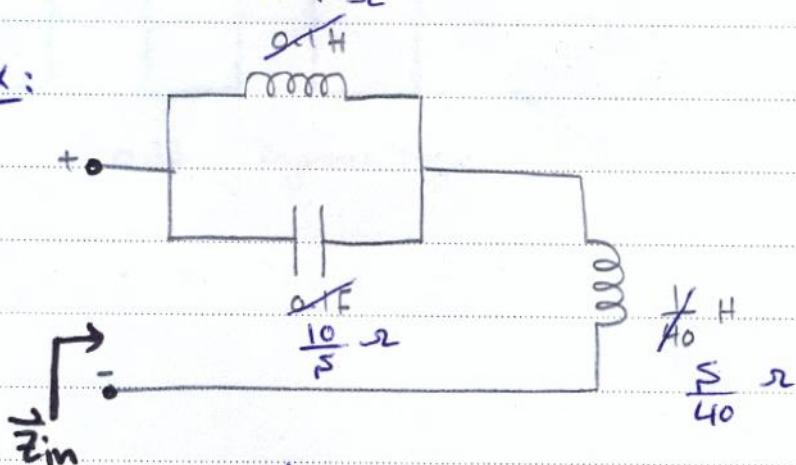

Sketch \vec{Z}_{in} ?

Sol:-


$$\vec{Z}_{in} = \frac{j\omega}{40} + \frac{(j\omega/10) * (10/j\omega)}{j\omega/10 + 10/j\omega} \quad \dots \textcircled{*}$$

$$= j\omega \left[\frac{100 - \omega^2 + 400}{40(100 - \omega^2)} \right]$$

$$\vec{Z}_{in} = \frac{j\omega}{40} \left[\frac{\omega^2 - 500}{\omega^2 - 100} \right] = \frac{j\omega}{40} \left[\frac{(\omega - \sqrt{500})(\omega + \sqrt{500})}{(\omega - 10)(\omega + 10)} \right]$$


$$\Rightarrow |\vec{Z}_{in}| = \frac{\omega}{40} \left(\frac{(\omega - 22.4)(\omega + 22.4)}{(\omega - 10)(\omega + 10)} \right)$$

mag. Spectrum

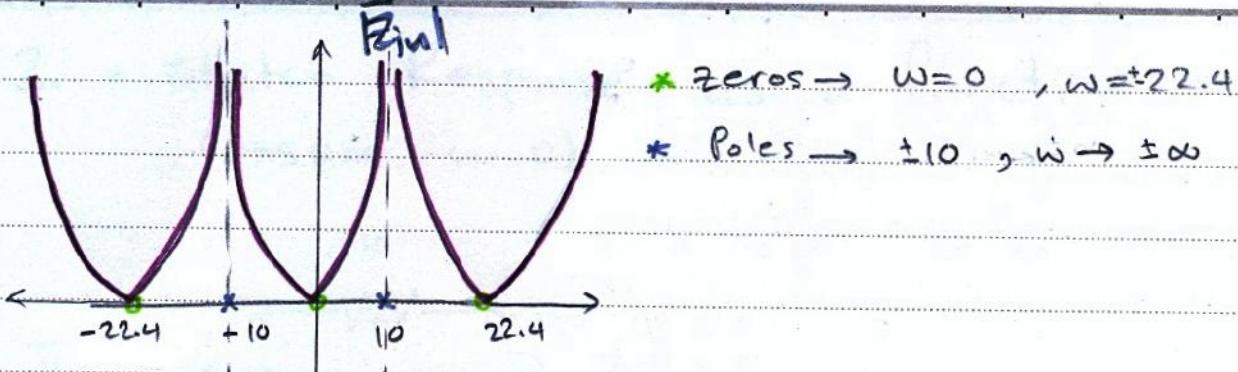


- * zeros $\rightarrow \omega = 0, \omega = \pm 22.4$
- * Poles $\rightarrow \pm 10, \omega \rightarrow \pm \infty$

even symmetry.

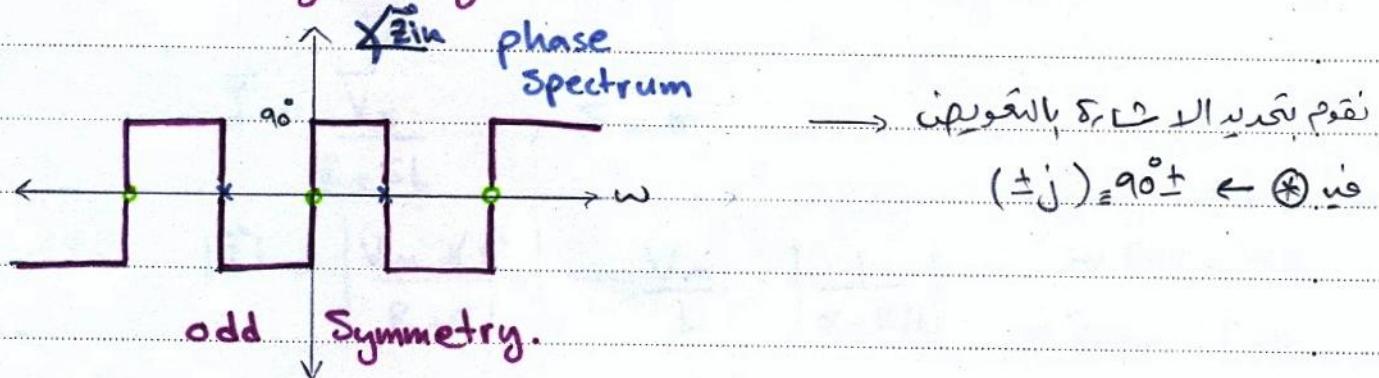

$$(\pm j) = 90^\circ \leftarrow \oplus$$

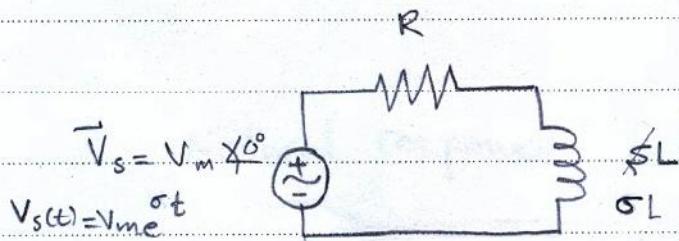Step 2. Sketch Response as a function of σ :
 (assume $\omega=0$)



$$\vec{I} = \frac{\vec{V}_s}{R + \sigma L}, \quad \sigma = \sigma$$

$$|\vec{I}| = \left| \frac{V_m X 0^\circ}{R + \sigma L} \right| = \frac{V_m}{L} \cdot \left| \frac{1}{\sigma + R/L} \right|$$

* Zeros of Denominator


→ Poles of \vec{I}

* Zeros of Numerator

→ Zeros of \vec{I}

* Zeros → @ $\sigma \rightarrow \pm \infty$

* pole → @ $\sigma = -R/L$

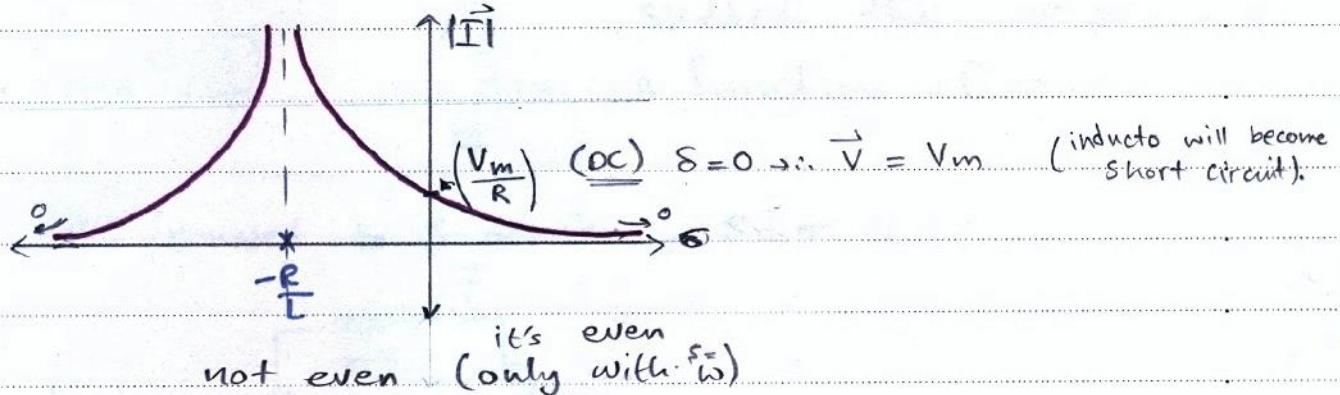


$$i(t) = \frac{V_m}{R + \sigma L} e^{\sigma t}$$

* pole at $-R/L$

means ⇒ if $\vec{V}_s = V_m e^{\sigma t}$ & $\sigma = -R/L$

then $I \rightarrow \infty$
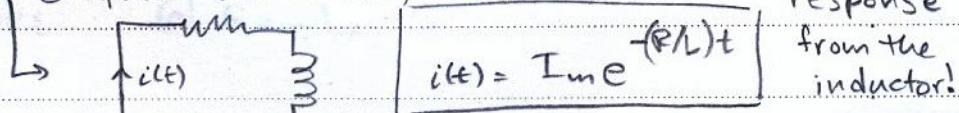
$$\therefore \frac{\vec{I}}{\vec{V}_s} = \infty = \frac{1}{0} ; \text{ when } \sigma = -\frac{R}{L}$$



Natural response from the inductor!

$$i(t) = I_m e^{-R/L t} \Rightarrow i(t) = I_m e^{-t/\tau}$$

; $\tau = \frac{L}{R}$; 'time constant'


\therefore Natural response in $i(t)$ equals:-

$$i_n(t) = I_m e^{-Rt/L}$$

natural response:
without any forcing
function.


\Rightarrow applying a zero - Amplitude forcing
function produces a non-zero forced
response.

ex:-

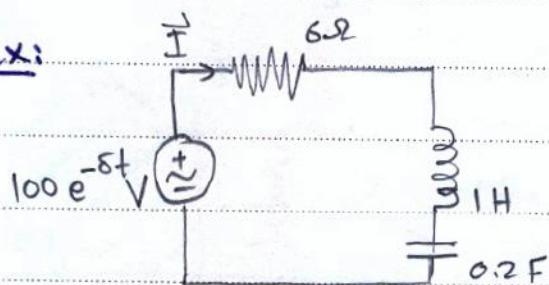

, sketch the response I as a function of σ

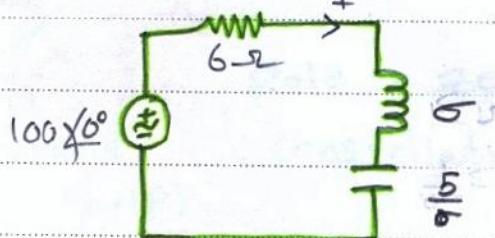Sol:- convert to ζ -domain, $\zeta = \sigma$:-




$$\vec{I} = \frac{100}{6 + \sigma + \frac{\zeta}{\sigma}} = \frac{100 \sigma}{6\sigma + \sigma^2 + 5} = \frac{100 \sigma}{(\sigma+1)(\sigma+5)}$$

* Critical points:-

- Zeros @ $\sigma = 0$


- Poles @ $\sigma = -1, -5$

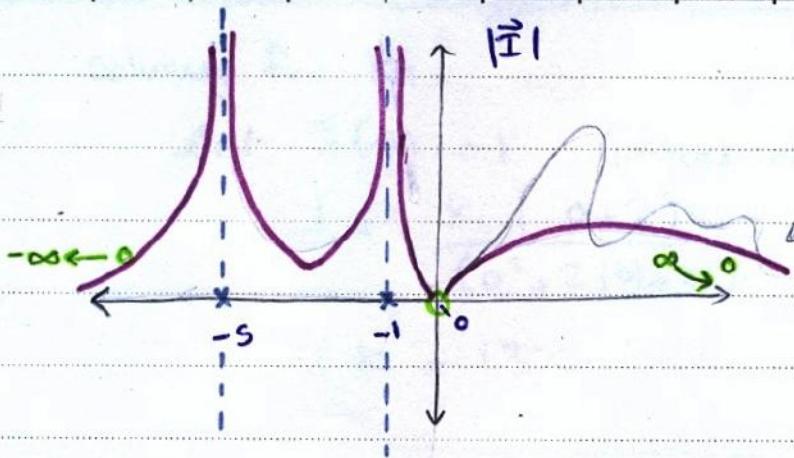

Natural response :-

$$i_n(t) = A e^{-1t} + B e^{-5t}$$

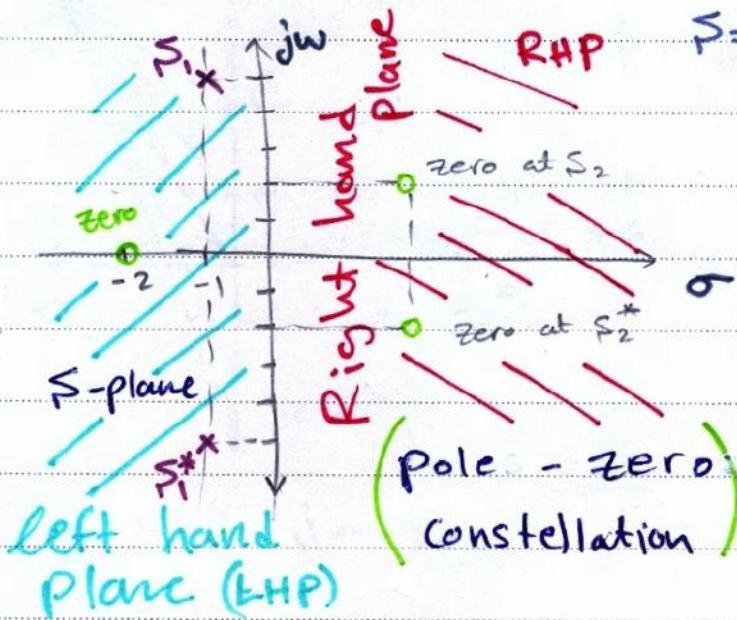Step 3 • Sketch with respect to $s = \sigma + jw$ (3D)!
* introducing the s -plane:



$s_1 = -1 + j5$ (pole)
if I have a pole at
 s_p , then another
pole must appear
at s_p^*

if these poles & zeros were for some impedance
 $\tilde{Z}(s)$, then:-

$$\begin{aligned}\tilde{Z}(s) &= K \frac{(s+2)}{(s+1-j5)(s+1+j5)} \Rightarrow \text{zeros}; \quad K \text{ is a constant} \\ &= K \frac{(s+2)}{s^2 + 2s + 26}\end{aligned}$$

Solving for k :

let $\vec{z}(0) = 1$ (initial condition)


$$1 = \frac{k(0+2)}{(0^2 + 2(0) + 26)} = \frac{k \cdot 2}{26}$$

$$\therefore k = 13$$

$$\rightarrow \vec{z}(s) = 13 \frac{(s+2)}{s^2 + 2s + 26}$$

So, we found this eqn.
from the s -plane!


Sketch with respect to w using s -plane:

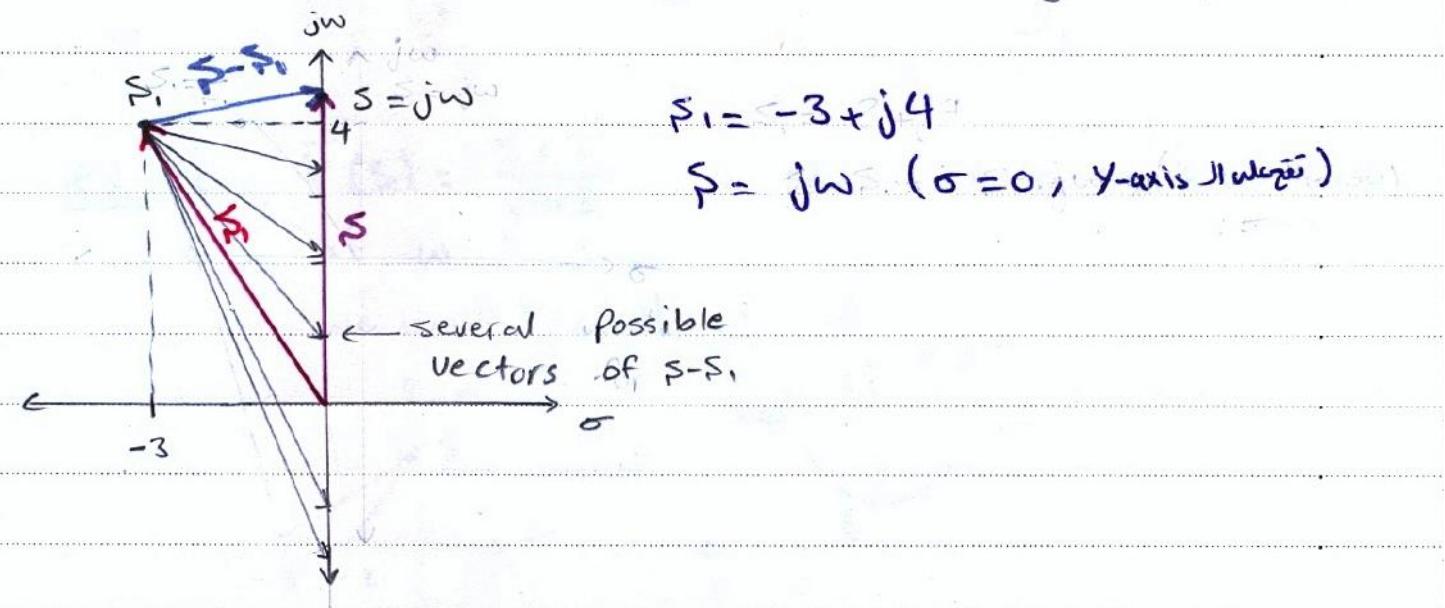


$$s - s_1 = jw - s_1$$

Ex:- $\vec{Y}(s) = \frac{s+2}{s-s_1} \Rightarrow$ Sketch Y with respect to w


Sol:- $s = jw$, $s_1 = -2$

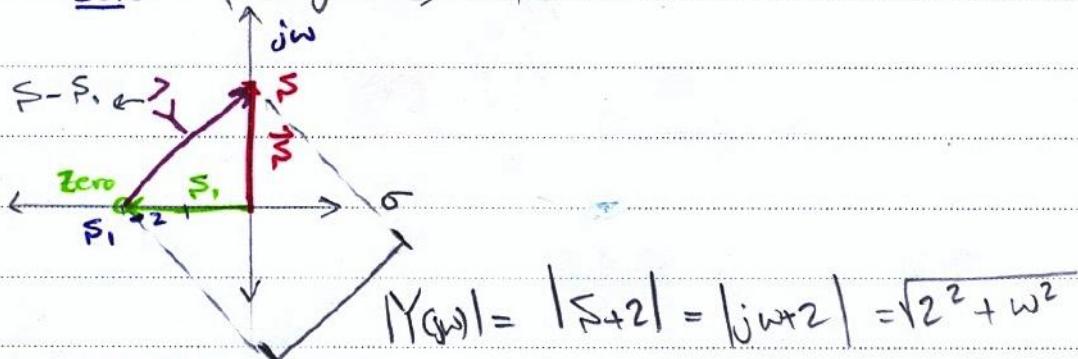

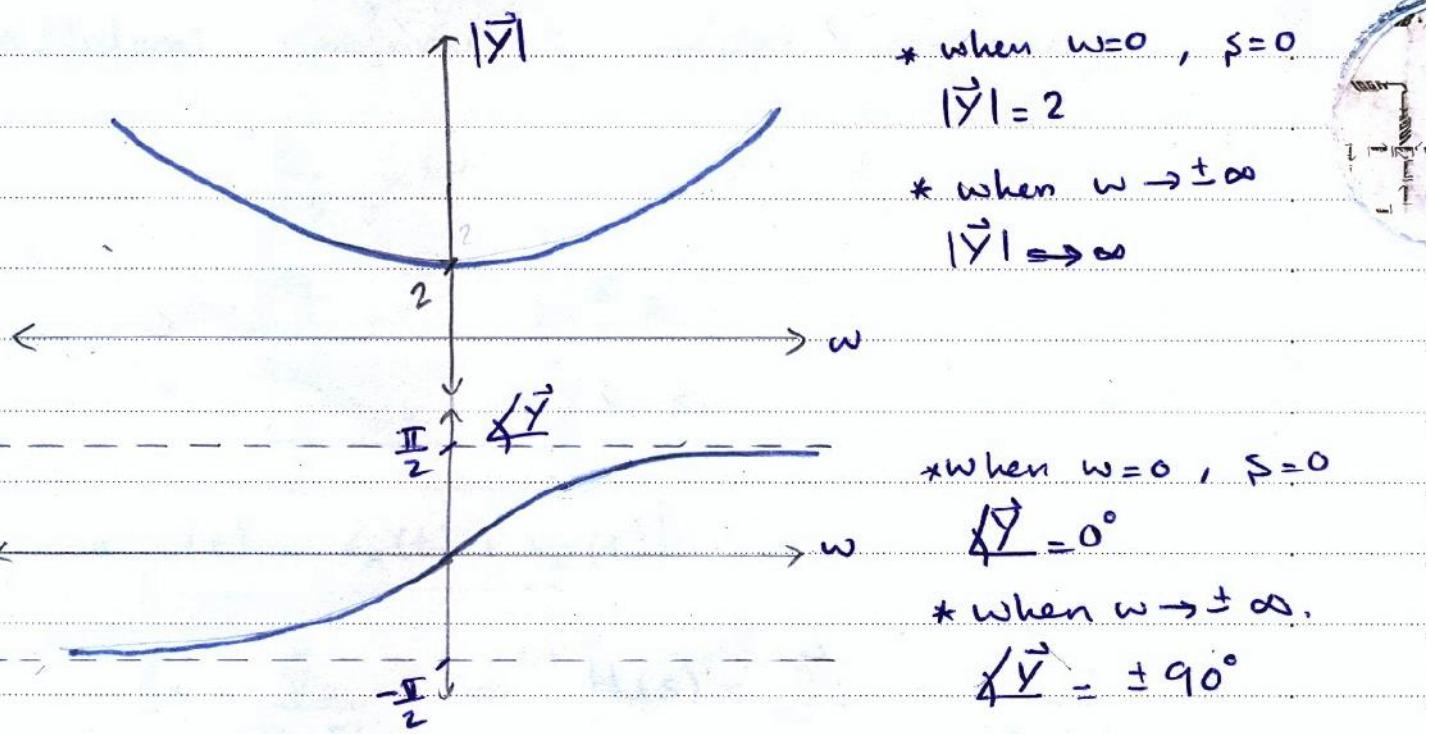


ex 2 :- $\vec{V}(s) = \frac{s+2}{s+3}$, Sketch \vec{V}_s as a function of ω .

we need $|V(j\omega)|$, $\angle V(j\omega)$

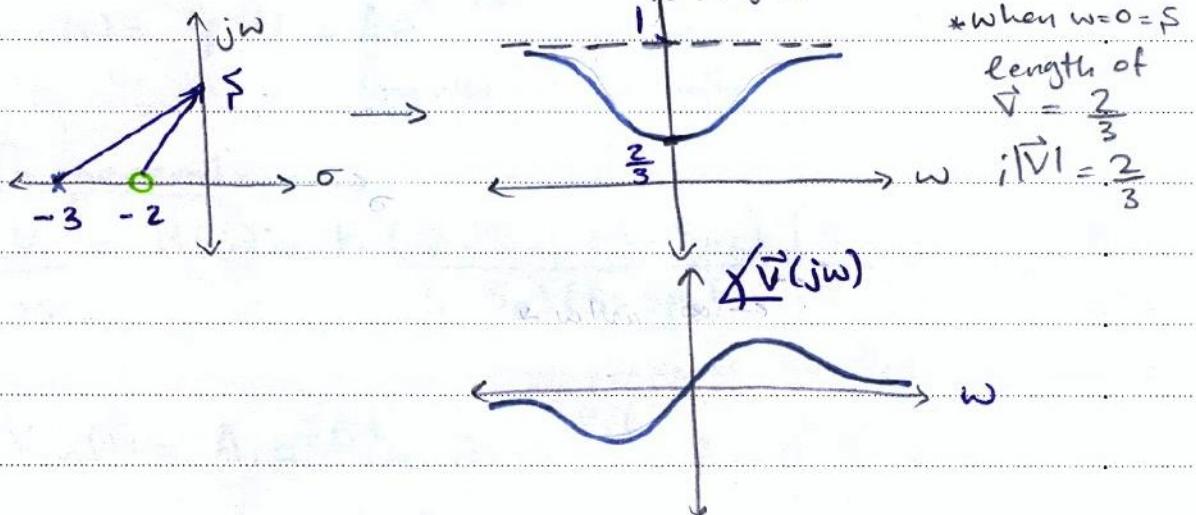

* Natural Response & complex frequency:

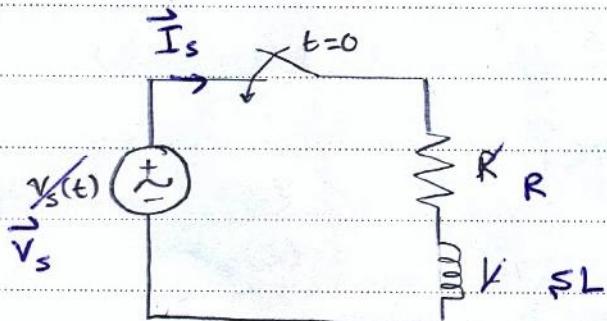

$$* \quad i(t) = i_n(t) + i_f(t)$$

$$\vec{I}_s = \frac{\vec{V}_s}{R + \frac{1}{L}} \Rightarrow H(s) = \frac{\vec{I}_s}{\vec{V}_s} = \frac{1}{R + \frac{1}{sL}}$$

$$\rightarrow s_p = -R/L \quad H(s) = \frac{1}{L} \cdot \frac{1}{s + R/L}$$

$$i_n(t) = Ae^{-\frac{R}{L}t}$$

$$\therefore i(t) = i_f(t) + Ae^{-(R/L)t}$$

from the initial condition.

In general:-

$$\text{if } \frac{V_2}{V_s} = H(s) = K \frac{(s - s_{o1})(s - s_{o2})(s - s_{o3}) \dots}{(s - s_{p1})(s - s_{p2})(s - s_{p3}) \dots} \text{ Zeros}$$

Poles.

$$\text{then } \rightarrow V_{2n}(t) = \underbrace{A_1 e^{s_p 1 t}}_{\text{from initial conditions.}} + \underbrace{A_2 e^{s_p 2 t}}_{\text{poles of the transfer function.}} + \underbrace{A_3 e^{s_p 3 t}}_{\dots} + \dots$$

$$\star \text{ if } \overline{s_p 3} = \overline{s_p 4^*} = \gamma + j\beta$$

$$V_{2n}(t) = A_1 e^{s_p 1 t} + A_2 e^{s_p 2 t} + e^{\gamma t} [a \cos(\beta t) + b \sin(\beta t)] +$$

from initial cond.s


ex:- find $i_1(t)$ & $i_2(t)$, $t > 0$

if $i_1(0) = 11A$

$i_2(0) = 11A$

Sol:
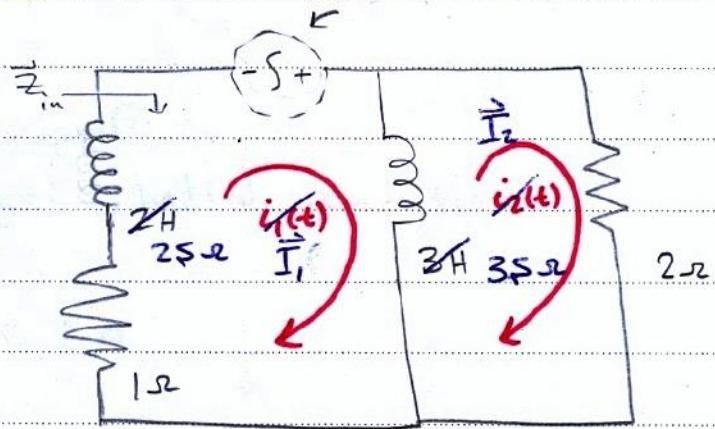
$$H(s) = \frac{\vec{I}_1(s)}{\vec{V}_s(s)}$$



* find $H(s)$

$$I_1(s) = \frac{\vec{V}_s}{(2s+1 + \frac{6s}{3s+2})}$$

Excluding independent voltage source V_s و موجة مستقلة V_s

V_s source affects current i_1 only

($I_{\text{source}} \approx V \approx i_1 \approx i_2$)

$$H(s) = \frac{I_1(s)}{V_s} = \frac{1}{2s+1 + \frac{6s}{3s+2}}$$

$$= \frac{3s+2}{6s^2+13s+2}$$

$$\begin{aligned} i_1(t) &= i_{m1}(t) \\ i_2(t) &= i_{m2}(t) \end{aligned}$$

$$H(s) = \frac{1}{2} \frac{s + \frac{2}{3}}{(s+2)(s+1/6)}$$

poles of $H(s)$; أضلاع العاشر

$$\bullet i_1(t) = A_1 e^{-2t} + B_1 e^{-\frac{1}{6}t} \quad \textcircled{a}$$

$$\bullet i_2(t) = A_2 e^{-2t} + B_2 e^{-\frac{1}{6}t} \quad \textcircled{b}$$

* finding initial conditions:

from the question

$$i_1(0) = 11A$$

$$i_2(0) = 11A$$

Plugging in \textcircled{a} and \textcircled{b} initial

$$i_1(0) \Rightarrow A_1 + B_1 = 11 \quad \textcircled{1}$$

• for (a):

$$i_1(0) = \boxed{A_1 + B_1 = 11} \quad \dots \textcircled{1}$$

we need another initial condition:

$$\left. \frac{di_1(t)}{dt} \right|_{t=0} = -2A_1 - \frac{1}{6}B_1 \quad \dots \textcircled{2}$$

KVL (the outer loop)

$$1i_1(t) + 2\frac{di_1(t)}{dt} + 2i_2(t) = 0$$

$$\frac{di_1(t)}{dt} = -\frac{1}{2} [i_1(t) + 2i_2(t)]$$

$$\left. \frac{di_1(t)}{dt} \right|_{t=0} = -\frac{1}{2} [i_1(0) + 2i_2(0)] = -\frac{33}{2}$$

plug in $\textcircled{2}$

$$-\frac{33}{2} = -2A_1 - \frac{1}{6}B_1 \quad \dots \textcircled{2}$$

solving $\textcircled{1}$ & $\textcircled{2}$ \rightarrow

$A_1 = 8$
$B_1 = 3$

$$i_1(t) = 8e^{-2t} + 3e^{-t/6}$$

for equ. (b):

$$i_2(0) = \boxed{A_2 + B_2 = 11} \dots \textcircled{3}$$

we need another initial condition:

$$\left. \frac{d i_2(t)}{dt} \right|_{t=0} = -2 A_2 - \frac{1}{6} B_2 \dots \textcircled{4}$$

KVL (the 2nd loop)

$$2 i_2(t) + 3 \frac{d(i_2(t) - i_1(t))}{dt} = 0$$

$$\frac{d i_2(t)}{dt} = \frac{d i_1(t)}{dt} - \frac{2}{3} i_2(t)$$

$$\left. \frac{d i_2(t)}{dt} \right|_{t=0} = -\frac{33}{2} - \frac{2}{3} \times 11 = -\frac{143}{6}$$

Plug in $\textcircled{4}$


$$-\frac{143}{6} = -2 A_2 - \frac{1}{6} B_2 \dots \textcircled{4}$$

solve $\textcircled{3} \& \textcircled{4} \rightarrow A_2 = 12, B_1 = -1$

$$i_2(t) = 12 e^{-2t} - e^{-t/6}$$

Ex:-

12Ω

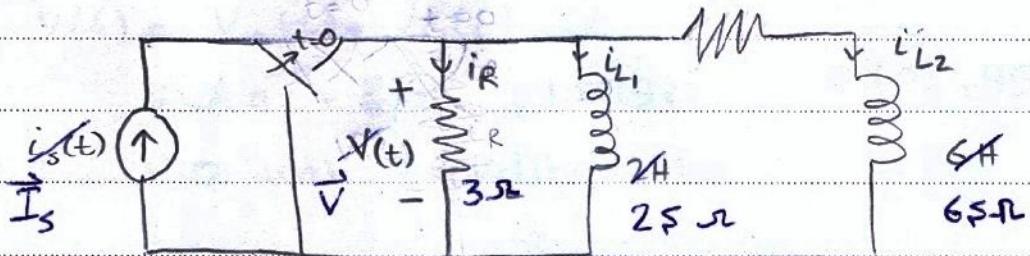

$$i_s(t) = e^{-t} \cos(2t) \text{ A} \rightarrow \vec{I}_s = 1 \times \hat{\phi}$$

$$s = -1 + j2, \text{ find } V(t)?$$

Sol:-

- $\boxed{V(t) = V_n(t) + V_f(t)} \dots \circledast$

$$\vec{V} = \frac{\vec{I}_s}{\text{admittance}} = \frac{\vec{I}_s}{\frac{1}{3} + \frac{1}{2S} + \frac{1}{12+6S}} = \frac{3S(S+2)}{(S+1)(S+3)} \vec{I}_s$$

- $H(s) = \frac{\vec{V}}{\vec{I}_s} = \frac{3S(S+2)}{(S+1)(S+3)} \Rightarrow \text{poles} = -1, -3$

$$\rightarrow V_n(t) = A e^{-t} + B e^{-3t} \quad \text{natural response.}$$

$$\begin{aligned} \rightarrow V_f(s) &= \vec{I}_s \times H(s) \\ &= \vec{I}_s \times \frac{3S(S+2)}{(S+1)(S+3)} \end{aligned}$$

$$V_f(-1+j2) = 1 \angle 0^\circ \cdot 3(-1+j2) \frac{(-1+j2+2)}{(-1+j2+1)(-1+j2+3)}$$

$$|V_f(s)| = 1.875\sqrt{2} \angle 45^\circ$$

$$V_f(t) = 1.875\sqrt{2} e^{-t} \cos(2t + 45^\circ)$$

back to ④ :-

$$V(t) = V_n(t) + V_f(t) \\ = A e^{-t} + B e^{-3t} + 1.875\sqrt{2} e^{-t} \cos(2t+45^\circ)$$

* I need 2 initial conditions to find A & B

$$\stackrel{t=0}{V(0)} = A + B + 1.875\sqrt{2} \cos 45^\circ \dots \textcircled{A}$$

$$\hookrightarrow i_{L_1}(0^+) = i_{L_2}(0^-) = 0$$

$$\therefore i_{L_1}(0^+) = i_{L_2}(0^+) = 0$$

$$V(0) = I_s(0) \times 3$$

$$= 1 \times 3 = 3 \text{ V}$$

plug in ④

$$3 = A + B + 1.875 \dots \textcircled{1}$$

$$2^{\text{nd}}) \frac{dv}{dt} = -Ae^{-t} - 3Be^{-3t} + 1.875\sqrt{2} \left[-2e^{-t} \sin(2t+45^\circ) - e^{-t} \cos(2t+45^\circ) \right]$$

$$\left. \frac{dv}{dt} \right|_{t=0} = -A - 3B - 5.625 \dots \textcircled{2}'$$

$$\hookrightarrow V(t) = 3i_R(t) =$$

$$= 3(i_s(t) - i_{L_1}(t) - i_{L_2}(t))$$

$$\frac{dv(t)}{dt} = 3 \left(\frac{di_s(t)}{dt} - \frac{di_{L_1}(t)}{dt} - \frac{di_{L_2}(t)}{dt} \right) \dots \textcircled{B}$$

$$\hookrightarrow \left. \frac{di_s(t)}{dt} \right|_{t=0} = -2e^{-t} \sin(2t) - e^{-t} \cos(2t)$$

$$\left. \frac{di_s(t)}{dt} \right|_{t=0} = -1$$

$$\rightarrow L_1 \left. \frac{di_L_1}{dt} \right|_{t=0} = V(t) \Big|_{t=0} \quad V(0) = 3$$

$$\frac{2}{2} \left. \frac{di_{L_1}}{dt} \right|_{t=0} = \frac{3}{2}$$

$$\rightarrow L_2 \left. \frac{di_{L_2}}{dt} \right|_{t=0} = V(0)$$

$$\frac{6}{6} \left. \frac{di_{L_2}}{dt} \right|_{t=0} = \frac{3}{6}$$

plug in ③

$$\left. \frac{dv}{dt} \right|_{t=0} = 3 \left(-1 - \frac{3}{2} - \frac{3}{6} \right) = -9 \quad \leftarrow \text{the 2nd initial condition } \left(\left. \frac{dv}{dt} \right|_{t=0} = -9 \right)$$

plug in ②

$$-A - 3B - 5.625 = -9 \quad \dots \textcircled{2}$$

solving ① & ② $\rightarrow A = 0, B = 1.125$

$$V(t) = \underbrace{1.125 e^{-3t}}_{V_n(t)} + \underbrace{1.875\sqrt{2} e^{-t} \cos(2t + 45^\circ)}_{V_f(t)} V$$

second
exam

In fig 1 below, the 3-phase source is balanced, P_1 reads upscale 4411 Watt, while P_2 reads downscale 1000 Watt, & $V_{AB} = 440 \angle 60^\circ V_{rms}$
 Determine:-

(2marks) The value of P.F for the load (is it leading or lagging?)

(4marks) I_{AA} and Z_p

(2marks) V_{an}

(2marks) the P.F at the source (is it leading or lagging?) & the total p complex power of the source-

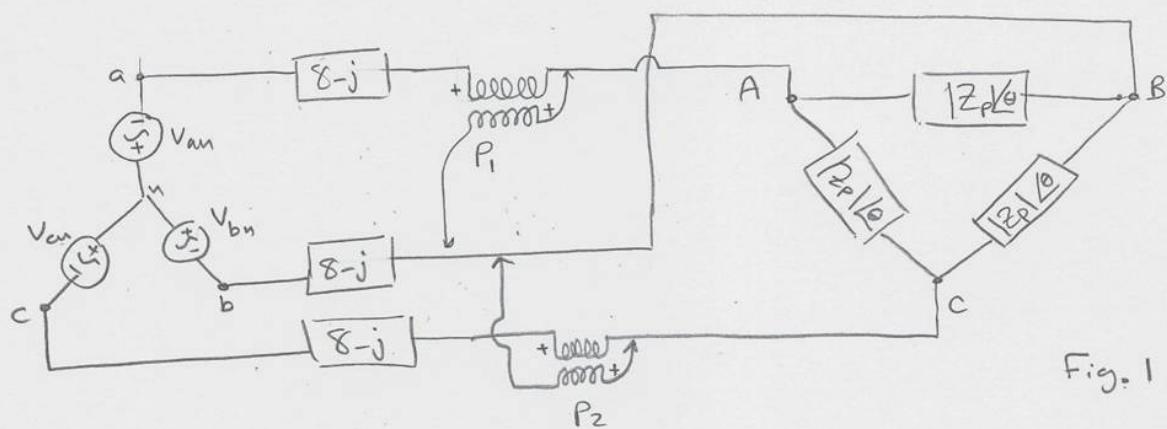


Fig. 1

$$\tan \theta = \sqrt{3} \frac{(P_2 - P_1)}{(P_2 + P_1)}, P_1 = 4411, P_2 = -1000$$

$$\tan \theta = \sqrt{3} \frac{(-1000 - 4411)}{(-1000 + 4411)} = -2.742$$

$$\Rightarrow \theta = \tan^{-1}(-2.742) = -70^\circ$$

$$\Rightarrow P.F_L = \cos(-70^\circ) = 0.342 \text{ leading.}$$

$$P_1 = |V_{AB}| |\vec{I}_{AA}| \cos(30^\circ + \theta) \Rightarrow \frac{4411}{440 \times \cos(40^\circ)} = 13.0867 = |\vec{I}_{AA}|$$

$$\Rightarrow \vec{I}_{AA} = \sqrt{3} \times 30^\circ \vec{I}_{AB} \Rightarrow |\vec{I}_{AB}| = \frac{13.0867}{\sqrt{3}} = 7.5556$$

$$|Z_p| = \frac{440}{7.5556} = 58.23484 \Rightarrow \boxed{\vec{Z}_p = 58.23484 \times 70^\circ}$$

$$\Rightarrow \vec{I}_{AB} = \frac{V_{AB}}{Z_p} = \frac{440 \times 30^\circ}{58.23484 \times 40^\circ} = 7.5556 \times 70^\circ$$

$$\Rightarrow \vec{I}_{an} = 13.0867 \times 40^\circ$$

$$\text{OR: } P_T = 4411 - 1000 = 3411 \Rightarrow P = \frac{3411}{3} = 1137 \text{ W}$$

$$P_P = |\vec{V}_{AD}| |\vec{I}_{AB}| \cdot P.F_L \Rightarrow |\vec{I}_{AB}| = \frac{1137}{440 \times 0.342} = 7.555$$

$$\Rightarrow \boxed{\vec{I}_{AB} = 7.555 \angle 70^\circ} \Rightarrow \boxed{\vec{I}_{aa} = 13.0867 \angle 40^\circ}$$

$$\vec{V}_{an} = (8-j) \vec{I}_{aa} + \frac{440 \angle 30^\circ}{\sqrt{3} \angle 30^\circ} = 316.39 \angle -12.73^\circ$$

$$\text{OR: } \vec{V}_{nb} = (8-j) \vec{I}_{aa} + \vec{V}_{AB} - (8-j) \vec{I}_{bb} \Rightarrow \vec{I}_{bb} = 13.0867 \angle -8^\circ$$

$$\Rightarrow \boxed{\vec{V}_{an} = \frac{\vec{V}_{nb}}{\sqrt{3} \angle 30^\circ} = 316.39 \angle -12.73^\circ}$$

$$\text{OR: } \vec{Z}_Y = \frac{\vec{Z}_\Delta}{3} \Rightarrow \vec{V}_{an} = [(8-j) + \vec{Z}_Y] \vec{I}_{aa}$$

$$S^1 = 3 \vec{V}_{an} \times \vec{I}_{aa}^*$$

$$= 12421.5 \angle -52.73^\circ$$

$$P.F_s = \cos(-12.73 - 40^\circ) = 0.60557 \text{ leading}$$

Section:.....

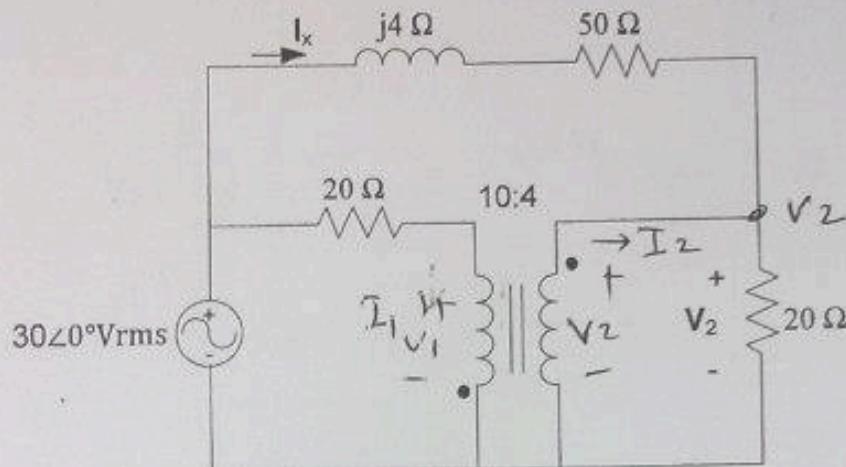
Q(2): (a) (6 marks) For the circuit shown in Fig.2 find: V_2 and I_x .

Fig. 2

$$\text{Mesh 1} \quad -30\angle 0^\circ + 20I_1 + V_1 = 0$$

$$V_1 = 30\angle 0^\circ - 20I_1 \quad \text{--- (1)}$$

$$\frac{I_1}{I_2} = 0.4 \quad \text{--- (2)}$$

$$\frac{V_2}{V_1} = -0.4 \quad \text{--- (3)}$$

$$\text{Nodal.} \quad \frac{30\angle 0^\circ - V_2}{50+j4} + V_2 = \frac{V_2}{20} \quad \text{--- (4)}$$

Solve for V_2, I_x .

$$I_x = 0.76 \angle -4.6^\circ$$

$$V_2 = 8.9 \angle -178^\circ$$

Section.....

- (b) (4 marks) For the circuit shown in Fig.3 given $v_s(t) = 20 \cos 10t$ V, find $v(t)$.

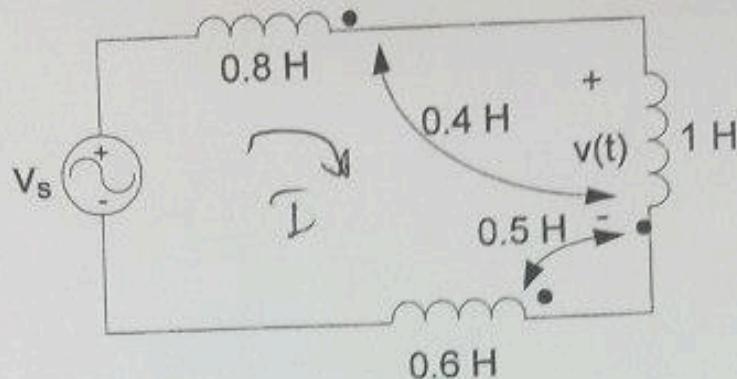


Fig. 3


$$-20 + j8I + j10I + j6I + j4I_1 + j4I \\ -j5I - j5I = 0$$

$$I = \frac{20}{j_{22}}$$

$$V = I [j10 + j4 - j5]$$

$$v(t) = 8.18 \cos 10t$$

Q3

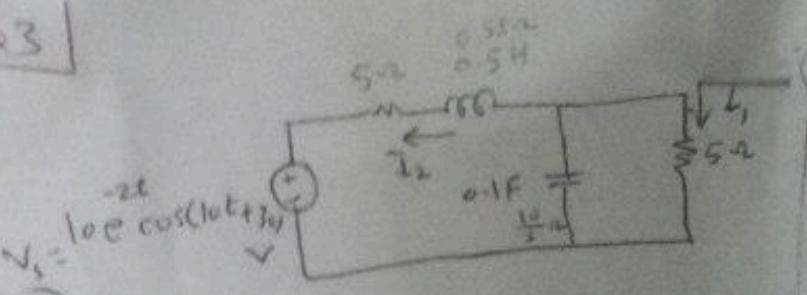


$$\frac{I_2}{V_s} = \frac{10 + 5s}{2.5s^2 + 30s + 100}$$

$$Z_2 = -\frac{w}{s} = -2 \quad (1)$$

$$P_1 =$$

$$P_2 =$$

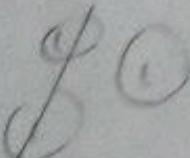

$$\textcircled{1} \quad i_1(t) = ?$$

- \textcircled{2} the natural response for i_2 in the s-domain
- \textcircled{3} Constestate all poles/zeros for i_2

$$s = -2 + j10.$$


$$\text{Given } V_s = 10e^{-2t} \cos(10t + 30^\circ) \quad \textcircled{1}$$

$$\therefore V_{sp} = 10e^{j30^\circ}$$

$$\begin{aligned} \text{using N.D.} \quad V_{so} &= \frac{V_p}{s + \frac{10}{2} + j10} \\ &= \frac{10e^{j30^\circ}}{\left(s + \frac{10}{2}\right)^2 + 10^2 + j10} \\ &= \frac{10e^{j30^\circ}}{2.5s^2 + 30s + 100} \\ &= \frac{500e^{j30^\circ}}{(-240 - j100 - 60t)300 + 100} \\ &= \frac{500e^{j30^\circ}}{-2000 + j200} = 1.76e^{j-105^\circ} \end{aligned}$$

$$i_1 = \frac{1.76e^{-105^\circ}}{5} = 0.352 e^{-105^\circ}$$

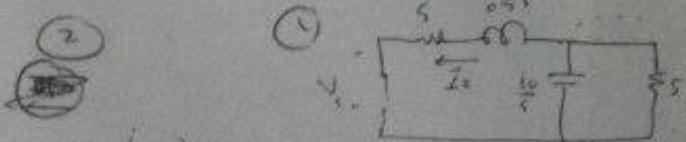
$$i_1(t) = 0.352 e^{-2t} \cos(10t - 105^\circ) \quad \textcircled{1}$$




$$i_1 = ?$$

$$\begin{aligned} V_s &= \left(\frac{50}{10+5s} + 0.5s + 5 \right) I_2 \quad \textcircled{1} \quad \frac{5(10)}{s+10+5s} \\ \therefore \frac{I_2}{V_s} &= \frac{1}{\frac{50}{10+5s} + 0.5s + 5} = \frac{10+5s}{50 + 5s^2 + 10s} \\ &= \frac{10+5s}{50 + 25s + 5s^2 + 2s^2 + 10s} \end{aligned}$$

Chapter # 16: Frequency Response:-

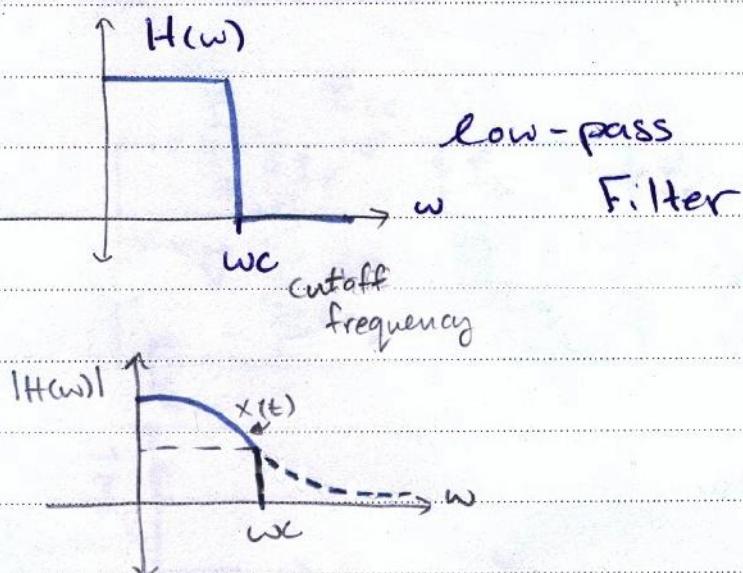


Resonance:-

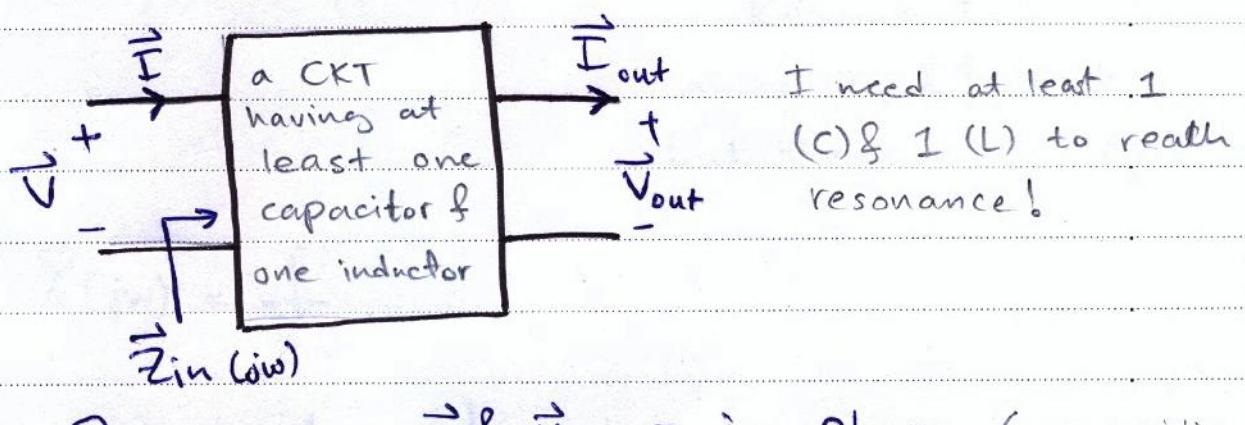

@ resonance:- \vec{I} & \vec{V} are in Phase (pure resistive \vec{Z}_in).
 $w = w_0 \rightarrow Z_{in} = R$

@ resonance:- the amplitude of the response is either max. or min. (\vec{V}, \vec{I})

→ Parallel resonant ckt:

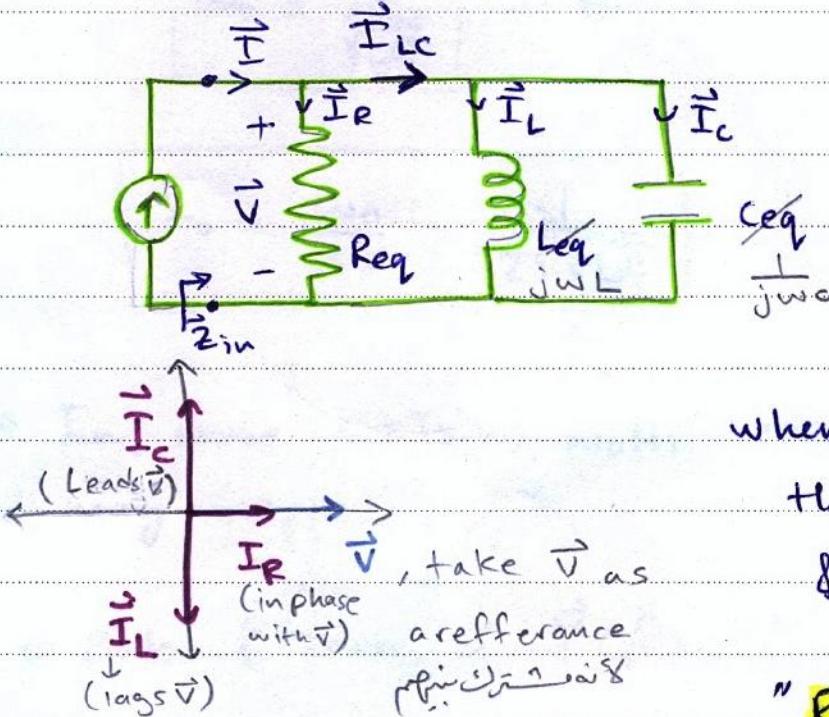

$$\text{when } |I_L| = |I_C|$$

they cancel each other
 $\& I = I_R$
 $\therefore Z_{in} = R$

"Resonant CKT"

where $I_C \& I_L \neq 0$

but they cancel each other

$$\vec{Y}(j\omega) = \frac{1}{Z_{in}}$$

$$= \frac{1}{R} + \frac{1}{j\omega L} + j\omega C \quad \text{it's easier to deal}$$

with admittance

$$\vec{Y}(j\omega) = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right) \dots \textcircled{*} \quad \text{since it's a parallel RLC CKT}$$

@ resonance

$$\vec{Y}(j\omega) = \frac{1}{R} \dots \textcircled{**}; \text{ since } Z_{in} = R$$

*maximum impedance @ resonance.

$\therefore 1^{st}$ condition of resonance from $\textcircled{*}, \textcircled{**}$

$$\omega_0 C - 1/\omega_0 L = 0$$

$$\Rightarrow \omega_0 C = \frac{1}{\omega_0 L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{--- A [rad/sec]}$$

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}} \quad [\text{Hz}]$$

- In some CKTs, multi resonance freq. may appear!

\Rightarrow Poles & zeros of $\vec{Y}(j\omega)$

$$\vec{Y}(s) = \frac{1}{R} + \frac{1}{sL} + sC$$

$$= C(s^2 + s/Rc + 1/Lc)$$

$$\vec{Y}(s) = \frac{C}{s} (s + \alpha - j\omega) (s + \alpha + j\omega)$$

$$\alpha = \frac{1}{2RC}$$

"exponential damping coefficient [Np/sec]"

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

"Natural resonant freq. [rad/sec]"

$$\therefore \vec{Y}(s) = C \frac{s^2 + 2\alpha s + \omega_0^2}{s}$$

$$s = \frac{-2\alpha \pm \sqrt{4\alpha^2 - 4\omega_0^2}}{2}$$

$$\Rightarrow s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$


$$= -\alpha \pm j(\sqrt{\omega_0^2 - \alpha^2}) ; \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2} \quad \text{--- (a)}$$

$$= -\alpha \pm j\omega_d$$

from (a)

$$\omega_0 = \sqrt{\omega_d^2 + \alpha^2} \quad \text{--- (3)} ; \quad \omega_0 : \text{resonance freq.}$$

for parallel RLC.

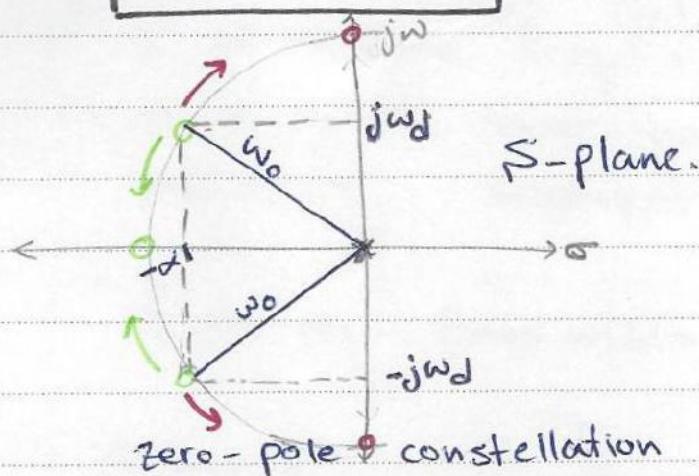

if ω_0 is constant & :

$$1. \sigma = 0, \alpha = 0$$

$$\therefore j\omega_0 = j\omega_d$$

$$2. j\omega_d \rightarrow 0$$


$$\omega_0 = \alpha$$

* Voltage response:-

$$\vec{V}(s) = \vec{I}(s) \vec{Z}(s)$$

$$\therefore \vec{Z}(s) = \frac{s/c}{(s + \alpha - j\omega_d)(s + \alpha + j\omega_d)} \leftarrow \vec{Y}(s)$$

$$* |\vec{V}(j\omega)| = |\vec{I}(j\omega)| \cdot |\vec{Z}(j\omega)|$$

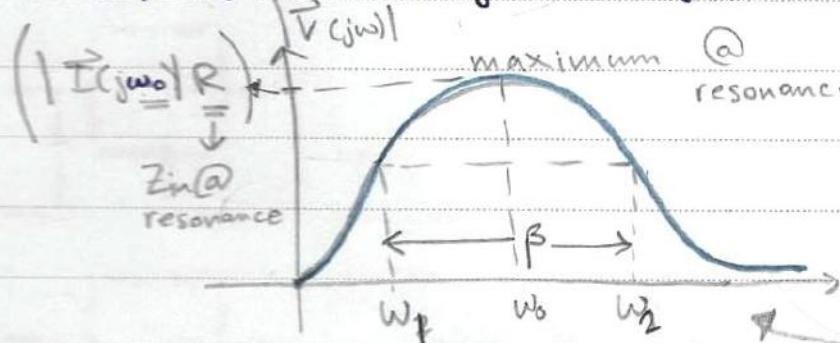

Sketch for the frequency, in the -ve part it must satisfy the even symmetry.

* calculate power @ $\omega = \omega_0$?

$$P(\omega_0) = |\vec{I}(j\omega_0)|^2 R$$

this CKT is a "Band pass filter", & ω_0 is called "center freq.".

if P at certain freq. $\stackrel{(w_1), (w_2)}{=} \frac{1}{2}$ maximum P (at resonance)
 w_1 is called lower half power frequency.
 w_2 " " \approx ~~high upper~~ " " " "

& $w_2 - w_1$ = Band width (β)

@ Resonance

$$|\vec{V}(j\omega_0)| = |\vec{I}(j\omega_0)| \cdot R$$

$$\vec{I}_L(j\omega_0) = \frac{\vec{V}(j\omega_0)}{j\omega_0 L} \leftarrow \vec{V}_L = \vec{V}_R = \vec{V}_C$$

$$I_L(j\omega_0) = \frac{\vec{I}(j\omega_0) R}{j\omega_0 L} \sim @$$

$$I_C(j\omega_0) = \vec{V}(j\omega_0) (j\omega_0 C)$$

$$= j\omega_0 R C \vec{I}(j\omega_0) \sim @$$

→ but, we know that $\omega_0 L = \frac{1}{\omega_0 C}$... from ①
from ②

$$\vec{I}_L(j\omega_0) = -j\vec{I}(j\omega_0) R (\omega_0 C) \quad \text{... ②'}$$

from ③



$$\vec{I}_C(j\omega_0) = j\vec{I}(j\omega_0) R C \omega_0 \quad \text{... ③'}$$

$$\begin{aligned} i. \quad I_C(j\omega_0) &= -\vec{I}_L(j\omega_0) * \\ &= j\omega_0 R C \vec{I}(j\omega_0) \end{aligned}$$

$$\therefore \vec{I}_{LC} = \vec{I}_L + \vec{I}_C = 0 \quad @ \text{resonance}$$


$$|\vec{I}_L(j\omega_0)| = |\vec{I}_C(j\omega_0)| = \omega_0 R C |\vec{I}(j\omega_0)| *$$

Quality Factor:

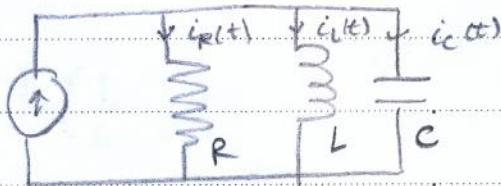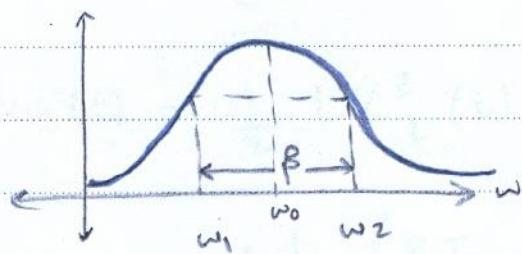

as Q increases : Sharpness ↑ , Bandwidth ↓ = freq. selectivity

Quality (δ, ξ)
Practical
inductor

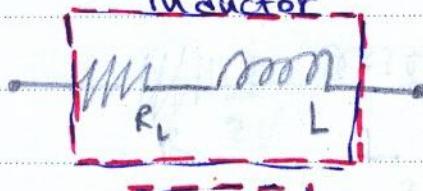

$$Q \rightarrow \infty$$

$R_L \rightarrow 0$ (pure inductance)

تجدد إيجابي

$$Q \rightarrow \infty$$

$R_C \rightarrow \infty$ (pure capacitance)

In general:

$$Q = 2\pi \times \frac{\text{maximum Energy stored in L & C}}{\text{total Energy lost per period (in R)}}$$

power

$$= 2\pi \frac{[W_L(t) + W_C(t)]_{\max} \dots @ \text{any freq.}}{P_R \frac{T}{\text{period}}} \dots \textcircled{1}$$

Q_0 : Quality factor at $\omega = \omega_0$ (resonance).

let $i(t) = I_m \cos(\omega_0 t)$ @ resonance

$$v(t) = R i(t) \quad \approx \text{(pure R)}$$

$$= R I_m \cos(\omega_0 t)$$

\vec{I} & \vec{V} are in-phase.

$$W_c(t) = \frac{1}{2} C V^2(t) = \frac{I_m^2 R^2 C}{2} \cos^2(\omega_0 t)$$

$$W_L(t) = \frac{1}{2} L i_L^2(t) = \frac{1}{2} L \left(\frac{1}{L} \int v(t) dt \right)^2$$

$$= \frac{1}{2L} \left(\frac{R I_m}{\omega_0} \sin(\omega_0 t) \right)^2$$

$$\text{but } \omega_0^2 = \frac{1}{LC}$$

$$= \frac{1}{2L} R^2 I_m^2 K_C \sin^2(\omega_0 t)$$

$$W_L(t) = \frac{1}{2} R^2 I_m^2 C \sin^2(\omega_0 t)$$

back to ①

$$\begin{aligned} & [W_c(t) + W_L(t)]_{\max} \rightarrow 1 \\ & = \frac{I_m^2 R^2 C}{2} (\cos^2(\omega_0 t) + \sin^2(\omega_0 t)) \\ & = \frac{I_m^2 R^2 C}{2} \text{ constant!} \quad \square \end{aligned}$$

$$P_R = \frac{1}{2} I_m^2 R$$

$$P_{RT} = \frac{1}{2} I_m^2 R \cdot \frac{1}{f_0} \quad \square$$

∴ plug $\square a$ & $\square b$ in ①

$$Q_0 = 2\pi \cdot \frac{I_m^2 R^2 C / 2}{I_m^2 R / 2f_0} = 2\pi f_0 R C = \omega_0 R C$$

$$Q_0 = \omega_0 R C$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q_0 = \omega_0 R C = \frac{L R C}{\sqrt{LC}} = R \sqrt{\frac{C}{L}}$$

$$\text{or } Q_0 = \frac{R}{|X_C(\omega_0)|} = \frac{R}{1/\omega_0 C} \text{ or } \frac{R}{\omega_0 L} = \frac{R}{|X_L(\omega_0)|}$$

\downarrow

$$\text{Im} \left\{ \frac{1}{Z} \right\} = \frac{1}{R j X} = \frac{1}{\frac{R}{\omega_0 C}} = \frac{\omega_0 C}{R} @ \text{resonance.}$$

$$\vec{I}_c(\omega_0) = -\vec{I}_L(\omega_0) = j\omega_0 R C \vec{I}(\omega_0)$$

from before

$$= j Q_0 \vec{I}(\omega_0)$$

* if $Q_0 > 1 \Rightarrow$ it's a current amplifier

$$\alpha = \frac{1}{ZRC}$$

; exponential damping coefficient.

$$= \frac{1}{Z(Q_0/\omega_0 C) C}$$

$$\alpha = \frac{\omega_0}{Z Q_0}$$

$$\omega_d = \sqrt{\omega^2 - \alpha^2}$$

$$= \sqrt{\omega_0^2 - \frac{\omega_0^2}{4Q_0^2}}$$

$$\omega_d = \omega_0 \sqrt{1 - \left(\frac{1}{2Q_0}\right)^2}$$

* Damping factor :-

$$Y(s) = C \frac{s^2 + s/\tau_C + 1/LC}{s}$$

$$= C \frac{(s + \alpha - j\omega_d)(s + \alpha + j\omega_d)}{s}$$

also

$$= C \frac{(s^2 + 2\alpha s + \omega_0^2)}{s}$$

$$s^2 + 2\alpha s + \omega_0^2$$

$$\hookrightarrow s^2 + 2\zeta \omega_0 s + \omega_0^2$$

ζ

ζ : Damping factor [dimension less]


$$\zeta = \frac{\alpha}{\omega_0} = \frac{1}{2Q_0}$$

$$\frac{\alpha}{\omega_0} = \frac{\omega_0/2Q_0}{\omega_0} = 1/2Q_0$$

$$\text{back to } \omega_d = \omega_0 \sqrt{1 - \left(\frac{1}{2Q_0}\right)^2}$$

$$\omega_d = \omega_0 \sqrt{1 - (\zeta)^2}$$

Q_0 , α , Z & complex frequency:

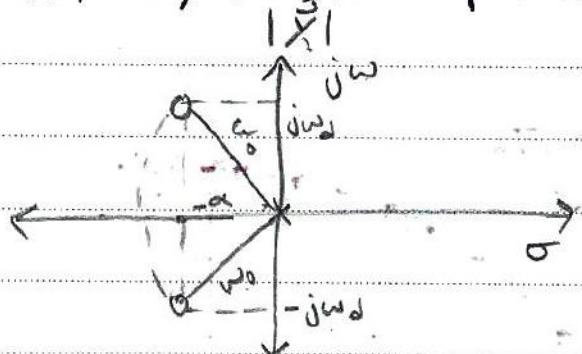


$$\alpha = 0$$

$$\omega_d = \omega_0$$

$$Q_0 = \infty$$

$$R = \infty$$

parallel

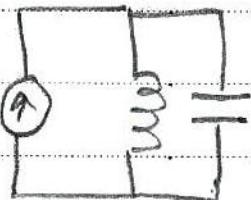

حالات
في الواقع!

when $\omega_d = 0$

$$(\alpha) = \omega_0$$

$$\rightarrow \left(\frac{\omega_0}{2Q_0} \right) = \omega_0 \quad \xrightarrow{\text{also}} \quad \alpha = \omega_0$$

$$\frac{1}{2RC} = \frac{1}{\sqrt{LC}}$$

$$\therefore Q_0 = \frac{1}{2}$$

$$R = \frac{\sqrt{LC}}{2C}$$

$$R = \frac{1}{2} \sqrt{\frac{L}{C}}$$

Ex:- A parallel resonant ckt is composed of elements

$$R = 8 \text{ k}\Omega, L = 50 \text{ mH}, C = 80 \text{ nF}$$

find:-

$$1) \omega_0 = \frac{1}{\sqrt{LC}} = 15.811 \text{ k rad/sec.}$$

$$2) Q_0 = \omega_0 RC = 10.119 ; \text{ very high } Q_0$$

$$3) \omega_d = \omega_0 \sqrt{1 - \left(\frac{1}{2Q_0} \right)^2} = \omega_0 \sqrt{1 - Z^2}$$

$$= (15.791) \text{ k rad/sec.}$$

$$4) \alpha = \frac{\omega_0}{2Q_0} = 781 \text{ Np/sec.}$$

$$5) Z = \frac{\omega_0}{\alpha} = 1/(2Q_0) = 0.0494$$


ex 2 :- find the components R, L, C for a parallel resonant CKT ; $\omega_0 = 1000 \text{ rad/sec}$.

$$\omega_d = 998 \text{ rad/sec. } \vec{Y}(\omega_0) = 1 \text{ mS}$$

@ resonance

Sol:-
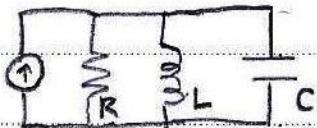
$$\vec{Y}_{in} = \frac{1}{R} \text{ at resonance}$$



$$(1 \times 10^3) \text{ S} = \frac{1}{R}$$

$$\rightarrow R = (1) \text{ k}\Omega$$

$$\omega_d = \omega_0 \sqrt{1 - \left(\frac{L}{2Q_0}\right)^2} \Rightarrow \left(\frac{\omega_d}{\omega_0}\right)^2 = 1 - \left(\frac{1}{2Q_0}\right)^2$$

$$\rightarrow Q_0 = \frac{1}{2\sqrt{1 - \left(\frac{\omega_d}{\omega_0}\right)^2}} = 7.909$$


$$Q_0 = \omega_0 R C$$

$$\rightarrow C = \frac{Q_0}{\omega_0 R} = 7.91 \mu F$$

$$\omega_0^2 = \frac{1}{LC}$$

$$L = \frac{1}{\omega_0^2 C} = 126.4 \text{ mH} \quad \approx$$

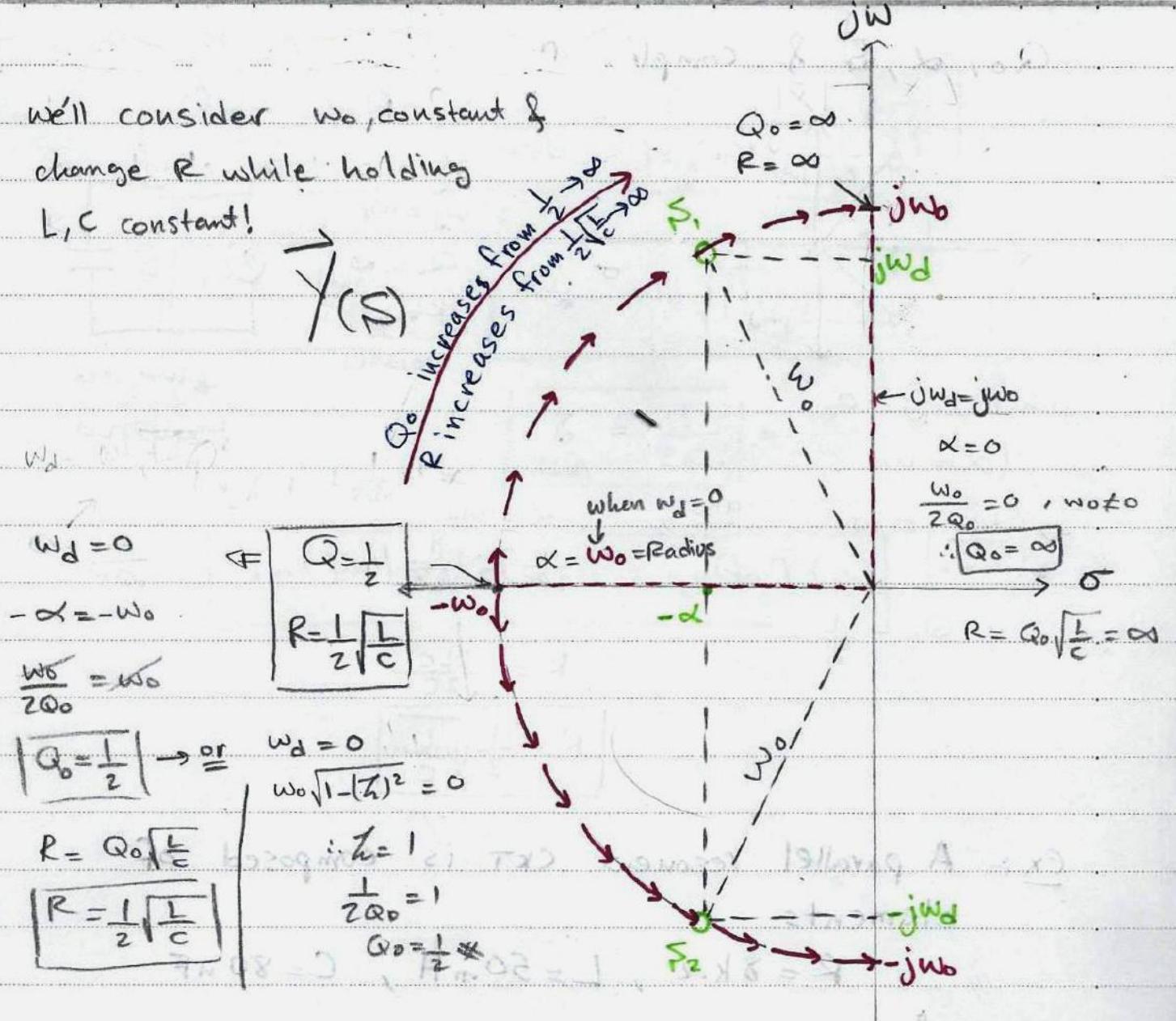We'll consider ω_0 constant & change R while holding L, C constant!



$$Y(s) = \frac{C}{s} (s + \alpha - jw_d)(s + \alpha + jw_d)$$

$$\text{Zeros at: } s = -\alpha \pm jw_d$$

Pole-Zero Constellation for parallel resonant CKTs


+Problem 15 page 683:

$$L = (1 \text{ m})H$$

$$\alpha = (50) \text{ s}^{-1}$$

$$\omega_d = (5000) \text{ rad/sec}$$

Find ω_0 & Z_{in} at ω_0

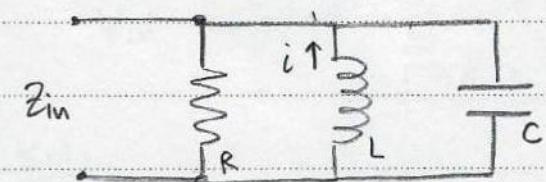

Sol:-

$$* \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$5000 = \sqrt{\omega_0^2 - 2500}$$

$$25 \times 10^6 = \omega_0^2 - 2500$$

$$\boxed{\omega_0 = (5000) \text{ rad/s}}$$

$$* \alpha = \frac{\omega_0}{2Q_0} \rightarrow Q_0 = \frac{\omega_0}{2\alpha}$$

$$\therefore Q_0 = \frac{5000}{2 \times 50} = 50$$


$$* Q_0 = \frac{R}{\omega_0 L} \rightarrow R = Q_0 \omega_0 L$$

$$\therefore R = 50(5000)(1 \times 10^{-3}) = 250 \Omega$$

$$\boxed{Z_{in}(\omega_0) = R = 250 \Omega}$$

$$++ Q_0 = \omega_0 R C \rightarrow C = \frac{Q_0}{\omega_0 R} = \frac{50}{5000(250)} = 40 \mu F$$

Problem 13:

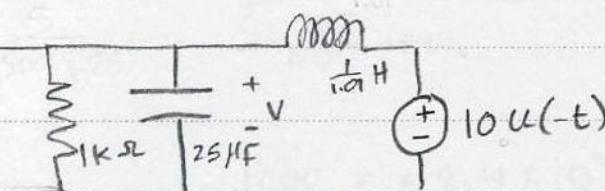

determine the resonant freq.
at $t > 0$.


Sol:-

at $t > 0$, source is short circuited.

$$\therefore \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(1.01)(25 \times 10^{-6})}} = 199.007 \text{ rad/s}$$

+ Problem 11 :-

find Y_{in} & ω_0 , $Z_{in}(j\omega)$

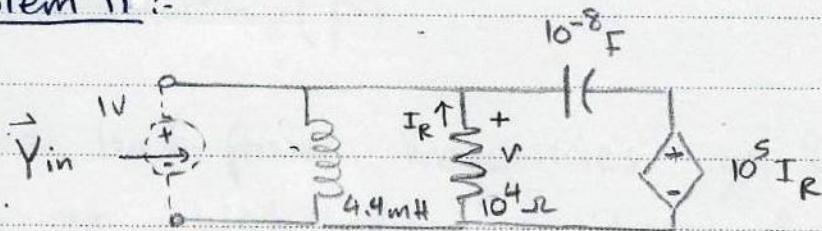

Sol:-

$I_R = \frac{V}{R} \Rightarrow$ we add a voltage source of (1V)

$$\therefore I_R = -\frac{1}{10^4} = -10^{-4} \text{ A}$$

$$Y_{in} = \frac{I_{in}}{V} = \frac{I_{in}}{1} = \left(\frac{1}{4.4 \times 10^{-3} s} \right) + \left(\frac{-1}{10^4} \right) + \left(1 + 10^5 \times \frac{1}{10^4} \right) 10^{-8} s$$

$$= \frac{10^4 + 4.4 \times 10^{-3} s + 484 \times 10^{-8} s^2}{44 s}$$

$$Y_{in}(j\omega) = \frac{1000 - 48.4 \times 10^{-8} \omega^2 + j4.4 \times 10^{-4} \omega}{j4.4 \omega}$$

at $\omega = \omega_0$, imaginary part = 0

$$\therefore \frac{1000 - 48.4 \times 10^{-8} \omega_0^2}{j4.4 \omega_0} = 0$$

$$1000 = 48.4 \times 10^{-8} \omega_0^3$$

$$\omega_0 = 45.45 \text{ rad/s}$$

$$Z_{in}(j\omega_0) = \frac{1}{Y(j\omega_0)} \dots$$


Band width (β)

→ half power frequencies w_1 & w_2 are frequencies at which the magnitude of the input admittance of a parallel resonant ckt is greater than the magnitude at resonance by a factor = $\sqrt{2}$
also the voltage response & the impedance at w_1, w_2 are $(\frac{1}{\sqrt{2}} / 0.707)$ times their maximum value

(@ resonance).

$$\bullet \boxed{\beta = w_2 - w_1}$$

$\frac{1}{2}$ -power
Band width

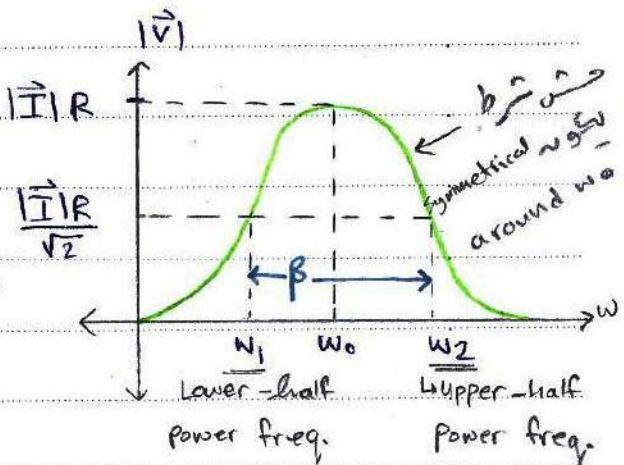

* Exact values of w_1 & w_2 :

$$\vec{Y}(jw) = \frac{1}{R} + j \left(\omega_c - \frac{1}{\omega L} \right) \quad \text{for parallel ckt}$$

$$= \frac{1}{R} + j \frac{1}{R} \left(\frac{\omega_c R w_0}{w_0} - \frac{R w_0}{w_0 \cdot \omega L} \right)$$

$$= \frac{1}{R} + j \frac{1}{R} \left(\frac{\omega_c Q_0}{w_0} - \frac{w_0 Q_0}{\omega} \right)$$

$$\boxed{\vec{Y}(jw) = \frac{1}{R} \left[1 + j Q_0 \left(\frac{\omega}{w_0} - \frac{w_0}{\omega} \right) \right]} \quad \text{...④}$$

@ w_1, w_2 :-

$$|\vec{Y}(jw_1)| = |\vec{Y}(jw_2)| = \sqrt{2} \left(\frac{1}{R} \right)$$

from $\textcircled{*}$:-

$$|\vec{Y}(j\omega)| = \frac{1}{R} \sqrt{1 + [Q_o \left(\frac{\omega - \omega_0}{\omega_0} \right)]^2}$$

$$|\vec{Y}(jw_1)| = \frac{\sqrt{2}}{R} \quad |\vec{Y}(jw_2)| = \frac{\sqrt{2}}{R}$$

$$\frac{1}{R} \sqrt{1 + [Q_o \left(\frac{\omega_1 - \omega_0}{\omega_0} \right)]^2} = \frac{\sqrt{2}}{R}$$

$$\frac{1}{R} \sqrt{1 + [Q_o \left(\frac{\omega_2 - \omega_0}{\omega_0} \right)]^2} = \frac{\sqrt{2}}{R}$$

$$Q_o \left(\frac{w_1}{w_0} - \frac{w_0}{w_1} \right) = -1$$

$$Q_o \left(\frac{w_2}{w_0} - \frac{w_0}{w_2} \right) = 1$$

$$w_2 > w_1$$

$$w_{1,2} = w_0 \left[\sqrt{1 + \left(\frac{1}{2Q_o} \right)^2} \pm \frac{1}{2Q_o} \right]$$

$$= w_0 \left[\sqrt{1 + \frac{1}{4Q_o^2}} \pm \frac{1}{2Q_o} \right]$$

$$\beta = w_2 - w_1 = \frac{w_0}{Q_o} = \frac{w_0}{w_0 RC} = \boxed{\frac{1}{RC}} = \boxed{2\alpha}$$

$$w_0^2 = w_1 w_2$$

$$w_0 = \sqrt{w_1 w_2}$$

as Q_o increases,
 β decreases.

* Approximations for high Q CKTs:-

$$\boxed{Q_0 > 5}$$

higher Q leads to narrower bandwidth & sharper response curve!

zeros:- $s = -\alpha \pm j\omega_d$

$$= -\frac{1}{2Q_0} \pm j\sqrt{1-\zeta^2}$$

$$= -0.1\omega_0 \pm j0.99\omega_0 \quad \text{at } Q_0=5$$

$$\boxed{0.9\omega_0 \leq \omega \leq 1.1\omega_0}$$

النطاق المقصود هو
النطاق المزدوج

$$\alpha = \frac{\omega_0}{2Q_0} \quad \left\{ \begin{array}{l} \text{no change} \end{array} \right.$$

$$\beta = 2\alpha$$

$$\omega_{1,2} = \omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0} \right)^2} \mp \frac{1}{2Q_0} \right]$$

$(2Q_0)^2 \rightarrow \infty$ نسبية

$$\approx \omega_0 \left(1 \mp \frac{1}{2Q_0} \right)$$

$$\boxed{\omega_{1,2} \approx \omega_0 \pm \frac{1}{2}\beta}$$

means that the response is symmetrical around $\omega = \omega_0$ ①

$$\boxed{\omega_0 \approx \frac{1}{2}(\omega_1 + \omega_2)}$$

the arithmetic mean of ω_1, ω_2
(avg freq)

the locations of s_1 & s_2 can be approximated :-


$$s_{1,2} = -\alpha \pm j\omega_d$$

$$s_{1,2} \approx -\frac{1}{2}\beta \pm j\omega_0$$

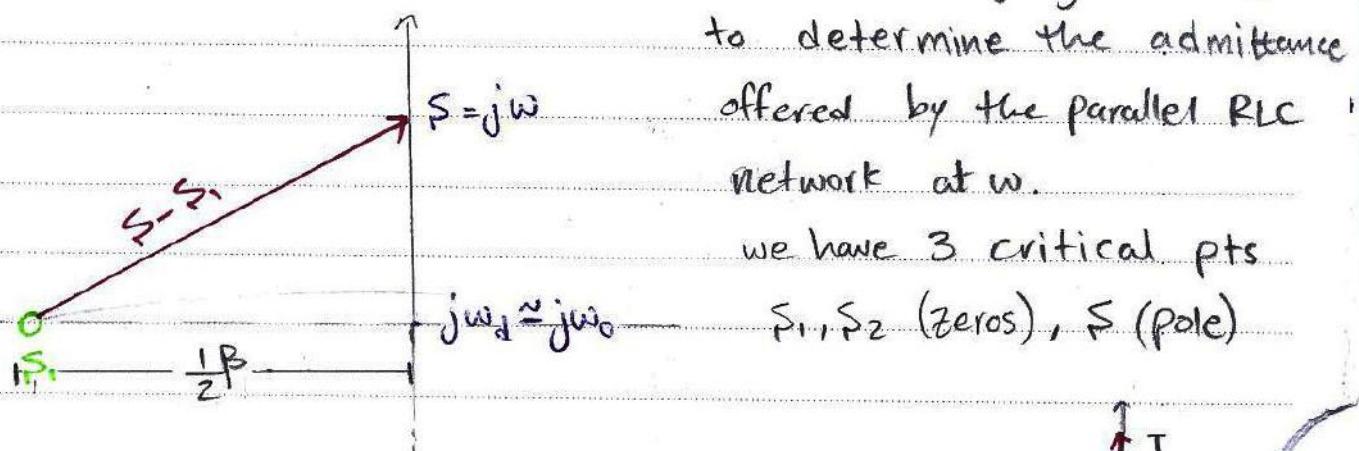f. from ① :-

$$\omega_{1,2} \approx \omega_0 \mp \frac{1}{2}\beta$$

now, $\vec{Y}(s) \approx ?$ where (w) is in the neighborhood of ω_0 .
 → take a test point $s = jw$ slightly above $j\omega_0$




$$\vec{Y} = C \frac{(s - s_1)(s - s_2)}{(s - 0)} \quad \textcircled{*}$$

$$\rightarrow s - s_1 = \frac{1}{2}\beta + j(\omega - \omega_0)$$

$$\rightarrow s - s_2 \approx j2\omega_0$$

$$\rightarrow s - 0 = jw$$

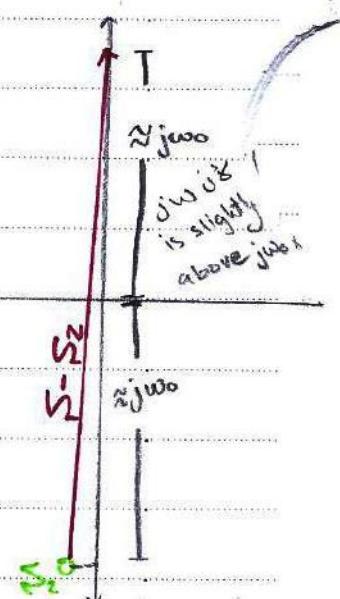

Plug in ④

$$\vec{Y}(s) \approx C \frac{(j\omega_0)(s - s_1)}{j\omega_0} = 2C(s - s_1)$$

$$\vec{Y}(s) \approx 2C \left[\frac{1}{2}\beta + j(\omega - \omega_0) \right]$$

$$\approx jC \cdot \frac{1}{2}\beta \left[1 + j \frac{(\omega - \omega_0)}{\frac{1}{2}\beta} \right]$$

$$\beta = \frac{1}{RC}$$

$$\vec{Y}(s) = \frac{1}{R} (1 + jN)$$

$$\vec{Y}(j\omega) = \frac{1}{R} \sqrt{1+N^2} \times \underline{\tan^{-1}(N)}$$

$$N = \frac{\omega - \omega_0}{\frac{1}{2}\beta} ; \text{ number of half-Bandwidths off resonance.}$$

- Values of N :-

@ ω_2 : $\omega_2 = \omega_0 + \frac{1}{2}\beta$

$$N = \frac{\omega_0 + \frac{1}{2}\beta - \omega_0}{\frac{1}{2}\beta} = 1$$

@ ω_1 : $\omega_1 = \omega_0 - \frac{1}{2}\beta$

$$N = \frac{\omega_0 - \frac{1}{2}\beta - \omega_0}{\frac{1}{2}\beta} = -1$$

Summary:-

Parallel resonant CKTs:-

- Resonance is the condition existing in any physical system, when a response of a max. amplitude is produced.
- There must be at least one capacitor & one inductor in a network in order to be able to reach resonance.
- Resonance condition can be achieved by adjusting ω or $1/C$, here we'll focus on ω as a variable, where ω_0 is the resonant frequency.

- At Resonance:-

$Z_{in} = R$	max. value of impedance	$\vec{I} \perp \vec{f} \perp \vec{V}$ are in-phase at ω_0
$\vec{Y}_{in} = 1/R$	minimum $\approx \infty$ admittance	

$\omega_0 = \frac{1}{\sqrt{LC}}$; resonant freq. [rad/s]	$f_0 = \frac{1}{2\pi\sqrt{LC}}$; [Hz]
----------------------------------	-----------------------------	----------------------------------------

$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$; Natural resonant frequency [rad/s]
-------------------------------------------	-----------------------------------------

$\alpha = \frac{1}{2RC}$; exponential damping coefficient [Np/s]
--------------------------	---------------------------------------------

$ I(j\omega_0) = I_C(j\omega_0) = \omega_0 RC I(j\omega_0) $

- Quality factor = $\frac{2\pi \text{ max. E stored in L/C}}{\text{max. E lost in R per period}}$

$$Q_0 = \omega_0 RC = \frac{R}{\omega_0 L} = \frac{R}{|X_{L/C}(j\omega_0)|} = R \sqrt{\frac{C}{L}}$$

$\therefore Q_0 \propto \omega_0$ Resonance $\propto \omega_0$ $\Rightarrow *$

$$\omega_d = \omega_0 \sqrt{1 - \left(\frac{1}{2Q_0}\right)^2} = \omega_0 \sqrt{1 - (\zeta)^2}$$

$$\zeta = \frac{1}{2Q_0} = \frac{\alpha}{\omega_0} ; \text{ damping factor}$$

[dimensionless]

$$\alpha = \frac{\omega_0}{2Q_0}$$

$$|I_C(j\omega_0)| = |I_L(j\omega_0)| = jQ_0 |\vec{I}(j\omega_0)|$$

- Bandwidth (β) & half-power frequencies (ω_1, ω_2)

$$\beta = 2\alpha = \frac{1}{RC} = \omega_2 - \omega_1 = \frac{\omega_0}{Q_0}$$

exact values of ω_1, ω_2

$$\omega_{1,2} = \omega_0 \left[\sqrt{1 + (\zeta)^2} \pm \zeta \right]$$

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

approximations:-

when $Q_0 \gg 5$

& $0.9\omega_0 \leq \omega \leq 1.1\omega_0$

$$\omega_{1,2} \approx \omega_0 \pm \frac{1}{2} \beta$$

$$\omega_0 \approx \frac{\omega_1 + \omega_2}{2}$$

exact:

$$Y(j\omega) = \frac{1}{R} \left[1 + jQ_0 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right]$$

approximation:-

$$\tilde{Y}(j\omega) = \frac{1}{R} (1 + jN) = \frac{1}{R} \sqrt{1 + N^2}$$

$$N = \frac{\omega - \omega_0}{\frac{1}{2}\beta}$$

* of half-Band widths off resonance

Ex1: determine the approximate value of $\tilde{Y}(\xi)$ for parallel RLC CKT, $R = 40\text{ k}\Omega$, $L = 1\text{ H}$, $C = \frac{1}{64}\text{ }\mu\text{F}$ at $\omega = 8.2\text{ K rad/s}$

Sol:- First we find ω_0 & Q_0 to check approximation conditions

$$\omega_0 = \frac{1}{\sqrt{LC}} = 8\text{ K rad/s}$$

$$Q_0 = \omega_0 RC = 5$$

$$\omega = 1.025 \omega_0 \quad \left[\begin{array}{l} Q_0 \geq 5 \\ 0.9\omega_0 < \omega < 1.1\omega_0 \end{array} \right] \quad \begin{array}{l} \checkmark \text{ we can use} \\ \text{approximations} \end{array}$$

$$\beta = \frac{\omega_0}{Q_0} = 1.6\text{ K rad/s}$$


$$N = \frac{\omega - \omega_0}{\frac{1}{2}\beta} = \frac{(8.2 - 8)\text{ K}}{\frac{1}{2}(1.6)\text{ K}} = 0.25$$

$$\therefore |\tilde{Y}| = \frac{1}{R} \sqrt{1 + N^2} = 25\text{ M} \sqrt{1 + (0.25)^2} = 25.77\text{ }\mu\text{s}$$

$$\angle \tilde{Y} = \tan^{-1}(N) = 14.03^\circ$$


$$\therefore \tilde{Y} = 25.77 \angle 14.03^\circ \text{ M}\xi$$

• Series Resonance:-

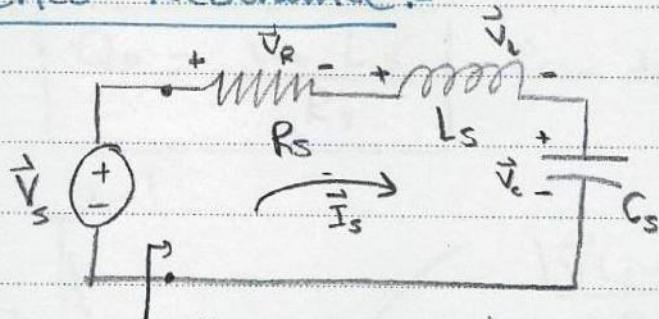

$Z_{in} (j\omega)$; dealing with Z_{in} in series is much easier than \vec{V}

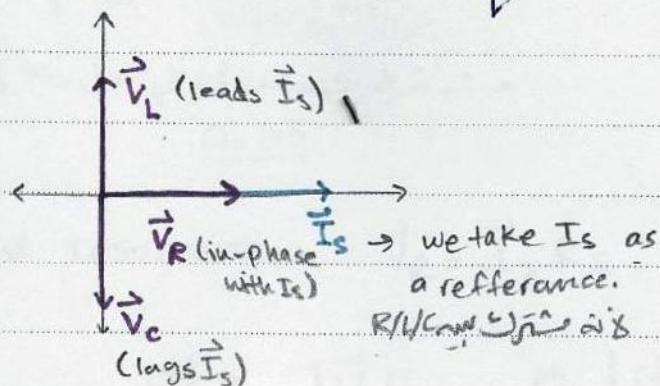Since Parallel & series RLC CKTs are dual circuit
then, we can apply duality concepts to find
Series resonance equations.



at resonance:-

$$\boxed{\begin{aligned}\vec{V}_s &= \vec{V}_R \\ \vec{V}_c &= -\vec{V}_L\end{aligned}}$$

$$\vec{Z}_{in} (j\omega) = R_s + j(\omega L_s - \frac{1}{\omega C_s}) \quad \dots \textcircled{1}$$

$$\text{at resonance } \text{Im} \{ \vec{Z}_{in} \} = 0 \quad \dots \textcircled{2}$$

$$\therefore \boxed{\vec{Z}_{in} (j\omega_0) = R_s}$$


from $\textcircled{1}$ & $\textcircled{2}$ at ω_0 :-

$$\omega_0 L_s = \frac{1}{\omega_0 C_s}$$

$$\boxed{\omega_0 = \frac{1}{\sqrt{L_s C_s}}} \quad \text{Parallel case}$$

$$Q_0 = \frac{\omega_0 L_s}{R_s}$$

from duality

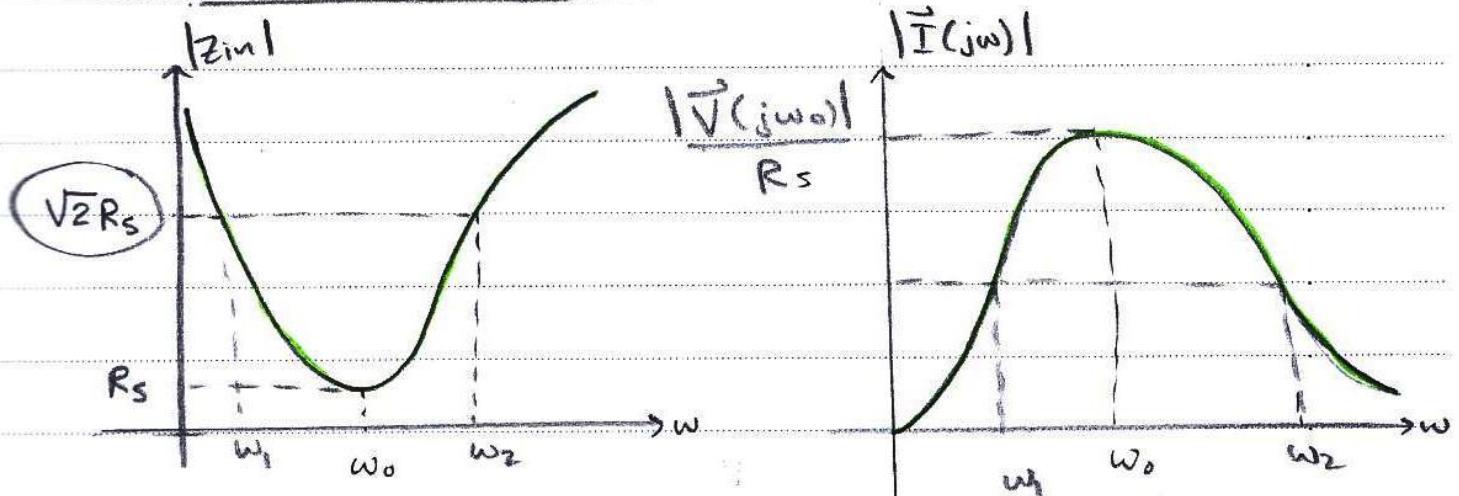

مقدار تردد ينبع فيه عاشر حول ω_0 إذا كان

$$Q_0 \geq 5$$

at resonance:- $\vec{V}_R = \vec{I}_s R_s = \vec{V}_s$

$$|\vec{V}_c| = |\vec{V}_L| = Q_0 |\vec{V}_s(j\omega_0)|$$

- if $Q_0 > 1 \rightarrow$ Voltage amplifier

exact: $\omega_{1,2} = \omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0}\right)^2} \pm \frac{1}{2Q_0} \right]$

$$\beta = \omega_2 - \omega_1 = \frac{\omega_0}{Q_0} = 2\alpha$$

$$\alpha = \frac{\omega_0}{2Q_0} = \frac{R_s}{2L_s}$$

duality!

in parallel
 $\alpha = \frac{1}{2RC}$

$$\begin{aligned} \omega_d &= \sqrt{\omega_0^2 - \alpha^2} \\ &= \omega_0 \sqrt{1 - \left(\frac{1}{2Q_0}\right)^2} \end{aligned}$$

$$\omega_0 = \sqrt{\omega_1 \omega_2} \quad \text{same}$$

$$\begin{array}{l} C \leftrightarrow L \\ R \leftrightarrow \frac{1}{L} \end{array}$$

approximation: $Q_0 \geq 5$ & $0.9w_0 \leq w \leq 1.1w_0$

$$- w_d \approx w_0$$

$$- w_{1,2} \approx w_0 \pm \frac{1}{2}\beta$$


$$- w_0 \approx \frac{1}{2}(w_1 + w_2)$$

Same α^2
parallel

$$\vec{Z}_{in}(jw) \approx R(1+jN) = R\sqrt{1+N^2} \times \tan^{-1}(N)$$

$$N = \frac{w - w_0}{\frac{1}{2}\beta}$$

ex:

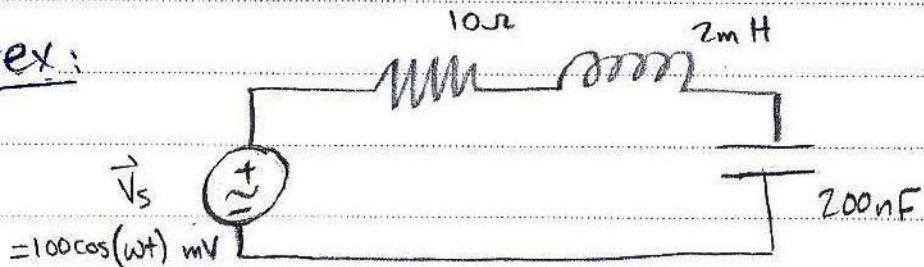

find $\vec{Z}_{in}(jw)$ & \vec{I} at $w = 48$ K rad/s b)
Exact & approx

Sol: a) check for the approximation conditions:-

$$w_0 = \frac{1}{\sqrt{LC_s}} = 50 \text{ K rad/s}$$

$$Q_0 = \frac{w_0 L_s}{R_s} = 10 \geq 5 \quad \checkmark$$

$$w = 0.96 w_0 \rightarrow 0.9w_0 \leq w \leq 1.1w_0 \quad \checkmark$$

use approx $\vec{Z}_{in} \approx R \sqrt{1+N^2} \times \tan^{-1} N$

$$N = \frac{w - w_0}{\frac{1}{2}\beta} = \frac{48 - 50}{\frac{1}{2}(\frac{50K}{10})} = -0.8$$

$$\vec{Z}_{in} = 12.81 \times -38.6^\circ$$

$$|\vec{I}(jw)| = \frac{100m}{12.81} = 7.806 \text{ mA}$$

b) exact:-

$$Z_{\text{exact}} = 10 + j(48)(2) - \frac{j}{48 \times 10^3 (200) \times 10^9} = 12.9 \angle -39^\circ$$

$$|I_{\text{exact}}| = \frac{|V|}{|Z_{\text{exact}}|} = \frac{100 \text{ m}}{12.9} = 7.75 \text{ mA}$$

\therefore Differences between Parallel & Series:-

Parallel

$$Q_0 = \omega_0 R C$$

$$\alpha = \frac{1}{2RC}$$

$$|I_L| = |I_C| = Q_0 |I_R| \quad \xrightarrow[\text{Resonance}]{\text{at}} \quad |V_L| = |V_C| = Q_0 |V_R|$$

Series

$$Q_0 = \frac{\omega_0 L}{R}$$


$$\alpha = \frac{R}{2L}$$

* The series resonant CKT is characterized by a minimum impedance at resonance, whereas the parallel resonant CKT produces a maximum resonant impedance, the latter CKT provides inductor & capacitor currents @ resonance greater than the source current by the factor Q_0 . While series resonant CKT provides inductor & capacitor voltages at resonance greater than the voltage source by a factor of Q_0 , so, when $Q_0 > 1 \rightarrow$ series CKTs work as a voltage amplifiers.

→ if the CKT is not purely series or parallel,
what to do? & how to deal with it?

Previous RLC Parallel & series CKTs were ideal! without R_L, R_C

• Other Resonant CKTs :-

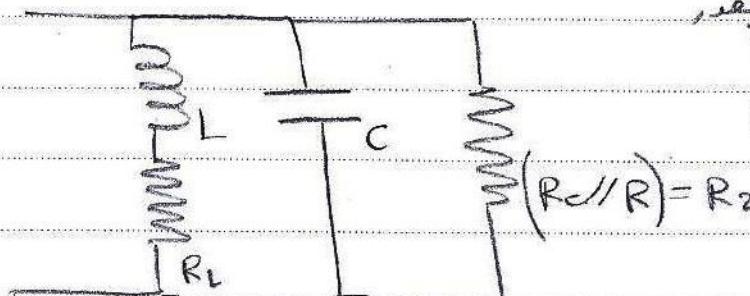

جذب الدارة هي مترافق
لـ $\omega^2 C = \omega^2 L$ ، $C = \frac{1}{\omega^2 L}$
و $\omega_0^2 = \frac{1}{L C}$

- Resistance of the inductor (R_L) is in series with L
- Capacitor (R_C) ~ ~ parallel ~ C

at Resonance:-

$$\vec{Y}(j\omega) = \frac{1}{R_2} + j\omega C + \frac{1}{R_L + j\omega L} \times \left(\frac{R_L - j\omega L}{R_L - j\omega L} \right)$$

$$= \frac{1}{R_2} + j\omega C + \frac{R_L - j\omega L}{R_L^2 + \omega^2 L^2}$$

* $\text{Im } \vec{Y}(j\omega) = 0$ at ω_0 (resonance)

* $\text{Re } \vec{Y}(j\omega) = \frac{L}{R}$

$$\text{Im } \vec{Y}(j\omega_0) = \omega_0 C - \frac{\omega_0 L}{R_L^2 + \omega_0^2 L^2} = 0$$




$$\therefore R_L^2 + \omega_0^2 L^2 = \frac{L}{C}$$

$$\therefore \omega_0^2 L^2 = \frac{L}{C} - R_L^2$$

$$\boxed{\omega_0 = \sqrt{\frac{1}{LC} - \left(\frac{R_L}{L}\right)^2}}$$

حيث $\omega_0 = \sqrt{\frac{1}{LC}}$ if $R_L = 0$ (1. لجأنا

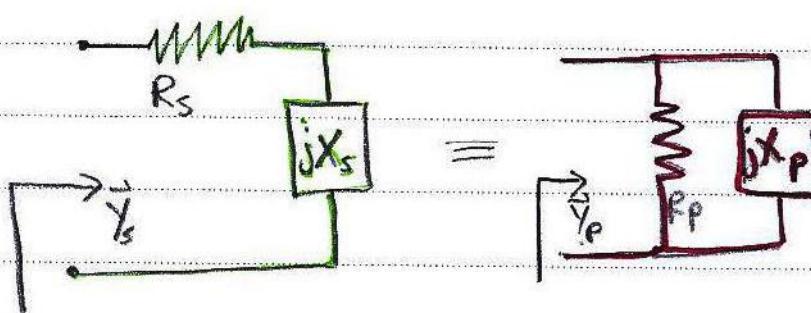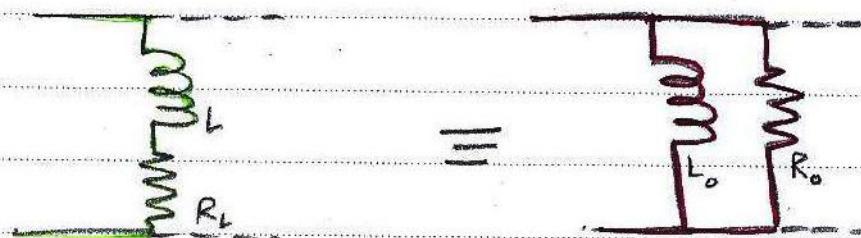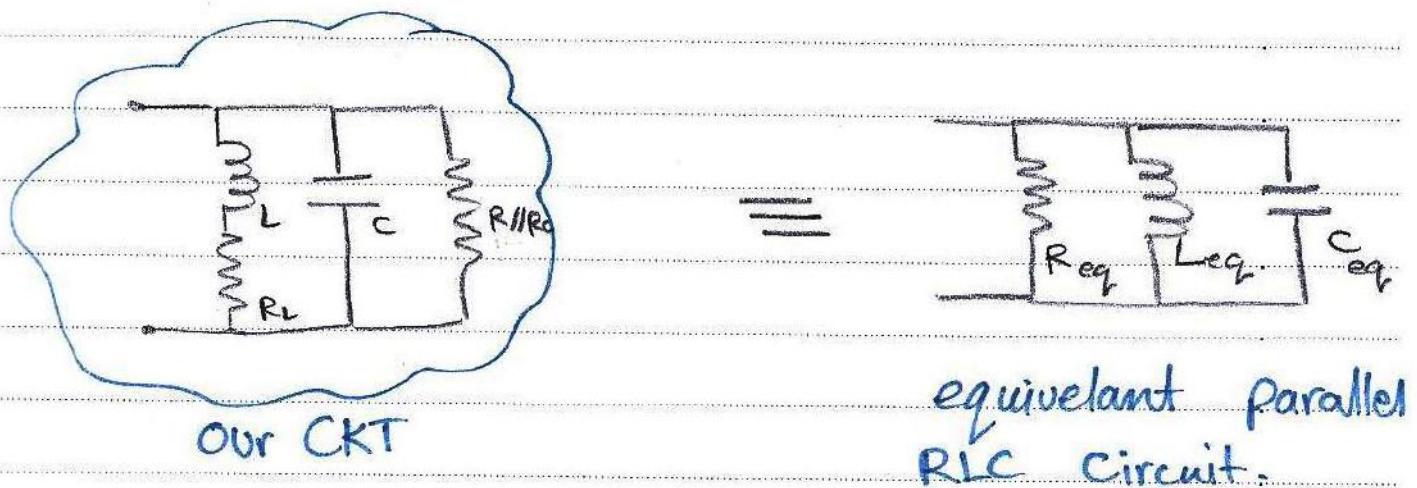actually, we won't follow the previous method each time, we have to find a way to replace the previous CKT with an equivalent parallel RLC circuit.



$$Q_s = \frac{|X_s|}{R_s}$$

$$Q_p = \frac{R_p}{|X_p|}$$

these 2 CKTs are equivalent if

$$\vec{Y}_s = \vec{Y}_p$$

$$\rightarrow \vec{Y}_s = \frac{1}{R_s + jX_s} = \frac{R_s - jX_s}{R_s^2 + X_s^2}$$

$$\rightarrow \vec{Y}_P = \frac{1}{R_P} - j \frac{1}{X_P}$$

but $\vec{Y}_S = \vec{Y}_P$

$$\therefore \boxed{\operatorname{Re}\{\vec{Y}_P\}} = \operatorname{Re}\{\vec{Y}_S\} \quad \& \quad \boxed{\operatorname{Im}\{\vec{Y}_P\}} = \operatorname{Im}\{\vec{Y}_S\}$$

$$\boxed{\frac{R_s^2 + X_s^2}{R_s} = R_p} \quad \text{... (1)}$$

$$\boxed{\frac{R_s^2 + X_s^2}{X_s} = X_p} \quad \text{... (2)}$$

divide (1) by (2) :-

$$\boxed{Q_s = Q_p / = Q}$$

- back to (1) :-

$$R_p = \frac{R_s^2 + X_s^2}{R_s} = R_s + \frac{X_s^2}{R_s}$$

5
V
Q°

$$R_p = R_s \left(1 + \frac{X_s^2}{R_s^2} \right)$$

$$\boxed{R_p = R_s (1 + Q^2)} \quad \text{... (1') } \quad s \rightarrow p$$

$$\hookrightarrow \boxed{R_s = \frac{R_p}{(1 + Q^2)}} \quad p \rightarrow s$$

- from (2) :-

$$X_p = \frac{R_s^2}{X_s} + X_s = X_s \left(1 + \frac{R_s^2}{X_s^2} \right) = X_s \left(1 + \left(\frac{1}{Q}\right)^2 \right)$$

$$\boxed{X_p = X_s \left(1 + \left(\frac{1}{Q}\right)^2 \right)} \quad \text{... (2')} \quad s \rightarrow p$$

$$\hookrightarrow \boxed{X_s = \frac{X_p}{1 + \left(\frac{1}{Q}\right)^2}} \quad s \rightarrow p$$

values

Exact


approximation $Q_0 \geq 5$

$$R_p = R_s Q^2$$

$$; R_p = R_s (1 + \frac{Q^2}{Q_0^2})$$


$$X_p = X_s$$
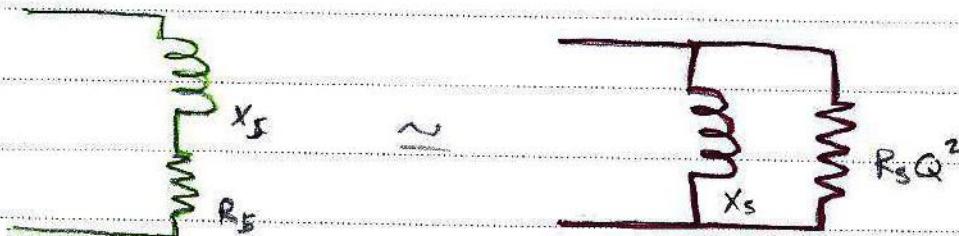
$$; X_p = X_s \left(1 + \frac{1}{Q^2}\right)$$



Ex:- at $\omega = 1000 \text{ rad/s}$, find a parallel Network that's equivalent to the series combination of $8H$ & 100Ω


Sol:-

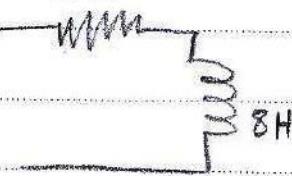

* First we have to check approximation condition!


$$Q = \frac{\omega L_s}{R_s} = \frac{1000 \times 8}{100} = 80 \gg 5$$

→ Use approx.

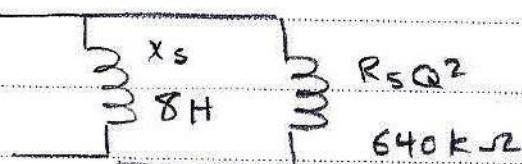


Ex 2:- find the series combination equivalent to a parallel $100k\Omega$ & $5H$ at $\omega = 1000 \text{ rad/s}$

Sol:-

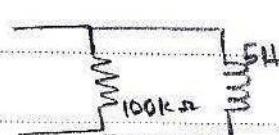

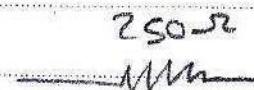
$$Q = \frac{100k}{1000 \times 5} = 20 \gg 5 \quad \xrightarrow{\text{use approx.}}$$



$$X_p = X_s = 5H$$

$$R_s = R_p / Q^2 \\ = 250 \Omega$$

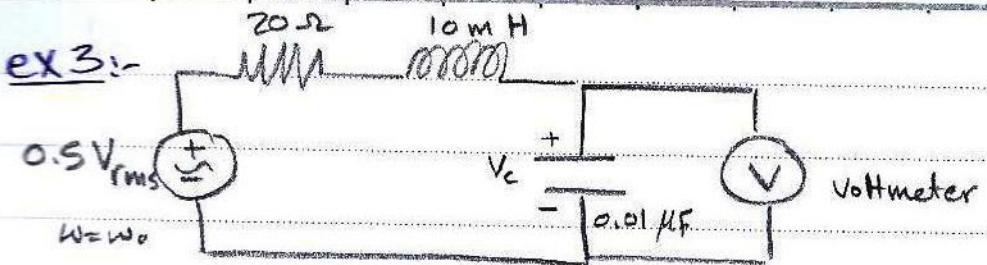

the Voltmeter has an internal impedance $= 100k\Omega$ pure R

→ Before adding \textcircled{V} :-


$$\omega_0 = \frac{1}{\sqrt{LC}} = 10^5 \text{ rad/s}$$

$$Q_0 = \frac{\omega_0 L}{R} = 50$$

$$|\vec{I}(j\omega_0)| = \frac{0.5}{20} = 25 \text{ mA}_\text{rms}$$

$$|V_c(j\omega_0)| = |\vec{V}_s| Q_0 = 0.5 \times 50 = 25 \text{ V}_\text{rms}$$

→ After adding \textcircled{V} :-

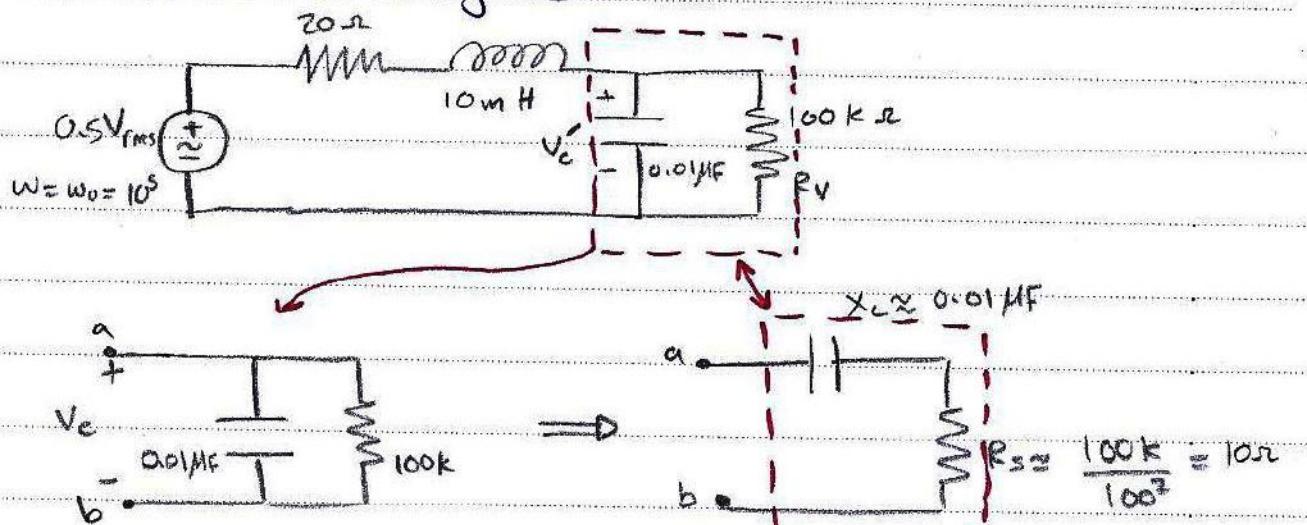


$$Q_{\text{branch}} = \frac{R_p}{X_p} = R_p(\omega C_p)$$

$$= 100k \left(10^5 + 0.01\mu \right) = 100 > 5$$

use approx.

back to the original CKT:-

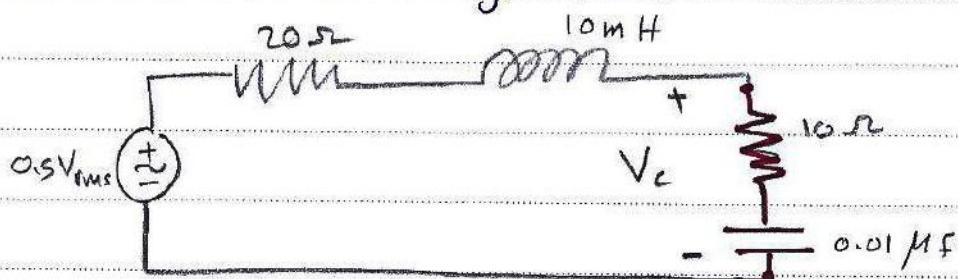

$$Q_0 \text{ new} = \frac{\omega_0 L}{R_{\text{eq}}} = \frac{10^5 \times 10 \text{ m}}{(20+10)} = 33.33$$


$$\rightarrow Q_0 \text{ old} = 50 \quad \boxed{Q_{\text{new}} = 33.33} \quad !$$

$$|V_c| = |\vec{I}| \left| 10 - \frac{1}{j(10^5 \times 0.01\mu)} \right| = \frac{0.5}{30} \times \sqrt{10^2 + \left(\frac{1}{10^3}\right)^2}$$

$$|V_c| = 16.67 \text{ V}_{\text{rms}} \quad \text{while } |V_c| = 25 \text{ V}$$

هذه الفرق في القراءات يظهر في إضافة الـ π وامثل مقاومة الـ π الأخرى!

Ex 3:

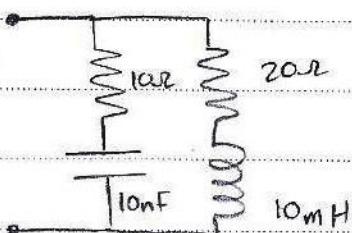

a) Find the approximated ω_0 :

$$\omega_0 = \frac{1}{\sqrt{LC}} = 100 \text{ K rad/s}$$


b) find Q_0 for the RC branch:

$$Q = \frac{|X_S|}{R_S} = \frac{1}{\omega_0 C R_S} = 100 \gg s$$


c) find Q_0 for the RL branch

$$Q_0 = \frac{|X_S|}{R_S} = \frac{\omega_0 L}{R_S} = 50 \gg s$$

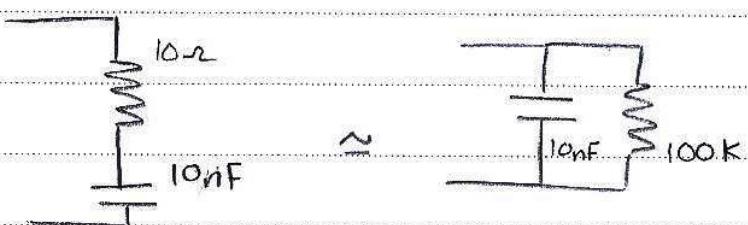
d) find the 3-elements equivalent of the original network?




$$Q = 100$$

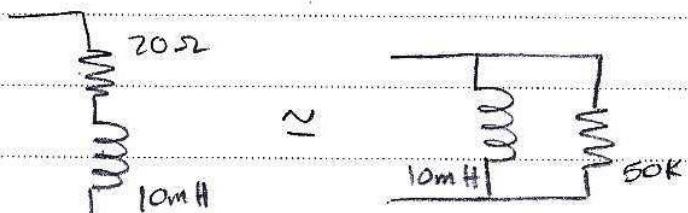

$$Q = 50$$

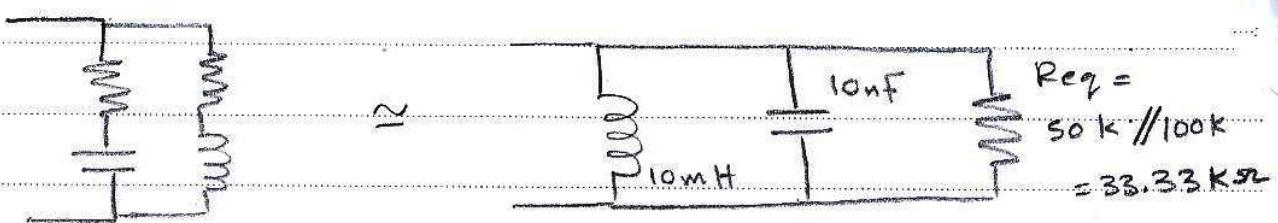


• Scaling:

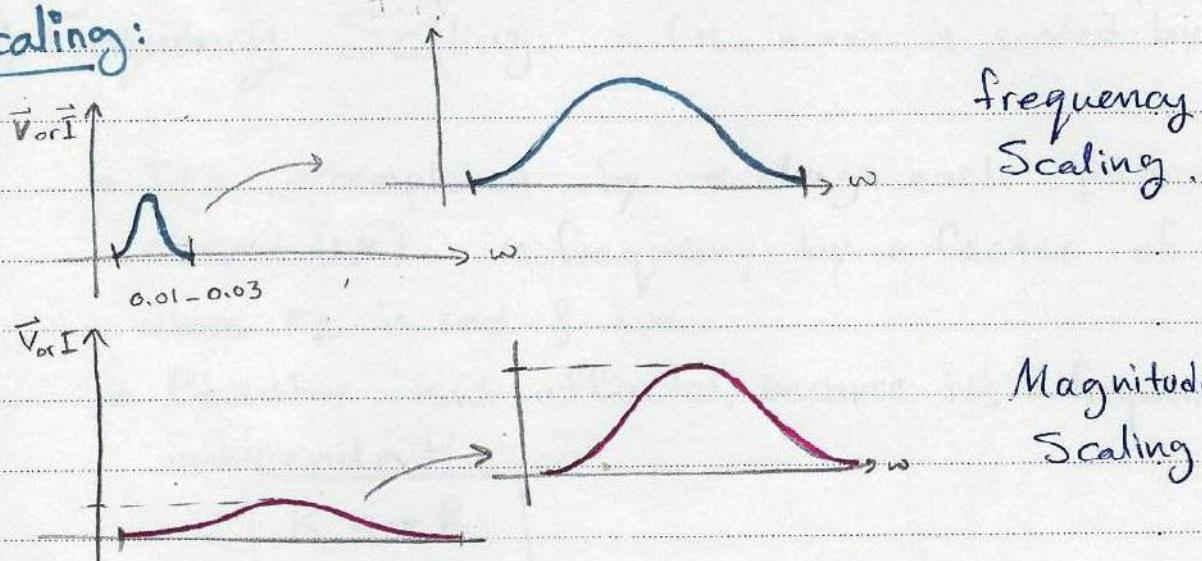

□ Magnitude Scaling :- (the Y-axis is scaled by k_m)

- frequency remains constant.
- The impedance of the two-terminals network is increased by a factor k_m , where k_m is real & positive and may be greater or less than unity.

ex2:

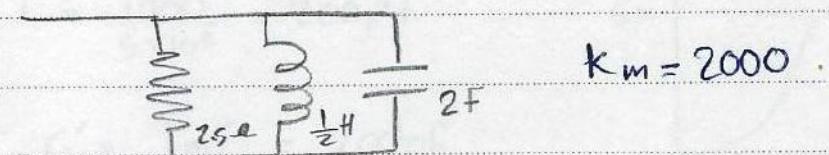

Magnitude

Scaling :

$$R' = k_m R = 5k\Omega$$

$$L' = k_m L = 1000 \text{ H}$$



$$C' = \frac{C}{k_m} = 1 \mu\text{F}$$

$$\omega_0' = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{k_m L \cdot \frac{C}{k_m}}} = \frac{1}{\sqrt{k_m L C}}$$

$$\omega_0' = \frac{1}{\sqrt{LC}} = \omega_0$$

Z before

after mag. Scaling!

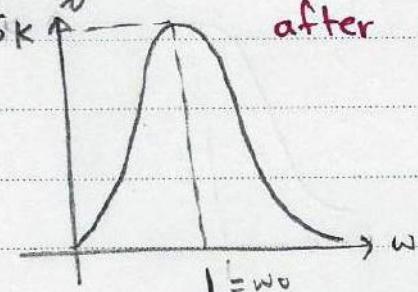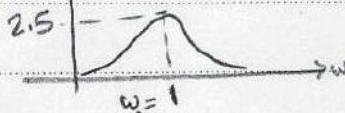

remains constant

[2] Frequency Scaling: (the x-axis is scaled by k_f)

- It's accomplished by scaling each passive element ($1/c$) in frequency by a factor of k_f , where k_f is real & +ve.
- Resistor isn't affected, because it's a frequency independent!


$$\begin{array}{l|l} R \leftrightarrow R & \\ L \rightarrow \frac{L}{k_f} & \\ C \rightarrow \frac{C}{k_f} & \end{array}$$

ex2:- from the previous example, $R = 5K$, $L = 1000H$, $C = 1mF$, if $k_f = 5 \times 10^6$, find R' , L' , C'

Sol:- $R' = 5K$ (no change) it's freq. independent

$$L' = \frac{1000}{5 \times 10^6} = 200 \mu F$$
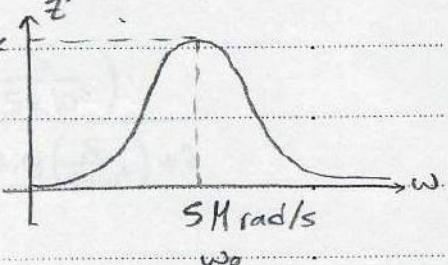
$$C' = \frac{1mF}{5 \times 10^6} = 200 \mu F$$



Scaling can be made:

1. element by element
2. for Z_{eq} .

- Scaling of $Z(s)$:

- Mag Scaling:-

$$Z'(s) = k_m Z(s)$$

for the CKT in (ex1) :-

$$Z(s) = \frac{s}{2s^2 + 0.4s + 2}, \text{ if } k_m = 2000$$

$$Z'(s) = \frac{2000 s}{2s^2 + 0.4s + 2} \quad \textcircled{1}$$

- freq. Scaling:-

$$Z'(s) = Z' \left(\frac{s}{k_f} \right)$$

for $Z'(s)$ in $\textcircled{1}$, if $k_f = 5 \times 10^6$

$$Z''(s) = \frac{2000 \left(\frac{s}{5 \times 10^6} \right)}{2 \left(\frac{s}{5 \times 10^6} \right)^2 + 0.4 \left(\frac{s}{5 \times 10^6} \right) + 2}$$

- Dealing with dependant sources:

* although scaling is a process normally applied to passive elements, dependent sources may also be scaled in magnitude & frequency.


* if the network containing the dependent source is scaled by k_m , then it's necessary only to treat k_x or k_y as if it was the type of element consistent with its dimensions ; that is if k_x or k_y is dimensionless \rightarrow it's left unchanged!

& if it is an admittance \rightarrow divide by k_m .

$\sim \sim \sim$ impedance \rightarrow multiply $\sim k_m$.

* Frequency scaling doesn't affect the dependent sources!


ex:-

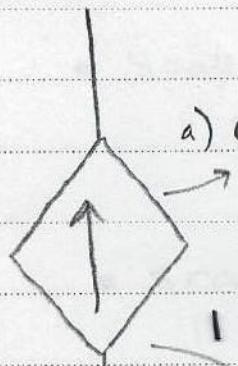

$$\text{a)} 0.02 V_x \rightsquigarrow [0.02] = \frac{A}{V} \text{ (since it's a current source)} \\ = S \text{ (admittance)}$$

$$\therefore 0.02 V_x \xrightarrow{\text{mag. scaling}} \frac{0.02 V_x}{k_m}$$
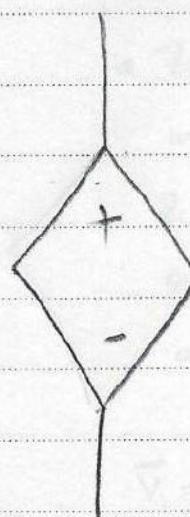
$$\text{b)} 0.02 I_x \rightsquigarrow [0.02] = \text{dimensionless} \rightarrow \text{leave it as is!}$$




$$\text{c)} 0.02 V_x \rightsquigarrow [0.02] = \text{dimensionless} \\ \text{leave it as is!}$$

$$\text{d)} 0.02 I_y \rightsquigarrow [0.02] = \frac{V}{A} = Z! \text{ impedance}$$

$$\therefore 0.02 I_y \xrightarrow{\text{Mag. scaling}} 0.02 k_m I_x$$

ex 16.8 with me

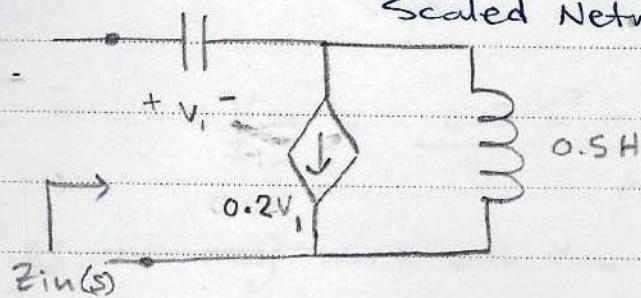Ex 2: Scale the following Network with $K_m = 20$ and $k_f = 50$.
0.05F then find $Z_{in}(s)$ for the scaled Network:



Sol:- • Scaling C :-

$$C' = \frac{C}{K_m * k_f} = \frac{0.05}{(20)(50)} = 50 \mu F$$

• Scaling L :-

$$L' = \frac{L * K_m}{k_f} = \frac{0.5 * 20}{50} = (0.2) H$$

• scaling the dependent source:- (only mag. scaling)

$\frac{0.2}{V_1} \leftrightarrow \frac{1}{Y}$ units of an admittance $\rightarrow K_x = \frac{0.2}{20} = 0.01 \rightarrow \frac{0.01}{V_1}$


• $Z_{in}(s)$?

in order to calculate

$Z_{in}(s)$, we need to

apply a current source

at the terminals a-b

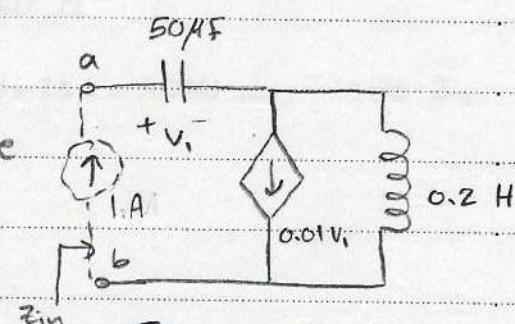


The Scaled Network

$$\tilde{V}_1 = \frac{20000}{s} (1) = \frac{20000}{s}$$

$$I_L = 1 - 0.01 \tilde{V}_1 = 1 - 0.01 \left(\frac{20000}{s} \right)$$

$$I_L = 1 - \frac{200}{s}$$

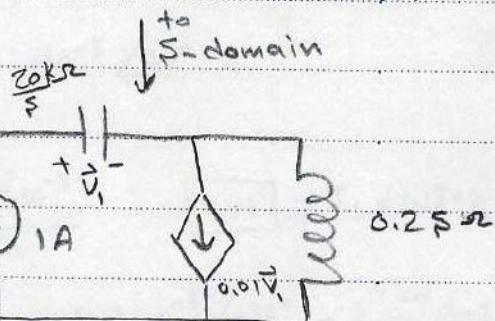

$$\vec{V}_L = I_L (0.2s - 40) \text{ V}$$

$$V_{in} = V_1 + V_L = \left(\frac{20000}{s} + 0.2s - 40 \right) \text{ V}$$


$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{0.2s^2 - 40s + 20000}{s} \text{ } \Omega$$

or we may work with the first (unscaled) network to calculate the (unscaled impedance) & then scale it (multiply it by k_m & replace each s with $(\frac{s}{k_f})$)

++ Problem 53 page 688: Scale the following network by $k_m = 250$, $k_f = 400$, then find thevenin equivalent of the scaled network at $\omega = 1 \text{ rad/s}$


$$\text{Sol: } C' = \frac{C}{k_m \times k_f} = \frac{0.1}{(250)(400)} = 1 \mu\text{F}$$
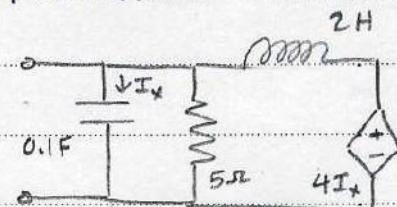
$$L' = \frac{L \times k_m}{k_f} = \frac{2 \times 250}{400} = 1.25 \text{ H}$$



$$R' = R \times k_m = 5 \times 250 = 1250 \Omega$$
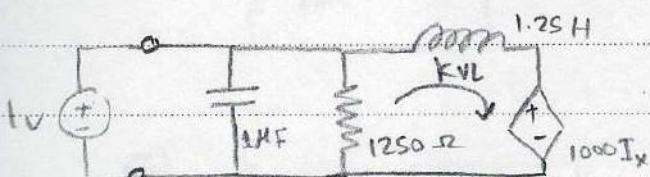
$$K_y = k_y \times k_m = 4(k_m) = 4 \times 250 = 1000 \rightarrow 1000 I_x$$



the scaled Network

$$I_x = \frac{V}{Z} = 1(j\omega) = j(1000)(1\mu\text{F}) = 10^{-3} \angle 90^\circ \text{ A}$$

$$I_R = \frac{V}{R} = \frac{1}{1250} = 0.8 \text{ mA}$$

$$I_L \Rightarrow I = j1000(1.25)I_L + \underbrace{j1000(1 \times 10^{-3})}_{1000 I_x}$$

$$\boxed{\text{KVL}} \rightarrow I_L = 1.13 \times 10^{-3} \angle 135^\circ$$

$$I_{\text{source}} = I_x + I_R + I_L = 10^{-3} \angle 90^\circ + 0.8 \text{ mA} + 1.13 \times 10^{-3} \angle 135^\circ = 2 \times 10^{-4} \angle 89.7^\circ \text{ mA}$$

$$\approx 2 \times 10^{-4} \text{ j}$$

$$Z_{th} = \frac{V_{\text{source}}}{I_{\text{source}}} = -j500\Omega$$

Problem 52 Page 688:-


use good approximation, find:-
 a) ω_0 , b) Q_0 , c)

ω_0, Q_0 , Scale the network

so it reaches resonance at

$\omega = 1 \text{ rad/s}$, then d)

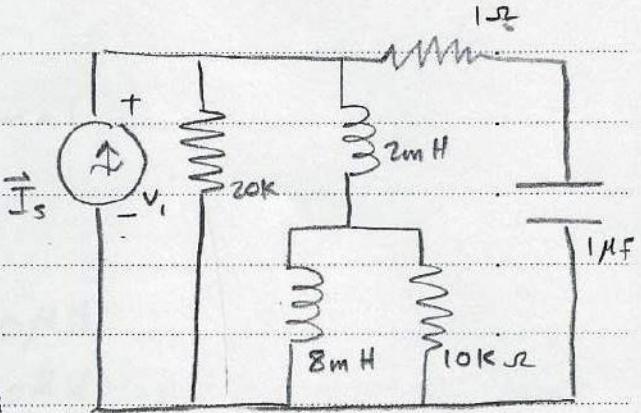$\omega_0 \& \beta$ for the scaled network.



Sol:- first we have to find the equivalent parallel RLC

CKT:-

$$1) \quad \omega_0 = \frac{1}{\sqrt{L_0 C_0}} = \frac{1}{\sqrt{(8+2) \times 10^{-3} \times (1 \times 10^{-6})}} = 1.0^4 \text{ rad/s}$$

$\rightarrow Q_p = \frac{R}{\omega_0 L} = \frac{10K}{10^4 (8m)} = 125$ ← Branch N ≈ 125

$\rightarrow R_s = \frac{R_p}{Q^2} = \frac{10K}{(125)^2} = 0.64 \Omega$! use approximation

$\rightarrow X_s = X_p = 8mH$

$$2) \quad \begin{array}{c} 2m \\ 0.64 \Omega \\ 8m \end{array} = \begin{array}{c} 10mH \\ 0.64 \Omega \end{array} = \begin{array}{c} 10m \\ 15.625K \end{array} \quad Q_s = \frac{\omega_0 L}{R} = \frac{10^4 \times 10m}{0.64} = 156.25$$

$$R_p = R_s Q^2 = 15.625 K \Omega$$

$$X_p = X_s = 10mH$$

$$3) \quad \begin{array}{c} 1 \\ 10K \\ 1\mu F \end{array} = \begin{array}{c} 1 \\ 10K \end{array} \quad Q_s = 1/(w_0 R C) = 1/(10^4)(1)(1 \times 10^{-6}) = 100 \geq 5$$

$$R_p = R_s Q^2 = 1/(100)^2 = 10K \Omega$$

$$X_p = X_s = 1\mu F$$

$$R_{eq} = 20K // 15.625K // 10K = 4.673 K \Omega$$

$$Q_0 = R/w_0 L = (4.673K) / (10^4)(10 \times 10^{-3}) = 4.673$$

c) Scaling :-

$$k_f = \frac{1M}{10^4} = 100, k_m = 1$$

- $R' = R$

- $C'_1 = (8 \times 10^{-3}) / 100 = 80 \mu F$

- $C'_2 = (2 \times 10^{-3}) / 100 = 20 \mu F$

- $L' = (1 mH) / 100 = 10 \mu H$

d) $\omega_0 = 1M \text{ rad/s}$


Q_0 remains the same

$$\beta' = \frac{\omega_0}{Q_0} = \frac{10^6}{47.73} = 21.4 \text{ krad/s}$$

++ Problem 51 page 687 :-

Find $Z_{in}(s) \Rightarrow$ and scale it

by $k_m = 2, k_f = 5$

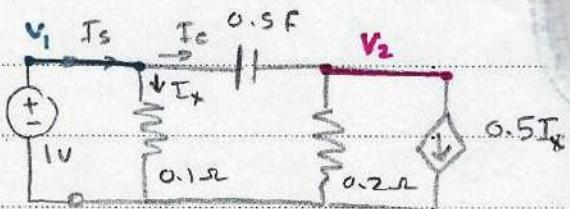

Sol:- add a (1V) voltage source:-

$$I_x = \frac{V}{R} = \frac{1}{0.1} = 10 \text{ A} \quad / \quad 0.5sI_x = 5 \text{ A}$$

$$I_s = I_x + I_c$$

$$= 10 + \frac{(1 - V_2)}{\frac{1}{0.5s}} = 10 + \frac{s(1 - V_2)}{2} \Rightarrow V_2 = \frac{s + 20 - 2I_s}{s}$$

using nodal analysis at node 2:-

$$\left(\frac{s(V_2 - 1)}{2} \right) + \frac{V_2}{0.2} + s = 0$$

$$10 - I_s + \frac{s + 20 - 2I_s}{0.2s} + s = 0$$

$$2s - 0.2sI + s + 20 - 2I + s = 0$$

$$4s + 20 = 0.2sI + 2I$$

$$I(0.2s + 2) = 4s + 20$$

$$I = \frac{(4s + 20)}{0.2s + 2}$$

$$Z_n(s) = \frac{V}{I} = \frac{0.25 + 2}{4s + 20} = \frac{s + 10}{20s + 100}$$

Scaling: $Z'(s) = 2 \left(\frac{s + 10}{20s + 100} \right)$ mag. scaling.

$$Z''(s) = Z'\left(\frac{s}{5}\right) = \frac{2\left(\frac{s}{5}\right) + 20}{20\left(\frac{s}{5}\right) + 100} = \frac{0.4s + 20}{4s + 100}$$

$$Z_{\text{scaled}} = \frac{0.4s + 20}{4s + 100} \times \frac{5}{10} = \boxed{\frac{s + 50}{10s + 250}}$$

*


• Bode diagram:-

- It's an approximation picture of the amplitude & phase variation of a given transfer function as function of ω .

- The Decibel (dB) scale:-

- the approximate response curve we construct is called asymptotic plot / bode plot / bode diagram.

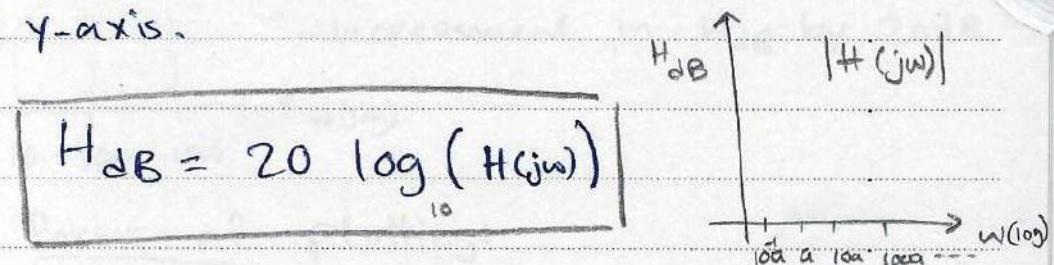- Magnitude & phase curves are shown using logarithmic frequency scale for the x-axis & logarithmic units called decibels (dB) for the y-axis.



• Log Properties:-

$$* \log 1 = 0$$

$$* \log 2 = 0.3$$

$$* \log 10 = 1$$

$$* \log 10^n = n \log 10 = n$$

$$* \log \frac{1}{10^n} = -n$$

$$* \log a = x \rightarrow \log \frac{1}{a} = -x$$

$$* \log(\frac{a}{b}) = \log a - \log b$$

$$* \log(a \cdot b) = \log a + \log b$$

$$* \log \sqrt{a} = \frac{1}{2} \log a$$

$$* \log a^x = x \log a$$

- Some common dB values:-

$$|H(j\omega)| = 1 \rightarrow H_{dB} = 0 \text{ dB} = 20 \log 1 = 0$$

$$|H(j\omega)| = 2 \rightarrow H_{dB} = 6 \text{ dB} = 20 \log 2 = 6$$

$$|H(j\omega)| = 10 \rightarrow H_{dB} = 20 \text{ dB}$$


$$|H(j\omega)| = 100 \rightarrow H_{dB} = 40 \text{ dB}$$

$$|H(j\omega)| = 10^r \rightarrow H_{dB} = 20r \text{ dB}$$

$$|H(j\omega)| = 5 = \frac{10}{2} \rightarrow H_{dB} = H_{dB}(10) - H_{dB}(2) = 20 - 6 = 14 \text{ dB}$$

$$|H(j\omega)| = \sqrt{2} \rightarrow H_{dB} = 3 \text{ dB}$$

$$|H(j\omega)| = \frac{1}{\sqrt{2}} \rightarrow H_{dB} = -3 \text{ dB}$$

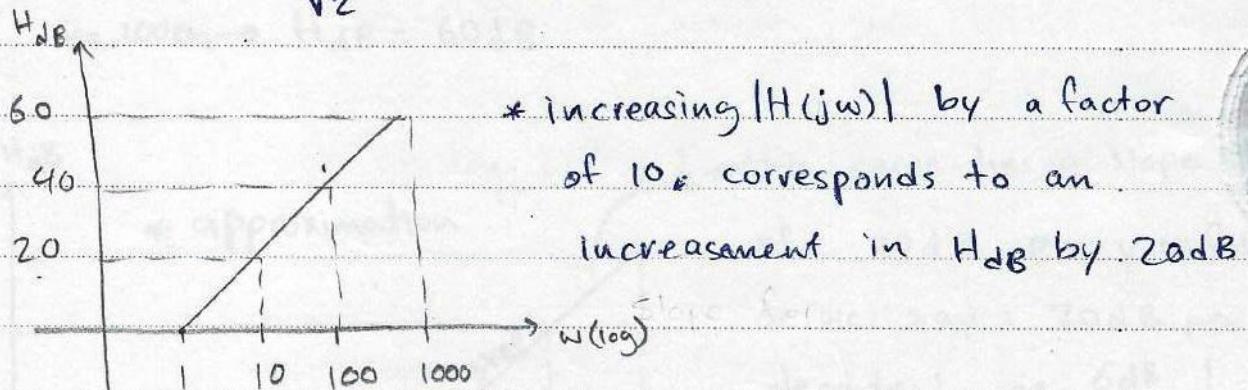

-Standard forms of plotting:

A) Assume $H(s) = 1 + \sum \frac{s}{a}$, a is constant

- Zero at $s = -a$

- to plot this form, we have to find what we'll call "the asymptotic curve (s)".

- we'll plot with respect to (w)!

$$H(j\omega) = 1 + \frac{j\omega}{a} \Rightarrow |H(j\omega)| = \sqrt{1 + \frac{\omega^2}{a^2}}$$

$$\therefore H_{dB} = 20 \log \sqrt{1 + \frac{\omega^2}{a^2}} = 10 \log \left(1 + \frac{\omega^2}{a^2}\right)$$

$$\rightarrow H_{dB} = 10 \log \left(1 + \frac{w^2}{a^2} \right)$$

Step 1 → to find the assym. curve we do the following approximation:- $w \ll a \rightarrow \log \left(1 + \frac{w^2}{a^2} \right) \xrightarrow{\approx 0} \log(1)$

$$\therefore H_{dB} \approx 10 \log(1) = 0$$


Step 2 → $w \gg a \rightarrow H_{dB} = 10 \log \frac{w^2}{a^2} = 20 \log \left(\frac{w}{a} \right)$
 $\approx 10 \log \left(1 + \frac{w^2}{a^2} \right) \xrightarrow{\gg 1} \therefore \text{we neglect } (1)$

approximately

Step 3 → $w=a \rightarrow H_{dB}=0$ Step 1 or 2 is up.

$$w=10a \rightarrow H_{dB}=20 \text{ dB}, w=100a \rightarrow H_{dB}=40 \text{ dB}$$
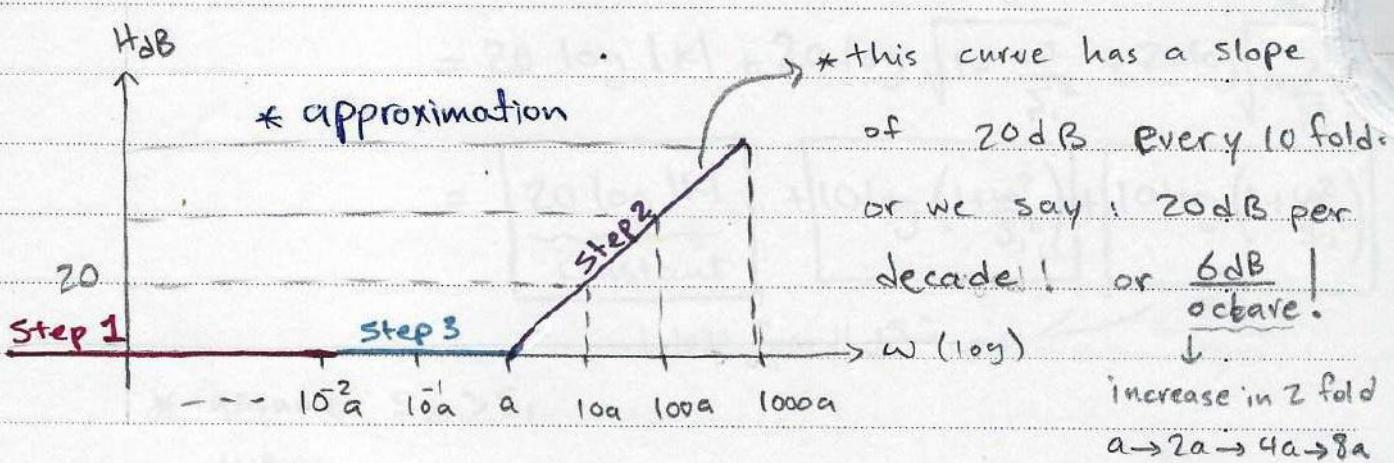
$$w=1000a \rightarrow H_{dB}=60 \text{ dB}$$




* Since it's an approximation, we have to do

Smoothing :- approx. is nice ! \rightarrow also P/B

• exact values:-

$$@ w=a \rightarrow H_{dB} = 20 \log \sqrt{1 + \frac{a^2}{a^2}} = 20 \log \sqrt{2} = 3 \text{ dB}$$
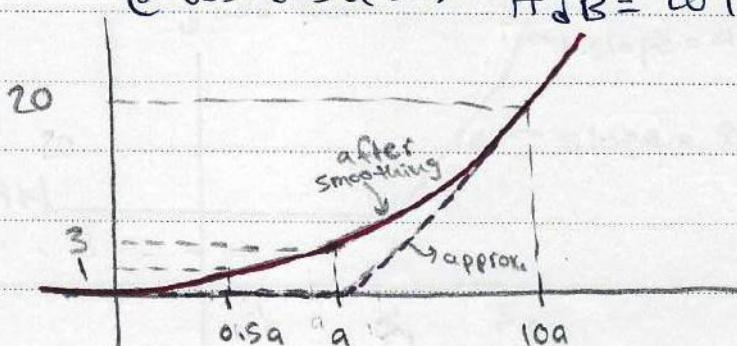
$$@ w=0.5a \rightarrow H_{dB} = 20 \log \sqrt{1+0.25} \approx 1 \text{ dB}$$



Standard form of plotting (cont)

B) * Multiple terms:

$$H(s) = K \left(1 + \frac{s}{s_1} \right) \left(1 + \frac{s}{s_2} \right)$$

- zeros at $s = -s_1, -s_2$

- $H_{dB} = 20 \log |H(j\omega)|$

$$= 20 \log \left| K \left(1 + \frac{j\omega}{s_1} \right) \left(1 + \frac{j\omega}{s_2} \right) \right|$$

→ in terms of $j\omega$


$$H_{dB} = 20 \log \left| K \left(1 + \frac{j\omega}{s_1} \right) \left(1 + \frac{j\omega}{s_2} \right) \right|$$


$$= 20 \log |K| + 20 \log \sqrt{1 + \frac{\omega^2}{s_1^2}} + 20 \log \sqrt{1 + \frac{\omega^2}{s_2^2}}$$

$$= \boxed{20 \log |K|} \quad \boxed{+ 10 \log \left(1 + \frac{\omega^2}{s_1^2} \right)} + \boxed{10 \log \left(1 + \frac{\omega^2}{s_2^2} \right)}$$

نفس شكل الأصل! ←

* assume $s_2 > s_1$

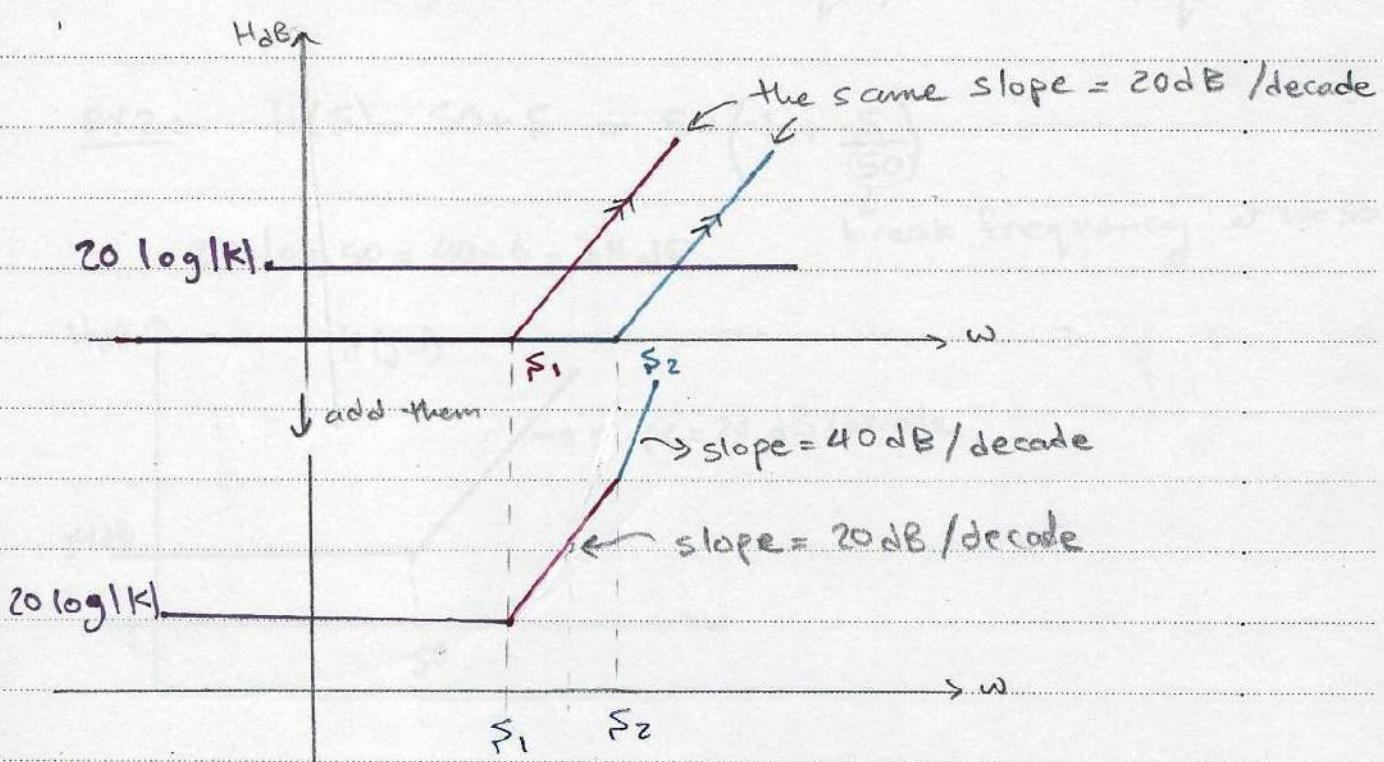


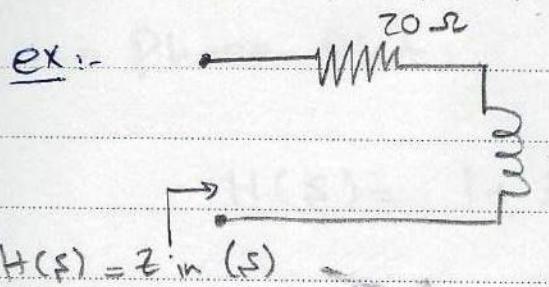

$$H(s) = Z_{in}(s) = 20 + 0.2s = 20 \left(1 + \frac{0.2s}{20}\right)$$

$s \approx 1.6\omega_0$ at corner frequency
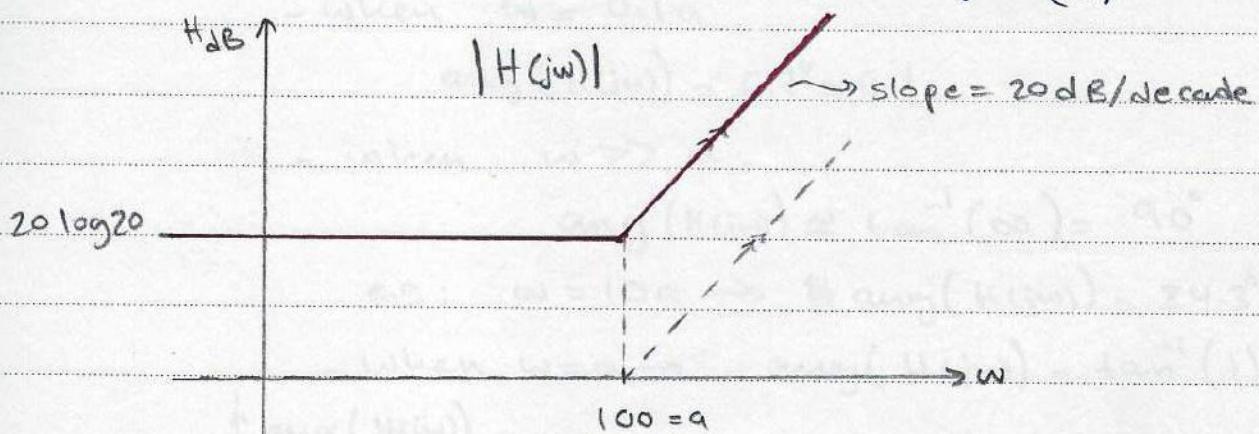
$$H_{dB} = 20 \log(20) + 20 \log \sqrt{1 + \left(\frac{\omega}{100}\right)^2}$$




bit's called : "corner frequency" /

"half power freq." / "break freq." /
"cutoff freq." / "3dB freq."

ex2:- $H(s) = 50 + s = 50 \left(1 + \frac{s}{50}\right)$

$$20 \log 50 = 40 - 6 = 34 \text{ dB}$$

break frequency at $\omega = 50$

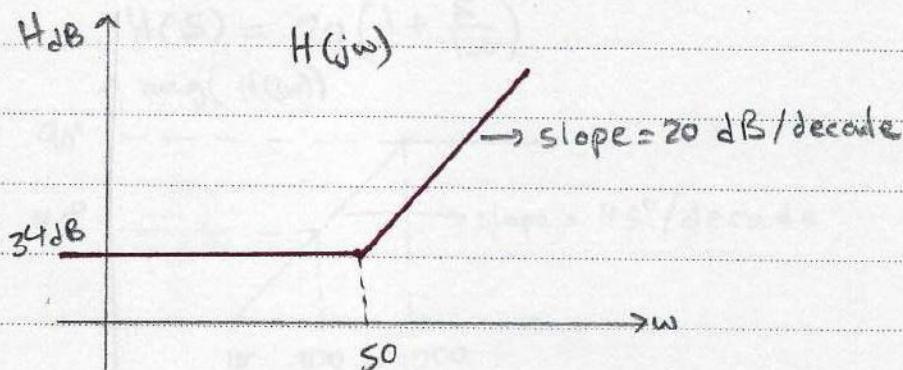

→ Phase Plot:

$$H(s) = 1 + \frac{s}{a}$$

$$\text{ang}(H(j\omega)) = \text{ang}\left(1 + \frac{j\omega}{a}\right) = \tan^{-1}\left(\frac{\omega}{a}\right)$$

- when $\omega \ll a \Rightarrow \text{ang}(H(j\omega)) \approx \tan^{-1}(0) = 0$

- when $\omega = 0.1a$

$$\text{ang}(H(j\omega)) = 5.7^\circ \approx 0 !$$


- when $\omega \gg a$,

$$\text{ang}(H(j\omega)) \approx \tan^{-1}(\infty) = 90^\circ$$

$$\text{e.g.: } \omega = 10a \rightarrow \text{ang}(H(j\omega)) = 84.3^\circ \approx 90^\circ$$

- when $\omega = a \rightarrow \text{ang}(H(j\omega)) = \tan^{-1}(1) = 45^\circ$


$\uparrow \text{ang}(H(j\omega))$

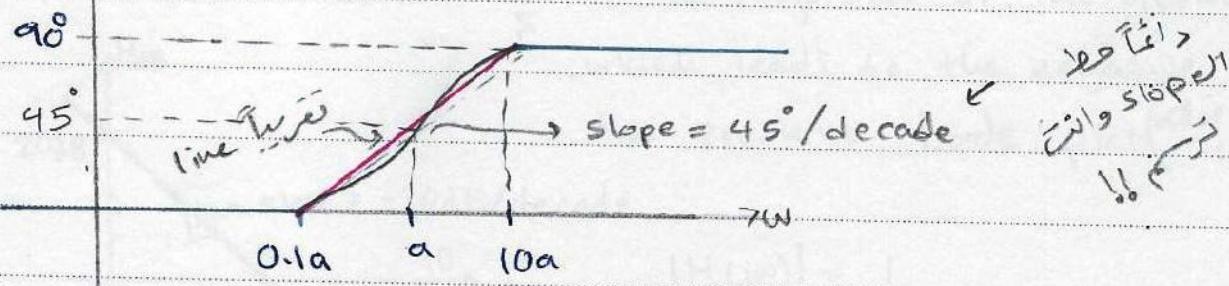

ex: Draw the Bode Phase Plot for:-

$$H(s) = 20 \left(1 + \frac{s}{100}\right)$$


$\uparrow \text{ang}(H(j\omega))$

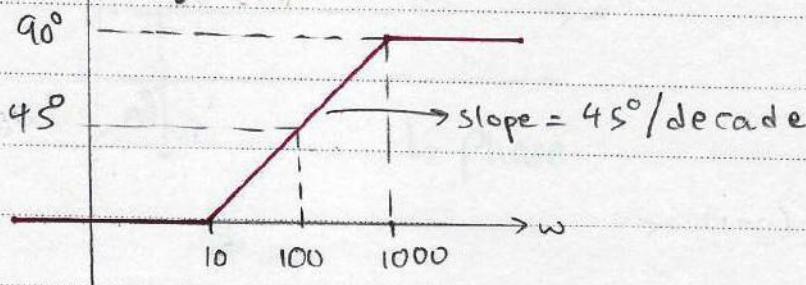

Zero at zero:-

$$\text{let } H(s) = \frac{1}{s} \rightarrow |H(j\omega)| = \omega$$

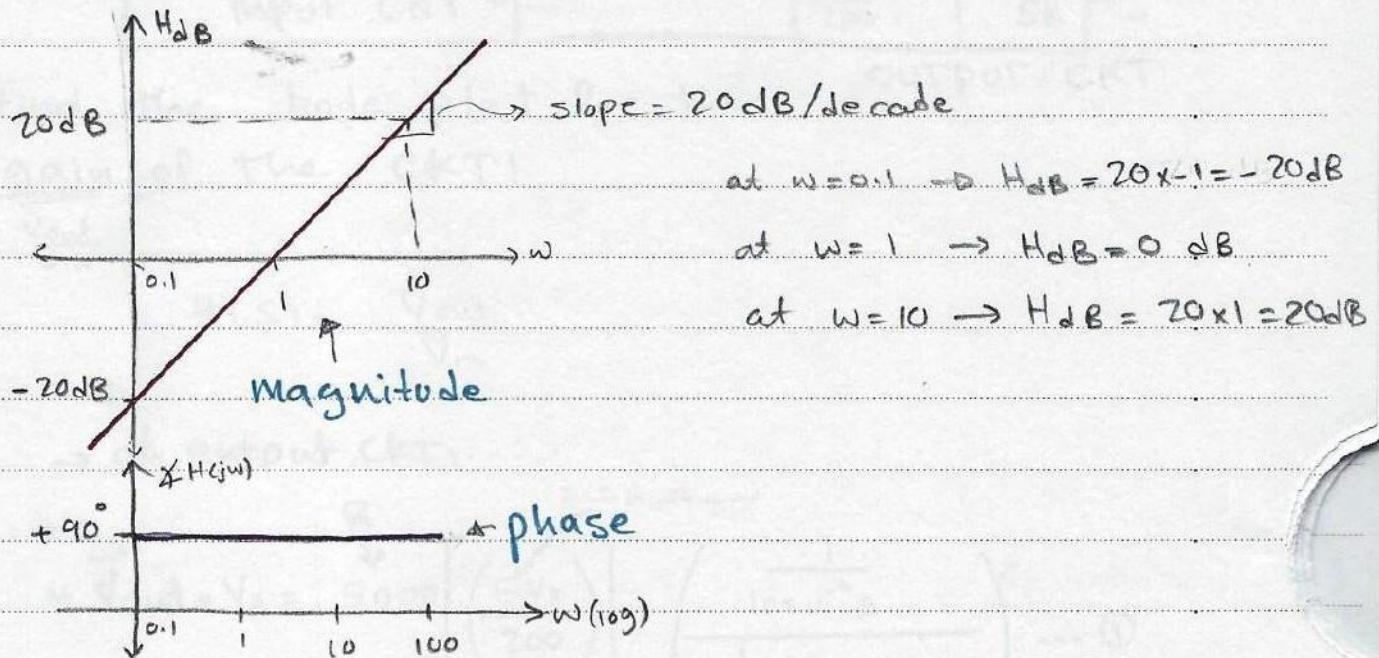
$$\hookrightarrow H(j\omega) = j\omega \quad H_{dB} = 20 \log(\omega)$$




Pole at zero:-

$$\text{let } H(s) = \frac{1}{s} \quad (\text{the reciprocal of the previous one})$$

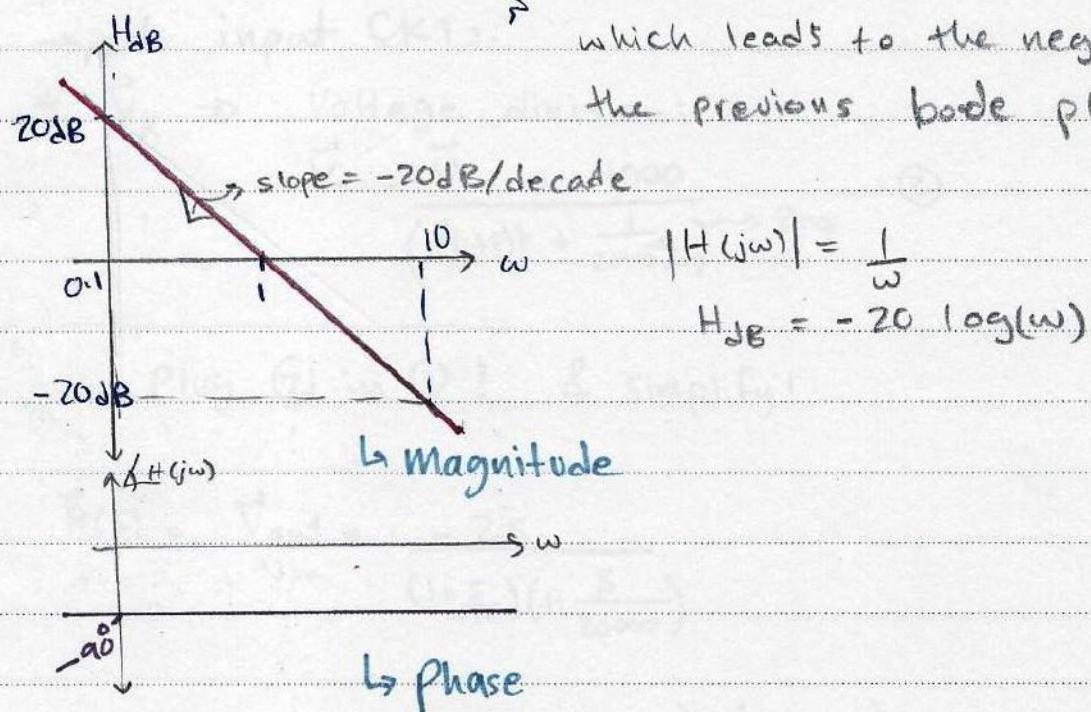which leads to the negative of
the previous bode plot ($\frac{\text{add}(1/\omega)}{\log(\omega)}$)



ex:-

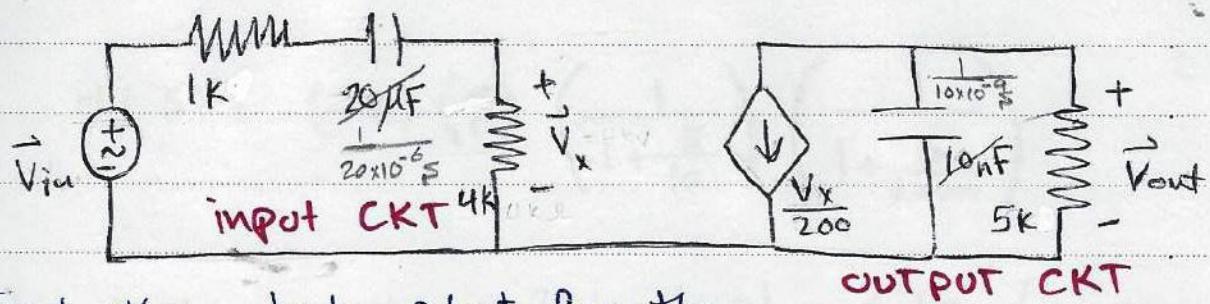

Find the bode plot for the gain of the CKT!

$$\frac{\vec{V}_{out}}{\vec{V}_{in}}$$

$$H(s) = \frac{\vec{V}_{out}}{\vec{V}_{in}}$$

→ at output CKT:-

$$* \vec{V}_{out} = V_p = 5000 \left[\left(\frac{\vec{V}_x}{200} \right) \right] \cdot \left(\frac{\frac{1}{10x10^{-9}s}}{\frac{1}{10x10^{-9}s} + 5000} \right) \dots \textcircled{1}$$

using $\vec{V}_p = R_i \vec{I}_p$

\vec{I}_{total}

\vec{V}_{IR} (current division)

→ at input CKT:-

* $\vec{V}_x \Rightarrow$ Voltage division:

$$\vec{V}_x = \frac{\vec{V}_{in} \times 4000}{(H+1)k + \frac{1}{20x10^{-6}s}} \rightarrow Z_{eq} \dots \textcircled{2}$$

Plug (2) in (1)! & simplify!

$$H(s) = \frac{\vec{V}_{out}}{\vec{V}_{in}} = \frac{-2s}{(1+\frac{s}{10})(1+\frac{s}{20000})}$$


$$= -2(s) \left(\frac{1}{1+\frac{s}{10}} \right) \left(\frac{1}{1+\frac{s}{20000}} \right) \rightarrow$$

$$H(s) = (-2)(s) \left(\frac{1}{1+\frac{s}{10}} \right) \left(\frac{1}{1+\frac{s}{20000}} \right)$$

1) $(-2) \Rightarrow H_{dB} = 20 \log | -2 | = 6 \text{ dB}$ (constant)

2) $(s) \Rightarrow H_{dB} = 20 \log(\omega)$ linear factor
 ↳ zero at $\omega=1$!
 slope = 20 dB/decade

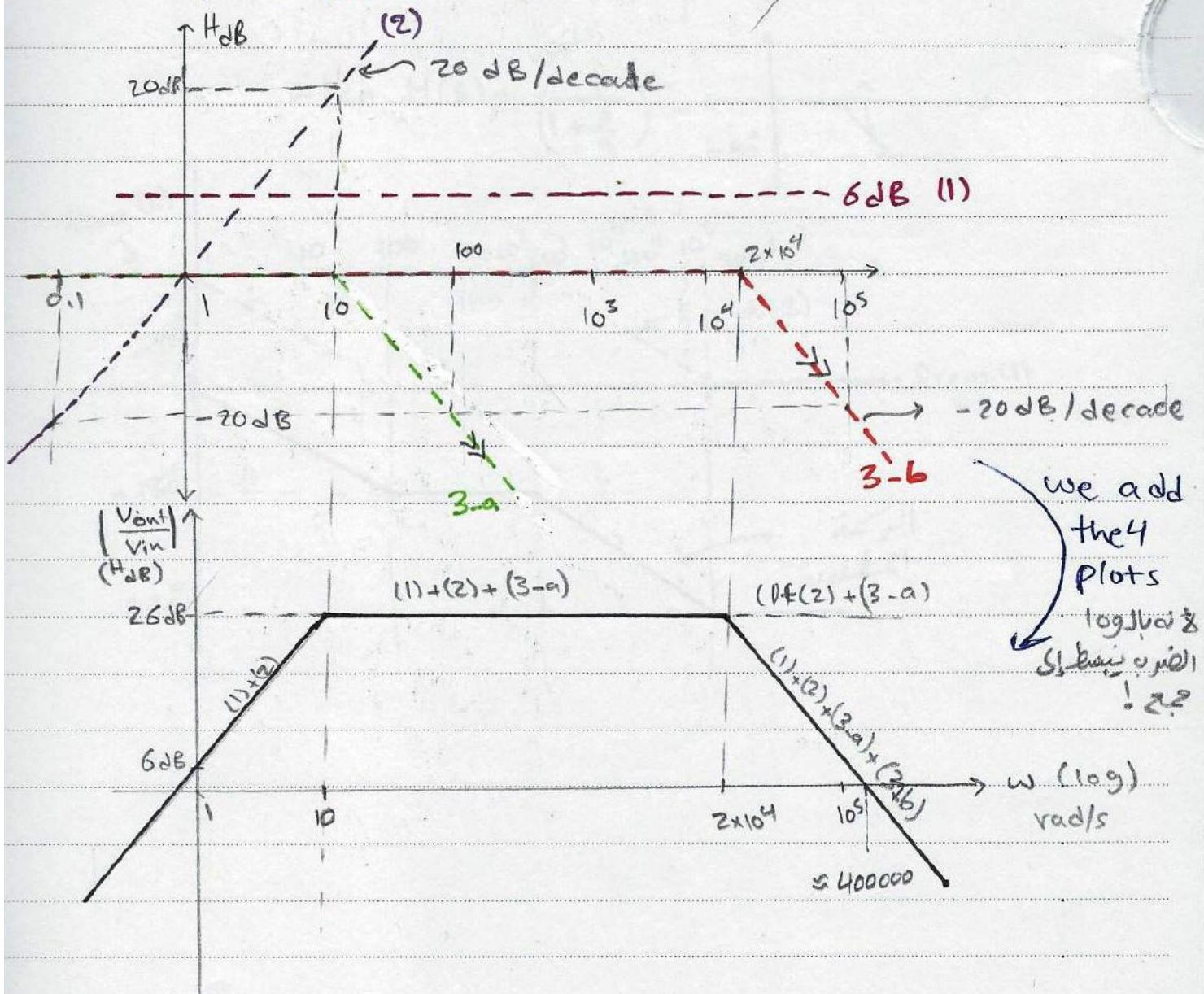3) we have break points at $\omega = 10 \text{ rad/s}$
 & $\omega = 20000 \text{ rad/s}$




$$H(s) = \frac{-2s}{\left[1 + \frac{s}{10}\right]\left[1 + \frac{s}{20000}\right]}, \text{ draw the phase bode plot for } H(s)$$


$$\rightarrow H(j\omega) = \frac{-2j\omega}{\left(1 + \frac{j\omega}{10}\right)\left(1 + \frac{j\omega}{20000}\right)}$$

1) the angle of the numerator is constant = -90°

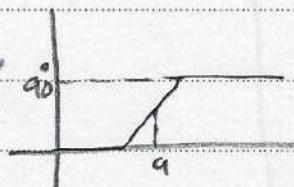2) when $H(s) = 1 + \frac{s}{a} \rightarrow$




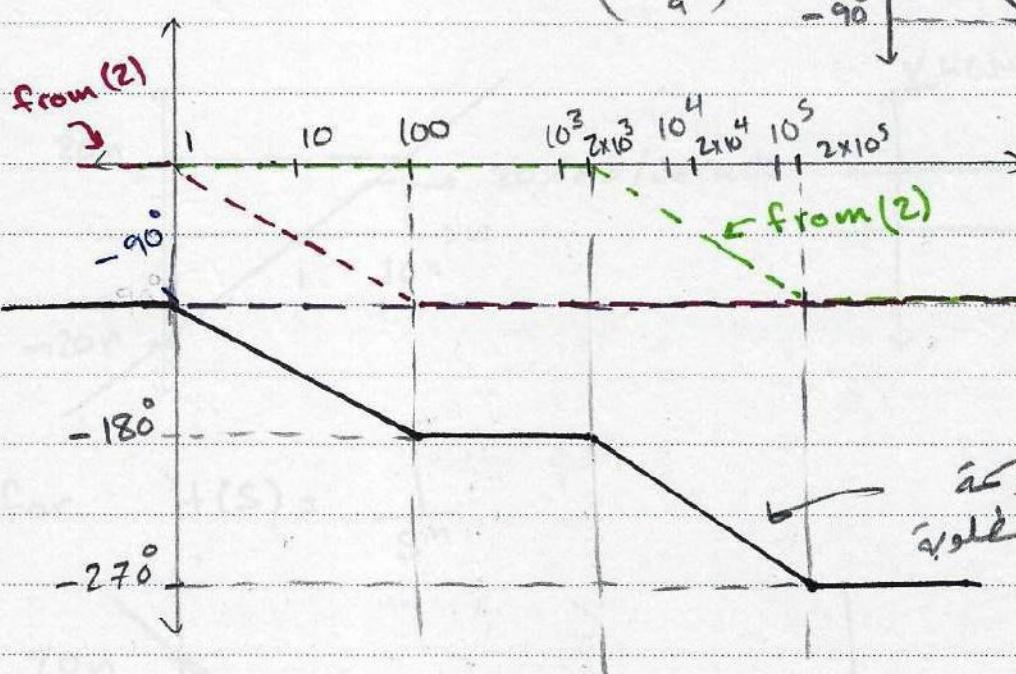
∴ when $H(s) = \frac{1}{\left(1 + \frac{s}{a}\right)}$




Higher order terms:

all the poles & zeros we've considered till now were from the first order e.g. $(s+1)$, $(1+0.2s)^{\pm 1}$

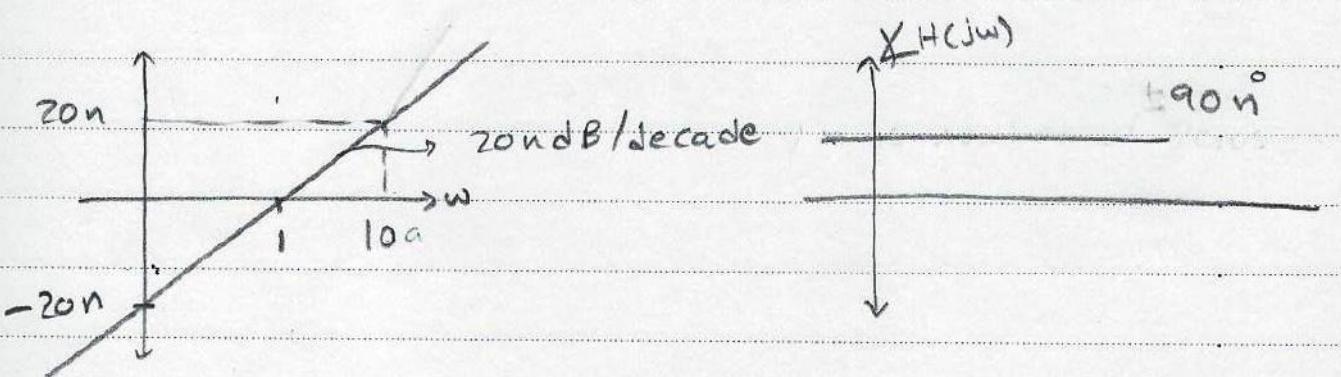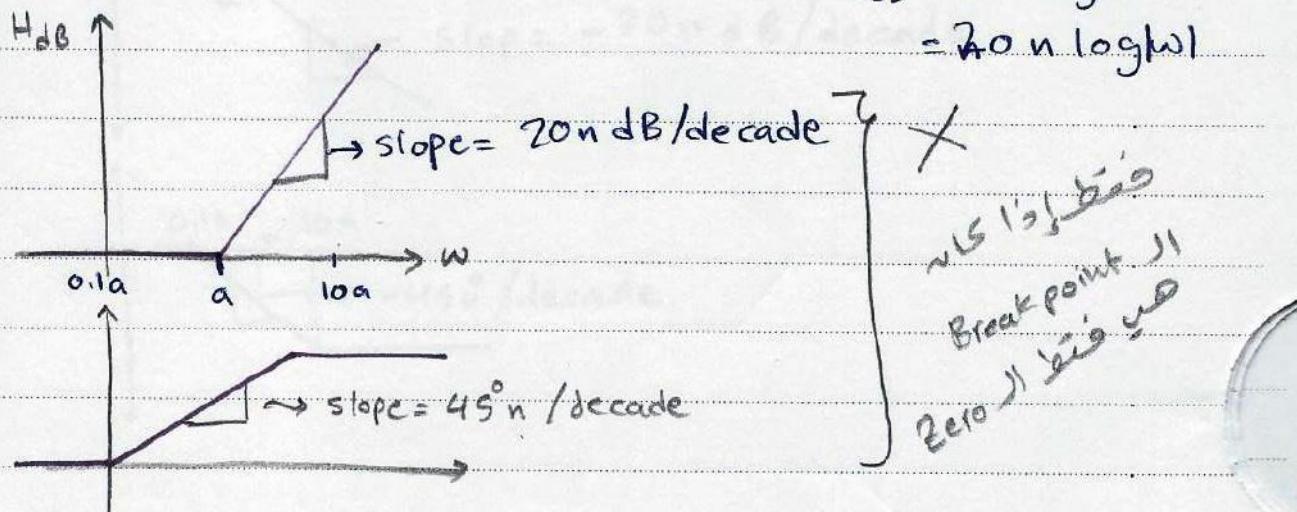
let's take $H(s) = s^n \rightarrow H_{dB} = 20 \log w^n = 20n \log w$



for $H(s) = \frac{1}{s^n}$

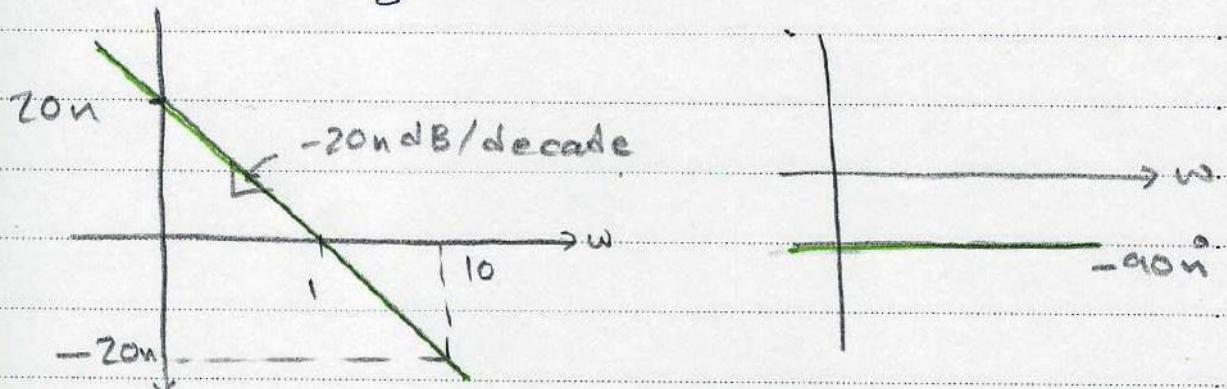

ex:-

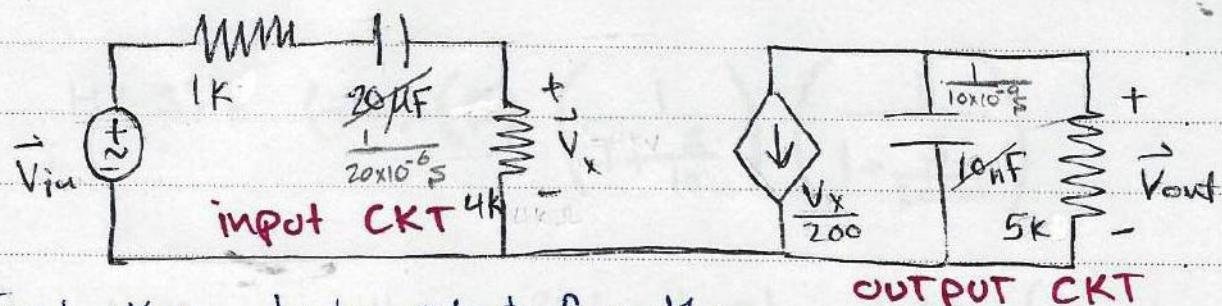

Find the bode plot for the gain of the CKT!

$$\frac{\vec{V}_{out}}{\vec{V}_{in}}$$

$$H(s) = \frac{\vec{V}_{out}}{\vec{V}_{in}}$$

→ at output CKT:-

$$* \vec{V}_{out} = V_p = 5000 \left[\left(\frac{\vec{V}_x}{200} \right) \right] \cdot \left(\frac{\frac{1}{10 \times 10^{-9} s}}{\frac{1}{10 \times 10^{-9} s} + 5000} \right) \dots ①$$

I_{total}

↳ I_R (current division)

→ at input CKT:-

* $\vec{V}_x \Rightarrow$ Voltage division:

$$\vec{V}_x = \frac{\vec{V}_{in} \times 4000}{(4+1)k + \frac{1}{20 \times 10^{-6} s}} \rightsquigarrow Z_{eq}, \dots ②$$


Plug ② in ①! & simplify!

$$H(s) = \frac{\vec{V}_{out}}{\vec{V}_{in}} = \frac{-2s}{(1 + \frac{s}{10})(1 + \frac{s}{20000})}$$

$$= -2(s) \left(\frac{1}{1 + \frac{s}{10}} \right) \left(\frac{1}{1 + \frac{s}{20000}} \right) \rightarrow$$


multi poles at $w=a$

$$H(s) = \frac{1}{(1 + \frac{s}{a})^n}$$





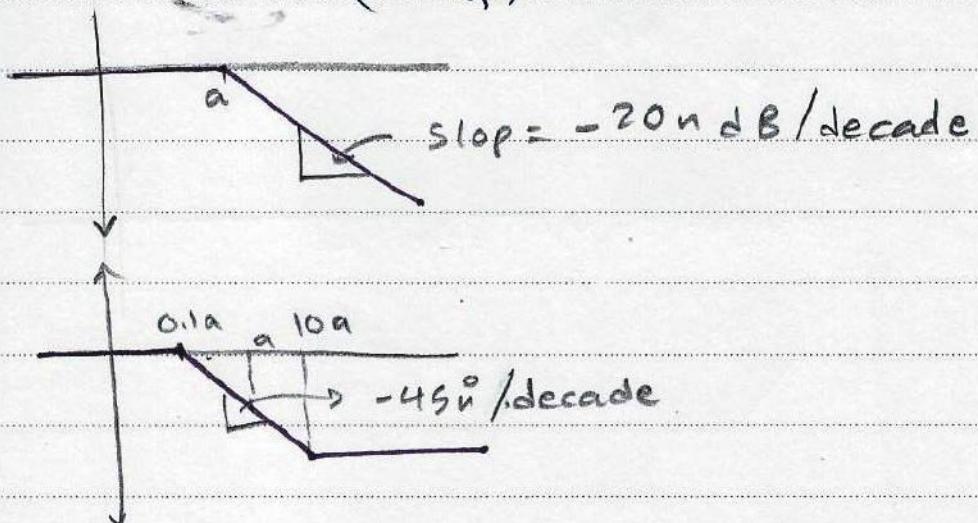


Filters :-


- Filter: it's a device used to select ^{certain} frequency band

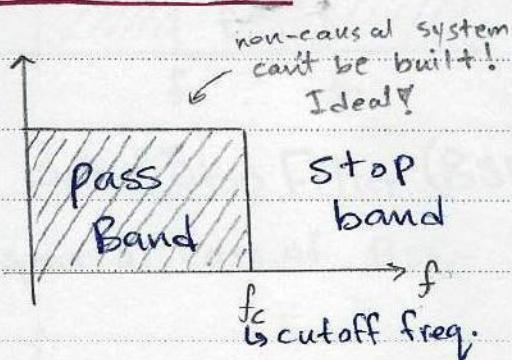Ideal Filters


for the -ve part we apply even symmetry.

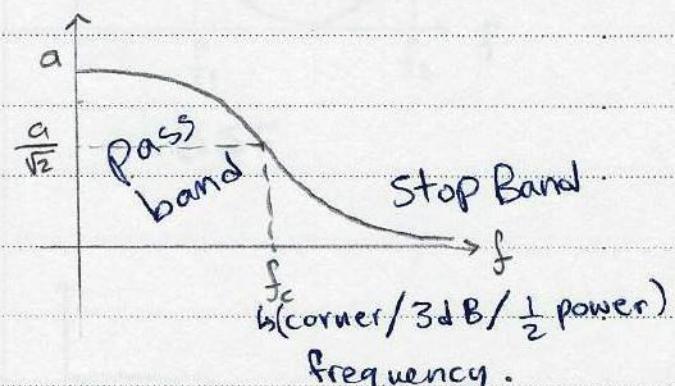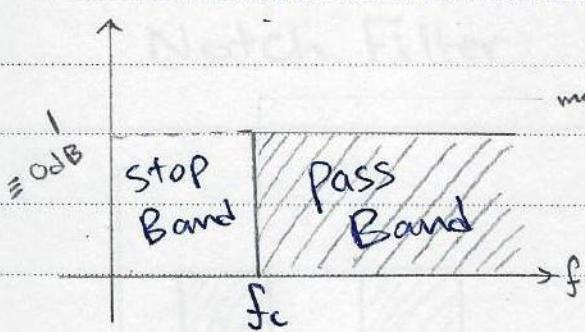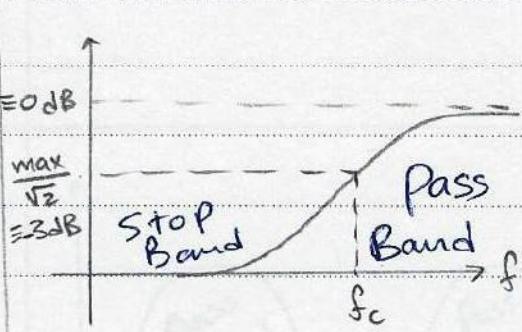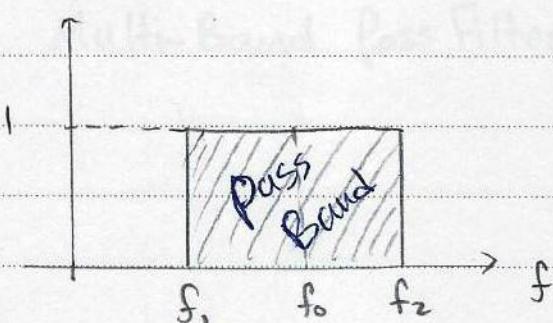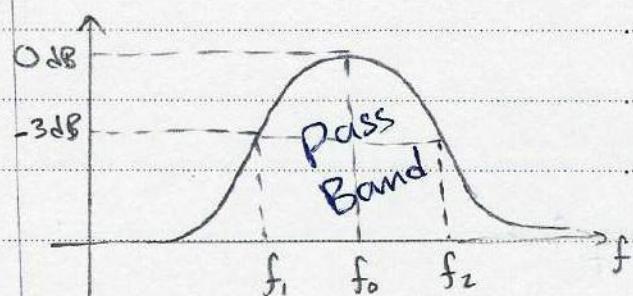Low Pass Filter (LPF)Non-ideal / Practical FiltersLPFHigh Pass Filter (HPF)HPFBand Pass Filter (BPF)BPF

Ideal

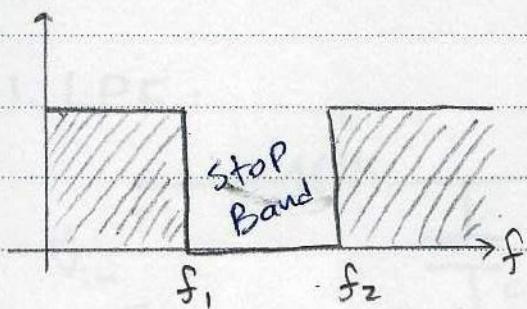


Practical

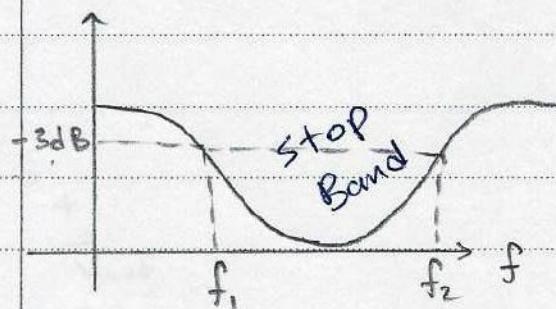




Band Stop Filter (BSF)

BSF

↳ special case of BSF:-

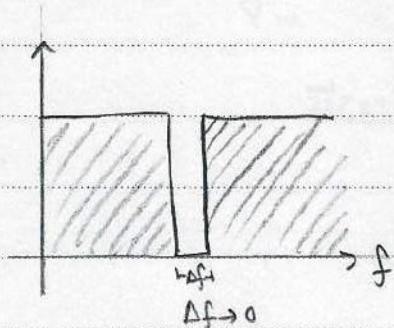


Notch Filter

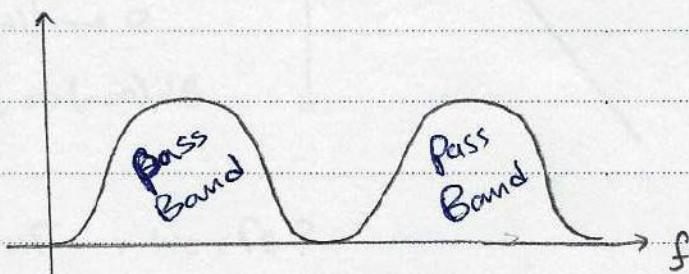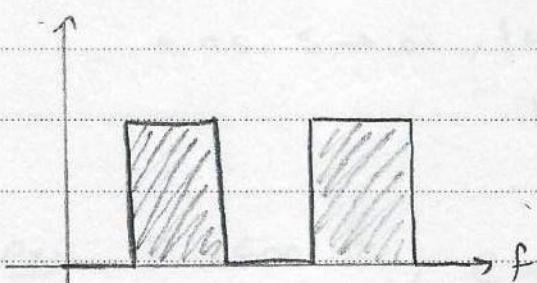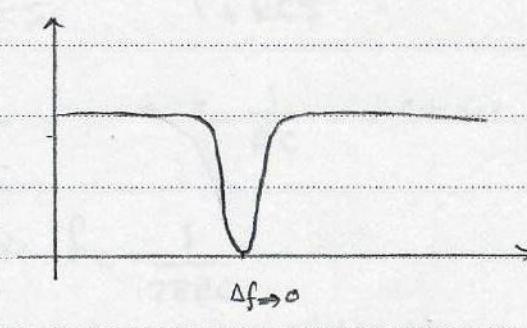

Multi-Band Pass Filter

Designing Filters


1. LPF:

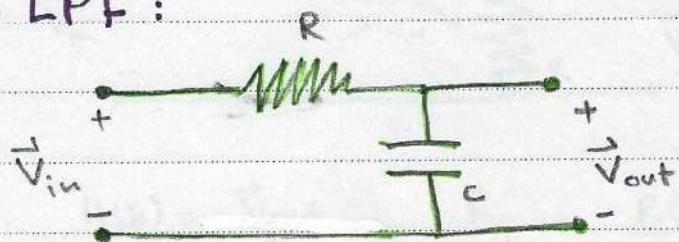

$$\tilde{H} = \frac{\tilde{V}_{out}}{\tilde{V}_{in}} = \frac{1/Cs}{R + 1/Cs} = \frac{1}{1 + RCs}$$

$$H(s) = \frac{1}{1 + \frac{s}{\omega_c}}, \quad \omega_c = \frac{1}{RC} \text{ ; corner freq.}$$
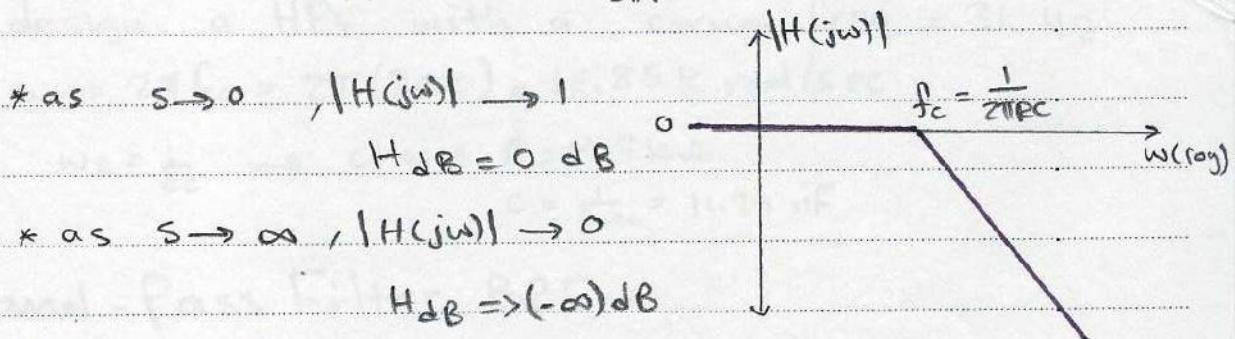
$$\omega_c = \frac{1}{RC} \Rightarrow f_c = \frac{1}{2\pi RC}$$



Ex:- $R = 500 \Omega$, $C = 2 \text{ nF}$, ω_c , f_c ?

Sol:-


$$\omega_c = \frac{1}{RC} = 1 \text{ Mrad/s}$$

$$f_c = \frac{1}{2\pi RC} = 159 \text{ KHz}$$

$$** |H(j\omega_c)| = \frac{1}{\sqrt{2}}$$

$$H_{dB} = -3 \text{ dB}$$

2. HPF

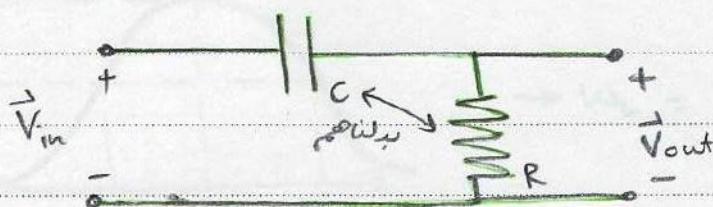


$$H(s) = \frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{Cs}} = \frac{RCS}{1 + RCS}, \quad \omega_c = \frac{1}{RC}; \text{ cutoff freq.}$$

as $s \rightarrow 0, |H(j\omega)| \rightarrow 0$

$$H_{dB} \rightarrow -\infty \text{ dB}$$

as $s \rightarrow \infty, |H(j\omega)| \rightarrow 1$

$$H_{dB} \rightarrow 0 \text{ dB}$$

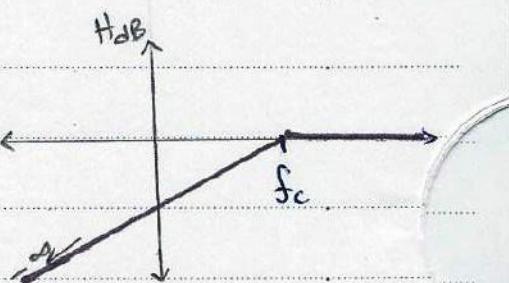


Ex:- design a HPF with a corner freq = 3K Hz

$$\omega_c = 2\pi f_c = 2\pi(3000) = 18.85 \text{ K rad/sec.}$$

$$\omega_c = \frac{1}{RC} \rightarrow \text{choose } R = 4.7 \text{ k}\Omega$$

$$C = \frac{1}{R\omega_c} = 11.29 \text{ nF}$$

3. Band-Pass Filter BPF:-

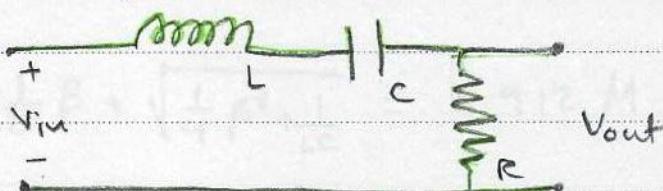

$$\tilde{H} = \frac{\tilde{V}_{out}}{\tilde{V}_{in}} = A_v = \frac{R}{R + Ls + \frac{1}{Cs}} = \frac{sRC}{s^2RC + Ls^2 + 1}$$


$$|\tilde{A}_v| = \frac{wRC}{\sqrt{(1-w^2LC)^2 + w^2R^2C^2}}$$

$$* w_b = \frac{1}{\sqrt{LC}}; \text{ it's called}$$

as $w \rightarrow 0 \Rightarrow |\tilde{A}_v| \approx wRC \rightarrow 0$

as $w \rightarrow \infty \Rightarrow |\tilde{A}_v| \approx \frac{R}{wL} \rightarrow 0$

the center freq.
sometimes

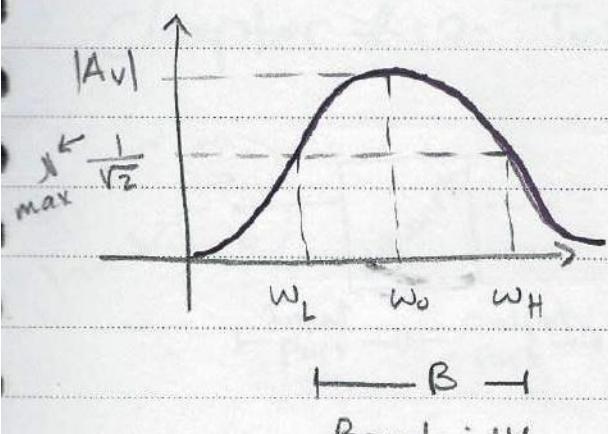

$$B = w_H - w_L$$

$$\rightarrow w_L = +\frac{R}{2L} + \frac{\sqrt{R^2 C^2 + 4LC}}{2LC}$$

$$\rightarrow w_H = +\frac{R}{2L} + \frac{\sqrt{R^2 C^2 + 4LC}}{2LC}$$

$$\beta = \frac{R}{L}$$

$$\therefore w_L = -\frac{\beta}{2} + \sqrt{\frac{1}{4}\beta^2 + \frac{1}{LC}}$$

$$w_H = +\frac{\beta}{2} + \sqrt{\frac{1}{4}\beta^2 + \frac{1}{LC}}$$

Ex:- design a Band pass filter characterized by a bandwidth of 1 MHz, $f_H = 1.1 \text{ MHz}$,

Sol:- $\beta = 2\pi(1 \times 10^6) = 6.283 \times 10^6 \text{ rad/s}$ $\beta = f_H - f_L$

$$w_L = 2\pi f_L = 6.283 \times 10^6 \text{ rad/s}$$

$$w_H = 2\pi f_H = 2\pi (1.1 \times 10^6) = 6.912 \text{ Mrad/s}$$


$$+\frac{1}{2}\beta + \sqrt{\frac{1}{4}\beta^2 + \frac{1}{LC}} = 6.912 \text{ M}$$

$$\therefore \frac{1}{LC} = 4.343 \times 10^{12}$$


let $L = 1 \text{ H}$ (arbitrarily)

$$C = 230.3 \text{ fF}$$
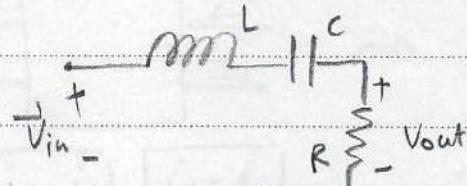
$$R = 6.283 \mu\Omega \quad (\beta = \frac{R}{L})$$





Chapter #17: Two-Ports Networks:

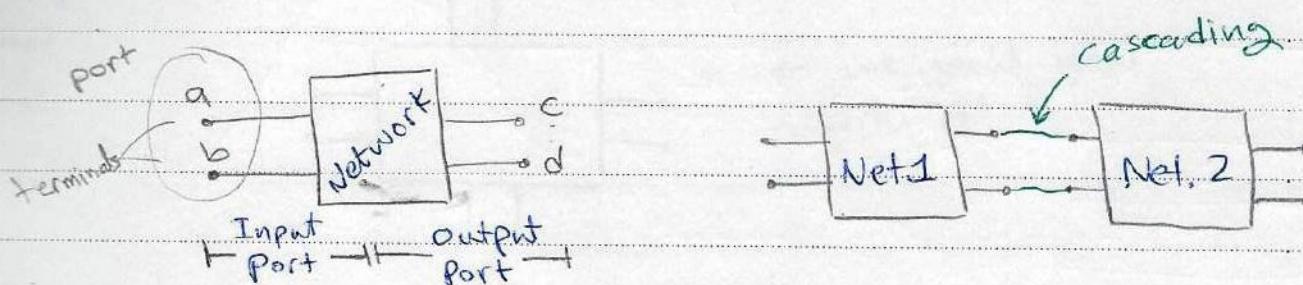


• Parameters.


→ Single-Port Network:

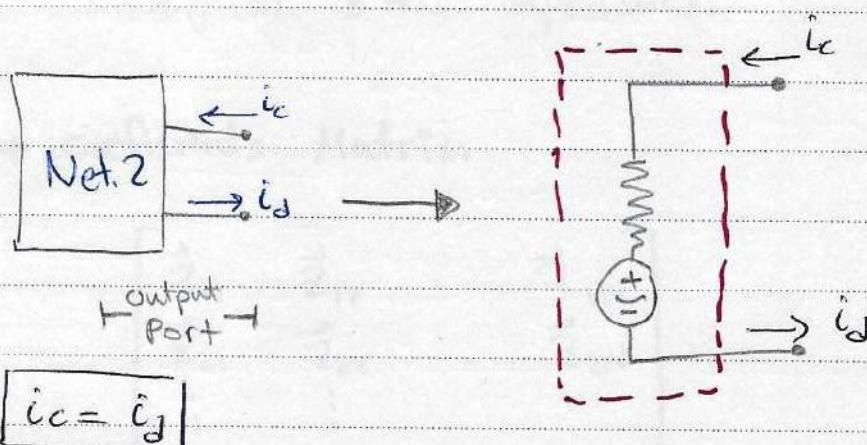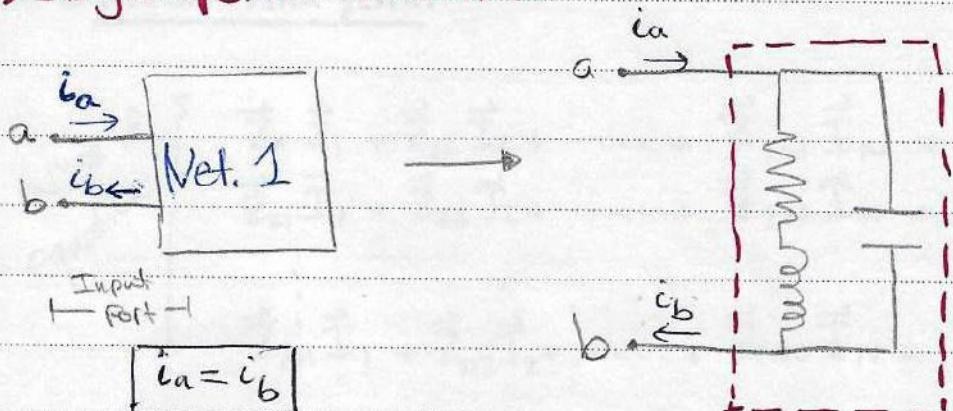

→ two-Port Network:

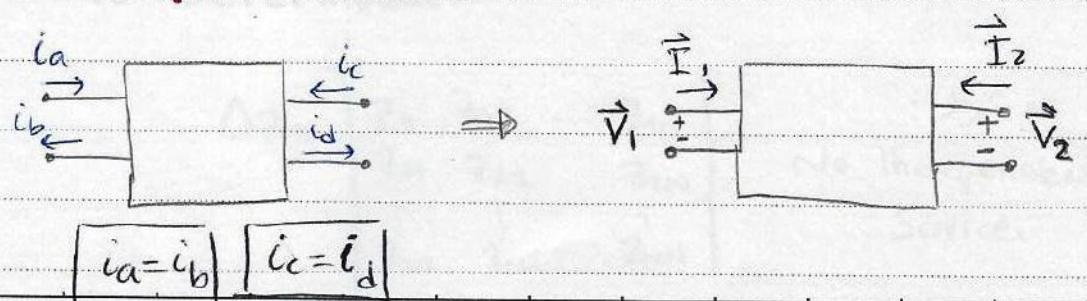

→ Multi-port Network:

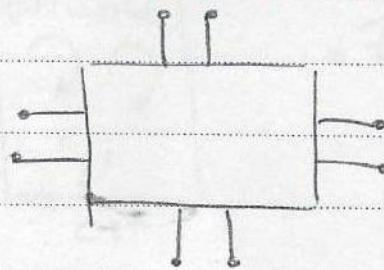

← we won't deal with it!

→ back to the single-port network:-

• Mesh Analysis:

$$\left. \begin{array}{l} \text{of } \\ \text{equations} \end{array} \right\} \begin{array}{l} \vec{Z}_{11} \vec{I}_1 + \vec{Z}_{12} \vec{I}_2 + \dots + \vec{Z}_{1N} \vec{I}_N = \vec{V}_1 \\ \vec{Z}_{21} \vec{I}_1 + \vec{Z}_{22} \vec{I}_2 + \dots + \vec{Z}_{2N} \vec{I}_N = \vec{V}_2 \\ \vdots \\ \vec{Z}_{N1} \vec{I}_1 + \vec{Z}_{N2} \vec{I}_2 + \dots + \vec{Z}_{NN} \vec{I}_N = \vec{V}_N \end{array}$$

$Z_{ij}(s)$ is the impedance.


• Coefficients Matrix:

$$\begin{bmatrix} \vec{Z}_{11} & \vec{Z}_{12} & \dots & \vec{Z}_{1N} \\ \vec{Z}_{21} & \vec{Z}_{22} & \dots & \vec{Z}_{2N} \\ \vdots & \vdots & & \vdots \\ \vec{Z}_{N1} & \vec{Z}_{N2} & \dots & \vec{Z}_{NN} \end{bmatrix}$$

→ determinant:

$$\Delta_Z = \begin{vmatrix} Z_{11} & Z_{12} & \dots & Z_{1N} \\ Z_{21} & Z_{22} & \dots & Z_{2N} \\ \vdots & \vdots & & \vdots \\ Z_{N1} & Z_{N2} & \dots & Z_{NN} \end{vmatrix}$$

: b/c *
No independent Source.

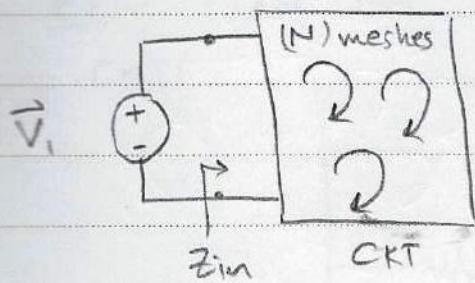

$$* \vec{Z}_{in} = \frac{\vec{V}_1}{I_1}$$

$$* \vec{V}_2 = \vec{V}_3 = \vec{V}_4 = \dots = \vec{V}_N = 0$$

Using cramer's rule:-


$$\vec{I}_1 = \frac{\begin{vmatrix} \vec{V}_1 & \vec{Z}_{12} & \vec{Z}_{13} & \dots & \vec{Z}_{1N} \\ 0 & \vec{Z}_{22} & \vec{Z}_{23} & \dots & \vec{Z}_{2N} \\ 0 & \vdots & \vdots & \ddots & \vdots \\ 0 & \vec{Z}_{N2} & \vec{Z}_{N3} & \dots & \vec{Z}_{NN} \end{vmatrix}}{\Delta Z}$$

$$\vec{I}_1 = \frac{\vec{V}_1 \Delta_{11}}{\Delta Z} \quad \text{minor}$$

$$\Rightarrow \vec{Z}_{in} = \frac{\vec{I}_1}{\vec{V}_1} = \frac{\Delta Z}{\Delta_{11}}$$

$$\Delta_{11} = \begin{vmatrix} \vec{Z}_{22} & \vec{Z}_{23} & \dots & \vec{Z}_{2N} \\ \vec{Z}_{32} & \vec{Z}_{33} & \dots & \vec{Z}_{3N} \\ \vdots & \vdots & \ddots & \vdots \\ \vec{Z}_{N2} & \vec{Z}_{N3} & \dots & \vec{Z}_{NN} \end{vmatrix}$$

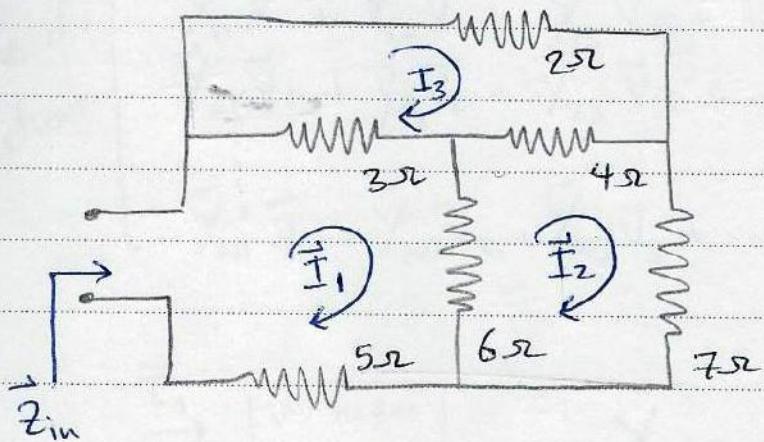ex:- find the input impedance for the following
CKT:



$$\begin{aligned} 14\vec{I}_1 - 6\vec{I}_2 - 3\vec{I}_3 &= \vec{V}_1 \quad \vec{V}_2 = 0 = \vec{V}_3 = \dots = \vec{V}_N \\ -6\vec{I}_1 + 17\vec{I}_2 - 4\vec{I}_3 &= 0 \\ -3\vec{I}_1 - 4\vec{I}_2 + 9\vec{I}_3 &= 0 \end{aligned}$$

$$\Delta Z = \begin{vmatrix} 14 & -6 & -3 \\ -6 & 17 & -4 \\ -3 & -4 & 9 \end{vmatrix} = 1297$$


$$\Delta_{11} = \begin{vmatrix} 17 & -4 \\ -4 & 9 \end{vmatrix} = 137$$

$$\vec{Z}_{in} = \frac{\Delta Z}{\Delta_{11}} = \frac{1297}{137} = 9.467 \Omega$$

Nodal analysis

$\left(\begin{array}{l} \text{# of} \\ \text{equations} \end{array} \right)$

$$\left\{ \begin{array}{l} \vec{Y}_{11}\vec{V}_1 + \vec{Y}_{12}\vec{V}_2 + \vec{Y}_{13}\vec{V}_3 + \dots + \vec{Y}_{1N}\vec{V}_N = \vec{I}_1 \\ \vec{Y}_{21}\vec{V}_1 + \vec{Y}_{22}\vec{V}_2 + \vec{Y}_{23}\vec{V}_3 + \dots + \vec{Y}_{2N}\vec{V}_N = \vec{I}_2 \\ \vdots \\ \vec{Y}_{N1}\vec{V}_1 + \vec{Y}_{N2}\vec{V}_2 + \vec{Y}_{N3}\vec{V}_3 + \dots + \vec{Y}_{NN}\vec{V}_N = \vec{I}_N \end{array} \right.$$

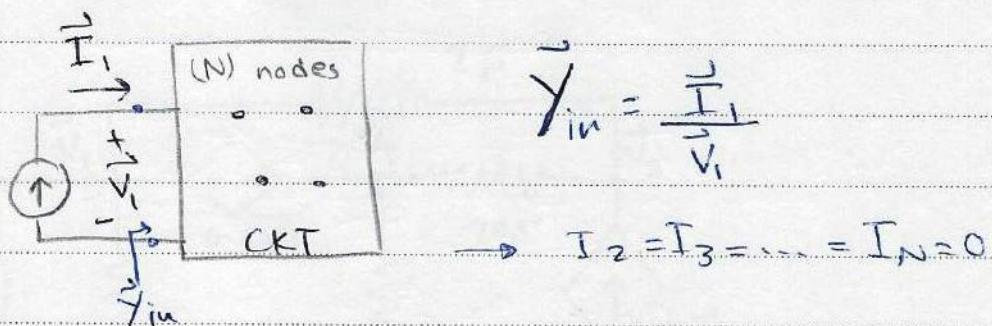

$$\vec{Y}_{1in} = \begin{bmatrix} \vec{Y}_{11} & \vec{Y}_{12} & \dots & \vec{Y}_{1N} \\ \vec{Y}_{21} & \vec{Y}_{22} & & \vec{Y}_{2N} \\ \vdots & & \ddots & \\ \vec{Y}_{N1} & \vec{Y}_{N2} & \dots & \vec{Y}_{NN} \end{bmatrix}$$

$$\Delta Y = \begin{vmatrix} \vec{Y}_{11} & \vec{Y}_{12} & \dots & \vec{Y}_{1N} \\ \vec{Y}_{21} & \vec{Y}_{22} & \dots & \vec{Y}_{2N} \\ \vdots & & \ddots & \\ \vec{Y}_{N1} & \vec{Y}_{N2} & \dots & \vec{Y}_{NN} \end{vmatrix}$$


from cramer,

$$\vec{V}_1 = \frac{\begin{vmatrix} \vec{I}_1 & \vec{Y}_{12} & \vec{Y}_{13} & \dots & \vec{Y}_{1N} \\ 0 & \vec{Y}_{22} & \vec{Y}_{23} & \dots & \vec{Y}_{2N} \\ \vdots & & \ddots & & \\ 0 & \vec{Y}_{N2} & \vec{Y}_{N3} & \dots & \vec{Y}_{NN} \end{vmatrix}}{\Delta Y}$$

$$Y_{1in} = \frac{\Delta Y}{\Delta Y_{11}}$$

$$\Delta_{Y_{11}} = \begin{vmatrix} Y_{22} & Y_{23} & \dots & Y_{2N} \\ Y_{32} & Y_{33} & \dots & Y_{3N} \\ \vdots & \vdots & \ddots & \vdots \\ Y_{N2} & Y_{N3} & \dots & Y_{NN} \end{vmatrix}$$

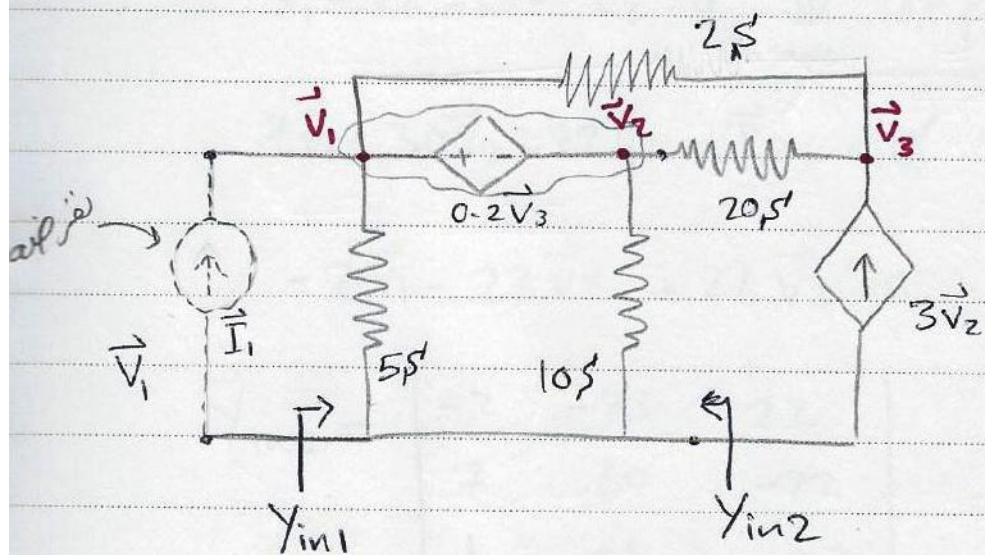ex: find input admittance Y_{in1} & Y_{in2}



$$V_1 - V_2 = 0.2 V_3 \quad \dots \textcircled{1} \quad \text{from the super node}$$

$$5\vec{V}_1 + 2\vec{V}_1 - 2\vec{V}_3 + 10\vec{V}_2 + 20\vec{V}_2 - 20\vec{V}_3 = \vec{I}_1$$

$$\hookrightarrow [7\vec{V}_1 + 30\vec{V}_2 - 22\vec{V}_3 = \vec{I}_1] \quad \dots \textcircled{2}$$


$$2\vec{V}_3 - 2\vec{V}_1 + 20\vec{V}_3 - 20\vec{V}_2 - 3\vec{V}_2 = 0$$

$$\hookrightarrow [-2\vec{V}_1 - 23\vec{V}_2 + 22\vec{V}_3 = 0] \quad \dots \textcircled{3}$$

$$\vec{Y}_{in1} = \frac{\begin{vmatrix} 7 & 30 & -22 \\ -2 & -23 & 22 \\ 1 & -1 & -0.2 \end{vmatrix}}{\begin{vmatrix} -23 & 22 \\ -1 & -0.2 \end{vmatrix}} = 10.684 \text{ S}$$

\vec{Y}_{in2} :
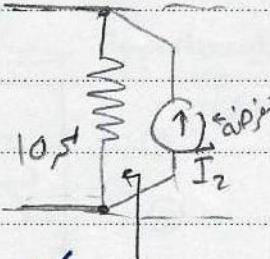
$$\vec{V}_1 - \vec{V}_2 - 0.2 \vec{V}_3 = 0 \quad \textcircled{1} \quad 10\Omega \text{ same}$$



$$7\vec{V}_1 + 30\vec{V}_2 - 22\vec{V}_3 = \vec{I}_2 \quad \textcircled{2} \quad Y_{in2}$$


$$-2\vec{V}_1 - 23\vec{V}_2 + 22\vec{V}_3 = 0 \quad \textcircled{3}'$$

$$\vec{Y}_{in2} = \frac{\begin{vmatrix} -2 & -23 & 22 \\ 7 & 30 & -22 \\ 1 & -1 & -0.2 \end{vmatrix}}{\begin{vmatrix} -2 & 22 \\ 1 & -0.2 \end{vmatrix}} = 13.1574 \text{ S} = [25]$$

9/5/2013

Admittance Parameters (Y-parameters)

or Short CKT admittance par.

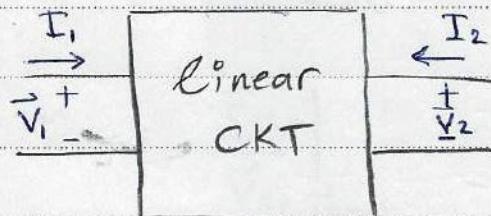

By Super position:-

	Proportionality constants	
$\vec{I}_1 = y_{11} \vec{V}_1 + y_{12} \vec{V}_2$...①	$[A/V]$
$\vec{I}_2 = y_{21} \vec{V}_1 + y_{22} \vec{V}_2$...②	

$[y_{ij}] = A/V = S$; short CKT admittance parameters
of Y-parameters

deriving the eq. $\frac{\vec{I}_1}{\vec{V}_1} \left| \begin{array}{cc} y_{11} & y_{12} \\ y_{21} & y_{22} \end{array} \right| \frac{\vec{I}_2}{\vec{V}_2}$

 $I = \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix}, V = \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix}$
 $Y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$

$I = Y \cdot V$

$\begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix} \rightarrow \vec{I}_1 = y_{11} \vec{V}_1 + y_{12} \vec{V}_2 \dots \text{①}$
 $\vec{I}_2 = y_{21} \vec{V}_1 + y_{22} \vec{V}_2 \dots \text{②}$

* finding Y-parameters:-

From eq 1:-

- $y_{11} = \frac{\vec{I}_1}{\vec{V}_1} \Big|_{\vec{V}_2=0}$; the short circuit input admittance
output is short-circuited

from eq ②:


$$\bullet \quad y_{21} = \left| \frac{\vec{I}_2}{\vec{V}_1} \right|_{\vec{V}_2=0} ; \text{ short CKT transfer admittance.}$$

$$\bullet \quad y_{12} = \left| \frac{\vec{I}_1}{\vec{V}_2} \right|_{\vec{V}_1=0} ; \text{ short CKT transfer admittance.}$$


$$\bullet \quad y_{22} = \left| \frac{\vec{I}_2}{\vec{V}_2} \right|_{\vec{V}_1=0} ; \text{ short CKT output admittance.}$$

Input is short-circuited

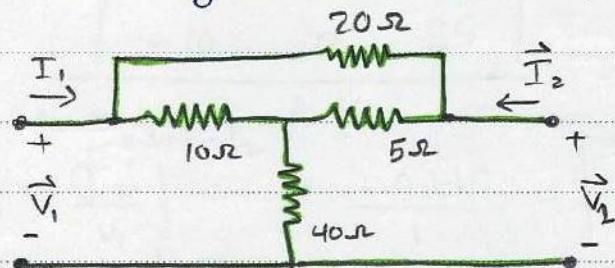ex:- Find the short CKT admittance parameters for the following resistive 2-ports network



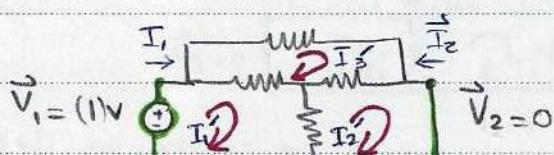Solution to find y_{11} , the output must be short-circuited i.e. $V_2=0$, then we assume a voltage source at the input terminals ($\vec{V}_1=(1)V$)



$$I_1 = I_1'$$

$$I_2 = -I_2' \quad \text{②}$$

mesh equations:-

$$50 I_1' - 40 I_2' - 10 I_3' = \vec{V}_1 \quad \text{①}$$

$$-40 I_1' + 45 I_2' - 5 I_3' = 0 \quad \text{②}$$

$$-10 I_1' - 5 I_2' + 35 I_3' = 0 \quad \text{③}$$

$\begin{bmatrix} 1 & -40 & -10 \\ -40 & 45 & -5 \\ -10 & -5 & 35 \end{bmatrix} \begin{bmatrix} I_1' \\ I_2' \\ I_3' \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix}$ (V matrix)

using cramer's rule:-

$$\bullet I_1' = \frac{\begin{vmatrix} 1 & -40 & -10 \\ 0 & 45 & -5 \\ 0 & -5 & 35 \end{vmatrix}}{\Delta Y} = 0.1192 A$$


$$\Delta Y \rightarrow \begin{vmatrix} 50 & -40 & -10 \\ -40 & 45 & -5 \\ -10 & -5 & 35 \end{vmatrix}$$

$$\rightarrow Y_{11} = \frac{I_1'}{\Delta Y} \Big|_{V_2=0} = \boxed{0.1192 S'}$$

$$\bullet I_2' = \frac{\begin{vmatrix} 50 & 1 & -10 \\ -40 & 0 & -5 \\ -10 & 0 & 35 \end{vmatrix}}{\Delta Y} = 0.1115 A$$

$$\rightarrow Y_{21} = \frac{I_2'}{\Delta Y} \Big|_{V_2=0} = \frac{-0.1115}{1} = \boxed{-0.1115 S'}$$

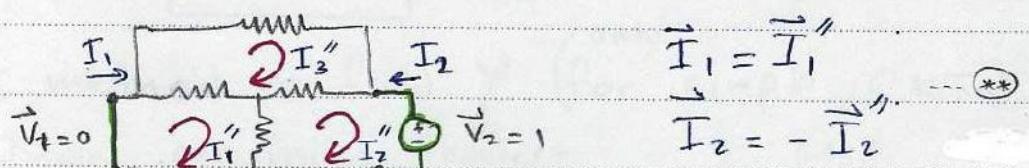* let $V_1 = 0$ (short CKT) & $V_2 = (1)V$



mesh equations:-

$$50 I_1'' - 40 I_2'' - 10 I_3'' = 0 \quad \text{--- (1')}$$

$$-40 I_1'' + 45 I_2'' - 5 I_3'' = -1 \quad \text{--- (2')}$$

$$-10 I_1'' - 5 I_2'' + 35 I_3'' = 0 \quad \text{--- (3')}$$

$$\bullet \quad I_1'' = \frac{\begin{vmatrix} 0 & -40 & -10 \\ -1 & 45 & -5 \\ 0 & -5 & 35 \end{vmatrix}}{\Delta Y} = -0.1115 \text{ S}$$


$$\rightarrow y_{12} = \frac{\vec{I}_2}{\vec{V}_2} \Big|_{\vec{V}_1=0} = \frac{\vec{I}_1''}{1} = \boxed{-0.1115 \text{ S}}$$

* Note:

when $y_{12} = y_{21}$, it's called a "bilateral CKT"

$$\bullet \quad I_2'' = \frac{\begin{vmatrix} 50 & 0 & -10 \\ -40 & -1 & -5 \\ -10 & 0 & 35 \end{vmatrix}}{\Delta Y} = -0.1269 \text{ A}$$

$$\rightarrow y_{22} = \frac{\vec{I}_2}{\vec{V}_2} \Big|_{\vec{V}_1=0} = \frac{-\vec{I}_2''}{1} = \boxed{0.1269 \text{ S}}$$

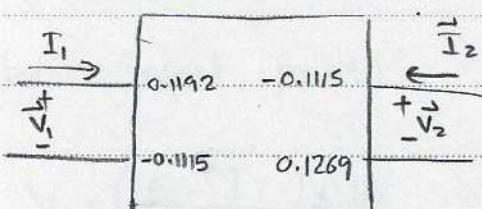


* another method to find \mathbf{Y} (for simple CKTs) ^{only}

→ using Nodal analysis: \approx convert
Nodal equations: to admittances

$$0.15 \vec{V}_1 - 0.05 \vec{V}_2 - 0.1 \vec{V}_3 = \vec{I}_1 \dots (1)$$

$$-0.05 \vec{V}_1 - 0.25 \vec{V}_2 + 0.2 \vec{V}_3 = \vec{I}_2 \dots (2)$$
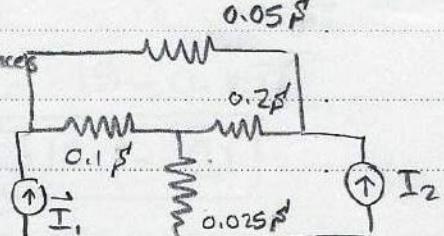
$$-0.1 \vec{V}_1 - 0.2 \vec{V}_2 + 0.325 \vec{V}_3 = 0 \dots (3)$$



3 eq \rightarrow 2 eq

$$\text{from (3)} \quad \vec{V}_3 = \frac{0.1 \vec{V}_1}{0.325} + \frac{0.2 \vec{V}_2}{0.325}$$

Substitute V_3 in ① & ②


$$\text{in ①: } \vec{I}_1 = (0.1192) \vec{V}_1 + (-0.1115) \vec{V}_2$$

y_{11} y_{12}

$$\text{in ②: } \vec{I}_2 = (-0.1115) \vec{V}_1 + (0.1269) \vec{V}_2$$

y_{21} y_{22}

* but, how to use Y-parameters?

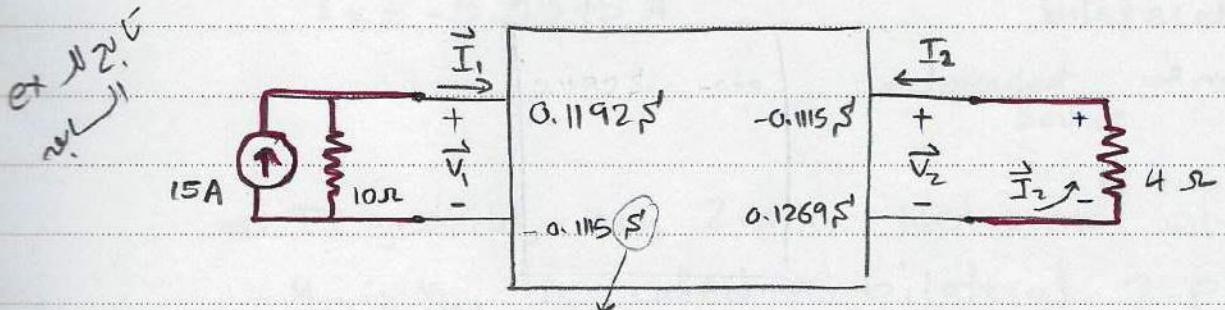

Y-parameters معرفة في وحدة جماعية

$$\begin{cases} 0.1192 \vec{V}_1 - 0.1115 \vec{V}_2 = \vec{I}_1 \\ -0.1115 \vec{V}_1 + 0.1269 \vec{V}_2 = \vec{I}_2 \end{cases}$$

Equation ①: $\vec{I}_1 = 0.1192 \vec{V}_1 - 0.1115 \vec{V}_2$
Equation ②: $\vec{I}_2 = -0.1115 \vec{V}_1 + 0.1269 \vec{V}_2$

• from the input part:

$$V_1 = (15 - \vec{I}_1) \times 10$$

$$* \vec{I}_1 = 15 - 0.1 \vec{V}_1 \quad \text{--- ③}$$

→ Sub. in ①

$$0.1192 \vec{V}_1 - 0.1115 \vec{V}_2 = 15 - 0.1 \vec{V}_1$$

$$0.2192 \vec{V}_1 - 0.1115 \vec{V}_2 = 15 \quad \text{--- ④'}$$

• from the output part:

$$\vec{V}_2 = -4 \vec{I}_2$$

$$* \vec{I}_2 = -0.25 \vec{V}_2 \quad \text{--- ⑤}$$

→ sub. in ④'

$$-0.1115 \vec{V}_1 + 0.1269 \vec{V}_2 = -0.25 \vec{V}_2$$

$$-0.1115 \vec{V}_1 + 0.3769 \vec{V}_2 = 0 \quad \text{--- ⑤'}$$

now I have 2 equations with 2 unknowns :-

Solve ① & ② for v_1, v_2 :-

$$\rightarrow \vec{v}_1 = 80.55 \text{ V}$$

* In this ex, $y_{12} = y_{21}$

$$\vec{v}_2 = 23.83 \text{ V}$$

: it's a bilateral CKT

Plug in ③ & ④

* & resistive CKTs

$$\rightarrow I_1 = 6.945 \text{ A}$$

are always

$$I_2 = -5.9575 \text{ A}$$

bilateral!

* dependent independent source

Source


\Rightarrow In general, any 2-port Network with $y_{12} = y_{21}$ is called a bilateral 2-port Network!

11/5/2013

Bilateral Networks:

محاضرة
مقدمة
لدورات

$$y_{12} = y_{21}$$

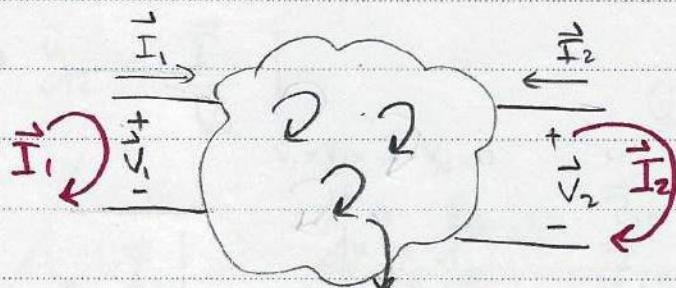

Multi-meshes

$$\vec{z}_{11} \vec{I}_1 + \vec{z}_{12} \vec{I}_2 + \vec{z}_{13} \vec{I}_3 + \dots + \vec{z}_{1N} \vec{I}_N = \vec{V}_1 \quad (1)$$

$$\vec{z}_{21} \vec{I}_1 + \vec{z}_{22} \vec{I}_2 + \vec{z}_{23} \vec{I}_3 + \dots + \vec{z}_{2N} \vec{I}_N = -\vec{V}_2 \quad (2)$$

$$\vec{z}_{31} \vec{I}_1 + \vec{z}_{32} \vec{I}_2 + \vec{z}_{33} \vec{I}_3 + \dots + \vec{z}_{3N} \vec{I}_N = \vec{V}_3 \quad (3)$$

$$\vdots$$

$$\vec{z}_{N1} \vec{I}_1 + \vec{z}_{N2} \vec{I}_2 + \vec{z}_{N3} \vec{I}_3 + \dots + \vec{z}_{NN} \vec{I}_N = \vec{V}_N \quad (N)$$

* assume, it's a one-port network : $V_2 = V_3 = V_4 = \dots = V_N = 0$

$$\rightarrow \vec{I}_1 = \frac{\vec{V}_1 | D_{11}}{\Delta Z} \rightarrow \vec{Z}_{in} | = \frac{\Delta Z}{\Delta Z} \\ \vec{V}_2 = \vec{V}_3 = \dots = \vec{V}_N = 0$$

$$y_{11} = \left. \frac{\vec{I}_1}{\vec{V}_1} \right|_{V_2=0} = \boxed{\frac{\Delta_{11}}{\Delta Z}} = Y_{in} = \frac{1}{Z_{in}}$$

$$y_{22} = \left. \frac{\vec{I}_2}{\vec{V}_2} \right|_{V_1=V_3=V_4=\dots=V_N=0} \rightarrow ? \boxed{y_{22} = \frac{\Delta_{22}}{\Delta Z}}$$

column 2 & row 2 used

$$\vec{I}_2 | = \frac{\begin{vmatrix} Z_{11} & 0 & Z_{13} & \dots & Z_{1N} \\ Z_{21} & -V_2 & Z_{23} & \dots & Z_{2N} \\ \vdots & 0 & \vdots & & \vdots \\ Z_{N1} & 0 & Z_{N3} & \dots & Z_{NN} \end{vmatrix}}{\Delta Z} = \frac{-(-\vec{V}_2) \Delta_{22}}{\Delta Z}$$

$$y_{12} = \left. \frac{\vec{I}_1}{\vec{V}_2} \right|_{V_1=V_3=\dots=V_N=0} = \frac{\Delta_{21}}{\Delta Z}$$

(1) الحود (2) الحود

$$\vec{I}_1 | = \frac{\begin{vmatrix} 0 & \vec{Z}_{12} & \dots & \vec{Z}_{1N} \\ 0 & -V_2 & \vec{Z}_{22} & \dots & \vec{Z}_{2N} \\ \vdots & 0 & \vec{Z}_{N2} & \dots & \vec{Z}_{NN} \end{vmatrix}}{\Delta Z} = \frac{-(-\vec{V}_2) \Delta_{21}}{\Delta Z}$$

Plug in y_{12} :

$$\boxed{y_{12} = \frac{\Delta_{21}}{\Delta Z}} \rightarrow \Delta_{21} = \begin{vmatrix} \vec{Z}_{12} & \vec{Z}_{13} & \dots & \vec{Z}_{1N} \\ \vec{Z}_{32} & \vec{Z}_{33} & \dots & \vec{Z}_{3N} \\ \vdots & \vec{Z}_{42} & \vec{Z}_{43} & \dots & \vec{Z}_{4N} \\ \vec{Z}_{N2} & \vec{Z}_{N3} & \dots & \vec{Z}_{NN} \end{vmatrix}$$

$$y_{21} = \frac{I_2}{V_1}$$

$$\vec{V}_2 = \vec{V}_3 = \dots = \vec{V}_N = 0$$

$$\rightarrow I_2 = \frac{\Delta_{12}}{\Delta_2} = \frac{\begin{vmatrix} Z_{11} & \vec{V}_1 & \vec{Z}_{13} & \dots & Z_{1N} \\ Z_{21} & 0 & Z_{23} & \vdots & Z_{2N} \\ \vdots & \vdots & \vdots & \vdots & \vdots \\ Z_{N1} & 0 & Z_{N3} & \vdots & Z_{NN} \end{vmatrix}}{\Delta_2} = \frac{V_1 \Delta_{12}}{\Delta_2}$$

Plug in y_{21} :

$$y_{21} = \frac{\Delta_{12}}{\Delta_2} \rightarrow \Delta_{12} = \begin{vmatrix} \vec{Z}_{21} & \vec{Z}_{23} & Z_{24} & \dots & Z_{2N} \\ Z_{31} & \vec{Z}_{33} & Z_{34} & \dots & Z_{3N} \\ \vdots & \vdots & \vdots & \vdots & \vdots \\ Z_{N1} & Z_{N3} & Z_{N4} & \dots & Z_{NN} \end{vmatrix}$$

since it's bilateral

$$\therefore y_{12} = y_{21}$$

$$\boxed{\frac{\Delta_{12}}{\Delta_2} = \frac{\Delta_{21}}{\Delta_2}}$$


$$\Delta_{12} = \Delta_{21} \rightarrow \therefore \boxed{Z_{ij} = Z_{ji}} \quad \begin{matrix} \text{after} \\ \text{transposing} \\ \Delta_{21} \end{matrix}$$

* if this is true for an element, it's called "a bilateral element", and if all the elements in the CKT are bilateral, then it's called a "bilateral CKT".


* Reciprocity Theorem:

- In any linear, Passive, bilateral network:-

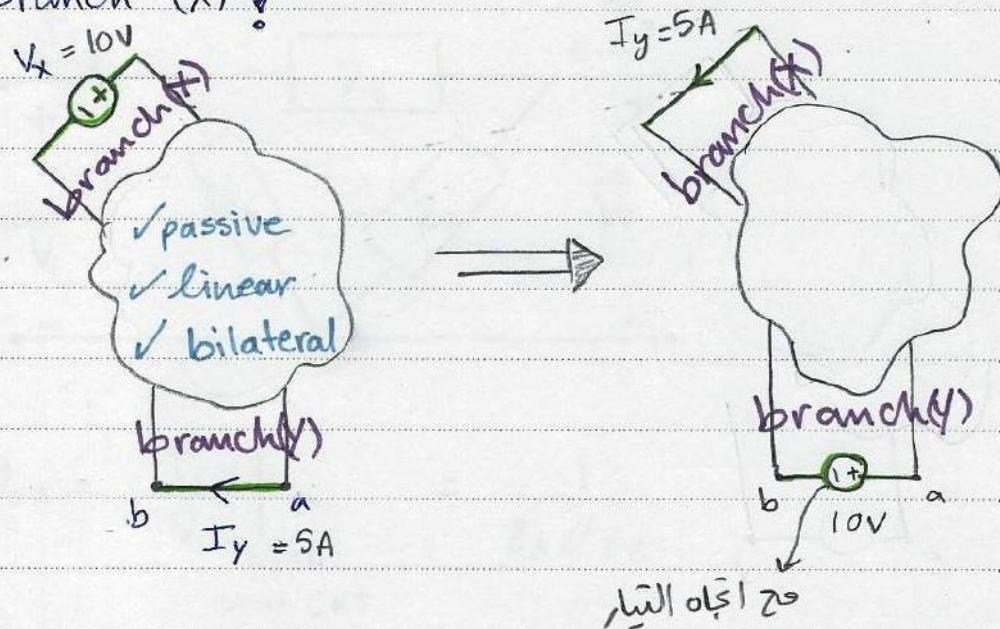
1. if the single voltage source (V_x) in branch (X) produces the current response (I_y) in branch (Y), then the removal of (V_x) from branch (X) and its insertion in branch(Y) will produce the current response \vec{I}_y in branch (X) !



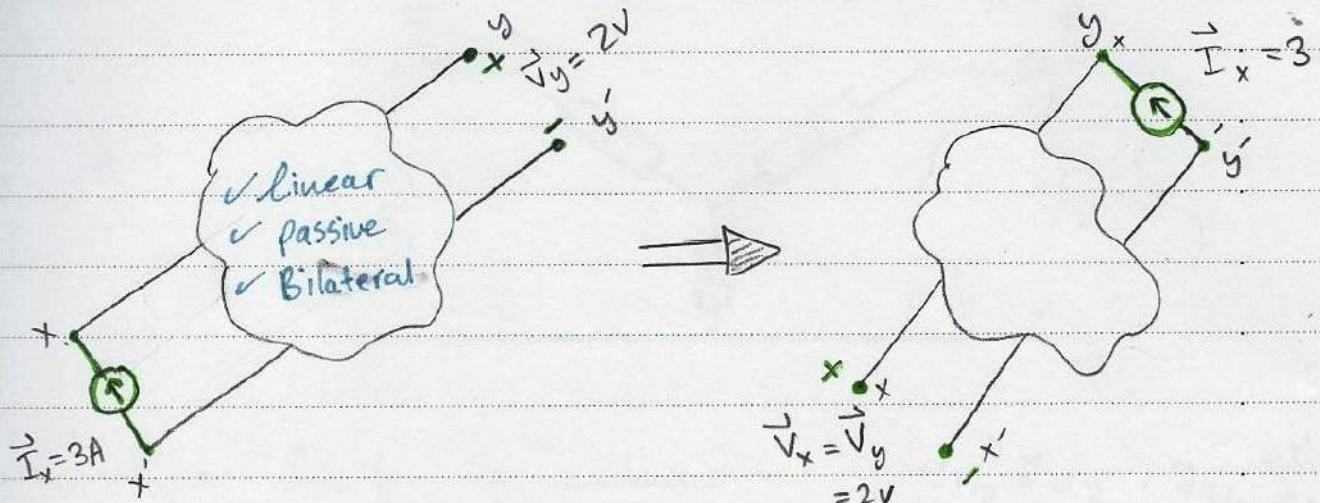2. if the single current source (I_x) between nodes $x \& x'$ produces the voltage response \vec{V}_x between nodes $y \& y'$, then the removal of the current source from nodes $x \& x'$ and its insertion between nodes $y \& y'$, will produce the voltage V_y between $x \& x'$



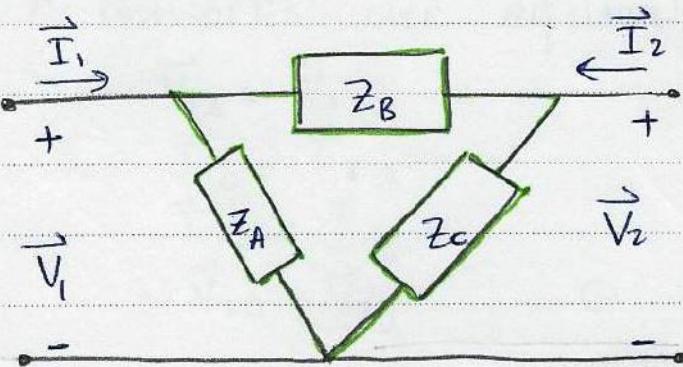$\Delta \leftrightarrow Y$ transformation!



$$Y_{11\Delta} = \left. \frac{\vec{I}_1}{V_1} \right|_{V_2=0} = \frac{1}{Z_A // Z_B}$$

Short CKT

$$Y_{12\Delta} = \left. \frac{\vec{I}_1}{V_2} \right|_{V_1=0} = -\frac{1}{Z_B + Z_C}$$


$$Y_{21\Delta} = \left. \frac{\vec{I}_2}{V_1} \right|_{V_2=0} = -\frac{1}{Z_A + Z_B}$$

$$\begin{aligned} I_1 &= -\frac{I_2 \cdot Z_C}{Z_B + Z_C} \\ \text{if } I_2 &= \frac{V_2}{Z_C} \end{aligned}$$

$$I_1 = -\frac{V_2}{Z_B + Z_C}$$

$$Y_{22\Delta} = \left. \frac{\vec{I}_2}{V_2} \right|_{V_1=0} = \frac{1}{Z_B // Z_C}$$
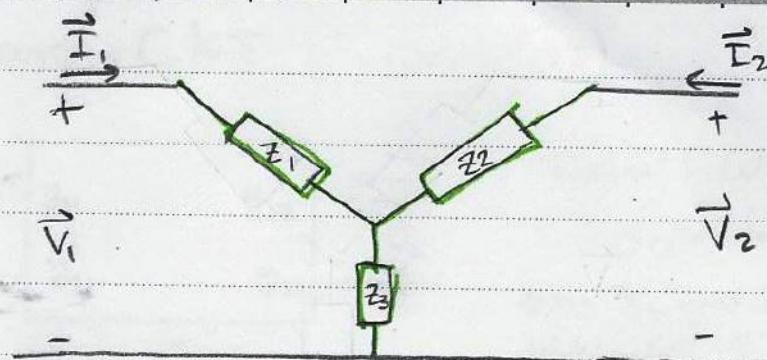
$$\therefore \frac{I_1}{V_1} = -\frac{1}{Z_B + Z_C}$$



$$Y_{11} = \left. \frac{\vec{I}_1}{\vec{V}_1} \right|_{V_2=0} = \frac{1}{z_2/z_3 + z_1}, \quad y_{12}, y_{21}, y_{22} \text{ are } \text{पूर्ण}$$

* Y & Δ networks are equivalent

$$\begin{aligned}\vec{V}_{1\Delta} &= \vec{V}_{1y} \\ \vec{I}_{1\Delta} &= \vec{I}_{1y} \\ \vec{I}_{2\Delta} &= \vec{I}_{2y} \\ \vec{V}_{2\Delta} &= \vec{V}_{2y} \quad \dots \text{④}\end{aligned}$$

For Δ:-

$$I_{1\Delta} = y_{11\Delta} \vec{V}_{1\Delta} + y_{12\Delta} \vec{V}_{2\Delta} \quad \dots 1$$

$$I_{2\Delta} = y_{21\Delta} \vec{V}_{1\Delta} + y_{22\Delta} \vec{V}_{2\Delta} \quad \dots 2$$

the same is done for (y)!


$$\hookrightarrow : \quad y_{11\Delta} = y_{11y}$$

$$y_{12\Delta} = y_{12y}$$

$$y_{21\Delta} = y_{21y}$$

$$y_{22\Delta} = y_{22y}$$

- Equivalent CKT (y -parameters)

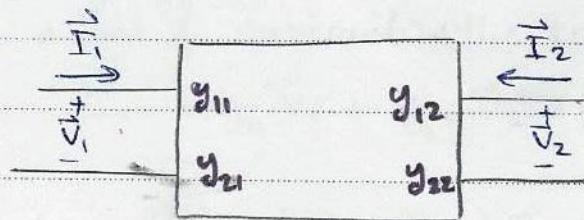

* المطلوب إيجاد المدار المكافئ

لـ y -parameters

الناتج المطلوب

يكون على الشكل

عما في المقدمة

حى المكافئ له!

for this network:-

$$\begin{cases} \vec{I}_1 = y_{11} \vec{V}_1 + y_{12} \vec{V}_2 & \dots ① \\ \vec{I}_2 = y_{21} \vec{V}_1 + y_{22} \vec{V}_2 & \dots ② \end{cases}$$

• The 1st equivalent CKT:-


- add & subtract the term ($y_{12}\vec{V}_1$) from ②

$$\vec{I}_2 = y_{21} \vec{V}_1 + y_{22} \vec{V}_2 + (y_{12} \vec{V}_1 - y_{12} \vec{V}_1)$$

$$\vec{I}_2 - (y_{21} - y_{12}) \vec{V}_1 = y_{12} \vec{V}_1 + y_{22} \vec{V}_2 \dots ②'$$

$\vec{I}_1 = y_{11} \vec{V}_1 + y_{12} \vec{V}_2 \dots ①'$ stays the same
from ① & ②' and from nodal analysis

the equivalent CKT will be:-

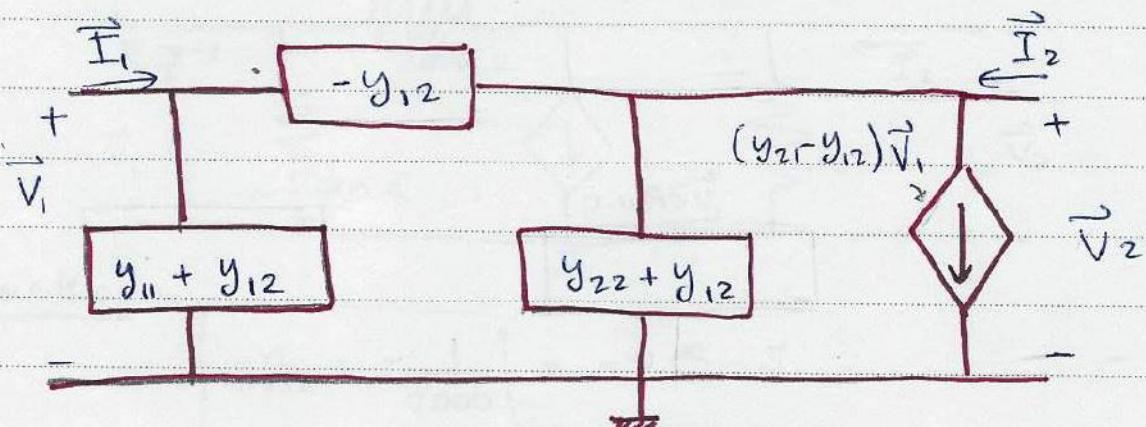

• 2nd equivalent CKT:-


- Add & subtract the term $(y_{21}\vec{V}_2)$ to ①

$$\vec{I}_1 = y_{11}\vec{V}_1 + y_{12}\vec{V}_2 + (y_{21}\vec{V}_2 - y_{21}\vec{V}_2)$$

$$\vec{I}_1 - (y_{12} - y_{21})\vec{V}_2 = y_{11}\vec{V}_1 + y_{22}\vec{V}_2 \dots \textcircled{1}$$

$$\vec{I}_2 = y_{21}\vec{V}_1 + y_{22}\vec{V}_2 \dots \textcircled{2} \text{ stays the same}$$


equ: CKT:-

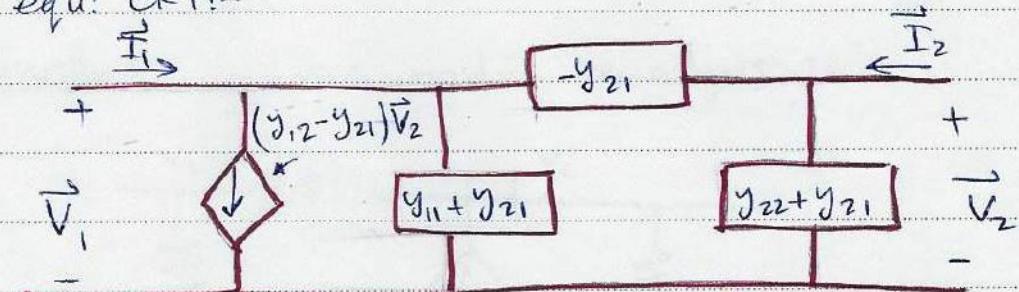


- for bilateral CKTs:-

$$y_{21} = y_{12}$$

current source will become an open CKT

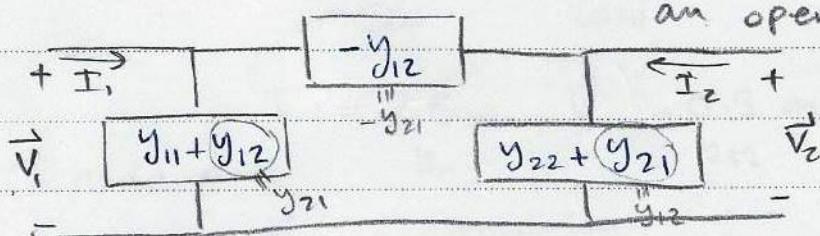

ex:- A) Determine the y-parameters :-

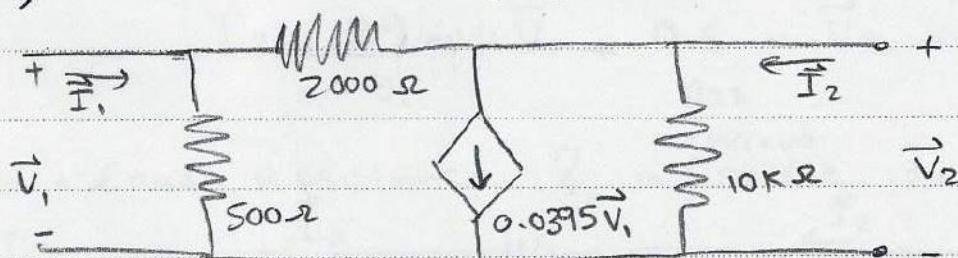

1st method :-

$$-y_{12} = -\frac{1}{2000} = -0.5 \text{ mS}$$

$$y_{11} + y_{12} = \frac{1}{500} \rightarrow y_{11} = 2.5 \text{ mS}$$


$$y_{22} + y_{12} = \frac{1}{10000} \Rightarrow y_{22} = 0.6 \text{ mS}$$

$$(y_{21} - y_{12}) = 0.0395 \Rightarrow y_{21} = 39 \text{ mS'}$$

$$\vec{I}_1 = 2.5 \text{ m} \vec{V}_1 - 0.5 \text{ m} \vec{V}_2 \quad \dots \textcircled{1}$$

$$\vec{I}_2 = 39 \text{ m} \vec{V}_1 + 0.6 \text{ m} \vec{V}_2 \quad \dots \textcircled{2}$$

2nd method, use nodal analysis :

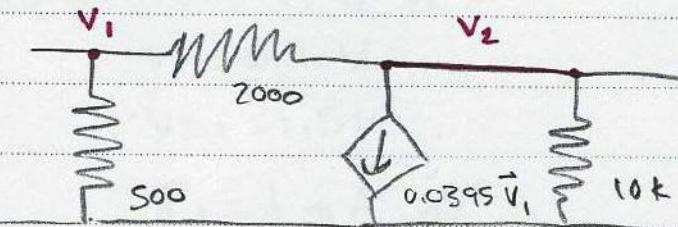

@ node 1:

$$\vec{I}_1 = \frac{\vec{V}_1}{500} + \frac{V_1 - V_2}{2000}$$

$$\vec{I}_1 = 2.5 \text{ m} \vec{V}_1 - 0.5 \text{ m} \vec{V}_2 \quad \dots \textcircled{1}$$


@ node 2:

$$\vec{I}_2 - 0.0395 \vec{V}_1 = \frac{\vec{V}_2}{10000} + \frac{\vec{V}_2 - \vec{V}_1}{2000}$$

$$\vec{I}_2 = 39 \text{ m} \vec{V}_1 + 0.6 \text{ m} \vec{V}_2 \quad \dots \textcircled{2}$$

B) add a load resistance & a ^{current} source to the previous

Ckt:-

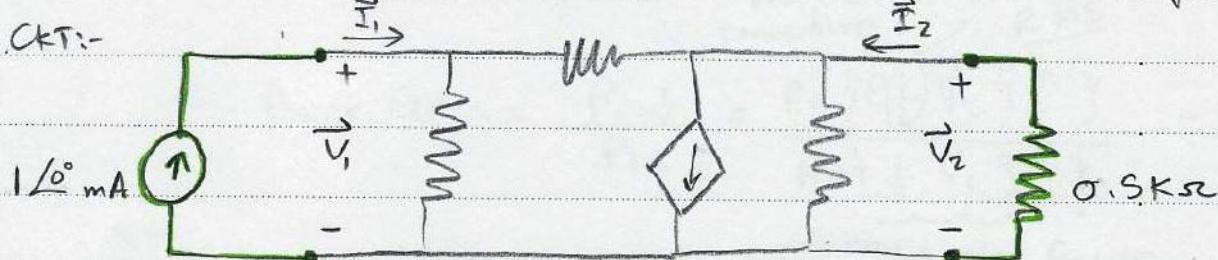

$$\vec{I}_1 = 110^\circ \text{ mA} \text{ for any value of } \vec{V}_1!$$

$$\vec{I}_2 = \frac{-\vec{V}_2}{0.5k} = -2m\vec{V}_2$$

Plug in ① & ②

$$1m = 2.5m\vec{V}_1 - 0.5m\vec{V}_2 \dots ①$$

$$-2m\vec{V}_2 = 39m\vec{V}_1 + 0.6m\vec{V}_2$$

$$39\vec{V}_1 + 2.6\vec{V}_2 = 0 \dots ②'$$

Solve for V_1 & V_2 :

$$V_1 = 0.1V$$

$$V_2 = -1.5V$$

$$I_1 = 1mA \times 0^\circ$$

$$I_2 = 3mA \times 0^\circ$$

c) find the Voltage Gain G_v

$$G_v = \frac{\vec{V}_2}{\vec{V}_1} = -15$$

$\frac{\text{output}}{\text{input}} = \text{Gain}$

d) find the Current Gain G_I

$$G_I = \frac{\vec{I}_2}{\vec{I}_1} = 3$$

e) Power Gain

from the
passive sign convention $\rightarrow R_{\text{MS}}$

$$\text{Power Gain} = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{P_{\text{in}} \left[\frac{1}{2} \vec{V}_2 \vec{I}_2^* \right]^2}{R_{\text{MS}} \underbrace{\left[\frac{1}{2} \vec{V}_1 \vec{I}_1^* \right]^2}_{\text{Complex Power}}} = 45$$

f) find the input impedance:-

$$Z_{in} = \frac{\vec{V}_1}{\vec{I}_1} = \frac{0.1}{1m} = 0.1 k\Omega$$

g) find the input impedance with the output short circuited: $(Z_{in}) = \frac{1}{y_{in}}$
 $\rightarrow V_2 = 0$


$$\left| Z_{in} \right| = \left| \frac{\vec{V}_1}{\vec{I}_1} \right| \quad V_2 = 0 \quad ?$$

$V_2 = 0$
 plug in ① $\rightarrow I_1 = 2.5m \vec{V}_1 + 0$

$$\frac{\vec{V}_1}{\vec{I}_1} = \frac{1}{2.5m} = 400 \Omega$$

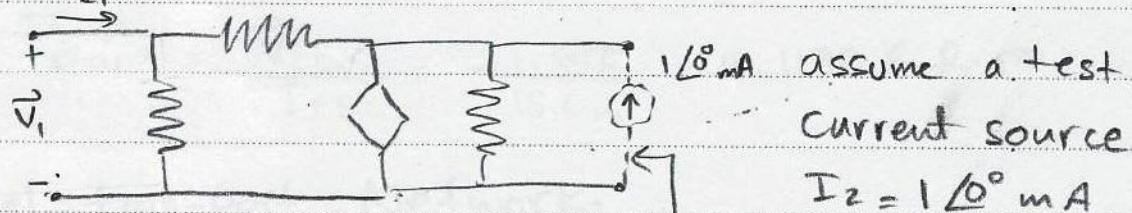h) the output impedance: (Z_{out}) (load source equivalent output)

1st method: $Z_{out} = \frac{\vec{V}_2}{\vec{I}_2}$



$$\vec{I}_1 = 0 \text{ (open CKT)}, \vec{I}_2 = 10^{\circ} \text{ mA}$$

plug in ① & ②

$$0 = 2.5 \vec{V}_1 - 0.5 \vec{V}_2 \dots ①'$$

$$1 = 39 \vec{V}_1 + 0.6 \vec{V}_2 \dots ②'$$

solve for V_1 & V_2


$$\vec{V}_2 = 0.1190 \text{ V}$$

$$\vec{V}_1 = 0.024 \text{ V}$$

$$Z_{out} = \frac{\vec{V}_2}{\vec{I}_2} = 0.1190 \text{ k}\Omega$$

OR 2nd method: $Z_{out} = Z_{Th} = -\frac{\vec{V}_{2oc}}{\vec{I}_{2sc}}$

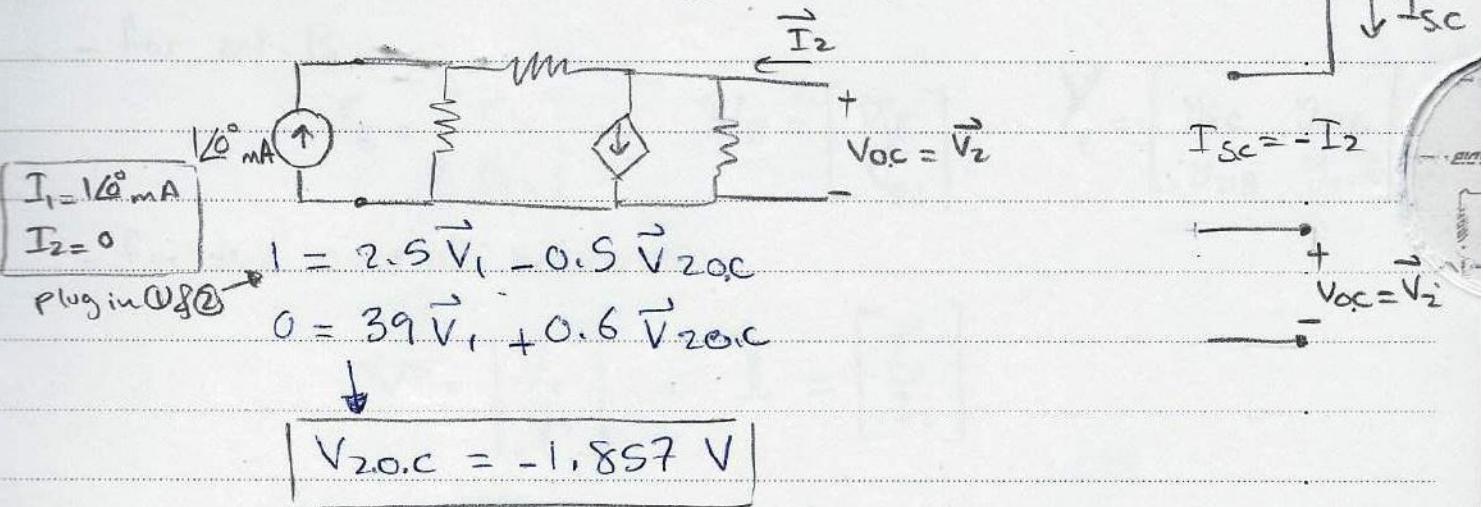assume a test current source $\vec{I}_1 = 1m10^6 A$




I_{2sc} ?

$$I = 2.5 \vec{V}_1 - 0 \quad \vec{V}_2 = 0 \text{ (s.c.)}$$

$$I_{2sc} = 39 \text{ mV}, +0 \Rightarrow \boxed{I_{2sc} = 15.6 \text{ mA}}$$

$$\vec{Z}_{out} = \frac{\vec{V}_{2oc}}{I_{2sc}} = \frac{-1.857}{15.6 \text{ mA}} = 0.1190 \text{ K} \Omega$$

• Parallel two-port Network:

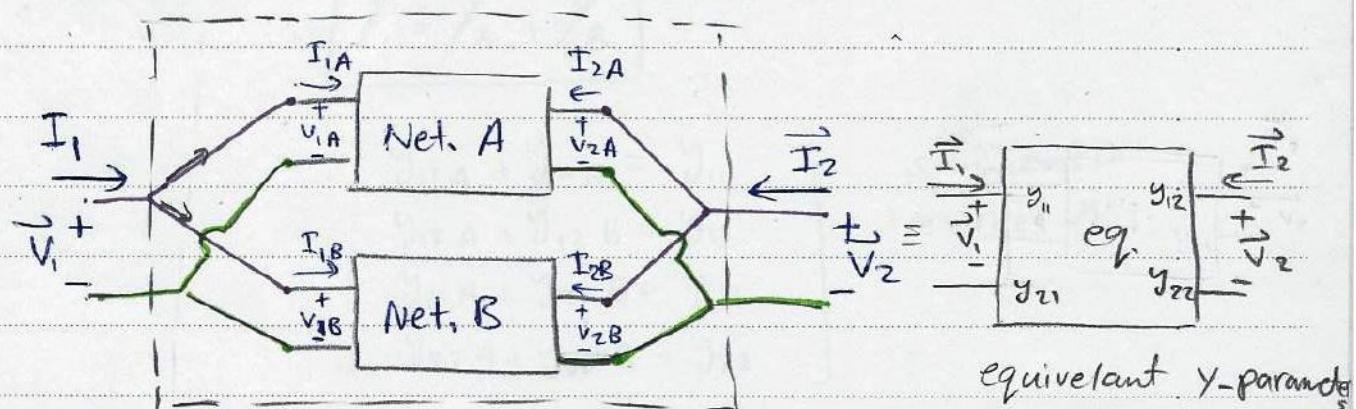

- $\vec{V}_1 = \vec{V}_{1B} = \vec{V}_{1A}$
 - $\vec{V}_2 = \vec{V}_{2A} = \vec{V}_{2B}$
 - $\vec{I}_1 = \vec{I}_{1A} + \vec{I}_{1B}$
 - $\vec{I}_2 = \vec{I}_{2A} + \vec{I}_{2B}$
- because the
are parallel

$$Y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

- for net. A:-

$$\mathbb{I}_A = \begin{bmatrix} \vec{I}_{1A} \\ \vec{I}_{2A} \end{bmatrix}, \quad \mathbb{V}_A = \begin{bmatrix} \vec{V}_{1A} \\ \vec{V}_{2A} \end{bmatrix}, \quad \mathcal{Y}_A = \begin{bmatrix} y_{11A} & y_{12A} \\ y_{21A} & y_{22A} \end{bmatrix}$$

- for net. B:-

$$\mathbb{I}_B = \begin{bmatrix} \vec{I}_{1B} \\ \vec{I}_{2B} \end{bmatrix}, \quad \mathbb{V}_B = \begin{bmatrix} \vec{V}_{1B} \\ \vec{V}_{2B} \end{bmatrix}, \quad \mathcal{Y}_B = \begin{bmatrix} y_{11B} & y_{12B} \\ y_{21B} & y_{22B} \end{bmatrix}$$

- for the overall network:-

$$\mathbb{V} = \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix}, \quad \mathbb{I} = \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix}$$

$$\mathbb{I}_A = \mathcal{Y}_A \mathbb{V}_A = \mathcal{Y}_A (\mathbb{V}) \rightarrow \mathbb{V}_A = \mathbb{V}_B = \mathbb{V}$$

$$\mathbb{I}_B = \mathcal{Y}_B \mathbb{V}_B = \mathcal{Y}_B \mathbb{V}$$


$$\begin{aligned} \mathbb{I} &= \mathbb{I}_A + \mathbb{I}_B = \mathcal{Y}_A \mathbb{V} + \mathcal{Y}_B \mathbb{V} \\ &= \mathbb{V} (\underbrace{\mathcal{Y}_A + \mathcal{Y}_B}_{\mathcal{Y}}) = \mathcal{Y} \end{aligned}$$

$$\therefore \boxed{\mathcal{Y} = \mathcal{Y}_A + \mathcal{Y}_B}$$

$$\left. \begin{array}{l} y_{11A} + y_{11B} = y_{11} \\ y_{12A} + y_{12B} = y_{12} \\ y_{21A} + y_{21B} = y_{21} \\ y_{22A} + y_{22B} = y_{22} \end{array} \right\} \begin{array}{l} \text{summing} \\ \text{matrices} \end{array}$$

II. Impedance (Z) Parameters:

(open CKT impedance Parameters).

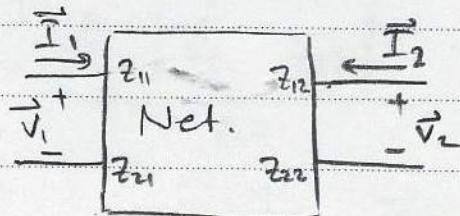

from mesh analysis

$$\vec{V}_1 = Z_{11} \vec{I}_1 + Z_{12} \vec{I}_2 \quad \dots \textcircled{1}$$

$$\vec{V}_2 = Z_{21} \vec{I}_1 + Z_{22} \vec{I}_2 \quad \dots \textcircled{2}$$

$$V = Z I \quad \text{matrices!}$$

$$; \quad V = \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix}, \quad I = \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix}, \quad Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

from \textcircled{1}

$$\bullet Z_{11} = \left. \frac{\vec{V}_1}{\vec{I}_1} \right|_{I_2=0}$$

o.c. that's why it's called o.c. z-parameters.

$$\bullet Z_{12} = \left. \frac{\vec{V}_1}{\vec{I}_2} \right|_{I_1=0} \quad \text{o.c.}$$

$$\bullet Z_{22} = \left. \frac{\vec{V}_2}{\vec{I}_2} \right|_{I_1=0} \quad \text{o.c.}$$

$$\bullet Z_{21} = \left. \frac{\vec{V}_2}{\vec{I}_1} \right|_{I_2=0}$$

* transformation from $Z \rightarrow Y$ parameters:

using cramer:

$$1. \vec{I}_1 = \frac{\begin{vmatrix} \vec{V}_1 & Z_{12} \\ \vec{V}_2 & Z_{22} \end{vmatrix}}{\Delta Z} = \frac{Z_{22} \vec{V}_1 - Z_{12} \vec{V}_2}{Z_{11}Z_{22} - Z_{12}Z_{21}}$$

$$Z_{11} \equiv \Delta_{11} \quad Z_{12} \equiv \Delta_{21}$$

$$\therefore \vec{I}_1 = \left(\frac{Z_{22}}{\Delta Z} \right) \vec{V}_1 - \left(\frac{Z_{12}}{\Delta Z} \right) \vec{V}_2 \quad \text{--- (1)}$$

$$\bullet Y_{11} = \frac{\Delta_{11}}{\Delta Z} = \frac{Z_{22}}{\Delta Z} \quad \text{--- (a)}$$

$$\bullet Y_{12} = -\frac{\Delta_{21}}{\Delta Z} = -\frac{Z_{12}}{\Delta Z} \quad \text{--- (b)}$$

$$2. \vec{I}_2 = \frac{\begin{vmatrix} \vec{Z}_{11} & \vec{V}_1 \\ \vec{Z}_{21} & \vec{V}_2 \end{vmatrix}}{\Delta Z} = \left(-\frac{Z_{21}}{\Delta Z} \right) \vec{V}_1 + \left(\frac{Z_{11}}{\Delta Z} \right) \vec{V}_2 \quad \text{--- (2)}$$

$$\bullet Y_{21} = -\frac{Z_{21}}{\Delta Z} = -\frac{\Delta_{12}}{\Delta Z} \quad \text{--- (c)}$$

$$\bullet Y_{22} = \frac{Z_{11}}{\Delta Z} = \frac{\Delta_{22}}{\Delta Z} \quad \text{--- (d)}$$

* transform from $Z \rightarrow Y$ parameters:

I have y-parameters:

$$\vec{I}_1 = Y_{11} \vec{V}_1 + Y_{12} \vec{V}_2 \quad \text{--- (1)}$$

$$\vec{I}_2 = Y_{21} \vec{V}_1 + Y_{22} \vec{V}_2 \quad \text{--- (2)}$$

$$\vec{V}_1 = \frac{\begin{vmatrix} \vec{I}_1 & Y_{12} \\ \vec{I}_2 & Y_{22} \end{vmatrix}}{\Delta y} \quad \& \quad \vec{V}_2 = \frac{\begin{vmatrix} Y_{11} & \vec{I}_1 \\ Y_{21} & \vec{I}_2 \end{vmatrix}}{\Delta y}$$

$$\therefore Z_{11} = \frac{Y_{22}}{\Delta y} = \frac{\Delta_{11}}{\Delta y} \quad \text{--- (e)} \quad \bullet Z_{21} = -\frac{Y_{21}}{\Delta y} = -\frac{\Delta_{12}}{\Delta y} \quad \text{--- (f)}$$

$$\bullet Z_{12} = -\frac{Y_{12}}{\Delta y} = -\frac{\Delta_{21}}{\Delta y} \quad \text{--- (g)} \quad \bullet Z_{22} = +\frac{Y_{11}}{\Delta y} = \frac{\Delta_{22}}{\Delta y} \quad \text{--- (h)}$$

if it's a bilateral CKT $\rightarrow Z_{12} = Z_{21}$!

* Equivalent CKT : (Z -parameters).

$$\vec{V}_1 = Z_{11} \vec{I}_1 + Z_{12} \vec{I}_2 \quad \dots \textcircled{1}$$

$$\vec{V}_2 = Z_{21} \vec{I}_1 + Z_{22} \vec{I}_2 \quad \dots \textcircled{2}$$


- 1st equivalent CKT:-

- add & subtract $(Z_{12} \vec{I}_1)$ from $\textcircled{2}$

$$\vec{V}_1 = Z_{11} \vec{I}_1 + Z_{12} \vec{I}_2 \quad \dots \textcircled{1}' \text{ stays the same.}$$

$$\vec{V}_2 = Z_{12} \vec{I}_1 + Z_{22} \vec{I}_2 + (Z_{21} - Z_{12}) \vec{I}_1 \quad \dots \textcircled{2}'$$

from mesh analysis:-

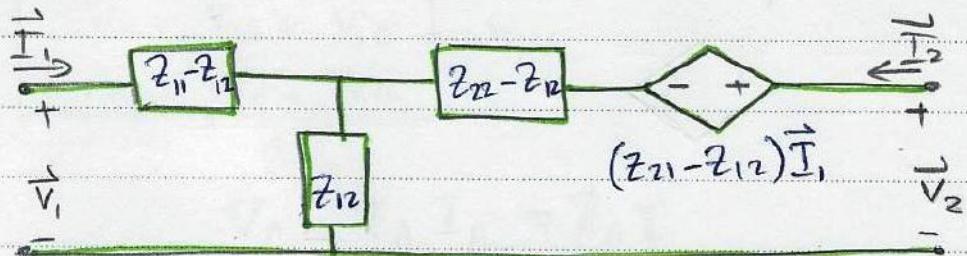


- 2nd equivalent CKT:-

- add & subtract $(Z_{21} \vec{I}_2)$ from $\textcircled{1}$:

$$\vec{V}_1 = Z_{11} \vec{I}_1 + Z_{12} \vec{I}_2 + (Z_{12} - Z_{21}) \vec{I}_2 \quad \dots \textcircled{1}'$$
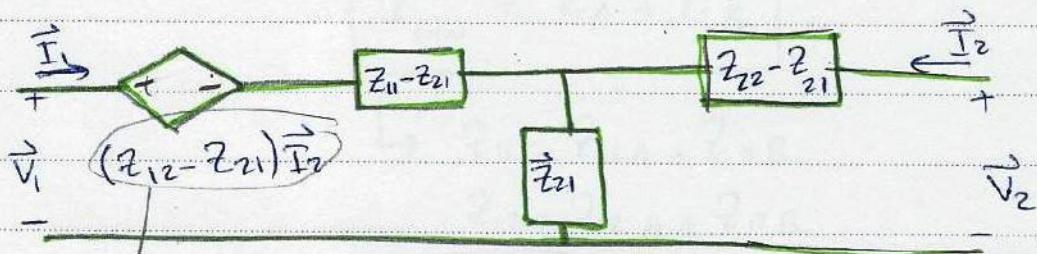
$$\vec{V}_2 = Z_{21} \vec{I}_1 + Z_{22} \vec{I}_2 \quad \dots \textcircled{2}' \text{ stays the same}$$




↳ if it is a bilateral CKT, this source will be short-circuited

watch out /

series \neq cascade

* Series 2Part network:

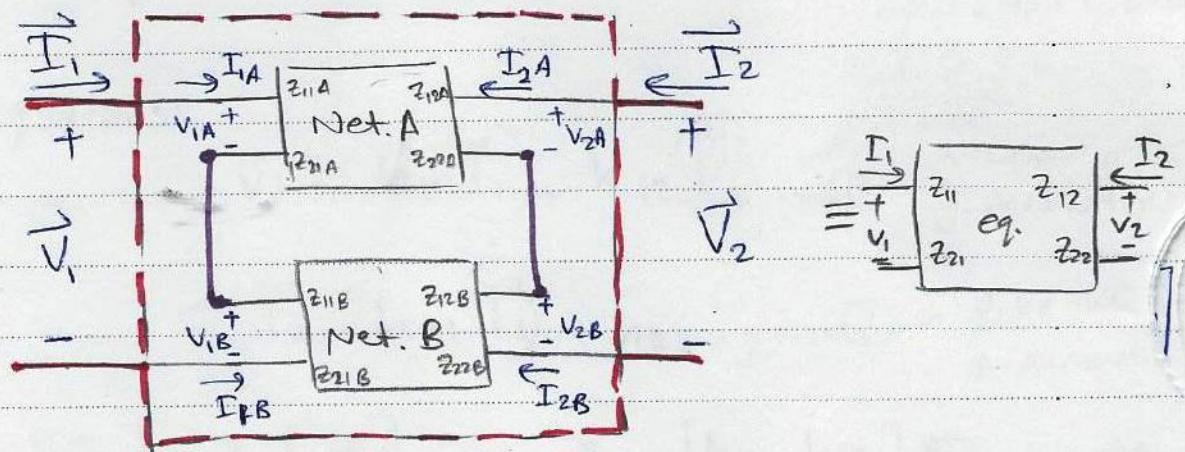

$I_{1A} = I_{1B} = I_1$	\Rightarrow	for X
$I_{2A} = I_{2B} = I_2$	\Rightarrow	in series
$V_1 = V_{1A} + V_{1B}$	$\dots \text{(*)}$	
$V_2 = V_{2A} + V_{2B}$		

$$V_A = Z_A I_A = R_A I$$

$$V_B = R_B I_B = Z_B I$$

$$V = V_A + V_B \quad \text{from (*)}$$

$$V = I \underbrace{(Z_A + Z_B)}_Z$$

$$\therefore R_{\text{total}} = R_A + R_B$$

$$\Rightarrow Z_{11} = Z_{11A} + Z_{11B}$$

$$Z_{12} = Z_{12A} + Z_{12B}$$

$$Z_{21} = Z_{21A} + Z_{21B}$$

$$Z_{22} = Z_{22A} + Z_{22B}$$

III. Hybrid Parameters (h)

معادلة عاشرة I_1 ملحوظ

$$I_1 = \frac{1}{h_{11}} \vec{V}_1 - \frac{h_{12}}{h_{11}} \vec{V}_2$$

• equations:

$$\vec{V}_1 = h_{11} \vec{I}_1 + h_{12} \vec{V}_2 \quad \text{---(1)} \quad \begin{matrix} \text{wolfe} \\ \text{y-parameters} \end{matrix}$$

$$\vec{I}_2 = h_{21} \vec{I}_1 + h_{22} \vec{V}_2 \quad \text{---(2)} \quad \begin{matrix} \text{like the} \\ \text{z-paramet.} \end{matrix}$$

$$\begin{bmatrix} \vec{V}_1 \\ \vec{I}_2 \end{bmatrix} = h \begin{bmatrix} \vec{I}_1 \\ \vec{V}_2 \end{bmatrix}, \quad h = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \quad \begin{matrix} \text{wolfe} \\ \text{Amplifier!} \end{matrix}$$

- $h_{11} = \left. \frac{\vec{V}_1}{\vec{I}_1} \right|_{V_2=0}$; Short CKT input impedance
= h_i

output S.C. $\frac{out}{in}$

- $h_{21} = \left. \frac{\vec{I}_2}{\vec{I}_1} \right|_{V_2=0}$; Forward Current Gain (G_f)
= h_f

output S.C. $\frac{in}{out}$

- $h_{12} = \left. \frac{\vec{V}_1}{\vec{V}_2} \right|_{I_1=0}$; Open CKT reverse Voltage Gain = h_r

- $h_{22} = \left. \frac{\vec{I}_2}{\vec{V}_2} \right|_{I_1=0}$; Open CKT output admittance
= h_o

* NOTE: for bilateral CKTs:

$$h_{12} = -h_{21}$$

* transform from $h \rightarrow z$:

my (h) equations: $\begin{cases} \vec{V}_1 = h_{11} \vec{I}_1 + h_{12} \vec{V}_2 \\ \vec{I}_2 = h_{21} \vec{I}_1 + h_{22} \vec{V}_2 \end{cases}$... (1) ... (2)

from (2):

$$\vec{V}_2 = \left(\frac{-h_{21}}{h_{22}} \right) \vec{I}_1 + \left(\frac{1}{h_{22}} \right) \vec{I}_2 \quad \text{in (2)'}$$

\vec{V}_2
substitute ↑ in (1) z_{11} z_{22}

$$\vec{V}_1 = h_{11} \vec{I}_1 + \frac{h_{12}}{h_{22}} (\vec{I}_2 - h_{21} \vec{I}_1)$$

$$\vec{V}_1 = \left(h_{11} - \frac{h_{12} h_{21}}{h_{22}} \right) \vec{I}_1 + \left(\frac{h_{12}}{h_{22}} \right) \vec{I}_2$$

z_{11} z_{21}

* transform from $h \rightarrow y$:

You can do it $h \rightarrow z$ then $z \rightarrow y$

from (1) $\vec{I}_1 = \left(\frac{1}{h_{11}} \right) \vec{V}_1 + \left(\frac{-h_{12}}{h_{11}} \right) \vec{V}_2$

y_{11} y_{12}


plug \vec{I}_1 in (2):

$$\vec{I}_2 = h_{21} \left(\frac{1}{h_{11}} \vec{V}_1 - \frac{h_{12}}{h_{11}} \vec{V}_2 \right) + h_{22} \vec{V}_2$$

$$\vec{I}_2 = \left(\frac{h_{21}}{h_{11}} \right) \vec{V}_1 + \left(\frac{-h_{21} h_{12}}{h_{11}} + h_{22} \right) \vec{V}_2$$


y_{21} y_{22}

* equivalent CKT:

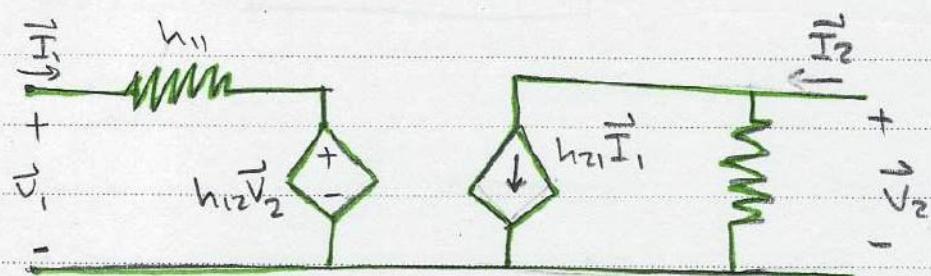

→ take two meshes to prove their equivalence.

* Series - Parallel Interconnection:

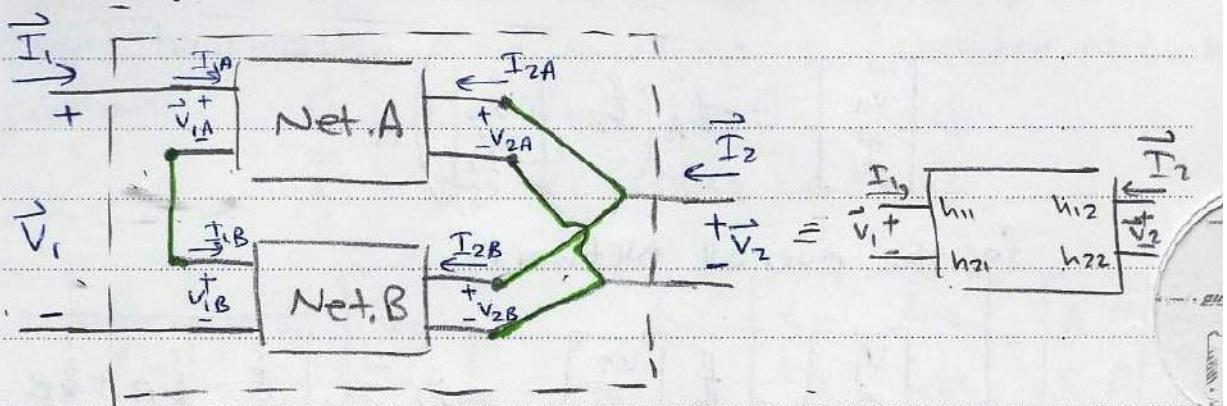

$$\vec{V}_1 = \vec{V}_{1A} + \vec{V}_{1B}, \quad \vec{I}_1 = \vec{I}_{1A} = \vec{I}_{1B}$$

$$\vec{V}_2 = \vec{V}_{2A} + \vec{V}_{2B}, \quad \vec{I}_2 = \vec{I}_{2A} + \vec{I}_{2B}$$

$$h_{\text{overall}} = h_A + h_B$$

Proof:-

- for Net.A $\begin{bmatrix} \vec{V}_{1A} \\ \vec{I}_{2A} \end{bmatrix} = h_A \begin{bmatrix} \vec{I}_{1A} \\ \vec{V}_{2A} \end{bmatrix} = h_A \begin{bmatrix} \vec{I}_1 \\ \vec{V}_2 \end{bmatrix} \dots \textcircled{a}$

- for Net.B $\begin{bmatrix} \vec{V}_{1B} \\ \vec{I}_{2B} \end{bmatrix} = h_B \begin{bmatrix} \vec{I}_{1B} \\ \vec{V}_{2B} \end{bmatrix} = h_B \begin{bmatrix} \vec{I}_1 \\ \vec{V}_2 \end{bmatrix} \dots \textcircled{b}$

- for overall net. $\begin{bmatrix} \vec{V}_1 \\ \vec{I}_2 \end{bmatrix} = h \begin{bmatrix} \vec{I}_1 \\ \vec{V}_2 \end{bmatrix} \dots \textcircled{c}$ Plug @ \textcircled{a} & \textcircled{b}

$$\begin{bmatrix} \vec{V}_{1A} + \vec{V}_{1B} \\ \vec{I}_{2A} + \vec{I}_{2B} \end{bmatrix} = \begin{bmatrix} \vec{V}_{1A} \\ \vec{I}_{2A} \end{bmatrix} + \begin{bmatrix} \vec{V}_{1B} \\ \vec{I}_{2B} \end{bmatrix}$$

$$= (h_A + h_B) \begin{bmatrix} \vec{I}_1 \\ \vec{V}_2 \end{bmatrix}$$

From \textcircled{c}:

$$h = h_A + h_B \quad \text{**}$$

IV Transmission Parameters: (t / ABCD - Parameters)

⇒ Usage: transmission line analysis & cascaded Networks

equations:- $\vec{V}_1 = t_{11} \vec{V}_2 - t_{12} \vec{I}_2 \dots (1)$

$$\vec{I}_1 = t_{21} \vec{V}_2 - t_{22} \vec{I}_2 \dots (2)$$

$$\begin{bmatrix} \vec{V}_1 \\ \vec{I}_1 \end{bmatrix} = t \begin{bmatrix} \vec{V}_2 \\ -\vec{I}_2 \end{bmatrix}, \quad t = \begin{bmatrix} t_{11} & t_{12} \\ t_{21} & t_{22} \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$t_{11} = \left. \frac{\vec{V}_1}{V_2} \right|_{I_2=0}$; open circuit Output $t_{21} = \left. \frac{\vec{I}_1}{V_2} \right|_{I_2=0}$; o.c output


$t_{12} = \left. -\frac{\vec{V}_1}{\vec{I}_2} \right|_{V_2=0}$; short CKT output $t_{22} = \left. -\frac{I_1}{I_2} \right|_{V_2=0}$; s.c o/p
! output! is not in phase

* NOTE:- for bilateral Networks:-

$$t = t_{11} t_{22} - t_{12} t_{21} = 1$$

* this Net. doesn't have an equivalent CKT !! :)

* Cascaded Networks:-

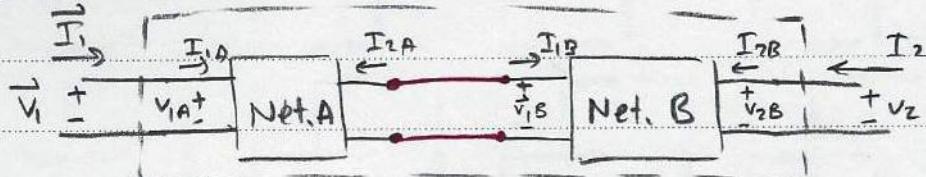

in the input side:- $\vec{I}_1 = \vec{I}_{1A}$, $\vec{V}_1 = \vec{V}_{1A}$

~ ~ output ~ :- $\vec{I}_2 = \vec{I}_{2B}$, $\vec{V}_2 = \vec{V}_{2B}$

~ ~ middle ~ :- $\vec{V}_{1B} = \vec{V}_{1B}$, $I_{2A} = -I_{1B}$

* I'm looking for the overall t :

$$t = t_A \cdot t_B \quad \text{be careful! it's matrix Multiplication}$$

$$t_A \cdot t_B \neq t_B \cdot t_A$$

for Net. A: $\begin{bmatrix} \vec{V}_1 \\ \vec{I}_1 \end{bmatrix} = t_A \begin{bmatrix} \vec{V}_{1A} \\ -\vec{I}_{2A} \end{bmatrix} = t_A \begin{bmatrix} \vec{V}_{1B} \\ \vec{I}_{1B} \end{bmatrix} \dots (a)$

for Net. B: $\begin{bmatrix} \vec{V}_{1B} \\ \vec{I}_{1B} \end{bmatrix} = t_B \begin{bmatrix} \vec{V}_{2B} \\ -\vec{I}_{2B} \end{bmatrix} = t_B \begin{bmatrix} \vec{V}_2 \\ -\vec{I}_2 \end{bmatrix} \dots (b)$

→ plug (b) in (a) ~~assuming~~ follows - cause?

$$\begin{bmatrix} \vec{V}_1 \\ \vec{I}_1 \end{bmatrix} = t_A \left(t_B \begin{bmatrix} \vec{V}_2 \\ -\vec{I}_2 \end{bmatrix} \right)$$

for the overall Network :-

$$\begin{bmatrix} \vec{V}_1 \\ \vec{I}_1 \end{bmatrix} = t \begin{bmatrix} \vec{V}_2 \\ -\vec{I}_2 \end{bmatrix} \Rightarrow \therefore \boxed{t = t_A + t_B} \quad \text{※}$$

* transform $t \rightarrow Z$

$$\vec{V}_1 = t_{11} \vec{V}_2 - t_{12} \vec{I}_2 \quad \text{--- (1)}$$

$$\vec{I}_1 = t_{21} \vec{V}_2 - t_{22} \vec{I}_2 \quad \text{--- (2)}$$

from (2) :

$$\vec{V}_2 = \left(\frac{1}{t_{21}} \right) \vec{I}_1 + \left(\frac{t_{22}}{t_{21}} \right) \vec{I}_2$$

sub. V_2 in (1)

$$\vec{V}_1 = \left(\frac{t_{11}}{t_{21}} \right) \vec{I}_1 + \left(\frac{t_{11} t_{22} - t_{12}}{t_{21}} \right) \vec{I}_2$$

now I can do

$$t \rightarrow y ; \quad t \rightarrow Z \text{ then } Z \rightarrow y$$

$$t \rightarrow h ; \quad t \rightarrow Z \text{ then } Z \rightarrow h$$

(CKT) معرف کانٹ پارامٹریں معلوم نہیں

final
exam

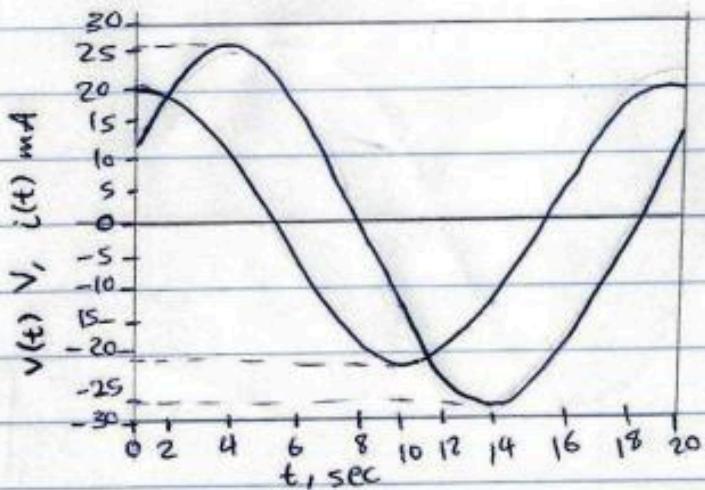


Figure: Q1

Question 1: In Fig. Q1:

- The minimum Power $P_{min} =$
- The average Power $P =$
- The reactive Power $Q =$
- The peak power $P_{max} =$

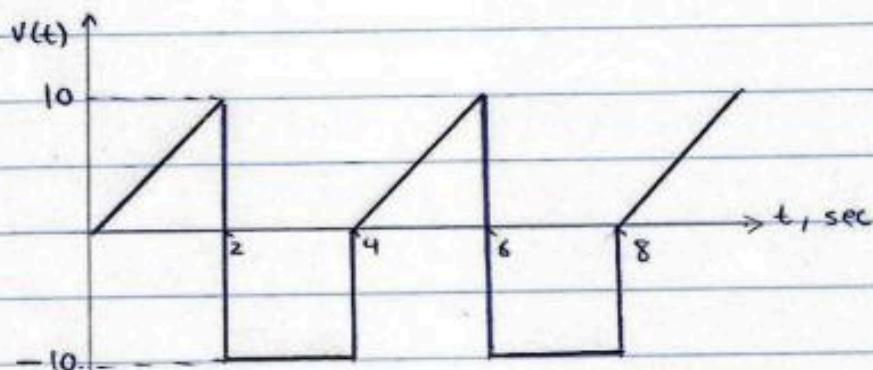


Figure: Q2

Question 2: The RMS value of the signal shown in Fig. Q2 is:

- 86.7 V.
- 8.166 V.
- 8.615 V.
- 6.867 V.

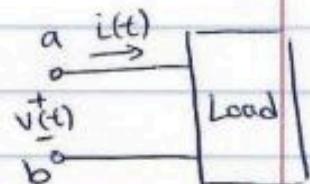
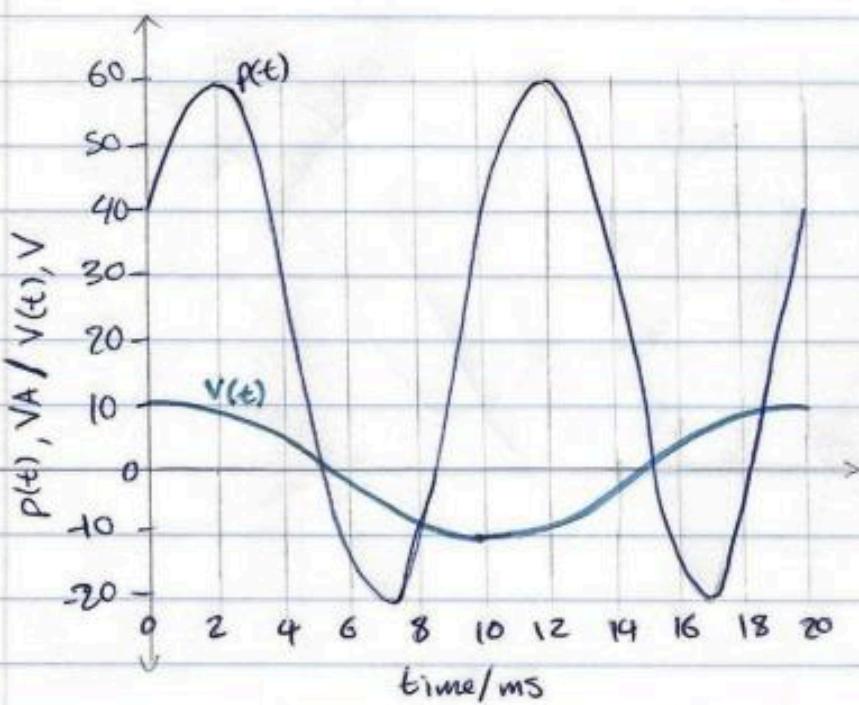


Figure: Q3

Question 3: If the load is composed of two elements in series, then the current $i(t)$ flows to the load is:

- a. $8 \cos(100\pi t - 60^\circ)$
- b. $15 \cos(100\pi t + 30^\circ)$
- c. $10 \cos(100\pi t - 30^\circ)$
- d. $12 \cos(100\pi t + 60^\circ)$

Question 7: Fig.Q7, shows the instantaneous power $p(t)$, where the voltage is given in the form

$$V(t) = 100 \cos(2\pi f t + 0^\circ) V.$$

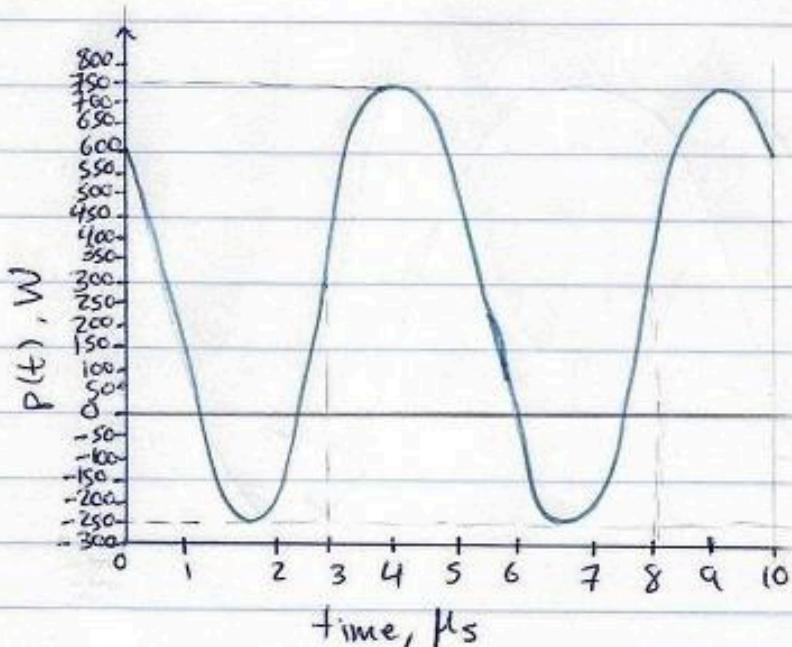


Figure: Q7

The frequency of the voltage f is:-

- a. 10 KHz
- b. 200 KHz
- c. 50 KHz
- d. 100 KHz

One of the numerical expressions of the instantaneous Power $p(t)$ is wrong:-

- a. $400 - 500 \cos 143.13^\circ \cos 2\omega t + 500 \sin 143.13^\circ \sin 2\omega t$
- b. none of these
- c. $400 - 500 \cos(2\omega t + 143.13^\circ)$
- d. $400 + 500 \cos(2\omega t - 36.87^\circ)$
- e. $400 + 400 \cos(2\omega t) + 300 \sin(2\omega t)$

Question 7:- Fig. Q7 shows the instantaneous power $p(t)$ absorbed by the load & the voltage $v(t)$ applied to it. The load composed of 2 elements in series. The current $i(t)$ is:-

- a. $15 \cos(100\pi t + 30^\circ)$
- b. none of these.
- c. $12 \cos(100\pi t + 60^\circ)$
- d. $8 \cos(100\pi t - 60^\circ)$
- e. $10 \cos(100\pi t - 30^\circ)$

Question 5:- a three-phase balanced voltage source feeds the load shown in Fig. Q5, the $V_{AB} = 400 \angle 30^\circ$.

The $|Z_{AB}| = |\vec{z}_{BC}| = |\vec{z}_{CA}|$ & the three-phase load absorbs 4000 W.

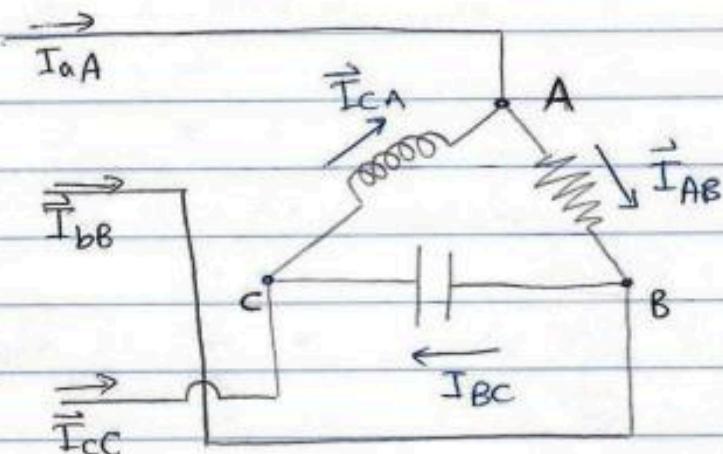


Figure: Q5

The line current \vec{I}_{AA} is:

- a. none of these
- b. $19.32 \angle -45^\circ$ A
- c. $10.0 \angle -30^\circ$ A
- d. $19.32 \angle 45^\circ$ A
- e. $10.0 \angle -45.0^\circ$ A

Q: A three-phase balanced voltage source feeds the load shown in fig. Q4 , $|Z_y| = 5/30^\circ \Omega$, $V_{AN} = 400/60^\circ V_{rms}$

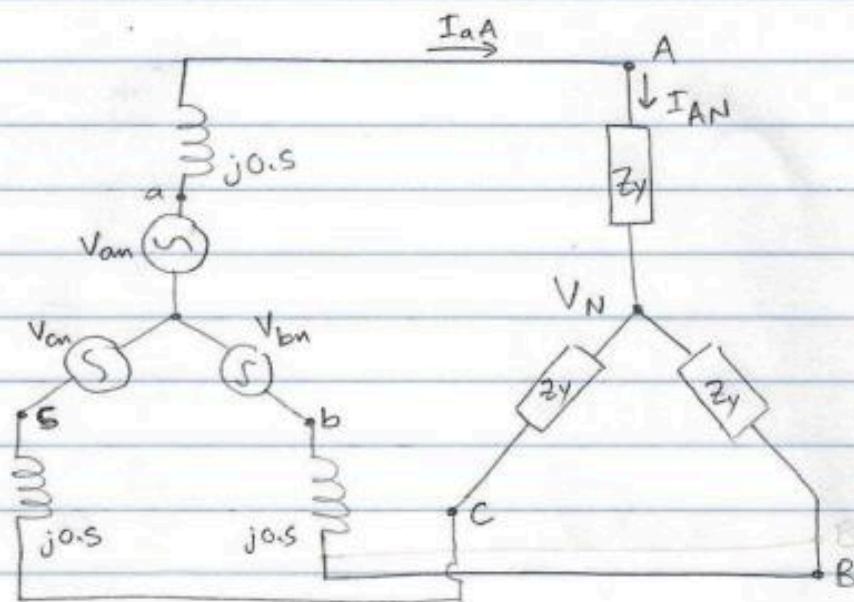


Figure: Q4

The $V_{bn} \approx$:

- $421.43/-55.3^\circ A$
- $252.0/-98^\circ A$
- $250.32/-30^\circ A$
- $267.5.0/-132^\circ A$
- $243.73/-186^\circ A$

Question 12:- To find P_{avg}

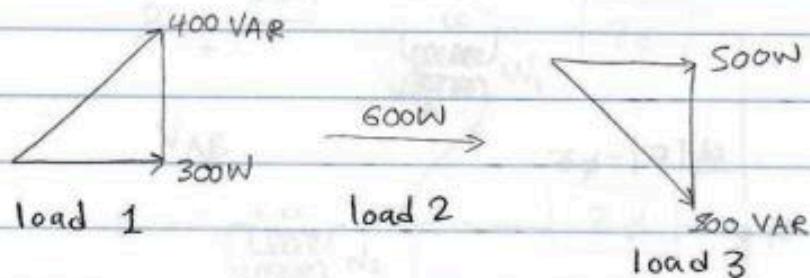
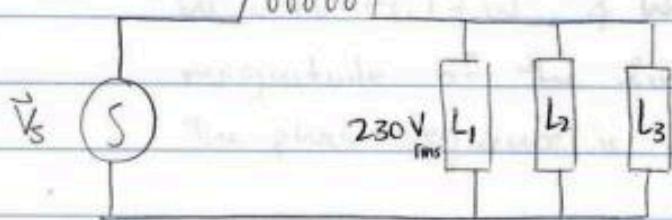


Figure: Q11

Question 11:- In fig. Q 11, the reactive power delivered by the source to the network is:-

- a. $j440 \text{ VAR}$
- b. $j359.9 \text{ VAR}$
- c. none of these
- d. $j35.59 \text{ VAR}$
- e. $-j359.9 \text{ VAR}$

Question 13:- In fig. Q13, The Line Voltage $V_{ab} = 230V$ & $\theta = 30^\circ$ and the load impedances are $Z_1 = 5 + j12 \Omega$ and $Z_2 = 10 + j10 \Omega$. Then two unknown values are

- a. $W_1 = 2351.6 \text{ W}$ & $W_2 = 11172.5 \text{ W}$
- b. $W_1 = 2351.6 \text{ W}$ & $W_2 = 16519.17 \text{ W}$
- c. $W_1 = 11275 \text{ W}$ & $W_2 = 29816 \text{ W}$
- d. None of these
- e. All of above & $W_3 = 11275 \text{ W}$

Question 12: The two-wattmeters in Fig. Q12, read as $W_1 = 16519.17 \text{ W}$, & $W_2 = 2119.170 \text{ W}$. The magnitude of the line voltage is $415 \text{ V}_{\text{rms}}$. The phase sequence is +ve.

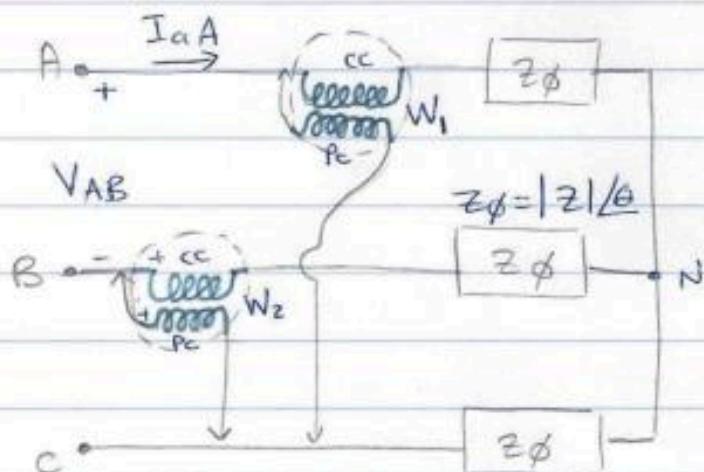


Figure: Q12

The power factor of the load P.F is:-

- a. none of these.
- b. 0.9823 Lagging
- c. 0.866 Lagging
- d. 0.8923 Lagging
- e. 0.5986 Lagging

Question 8: In Fig. Q12, The line voltage $V_{AB} = 416 \text{ V}_{\text{rms}}$ & positive sequence, The load impedance $Z_\phi = 5145^\circ$. The two-wattmeters read as:-

- a. $W_1 = 2781.6 \text{ W}$ & $W_2 = 11172.5 \text{ W}$
- b. $W_1 = 2981.6 \text{ W}$ & $W_2 = 16519.17 \text{ W}$.
- c. $W_1 = 11127.5 \text{ W}$ & $W_2 = 2981.6 \text{ W}$.
- d. None of these
- e. $W_1 = 2981.6 \text{ W}$ & $W_2 = 11127.5 \text{ W}$

Question 9:- In Fig. Q9, the source delivers 7500 VA at $\vec{V}_s = 250 \angle 30^\circ V_{\text{rms}}$ with power factor of 0.8660205 lagging.

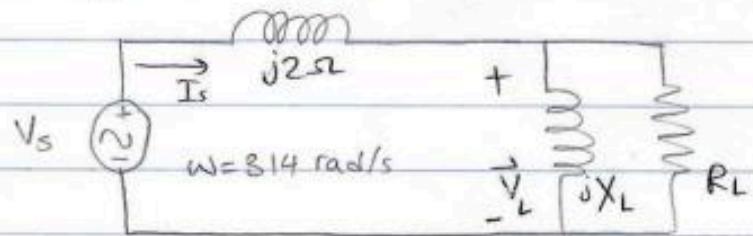


Figure : Q9

The value of X_L is:-

- a. 32.38 Ω
- b. 18.70 Ω
- c. none of these
- d. 11.0 Ω
- e. 12.47 Ω