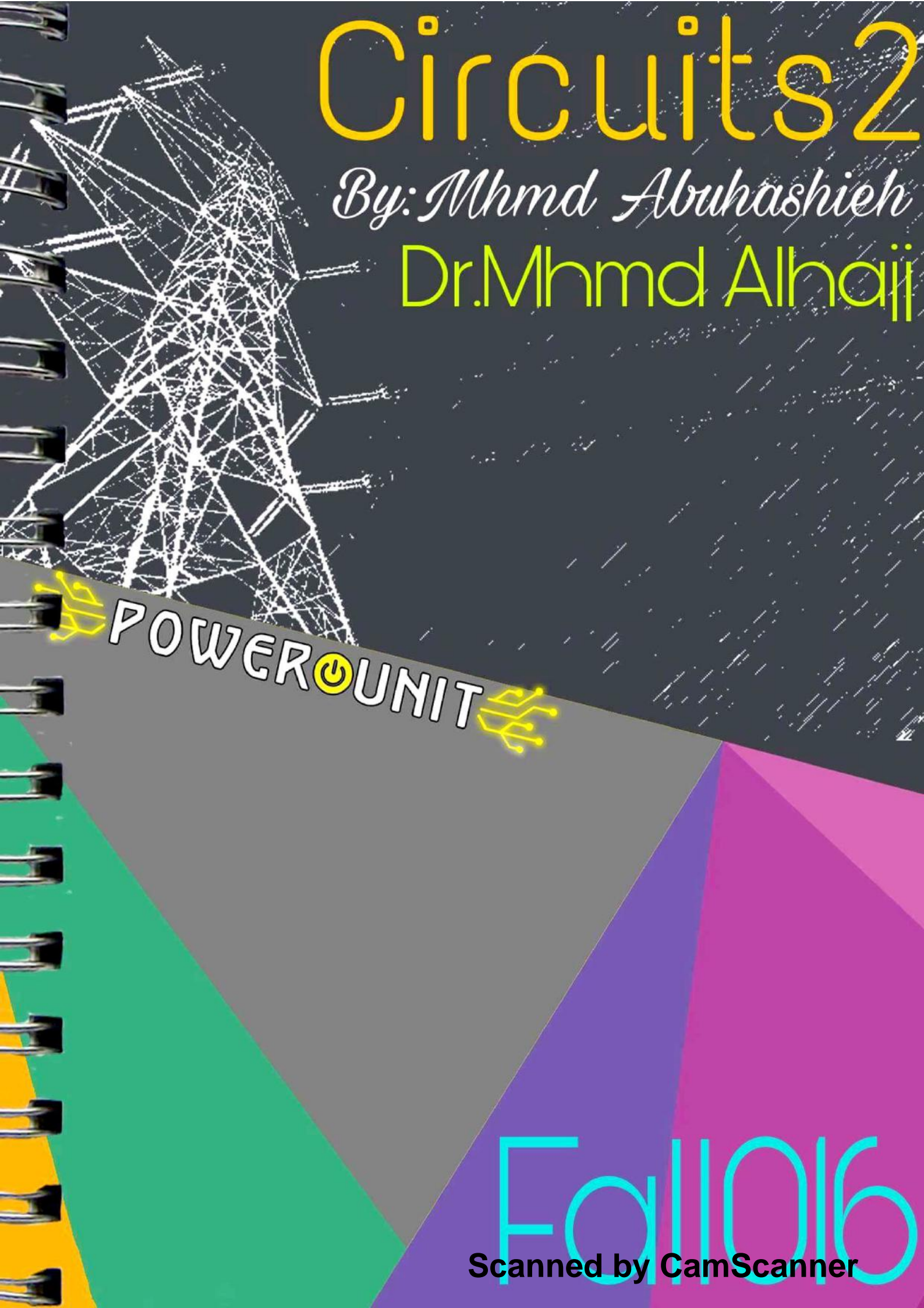


Circuits 2

By: Mhmd Abukashieh

Dr. Mhmd Alhajj




POWER UNIT

Fall 016




Introduction:

$P = I * V$


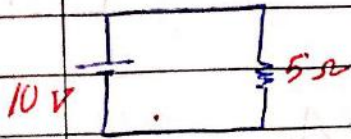


$\Rightarrow I = 2A$

$P = (2)(10) = 20W$

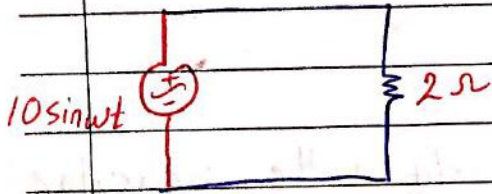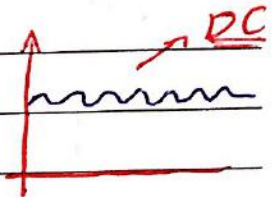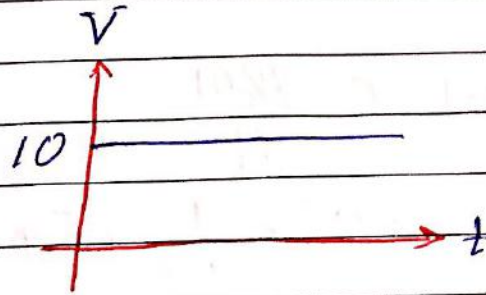



$I = \frac{V}{R} = 5 \sin \omega t$

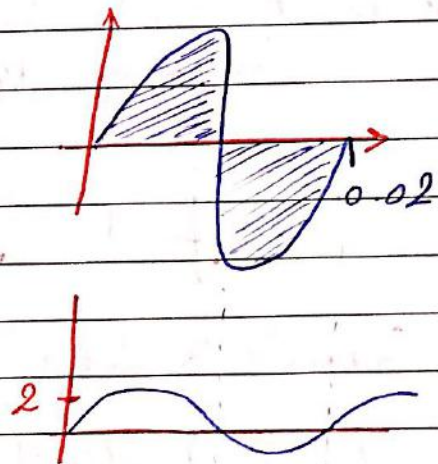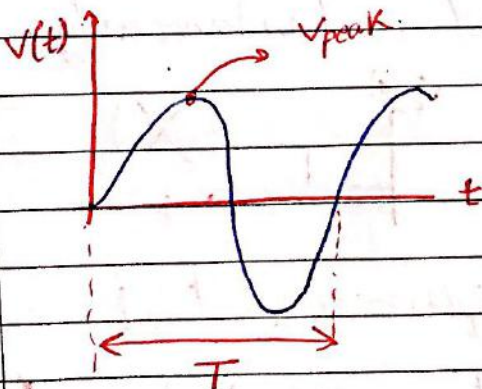

average $P = VI = 10 * 2 = 20$

$P(0.05) = 2 * 10 = 20$

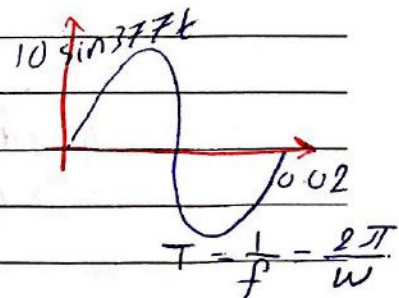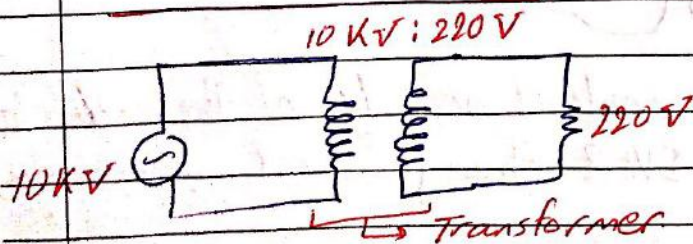$V_{avg} = \frac{1}{T} \int_0^T 10 \sin \omega t dt = \frac{1}{0.02} \int_0^{\frac{1}{2}T} 10 \sin 377t dt = 0$






$Z = R + jX$
 Impedance = Resistance + Reactance

* Calculate & sketch $i_c(t)$ when $v_c(t) = 5(1 - e^{-t/10^{-6}}) \text{ V}$



$$i_c(t) = C \frac{dv_c(t)}{dt}$$

$$= 10^{-7} * \frac{1}{10^{-6}} * 5 * e^{-t/10^{-6}} = 0.5 e^{-t/10^{-6}} \text{ A.}$$

$$C = 10^{-7}$$

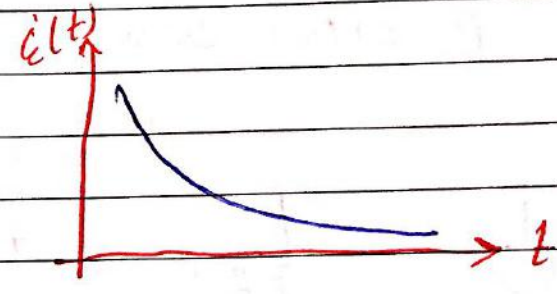
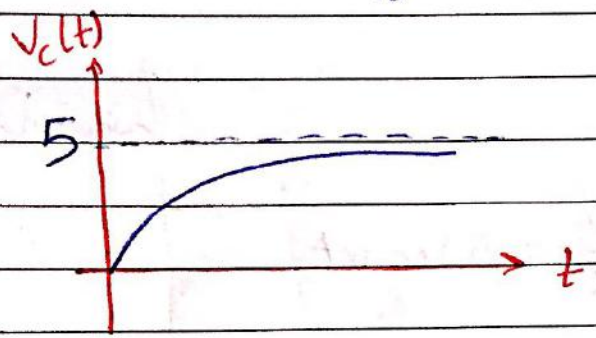
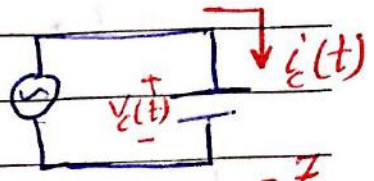


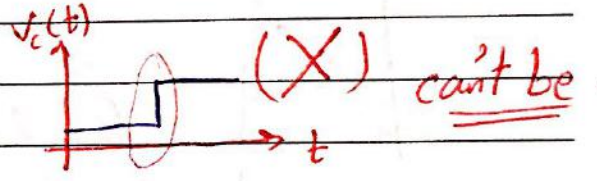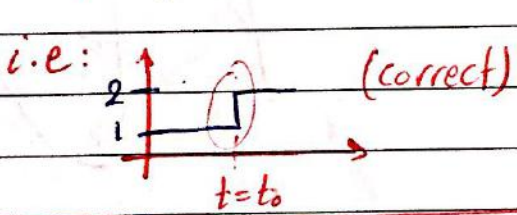* Note: I_c can be changed instantaneously in the capacitor.
 $\Rightarrow V_c$ can NOT be changed instantaneously.




* Calculate & sketch $v_L(t)$ when $i_L(t) = 20t e^{-2t}$, $L = 0.1 \text{ H}$
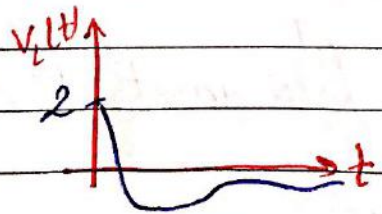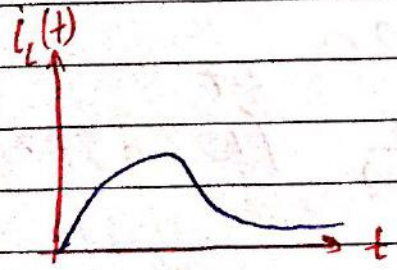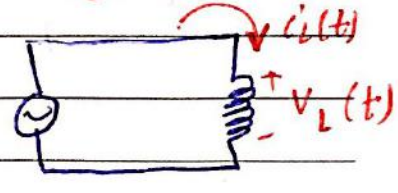
$$v_L(t) = L \frac{di_L(t)}{dt} = 0.1 * [-40e^{-2t} t + 20e^{-2t}] = 2e^{-2t} (1 - 2t) \text{ V.}$$



* Note: v_L can be changed instantaneously in the inductor.
 $\Rightarrow i_L$ can NEVER EVER change instantaneously.


No. _____

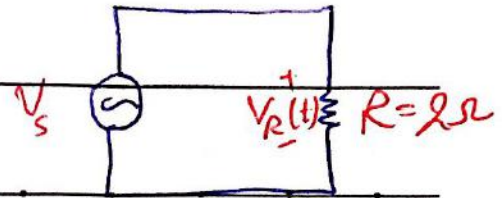

Ex.

$$i_R(t) = \frac{V_R(t)}{R} = \boxed{5 \cos \omega t}$$

$$V_s(t) = 10 \cos \omega t.$$

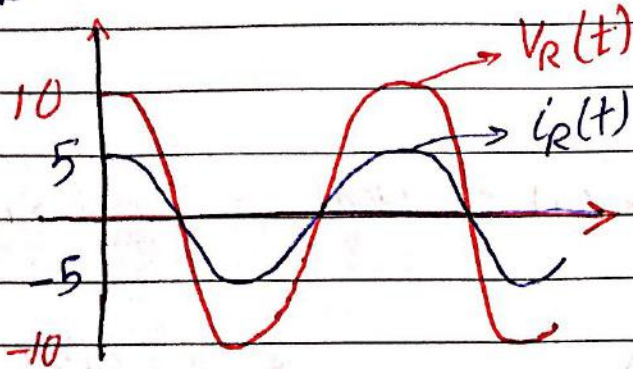

* phase shift: is a compare between two waves form.

* The first wave interact with x-axis \Rightarrow it will be the lead to the other one.

\Rightarrow The red wave form **leads** the blue wave form.



* Resistor voltage & current are "in phase".

* Find the inductor current if $I_L(0^-) = \text{Zero}$, $\omega = 1000$

$$V_L(t) = L \frac{di_L}{dt}$$

$$\Rightarrow i_L(t) = \frac{1}{L} \int_0^t V_L(t') dt' + i_L(0^-)$$
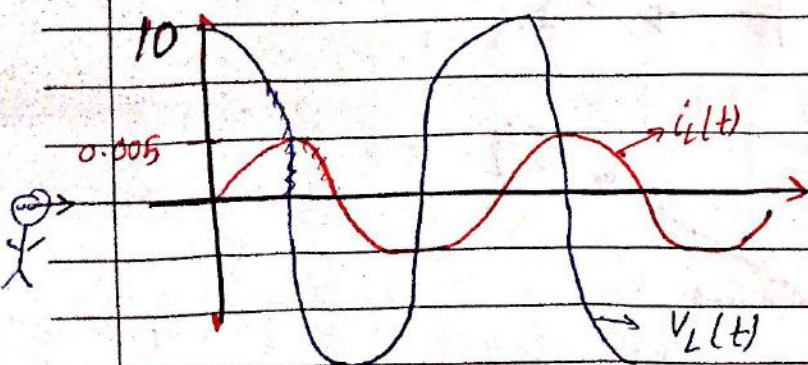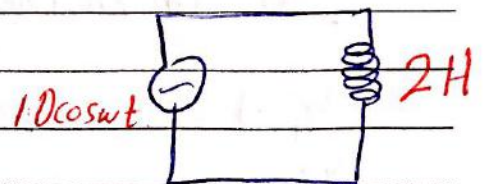
$$= \frac{1}{2} * 10 * \frac{1}{1000} \sin 1000t = \boxed{0.005 \sin 1000t} \text{ A.}$$





* In inductor the voltage leads the current by $(\frac{\pi}{2})$.

* Find $i_c(t)$, $i_c(0^-) = 0$, $V_c(0) = 0$

$$i_c(t) = C \frac{dV_c(t)}{dt}$$
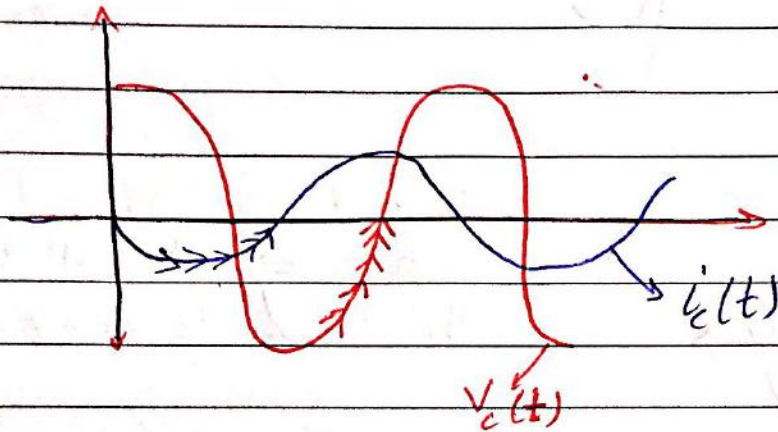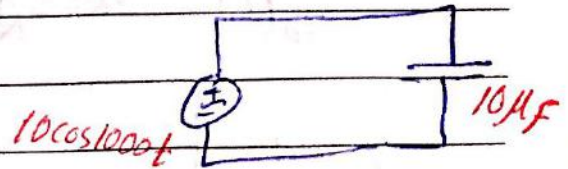
$$= 10^{-5} * 10 * 1000 * (-1) \sin 1000t = \boxed{-0.1 \sin(1000t)} \text{ A}$$



* In capacitor the current leads voltage.

* Phasors:


$$V_1(t) = 340 \cos(100\pi t) \Rightarrow V_1 = 340 \angle 0^\circ$$

$$i(t) = 10 \cos(100\pi t - 45^\circ) \Rightarrow I = 10 \angle -45^\circ$$


$$i'(t) = 20 \cos(100\pi t - 10^\circ) \Rightarrow I = 20 \angle -10^\circ$$

$$V_2(t) = 340 \cos(100\pi t + 120^\circ) \Rightarrow V_2 = 340 \angle +120^\circ$$
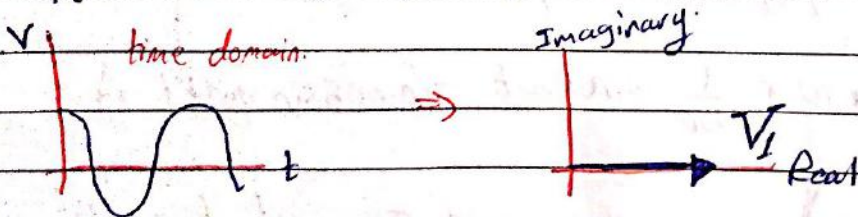
$$V_1(t) = \cos \omega t = 1 \cos(\omega t + 0)$$



$$V_2(t) = 3 \cos(\omega t + 30^\circ)$$

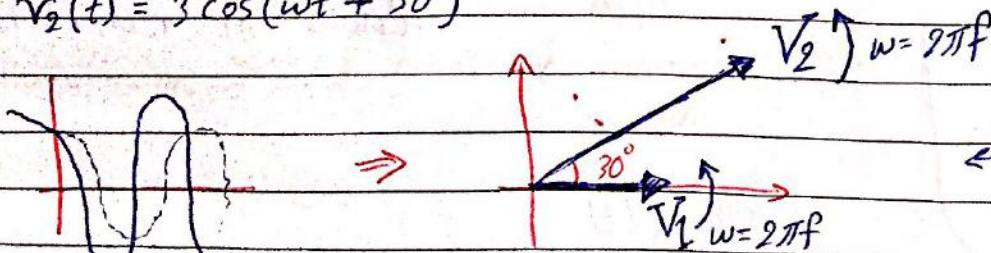


V_2 reach x-axis firstly.

V_2 leading.
 V_1 lagging.

V_2 leads V_1

$$V_3(t) = 2 \sin \omega t$$
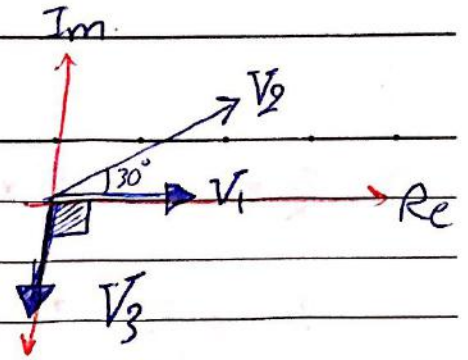
$$= 2 \cos\left(\frac{\pi}{2} - \omega t\right) = \underline{\underline{2 \cos\left(\omega t - \frac{\pi}{2}\right)}}$$



Ex. Draw the currents phasors:

$$V(t) = \cos \omega t \Rightarrow V = 1 \angle 0^\circ$$

$$I_R = \frac{1 \angle 0^\circ}{5} = \underline{\underline{0.2 \angle 0^\circ}}$$




$$I_C = \frac{1 \angle 0^\circ}{-j20} = \underline{\underline{j0.05}}$$

$$I_L = \frac{1 \angle 0^\circ}{j10} = \underline{\underline{-j0.1}}$$

$$I_{Total} = I_C + I_R + I_L = \underline{\underline{0.2 - j0.05}}$$

$$\phi = \tan^{-1}\left(\frac{-0.05}{0.2}\right)$$



⊙ put in your mind in what quarter ϕ in.

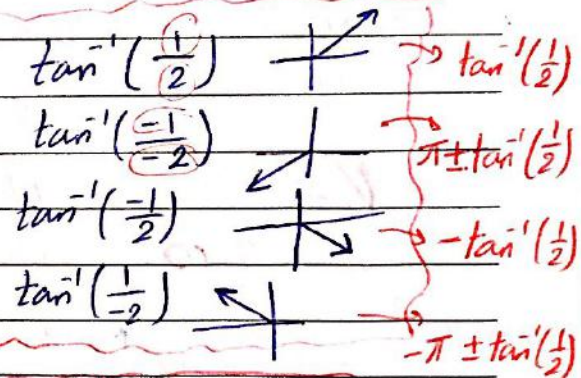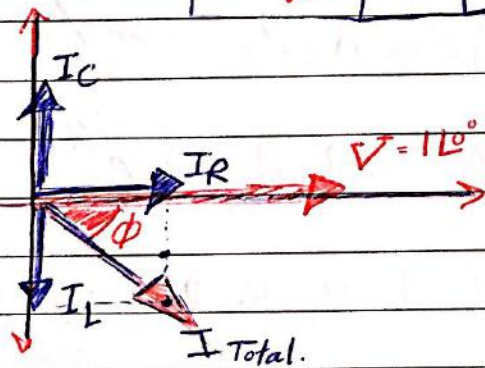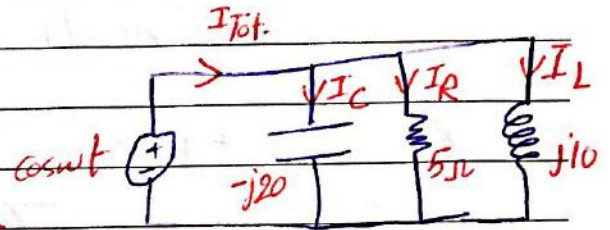

Ex. Draw the phasors:

$$I_{total} = \frac{10 \angle 30^\circ}{j2.5 + \frac{2 * -j}{2-j}} = \underline{\underline{2.92 - j4.17}}$$
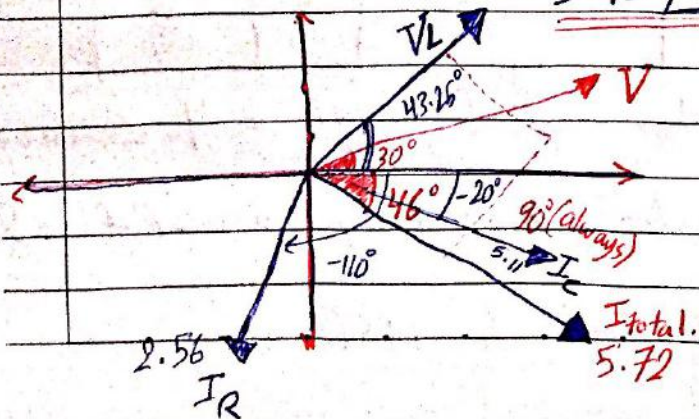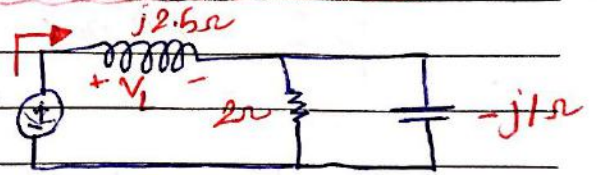
$$= \underline{\underline{5.72 \angle -46.75^\circ}}$$



* since V leads I_{Tot} , the main part in the circuit is the inductor.

$$\text{for } V_L = I_L * j2.5$$

$$\underline{\underline{V_L = 14.3 \angle 43.25^\circ}}$$

* I_R is in phase just with V_R .

No. _____

$$\Rightarrow I_R = 5.72 \angle 46.75^\circ * \left[\frac{-j1}{2-j1} \right] = \boxed{2.56 \angle -110^\circ}$$

$$I_C = 5.72 \angle 46.75^\circ * \left[\frac{2}{2-j1} \right] = \boxed{5.11 \angle -20^\circ}$$

* Euler's Equation:

$$\left[e^{j\theta} = \cos\theta + j\sin\theta \right] \quad \left\{ \begin{array}{l} \text{Re}[Ae^{j\theta}] = A\cos\theta \\ \text{Im}[Ae^{j\theta}] = jA\sin\theta \end{array} \right\}$$

$$\left(Ae^{j\theta} = A\angle\theta \right) \Rightarrow$$

$$A\cos(\omega t + \theta) = A e^{j\theta + j\omega t} = A e^{j\theta} e^{j\omega t} = \underline{Ae^{j\theta}}$$



Ex: Find $V_1 + V_2$? $V_1 = 15 \cos(\omega t + \frac{\pi}{4})$
 $V_2 = 10 \cos(\omega t + \frac{\pi}{6})$

$$\Rightarrow V_1 = 15 \angle \frac{\pi}{4} = 15 \cos \frac{\pi}{4} + j15 \sin \frac{\pi}{4}$$

$$V_2 = 10 \angle \frac{\pi}{6} = 10 \cos \frac{\pi}{6} + j10 \sin \frac{\pi}{6}$$

Ex: $V_1 = 15 \cos(100\pi t + \frac{\pi}{4}) = 15 \cos(100\pi) * \cos \frac{\pi}{4} - 15 \sin 100\pi t \sin \frac{\pi}{4}$
 $V_2 = 10 \cos(120\pi t + \frac{\pi}{6})$

* we can't add them if ω different.

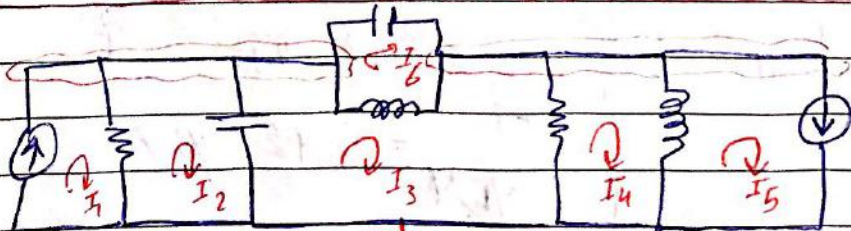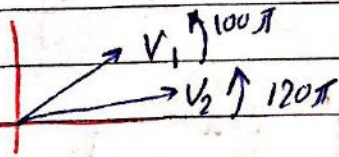

mesh analysis: # of meshes - # of current sources = 4 variables.


nodal analysis: # of nodes - # of voltage sources - Ref. = 2.

nodal best to use.

Find V_1 & V_2 ?

No. _____

Ex 10.8 (Hayt)

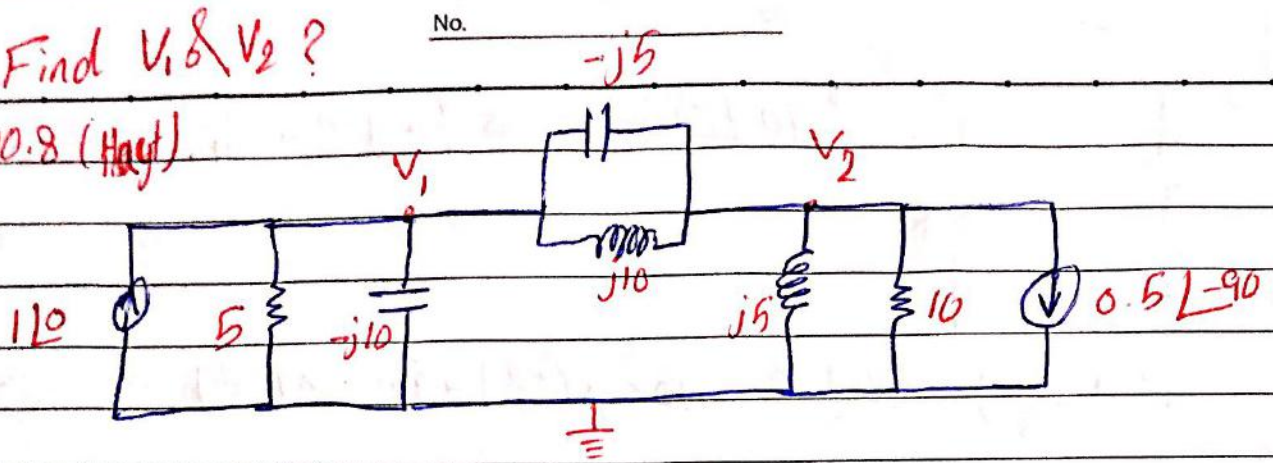

⇒ Nodal analysis:

at V_1 :

$$110 + \frac{0 - V_1}{5} + \frac{0 - V_1}{-j10} + \frac{V_2 - V_1}{-j5} + \frac{V_2 - V_1}{j10} = 0$$

solving:

$$\begin{aligned} V_1 &= 2.24 \angle -63.4^\circ \\ V_2 &= 4.47 \angle 16.6^\circ \end{aligned}$$

at V_2 : $-0.5 \angle -90^\circ + \frac{0 - V_2}{10} + \frac{0 - V_2}{j5} + \frac{V_1 - V_2}{-j5} + \frac{V_1 - V_2}{j10} = 0$



⇒ V_1 in time domain: $v_1(t) = 2.24 \cos(\omega t - 63.4^\circ)$ volt.

Time domain

phasor domain


R	R
L	$j\omega L$
C	$1/j\omega C$
$V_L(t) = L \frac{di_L(t)}{dt}$	$V_L = j\omega L I$
$i_C(t) = C \frac{dV_C(t)}{dt}$	$I_C = j\omega C V_C$

* phase shift:

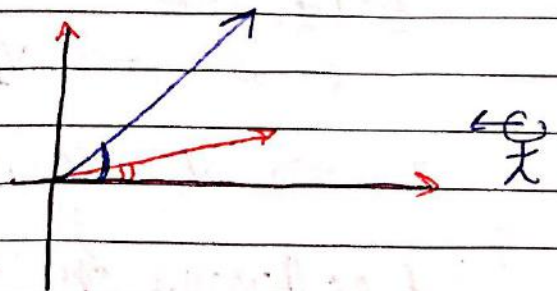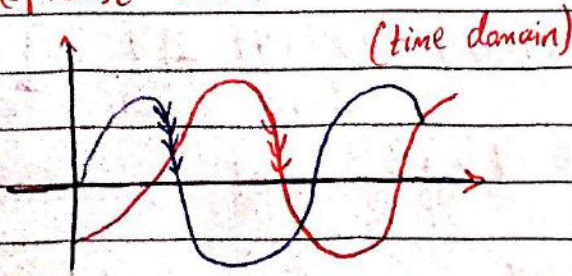

the blue wave leading.

the blue wave leading.

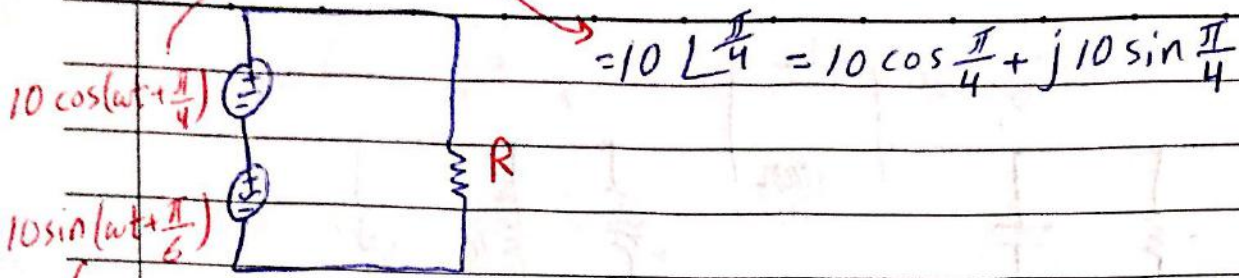


$$= 10 \angle \frac{\pi}{4} = 10 \cos \frac{\pi}{4} + j 10 \sin \frac{\pi}{4}$$

$$\hookrightarrow 10 \cos(\omega t - \frac{\pi}{3}) = 10 \angle -\frac{\pi}{3} = 10 \cos(\frac{-\pi}{3}) + j 10 \sin(\frac{-\pi}{3})$$

$$\Rightarrow i(t) = \frac{10 \cos(\omega t + \frac{\pi}{4})}{R} + \frac{10 \sin(\omega t + \frac{\pi}{6})}{R}$$

$$\Rightarrow I = \frac{V}{R}$$

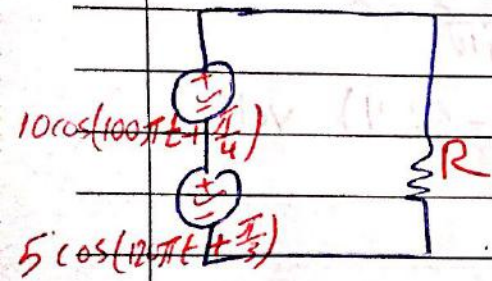

\Rightarrow "super position"

$$I = I' + I'', \quad I' = \frac{5 \cos(120\pi t + \frac{\pi}{3})}{R}$$


Ex. Find V_1 using super position?

$$V_1 = V_1' + V_1''$$

Killing current source:

$$V_1' = 11 \angle 0 \times \frac{(4-j2)(2+j4)}{6-j8}$$


$$= \boxed{2-j2} \text{ volt.}$$

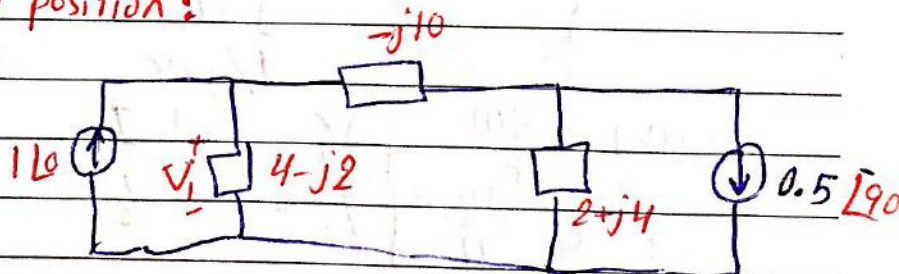


Killing voltage source: $\Rightarrow V_1'' = (0.5 \angle -90^\circ) \frac{(2+j4)}{6-j8} = \boxed{1} \text{ volt.}$

$$\Rightarrow V_1 = (2-j2) - 1 = \boxed{1-j2} \text{ volt.}$$

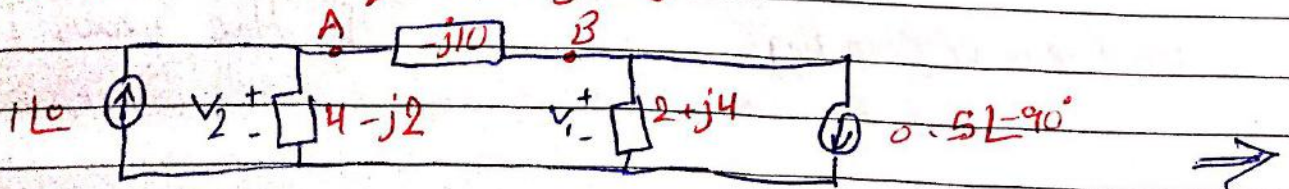Ex. Find the thevenin eq. seen by $-j10$:



No.

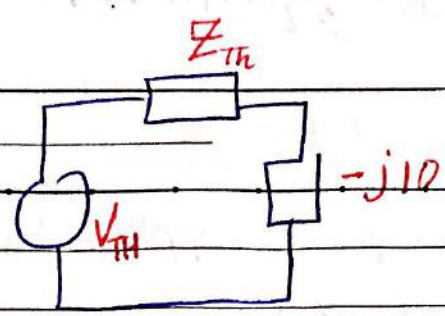

⇒ The expected circuit:

since there is no dependent sources; (Kill the sources)


$$Z_{TH} = \frac{V_{oc}}{I_{sc}}$$

$$Z_{TH} = (4 - j2) + (2 + j4) = \boxed{6 + j2} \Omega$$

$$\Rightarrow V_{oc} = V_2 - V_1$$

$$V_1 = -(2 + j4)(0.5 \angle -90^\circ)$$

$$V_2 = 1 \angle 0^\circ * (4 - j2)$$

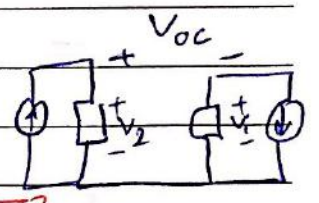


$$V_{oc} = (4 - j2)(1 \angle 0^\circ) + (2 + j4)(0.5 \angle -90^\circ) = \boxed{6 - j3} \text{ volt.}$$

New Subject:

* Instantaneous Power:

* in DC systems: $P = VI$

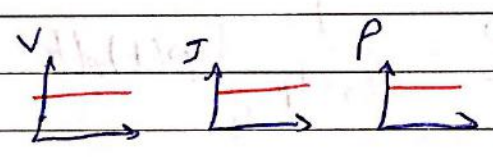


* in AC systems: $R: P(t) = v(t)i(t) = i^2(t) * R = \frac{v^2(t)}{R}$

$$L: P(t) = i(t)v(t) = i(t)L \frac{di(t)}{dt} = v(t) * \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$

$$C: P(t) = i(t)v(t) = v(t)C \frac{dv(t)}{dt} = i(t) * \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$

Ex. given: $v(t) = V_0 u(t)$
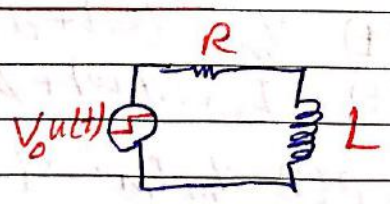
$$i(t) = \frac{V_0}{R} \left[1 - e^{-\frac{Rt}{L}} \right] u(t)$$



* inst. power supplied by the source:

$$P(t) = \frac{V_0^2}{R} \left[1 - e^{-\frac{Rt}{L}} \right] u(t)$$

Note:
 $u(t) = \begin{cases} 1, & t > 0 \\ 0, & t < 0 \end{cases}$

* inst. power absorbed by the resistor:


$$P(t) = i^2(t) R = \frac{V_0^2}{R} \left[1 - e^{-\frac{Rt}{L}} \right]^2 u(t)$$

* absorbed power by the inductor:

$$P(t) = i(t) * L \frac{di(t)}{dt} = \frac{V_0}{R} \left[1 - e^{-\frac{Rt}{L}} \right] * L * \left(-\frac{R}{L} \right) * \frac{V_0}{R} e^{-\frac{Rt}{L}} u(t) = \frac{V_0^2}{R} \left(-\frac{R}{L} \right) \left(1 - e^{-\frac{Rt}{L}} \right) e^{-\frac{Rt}{L}} u(t)$$

*Note:
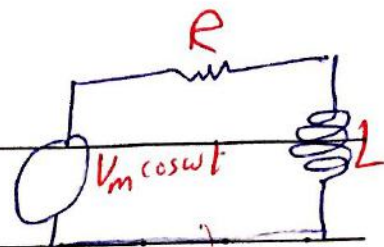
$$\cos A \cos B = \frac{1}{2} [\cos(A+B) + \cos(A-B)]$$



Ex. Sinusoidal ckt:

Find the power supplied by the source?

$$P(t) = i(t) v(t)$$

$$= V_m \cos \omega t * I_m \cos(\omega t + \phi)$$

Let's suppose


$$i(t) = I_m \cos(\omega t + \phi)$$

$$= \frac{V_m I_m}{2} [\cos(2\omega t + \phi) + \cos \phi]$$

⇒ ** Average Power:

↳ more accurate & more descriptive.
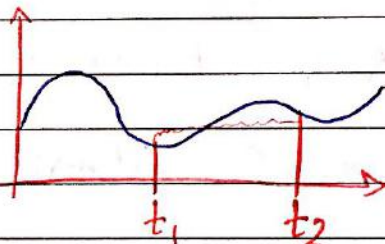
$$P = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} P(t) dt$$



⇒ for a periodic signal:

$$P = \frac{1}{T} \int_T P(t) dt$$

Let us assume for a sinusoidal ckt:

$$v(t) = V_m \cos(\omega t + \theta)$$

$$i(t) = I_m \cos(\omega t + \phi)$$

For any element.

$$\Rightarrow P(t) = V_m I_m \cos(\omega t + \theta) \cos(\omega t + \phi) = \frac{V_m I_m}{2} [\cos(2\omega t + \theta + \phi) + \cos(\theta - \phi)]$$

Average Power:

$$P = \frac{1}{T} \int_T P(t) dt = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

let $T = 2\pi$

$$P = \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi) dt + \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m}{2} \cos(\theta - \phi) dt$$

$$= \frac{1}{2\pi} \frac{V_m I_m}{2} \cos(\theta - \phi) * 2\pi = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

voltage for Z Not V on R .

Ex. $v(t) = 4 \cos\left(\frac{\pi}{6}t\right)$, $Z = 2 \angle 60^\circ$

* find the average power absorbed by the impedance?

$V = 4 \angle 0^\circ$, $I = \frac{V}{Z} = \frac{4 \angle 0^\circ}{2 \angle 60^\circ} = 2 \angle -60^\circ$


$\Rightarrow P = \frac{1}{2} V_m I_m \cos(\theta - \phi) = \frac{1}{2} \times 4 \times 2 \times \cos(0 - 60) = \boxed{2} \text{ W}$

* find the instantaneous power?

$v(t) = 4 \cos\left(\frac{\pi}{6}t\right)$ & $i(t) = 2 \cos\left(\frac{\pi}{6}t - 60^\circ\right)$

$\Rightarrow p(t) = 8 \cos\left(\frac{\pi}{6}t\right) \cos\left(\frac{\pi}{6}t - 60\right) = \boxed{2 + 4 \cos\left(\frac{\pi}{3}t - 60\right)}$


In a Resistor:

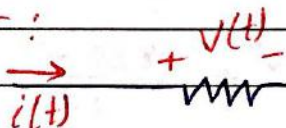


Average Power absorbed in R :

$P = \frac{V_m I_m}{2} \cos(\theta - \phi) = \boxed{\frac{V_m I_m}{2}}$ ***

In inductor:

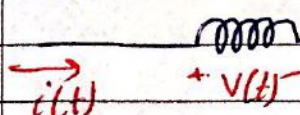

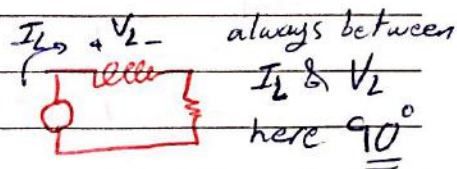$P = \frac{V_m I_m}{2} \cos(\theta - \phi) = \boxed{0}$ ***



First 2 weeks

* average power (R) = $\frac{1}{2} V_m I_m = \frac{1}{2} \frac{V_m^2}{R} = \frac{1}{2} I_m^2 R$

(ex.) Find the average power delivered to the impedance $Z_L = 8 - j11$ when $I = 3 + j4$

** $P_{avg} = 0$ for any X .

$P_{avg} = \frac{1}{2} R I_m^2 = \frac{1}{2} (8) (5)^2 = \boxed{100} \text{ W}$

for instantaneous power: $p(t) = i(t) v(t)$

$i(t) = 5 \cos(\omega t + \phi)$; $\phi = \tan^{-1}\left(\frac{4}{3}\right)$


$$\Rightarrow V = (8 - j11)(3 + j4)^{\text{No.}} = 6.4 - j = 6.8 \angle -0.84$$

$$v(t) = 6.8 \cos(\omega t - 0.84)$$

$$\Rightarrow P = i(t) * v(t) = 100 + 170 \cos(\omega t + 52.26^\circ)$$

Ex: Find the average power absorbed by elements and generated by sources?

$$P_{\text{avg}} = \text{Zero.}$$

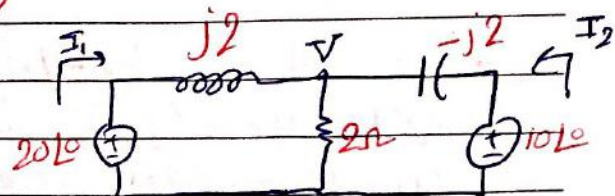

* Nodal analysis:

$$\text{At } V: \frac{20 \angle 0 - V}{j2} + \frac{0 - V}{2} + \frac{10 \angle 0 - V}{-j2} = 0$$

$$\Rightarrow -j10 + 0.5jV - 0.5V + j5 - 0.5jV = 0$$

$$\Rightarrow V = 10 \angle -90^\circ$$


$$P_{\text{avg}} = \frac{V^2}{2R} = \frac{100}{2 \times 2} = 25 \text{ W}$$

$$I_1 = \frac{20 \angle 0 - 10 \angle -90}{j2} = 11.18 \angle -63.43^\circ$$

$$P_{\text{avg}} = \frac{20 \times 11.18 \cos(0 + 63.43^\circ)}{2} = 50 \text{ W}$$

$$I_2 = \frac{10 \angle 0 - 10 \angle -90}{-j2} = 7.07 \angle -45^\circ \Rightarrow P_{\text{avg}} = \frac{7.07 \times 10 \cos(45^\circ)}{2} = 25 \text{ W}$$


Maximum Power Transfer:

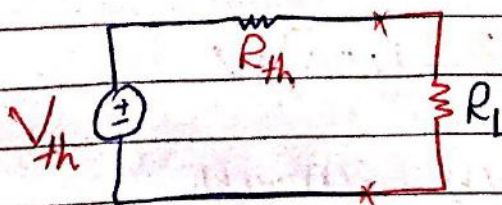

\Rightarrow occurs: $R_{\text{th}} = R_L$



* maximum power transfer: (occurs)

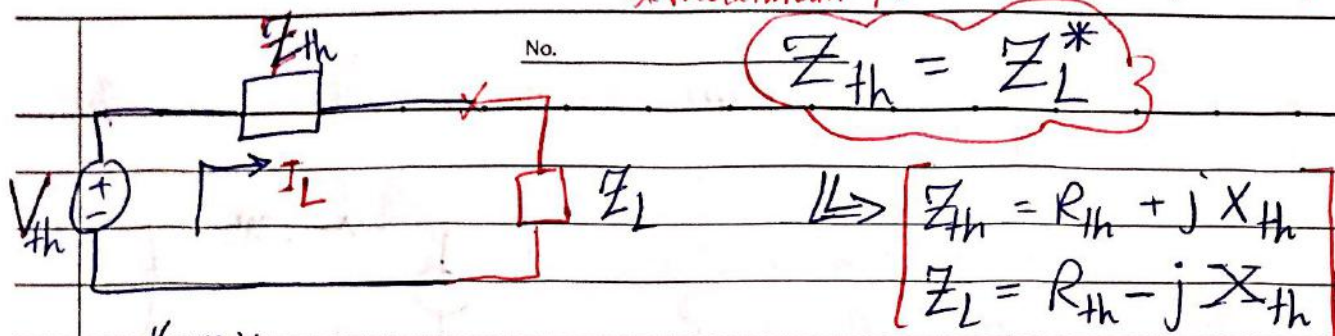

we know:

$$I_L = \frac{V_{th}}{Z_{th} + Z_L} = \frac{V_{th}}{R_{th} + jX_{th} + R_L + jX_L}$$

also: $V_L = V_{th} * \frac{Z_L}{Z_L + Z_{th}} = \frac{V_{th} (R_L + jX_L)}{R_L + jX_L + R_{th} + jX_{th}}$

so, $P_{avg} = \frac{1}{2} |V_L| |I_L| \cos(\theta - \phi)$

$$|I_L| = \frac{|V_{th}|}{\sqrt{(R_L + R_{th})^2 + (X_L + X_{th})^2}}$$

$$\angle I_L = \angle V_{th} - \tan^{-1} \left(\frac{X_{th} + X_L}{R_{th} + R_L} \right)$$

$$|V_L| = \frac{|V_{th}| \times \sqrt{R_L^2 + X_L^2}}{\sqrt{(R_L + R_{th})^2 + (X_L + X_{th})^2}}$$

$$\angle V_L = \angle V_{th} + \tan^{-1} \left(\frac{X_L}{R_L} \right) - \tan^{-1} \left(\frac{X_{th} + X_L}{R_{th} + R_L} \right)$$

Now: $P = \frac{|V_{th}|^2 \sqrt{R_L^2 + X_L^2}}{2[(R_L + R_{th})^2 + (X_L + X_{th})^2]} * \cos \left| \tan^{-1} \left(\frac{X_L}{R_L} \right) \right|$

Derive P w.r.t $R_L \Rightarrow R_L = R_{th}$


Derive P w.r.t $X_L \Rightarrow X_L = -X_{th}$

so $Z_{th} = Z_L^*$ maximize the power.

(ex) Find Z_L that maximize the power to the load?


$Z_{th} = 500 + j3$

$Z_L = Z_{th}^* = 500 - j3$

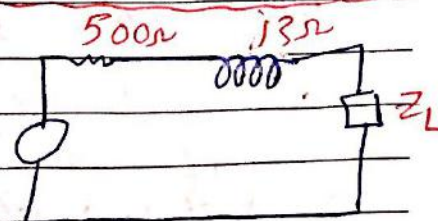

* what is the maximum power transfer for the shown ckt:

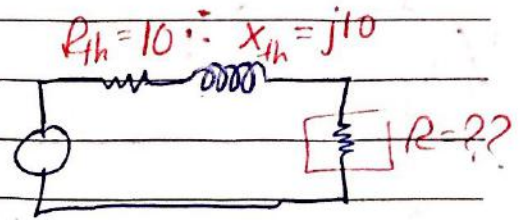⇒ what is R that maximize the transferred power?



$$R_L = \sqrt{R_{th}^2 + X_{th}^2} \Rightarrow R_L = 10\sqrt{2} \Omega$$

* Non-periodic signals:

Let's suppose:

$$i(t) = \sin t + \sin \pi t, R = 1$$

find the average power?

$$P = \frac{1}{T} \int p(t) dt; p(t) = i^2(t) * R$$

$$\Rightarrow p(t) = (\sin^2 t + 2 \sin t \sin \pi t + \sin^2 \pi t) R$$

$$\Rightarrow P = \frac{R}{T} \int \sin^2 t dt + \frac{R}{T} \int 2 \sin t \sin \pi t dt + \frac{R}{T} \int \sin^2 \pi t dt$$

$$\left(\frac{1}{2}\right) - \frac{1}{2} \cos 2t$$

using trigonometric rules

$$\left(\frac{1}{2}\right) - \frac{1}{2} \cos 2\pi t$$

it will give Zero

$$P = \frac{R}{T} \left(\frac{T}{2} + \frac{T}{2}\right) = 1 \text{ W}$$

* Suppose $i(t) = I_{m1} \sin \omega_1 t + I_{m2} \sin \omega_2 t + I_{m3} \sin \omega_3 t + \dots$

$$P_{avg} = \frac{1}{2} I_{m1}^2 R + \frac{1}{2} I_{m2}^2 R + \frac{1}{2} I_{m3}^2 R + \dots$$



$$P_{avg} = \frac{V_{m1}^2}{2R} + \frac{V_{m2}^2}{2R} + \dots$$

(ex) find the average power: $i(t) = 3 \cos 10t - 4 \sin 20t$
 $R = 5 \Omega$?

$$P_{avg} = \frac{1}{2} I_{m1}^2 R + \frac{1}{2} I_{m2}^2 R = \frac{1}{2} * 9 * 5 + \frac{1}{2} * 16 * 5 = 62.5 \text{ W}$$

it is Not (-)

always the magnitude +ve.


(ex.) Find the average power:

$$i(t) = 2 \cos 10t - 3 \sin 10t, \quad R = 4$$

$$\hookrightarrow i(t) = -\cos 10t \Rightarrow P_{avg} = \frac{1}{2} (1)^2 \times 4 = \boxed{2} \text{ W.}$$

(ex.) $i(t) = 2 \cos 10t + 3 \sin 10t$ find P_{avg} ?

✱ Root Mean Square values [RMS]:


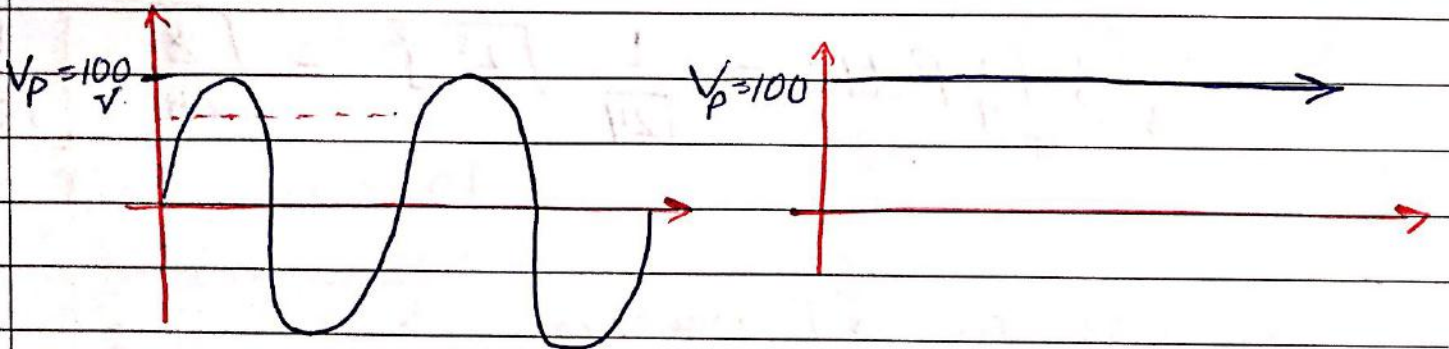


$$V_p = ??$$

$$V_{avg} = \text{Zero}$$

* Compare between:

RMS

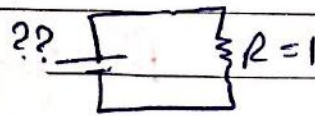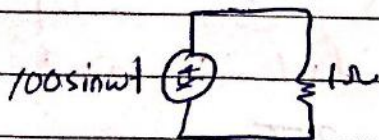

$$P = \frac{1}{2} \frac{V_m^2}{R}$$

$$= 5000 \text{ W}$$

$$?? \quad 5000 = \frac{V^2}{R}$$

$$\Rightarrow \boxed{V = 70.7 \text{ Volt}}$$


$$P_{ac} = P_{dc} \Rightarrow \frac{1}{R} \times \frac{1}{T} \int_V v^2(t) dt = \frac{V^2}{R}$$

$$\Rightarrow \boxed{V_{eff} = V_{DC} = V_{RMS} = \sqrt{\frac{1}{T} \int_V v^2(t) dt}}$$

(Ex.) Find the RMS value for the shown ^{No.}

$\Rightarrow T = 2 \text{ sec.}$
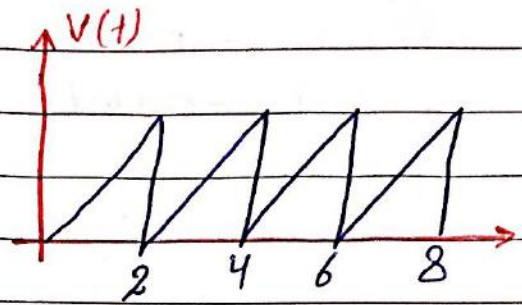
$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$




Find $v(t) \Rightarrow v(t) = \frac{1}{2}t \text{ volt}$

$$V_{rms} = \sqrt{\frac{1}{2} \int_0^2 \frac{1}{4} t^2 dt} = \frac{1}{\sqrt{24}} \sqrt{t^3 \Big|_0^2} = \sqrt{\frac{8}{24}} = \boxed{\frac{1}{\sqrt{3}}} \text{ Volt}$$

* Rms value for ST waveform:

$$I_{rms} = \frac{1}{\sqrt{3}}$$

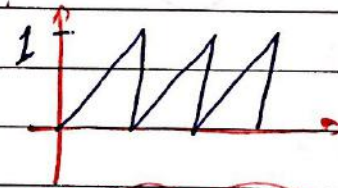

\Rightarrow in general for ST

$I_m \rightarrow \text{peak}$

$$\Rightarrow I_{rms} = \frac{I_m}{\sqrt{3}}$$

* Rms value for a sinusoidal signal:

$$i(t) = I_m \cos(\omega t + \phi), \quad T = \frac{2\pi}{\omega}$$

$$I_{rms}^2 = \frac{1}{T} \int_0^T i^2(t) dt = \frac{\omega}{2\pi} \int_0^{2\pi/\omega} I_m^2 \left[\frac{1}{2} + \frac{1}{2} \cos(2\omega t + 2\phi) \right] dt$$

$$I_{rms}^2 = \frac{\omega}{2\pi} \times \frac{I_m^2}{2} \times \frac{2\pi}{\omega} \Rightarrow I_{rms} = \frac{I_m}{\sqrt{2}}$$

* * Note: Always if the question doesn't determine that the value peak or rms \Rightarrow solve as rms.

$$v(t) = 10 \cos(\omega t + \phi)$$

\hookrightarrow always it is a peak value.

10 volt \rightarrow it is rms value.

* For a sinusoidal signals: [for a Resistor]

$$P_{avg} = \frac{1}{2} V_m I_m = \frac{1}{2} (\sqrt{2} V_{rms}) (\sqrt{2} I_{rms}) = V_{rms} I_{rms}$$


$$\Rightarrow P_{avg} = V_{rms} I_{rms} = V_{eff} I_{eff} \Rightarrow P_{avg} = \frac{V_{rms}^2}{R} = I_{rms}^2 R$$

* In general:

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = V_{rms} I_{rms} \cos(\theta - \phi)$$

(ex) Find the rms value for: $i(t)$
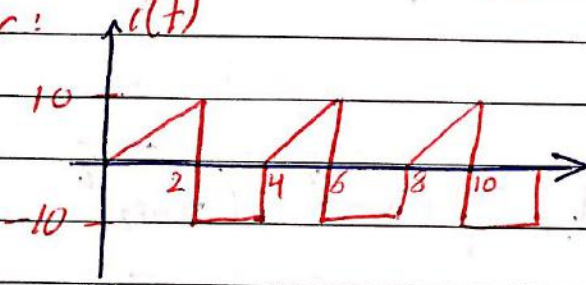
$$T = 4, i(t) = \begin{cases} 5t, & 0 < t < 2 \\ -10, & 2 < t < 4 \end{cases}$$




$$I_{rms}^2 = \frac{1}{4} \left[\int_0^2 25t^2 dt + \int_2^4 100 dt \right] = \frac{1}{4} \left[\frac{25(8)}{3} + 200 \right]$$

$$\Rightarrow I_{rms} = \frac{1}{2} \sqrt{\frac{25(8)}{3} + 200} = \boxed{8.165 \text{ A}}$$

(ex) find rms value for:

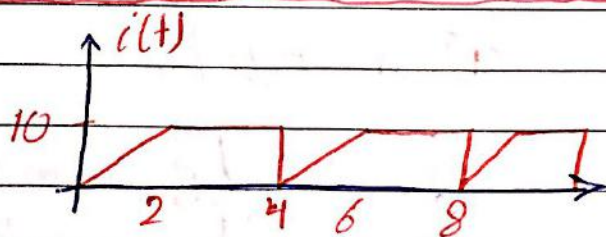
\Rightarrow the same as the previous example



$$\Rightarrow \boxed{I_{rms} = 8.165 \text{ A}}$$

(ex) find rms:
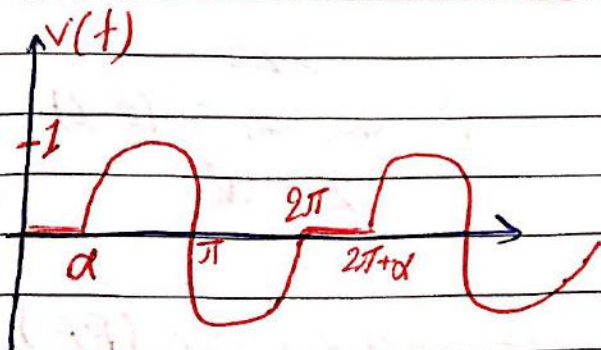
$$T = 2\pi, v(t) = \begin{cases} 0, & 0 < t < \alpha \\ \sin t, & \alpha < t < 2\pi \end{cases}$$



$$I_{rms}^2 = \frac{1}{2\pi} \int_{\alpha}^{2\pi} \sin^2 t dt$$

$$\left(\frac{1}{2} - \frac{1}{2} \cos 2t \right)$$

Effective value for signals with multiple frequencies:


$$P_{avg} = \frac{1}{2} (I_{m1}^2 + I_{m2}^2 + I_{m3}^2 + \dots) R$$

↪ $(\sqrt{2} I_{rms1})$

$$\Rightarrow P_{avg} = (I_{rms1}^2 + I_{rms2}^2 + \dots) R \quad \text{***}$$

$$I_{rms} = \sqrt{I_{rms1}^2 + I_{rms2}^2 + I_{rms3}^2 + \dots} \quad \text{***}$$

Ex. Find rms value:

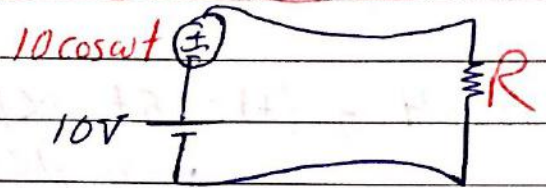


$$V_{rms} = \sqrt{(V_{rms1})^2 + (V_{rms2})^2}$$

$$= \sqrt{\left(\frac{10}{\sqrt{2}}\right)^2 + 100} = \sqrt{150} \text{ Volt}$$

* if he asked about average power: $P_{avg} = \frac{V_{rms}^2}{R}$
 $= \frac{150}{R} \text{ watt.}$


Power Factor:

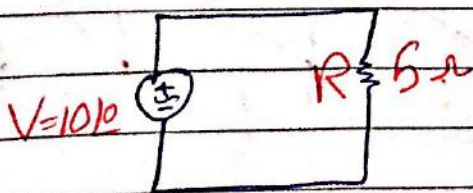

$$I = 2 \angle 0^\circ$$

$$P = V_{rms} I_{rms} \cos(\theta - \phi)$$

$$= 20 \text{ W}$$

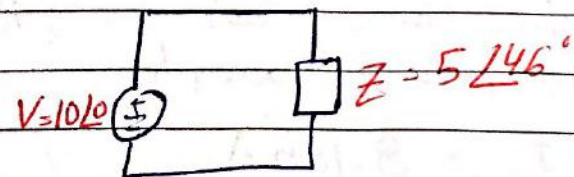

$$I = 2 \angle -45^\circ$$

$$P = V_{rms} I_{rms} \cos(\theta - \phi)$$

$$= 10 \times 2 \times \frac{1}{2} = \frac{20}{2} \text{ W}$$

$$\Rightarrow \text{Power factor (PF)} = \frac{\text{Real Power}}{\text{Apparent Power}}$$

$$= \frac{V_{rms} I_{rms} \cos(\theta - \phi)}{V_{rms} I_{rms}} = \cos(\theta - \phi) = \text{PF}$$

* Power factor for a sinusoidal signal:

for R Loads $\rightarrow \cos(\theta - \phi) = 1$

for X Loads $\rightarrow \cos(\theta - \phi) = 0$


for RX Loads $\rightarrow [0 - 1]$

(ex.) Find the source PF?


$V = 60 \angle 0^\circ$ (it is rms value)

$$I_{rms} = \frac{V_{rms}}{3 + j4} = 12 \angle -53.13^\circ$$
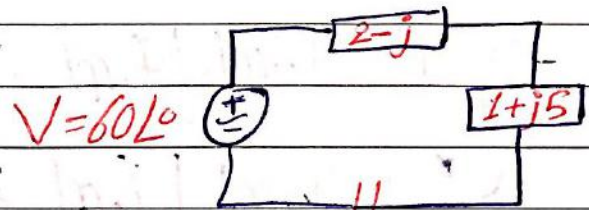
$$PF_{source} = \cos(0 + 53.13^\circ) = 0.6 \text{ (lagging)}$$




↓ inductive

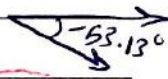


(ex.) $I_{rms} = \frac{V_{rms}}{3 - j4} = 12 \angle +53.13^\circ$
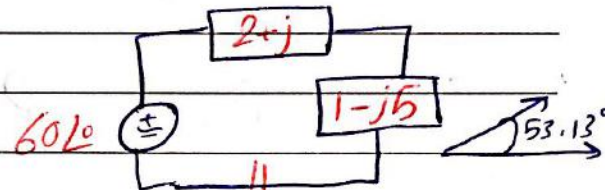
$$PF_{source} = \cos(0 - 53.13^\circ) = 0.6 \text{ (leading)}$$



↓ Capacitive

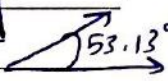



Another way

$$PF = \frac{\text{Real Power}}{\text{Apparent Power}} \quad ; \quad \text{Apparent power} = 60 \times 12 = 720 \text{ W}$$

$$; \text{ Real Power} = (I_{rms})_1^2 + (I_{rms})_2^2 = 144 \times 1 + 288 = 432 \text{ W}$$

$$PF = \frac{432}{720} = 0.6$$

* Complex Power: [some power is lost]

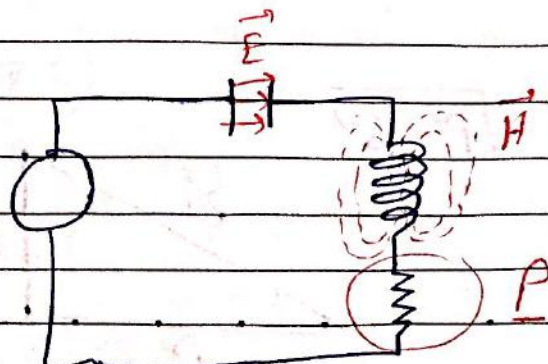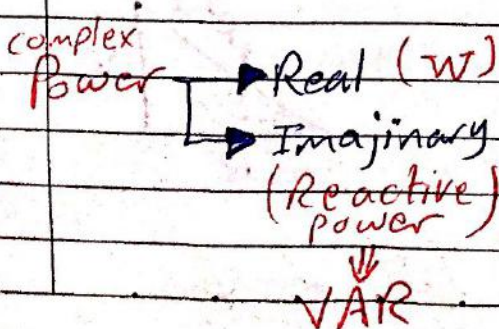

Complex Power \rightarrow Real (W)
 \rightarrow imaginary (Reactive power) \Rightarrow VAR

\rightarrow Rate of energy transfer in L & C.
 \rightarrow Rate of charge & discharge.

* Suppose $V = |V_{eff}| \angle \theta$, $I = |I_{eff}| \angle \phi$

$$\Rightarrow P = |V_{eff}| |I_{eff}| \cos(\theta - \phi) = |V_{eff}| |I_{eff}| \operatorname{Re} \left\{ e^{j(\theta - \phi)} \right\}$$

$$S = |V_{eff}| |I_{eff}| e^{j(\theta - \phi)}$$

$$= \underbrace{|V_{eff}| e^{j\theta}}_V \underbrace{|I_{eff}| e^{-j\phi}}_{I^*} = \boxed{V I^*} = S$$

$\cos(\theta - \phi) + j \sin(\theta - \phi)$

Complex Power = Real Power + Reactive Power

$$\boxed{S = P + jQ} \quad ***$$

$$\Rightarrow S = V_{rms} I_{rms}^* = \frac{1}{2} V_m I_m^* \quad \text{VA}$$



$$P = V_{rms} I_{rms} \cos(\theta - \phi) \quad \text{W}$$

$$Q = V_{rms} I_{rms} \sin(\theta - \phi) \quad \text{VAR}$$

$$|S| = |V_{rms}| * |I_{rms}| \quad \text{VA}$$

* Power Triangle:

$$|S| = \sqrt{P^2 + Q^2}$$

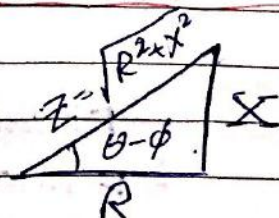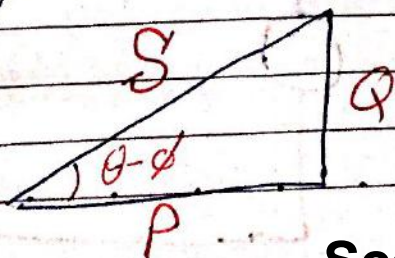


$$\Rightarrow \angle S = \theta - \phi$$

(ex.) Find the Complex Power absorbed/produced
By sources & elements:

assume I_{total} flowing from the voltage source:

$$I_{total} = \frac{120 \angle 0}{5}$$
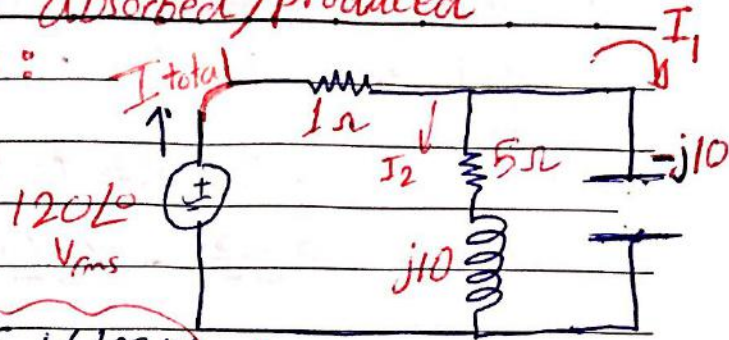
$$= \frac{120 \angle 0}{1 + \frac{(5+j10) \times (-j10)}{5}} = 5.16 \angle 25.46^\circ \text{ A}$$



*the resistor always give a real power.

$$P_{avg}(1\Omega) = I_{rms}^2 R = (5.16)^2 \times 1 = 26.6 \text{ W}$$

$$S(1\Omega) = V_{rms} \times I_{rms}^* = 5.16 \angle 25.46^\circ + 5.16 \angle -25.46^\circ = 26.6 \text{ VA}$$

$$S_{(-j10)} = V_{rms} I_{rms}^*$$

$$I_1 = I_{total} \times \frac{5+j10}{5} = 11.53 \angle 88.89^\circ \text{ A}$$

$$V_{rms(-j10)} = I_{rms} (-j10) = (11.53 \angle 88.89^\circ) (-j10) = 115.3 \angle -1.11^\circ \text{ Volt}$$

$$S_{(-j10)} = (115.3 \angle -1.11^\circ) (11.53 \angle -88.89^\circ) = 1331 \angle -90^\circ = -j1331 \text{ VA}$$

$$\Rightarrow Q = V_{rms} I_{rms} \sin(-1.11 - 88.89) \quad \text{VAR}$$

since it represent Q here.

$$= -1331 \text{ VAR}$$

$$S_{(5+j10)} = V_{rms} I_{rms}^* \Rightarrow I_2 = I_{tot} - I_1 = 10.31 \angle -64.53^\circ \text{ A}$$

$$V_{(5+j10)} = 115.3 \angle -1.11^\circ \text{ V}$$

$$= (115.3 \angle -1.11^\circ) (10.31 \angle +64.53^\circ)$$

$$= 531.48 + j1062.96 \text{ VA}$$

$$S_{(source)} = (120 \angle 0) (5.16 \angle -25.46^\circ) = 558.98 - j266.14 \text{ VA}$$

* Find the average power across $4\ \Omega$ Resistor when:

$$v(t) = 8 \sin(200t) - 6 \cos(200t - 45^\circ)$$

$$\hookrightarrow 8 \cos(200t - \frac{\pi}{2})$$

$$\Rightarrow V = 8 \angle \frac{-\pi}{2} - 6 \angle -45^\circ = 8 \cos(\frac{-\pi}{2}) + j \sin(\frac{-\pi}{2}) - 6 \cos(-45^\circ) - j 6 \sin(-45^\circ)$$

$$V = -4.24 - j 3.75$$

$$|V| = 5.66 \Rightarrow P = \frac{V_m^2}{2R} = \boxed{4.01\ W}$$

\Rightarrow if we add (4) to $v(t)$:


$$V(t) = \underbrace{8 \sin 200t - 6 \cos(200t - 45^\circ)}_{P_1} + \underbrace{4}_{P_2}$$

$$V_{rms} = \sqrt{V_{rms1}^2 + V_{rms2}^2} = \sqrt{\left(\frac{5.66}{\sqrt{2}}\right)^2 + (4)^2} = \boxed{5.66\ volt}$$

(ex) Find the RMS value for: $v(t)$

$$T = 0.02\ sec.$$
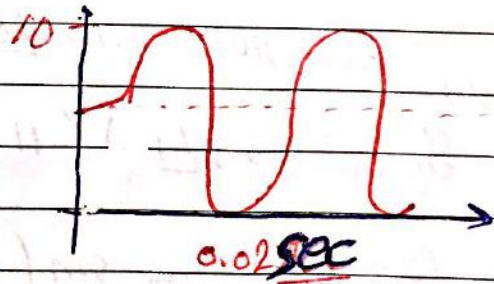
$$v(t) = 5 + 5 \sin\left(\frac{2\pi}{0.02} t\right)$$



$$V_{rms} = \sqrt{\frac{1}{0.02} \int_0^{0.02} (5 + 5 \sin(100\pi t))^2 dt}$$

$$\text{if we want } V_{avg} = \frac{1}{0.02} \int_0^{0.02} (5 + 5 \sin(100\pi t)) dt$$

gives zero

$$= \frac{1}{0.02} \times 0.1 = \boxed{5\ volt}$$

* Another way to find V_{rms} ?

$$V_{rms} = \sqrt{V_{rms1}^2 + V_{rms2}^2} = \sqrt{(5)^2 + \left(\frac{5}{\sqrt{2}}\right)^2} = \boxed{6.124\ volt}$$


* (ex) Find the PF for $i(t) = 4 \cos(100\pi t + 10^\circ)$ A

$$v(t) = 120 \cos(100\pi t - 20^\circ) \text{ V}$$

$$PF = \cos(\theta - \phi) = \cos(-30) = \frac{\sqrt{3}}{2} \text{ Leading}$$

$$Z = \frac{120 \angle -20^\circ}{4 \angle 10^\circ} = 30 \angle -30^\circ$$

$$PF = \cos(-30) = \frac{\sqrt{3}}{2}$$

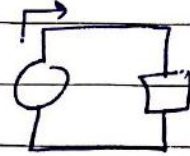


(ex) Load power factor:

$$PF = \cos(-30) = \frac{\sqrt{3}}{2} = 0.866$$

Source PF:

$$PF = \cos(\theta - \phi)$$
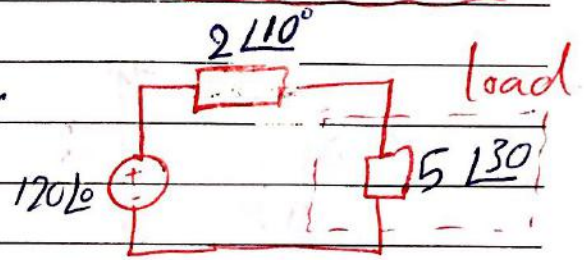
$$I = \frac{120}{2 \angle 10^\circ + 5 \angle 30^\circ} = 17.36 \angle -24.32^\circ \Rightarrow PF = \cos(24.32) = 0.911$$



(ex) Determine the load impedance Z_L that maximize the average power drawn from the ckt & what is that average max power?

Need Z_{th} at first.

Killing the source

$$\text{we have } (4 \Omega) \parallel (8 - j6) = Z$$

then Z series with $(j5)$ gives Z_{th} .


$$Z_{th} = j5 + \frac{(4)(8 - j6)}{12 - j6} = 2.933 + j4.467 \Omega$$

$$\text{So, } Z_L = 2.933 - j4.467 \Omega$$


using voltage division to find V_{th} :

$$V_{th} = 10 \angle 0 \frac{(8 - j6)}{12 - j6} = 7.454 \angle -10.3^\circ$$

$$\Rightarrow P_{max} = \frac{|V_{th}|^2}{8 |Z_{th}|} = 1.3 \text{ W}, \quad P_{avg} = \frac{V_{th}^2}{8R} = 2.368 \text{ W}$$

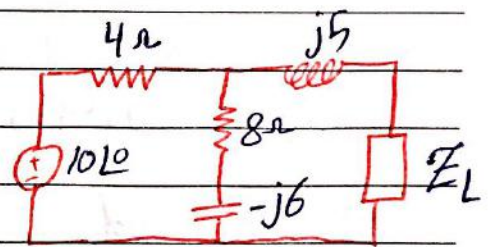


Thevenin Equivalent:

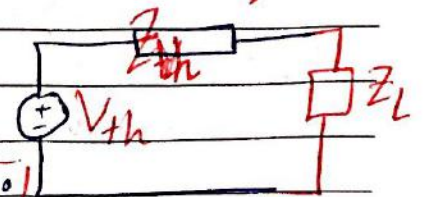



* PF Correction:

No. _____

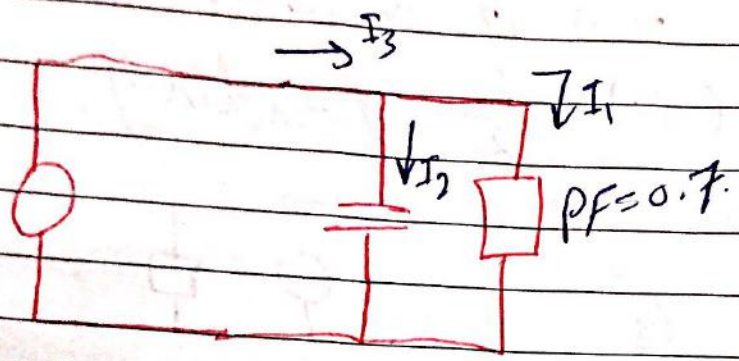

* After adding the capacitor:

* Before adding the capacitor:

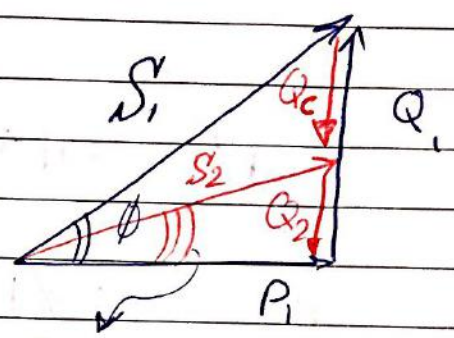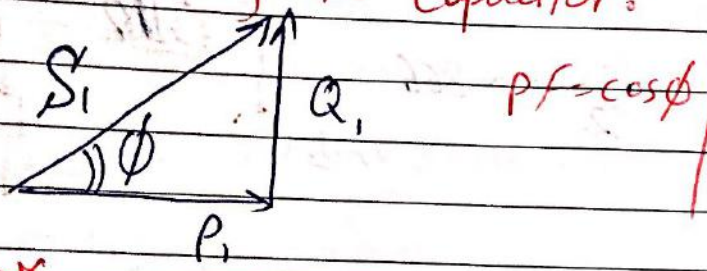


the angle $\angle \phi$ so PF will increase.

$$Q_2 = Q_1 + Q_c$$

(total)


EX Induction motor is operating @ 50KW & 0.8 Lagging PF & $V_s = 230V_{rms}$. (given $f = 50Hz$)

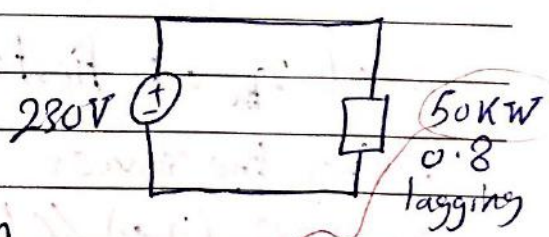demand: \Rightarrow we need to make the $PF = 0.95$



\Rightarrow we need to add a capacitor in parallel with the motor.

Before:

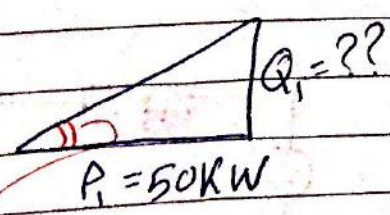

if he want S_2

$$S = \sqrt{(Q_1)^2 + (P)^2} = 62.5 \text{ KVA}$$


from the unit you must know it is Real power here.

$$\phi = \cos^{-1}(0.8) = 36.87^\circ$$

$$\tan(36.87) = \frac{Q_1}{P_1} \Rightarrow Q_1 = 37.5 \text{ KVAR}$$


After:
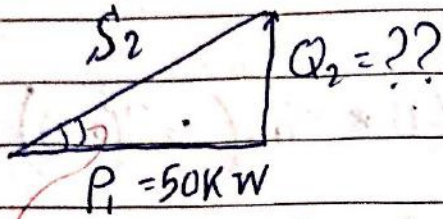
$$\Rightarrow \tan 18.19 = \frac{Q_2}{50 \text{ kW}}$$



$$Q_2 = 16.43 \text{ KVAR}$$

$$\cos(0.96) = 18.19$$

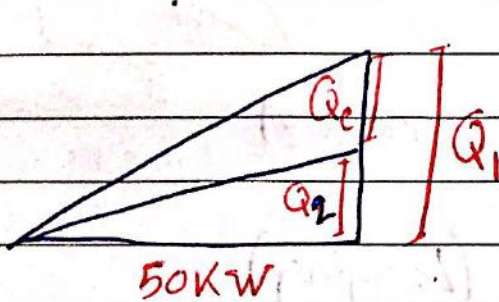

$$Q_c = 16.43 - 37.5$$

$$= -21.06 \text{ KVAR}$$

$$Q_2 = Q_1$$

Now How to find the capacitance?

$$Q = V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i) \Rightarrow |Q_c| = |V_{\text{rms}}| |I_{\text{rms}}|$$

$$= \frac{|V_{\text{rms}}|}{|X_c|}$$

$$X_c = \frac{1}{j\omega C} \Rightarrow |X_c| = \frac{1}{\omega C}$$

$$\text{so } Q_c = |V_{\text{rms}}|^2 \omega C \Rightarrow C = \frac{|Q_c|}{|V_{\text{rms}}|^2 \omega}$$

$$C = \frac{|Q_c|}{|V_{\text{rms}}|^2 \omega}$$

$$\Rightarrow C = \frac{21.67 \times 10^3}{(230)^2 \times 2\pi \times 50} = 1.3 \text{ mF}$$

suggested problems: 10.7/10.11/10.26/10.38/10.43/10.49/10.53/10.56/10.60

CH II (2, 5, 12, 13, 14, 18, 22, 24, 26, 28, 32, 34, 38, 41, 42, 46 → 54, 69, 72, 73, 74, 75) sixth edition of sadiku


Problem 11.52 sadiku sixth edition:

given:

A: 2 kW @ 0.8 pf Lag.

B: 3 KVA @ 0.4 pf leading.

C: consumes 1 kW & receives 500 VAR.

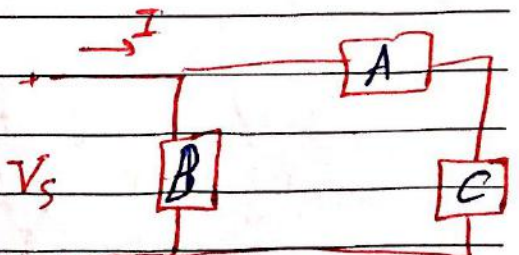

①

find PF of the source?

No.

since it is leading.


for B: $S = 3 \text{ kVA}$, $\text{PF} = 0.4$ lead

$P = 1.2 \text{ kW}$, $Q = |S| \sin(\cos^{-1}(0.4))$

for A: $P = 2 \text{ kW}$, $Q = P \tan(\cos^{-1}(0.8))$

for C: $P = 1 \text{ kW}$

$Q = 500 \text{ VAR}$

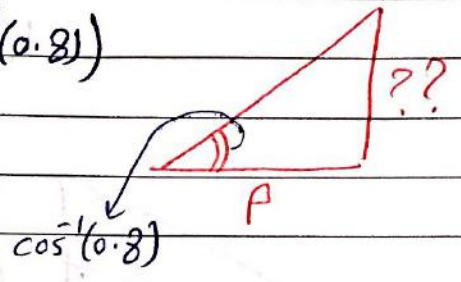

positive : always receiving or consuming means (Lagging)

* generating \equiv leading *

$P_{\text{total}} = P_A + P_B + P_C$ & $Q_{\text{total}} = Q_A + Q_B + Q_C$

final answer:


$\text{PF} = 0.98443$

$\Rightarrow \phi = \tan^{-1} \frac{Q_{\text{total}}}{P_{\text{total}}} \Rightarrow \text{PF} = \cos \phi$ leading.


② Find I if $V_s = 120 \angle 45^\circ$?

$S = V I^* \Rightarrow I^* = \frac{S_{\text{total}}}{V_s} \Rightarrow$ then we find I .

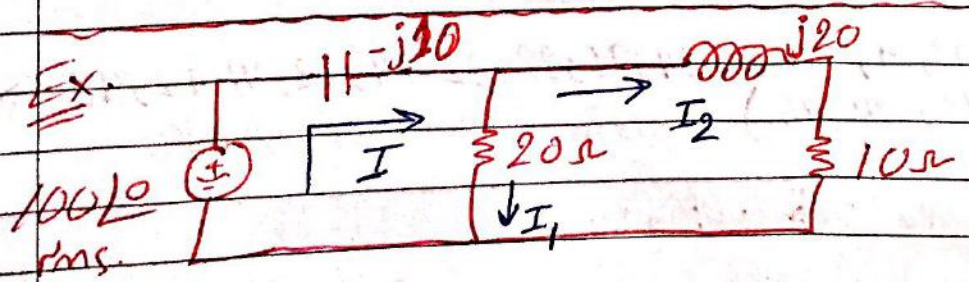final answer: $I = 35.554 \angle 55.12^\circ \text{ A}_{\text{rms}}$



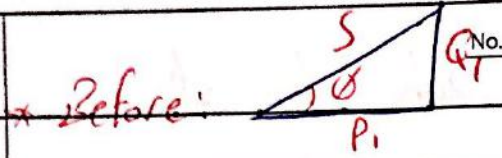
Need value of (C) parallel to (10 Ohms) that will make pf on the source 0.95? assume $f = 50 \text{ Hz}$



$$P_1 = I_1^2 \times 20 + I_2^2 \times 10 \Rightarrow \phi = \tan^{-1} \frac{Q}{P}$$

$$Q_1 = I_2^2 \times j20 = I^2 \times j20 \quad \text{pf} = \cos \phi$$

* After:

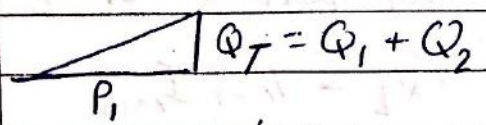

$$\phi = \cos^{-1} 0.95$$

$$Q_T = P_1 \tan 18.19^\circ$$


$$\Rightarrow Q_C = Q_T - Q_1$$

$$C = \frac{Q_C}{\omega |V|_{rms}^2}$$

$\omega = 2\pi \times 50$

voltage on the 10Ω resistor.

11.74

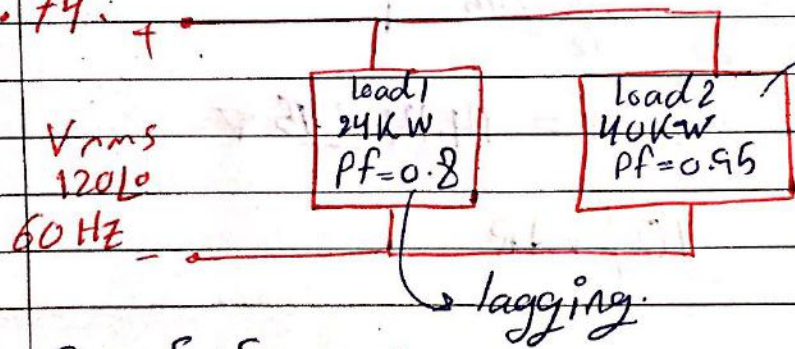

- ① find Pf for the combined load.
- ② find (C) that make Pf=1

①

$$S_{total} = S_1 + S_2$$

$$P_{total} = P_1 + P_2$$

$$Q_{total} = Q_1 + Q_2$$

$$P_1 = 24 \text{ kW}$$

$$Q_1 = P_1 \tan 36.81^\circ = 18 \text{ kVAR}$$

$$P_2 = 40 \text{ kW}$$

$$Q_2 = P_2 \tan 18.19^\circ = 14.73 \text{ kVAR}$$

$$P_{total} = 64 \text{ kW}, \quad Q_{total} = 32.73 \text{ kVAR}$$

$$\phi = \tan^{-1} \frac{Q_{tot}}{P_{tot}} \Rightarrow \text{pf} = \cos \phi$$

② $\text{pf} = 1 \Rightarrow \phi = 0 \Rightarrow Q_T = \text{Zero}$

So $Q_C = Q_T - Q_1 = -32.73 \text{ kVAR}$

Q_{total} before.


Now:

$$C = \frac{|Q_C|}{|V|_{rms}^2 \omega}$$

$\omega = 2\pi \times 60$

11.54: find the reactive power for each element in the following ckt:

directly Q on 10Ω & 20Ω is equal to Zero

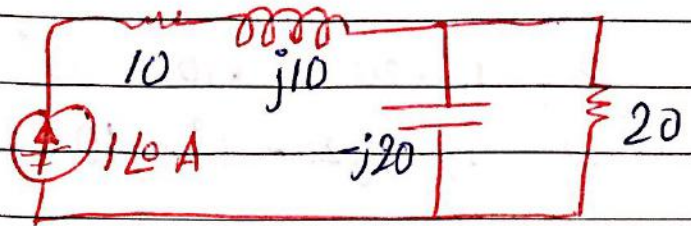

$$Q = V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$

for pure C or L:

$$Q_L = V_{rms} I_{rms}$$

$$Q_C = -V_{rms} I_{rms}$$

comes from $\sin(-90)$

$$\Rightarrow V_L = 10 \times j10 = 10 \angle 90^\circ$$

$$Q_L = 10 \times 1 = \boxed{10 \text{ VAR}}$$


$$I_{(\text{capacitor})} = \frac{10 \times 20}{20 - j20} = \frac{1}{\sqrt{2}} \angle 45^\circ \text{ A}$$

$$V_{rms(\text{capacitor})} = \frac{1}{\sqrt{2}} \angle 45^\circ \times 20 \angle -90^\circ = 14.14 \angle -45^\circ \text{ V}$$

$$Q_C = 14.14 \times \frac{1}{\sqrt{2}} = \boxed{10 \text{ VAR}}$$


CHAPTER (12): Poly Phase Systems:

No.


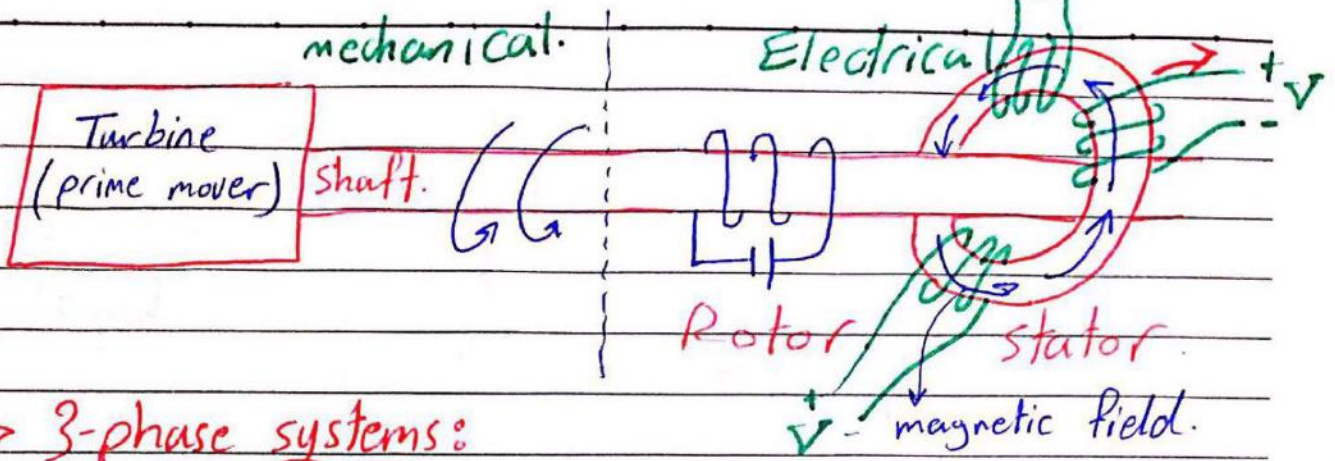


→ 3-phase systems:

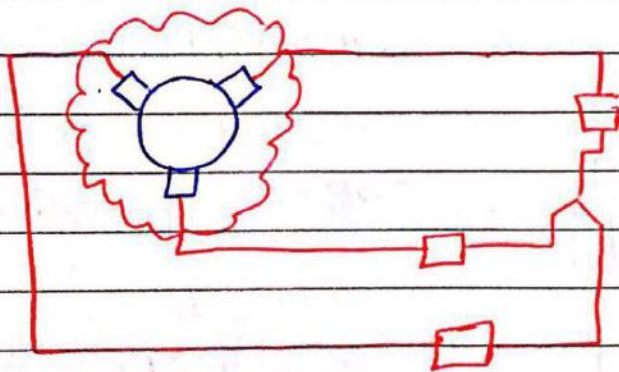
- ① over all system is more economical.
- ② less generator vibration. \Rightarrow since $P_{avg} = \text{constant}$.
- ③ Stability of the system.



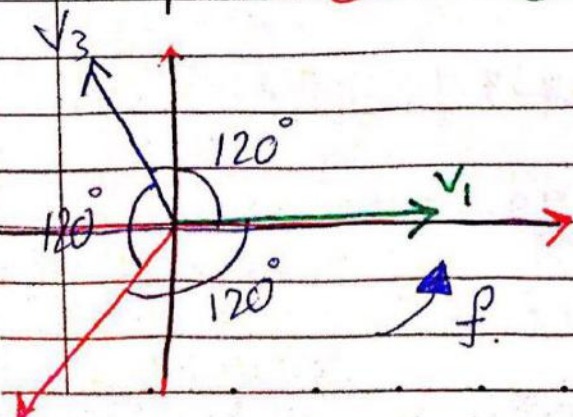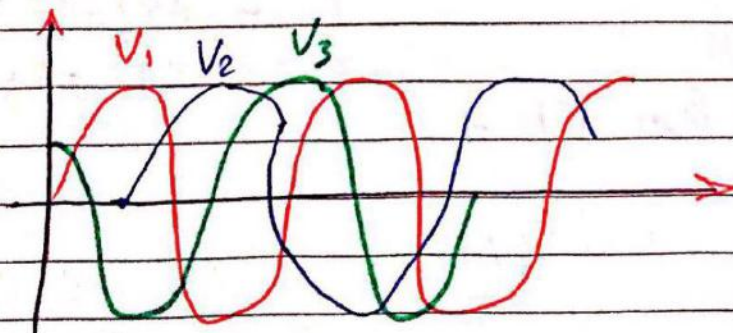* all the three loads have same voltage but different in phase shift.




3 phase generator

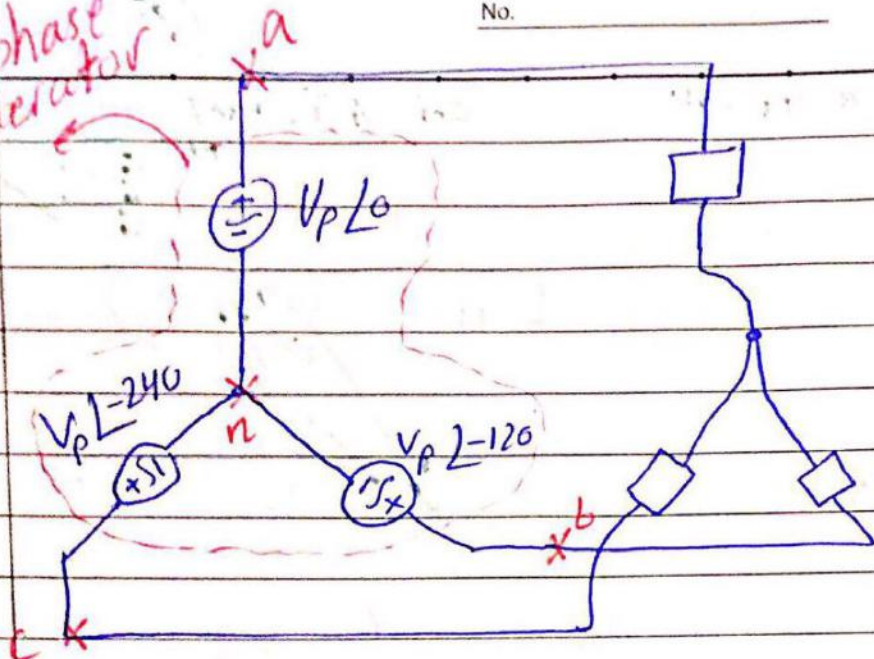

* Instead of using:
 V_1, V_2, V_3
 $\Rightarrow V_{an}, V_{bn}, V_{cn}$

* Single phase 3-wire systems

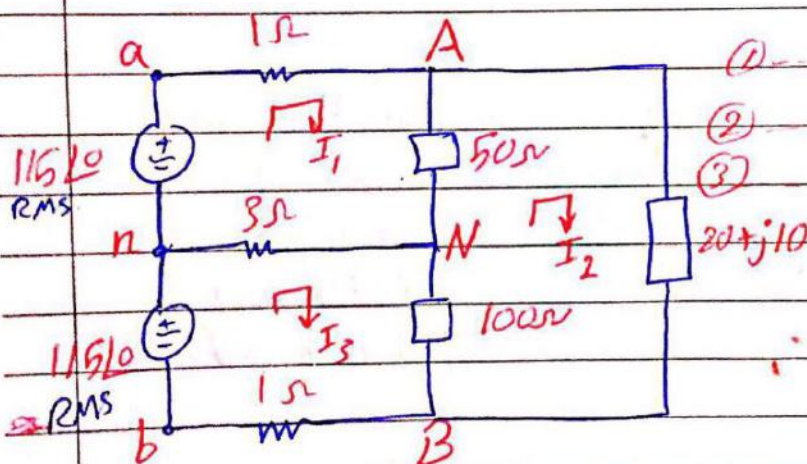

$$\begin{aligned} \textcircled{1} & -115\angle 0 + I_1 + 50(I_1 - I_2) + 3(I_1 - I_3) = 0 \\ \textcircled{2} & (20 + j10)I_2 + 100(I_2 - I_3) + 50(I_2 - I_1) = 0 \\ \textcircled{3} & -115\angle 0 + 3(I_3 - I_1) + (I_3 - I_2)100 + I_3 = 0 \end{aligned}$$

solving:

$$\begin{aligned} I_1 &= 11.24 \angle -14.83^\circ \\ I_2 &= 9.381 \angle -24.47^\circ \\ I_3 &= 10.37 \angle -21.8^\circ \end{aligned}$$

I_{aA} : the current flow from a to A.

$$\Rightarrow I_{aA} = I_1$$

I_{bB} : the current flow from b to B

$$\Rightarrow I_{bB} = -I_3$$



$$I_{nN} \Rightarrow I_{nN} = I_3 - I_1 = 0.9459 \angle -177.7^\circ$$

$$P_{(50\Omega)} = 50 \times |I_1 - I_2|^2 = 206 \text{ W}$$

$$P_{(100\Omega)} = 100 \times |I_3 - I_2|^2 = 117 \text{ W}$$

$$P_{(20+j10)} = 20 \times I_2^2 = 1763 \text{ W}$$

* A Balanced 3 ϕ system Connected Y-Y:

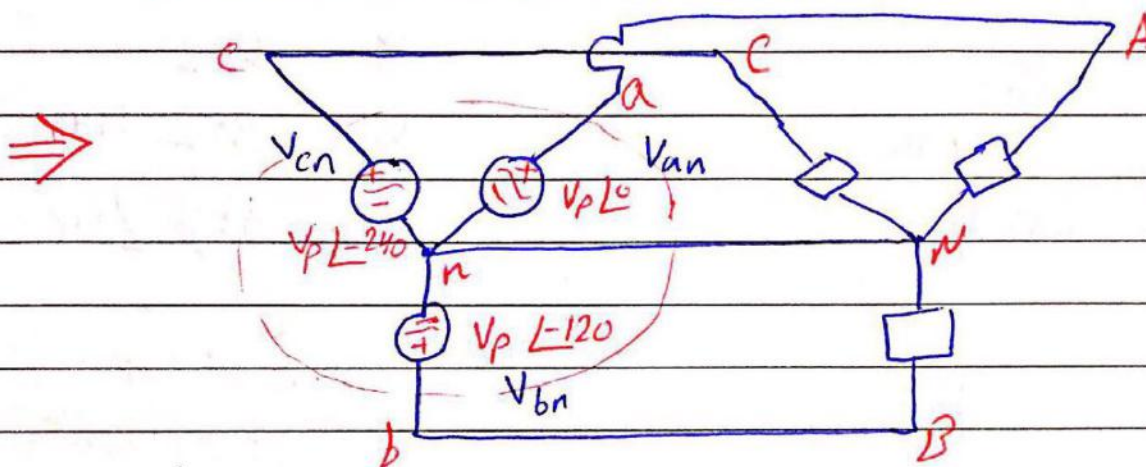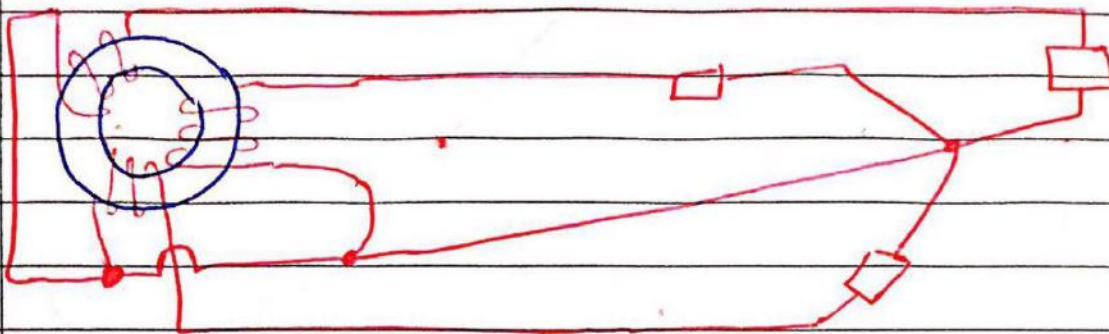

Y_{source}: the neutrals of the phase are connected together.

Y_{load}: the neutrals of the loads are connected together.

$$|V_{an}| = |V_{bn}| = |V_{cn}|$$

$$V_{an} = V_p \angle 0$$

$$V_{bn} = V_p \angle -120$$

$$V_{cn} = V_p \angle -240$$

same 120

⇒

$$V_{an} + V_{bn} + V_{cn} = 0$$

$$V_p \angle 0 + V_p \angle -120 + V_p \angle +120 = 0$$



$$\Rightarrow V_p + V_p \cos(-120) + j V_p \sin(-120) + V_p \cos(120) + j V_p \sin(120) = 0$$

$$V_p - \frac{V_p}{2} - \frac{V_p}{2} = 0 \Rightarrow \underline{V_p - V_p = 0}$$



positive sequence.

negative sequence.

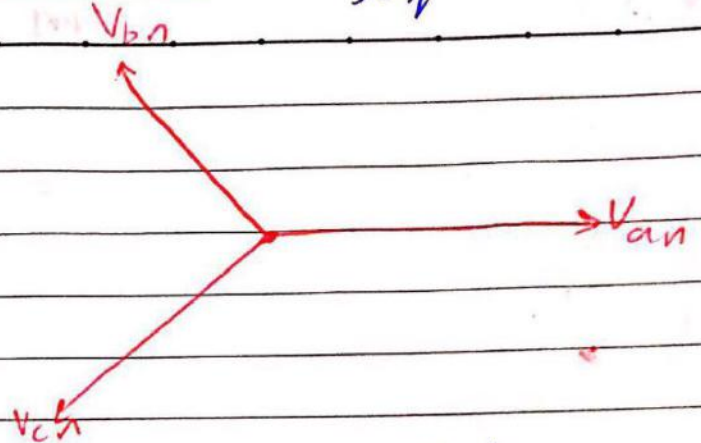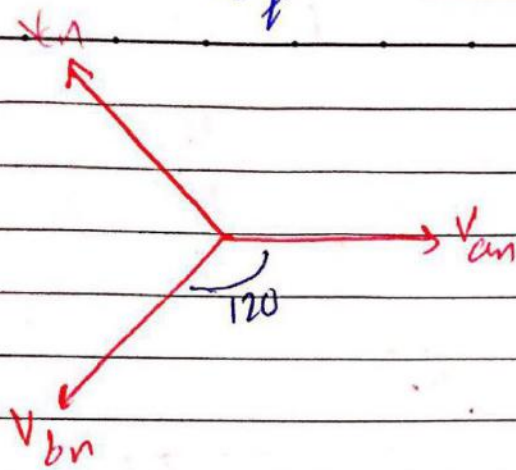


$$\begin{aligned} V_{an} &= V_p \angle 0 \\ V_{bn} &= V_p \angle -120 \\ V_{cn} &= V_p \angle +120 \end{aligned}$$

$$\begin{aligned} V_{an} &= V_p \angle 0 \\ V_{cn} &= V_p \angle -120 \\ V_{bn} &= V_p \angle +120 \end{aligned}$$

used in the rest of the world.

used in California.

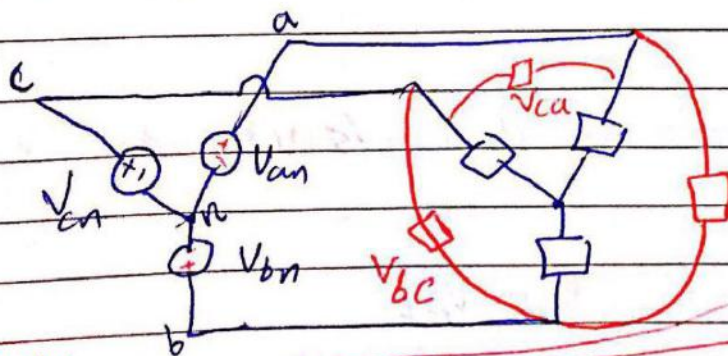

$V_{ab} = ??$

line-to-neutral voltage.
line-to-neutral voltage.

KVL:

$$\begin{aligned} \Rightarrow V_{ab} &= V_{an} - V_{bn} = V_p \angle 0 - V_p \angle -120 \\ &= V_p - [V_p \cos(-120) + j V_p \sin(-120)] \\ &= V_p + \frac{V_p}{2} + j V_p \frac{\sqrt{3}}{2} \end{aligned}$$

$$\Rightarrow = V_p \left(\frac{3}{2} + j \frac{\sqrt{3}}{2} \right) = \sqrt{3} V_p \left(\frac{\sqrt{3}}{2} + j \frac{1}{2} \right)$$

$$V_{ab} = \sqrt{3} V_p \angle 30^\circ$$

$$V_{bc} = V_{bn} - V_{cn} = V_p \angle -120 - V_p \angle +120$$

$$= V_p \cos(-120) + jV_p \sin(-120) - V_p \cos(120) - jV_p \sin(120)$$

$$= -j \frac{\sqrt{3}}{2} V_p - j \frac{\sqrt{3}}{2} V_p = -j \sqrt{3} V_p = \sqrt{3} V_p \angle -90^\circ$$


$V_{bc} = \sqrt{3} V_p \angle -90^\circ$ "Line-to-Line Voltage"

$$V_{ca} = V_{cn} - V_{an} = V_p \angle +120 - V_p = V_p \cos 120 + jV_p \sin 120 - V_p$$

$$= -\frac{V_p}{2} + jV_p \frac{\sqrt{3}}{2} - V_p = V_p \left(-\frac{3}{2} + j \frac{\sqrt{3}}{2} \right)$$

$$= \sqrt{3} V_p \left(-\frac{\sqrt{3}}{2} + j \frac{1}{2} \right) = \sqrt{3} V_p \angle 150$$

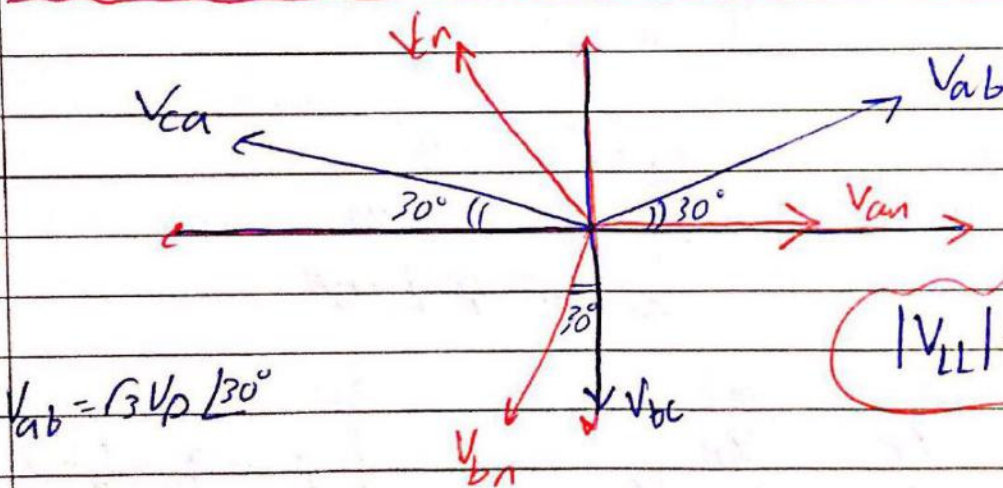
$\Rightarrow V_{ca} = \sqrt{3} V_p \angle 150^\circ$ "Line-Line Voltage"



$|V_{LL}| = \sqrt{3} V_{LN}$

in 30 balanced Y system

For a Y-Y system:

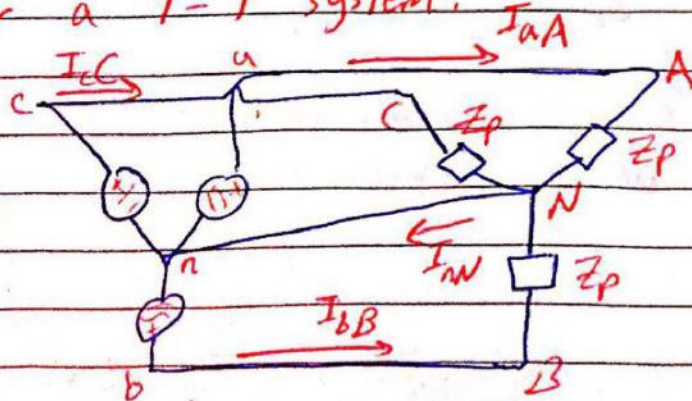

$I_{aA} = I_a = \frac{V_{an}}{Z_p} = \frac{V_p \angle 0}{Z_p}$

$I_{bB} = I_b = \frac{V_{bn}}{Z_p} = \frac{V_p \angle -120}{Z_p}$


$I_b = I_a \angle -120$

$I_{cC} = I_c = \frac{V_{cn}}{Z_p} = \frac{V_p \angle +120}{Z_p} = I_a \angle +120$

$$\begin{aligned}
 \rightarrow I_{Nn} &= I_a + I_b + I_c \\
 &= I_a + I_a \angle 120^\circ + I_a \angle -120^\circ \\
 &= I_a + I_a \cos(120^\circ) + I_a j \sin(-120^\circ) + I_a \cos(120^\circ) + I_a j \sin(120^\circ) \\
 &= I_a + \frac{-I_a}{2} - \frac{I_a}{2} = I_a - I_a = \text{Zero}
 \end{aligned}$$

☆ التيار العار بالنيوترال صفر لذلك لو قلنا بإزالة الوصل للنيوترال

Y-Y connected ckts:

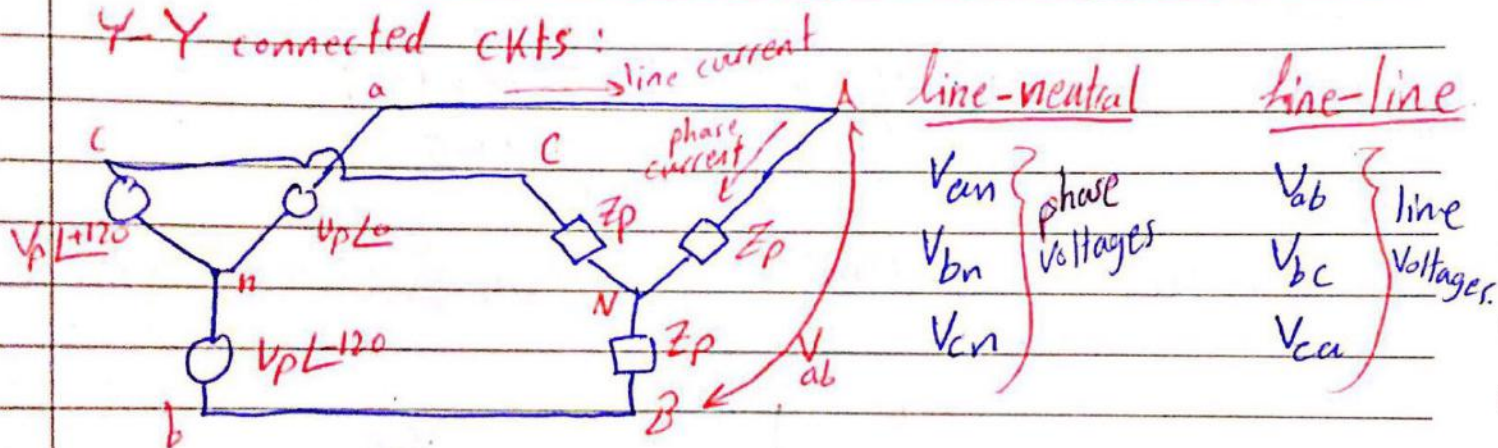

$ \begin{aligned} V_{an} &= V_p \angle 0^\circ \\ V_{bn} &= V_p \angle -120^\circ \\ V_{cn} &= V_p \angle +120^\circ \end{aligned} $	$ \begin{aligned} V_{ab} &= \sqrt{3} V_p \angle 30^\circ \\ V_{bc} &= \sqrt{3} V_p \angle -90^\circ \\ V_{ca} &= \sqrt{3} V_p \angle +150^\circ \end{aligned} $
--	---

$ \begin{aligned} I_{aA} = I_a &= \frac{V_{an}}{Z_p} = \frac{V_p \angle 0^\circ}{Z_p} \\ I_{bB} = I_b &= \frac{V_{bn}}{Z_p} = \frac{V_p \angle -120^\circ}{Z_p} = I_a \angle -120^\circ \\ I_{cC} = I_c &= \frac{V_{cn}}{Z_p} = \frac{V_p \angle +120^\circ}{Z_p} = I_a \angle +120^\circ \end{aligned} $	$ I_{Nn} = I_a + I_b + I_c = 0 $
---	------------------------------------

Example: for the Y-Y system shown find:

- (a) the phase current and line currents.
- (b) find the line voltages.
- (c) total real power absorbed by the load.

phase voltages:

$$V_{an} = 200 \angle 0^\circ$$

$$V_{bn} = 200 \angle -120^\circ$$


$$V_{cn} = 200 \angle +120^\circ$$

(b) line voltages:

$$V_{ab} = \sqrt{3} \cdot 200 \angle 30^\circ = 346 \angle 30^\circ$$

$$V_{bc} = 346 \angle -90^\circ$$

$$V_{ca} = 346 \angle +150^\circ$$

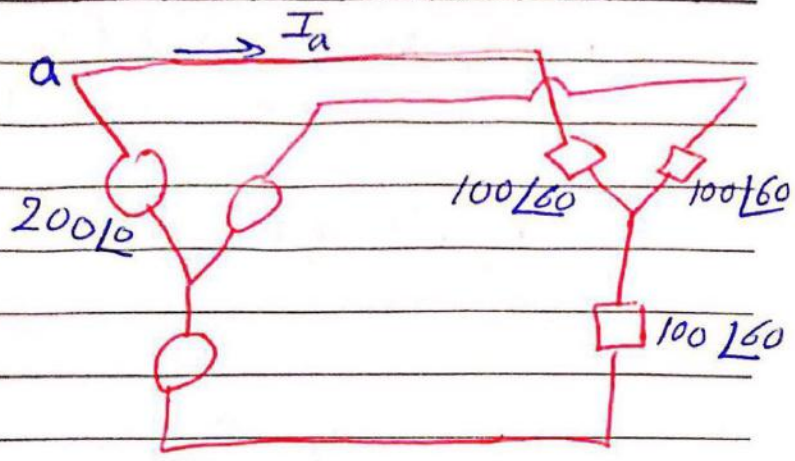

(a) phase currents: & line currents:

$$I_a = \frac{V_{an}}{Z_p} = \frac{200 \angle 0^\circ}{100 \angle 60^\circ} = 2 \angle -60^\circ \Rightarrow \text{phase current} = \text{line current} \left[\begin{array}{l} \text{Always} \\ \text{in Y} \end{array} \right]$$

$$I_b = \frac{V_{bn}}{Z_p} = \frac{200 \angle -120^\circ}{100 \angle 60^\circ} = 2 \angle -180^\circ \text{ or } I_b = I_a \angle -120^\circ = 2 \angle -180^\circ$$

$$I_c = I_a \angle +120^\circ = 2 \angle +60^\circ$$

(b) power in phase A: $P_A = V_A I_A \cos(\theta)$

$$= 200 \times 2 \times \cos 60 = 200 \text{ W}$$

$$P_B = V_B I_B \cos(\theta)$$

$$= 200 \times 2 \times \cos(-120 + 180) = 200 \text{ W}$$

$$P_C = 200 \times 2 \times \cos(120 - 60)$$

$$= 200 \text{ W}$$

$$P_{\text{total}} = P_A + P_B + P_C = 600 \text{ W}$$

→ Always in balanced systems:

$$P_{3\phi} = 3 P_{1\phi} \quad \text{***}$$

* Instantaneous Power:

→ peak value.

$$v_a(t) = 200 \cos \omega t \times \sqrt{2} = 200\sqrt{2} \cos \omega t$$

$$i_a(t) = 2\sqrt{2} \cos(\omega t - 60)$$

$$P_a(t) = 800 \cos(\omega t) \cos(\omega t - 60)$$


$$= 400 [\cos(-60) + \cos(2\omega t - 60)]$$

$$= 200 + 400 \cos(2\omega t - 60)$$

remember:
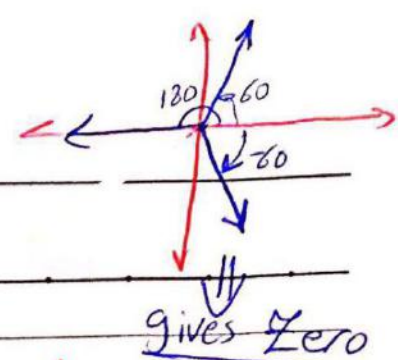
$$\cos \alpha \cos \beta = \frac{1}{2} [\cos(\alpha + \beta) + \cos(\alpha - \beta)]$$






No. $P_a(t) = 200 + 400 \cos(2\omega t - 60)$

$P_b(t) = 200 + 400 \cos(2\omega t + 60)$

$P_c(t) = 200 + 400 \cos(2\omega t + 180)$

$\Rightarrow P_{3\phi}(t) = P_A(t) + P_B(t) + P_C(t) = 600 + 0 = \underline{600 W}$

since also $V_a + V_b + V_c = 0$

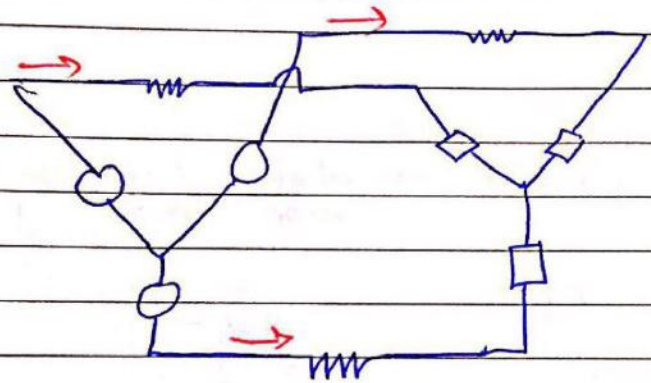

* Losses = $I_a^2 R + I_b^2 R + I_c^2 R$
 $= 4R + 4R + 4R$
 $= \underline{12R} W.$


* What if single phase is used:

$P = V_{rms} I_{rms} \cos \theta \Rightarrow 600 = 200 I_{rms} * \frac{1}{2}$


$I_{rms} = 6 \text{ Amp}$

$\Rightarrow \text{losses} = |I_{rms}|^2 R$
 $= \underline{36R} W.$

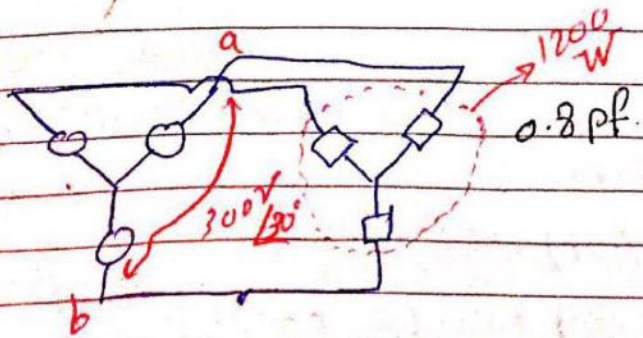(ex). A balanced 3 ϕ system with $V_L = 300 V$ & supplying a balanced Y-connected load with $1200 W$ @ 0.8 pf leading find the current & the per-phase load impedance.



* single phase equivalent ckt:

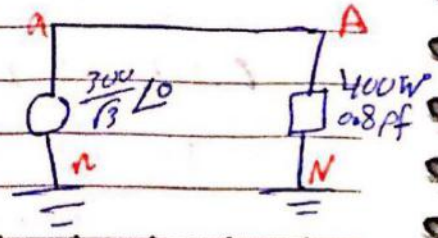

$$\Rightarrow |V_{ab}| = 300V \Rightarrow V_{an} = \frac{300}{\sqrt{3}}$$

* Take V_{an} as your reference.

$$P = V_{an} I_a \cos \theta \Rightarrow 400 = \frac{300}{\sqrt{3}} I_a \times 0.8$$


$$\Rightarrow |I_a|_{rms} = 2.89 \angle \cos^{-1}(0.8) \Rightarrow |I_a| = 2.89 \angle 36.87^\circ \text{ A.}$$

$$\Rightarrow Z = \frac{300/\sqrt{3} \angle 0^\circ}{2.89 \angle 36.87^\circ} = 60 \angle -36.87^\circ \Omega$$

* if the question doesn't determine the pf.

\Rightarrow pure resistor (pf=1)

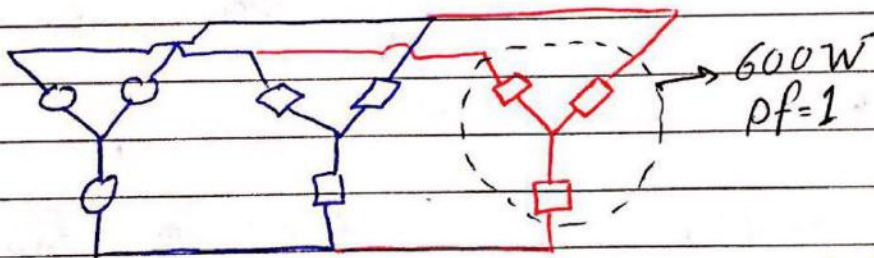(ex) a balanced 600 W is added to the system in parallel. Find the new line current?



$$P = V_{an} I_a$$

$$\Rightarrow I_a = \frac{200}{300/\sqrt{3}} = 1.15 \angle 0^\circ \text{ A}$$

$$\Rightarrow I_{line} = 2.89 \angle 36.87^\circ + 1.15$$

$$= 3.87 \angle 26.6^\circ \text{ A}$$

we also could find:

$$V_{an} = \frac{300}{\sqrt{3}}$$

$$V_{bn} = \frac{300}{\sqrt{3}} \angle 120^\circ$$

$$V_{cn} = \frac{300}{\sqrt{3}} \angle 240^\circ$$


$$V_{ab} = 300 \angle 30^\circ$$

$$V_{bc} = 300 \angle -90^\circ$$

$$V_{ca} = 300 \angle 150^\circ$$


case 1: $I_a = 2.83 \angle 36.87^\circ$ $I_b = 2.83 \angle 36.87 - 120^\circ$ $I_c = 2.83 \angle 36.87 + 120^\circ$

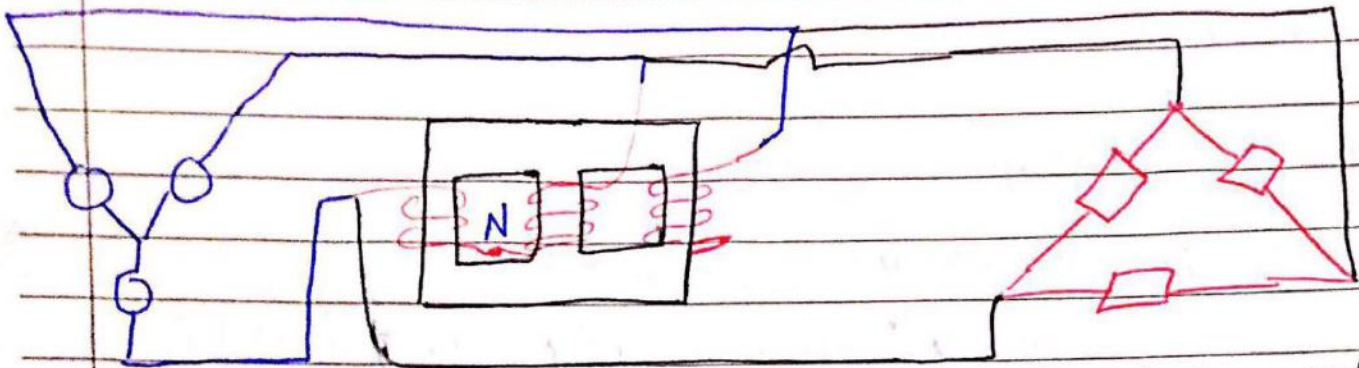case 2: $I_a = 3.87 \angle 26.6^\circ$ $I_b = 3.87 \angle 26.6 - 120^\circ$ $I_c = 3.87 \angle 26.6 + 120^\circ$



Δ-connection.

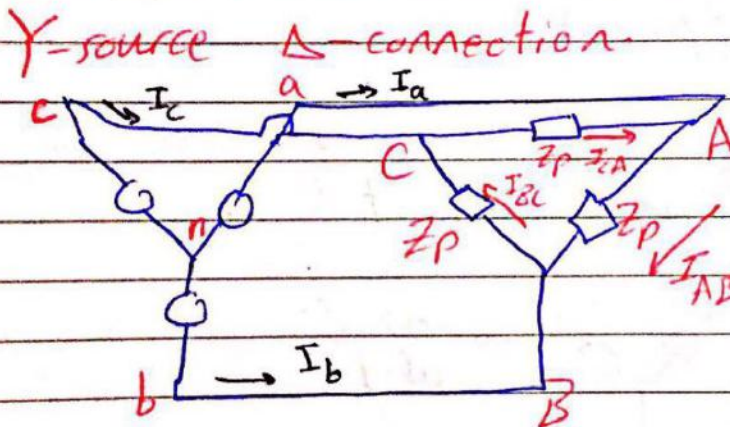we use it since we can't access the Neutral point.



In Δ-connection:

$$V_{\text{phase}} = V_{\text{line-line}}$$

$$I_{AB} = \frac{V_{AB}}{Z_p}$$

$$I_{BC} = \frac{V_{BC}}{Z_p} = I_{AB} \angle -120^\circ$$

$$I_{CA} = \frac{V_{CA}}{Z_p} = I_{AB} \angle +120^\circ$$

⇒ in Δ-connection:

$$I_{\text{phase}} \neq I_{\text{line}}$$

$$I_a + I_{CA} = I_{AB} \Rightarrow I_a = I_{AB} - I_{CA}$$

$$= I_{AB} - I_{AB} \angle 120^\circ$$

$$= I_{AB} - I_{AB} \cos 120 - j I_{AB} \sin 120 = I_{AB} \left(1 + 0.5 - j \frac{\sqrt{3}}{2} \right)$$

$$I_a = I_{AB} \sqrt{3} \angle -30^\circ$$

line current → phase current.





$$V_{LL} = \sqrt{3} V_{LN} \angle 30^\circ$$







$$V_{LL} = V_{\text{phase}}$$

$$I_L = I_p$$

$$I_L = \sqrt{3} I_p \angle -30^\circ$$

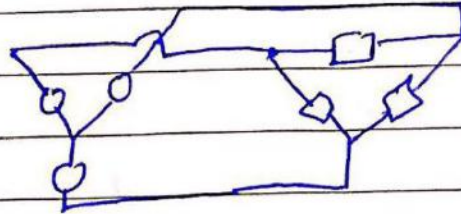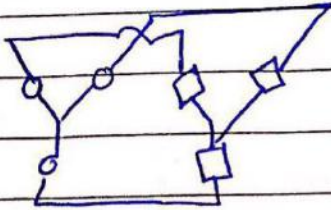



*Assume an inductive load:

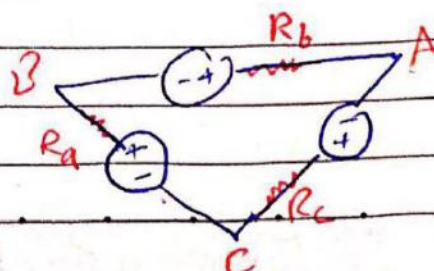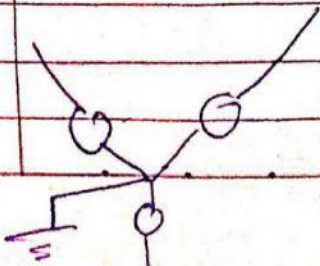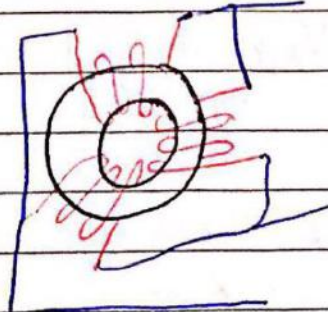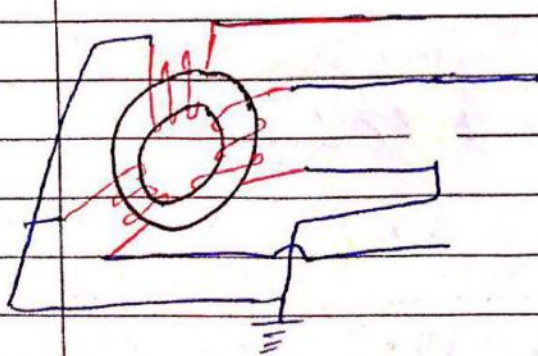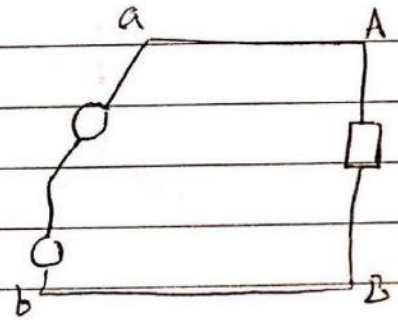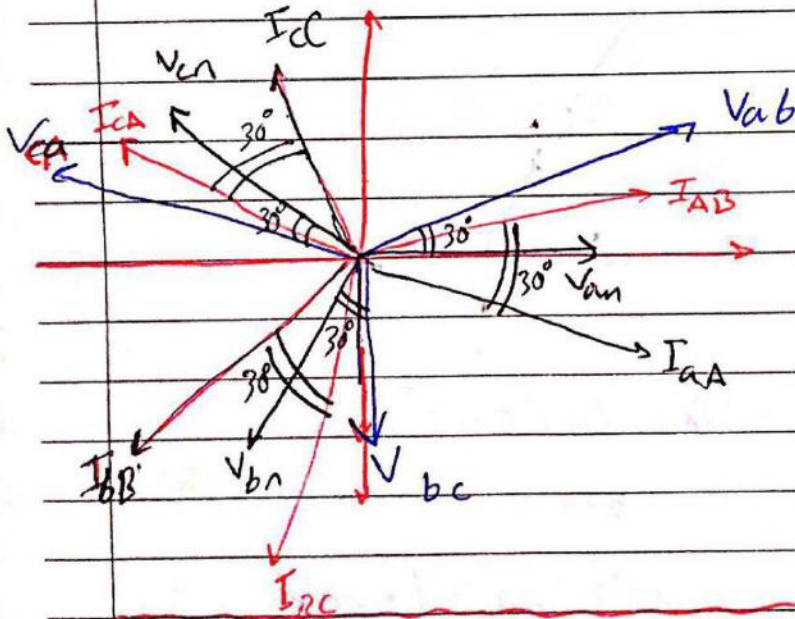

*4 types of connection:

- ① $Y_{source} Y_{load}$ ② $Y_{source} \Delta_{load}$
 ③ $\Delta_{source} Y_{load}$ ④ $\Delta_{source} \Delta_{load}$

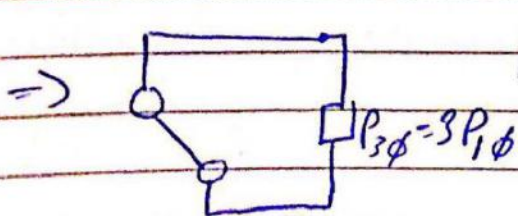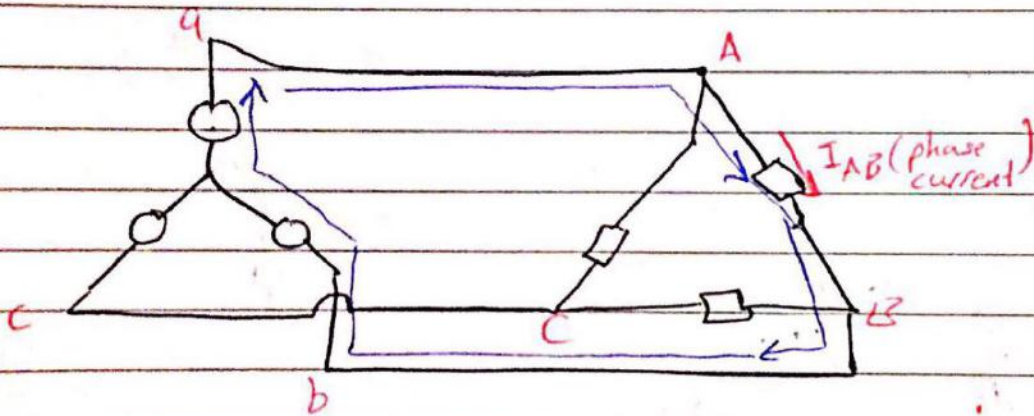[Ex]. What are the line currents in a 3 ϕ system with line voltage of 300 V & supplies 1200 W to Δ connection load at lagging pf = 0.8 & find the phase impedance.



$$P = V_{AB} I_{AB} \cos \theta$$

$$400 = 300 I_{AB} (0.8)$$

$$\Rightarrow I_{AB} = 1.667$$

\Rightarrow Take V_{AB} as your reference: $V_{AB} = 300 \angle 0^\circ$
 so $I_{AB} = 1.667 \angle -\cos^{-1}(0.8) = 1.667 \angle -36.87^\circ$

$$\Rightarrow I_a = 1.667 \times \sqrt{3} \angle -36.87 - 30 = 2.89 \angle -66.87$$

$$I_c = 2.89 \angle -66.87 + 120^\circ$$

$$I_b = 2.89 \angle -66.87 - 120^\circ$$



$$\Rightarrow I_{BC} = 1.66 \angle -36 - 120$$

$$I_{CA} = 1.66 \angle -36 + 120$$

$$Z_p = \frac{V_{AB}}{I_{AB}} = \frac{300 \angle 0}{1.66 \angle -36.87}$$

$$= 180 \angle 36.87$$

⇒ what if the load is Y connection:

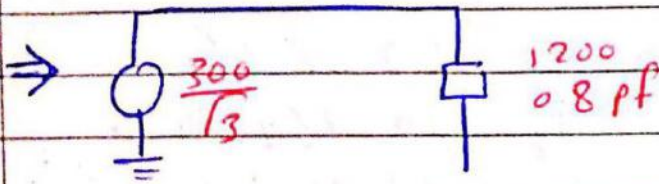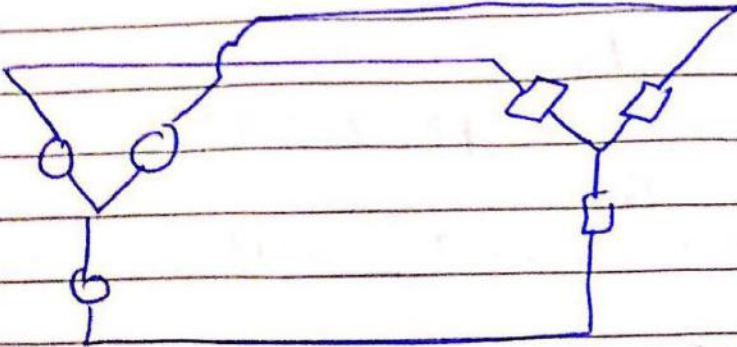

$$P = V_{an} I_a \cos \theta$$

$$400 = \frac{300}{\sqrt{3}} \times I_a \times 0.8$$


$$\Rightarrow I_a = 2.89 \text{ A}$$

Take V_{an} as your ref.


$$V_{an} = \frac{300}{\sqrt{3}} \angle 0 \Rightarrow I_a = 2.89 \angle -36.87^\circ$$

$$Z_p = \frac{V_{an}}{I_a} = 60 \angle 36.87^\circ$$
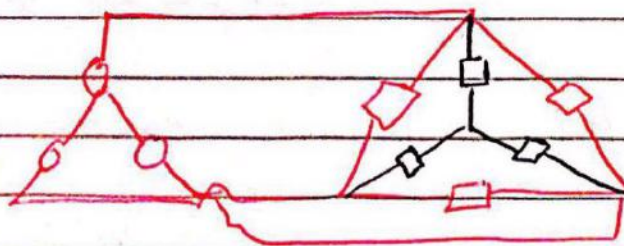
$$\Rightarrow Z_\Delta = 3 Z_Y \quad Z_Y = \frac{1}{3} Z_\Delta$$



Δ-Δ connection!

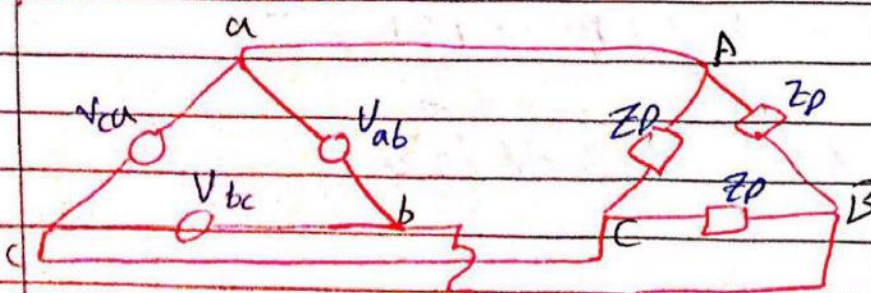

$$I_{AB} = \frac{V_{ab}}{Z_p}$$

$$I_{BC} = \frac{V_{bc}}{Z_p}$$

$$I_{CA} = \frac{V_{ca}}{Z_p}$$

$$I_a = \sqrt{3} I_{AB} \angle -30^\circ$$

(ex) Δ - Δ connection system with load $20-j15$ is connected to Δ source with $V_{ab} = 330 \angle 0^\circ$
find I_{phase} & I_{line} ?

$$I_{AB} = \frac{V_{AB}}{Z_p} = \frac{330 \angle 0^\circ}{20-j15} = 13.2 \angle 36.87^\circ \text{ A}$$

$$I_{BC} = 13.2 \angle 36.87-120 = 13.2 \angle -83.13^\circ \text{ A}$$

$$I_{CA} = 13.2 \angle 156.87^\circ \text{ A}$$




$$\Rightarrow I_a = \sqrt{3} I_{AB} \angle -30^\circ \Rightarrow$$

$$I_a = 22.86 \angle 6.87^\circ \text{ A}$$

$$I_b = 22.86 \angle -113.13^\circ \text{ A}$$

$$I_c = 22.86 \angle 126.87^\circ \text{ A}$$

Δ -Y connection:

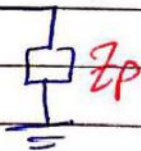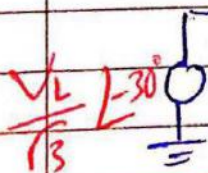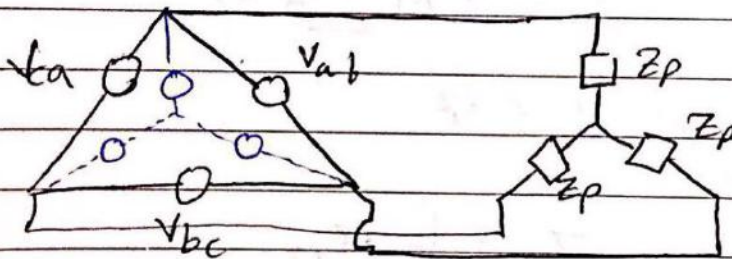

$$I_a = \frac{V_{an}}{Z_p} = \frac{V_{ab} \angle -30^\circ}{\sqrt{3} Z_p}$$

(ex) a balanced Y connected load with $Z_p = 40 + j25$ is supplied by Δ source with line voltage $V_{ab} = 210 \angle -20^\circ$ calculate the phase current?

$$V_{an} = \frac{V_{ab}}{\sqrt{3}} \angle -30 = \frac{210}{\sqrt{3}} \angle -50 = 121.2 \angle -50^\circ$$

$$I_a = \frac{V_{an}}{Z_p} = \frac{121.2 \angle -50^\circ}{40 + j25} = 2.57 \angle -82^\circ \text{ A}$$

$$I_b = 2.57 \angle -202^\circ \text{ A}$$

$$I_c = 2.57 \angle 138^\circ \text{ A}$$

* Power in 3φ systems:

- for a Y connected load:

$$v_{an} = \sqrt{2} V_p \cos \omega t, \quad v_{bn} = \sqrt{2} V_p \cos(\omega t - 120^\circ), \quad v_{cn} = \sqrt{2} V_p \cos(\omega t + 120^\circ)$$

↳ peak value
since V_p (rms)

* suppose an inductive load (Z/θ):

$$i_{an} = \sqrt{2} I_p \cos(\omega t - \theta), \quad i_{bn} = \sqrt{2} I_p \cos(\omega t - 120^\circ - \theta), \quad i_{cn} = \sqrt{2} I_p \cos(\omega t + 120^\circ - \theta)$$

$$\Rightarrow P_A = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = V_p I_p \cos \theta$$

$$P_B = V_p I_p \cos \theta$$

$$P_C = V_p I_p \cos \theta$$

$$\Rightarrow P_{3\phi} = 3P_{1\phi} = 3V_p I_p \cos \theta$$

$$Q_{3\phi} = 3Q_{1\phi} = 3V_p I_p \sin \theta$$

$$|S_{3\phi}| = 3|S_{1\phi}| = 3|V_p| |I_p|$$

$$* P_{Total} = 3V_p I_p \cos \theta$$

$$\Rightarrow \text{in } Y: V_p = \frac{V_L}{\sqrt{3}} \text{ \& } I_L = I_p$$

$$\text{in } \Delta: V_p = V_L \text{ \& } I_p = \frac{I_L}{\sqrt{3}}$$

⇒ so in Y/Δ Δ:

$$P_{Total} = \sqrt{3} V_L I_L \cos \theta$$

$$Q_{Total} = \sqrt{3} V_L I_L \sin \theta$$



$$S_{Total} = \sqrt{3} V_L I_L^*$$

* Ex. Find the source & the load real & reactive & complex power? (find the losses)?

* since it is Balanced

so $(5+j5) \Rightarrow$ has No effect.

since $I_N = 0$

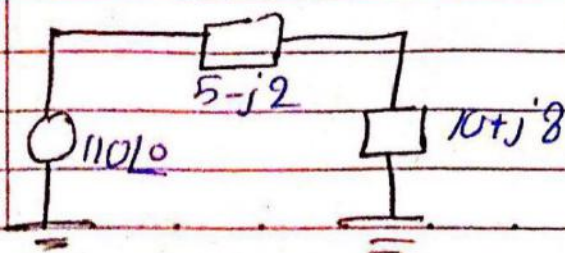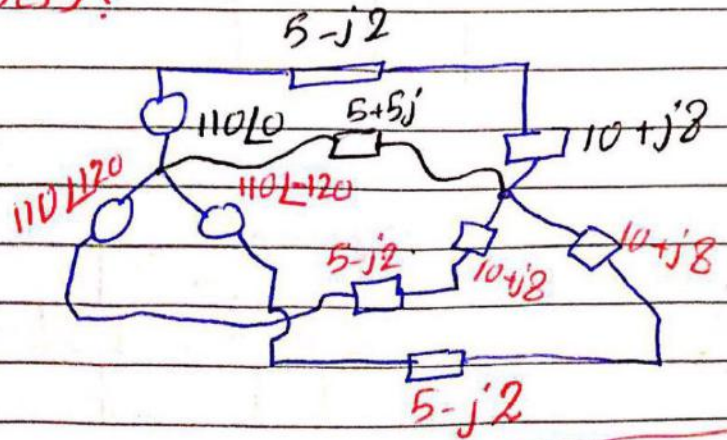

$$I_p = \frac{110 \angle 0^\circ}{5-j2 + 10+j8} = 6.8 \angle -21.8^\circ$$

$$\Rightarrow P_{3\phi} = 3V_p I_p^* = 3 \times (110/0) \times (6.8) \angle 21.8^\circ$$

(source)

$$= \frac{2247 \angle 21.8^\circ}{S_{3\phi}} = \frac{2087 + j 834.6}{P_{3\phi} \quad Q_{3\phi}}$$

at load:

$$S_L = 3V_p I_p^* = 3(Z_p I_p) \times I_p^* = 3|I_p|^2 Z_p$$

$$= \frac{1782 \angle 38.66^\circ}{S_{3\phi}} = \frac{1392 + j 1113}{P_{3\phi} \quad Q_{3\phi}}$$

Losses:


method(1): $S_{losses} = S_{source} - S_{load} = 695.6 - j 278$

method(2): $S_{losses} = 3|I_p|^2 Z_{T.L} = 3 \times (6.8)^2 \times (5 - j2)$
 $= 695.6 - j 278$

* Power Measurements:


(in single phase):

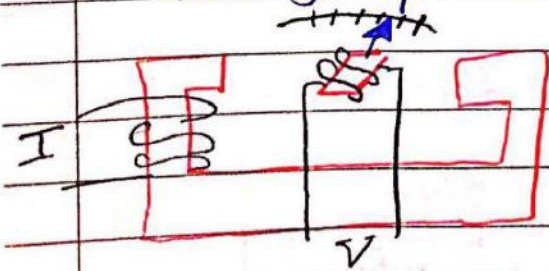Wattmeter: is an instrument used to measure the average power.



Deflection is proportional with V & I .

* structure of wattmeter:

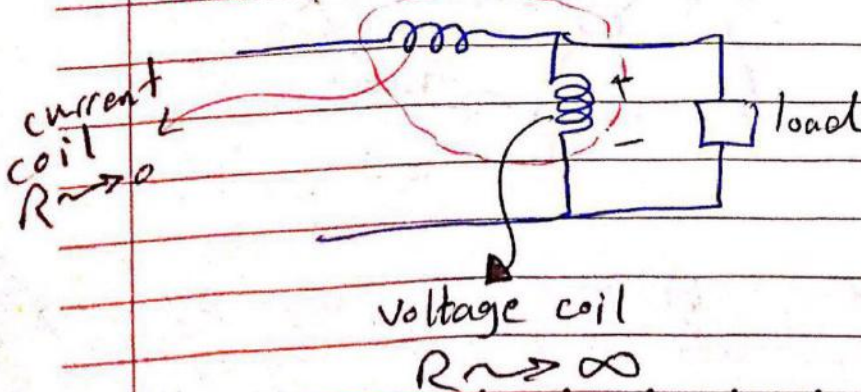

$$P = |V_{rms}| |I_{rms}| \cos(\theta_v - \theta_i)$$

* Ex. Find the wattmeter reading for the shown CK+:

$$I_{rms} = \frac{150 \angle 0}{12 + j10 + 8 - j6}$$


$$= 7.35 \angle -11.3^\circ \text{ A}$$

$$V_{rms} (\text{load}) = (8 - j6) (7.35 \angle -11.3^\circ) = 73.5 \angle -48^\circ \text{ V}$$


wattmeter reading $\equiv P = |V_{rms}| |I_{rms}| \cos(\theta_v - \theta_i)$

$$= 432.1 \text{ W}$$

* in three phase:

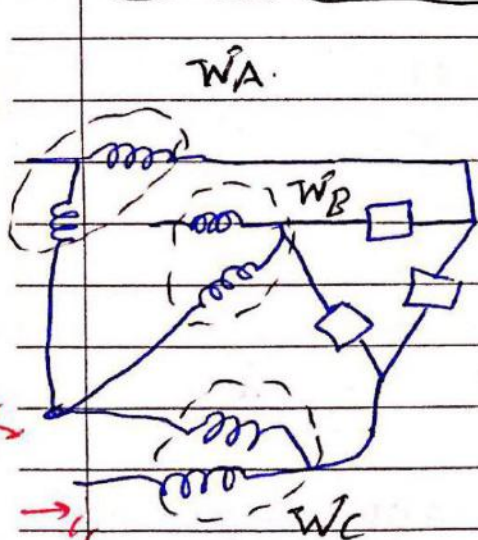

using

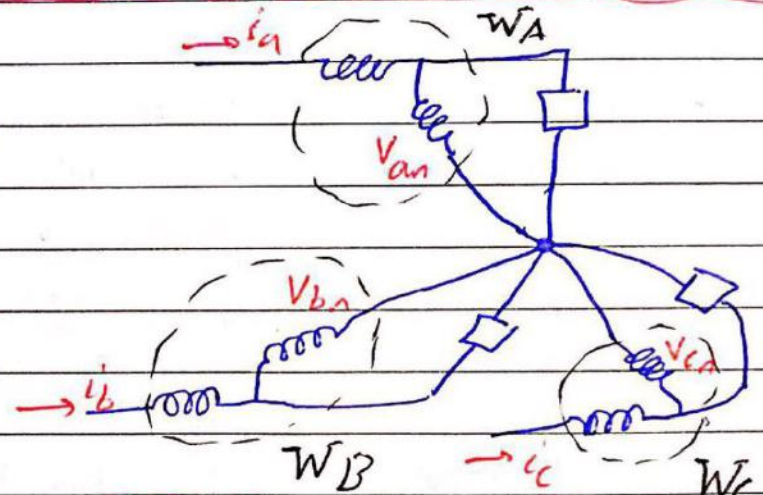

$$\begin{aligned} P_A &\Rightarrow I_a, V_{ax} \\ P_B &\Rightarrow I_b, V_{bx} \\ P_C &\Rightarrow I_c, V_{cx} \end{aligned} \quad \left\{ \begin{aligned} V_{ax} &= V_{an} + V_{nx} \\ V_{bx} &= V_{bn} + V_{nx} \\ V_{cx} &= V_{cn} + V_{nx} \end{aligned} \right.$$

$$\begin{aligned} \Rightarrow P_{3\phi} &= V_{ax} I_a \cos\theta + V_{bx} I_b \cos\theta + V_{cx} I_c \cos\theta \\ &= (V_{an} + V_{nx}) I_a \cos\theta + (V_{bn} + V_{nx}) I_b \cos\theta + (V_{cn} + V_{nx}) I_c \cos\theta \\ &= V_{an} I_a \cos\theta + V_{bn} I_b \cos\theta + V_{cn} I_c \cos\theta + V_{nx} (I_a + I_b + I_c) \cos\theta \end{aligned}$$

$$P_{3\phi} = V_{an} I_a \cos\theta + V_{bn} I_b \cos\theta + V_{cn} I_c \cos\theta$$

Conclusion:

→ The choice of x does not change the total power measured.

(Ex) Find the 3-wattmeters reading when $x @ n$?

Given: $V_{ab} = 100 \text{ V}$, $Z_a = -j10$, $Z_b = j10$, $Z_c = 10$


$W_1: V_{an}, I_a$ $W_2: V_{bn}, I_b$

$W_3: V_{cn}, I_c$

$$V_{an} = \frac{100}{\sqrt{3}} \angle -30^\circ$$

$$V_{bn} = \frac{100}{\sqrt{3}} \angle -150^\circ$$
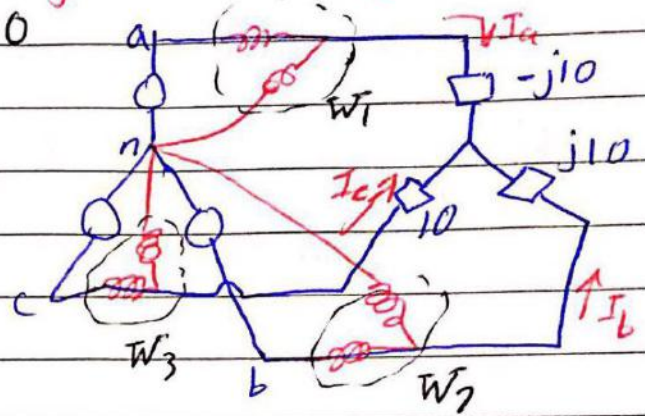
$$V_{cn} = \frac{100}{\sqrt{3}} \angle +90^\circ$$



taking loops in two phases:

$$-V_{an} - j10 I_a - 10 I_c + V_{cn} = 0 \quad \text{--- (1)}$$

$$-V_{cn} - j10 I_a - j10 I_b + V_{bn} = 0 \quad \text{--- (2)}$$

$$-V_{bn} + j10 I_c - 10 I_b + V_{cn} = 0 \quad \text{--- (3)}$$

→ Hard to solve it will be very long.

⇒ A way to solve:

$$I_a = \frac{V_{an} - V_n}{-j10}, \quad I_b = \frac{V_{bn} - V_n}{j10}, \quad I_c = \frac{V_{cn} - V_n}{10}$$

use: $I_a + I_b + I_c = 0$

Answers: $I_a = 19.32 \angle 115^\circ \text{ A}$
 $I_b = 19.32 \angle 165^\circ \text{ A}$
 $I_c = 10.00 \angle -90^\circ \text{ A}$

so Now:

$$P_1 = \frac{100}{\sqrt{3}} \times 19.32 \cos(-30 - 115) = 788.7 \text{ W}$$

$$P_2 = \frac{100}{\sqrt{3}} \times 19.32 \cos(-150 - 165) = 788.7 \text{ W}$$



$$P_3 = \frac{100}{\sqrt{3}} \times 10 \cos(90 + 90) = -577.4 \text{ W}$$

$$\text{so } P_{\text{total}} = P_1 + P_2 + P_3 = 1000 \text{ W}$$

$$I_a + I_b + I_c = 0$$

$$\rightarrow V_N \neq 0$$

Note:

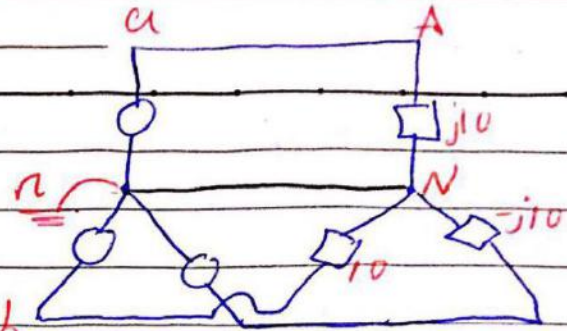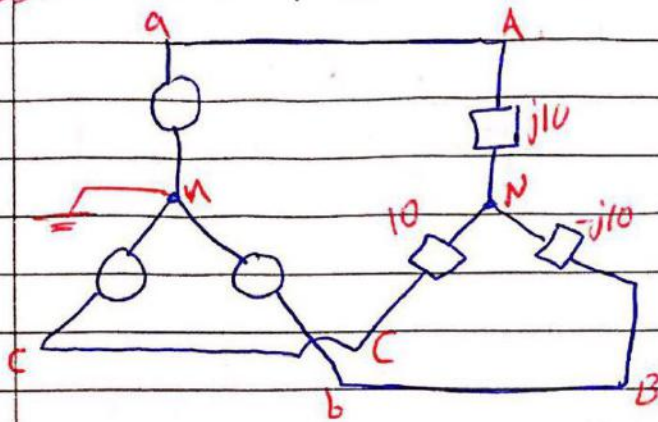


$$I_{nN} = I_a + I_b + I_c$$

$$V_N = V_n = 0$$

if there is $Z_n \Rightarrow V_N \neq 0$

The Two Wattmeter Method:

$$P_T = P_1 + P_2$$

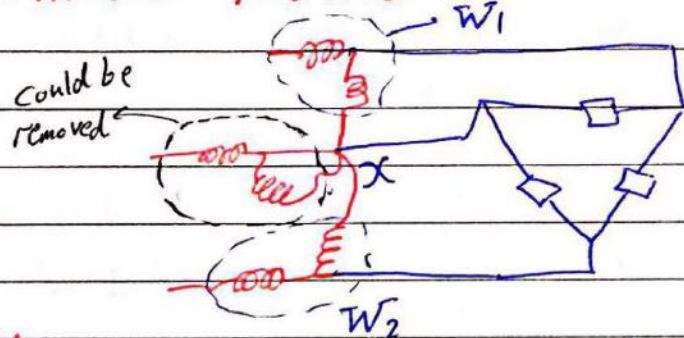

for the last ex.:

$$W_1: V_{ab}, I_a$$

$$W_2: V_{cb}, I_c$$

$$\Rightarrow V_{ab} = 100 \angle 0$$

$$V_{cb} = -V_{bc} = -100 \angle -120 = 100 \angle +60$$


$$I_a = 19.32 \angle 15$$

$$I_c = 10 \angle -90$$

$$\Rightarrow P_1 = 100 * 19.32 \cos(0 - 15) = 1866 \text{ W}$$

$$P_2 = 100 * 10 \cos(60 + 90) = -866 \text{ W}$$
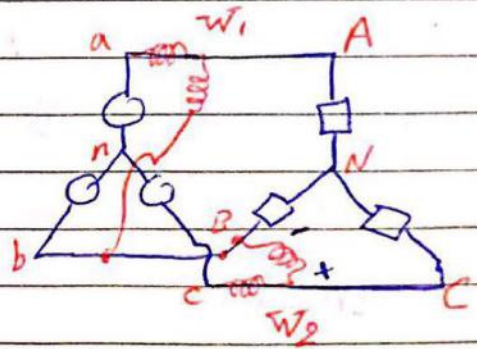
$$\Rightarrow P_T = P_1 + P_2 = 1000 \text{ W}$$




P_1 & $P_2 \Rightarrow$ they are just reading. (so actually they have no meaning)

$P_T \Rightarrow$ The power supplied by the source

(Ex.) Given $V_{ab} = 230 \angle 0^\circ$ find the power measured by each wattmeter & the total power

$$P_T = P_1 + P_2$$
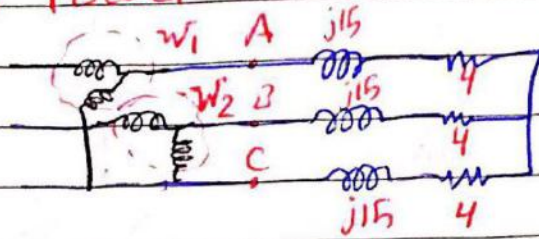
$$P_1 \Rightarrow V_{ac} \Rightarrow I_a \quad P_2 \Rightarrow V_{bc} \Rightarrow I_b$$



$$V_{ab} = 230 \angle 0^\circ$$

$$V_{bc} = 230 \angle -120^\circ$$

$$V_{ca} = 230 \angle +120^\circ \Rightarrow V_{ac} = 230 \angle 120^\circ - 180^\circ = 230 \angle -60^\circ$$

$$\Rightarrow I_a = \frac{V_{an}}{Z_p} = \frac{230/\sqrt{3} \angle -30^\circ}{4 + j15} = 8.554 \angle -105^\circ$$

$$\Rightarrow I_b = 8.554 \angle -225^\circ$$

$$\text{so } P_1 = V_{ac} I_a \cos(\theta_{V_{ac}} - \theta_{I_a}) = 1389 \text{ W}$$

$$P_2 = V_{bc} I_b \cos(\theta_{V_{bc}} - \theta_{I_b}) = -512 \text{ W}$$



$$P_T = P_1 + P_2$$

$$P_T = 876.5 \text{ W}$$

How to calculate PF using the wattmeters readings:

$$W_1: V_{AB} \Rightarrow I_a \quad W_2: V_{CB} \Rightarrow I_c$$

consider an inductive load:

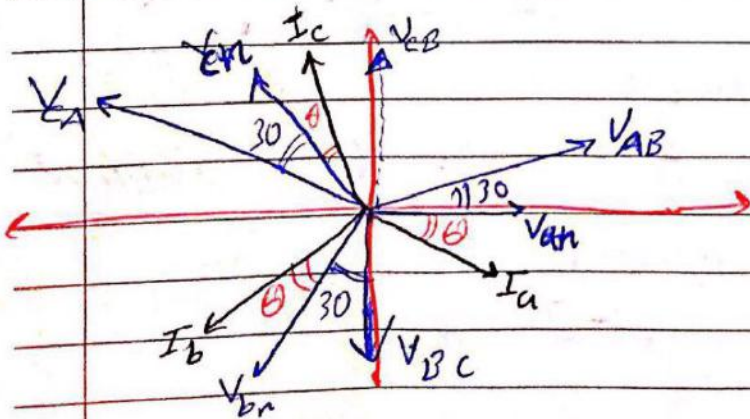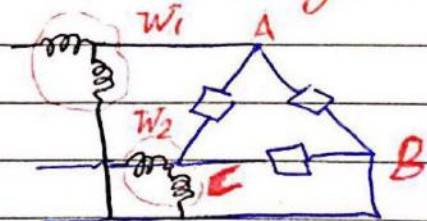

$$P_1 = V_{AB} I_a \cos(\theta_{V_{AB}} - \theta_{I_a})$$

$$= V_{AB} I_a \cos(30 + \theta)$$

$$= V_{LL} I_L \cos(30 + \theta)$$

$$P_2 = V_{CB} I_c \cos(\theta_{V_{CB}} - \theta_{I_c})$$

$$= V_{CB} I_c \cos(30 - \theta)$$

$$= V_{LL} I_L \cos(30 - \theta)$$

$$\text{Now: } \frac{P_1}{P_2} = \frac{V_{LL} I_L \cos(\theta + 30)}{V_{LL} I_L \cos(30 - \theta)}$$

$$\Rightarrow$$

* All relations in this page work on Δ & Y *

No. _____

$$\Rightarrow \frac{P_1}{P_2} = \frac{\cos\theta \cos 30^\circ - \sin\theta \sin 30^\circ}{\cos\theta \cos 30^\circ + \sin\theta \sin 30^\circ} = \frac{\frac{\sqrt{3}}{2} \cos\theta - \frac{1}{2} \sin\theta}{\frac{\sqrt{3}}{2} \cos\theta + \frac{1}{2} \sin\theta}$$

$$= \frac{\sqrt{3} - \tan\theta}{\sqrt{3} + \tan\theta} \Rightarrow \sqrt{3} P_1 + P_1 \tan\theta = \sqrt{3} P_2 - P_2 \tan\theta$$

$$\Rightarrow \tan\theta (P_1 + P_2) = \sqrt{3} (P_2 - P_1)$$

$$\Rightarrow \tan\theta = \frac{\sqrt{3} (P_2 - P_1)}{P_1 + P_2} \Rightarrow \text{PF} = \cos\theta$$

capacitive load. $P_1 > P_2$ $P_1 = P_2$ resistive load. $P_2 > P_1$ inductive load.

$$P_1 = V_{LL} I_L \cos(30^\circ + \theta) \Rightarrow P_T = V_{LL} I_{LL} \cos 30^\circ \cos\theta - V_{LL} I_{LL} \sin 30^\circ \sin\theta$$

$$P_2 = V_{LL} I_L \cos(30^\circ - \theta) + V_{LL} I_L \cos 30^\circ \cos\theta + V_{LL} I_L \sin 30^\circ \sin\theta$$

$$= 2 V_{LL} I_L \frac{\sqrt{3}}{2} \cos\theta$$

$$\Rightarrow P_T = \sqrt{3} V_{LL} I_L \cos\theta$$

How to calculate Q :

$$P_1 - P_2 = V_{LL} I_L \cos(30^\circ + \theta) - V_{LL} I_L \cos(30^\circ - \theta) = -2 V_L I_L \sin\theta \sin 30^\circ$$

$$= -V_L I_L \sin\theta$$

$$\text{we know that } Q_T = \sqrt{3} V_{LL} I_L \sin\theta$$

$$\text{So, } Q_T = \sqrt{3} (P_2 - P_1)$$

$$S_T = \sqrt{Q_T^2 + P_T^2}$$

(EX) The two wattmeters reading are $P_1 = 1560 \text{ W}$ & $P_2 = 2100 \text{ W}$ when connected to Δ -load.

Find:

$$(1) \text{PF} = \cos\theta$$

$$(1) P_{1\phi} = \frac{P_2}{3} = \frac{P_1 + P_2}{3} = \boxed{1220 \text{ W}}$$

$$= \boxed{0.9688}$$


$$(2) Q_{1\phi} = \frac{Q_T}{3} = \frac{\sqrt{3} (P_2 - P_1)}{3} = \boxed{311.77 \text{ VAR}}$$

lagging. since $P_2 > P_1$

$$(3) \theta = \tan^{-1} \left(\frac{Q_T}{P_T} \right) = \boxed{14.34^\circ}$$


Ex) Find V_{BC} ?

No. _____

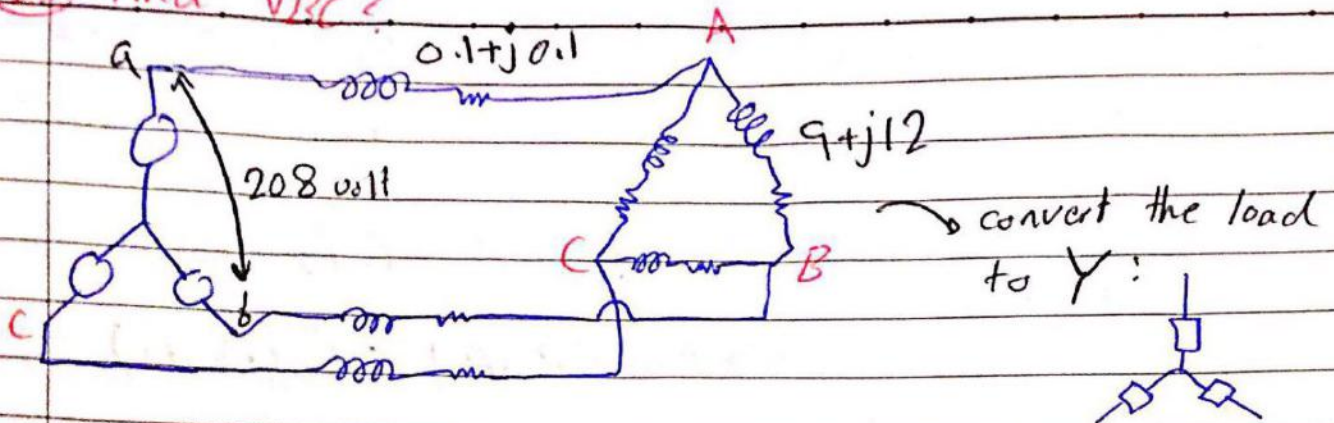

equivalent ckt: (single phase):

$$Z_Y = \frac{1}{3} Z_{\Delta}$$

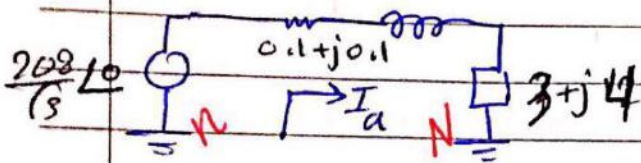

$$\Rightarrow V_{an} = \frac{208}{\sqrt{3}} L_0$$

$$I_a = \frac{\frac{208}{\sqrt{3}} L_0}{0.1 + j0.1 + 3 + j4}$$



$$\Rightarrow V_{AN} = I_a \times Z$$

$$= I_a \times (3 + j4) = 117 L_{0.22} \text{ volt}$$

$$\text{so } V_{AB} = \sqrt{3} \times 117 / 30.22 = 203 L_{30.22^\circ}$$

$$\text{so } V_{BC} = 203 L_{-89.78^\circ}$$

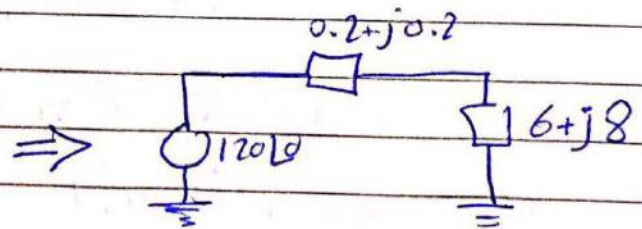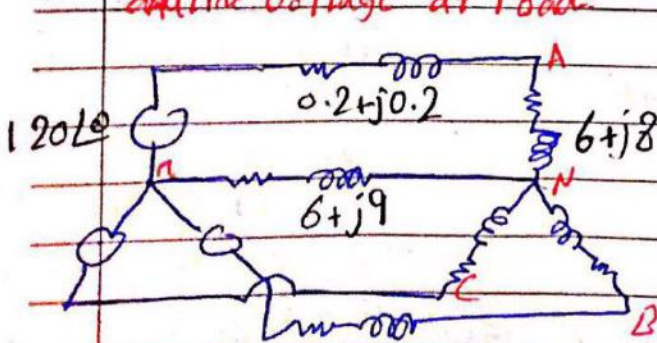* For the figure shown solve for line current, phase voltage and line voltage at load:



$$I_a = \frac{120 L_0}{6.2 + j8.2} = 11.7 L_{-52^\circ}$$

$$I_b = 11.7 L_{-52-120^\circ}$$

$$I_c = 11.7 L_{-52+120^\circ}$$

$$V_{AN} = (6 + j8) (11.7 L_{-52^\circ}) = 117 L_{0.23}$$

$$V_{AB} = 117 \sqrt{3} / 30.23^\circ$$

$$= 202.6 L_{30.23^\circ}$$

(ex.) Solve for I_a, I_b, I_c, I_{Nn} ?

since No load on the Neutral

$$V_N = 0$$


$$\text{so } I_a = \frac{V_{an}}{5} \Rightarrow \boxed{I_a = 24 \text{ A}}$$

$$I_b = \frac{V_{bn}}{-j5} \Rightarrow \boxed{I_b = 24 \angle -30^\circ \text{ A}}$$

$$I_c = \frac{V_{cn}}{j5} \Rightarrow \boxed{I_c = 24 \angle 30^\circ \text{ A}}$$

$$\Rightarrow I_{nN} = -(I_a + I_b + I_c)$$
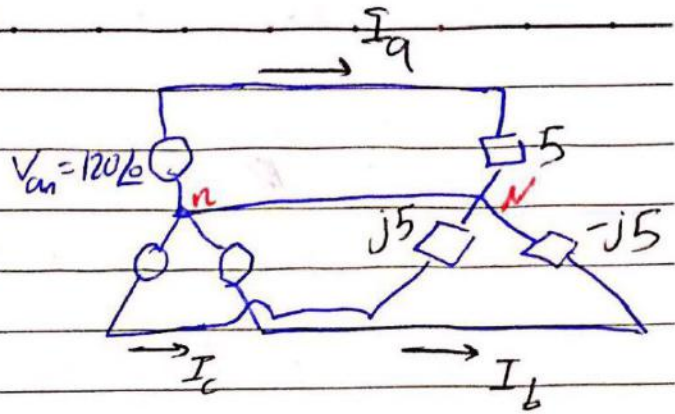
$$\boxed{I_{Nn} = I_a + I_b + I_c} \approx \underline{\underline{65.6 \text{ A}}}$$



(ex.) find I_a, I_b, I_c, I_{Nn} ?


$$I_a = \frac{V_{an} - V_N}{5}, \quad I_b = \frac{V_{bn} - V_N}{-j5}$$

$$I_c = \frac{V_{cn} - V_N}{j5}$$

$$I_a + I_b + I_c = I_{Nn} = \frac{V_N - V_n}{5 + j5} \rightarrow \text{Zero (Always } V_n \text{ equal zero)}$$

$$\frac{120 - V_N}{5} + \frac{120 \angle 120 - V_N}{-j5} + \frac{120 \angle 120 - V_N}{j5} = \frac{V_N}{5 + j5}$$

⇒ we find V_N then find the currents...

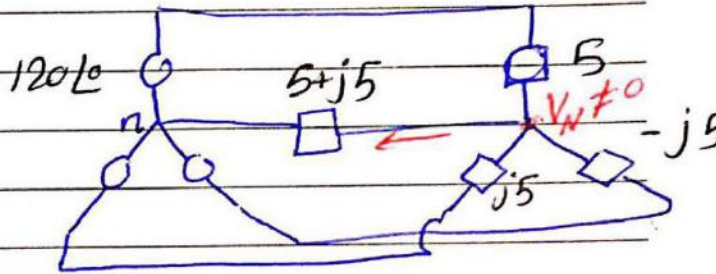


(ex.) given voltage of generator 208


& $Z_Y = 20 \angle 0^\circ$ & $Z_\Delta = 90 \angle 0^\circ$

convert the $\Delta \rightarrow Y$
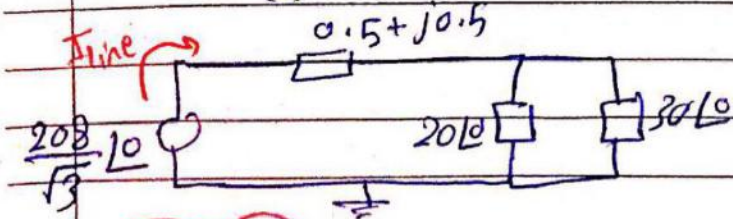
$$\Rightarrow Z_{Y(\Delta)} = 30 \angle 0^\circ$$


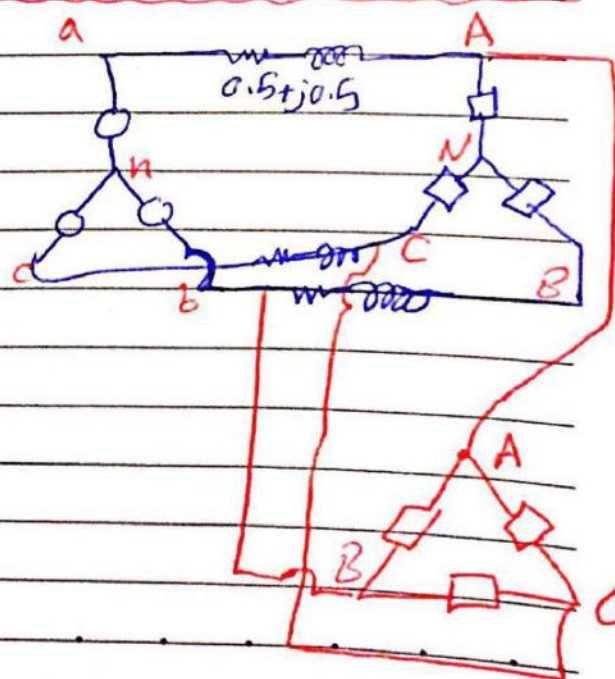
$$\boxed{I_{\text{line}} = \frac{120 \angle 0^\circ}{12.5 + j0.5} = 9.6 \angle -2.3^\circ}$$



→ Need $I_{(20\Omega)}$ & $I_{(30\Omega)}$

$$I_{(30\Omega)} = I_{line} \frac{20}{50} \quad I_{(20\Omega)} = I_{line} \frac{30}{50} = \underline{\underline{5.761-23 \text{ A}}}$$

But for Δ we need the current to (Δ) :


we have the Δ -line current ($I_{(30\Omega)}$)

$$\text{so } I_{line(\Delta)} = \frac{I_{30\Omega}}{\sqrt{3}} \angle 30^\circ = \underline{\underline{2.22 \angle 27.7 \text{ A}}}$$


After first

End of CH12

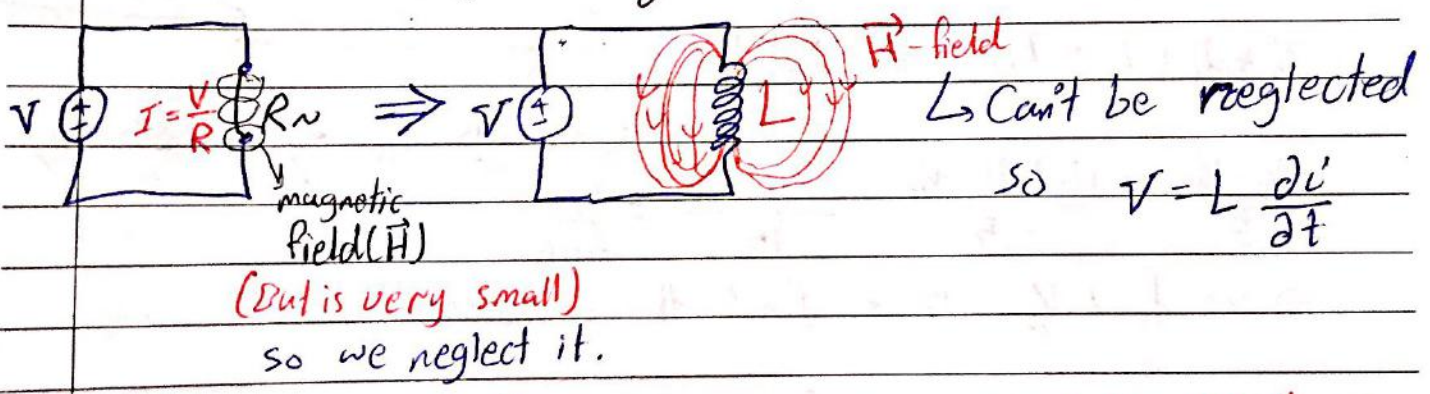CHAPTER(13): Magnetically coupled circuits:




⇒ magnetically coupled circuit.

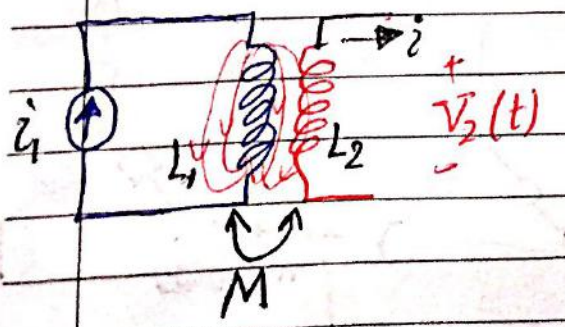

$$v_2(t) = M_{21} \frac{di_1(t)}{dt}$$

effect source

M_{12}
effect source

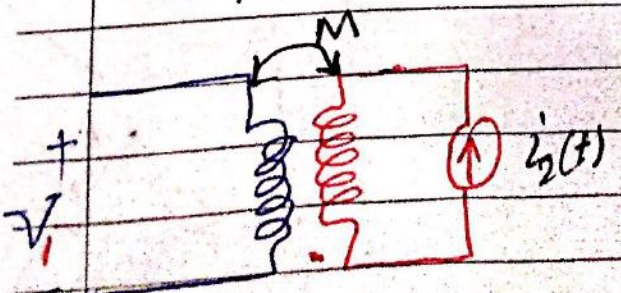

$$v_1 = M_{12} \frac{di_2(t)}{dt}$$


^A
 (ex.) Determine V_1 if $i_2 = 5 \sin 45t$ A, $i_1 = 0$

No. _____

$M = 2H$

$$V_1 = M \frac{di_2}{dt} = (2)(5)(45) \cos 45t$$




$$V_1 = 450 \cos 45t \text{ volt.}$$

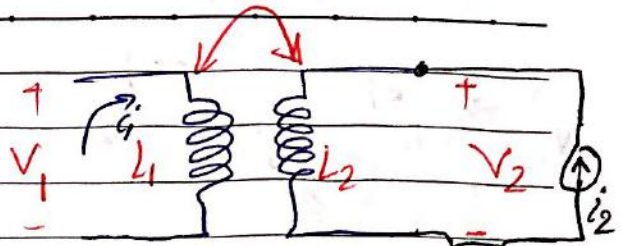

(2) Determine V_2 if $i_1 = -8e^{-t}$
 and $i_2 = 0$



$$V_2 = M \frac{di_1}{dt} = (2)(-8)(-1)e^{-t}$$

$$V_2 = 16e^{-t} \text{ volt.}$$

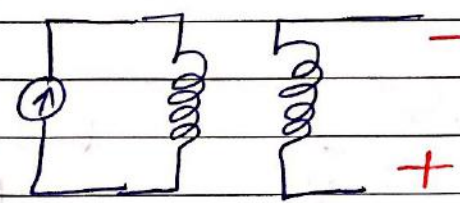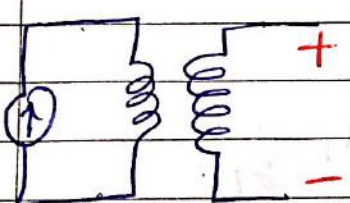
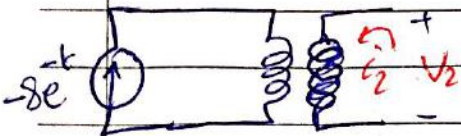


→ Dot Convention:

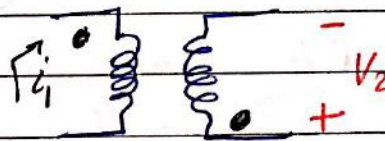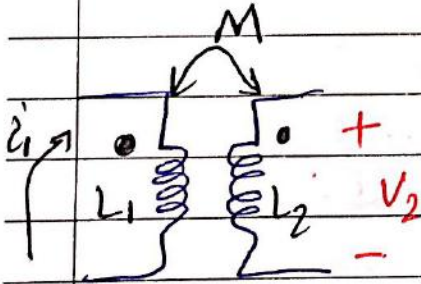(1) if i enters the dot in one coil it makes the dotted terminal on the other coil positive.




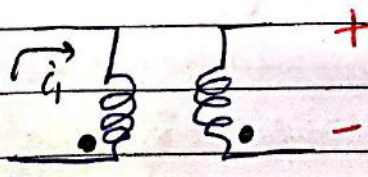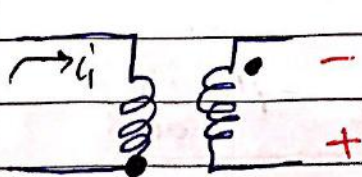(2) if i leaves the dot in one coil, it makes the dotted terminal on the other coil negative.



New Back to the ex after we know about Dot convention:

No. _____

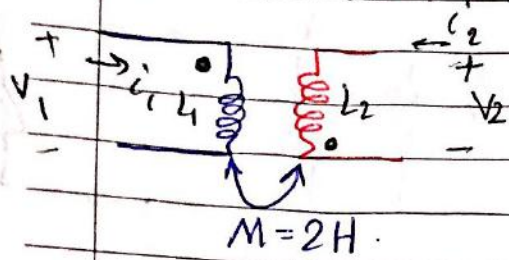


(1) $i_2 = 5 \sin 45t$, $i_1 = 0$, find V_1 ?

$$V_1 = -M \frac{di_2}{dt} = -450 \cos 45t \text{ volt.}$$

since i_2 leaving it make the other (ve).

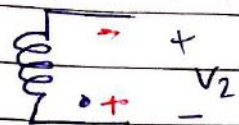
(2) find V_2 if $i_1 = -8e^{-t}$, $i_2 = 0$?

since i_1 entering it make the other (+ve).



$$V_2 = -M \frac{di_1}{dt} = -16e^{-t} \text{ volt.}$$

Ex.

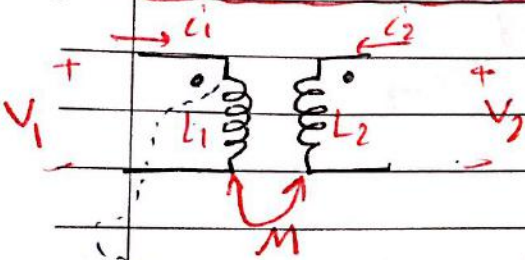

$$V_1 = \underbrace{L_1 \frac{di_1}{dt}}_{\text{self inductance}} + \underbrace{M \frac{di_2}{dt}}_{\text{Mutual inductance}}$$

* so you can reach this by KVL

Assume here like a voltage source $M \frac{di_2}{dt}$


$$-V_1 + M \frac{di_2}{dt} + L_1 \frac{di_1}{dt} = 0$$

$$\Rightarrow V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

* Do the same for the other one:

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

Ex.

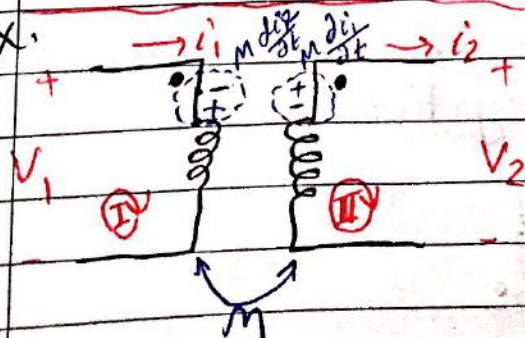

from loop (I):


$$-V_1 - M \frac{di_2}{dt} + L_1 \frac{di_1}{dt} = 0$$

$$\Rightarrow V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

from loop (II):

$$V_2 + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} = 0$$
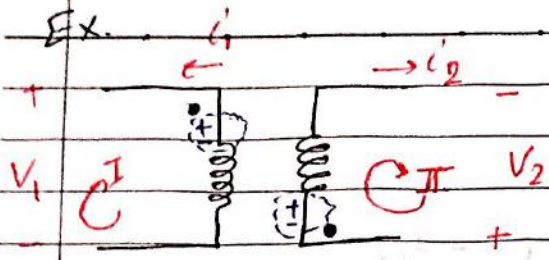
$$\Rightarrow V_2 = -L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$




loop (I): $V_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = 0$
 $\Rightarrow V_1 = -L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$

loop (II): $-V_2 - M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} = 0$

In Frequency Domain:

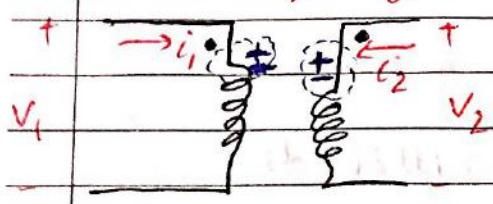
$\Rightarrow V_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$



$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$
 $\Rightarrow V_1 = j\omega L_1 I_1 + j\omega M I_2$
 $V_2 = j\omega L_2 I_2 + j\omega M I_1$

→ Do the same for all previous examples.

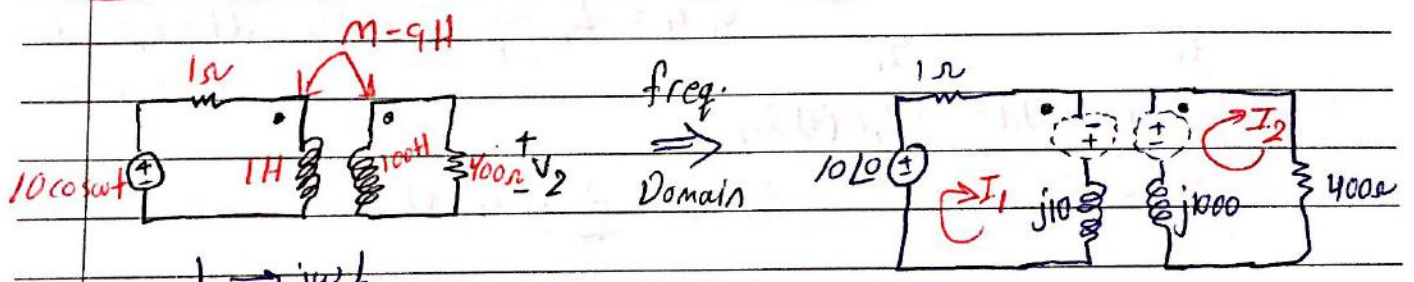Ex. Find V_2 for the shown ckt: ($\omega = 10$)



$L \rightarrow j\omega L$
 $M \rightarrow j\omega M$


mesh analysis:

$-10\angle 0 + I_1 + j10I_1 - j90I_2 = 0 \dots (1)$
 $I_2(400 + j1000) - j90I_1 = 0 \dots (2)$

⇒ solving for (1) & (2):

$I_2 = 0.172 \angle -16^\circ$
 so $V_2 = I_2 R \Rightarrow V_2 = 68.8 \angle -16^\circ$ volt.

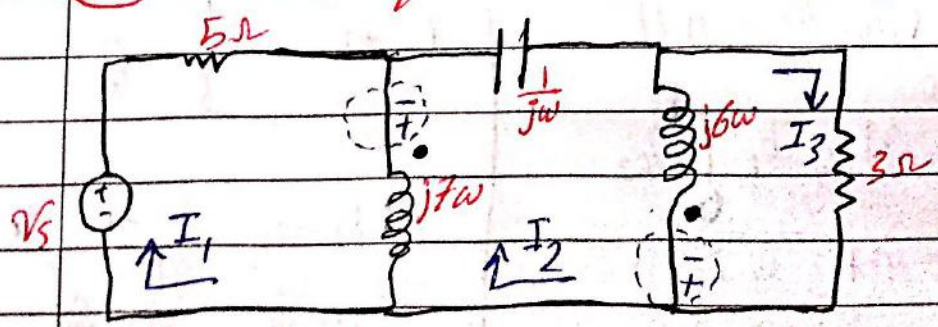Ex. Write the equations for the meshes in the shown ckt'



$I_2 - I_3$ (leaving)
 $I_1 - I_2$ (entering)

$M = j2\omega$


* mesh(1): (one virtual source).

$$-V_s + 5I_1 + j7\omega(I_1 - I_2) - j2\omega(I_2 - I_3) = 0$$

* mesh(3): (one virtual source)

$$3I_3 + j6\omega(I_3 - I_2) + j2\omega(I_1 - I_2) = 0$$


* mesh(2): (two virtual sources)

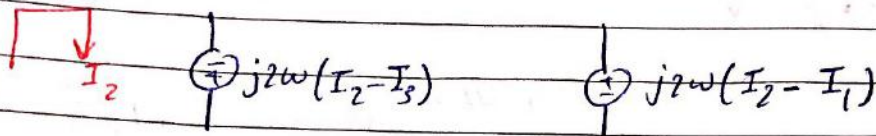

$$\Rightarrow \frac{1}{j\omega} I_2 + j6\omega(I_2 - I_3) + j7\omega(I_2 - I_1) + j2\omega(I_2 - I_1) + j2\omega(I_2 - I_3) = 0$$

* Energy stored in a ckt with mutual inductance:
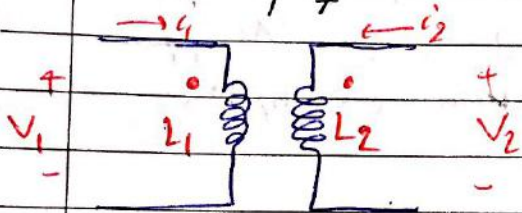
$$P = \frac{1}{T} \int v(t) \cdot i(t) dt, \quad W = \int v(t) i(t) dt.$$



*** set $I_2 = 0$
lets make $i_1: 0 \rightarrow I_1$
 $t: 0 \rightarrow t_1$

$$v_1 i_1 = L_1 \frac{di_1}{dt} i_1 \Rightarrow v_1 i_1 dt = L_1 i_1 di_1$$

integrate...

$$\Rightarrow \int_0^{t_1} v_1(t) i_1(t) dt = \int_0^{I_1} L_1 i_1(t) di_1$$

W

$$\Rightarrow W = \frac{1}{2} L_1 i_1^2(t)$$

set $i_1(t) = I_1$
let $i_2(t): 0 \rightarrow I_2$
 $t: t_1 \rightarrow t_2$


$$\Rightarrow \int_{t_1}^{t_2} v_2 i_2 dt = \int_0^{I_2} L_2 i_2(t) di_2$$

W

$$\Rightarrow W = \frac{1}{2} L_2 i_2^2(t)$$

$$v_1(t) = M_{12} \frac{di_2}{dt}$$
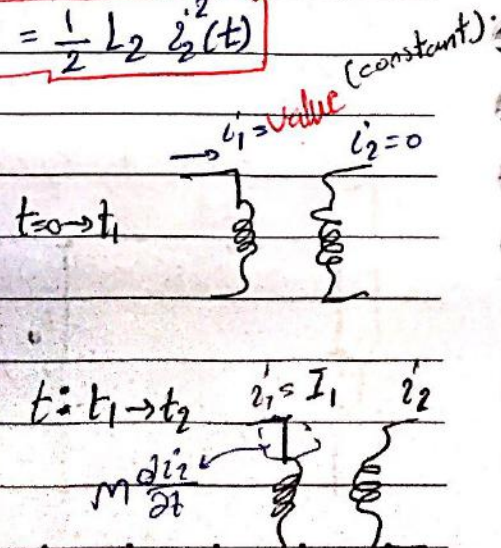
$$\begin{aligned} \text{so } \int_{t_1}^{t_2} v_1(t) i_1(t) dt &= \int_0^{I_2} M_{12} \frac{di_2}{dt} i_1(t) dt \\ &= M_{12} I_1 \int_0^{I_2} di_2 \\ &= M_{12} I_1 I_2 \end{aligned}$$



Total energy:


$$W_{\text{total}} = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M_{12} I_1 I_2$$

$$W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M_{21}^{\text{No.}} I_1 I_2$$

$$\Rightarrow M_{12} = M_{21} = M$$

instantaneous energy:
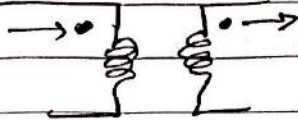
$$W(t) = \frac{1}{2} L_1 i_1^2(t) + \frac{1}{2} L_2 i_2^2(t) + M i_1(t) i_2(t)$$



$$W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 - M I_1 I_2$$



- * if the two current leaving or entering the dot (M (+ve)).
- * if one of the current leaving & the other entering (M (-ve)).

⇒ Set an upper limit for M :

$$W > 0, i_1 > 0, i_2 > 0$$

$$\Rightarrow \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 - M I_1 I_2 > 0$$

$$\Rightarrow \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + I_1 I_2 \sqrt{L_1 L_2} - I_1 I_2 \sqrt{L_1 L_2} - M I_1 I_2 > 0$$

$$\Rightarrow \frac{1}{2} (I_1 \sqrt{L_1} - I_2 \sqrt{L_2})^2 + I_1 I_2 (\sqrt{L_1 L_2} - M) > 0$$

To guarantee that $W > 0 \Rightarrow I_1 I_2 (\sqrt{L_1 L_2} - M) > 0$


$$\Rightarrow \sqrt{L_1 L_2} - M > 0 \Rightarrow \sqrt{L_1 L_2} > M$$

this is the upper limit.

* Coupling Coefficient:

$$K = \frac{M}{\sqrt{L_1 L_2}}$$

$$0 \leq K \leq 1$$

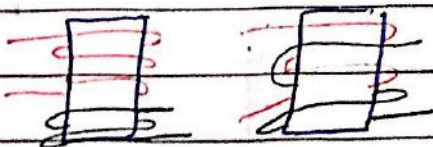


Ex) find $v_1(t)$, $w(t)$:

$K = 0.6$

given:

$i_1 = 20 \cos(500t - 20) \text{ mA}$

$i_2 = 5 \cos(500t - 20) \text{ mA}$

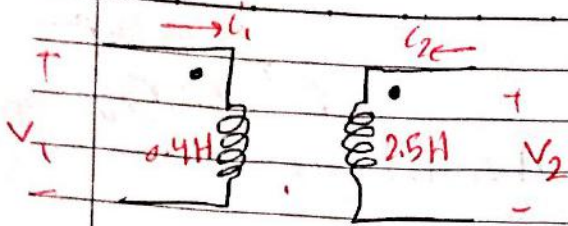

first find M :

$M = K \sqrt{L_1 L_2} = 0.6 \text{ H}$

$v_1(t) = L_1 \frac{di_1(t)}{dt} + M \frac{di_2(t)}{dt}$

$w(t) = \frac{1}{2} i_1^2(t) L_1 + \frac{1}{2} L_2 i_2^2(t) + M i_1(t) i_2(t)$


$v_1(t) = 0.4 \times [-20 \times 500 \sin(-20)] + 0.6 [-5 \times 500 \sin(-20)]$

$= \frac{1}{2} [20 \cos(-20)]^2 \times 0.4 + \frac{1}{2} [5 \cos(-20)]^2 \times 2.5 + 0.6 \times 20 \cos(-20) \times 5 \cos(-20)$

$v_1(0) = 1.881 \text{ Volt}$


$w(0) = 151.2 \text{ } \mu\text{J}$

Transformer:

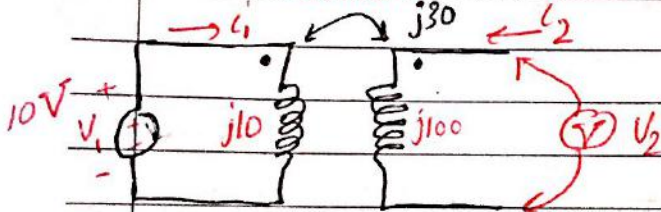


$10 = v_1 = j10 I_1 + j30 I_2$

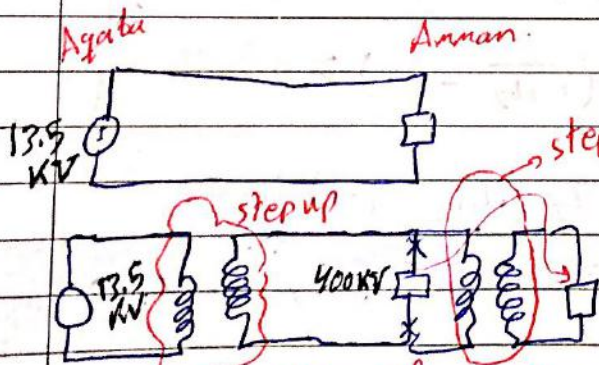$10 = v_2 = j100 I_2 + j30 I_1$
(acceptable)




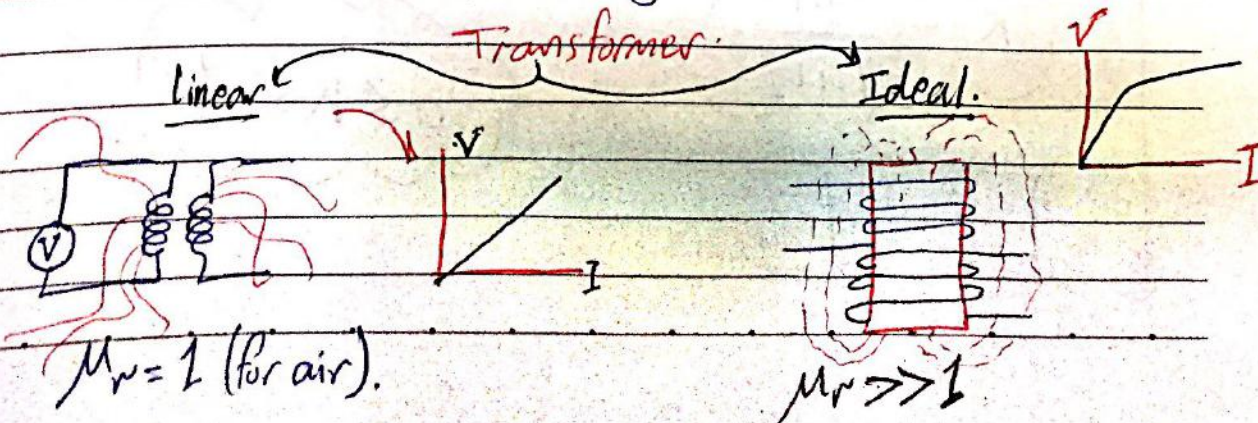Transformer: used to step up & step down the voltage.



* Linear Transformer:

Linear Transformer

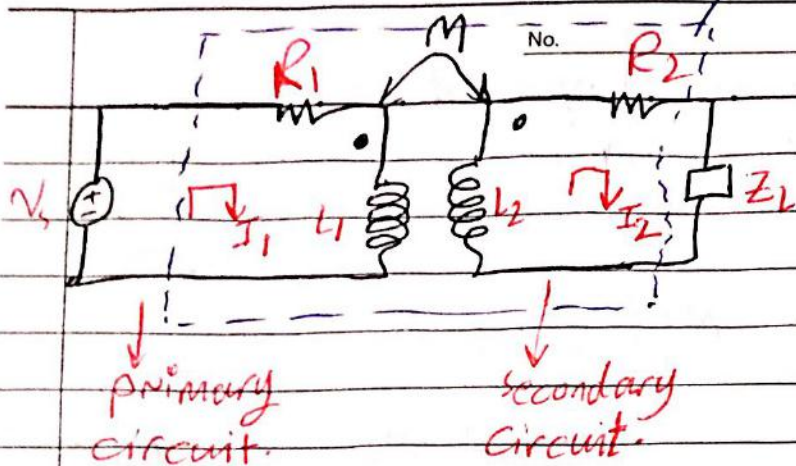

from the two meshes:

$$V_s = (R_1 + j\omega L_1)I_1 - j\omega M I_2$$

$$0 = (j\omega L_2 + R_2 + Z_L)I_2 - j\omega M I_1$$

$$\Rightarrow Z_{11} = R_1 + j\omega L_1$$

$$Z_{22} = R_2 + Z_L + j\omega L_2$$

The mesh equ. become

$$\Rightarrow V_s = Z_{11} I_1 - j\omega M I_2$$

$$0 = -j\omega M I_1 + Z_{22} I_2$$

$$\Rightarrow \begin{bmatrix} V_s \\ 0 \end{bmatrix} = \begin{bmatrix} Z_{11} & -j\omega M \\ -j\omega M & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\Rightarrow I_2 = \left(\frac{j\omega M}{Z_{22}} \right) I_1 \Rightarrow V_s = Z_{11} I_1 - j\omega M I_1 \left(\frac{j\omega M}{Z_{22}} \right)$$

$$\Rightarrow V_s = Z_{11} I_1 + \frac{\omega^2 M^2}{Z_{22}} I_1 \Rightarrow \frac{V_s}{I_1} = Z_{in}$$


$$\Rightarrow Z_{in} = Z_{11} + \frac{\omega^2 M^2}{Z_{22}} = Z_{11} + \frac{\omega^2 M^2}{R_{22} + jX_{22}} * \frac{(R_{22} - jX_{22})}{(R_{22} - jX_{22})}$$

$$\Rightarrow Z_{in} = Z_{11} + \frac{\omega^2 M^2 R_{22}}{R_{22}^2 + X_{22}^2} - j \frac{\omega^2 M^2 X_{22}}{R_{22}^2 + X_{22}^2}$$

* The presence of secondary increase losses in the primary:

Reflected Impedance

* The T-equivalent circuit:

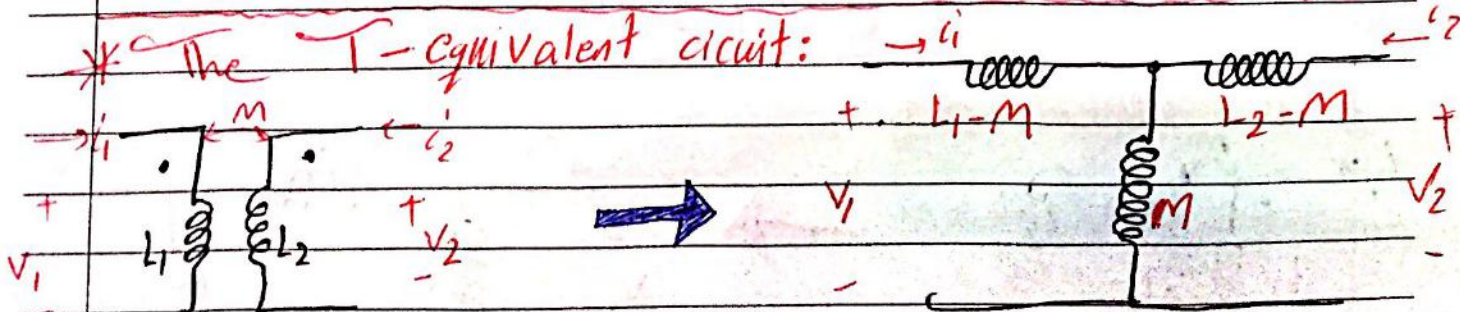


$$V_1 = j\omega L_1 I_1 + j\omega M I_2$$

$$V_2 = j\omega L_2 I_2 + j\omega M I_1$$


if the currents leaving the dot.

⇒ left mesh: $V_1 = (j\omega L_1 - j\omega M) I_1 + j\omega M(I_1 + I_2)$
 $= j\omega L_1 I_1 - j\omega M I_1 + j\omega M I_1 + j\omega M I_2 = j\omega L_1 I_1 + j\omega M I_2$

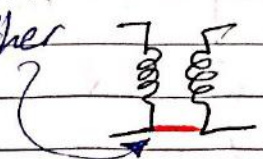* There is one condition ^{No.} To use T-equivalent ckt:
 that the two coil must be connected together




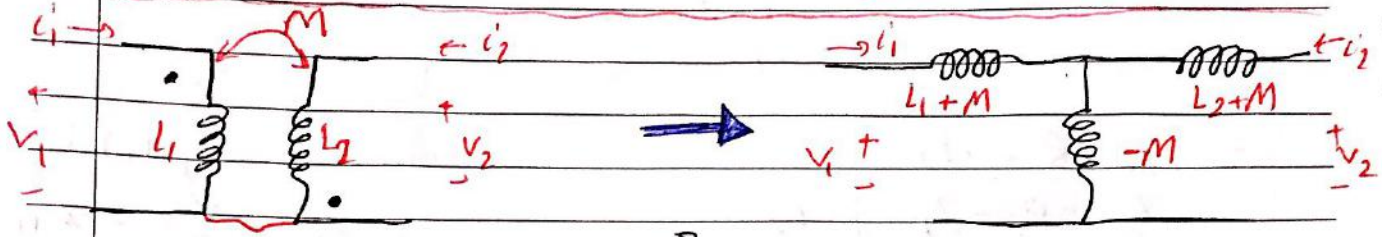
⇒ right mesh:
 $V_2 = (j\omega L_2 - j\omega M) I_2 + j\omega M(I_1 + I_2) = j\omega L_2 I_2 + j\omega M I_1$



if one of the currents enter the dot & the other leave.


ex Find the T-equivalent ckt.

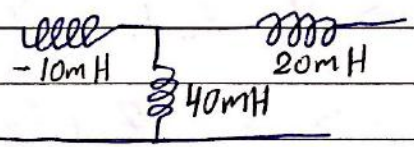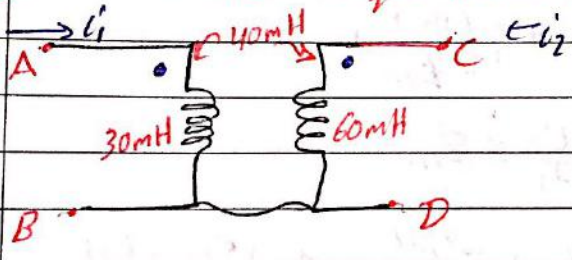since the two currents entering it would be the first figure for T-equ. ckt.



* if $V_{AB} = 10 \angle 0^\circ$ & $\omega = 100$
 find I_1 & V_{CD} ?

converting to freq. domain.

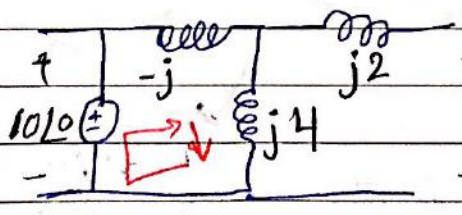


$I_1 = \frac{10 \angle 0^\circ}{j3} = 3.33 \angle -90^\circ$


$i_1(t) = 3.33 \cos(100t - 90^\circ) A$

so $V_{CD} = j4 \times I_1 = 13.33 \angle 0^\circ$ volt.

* T-equivalent ckt:

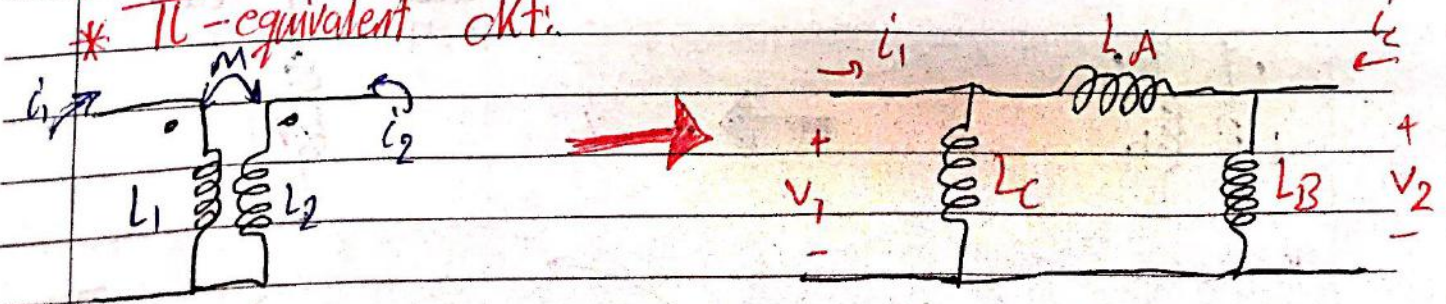

To know the values of L_A & L_B & L_C :

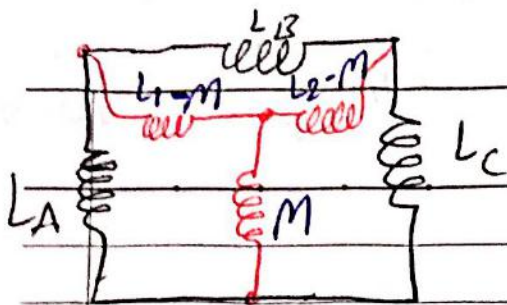


this situation if the two currents entering the dot or leaving.

$$\rightarrow L_B = \frac{(L_1 - M)(L_2 - M) + (L_1 - M)M + (L_2 - M)M}{M} = \frac{L_1 L_2 - M^2}{M}$$


$$L_A = \frac{L_1 L_2 - M^2}{L_2 - M}$$

$$L_C = \frac{L_1 L_2 - M^2}{L_1 - M}$$

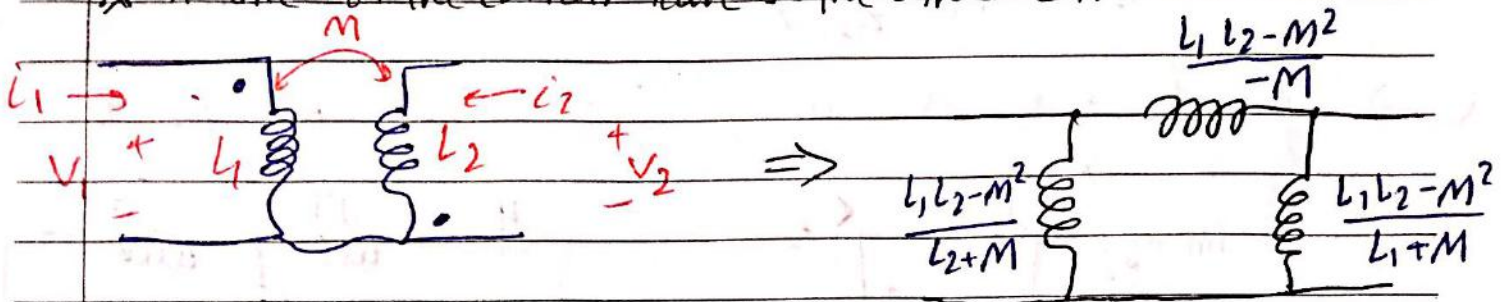* if one of the current leave & the other enter:




(Ex) Find the π -equivalent ckt for:

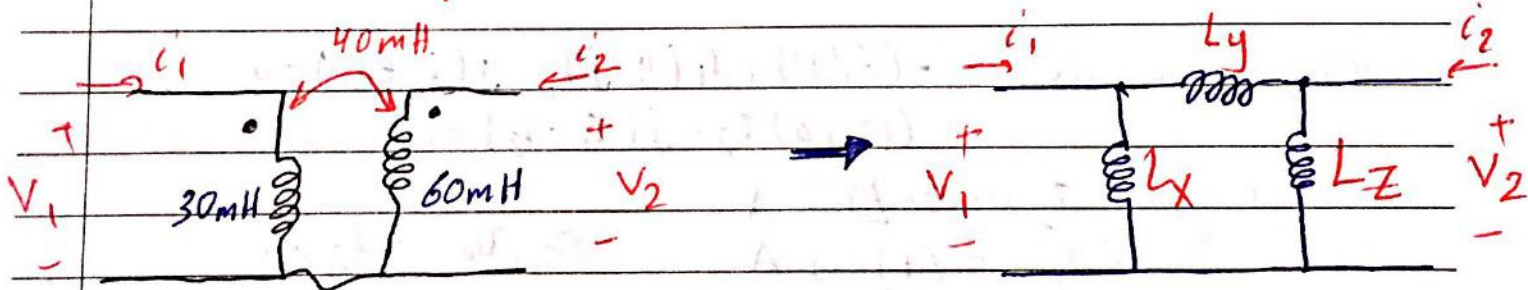

$$\Rightarrow L_x = \frac{L_1 L_2 - M^2}{L_2 - M} = \boxed{10 \text{ mH}} \quad \Rightarrow L_y = \frac{L_1 L_2 - M^2}{M} = \boxed{5 \text{ mH}}$$

$$\Rightarrow L_z = \frac{L_1 L_2 - M^2}{L_1 - M} = \boxed{-20 \text{ mH}}$$

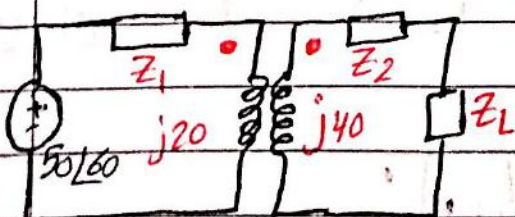(Ex) Calculate the input impedance & current I_1 for:



given: $Z_1 = 60 - j100$

$Z_2 = 30 + j40$

$Z_L = 80 + j60$

$$Z_{11} = Z_1 + j20 = 60 - j80 \quad , \quad Z_{22} = Z_1 + Z_2 + j40 = 110 + j140$$

$$Z_{in} = Z_{11} + \frac{\omega^2 M^2}{Z_{22}} \Rightarrow \text{we have } \omega M = 5 \Rightarrow Z_{in} = 60 - j80 + \frac{25}{110 + j140}$$

No. _____

so $Z_{in} = 100.14 \angle -53^\circ$


$$Z_{in} = \frac{V_1}{I_1} \Rightarrow I_1 = \frac{V_1}{Z_{in}} = \frac{50 \angle 160}{100.14 \angle 53^\circ} \Rightarrow I_1 = 0.5 \angle 113^\circ$$

if he asked about I_2 :

we can take the right mesh; But more easier:

$$\Rightarrow I_2 = I_1 \left(\frac{j\omega M}{Z_{22}} \right) \Rightarrow \text{Answer} = 0.014 \angle 151.2^\circ$$

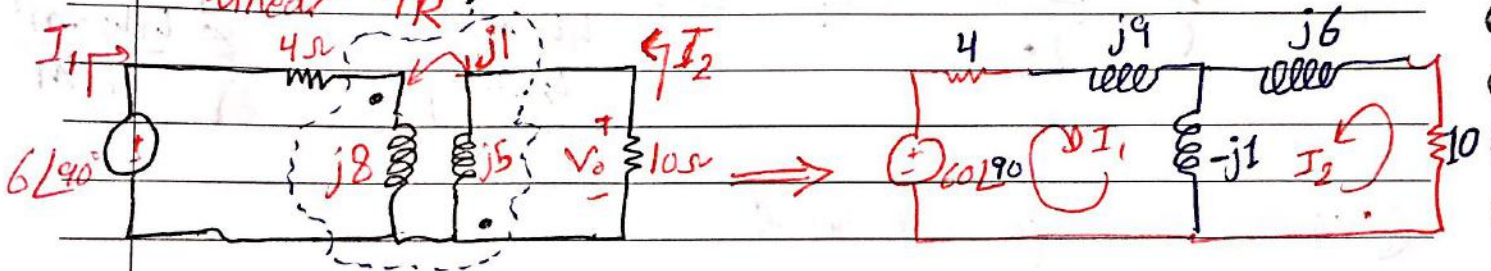Ex. Solve for I_1, I_2, V_0 using T-equivalent ckt for the linear TR:



Using mesh analysis: $-(6 \angle 90) + I_1(4 + j9) - j(I_1 + I_2) = 0 \quad \dots (1)$

$(10 + j6)I_2 - j(I_1 + I_2) = 0 \quad \dots (2)$


Solving: $I_2 = 0.06 \angle 90^\circ \text{ A}$
 $I_1 = 0.6 + j0.3 \text{ A}$

$\Rightarrow V_0 = -I_2 \times 10$

$\Rightarrow V_0 = 0.6 \angle -90^\circ$

* Second material *


* Ideal Transformer *

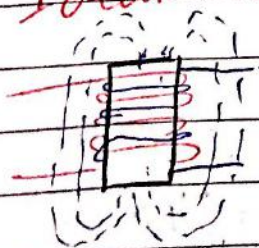

$M \neq 1$

Assuming the two coils purely inductive $\Rightarrow R_1 = 0 = R_2$

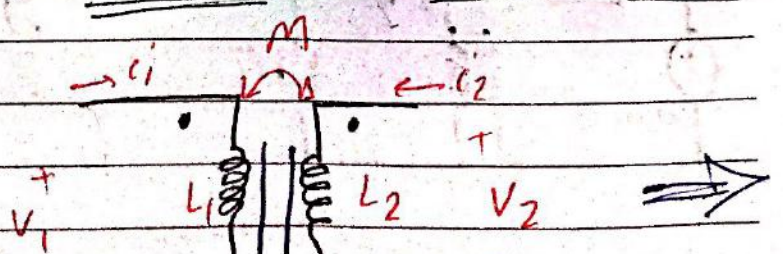Also $\Rightarrow L_1 = \infty = L_2$ & $K = 1$ so $M = \infty$



$$\begin{aligned} \Rightarrow V_1 &= j\omega L_1 I_1 + j\omega M I_2 \Rightarrow I_1 = \frac{V_1 - j\omega M I_2}{j\omega L_1} \\ V_2 &= j\omega L_2 I_2 + j\omega M I_1 \Rightarrow V_2 = j\omega L_2 I_2 + j\omega M \left(\frac{V_1 - j\omega M I_2}{j\omega L_1} \right) \end{aligned}$$


$$V_2 = j\omega L_2 I_2 + \frac{M}{L_1} V_1 - j\omega \frac{M^2}{L_1} I_2 = j\omega L_2 I_2 + \frac{\sqrt{L_1 L_2}}{L_1} V_1 - j\omega \frac{(L_1 L_2)}{L_1} I_2$$

$$\Rightarrow V_2 = \sqrt{\frac{L_2}{L_1}} V_1 \quad \text{***}$$

$$\Rightarrow V_2 = \frac{N_2}{N_1} V_1 \quad \text{***}$$

I_1 primary
= I_2 secondary

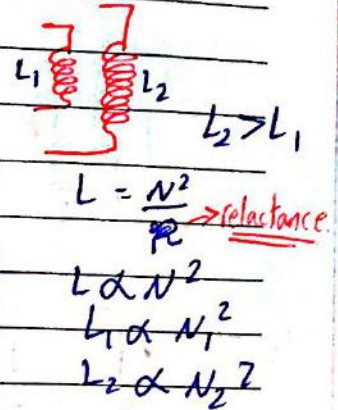turns ratio (a)
 $L \propto N^2$
 $L_1 \propto N_1^2$
 $L_2 \propto N_2^2$



$$|S_1| = |S_2| \Rightarrow V_1 I_1 = V_2 I_2$$

$$\Rightarrow \frac{V_2}{V_1} = \frac{I_1}{I_2} = a = \frac{N_2}{N_1} \quad \text{***}$$

* if $N_2 > N_1 \Rightarrow$ step up transformer

ex) An ideal transformer is rated 2400/120 V, 9.6 kVA and it has 50 turns on the secondary find:

* if $N_1 > N_2 \Rightarrow$ step down transformer.

① turns ratio. $\frac{2400}{120} = \frac{V_1}{V_2} \Rightarrow a = \frac{N_2}{N_1} = \frac{V_2}{V_1} = \frac{120}{2400} = \boxed{0.05}$

② turns on primary side. $\frac{N_2}{N_1} = a = \frac{50}{N_1} = 0.05 \Rightarrow \boxed{N_1 = 1000}$ turns.

③ The rated currents on primary & secondary.


$$|S_1| = |S_2| \quad S_1 = V_1 I_1 \Rightarrow I_1 = \frac{9.6 \times 10^3}{2400} = \boxed{4A}$$

$$S_2 = V_2 I_2 \Rightarrow I_2 = \frac{9.6 \times 10^3}{120} = \boxed{80A}$$

* 2 Rules to define the voltage polarities & current directions:


① If V_1, V_2 are both (+ve) or both (-ve) at the dotted terminals use +n for V_2 or (-n, otherwise).

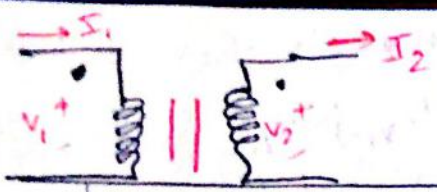② If I_1, I_2 both enter into or both leave the dotted terminals use -n for I_1, I_2 ; otherwise use +n.




\Rightarrow since V_1, V_2 both +ve $\Rightarrow \frac{V_2}{V_1} = a$
 \Rightarrow since one enter & one leave for currents


No. $\Rightarrow \frac{I_1}{I_2} = a$

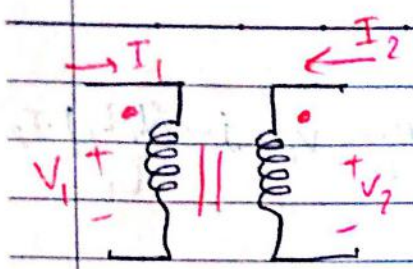

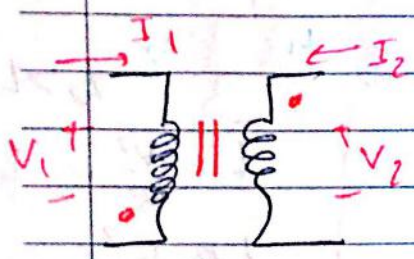$\Rightarrow \frac{V_2}{V_1} = a$, $\frac{I_1}{I_2} = -a$



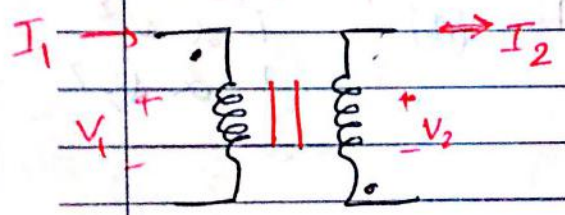$\frac{V_2}{V_1} = -a$, $\frac{I_1}{I_2} = a$



$\frac{V_2}{V_1} = -a$, $\frac{I_1}{I_2} = -a$

Complex Power in the transformer: (lossless)


$$S_1 = V_1 I_1^* = \left(\frac{V_2}{n}\right) (n I_2^*) = V_2 I_2^* = S_2$$

Input Impedance: $\frac{N_2}{N_1} = n$


$$Z_{in} = \frac{V_1}{I_1} = \frac{V_2/n}{n I_2}$$

$$= \frac{1}{n^2} \frac{V_2}{I_2} = \frac{1}{n^2} Z_L$$

"Reflected Impedance"

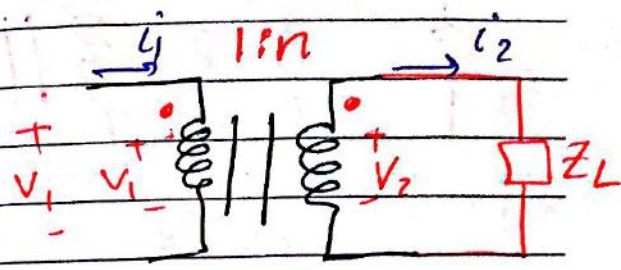
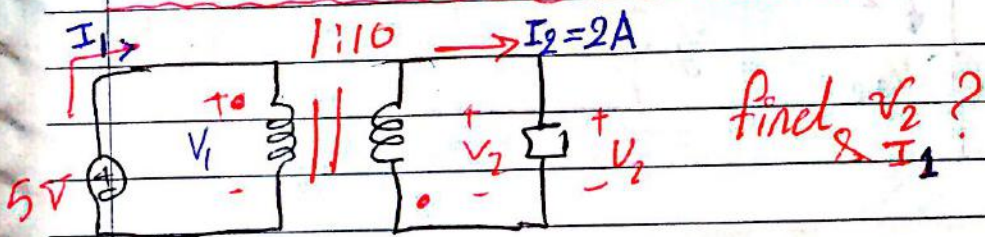
$$Z_2 = \frac{V_2}{I_2}, \quad \frac{V_2}{V_1} = \frac{1}{n}$$
$$\frac{I_1}{I_2} = n$$




since the dots one (-ve) & one (+ve)

$$\frac{V_2}{V_1} = -n$$
$$\Rightarrow V_2 = -50 \text{ volt.}$$

since both currents entering


$$\frac{I_1}{I_2} = -n \Rightarrow I_1 = -20A$$

for the ckt in the top of this page:

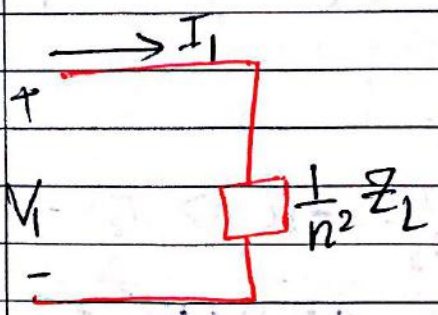


Equivalent ckt refer to Primary

* Equivalent ckt:

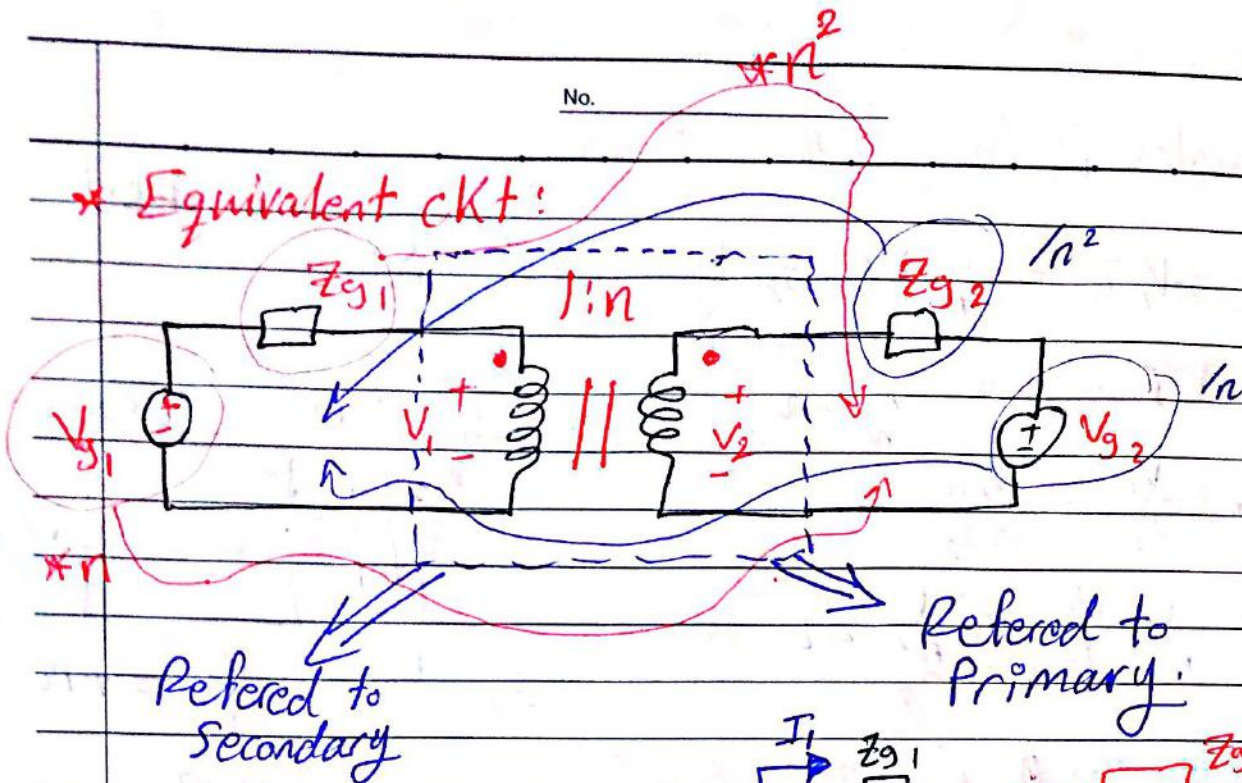



Referred to Secondary

Referred to Primary

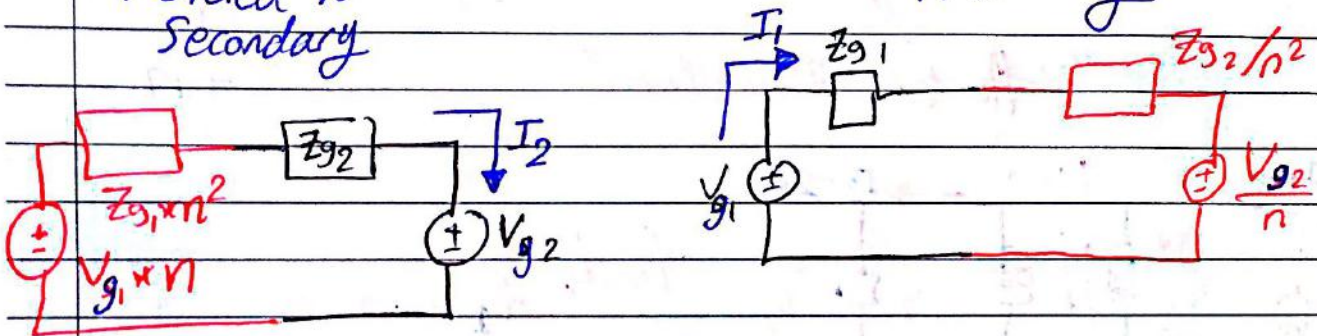

(ex) For the shown ideal TR find the source current I_1 , the output voltage V_o , the complex power supplied by the source.

using Reflection:

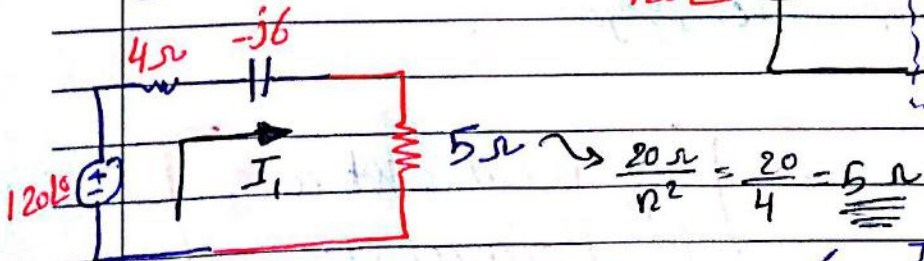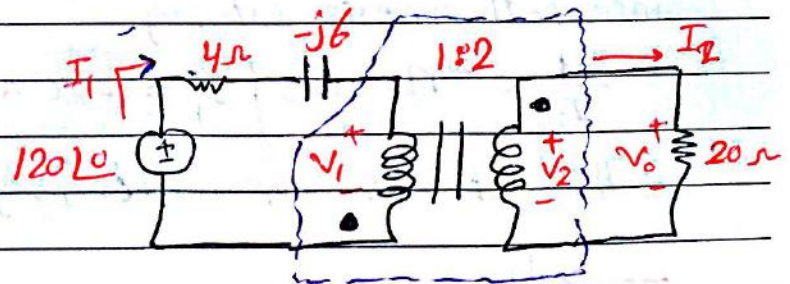

$$I_1 = \frac{120 \angle 0^\circ}{9 - j6} = 11.01 \angle 33.7^\circ$$

$$\frac{I_1}{I_2} = -n \Rightarrow I_2 = -5.505 \angle 133.7^\circ$$

$$\Rightarrow V_o = 110.9 \angle 213.7^\circ$$

from the main ckt:

$$V_o = I_2 \times 20$$

* Another method to find V_0 :
 $V_0 = 5 \times (11.1 \angle 33.7^\circ) \Rightarrow$ it is a reflected voltage

new CKI

$$\equiv V_0'$$

No. _____

$$\frac{V_2}{V_1} = -2 \Rightarrow V_2 = -2V_1 = -2 \times 5 \times I_1 = 110.9 \angle 213.7^\circ$$


* complex power:

$$S_i = V_1 (I_1^*) = 120 (11.1 \angle -33.7^\circ) = 1330.8 \angle -33.7^\circ \text{ VA}$$

(ex) Calculate the power supplied to the 10Ω Resistor:

⊘ We Can't do Reflection.

using (KVL):

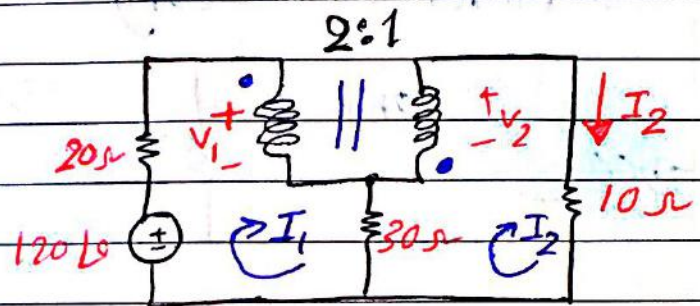

mesh(1):

$$-120 + 20I_1 + V_1 + 30(I_1 - I_2) = 0 \quad (1)$$

mesh(2):

$$30(I_2 - I_1) - V_2 + 10I_2 = 0 \quad (2)$$

$$\Rightarrow \text{also } \frac{V_2}{V_1} = -\frac{1}{2}$$


solving:

put them in (1) & (2) $\Rightarrow \frac{I_1}{I_2} = -\frac{1}{2}$

$$I_2 = -0.7272 \text{ A}$$

$$\Rightarrow P = I_2^2 R \Rightarrow P_{10\Omega} = 5.3 \text{ W}$$

(ex)

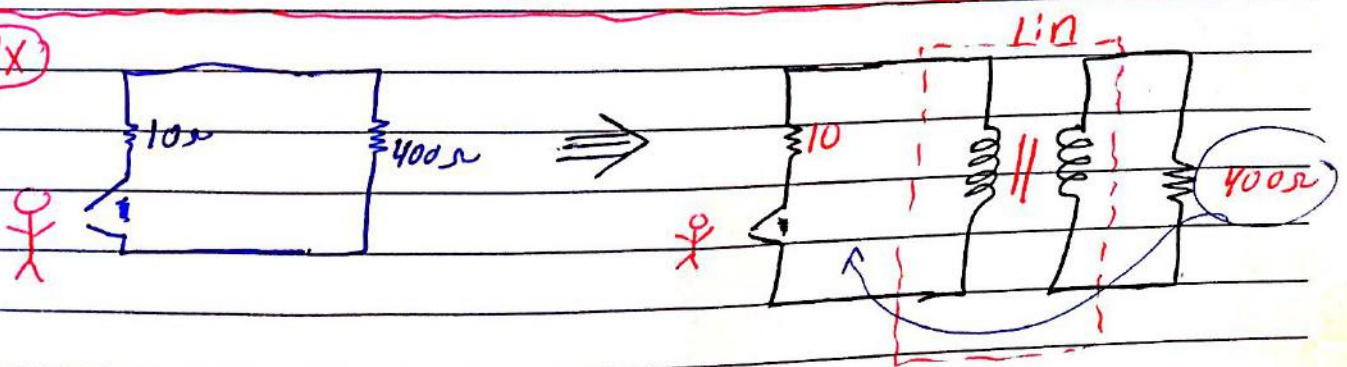


$$Z_{\text{reflected}} = 10 = \frac{1}{n^2} \times 400$$

$$n = \sqrt{40}$$


Reflected the following ckt to primary & to secondary:

No. _____


(ex)

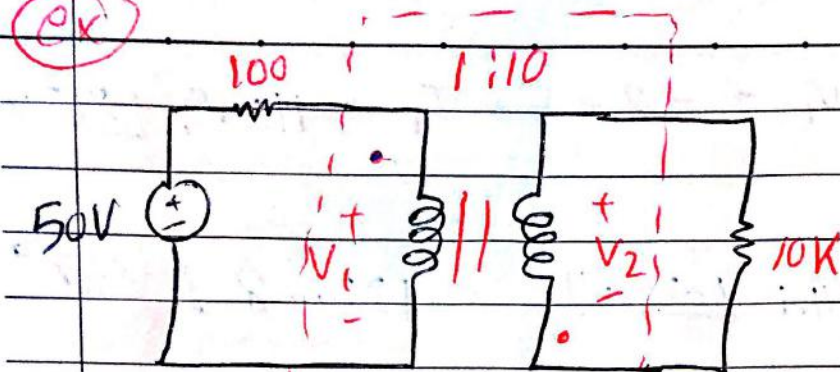

→ Refer to primary:

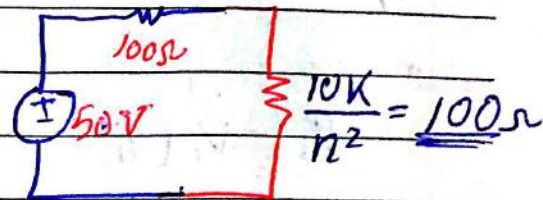

→ Refer to Secondary:

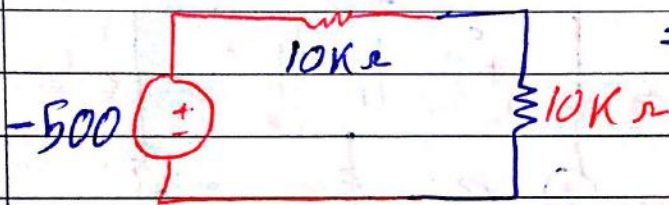

* Be aware for the sign of n.

$$\frac{V_2}{V_1} = -10$$




$$\Rightarrow (50)(-10) = -500 \text{ volt}$$

End of CH3



CHAPTER (14)


Frequency Response.

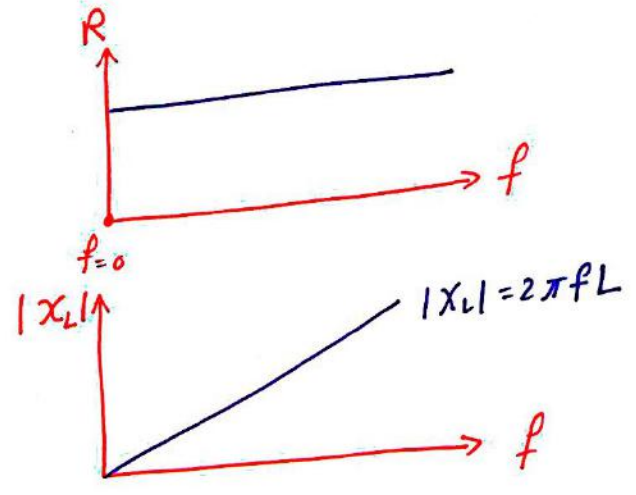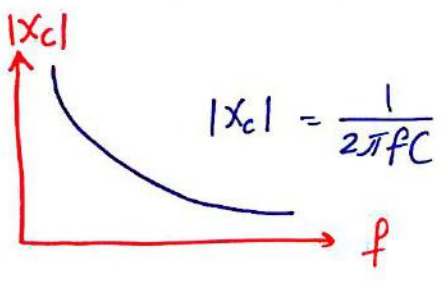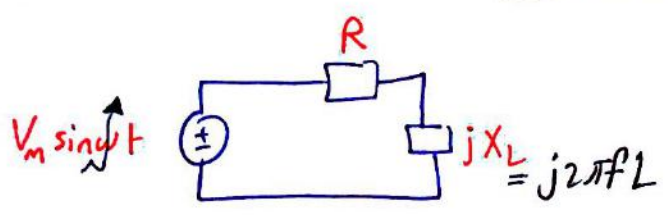

These 3-figures for Z.

* Parallel Resonance:




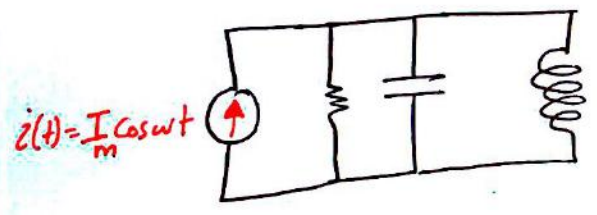
*What is Resonance CKT? it is a CKT that contains R, L, C when in Parallel or in series or combination.



$$Z_{eq} = R // X_C // X_L$$

$$Y_{eq} = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C$$

The following 3-figures for Y.

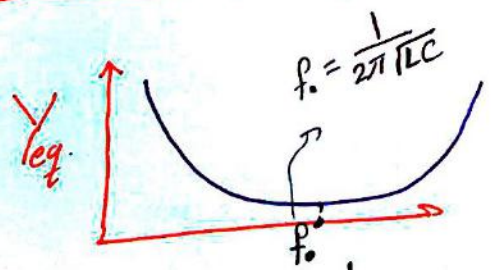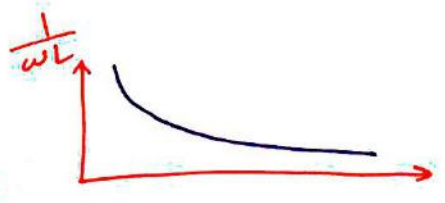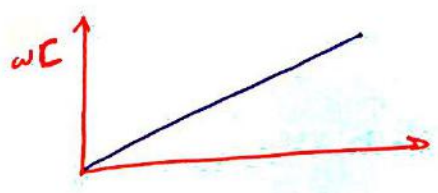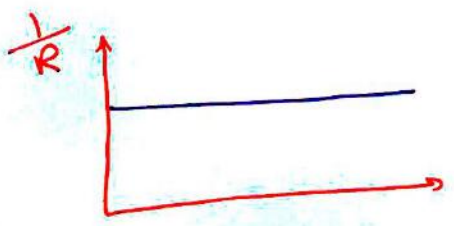


$$Y_{eq} = \sqrt{\left(\frac{1}{R}\right)^2 + \left(\omega C - \frac{1}{\omega L}\right)^2}$$



lets Assume $|\omega C| = \frac{1}{\omega L}$
 $\Rightarrow \omega C = \frac{1}{\omega L} \Rightarrow \omega^2 = \frac{1}{LC} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$ "Resonance Frequency."

\Rightarrow At Resonance: $Y_{eq} = \frac{1}{R}$

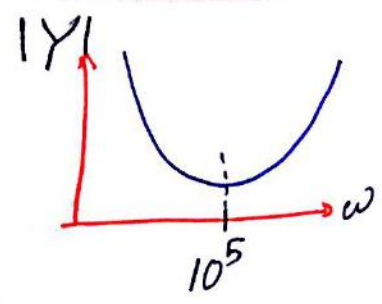Ex. $L = 1\text{mH}, C = 0.1\mu\text{F}$
 $\omega = \frac{1}{\sqrt{LC}} = 10^5 \text{ rad/sec.}$




$V = IZ$
 $|V| = |I_m| |Z|$

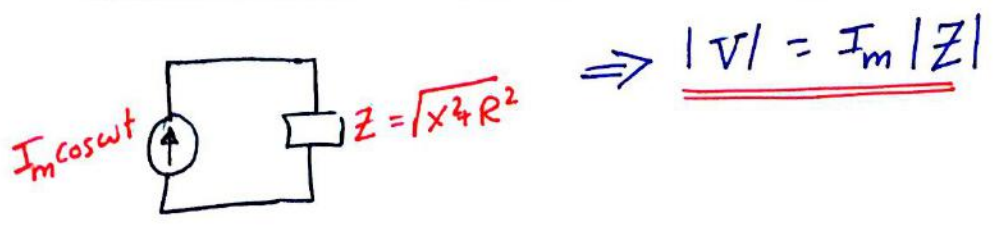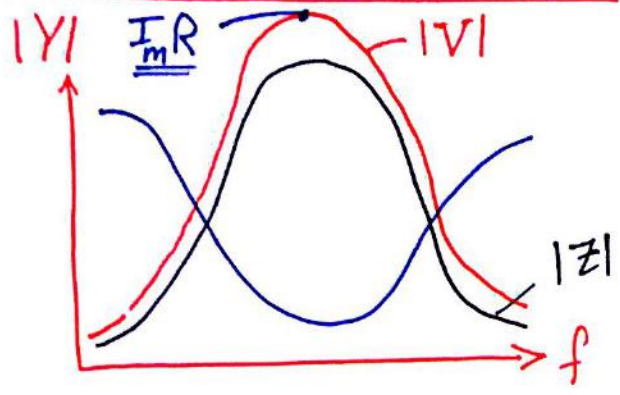

* At parallel Resonance: the voltage is maximum.

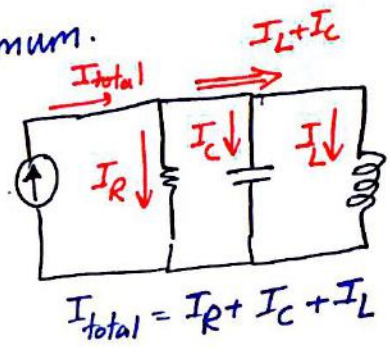* There is a current in L, C at resonance.
 , But these currents are equal and opposite, They may exceed source current.



$I_{L,0} + I_{C,0} = 0 \Rightarrow |I_{C,0}| = |I_{L,0}|$
 ↳ means @ resonance.


@ resonance
 $I_{total} = I_R$
 pass through R.

$I_{L,0} = \frac{V_0}{j\omega_0 L}$ the voltage @ resonance: $= IR$


$I_{L,0} = \frac{IR}{j\omega_0 L} \dots (1) \Rightarrow I_{C,0} = \frac{V_0}{1/j\omega_0 C} = jIR\omega_0 C \dots (2)$

$I_{C,0} = -I_{L,0}$

Ex. find the readings for each (A)?

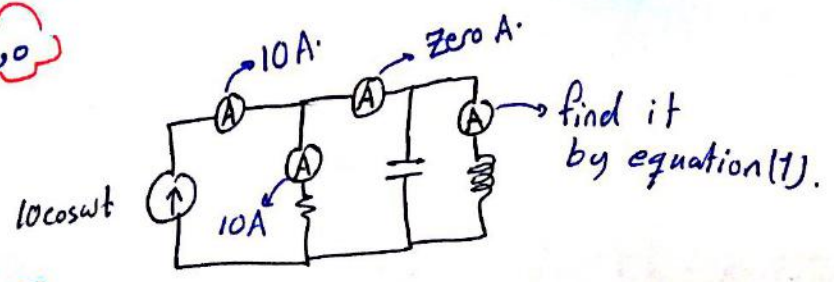

* FM station:

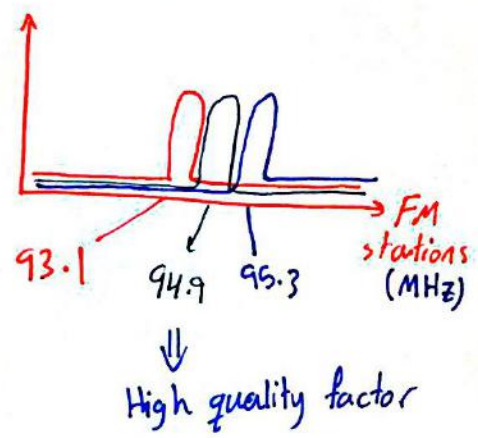

* AM station:



* Quality Factor:

it is a parameter that represents the Bandwidth of the signal.
↳ The region that contains the most of the power of the signal.

Quality factor. $Q \propto \frac{1}{B}$ Bandwidth.

$Q = 2\pi \frac{\text{maximum energy stored}}{\text{Total energy lost per period}}$

$Q = 2\pi \frac{[\omega_L + \omega_C]}{P_R T}$

$W = \int_0^T v(t)i(t) dt$
 $P = \frac{1}{T} \int_0^T v(t)i(t) dt$
 $\Rightarrow W = PT$

* suppose that $i(t) = I_m \cos \omega t$

\Rightarrow @ resonance: $i(t) = I_m \cos \omega_0 t$, $\omega_0 = \frac{1}{\sqrt{LC}}$

$\Rightarrow v(t) = R I_m \cos \omega_0 t$ @ resonance I_m pass just through "R".

**
 $W_C(t) = \frac{1}{2} C V^2 = \frac{1}{2} C \times R^2 I_m^2 \cos^2 \omega_0 t$; $\int v_L dt = \frac{R I_m \sin \omega_0 t}{\omega_0}$
 $W_L(t) = \frac{1}{2} L i^2 = \frac{1}{2} L \left[\frac{1}{L} \int v_L dt \right]^2$
remember: $i_L = \frac{1}{L} \int v_L dt$ $\Rightarrow = \frac{1}{2} \frac{R^2 I_m^2 \sin^2 \omega_0 t}{L \omega_0^2}$

\Rightarrow where $\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \omega^2 = \frac{1}{LC}$

so $W_L(t) = \frac{1}{2} \frac{CR^2 I_m^2 \sin^2 \omega_0 t}{1}$

$\Rightarrow W_C(t) + W_L(t) = \frac{1}{2} CR^2 I_m^2 [\sin^2 \omega_0 t + \cos^2 \omega_0 t]$
 $= \frac{1}{2} CR^2 I_m^2$


also $P_R = \frac{1}{2} I_m^2 R \Rightarrow P_{RT} = \frac{1}{2} I_m^2 R T_0 = \frac{1}{2} \frac{I_m^2 R}{f_0}$

Now: $Q = 2\pi \frac{\frac{1}{2} CR^2 I_m^2}{\frac{1}{2} I_m^2 R \frac{1}{f_0}} = \underline{CR\omega_0} = \frac{2\pi f_0 RC}{\frac{1}{\sqrt{LC}}} = R\sqrt{\frac{C}{L}}$
 $= \frac{R}{X_{C,0}} = \frac{R}{X_{L,0}}$

$Q = \omega_0 CR$
 $= R\sqrt{C/L}$
 $= R/X_{C,0}$
 $= R/X_{L,0}$

* * *

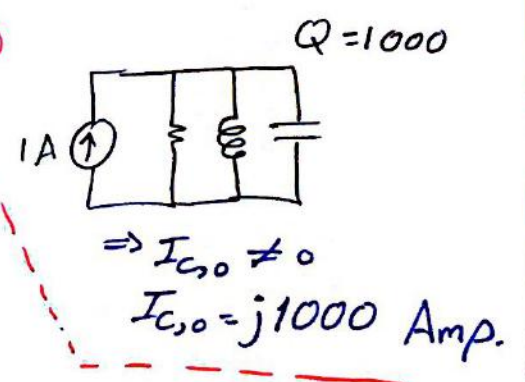* $I_{C,0} = -I_{L,0} = \underbrace{j\omega_0 CR I}_{Q} = jQ_0 I$



ex. Parallel RLC ckt with $L=2\text{mH}$,
 $Q_0=5$, $C=10\text{nF}$ find R & admittance
 at $\omega_0, 0.9\omega_0, 1.1\omega_0$?

Solution:

$Q = R\sqrt{\frac{C}{L}}$
 $\Rightarrow R = Q\sqrt{\frac{L}{C}}$
 $= 5 \sqrt{\frac{2 \times 10^{-3}}{10 \times 10^{-9}}}$

so $R = 2.236 \text{ K}\Omega$


$Y(\omega) = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$

@ $0.9\omega_0$: $0.9\omega_0 = 0.9 \times 223.6 \text{K}$

$\omega_0 = \frac{1}{\sqrt{LC}} = 223.6 \text{K rad/s.}$



$Y(0.9\omega_0) = \frac{1}{2.236 \times 10^3} + j \times 0.9 \times 223.6 \times 10^3 \times 10^{-8} + \frac{1}{j \times 0.9 \times \omega_0 \times 2 \times 10^{-3}}$

$|Y(0.9\omega_0)| = 6.504 \times 10^{-4} \text{ S}$


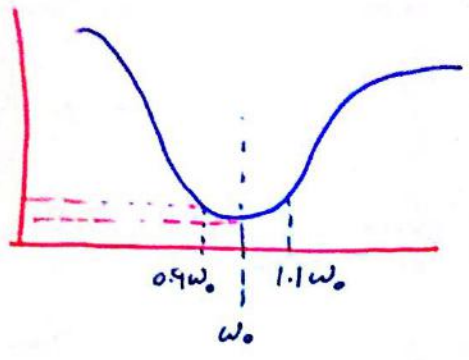


@ ω_0 : $Y(\omega_0) = \frac{1}{R}$
 $|Y(\omega_0)| = 4.472 \times 10^{-4}$

@ $1.1\omega_0$:
 $|Y(1.1\omega_0)| = 6.182 \times 10^{-4}$

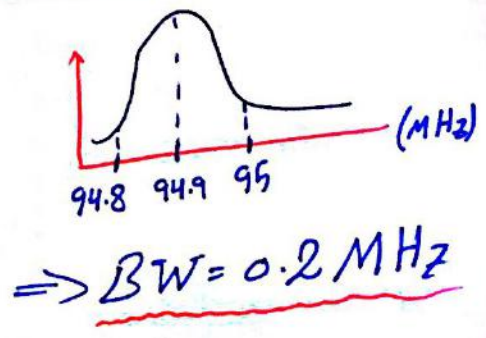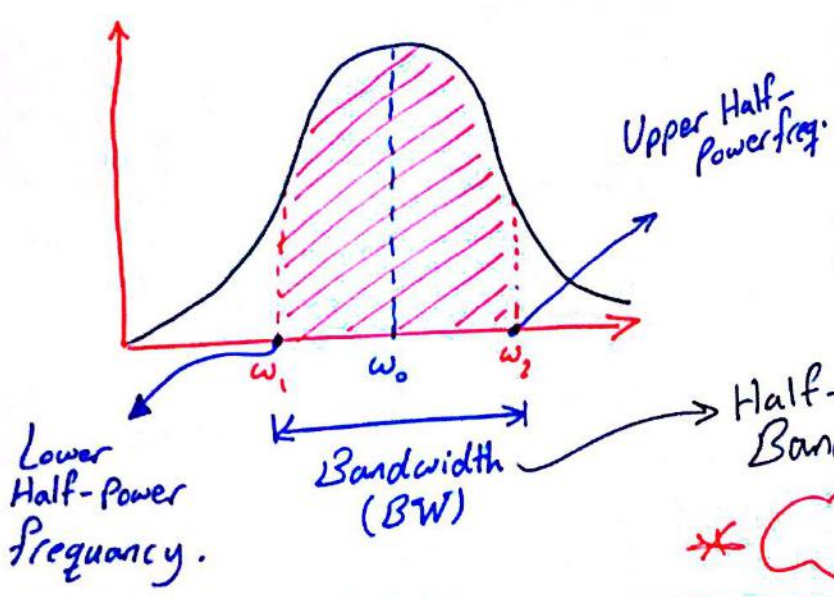

$BW = \omega_2 - \omega_1$

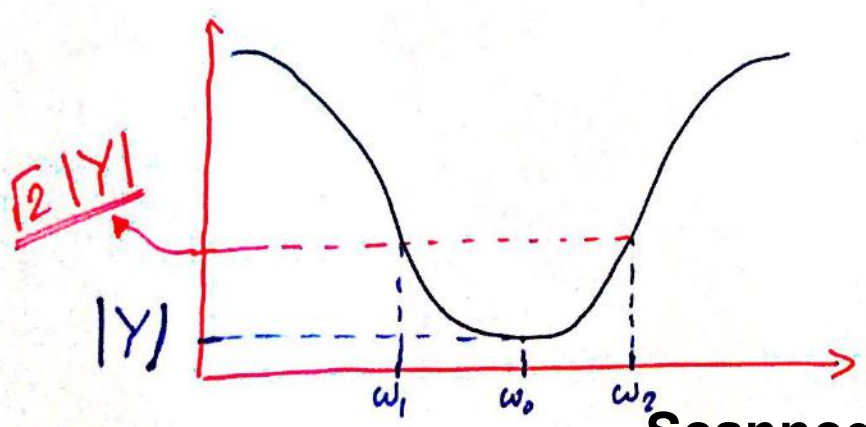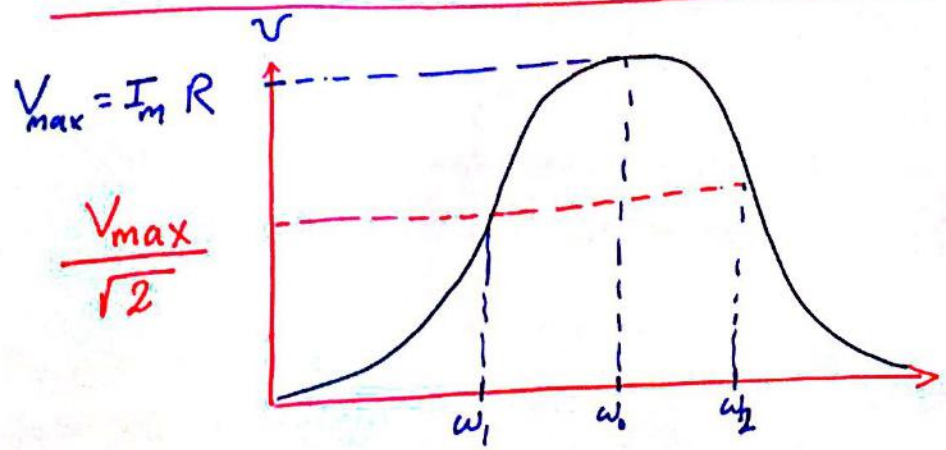

$Y = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$
 $Y(\omega_0) = \frac{1}{R}$
 $Y(\omega_1) = \sqrt{2} \left(\frac{1}{R} \right)$

6

$$Y(\omega_1) = \sqrt{2} \left(\frac{1}{R} \right) = \frac{1}{R} \sqrt{1+1}$$

$$Y = \frac{1}{R} + j\omega C + \frac{1}{j\omega L} \quad \text{use } Q_0 = \omega_0 RC$$

$$\rightarrow Y = \frac{1}{R} + j \frac{1}{R} \left[\frac{\omega \omega_0 CR}{\omega_0} - \frac{\omega_0 R}{\omega \omega_0 L} \right]$$

$$\Rightarrow Y = \frac{1}{R} + j \frac{Q_0}{R} \left[\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right] \quad \text{where: } |Y(\omega_1)| = \sqrt{2} |Y(\omega_0)| = \sqrt{2} \frac{1}{R}$$

$$|Y(\omega_1)| = \sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{Q_0}{R}\right)^2 \left[\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right]^2} = \sqrt{2} \frac{1}{R}$$

$$\Rightarrow \frac{1}{R} \sqrt{1 + Q_0^2 \left[\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right]^2} = \sqrt{2} \frac{1}{R}$$

$$\text{so } Q_0^2 \left[\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right]^2 = 1 \Rightarrow \text{we have: } \begin{cases} Q_0 \left(\frac{\omega_1}{\omega_0} - \frac{\omega_0}{\omega_1}\right) = 1 \\ \text{OR } Q_0 \left(\frac{\omega_2}{\omega_0} - \frac{\omega_0}{\omega_2}\right) = -1 \end{cases}$$

⇒ After simplify:

$$\omega_1 = \omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0}\right)^2} - \frac{1}{2Q_0} \right]$$
$$\omega_2 = \omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0}\right)^2} + \frac{1}{2Q_0} \right]$$

** These two expressions could take very long time to calculate ω_1 & ω_2 so be sure that $Q_0 < 5$ before use them.

⇒ from equations of ω_1 & ω_2 :

$$\text{Bandwidth: } \beta = \omega_2 - \omega_1 = 2\omega_0 * \frac{1}{2Q_0} = \frac{\omega_0}{Q_0} \Rightarrow \boxed{\beta = \frac{\omega_0}{Q_0}}$$

also we could derive that:

$$\boxed{\omega_0 = \sqrt{\omega_1 \omega_2}}$$

* Approximations for High Q_0 cKts [$Q_0 \geq 5$]:

for example take $Q_0 = 5$

$$\sqrt{1 + \left(\frac{1}{10}\right)^2} = \sqrt{1 + 0.01} \approx 1$$

so:

$$\omega_1 = \omega_0 \left[1 - \frac{1}{2Q_0}\right]$$

$$\omega_2 = \omega_0 \left[1 + \frac{1}{2Q_0}\right]$$

$$\Rightarrow \omega_1 = \omega_0 - \frac{\omega_0}{2Q_0} \rightarrow \beta$$

$$\Rightarrow \omega_1 = \omega_0 - \frac{1}{2} \beta, \quad \omega_2 = \omega_0 + \frac{1}{2} \beta, \quad \omega_0 = \frac{1}{2} [\omega_1 + \omega_2]$$

* Approximate Admittance:

$$Y = \frac{1}{R} [1 + jN]$$


N : is the number of Half-Band width off response.

$$N = \frac{\omega - \omega_0}{\frac{1}{2} \beta}$$

ex.

if $\omega_1 = 950$ rad/s
 $\omega_2 = 1050$ rad/s

find N @ $\omega = 1300$ rad/sec?

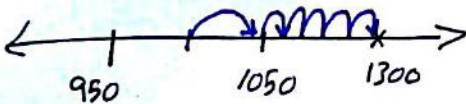

$$\Rightarrow \beta = 100 \text{ rad/sec.}$$


$$\omega_0 = 1000 \text{ rad/sec}$$

$$N = \frac{1300 - 1000}{\frac{1}{2} * 100} = 6 \Rightarrow \boxed{N=6}$$

ex.

if $\omega_0 = 600$ rad/sec.
 $\beta = 50$ rad/sec.

find N @ $\omega = 675$ rad/sec?

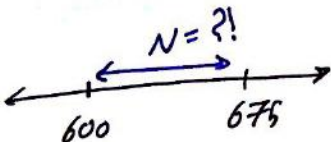

$$N = \frac{\omega - \omega_0}{\frac{1}{2} \beta} = \frac{675 - 600}{25}$$

$$= \frac{75}{25} \Rightarrow \boxed{N=3}$$

also N @ $\omega = 660$ rad/sec:

$$N = \frac{660 - 600}{25} = \frac{12}{5} \Rightarrow \boxed{N=2.4}$$

Ex. Parallel RLC ckt with $R = 40k\Omega$, $L = 1H$, $C = \frac{1}{64}\mu F$

- ① Find the locations of the two Half power frequencies.
- ② Find the approximate value for admittance @ $\omega = 8200$ rad/sec.

Solution:

① * Always the first step find $Q_0 \Rightarrow$ To know which expressions of ω_1 & ω_2 you will use.

$$Q_0 = \omega_0 RC$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 8k \text{ rad/sec.} \Rightarrow Q_0 = 8 \times 10^3 \times 40 \times 10^3 \times \frac{1}{64} \times 10^{-6}$$

$$\Rightarrow Q_0 = 5 \text{ since } Q_0 \geq 5$$

method (1):

$$\omega_1 = \omega_0 \left(1 - \frac{1}{2Q_0}\right) = 7200 \text{ rad/sec}$$

$$\omega_2 = \omega_0 \left(1 + \frac{1}{2Q_0}\right) = 8800 \text{ rad/sec.}$$

use approximation @ resonance.

[Approximate relations]

method (2):

$$\beta = \frac{\omega_0}{Q_0} = 1600 \text{ rad/sec.}$$

$$\omega_1 = \omega_0 - \frac{1}{2}\beta$$

$$\omega_2 = \omega_0 + \frac{1}{2}\beta$$

$$\omega_1 = 7200 \text{ rad/sec.}$$

$$\omega_2 = 8800 \text{ rad/sec.}$$

② $Y(\omega) = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$

$$Y(8200) = 25.75 \angle 13.9^\circ \mu S$$


* Approximate Y : $Y = \frac{1}{R} [1 + jN]$

we need N :

$$N = \frac{\omega - \omega_0}{\frac{1}{2}\beta} = \frac{8200 - 8000}{800} = 0.25$$

$$\Rightarrow Y = \frac{1}{40k} [1 + j(0.25)] = 25.77 \angle 14.04^\circ \mu S$$

Series RLC Resonance:

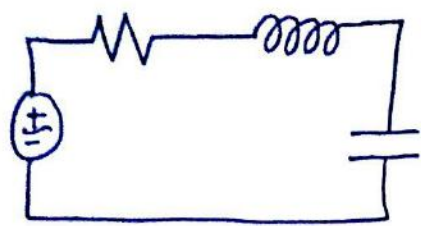

$$\Rightarrow Z_{eq} = R + j\omega L + \frac{1}{j\omega C}$$


@ resonance $Z_{eq} = R$:

so $0 = j\omega L + \frac{1}{j\omega C}$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$
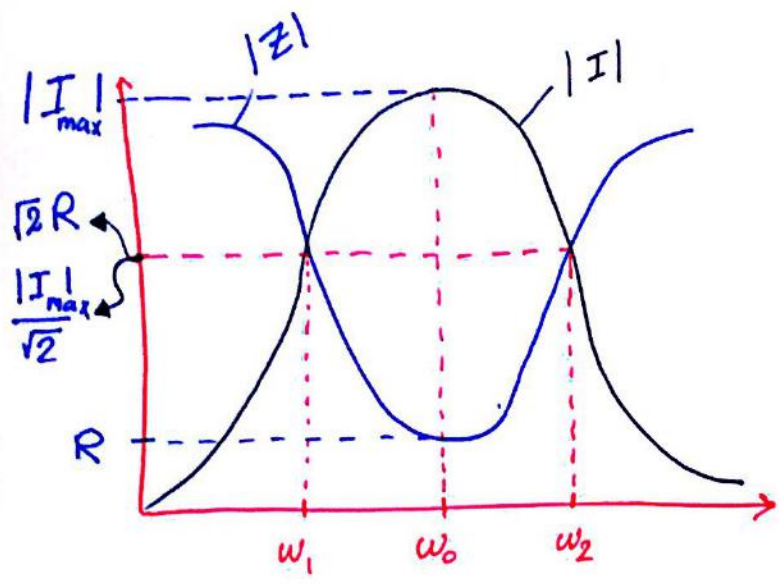
$$\beta = \omega_2 - \omega_1 = \frac{\omega_0}{Q_0}$$



$$\Rightarrow |Z(\omega_0)| = R$$

$$|Z(\omega_1)| = \sqrt{2} R$$

$$|Z(\omega_2)| = \sqrt{2} R$$

*As the same we did to parallel resonance
Do the same you can reach that:

$$Q_0 = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC} = \frac{\omega_0}{\beta}$$

ALSO:

$$\omega_1 = \omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0}\right)^2} - \frac{1}{2Q_0} \right], \quad \omega_2 = \omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0}\right)^2} + \frac{1}{2Q_0} \right]$$

⇒ For ckts with High Q_0 [$Q_0 \geq 5$]:

$$\omega_1 \approx \omega_0 - \frac{1}{2} \beta$$

$$\omega_2 \approx \omega_0 + \frac{1}{2} \beta$$

$$Z_{eq} = R(1 + jN)$$

where: $N = \frac{\omega - \omega_0}{\frac{1}{2} \beta}$

Approximate impedance.

* Note: (1) Always if ω is unknown it means that the freq. is changing (resonance subject).

(2) Always the Ammeter reads RMS value.

(Ex.) Given $V_s = 100 \cos \omega t$ mV, for series RLC ckt with $R = 10 \Omega$, $C = 200 \text{ nF}$, $L = 2 \text{ mH}$.

① Calculate $|I|$ if $\omega = 48 \text{ K rad/sec}$.

② Calculate the approximate value of $|I|$ @ $\omega = 48 \text{ K rad/sec}$.

Solution:

① $|I| = \frac{|V|}{|Z_{eq}|} \Rightarrow$ we need Z_{eq} :

$$Z_{eq} = R + j\omega L + \frac{1}{j\omega C}$$

$$= 10 + j * 48 \text{ K} * 2 \text{ m} + \frac{1}{j * 48 \text{ K} * 200 \text{ n}}$$

$$Z_{eq} = 12.91 \angle -39.24^\circ$$

$$|I| = \frac{100 \text{ m}}{12.91}$$

$$\Rightarrow |I| = 7.746 \text{ mA}$$

② $\omega_0 = \frac{1}{\sqrt{LC}} = 50 \text{ K rad/sec}$.

find Q_0 to know if it is allow to use approximation:

$$Q_0 = \frac{\omega_0 L}{R} = 10 (\geq 5) \Rightarrow \text{use approximation.}$$

$$\Rightarrow \beta = \frac{\omega_0}{Q_0} = 5 \text{ K rad/sec}$$


$$\Rightarrow \text{find } N: N = \frac{\omega - \omega_0}{\frac{1}{2} \beta} = -0.8$$

$$Z_{eq} = R(1 + jN)$$


$$\Rightarrow Z_{eq} = 12.81 \angle -38.66^\circ$$

$$\Rightarrow |I| = \frac{|V|}{|Z_{eq}|} \Rightarrow |I| = 7.806 \text{ mA}$$

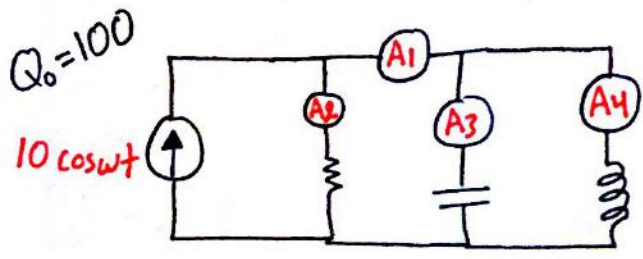ex. Find the Ammeters reading in the circuit shown in figure(1) & the Voltmeters reading in the circuit shown in figure(2):



figure(1).

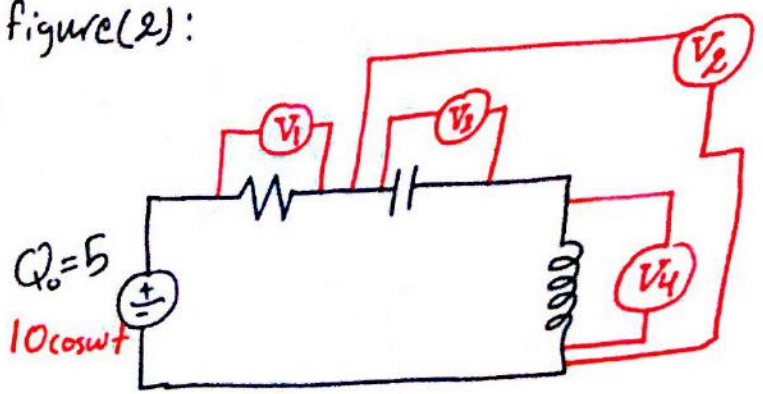

figure(2).

@ resonance:

$A_1 = 0$
 $A_2 = \frac{10}{\sqrt{2}} \text{ Arms or } A_2 = 10 \text{ A. (peak)}$
 $A_3 = j I Q_0 = j 1000 \text{ A} \Rightarrow |A_3| = 1000 \text{ A.}$
 $A_4 = \frac{I Q_0}{j} = -j 1000 \text{ A} \Rightarrow |A_4| = 1000 \text{ A}$

@ resonance:

$V_1 \text{ (peak)} = 10 \text{ volt.}$
 $V_2 = \text{Zero.}$
 $V_3 = j Q_0 V = j 50 \text{ volt.}$
 $\Rightarrow |V_3| = 50 \text{ volt.}$
 $V_4 = \frac{Q_0 V}{j} = -j 50 \text{ volt.}$
 $\Rightarrow |V_4| = 50 \text{ volt.}$

* A summary for series RLC & Parallel RLC resonance:

=> The common relations for both:

$\omega_0 = \frac{1}{\sqrt{LC}}$
 $f_0 = \frac{1}{2\pi\sqrt{LC}}$
 $\omega_0 = \sqrt{\omega_1 \omega_2}$
 $\omega_{1/2} = \omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0}\right)^2} \pm \frac{1}{2Q_0} \right]$
 $\beta = \frac{\omega_0}{Q_0}$

* Approximate relations:

$\omega_{1/2} = \omega_0 \pm \frac{1}{2} \beta$
 $\omega_0 = \frac{1}{2} (\omega_1 + \omega_2)$
 $N = \frac{\omega - \omega_0}{\frac{1}{2} \beta}$

Parallel RLC Resonance.

$$Q_0 = \omega_0 RC = \frac{R}{\omega_0 L}$$

$$|I_L(\omega_0)| = |I_C(\omega_0)| = Q_0 I$$

$$Y = \frac{1}{R} \left[1 + jQ_0 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right]$$

$$Y = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$$

* Approximate:

$$Y = \frac{1}{R} (1 + jN)$$

@ Resonance:

- * V has maximum.
- * Z has maximum.
- * Y has minimum.

Series RLC Resonance.

$$Q_0 = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

$$|V_L(\omega_0)| = |V_C(\omega_0)| = Q_0 V$$

$$Z = R \left[1 + jQ_0 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right]$$

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

* Approximate:


$$Z = R (1 + jN)$$

@ Resonance:

- * I has maximum.
- * Y has maximum.
- * Z has minimum.

EX. For the series resonance ckt shown:

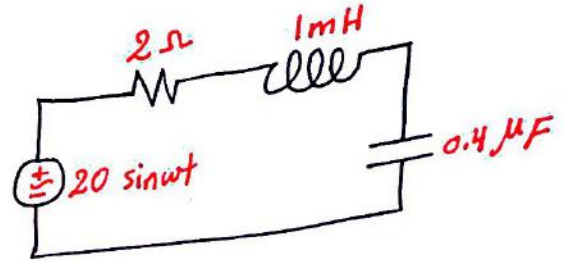- ① Find the resonance frequency & Half-power frequencies.
- ② Find Q_0 & β .
- ③ Find the Amplitude of the current @ $\omega_0, \omega_1, \omega_2$.



Solution:

① $\omega_0 = \frac{1}{\sqrt{LC}} = 50 \text{ Krad/sec.}$

⇒ As always find Q_0 at first:

$Q_0 = \frac{1}{\omega_0 RC} = \frac{\omega_0 L}{R} = 25 \geq 5 \Rightarrow$ so use approximations.

⇒ $\beta = \frac{\omega_0}{Q_0} = 2 \text{ Krad/sec.} \Rightarrow$

$\omega_1 = \omega_0 - \frac{1}{2}\beta \rightarrow \omega_1 = 49 \text{ Krad/sec.}$
 $\omega_2 = \omega_0 + \frac{1}{2}\beta \rightarrow \omega_2 = 51 \text{ Krad/sec.}$

② As found in part (1)

$Q_0 = 25$
 $\beta = 2 \text{ Krad/sec.}$

③ $|I(\omega_0)| = \frac{20}{2} = 10 \text{ Amp.}$

$|I(\omega_1)| = |I(\omega_2)| = \frac{10}{\sqrt{2}} \text{ Amp.}$

If he asked to find the angle:
 it would be the same angle of voltage since @ resonance I & V are in phase.


so $\theta_I = \theta_V = 0$

↓
If he asked about the angles:

⇒ you have to find Z:

$Z = R(1 + jN) \Rightarrow N = \frac{51 - 50}{1} = 1$
 $N = \frac{49 - 50}{1} = -1$

so $Z = 2 \pm j2$

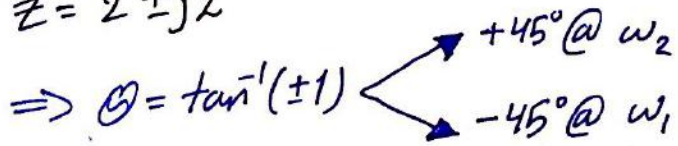

Warning: $|I(\omega)| = \frac{10}{\sqrt{2}}$ it is Not a RMS value
 \Rightarrow it is peak value.

ex. For the shown ckt, Given that: $R = 8k\Omega$
 $L = 0.2mH$
 $C = 8\mu F$

- ① Find $\omega_0, Q, \beta, \omega_1, \omega_2$.
- ② Find the power dissipated @ $\omega_0, \omega_1, \omega_2$.


Solution:

① $\omega_0 = \frac{1}{\sqrt{LC}} = 25 \text{ Krad/sec}$

$Q_0 = \omega_0 RC = 1600$


$\beta = \frac{\omega_0}{Q_0} = 15.625 \text{ rad/sec}$

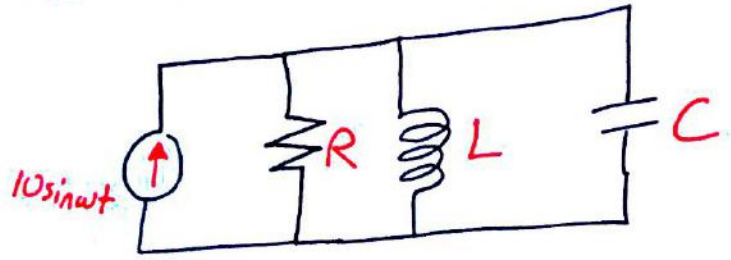$\omega_1 = \omega_0 - \frac{\beta}{2} \rightarrow \omega_1 = 24.992 \text{ Krad/sec}$
 $\omega_2 = \omega_0 + \frac{\beta}{2} \rightarrow \omega_2 = 25.008 \text{ Krad/sec}$



***Note that:**

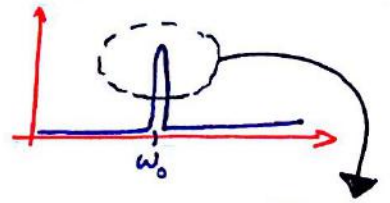15.625 very small value with respect to 25K so the figure is:




This is called: **Highly Selective Circuit.**

② $P_R(\omega_0) = \frac{1}{2} I^2 R = 400 \text{ KW}$

$P_R(\omega_1)$
 $P_R(\omega_2)$ \Rightarrow They will be half of $P_R(\omega_0)$

$\Rightarrow P_R(\omega_1) = P_R(\omega_2) = 200 \text{ KW}$

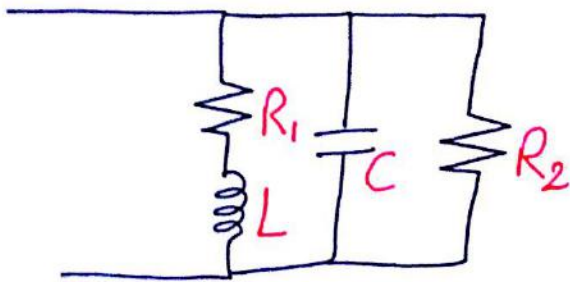Other Resonance Forms [Not series, Not parallel]:



Key

$$\text{Imag}\{Y\} = 0$$

OR $\text{Imag}\{Z\} = 0$

⇒ Here it is easier to deal with Y.

$$\Rightarrow Y = \frac{1}{j\omega L + R_1} + j\omega C + \frac{1}{R_2}$$

→ * $\frac{(R_1 + j\omega L)}{(R_1 - j\omega L)}$ equal zero @ resonance.

$$Y = \frac{1}{R_2} + j\omega C + \frac{R_1 - j\omega L}{R_1^2 + (\omega L)^2}$$

$$\text{Imag}\{Y\} = 0 @ \omega_0 \Rightarrow j\omega_0 C - \frac{j\omega_0 L}{R_1^2 + (\omega_0 L)^2} = 0$$

$$\text{so } C = \frac{L}{R_1^2 + (\omega_0 L)^2} \Rightarrow (\omega_0 L)^2 = \frac{L}{C} - R_1^2$$
$$\Rightarrow \omega_0^2 = \frac{1}{LC} - \left(\frac{R_1}{L}\right)^2$$

$$\Rightarrow \omega_0 = \sqrt{\frac{1}{LC} - \left(\frac{R_1}{L}\right)^2}$$

* * Now you can derive ^{ω₀ to} any ckt: All the idea build on the KEY and you just choose what is the best using Y or Z depending on the shape of the ckt.

(ex.) Determine the resonance frequency for the given ckt:


(16)

solution:

As derived before

$$\omega_0 = \sqrt{\frac{1}{LC} - \left(\frac{R_1}{L}\right)^2}$$
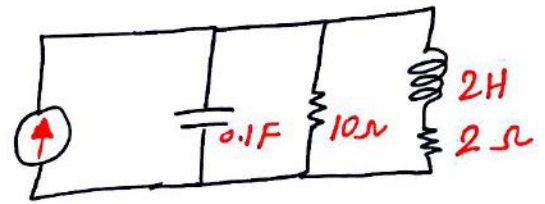
$$= \sqrt{\frac{1}{2 * 0.1} - \left(\frac{2}{2}\right)^2} \Rightarrow \boxed{\omega_0 = 2 \text{ rad/sec.}}$$



Frequency Response:

⇒ It is a relation between input & output at different frequencies.




OR *any relation between in & out.

* Transfer function is $\frac{V_{out}}{V_{in}}$.

(ex.) Find the voltage transfer function for the shown ckt:

$$V_{out} = I * \frac{1}{j\omega C}$$

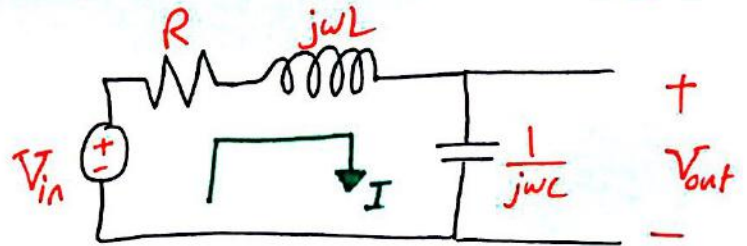
$$V_{in} = I \left(R + j\omega L + \frac{1}{j\omega C} \right)$$



$$H_V(\omega) = \frac{V_{out}}{V_{in}} = \frac{I * \frac{1}{j\omega C}}{I * \left(R + j\omega L + \frac{1}{j\omega C} \right)}$$

$$* \frac{j\omega C}{j\omega C}$$
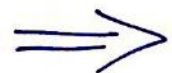
$$= \frac{1}{j\omega C R + (1 - CL\omega^2)}$$




Now:

$$|H_V(\omega)| = \frac{1}{\sqrt{(\omega CR)^2 + (1 - CL\omega^2)^2}}$$

↳ we want to draw this function

it is similar to $f(x) = \frac{1}{\sqrt{x^2 + (1-x^2)^2}}$

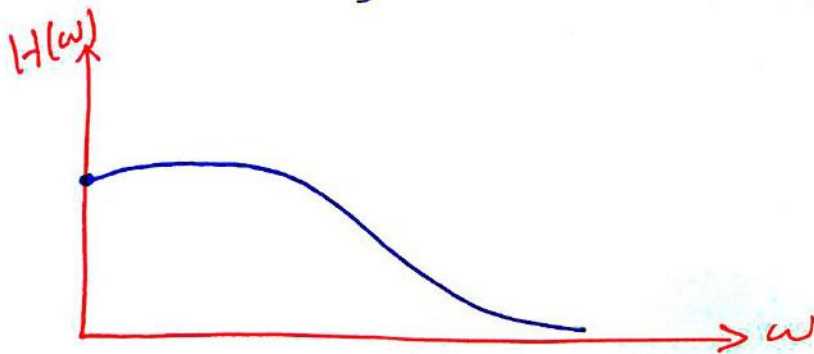By substituting some values take @ $x=0$ & $x=\infty$




Ⓧ Obtain the T.F V_o/V_s of the RL ckt:

Solution:

$$H_V(\omega) = \frac{V_o}{V_s}$$

$$V_o = I * j\omega L$$


$$V_s = I * (R + j\omega L)$$

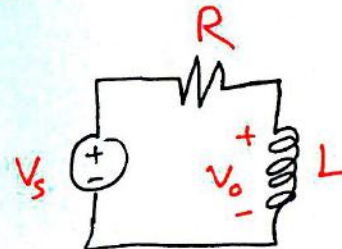

$$\rightarrow = \frac{I j\omega L}{I (R + j\omega L)}$$

$$|H_V(\omega)| = \frac{\omega L}{\sqrt{R^2 + (\omega L)^2}}$$

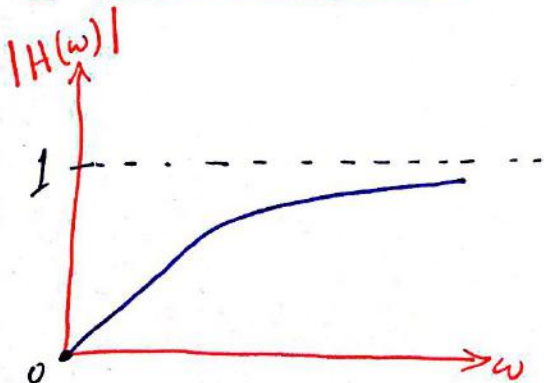To Draw it: $H(0) = \text{Zero}$
 $H(\infty) = 1$



To find the angle:



$$H_V(\omega) = \frac{j\omega L}{R + j\omega L} * \frac{R - j\omega L}{R - j\omega L}$$

$$= \frac{(\omega L)^2 + jR\omega L}{R^2 + (\omega L)^2}$$


$$\angle H(\omega) = \tan^{-1} \left(\frac{\text{Im}}{\text{Re}} \right) = \tan^{-1} \left(\frac{R}{\omega L} \right)$$

✖ Filters: [frequency selective circuit]

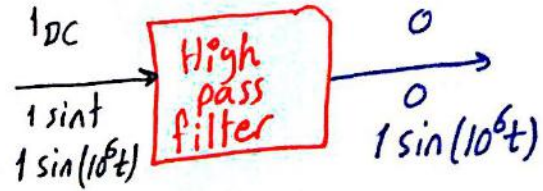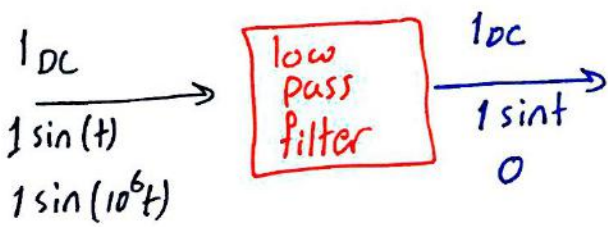
↳ It is a ckt/device that is designed to pass signals with desired frequency & reject others.




** Types: [Passive Filters]

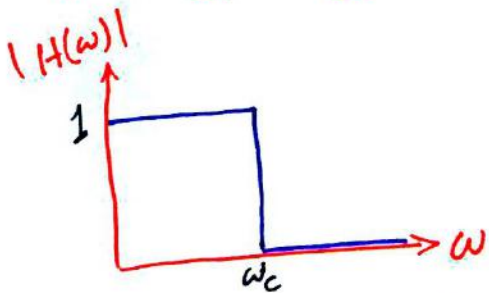


"Low pass Filter"

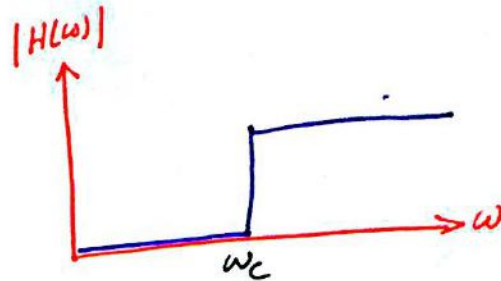

"High pass filter"


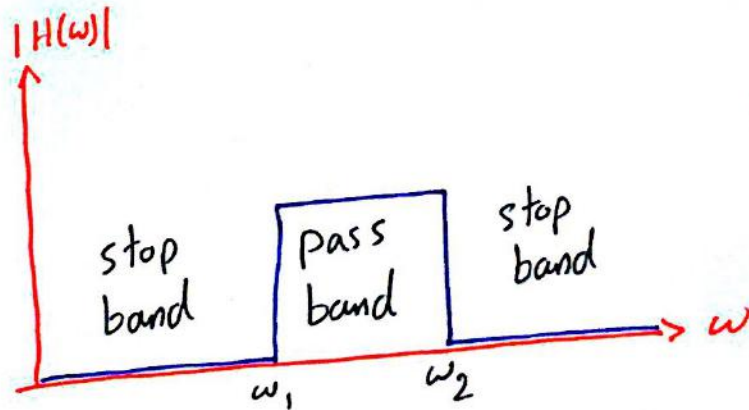


"Band pass filter"

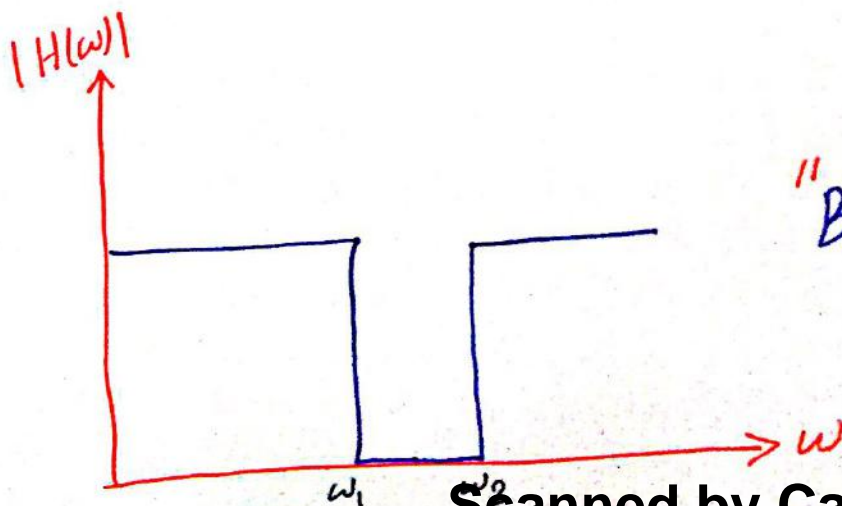

"Band stop filter"

* Low Pass Filter:

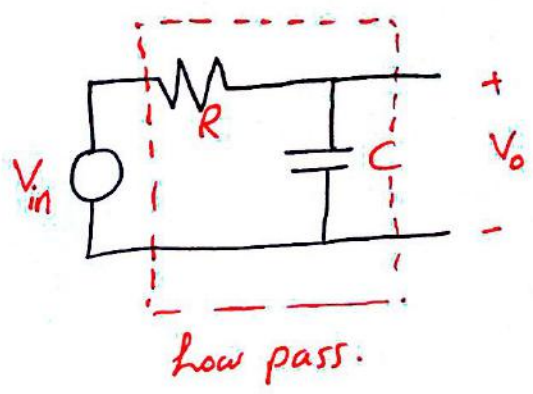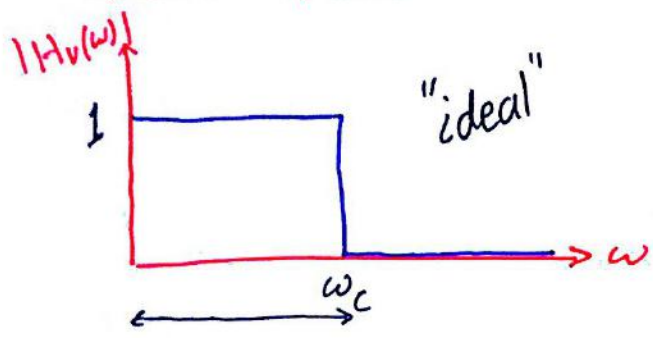


⇒ The output of an RC ckt is taken off the capacitor.

$$H_V(\omega) = \frac{V_{out}}{V_{in}} = \frac{I * \frac{1}{j\omega C}}{I * (\frac{1}{j\omega C} + R)} = \frac{1}{1 + j\omega CR}$$

$$\Rightarrow |H_V(\omega)| = \frac{1}{\sqrt{1 + (\omega CR)^2}}$$

→ $H(0) = 1$
 $H(\infty) = 0$

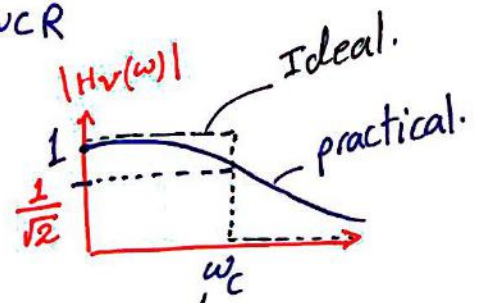

called:
"Cutoff frequency"

we know:

$$|H_V(\omega_c)| = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (\omega_c RC)^2}}$$

solving:

$$\Rightarrow \omega_c = \frac{1}{RC} \text{ rad/sec.}$$


if we want $\omega_c = 1000 \text{ rad/sec}$
we choose: (for ex.)
 $R = 4.7 \text{ K}\Omega$
 $C = 0.2 \mu\text{F}$



$$H_V(\omega) = \frac{R}{R + j\omega L}$$

$$|H_V(\omega)| = \frac{R}{\sqrt{R^2 + (\omega L)^2}}$$

$H(0) = 1$
 $H(\infty) = 0$

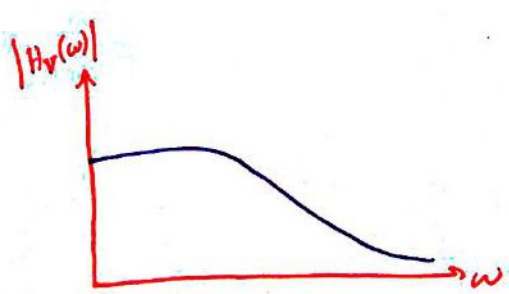


⇒ it is also a low pass filter.

⇒ Now for the angles:

in the previous RC ckt:

$H_V(\omega) = \frac{1}{1+j\omega RC} \Rightarrow \angle H_V(\omega) = \tan^{-1}(-\omega RC)$

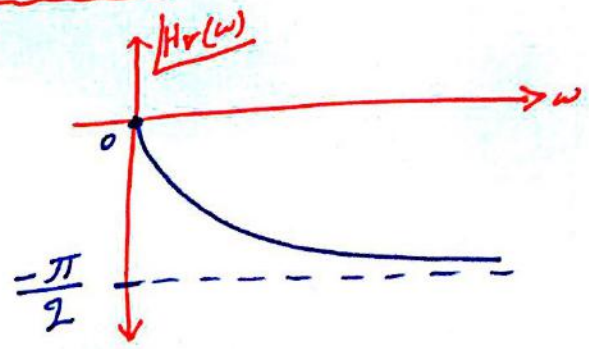$\angle H_V(0) = \text{Zero}$
 $\angle H_V(\infty) = -\frac{\pi}{2}$



in the previous RL ckt:


$H_V(\omega) = \frac{R}{R+j\omega L} \Rightarrow \angle H_V(\omega) = \tan^{-1}(\frac{-\omega L}{R})$

$\angle H_V(0) = 0$
 $\angle H_V(\infty) = -\frac{\pi}{2}$

⇒ it will be like the previous graph.

✘ High Pass Filter:

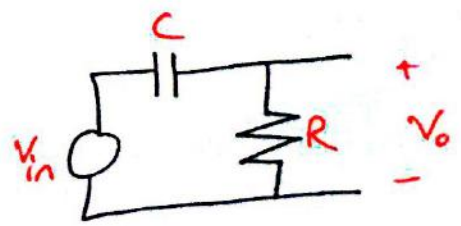
⇒ is one that passes the frequencies above the cutoff frequency.



⇒ RC ckt with output at R.

$H_V(\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$

$|H_V(\omega)| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$

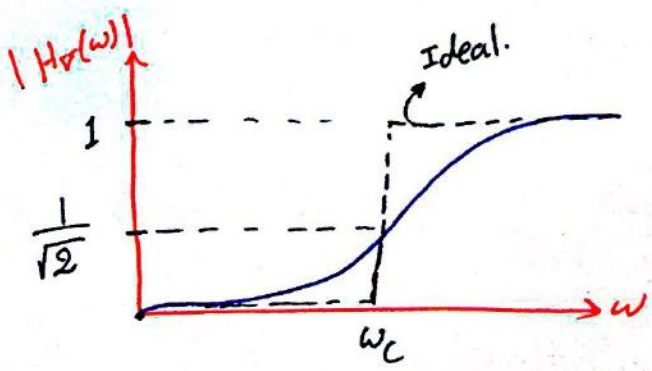


$|H_V(0)| = 0$
 $|H_V(\infty)| = 1$

we have: $|H(\omega_c)| = \frac{1}{\sqrt{2}} \Rightarrow \omega_c = \frac{1}{RC}$ rad/sec.
 "cutoff frequency."

* Another ckt to build High Pass Filter: (RL ckt).



$$H_V(\omega) = \frac{j\omega L}{R + j\omega L}$$

$$|H_V(\omega)| = \frac{\omega L}{\sqrt{R^2 + (\omega L)^2}}$$

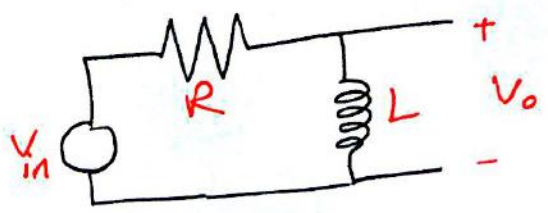

* Band Pass Filter:

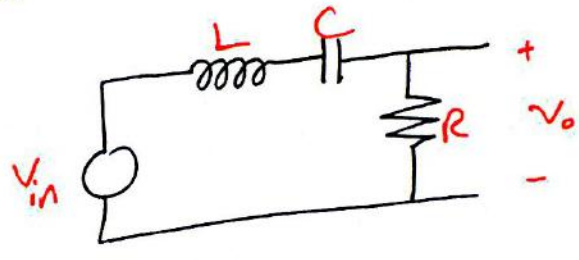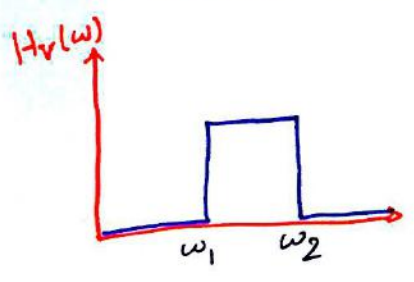
⇒ Series RLC ckt with the output is taken off the resistor.



$$H_V(\omega) = \frac{V_o}{V_{in}} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{j\omega RC}{j\omega RC - \omega^2 LC + 1}$$

$$|H_V(\omega)| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

$H(0) = 0$
 $H(\infty) = 0$

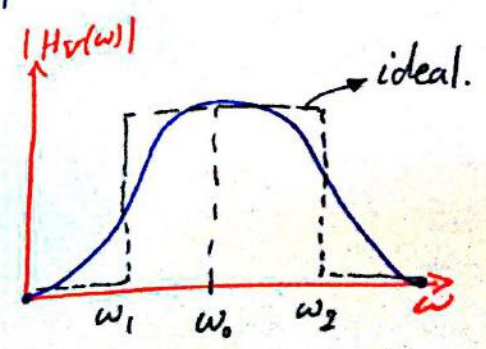

⇒ $\omega_1, \omega_2, \omega_0$: as defined in series resonance:



$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_{1,2} = \omega_0 \left[1 + \left(\frac{1}{2Q_0} \right)^2 \pm \frac{1}{2Q_0} \right]$$

* Band Stop Filter:

⇒ a filter that prevents a band of frequencies between two values (ω_1, ω_2)


⇒ RLC series ckt with output at LC.

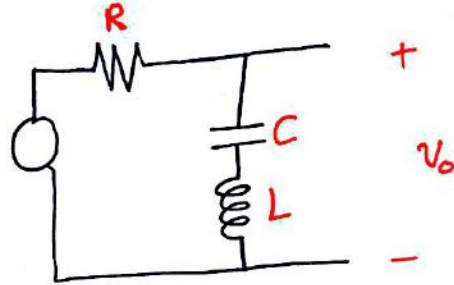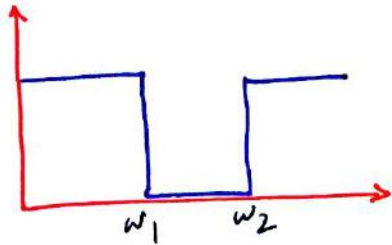

$$H(\omega) = \frac{v_o}{v_{in}} = \frac{j(\omega L - \frac{1}{\omega C})}{R + j(\omega L - \frac{1}{\omega C})}$$

$$|H(\omega)| = \frac{(1 - \omega^2 LC)}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$


$H(0) = 1$
 $H(\infty) = 1$

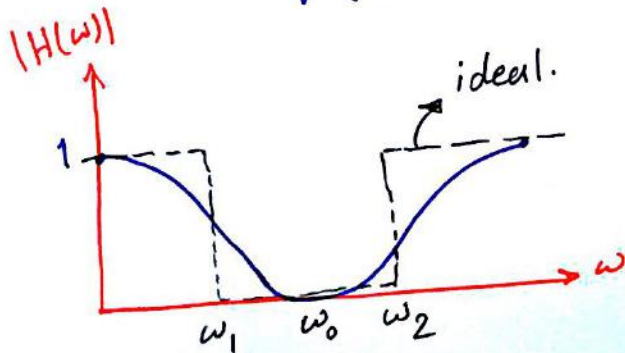

⇒ $\omega_0 = \frac{1}{\sqrt{LC}}$

ex. Determine what type of filter is shown in the figure, what is the corner frequency:

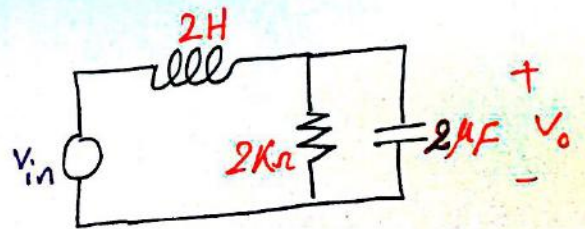solution: $H(\omega) = \frac{v_o}{v_{in}} = \frac{R // \frac{1}{j\omega C}}{R // \frac{1}{j\omega C} + j\omega L}$




$$= \frac{R * \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R / (1 + j\omega RC)}{R / (1 + j\omega RC) + j\omega L} = \frac{R}{- \omega^2 RLC + j\omega L + R}$$

$H(0) = 1$
 $H(\infty) = 0$



$$|H(\omega)| = \frac{R}{\sqrt{(R - \omega^2 RLC)^2 + (\omega L)^2}}$$

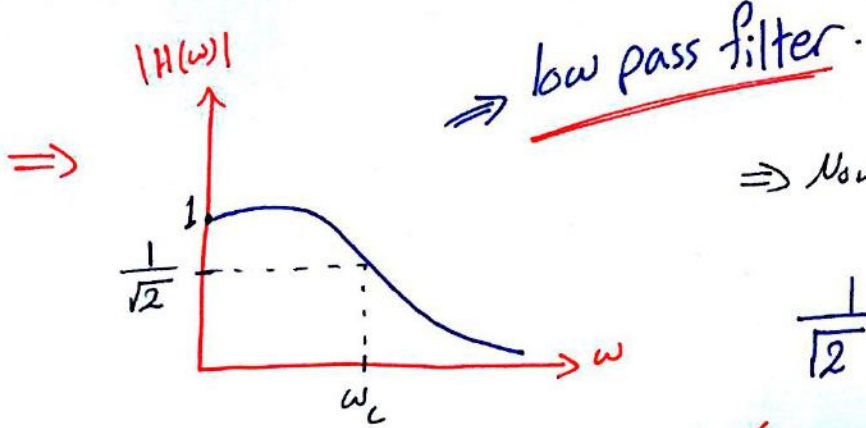

⇒ Now finding the cutoff freq:

$$\frac{1}{\sqrt{2}} = \frac{R}{\sqrt{(R - \omega_c^2 RLC)^2 + (\omega_c L)^2}}$$

↙ solve this equation for ω_c :

⇒ $\omega_c^2 = 0.5509$ or -0.1134



in this course we won't take the negative ω^2 that will give us complex freq.

⇒ $\omega_c = 0.792 \text{ Krad/sec.}$

ex. A Band-Stop Filter is designed to reject a 200 Hz frequency while passing other frequencies. Calculate L & C?

Take $R = 150 \Omega$ & $BW = 100 \text{ Hz.}$

solution:

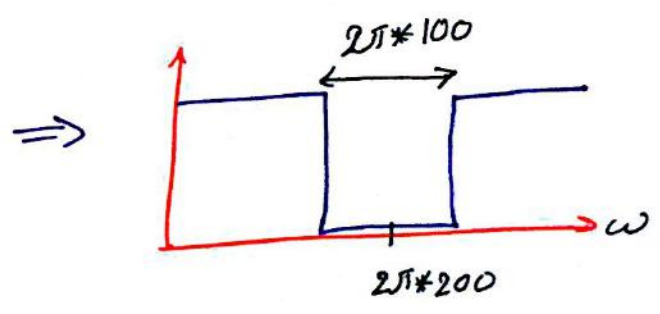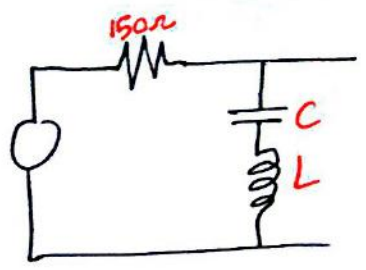

$$\beta = \frac{\omega_0}{Q_0} = \frac{\omega_0}{\frac{\omega_0 L}{R}} = \frac{R}{L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 400\pi$$

⇒ $L = \frac{150}{200\pi} \Rightarrow L = 0.238 \text{ H}$

so $C = 2.65 \mu\text{F}$

ex. Design a high-pass-filter with corner frequency 3 KHz ?

solution:


Assume it is RC ckt:

⇒ $\omega_c = \frac{1}{RC} = 3\text{K} * 2\pi$

we can choose any value and find the other from the equation.


Take $R = 4.7 \text{ K}\Omega$

⇒ $C = 11.29 \text{ nF}$

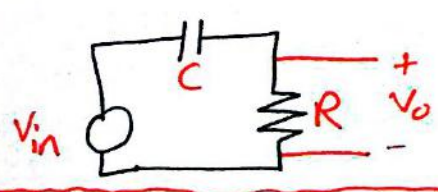

* The Decibel Scale:

(24)

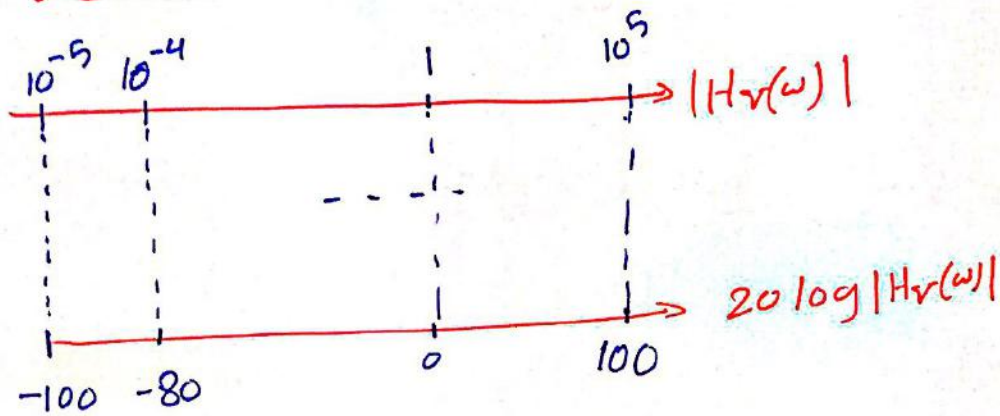

* Bode Plots:

* To Draw $|Hv(\omega)|$

⇒ Approximate, yet accurate, drawing of the logarithmic gain & phase as functions of frequency.

$$* H(\omega) = \frac{N(\omega)}{D(\omega)} = \frac{K (j\omega)^{\pm 1} \left[1 + \frac{j\omega}{Z_1}\right]}{\left[1 + \frac{j\omega}{P_1}\right]} * \Rightarrow \text{general form. (standard form).}$$

where:

K : constant.

$(j\omega)^{\pm 1}$: pole or zero.

$\left[1 + \frac{j\omega}{Z_1}\right]$: zero at Z_1 .

$\left[1 + \frac{j\omega}{P_1}\right]$: pole at P_1 .

(ex.) write $H(\omega)$ in the standard form:


$$H(\omega) = \frac{200 j\omega (j\omega + 50)}{(j\omega + 2)(j\omega + 10)}$$

$$\Rightarrow H(\omega) = \frac{200 * j\omega * 50 \left[1 + \frac{j\omega}{50}\right]}{2 * \left[\frac{j\omega}{2} + 1\right] * 10 * \left[\frac{j\omega}{10} + 1\right]} = \frac{500 * (j\omega) * \left[\frac{j\omega}{50} + 1\right]}{\left[\frac{j\omega}{2} + 1\right] * \left[\frac{j\omega}{10} + 1\right]}$$



****** $H(\omega) = \frac{K(j\omega) \left[1 + \frac{j\omega}{z_1}\right]}{\left[1 + \frac{j\omega}{p_1}\right]}$

$\Rightarrow 20 \log |H(\omega)| = 20 \log |K| + 20 \log |j\omega| + 20 \log \left|1 + \frac{j\omega}{z_1}\right| - 20 \log \left|1 + \frac{j\omega}{p_1}\right|$


* Constant term K:

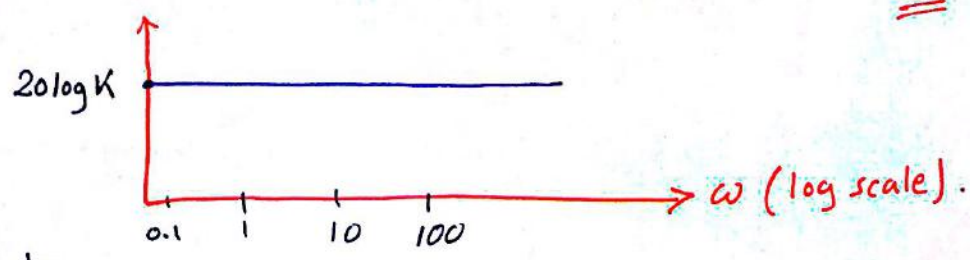


ex. if $H(\omega) = 10$

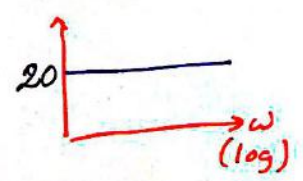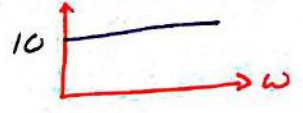

\Rightarrow Angle:

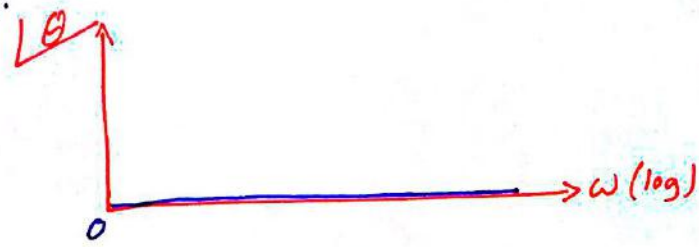


* Zero at Zero $H(\omega) = j\omega$

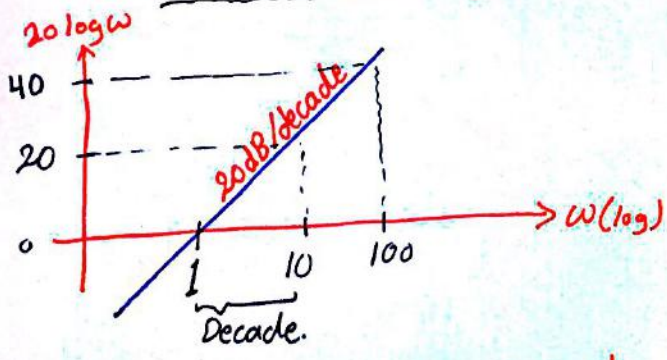


\Rightarrow Angle: $\theta = \tan^{-1}\left(\frac{\omega}{0}\right) = \tan^{-1}(\infty) = \frac{\pi}{2}$



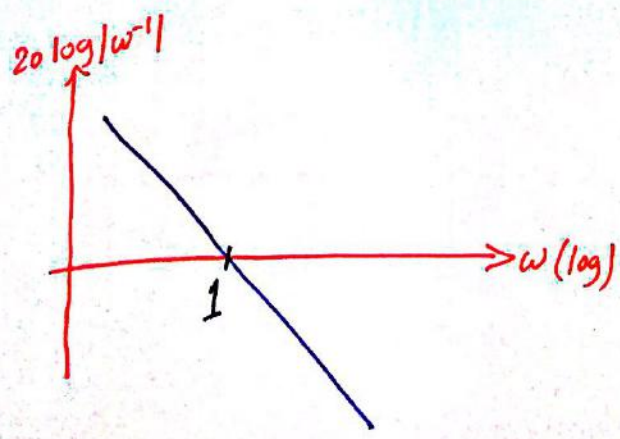* Pole at Zero $H(\omega) = \frac{1}{j\omega}$




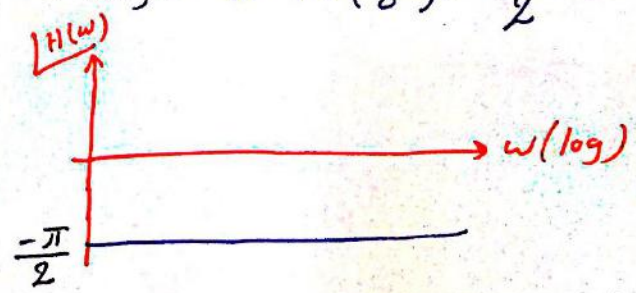\Rightarrow Angle: $\theta = \tan^{-1}\left(\frac{-1}{0}\right) = \frac{-\pi}{2}$




* Simple Zero: $H(\omega) = [1 + \frac{j\omega}{Z_1}]$



$$H(\omega)_{log} = 20 \log \left| 1 + \frac{j\omega}{Z_1} \right| = \begin{cases} 0, & Z_1 \gg \omega \rightarrow \text{imaginary part will be neglected.} \\ 20 \log \frac{\omega}{Z_1}, & \omega \gg Z_1 \rightarrow \text{real part will be neglected.} \end{cases}$$

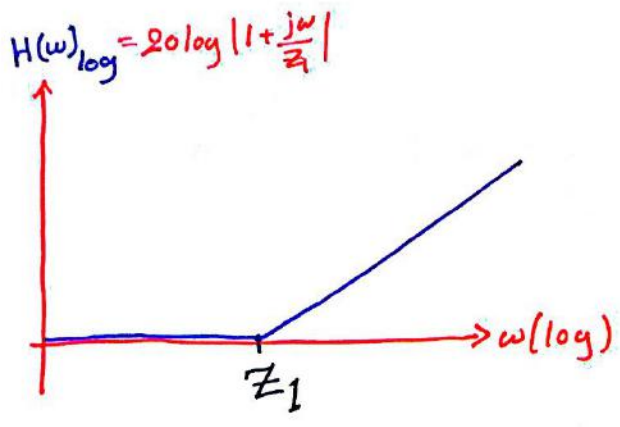

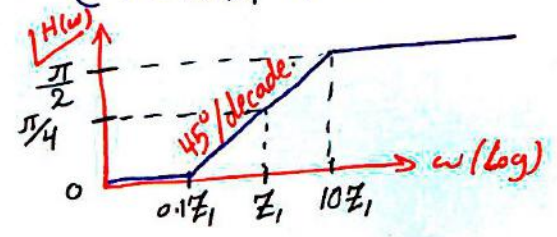⇒ Angle: @ $\omega = 0.1 Z_1 \Rightarrow \theta = 0$
 @ $\omega = Z_1 \Rightarrow \theta = 45^\circ$
 @ $\omega = 10 Z_1 \Rightarrow \theta = 90^\circ$



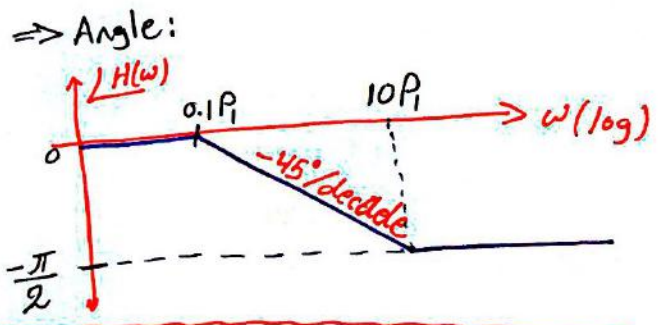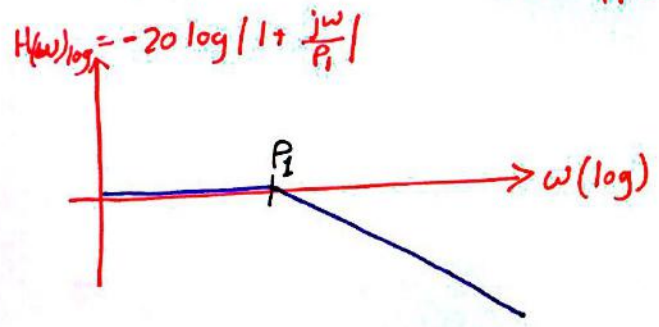* Simple Pole: $H(\omega) = \frac{1}{[1 + \frac{j\omega}{P_1}]}$




(ex.) Construct the Bode Plot for $H(\omega) = \frac{200(j\omega)}{(j\omega+2)(j\omega+10)}$

Solution:

$$\begin{aligned} H(\omega) &= \frac{200(j\omega)}{2(1 + \frac{j\omega}{2}) * 10(\frac{j\omega}{10} + 1)} \\ &= \frac{10(j\omega)}{(1 + \frac{j\omega}{2})(1 + \frac{j\omega}{10})} \end{aligned}$$

⇒ See the drawing on the next page.



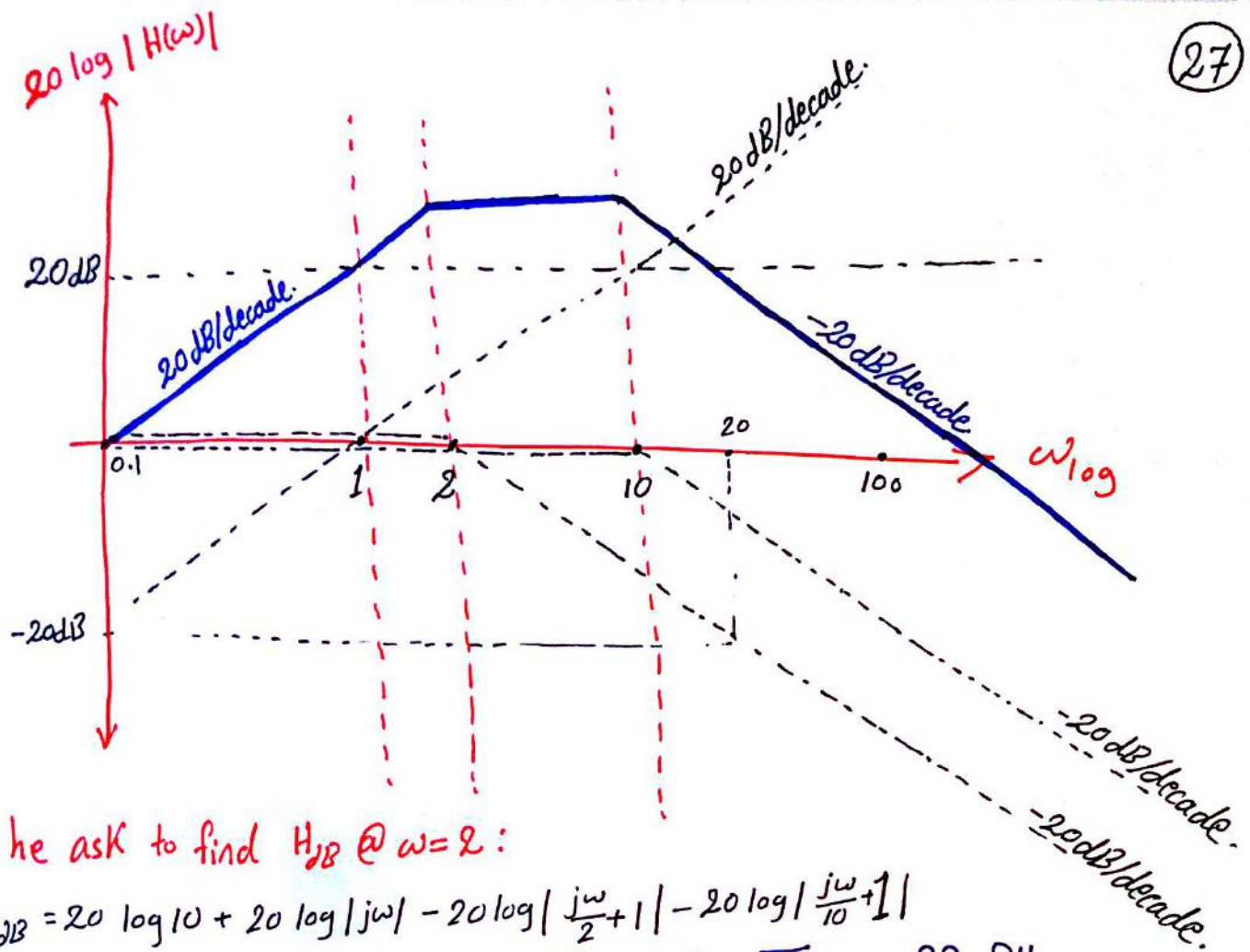


if he ask to find H_{dB} @ $\omega = 2$:

$$\begin{aligned}
 H_{dB} &= 20 \log 10 + 20 \log |j\omega| - 20 \log \left| \frac{j\omega}{2} + 1 \right| - 20 \log \left| \frac{j\omega}{10} + 1 \right| \\
 &= 20 \log 10 + 20 \log 2 - 20 \log \sqrt{2} - 20 \log \sqrt{1.04} = \underline{\underline{22.84}}
 \end{aligned}$$

Now for the angle:
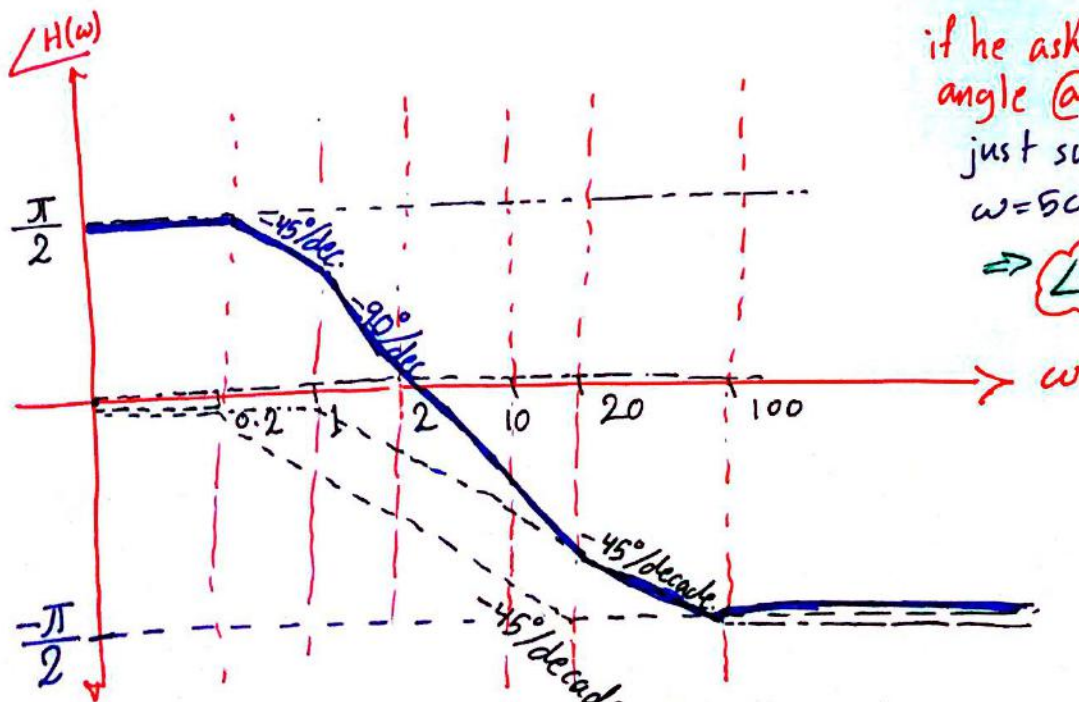
$$\angle H(\omega) = 0 + 90 - \tan^{-1} \frac{\omega}{2} - \tan^{-1} \frac{\omega}{10}$$




if he ask about the angle @ $\omega = 50$:
 just substitute $\omega = 50$ in the equation.
 $\Rightarrow \angle H(50) = -76.4^\circ$

ex. $H(\omega) = \frac{5(j\omega + 2)}{j\omega(j\omega + 10)}$
 solution:


$$\Rightarrow H(\omega) = \frac{5 * 2 [1 + \frac{j\omega}{2}]}{j\omega * 10 [1 + \frac{j\omega}{10}]} = \frac{(1 + \frac{j\omega}{2})}{j\omega (1 + \frac{j\omega}{10})}$$

$$H_{dB} = 20 \log |1 + \frac{j\omega}{2}| - 20 \log |j\omega| - 20 \log |1 + \frac{j\omega}{10}|$$

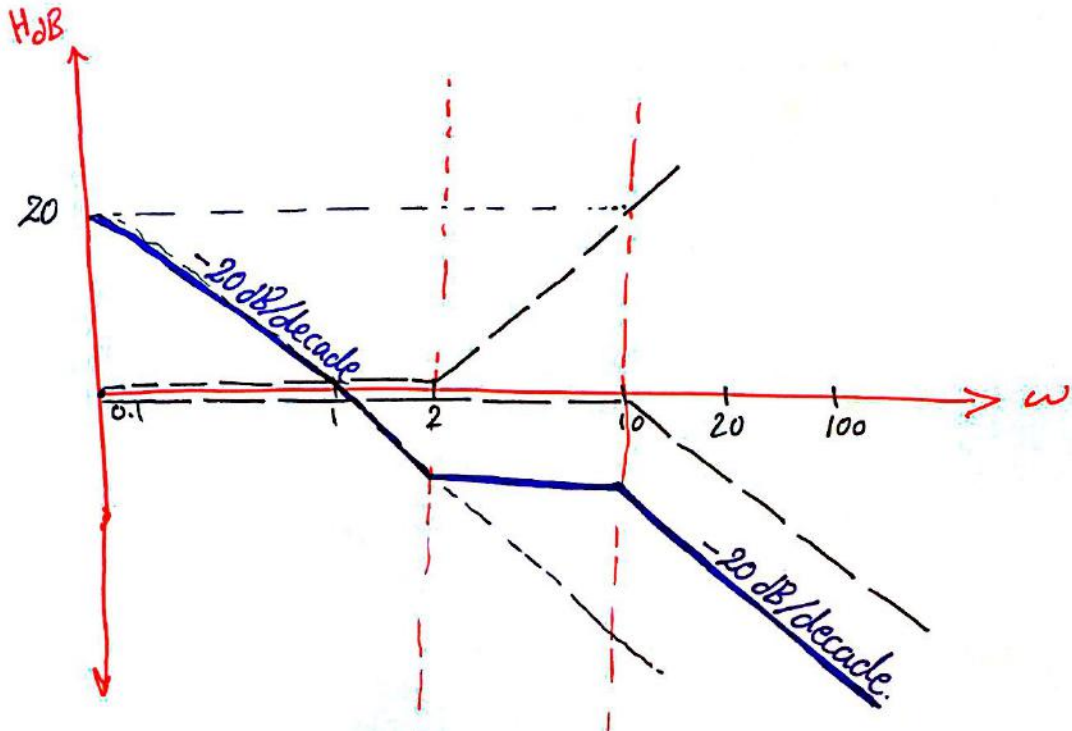

Now for the angle:
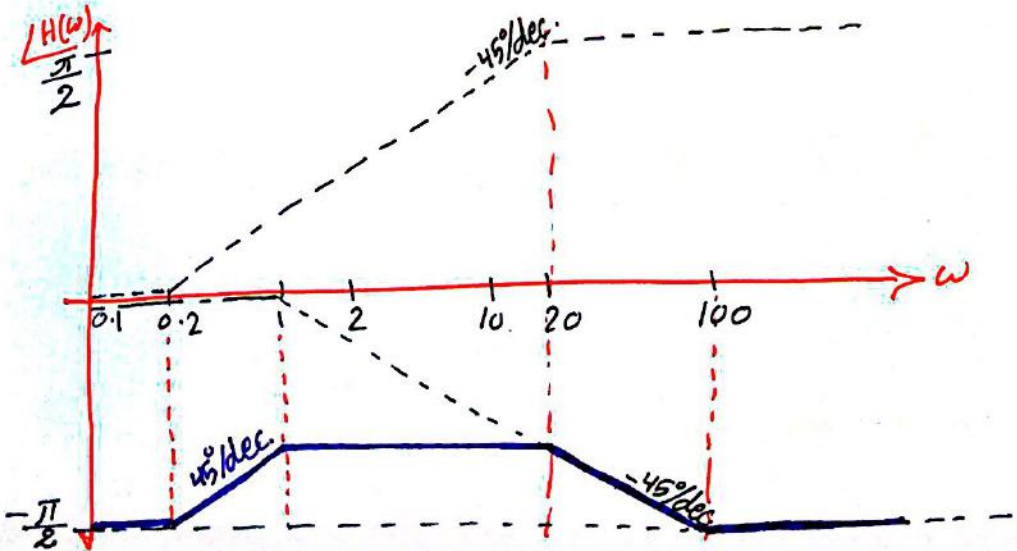
$$\angle H(\omega) = \tan^{-1}(\frac{\omega}{2}) - 90 - \tan^{-1}(\frac{\omega}{10})$$




ex. $H(\omega) = \frac{j\omega + 10}{j\omega(j\omega + 5)^2}$

Solution:


$$\Rightarrow H(\omega) = \frac{10(1 + \frac{j\omega}{10})}{j\omega * 25(\frac{j\omega}{5} + 1)^2} = \frac{0.4(1 + \frac{j\omega}{10})}{j\omega(1 + \frac{j\omega}{5})^2}$$

$$\Rightarrow H_{dB} = \underbrace{20 \log 0.4}_{-7.96} + 20 \log |1 + \frac{j\omega}{10}| - 20 \log |j\omega| - 40 \log |1 + \frac{j\omega}{5}|$$

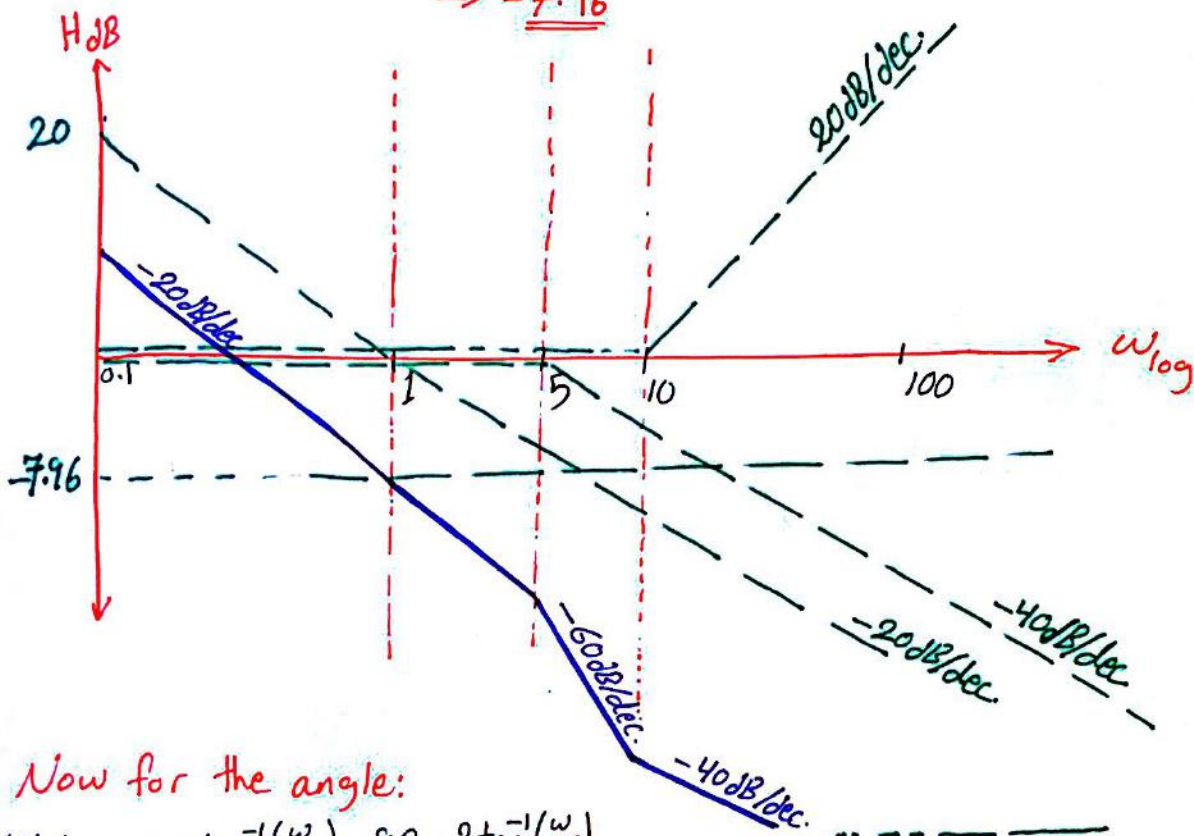

Now for the angle:


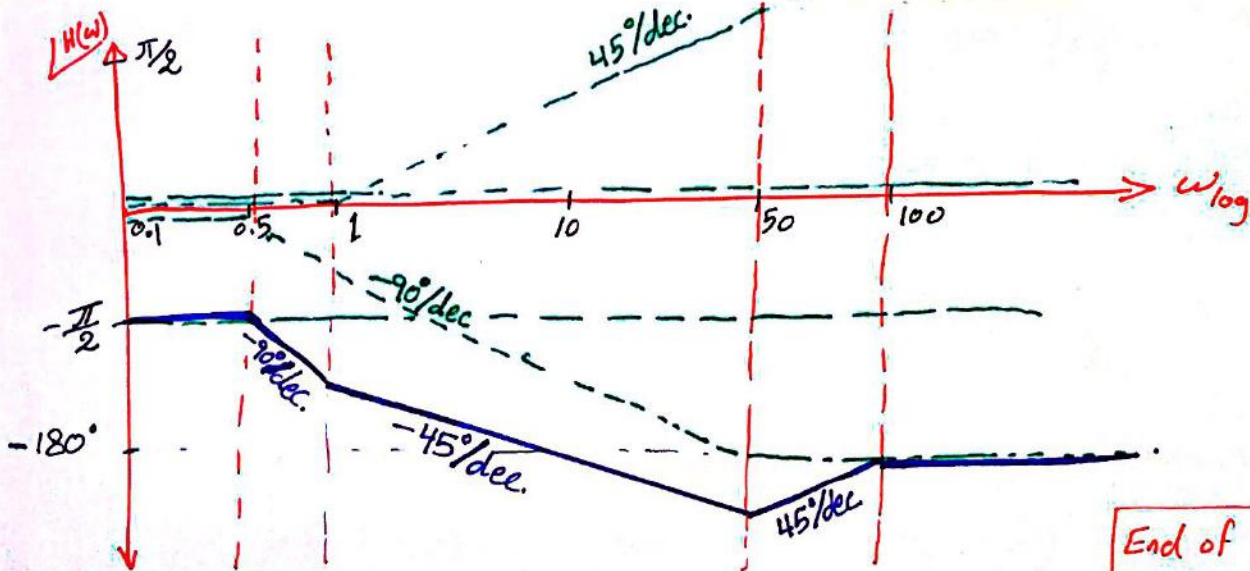
$$\angle H(\omega) = 0 + \tan^{-1}(\frac{\omega}{10}) - 90 - 2 \tan^{-1}(\frac{\omega}{5})$$



End of CH14

CHAPTER (19)

Two-Port Networks

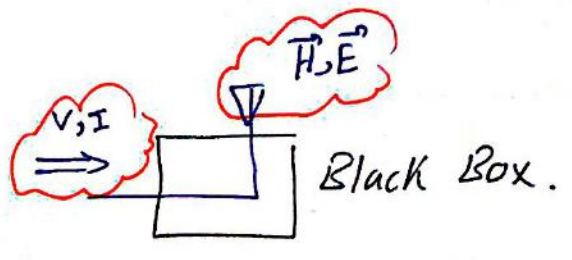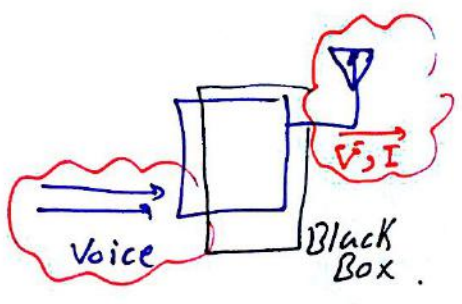

⇒ What happens on one of the ports if we change the other one?!


* Z-Parameters:

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

In matrix form:
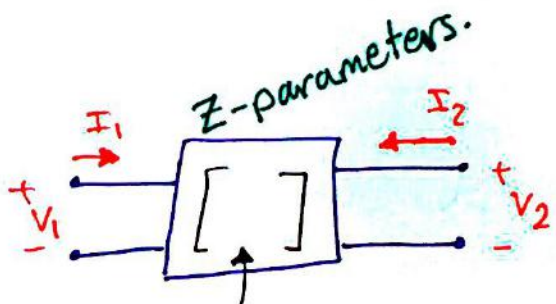
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$



$$\Rightarrow [V] = [Z][I]$$

⇒ Lets put $I_2 = 0$: (open ckt to the right side)

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

⇒ Lets put $I_1 = 0$: (open ckt to the left side)

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$


Z_{11} : open ckt input impedance.

Z_{22} : open ckt output impedance.


Z_{21} : open ckt transfer impedance from port 2 to port 1.

Z_{12} : open ckt transfer impedance from port 1 to port 2.


* To obtain Z_{11} & Z_{21} :

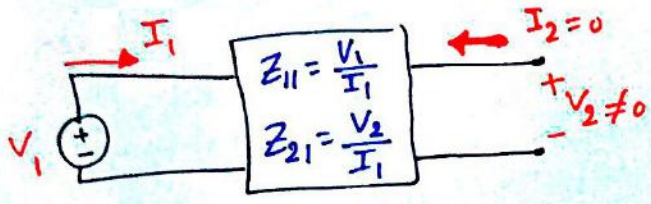

* To obtain Z_{12} & Z_{22} :

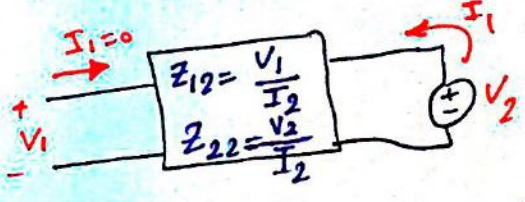

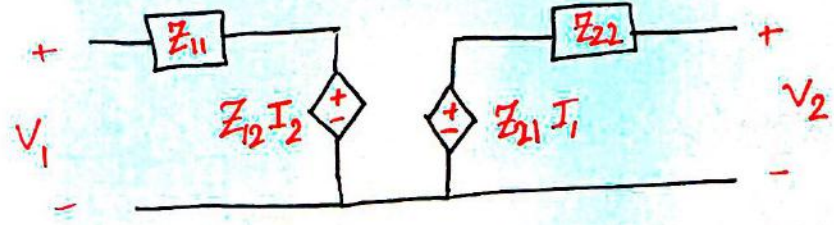* Equivalent ckt for a 2-port network (with dependent power sources):




$$V_1 = Z_{11} I_1 + Z_{12} I_2$$


$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

⇒ The same two equations that were obtained before.

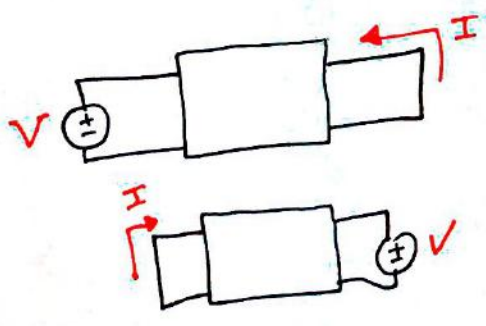* Special Case: if the networks have NO dependent power sources, we say that the system is "reciprocal".




⇒

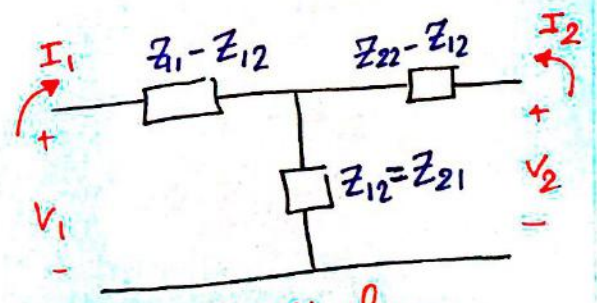


Equivalent ckt for a reciprocal network.

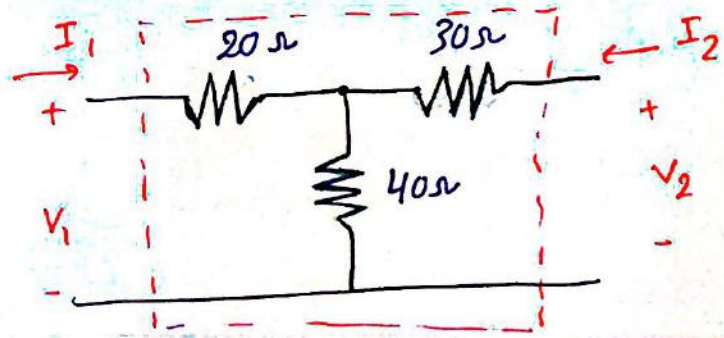(ex.) Determine the Z-parameters for the ckt:



⇒ Solution:


method (1):

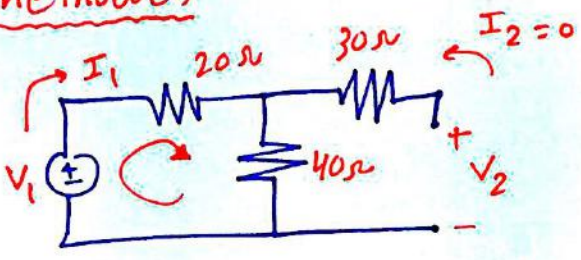

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$Z_{11} = \frac{I_1 (20+40)}{I_1} = \boxed{60 \Omega}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = \frac{40 I_1}{I_1} = \boxed{40 \Omega}$$

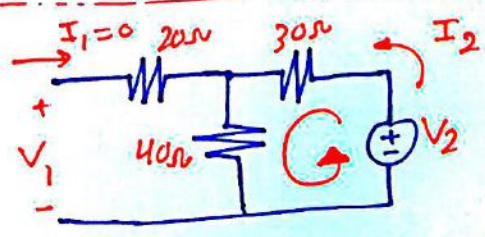

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = \frac{40 I_2}{I_2} = \boxed{40 \Omega}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = \frac{(40+30) I_2}{I_2} = \boxed{70 \Omega}$$

* What is the voltage where $V_1 = 10 \text{ volt}$ & $I_1 = 5 \text{ A}$.


$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

⇒ solve for V_2 & I_2

$$\boxed{I_2 = -7.25 \text{ A}, V_2 = -307.5 \text{ volt}}$$

method (2):

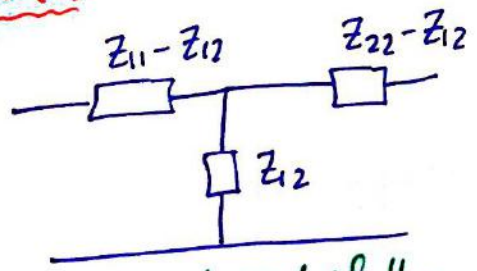

⇒ $\boxed{Z_{12} = Z_{21} = 40 \Omega}$

$$20 = Z_{11} - Z_{12}$$


$$\Rightarrow \boxed{Z_{11} = 60 \Omega}$$

$$30 = Z_{22} - Z_{12}$$

$$\Rightarrow \boxed{Z_{22} = 70 \Omega}$$

This method just used if the ckt was in the shape of the special case "reciprocal network"

Ⓧ Find I_1 & I_2 in the ckt shown:

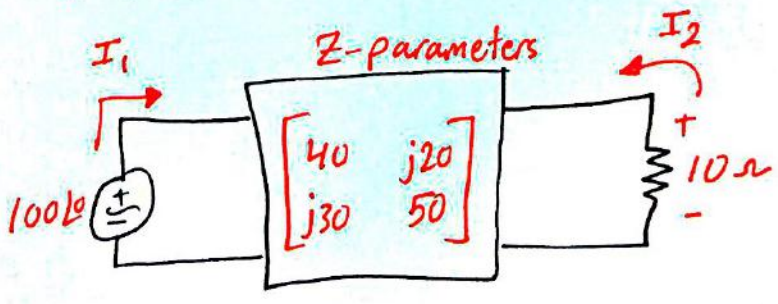

Solution:

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \Rightarrow 100 \angle 0 = 40 I_1 + j20 I_2$$


$$V_2 = Z_{21} I_1 + Z_{22} I_2 \Rightarrow -10 I_2 = j30 I_1 + 50 I_2$$

solving:

$$I_1 = 2 \angle 0 \text{ A}$$

$$I_2 = 1 \angle -90^\circ \text{ A}$$

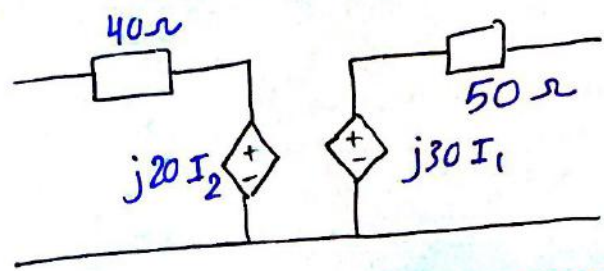
if he asked about the equivalent ckt for this example:



ex. Z is given by $\begin{bmatrix} 10^3 & 10 \\ -10^6 & 10^4 \end{bmatrix} \Omega$, find the voltage, current & power gain if the 2-port network is driven by V_s in series with 500Ω & terminated by $10 \text{ k}\Omega$ resistor.

Solution:

* Driven \Rightarrow it means input.

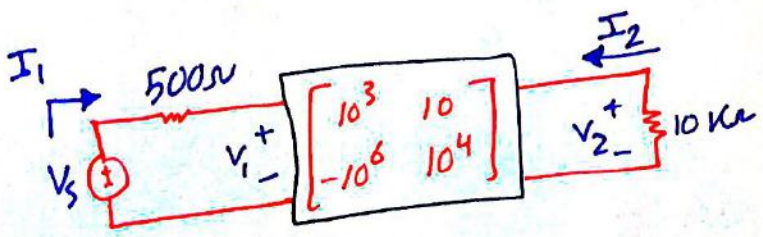

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \dots (0)$$

$$\Rightarrow (V_s - 500 I_1) = 10^3 I_1 + 10 I_2 \dots (1)$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$-10^4 I_2 = -10^6 I_1 + 10^4 I_2 \dots (2)$$

from (2): $\Rightarrow I_2 = 50 I_1 \dots (3)$

substitute (3) in (0):

$$V_s = 1500 I_1$$

also (3) in (1):

$$V_s = 2000 I_1$$



$$\Rightarrow I_1 = \frac{V_s}{2000}, \quad I_1 = \frac{V_1}{1500}$$

$$V_2 = -10^6 I_1 + 10^4 [50 I_1] = \underline{\underline{-0.5 * 10^6 I_1}}$$

$$V_{gain} = \frac{V_2}{V_1} = \frac{-0.5 * 10^6 I_1}{1500 I_1} = \boxed{-333.33}$$

$$\text{Gain}_I = \frac{I_2}{I_1} = \boxed{50}$$

$$\text{Gain}_p = \frac{-\frac{1}{2} V_2 I_2}{\frac{1}{2} V_1 I_1} = \frac{-\frac{1}{2} * -\frac{1}{2} * 10^6 I_1 * 50 I_1}{\frac{1}{2} * 1500 I_1 * I_1} = \boxed{16670}$$

⇒ if he asked to find Z_{in} & Z_{out} ?!

$$Z_{in} = \frac{V_1}{I_1} \quad \& \quad Z_{out} = Z_{22} - \frac{Z_{12} Z_{21}}{Z_{11} + Z_g}$$

for the last example:

$$\boxed{Z_{in} = 1500 \Omega}$$

$$\boxed{Z_{out} = 16.67 \text{ K}\Omega}$$

generator impedance or source impedance.

✘ Y-parameters:

⇒ Some times Z parameters do not exist
⇒ Use the Y-parameters.

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \underbrace{\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}}_{\text{Y-parameters}} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \Rightarrow [I] = [Y][V]$$


Equations: $I_1 = Y_{11}V_1 + Y_{12}V_2$
 $I_2 = Y_{21}V_1 + Y_{22}V_2$

\Rightarrow set $V_2 = 0$ (short ckt on the right side)

$$Y_{11} = \frac{I_1}{V_1}$$

$$Y_{21} = \frac{I_2}{V_1}$$

when $V_2 = 0$.

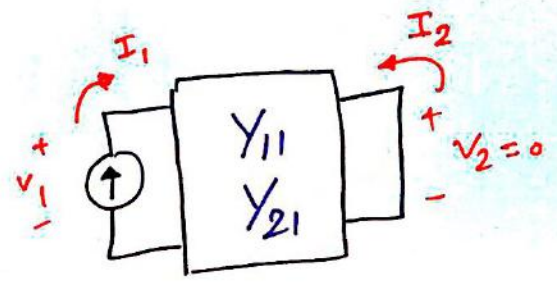


\Rightarrow set $V_1 = 0$ (short ckt on the left side)

$$Y_{12} = \frac{I_1}{V_2}$$


$$Y_{22} = \frac{I_2}{V_2}$$

when $V_1 = 0$.

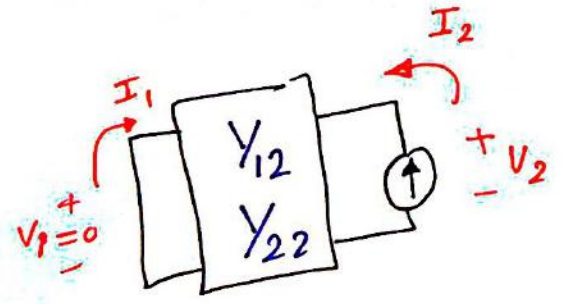

- Y_{11} : short ckt input admittance.
- Y_{12} : short ckt transfer admittance from port 1 to port 2.
- Y_{21} : short ckt transfer admittance from port 2 to port 1.
- Y_{22} : short ckt output admittance.

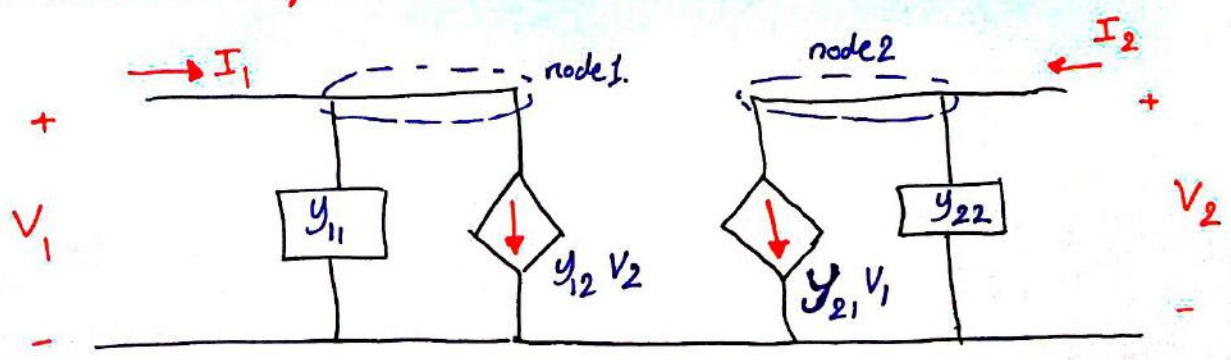* General equivalent ckt for 2-port network:



⇒ You can reach for the main two equations:

By nodal analysis:


@ node 1: $I_1 + (0 - V_1) y_{11} - y_{12} V_2 = 0$

⇒ $\left\{ \begin{aligned} I_1 &= V_1 y_{11} + y_{12} V_2 \\ I_2 &= V_2 y_{22} + y_{21} V_1 \end{aligned} \right\}$ as obtained before.

@ node 2:

* Reciprocal ckt: [NO dependent power sources]

⇒ $Y_{12} = Y_{21}$


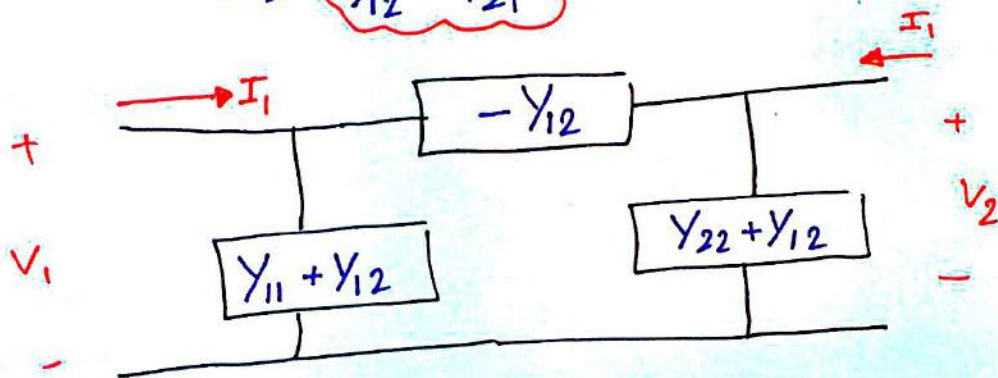


Ex. Obtain the Y-parameters for the network shown:

Solution:

method (1):

for y_{11} & y_{22}

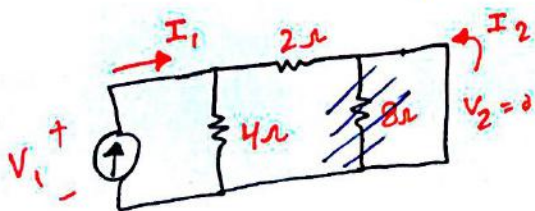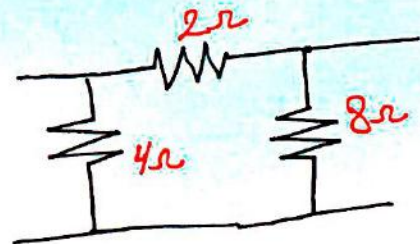

$4 // 2 \Rightarrow \frac{8}{6} \Omega$

so $I_1' = I_1 * \frac{8}{6}$

$y_{11} = \frac{I_1}{V_1} \Rightarrow y_{11} = \frac{6}{8} \Omega^{-1}$

$y_{21} = \frac{I_2}{V_1}$


current division:

$I_2 = -I_1 \frac{4}{6}$

$= \frac{-4}{6} I_1$
 $\frac{8}{6} I_1$

⇒ $y_{21} = -0.5 \Omega^{-1}$

Now for y_{22} & y_{12} :

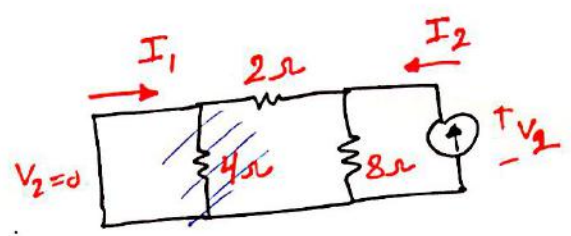

$$y_{22} = \frac{I_2}{V_2}$$



$$2 \parallel 8 \Rightarrow \frac{8}{5} \Omega$$

$$\Rightarrow y_{22} = \frac{I_2}{\frac{8}{5} I_2} \Rightarrow \boxed{y_{22} = \frac{5}{8} S}$$

$$\text{so } V_2 = \frac{8}{5} I_2$$

$$y_{12} = \frac{I_1}{V_2} = \frac{-\frac{8}{10} I_2}{\frac{8}{5} I_2} \Rightarrow \boxed{y_{12} = -0.5 S}$$

method(2):

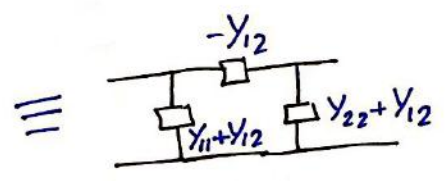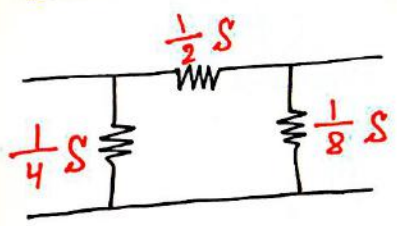

Y parameters

$$= \begin{bmatrix} 0.75 & -0.5 \\ -0.5 & 0.625 \end{bmatrix}$$

$$\Rightarrow -y_{12} = \frac{1}{2} \Rightarrow \boxed{y_{12} = -0.5 = y_{21}}$$


$$\frac{1}{8} = y_{22} + y_{12} \Rightarrow y_{22} = \frac{1}{8} - (-0.5) \Rightarrow \boxed{y_{22} = 0.625 S}$$

$$\frac{1}{4} = y_{11} + y_{12}$$

$$\Rightarrow y_{11} = \frac{1}{4} - (-0.5)$$


$$\Rightarrow \boxed{y_{11} = 0.75}$$

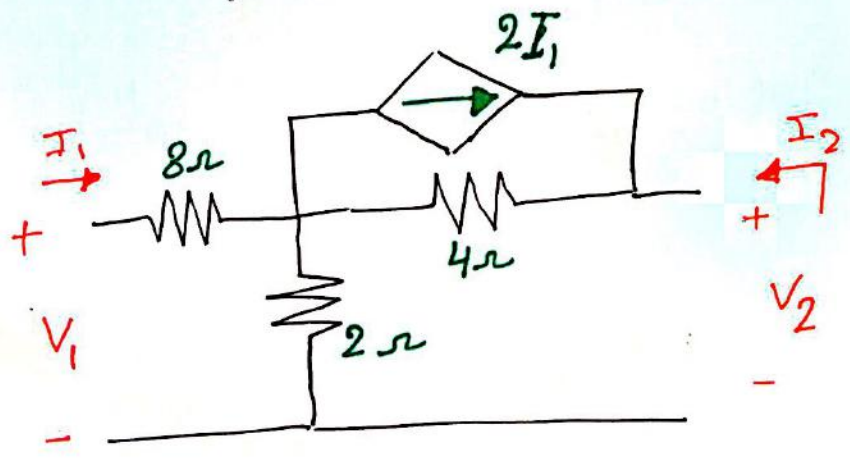(ex.) Determine the Y-parameters for the 2-port network:



Solution: To find y_{11}, y_{21} :

(38)

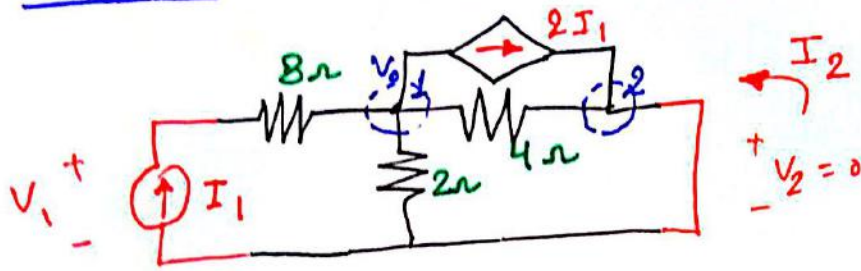

$$y_{11} = \frac{I_1}{V_1}$$

$$y_{21} = \frac{I_2}{V_1}$$

@ node(1): $\frac{V_1 - V_0}{8} + \frac{-V_0}{2} + \frac{-V_0}{4} - 2I_1 = 0$

$$\Rightarrow I_1 = \frac{V_1 - V_0}{8} \dots (*)$$

$$\Rightarrow \frac{V_1}{8} - \frac{V_0}{8} - \frac{V_0}{2} - \frac{V_0}{4} - \frac{V_1}{4} + \frac{V_0}{4} = 0$$

solving $\Rightarrow V_1 = -5V_0$

for equ. (*):

$$I_1 = \frac{V_1 - V_0}{8} = \frac{-5V_0 - V_0}{8} = -0.75V_0$$

$I_1 = -0.75V_0$

$$\Rightarrow y_{11} = \frac{I_1}{V_1} = \frac{-0.75V_0}{-5V_0}$$

$\Rightarrow y_{11} = 0.15 S$

@ node(2):

$$2I_1 + I_2 + \frac{V_0 - 0}{4} = 0 \Rightarrow 2I_1 + I_2 + \frac{V_0}{4} = 0$$


$$-1.5V_0 + I_2 + \frac{V_0}{4} = 0$$

$\Rightarrow I_2 = 1.25V_0$

$$y_{21} = \frac{I_2}{V_1}$$

$$y_{21} = \frac{1.25V_0}{-5V_0} \Rightarrow y_{21} = -0.25 S$$

\Rightarrow continue.

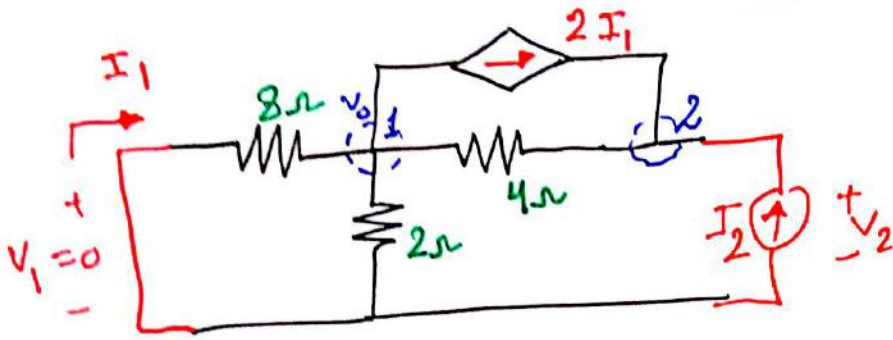

$$y_{12} = \frac{I_1}{V_2}$$

$$y_{22} = \frac{I_2}{V_2}$$

@ node(1):

$$\frac{0-V_0}{8} + \frac{0-V_0}{2} + \frac{V_2-V_0}{4} - 2I_1 = 0 \Rightarrow I_1 = -\frac{V_0}{8}$$

solving $V_2 = 2.5V_0$

$$y_{12} = \frac{I_1}{V_2} \Rightarrow y_{12} = \frac{-V_0/8}{2.5V_0} \Rightarrow y_{12} = -0.05 S$$

@ node(2): $I_1 = -\frac{V_0}{8}$ $V_2 = 2.5V_0$

$$I_2 + 2I_1 + \frac{V_0 - V_2}{4} = 0 \Rightarrow I_2 = 0.625V_0$$

$$y_{22} = \frac{I_2}{V_2} \Rightarrow y_{22} = \frac{0.625V_0}{2.5V_0} \Rightarrow y_{22} = 0.25 S$$

so Y-parameters is:

$$Y = \begin{bmatrix} 0.15 & 0.05 \\ -0.25 & 0.25 \end{bmatrix}$$


ex. Construct The Bode Plot for the following:

$$H(\omega) = \frac{5 (j\omega)^2 (j\omega + 10)}{(j\omega + 5)(j\omega + 2)}$$


writing $H(\omega)$ in the standard form:

$$H(\omega) = \frac{5 (j\omega)^2 (1 + \frac{j\omega}{10})}{(1 + \frac{j\omega}{5})(1 + \frac{j\omega}{2})}$$
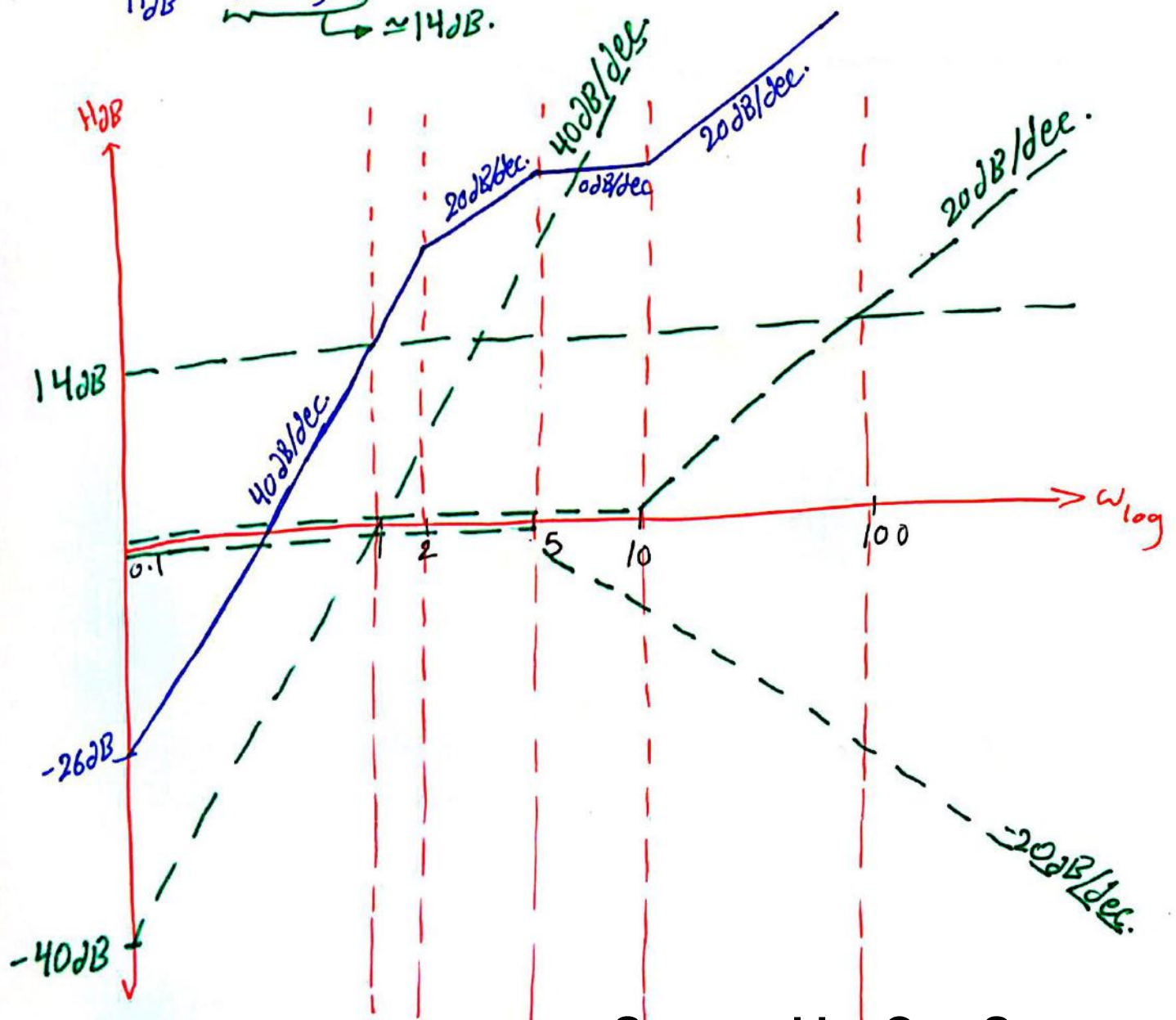
$$H_{dB} = \underbrace{20 \log 5}_{\approx 14dB} + 40 \log(j\omega) + 20 \log(1 + \frac{j\omega}{10}) - 20 \log(1 + \frac{j\omega}{5}) - 20 \log(1 + \frac{j\omega}{2})$$


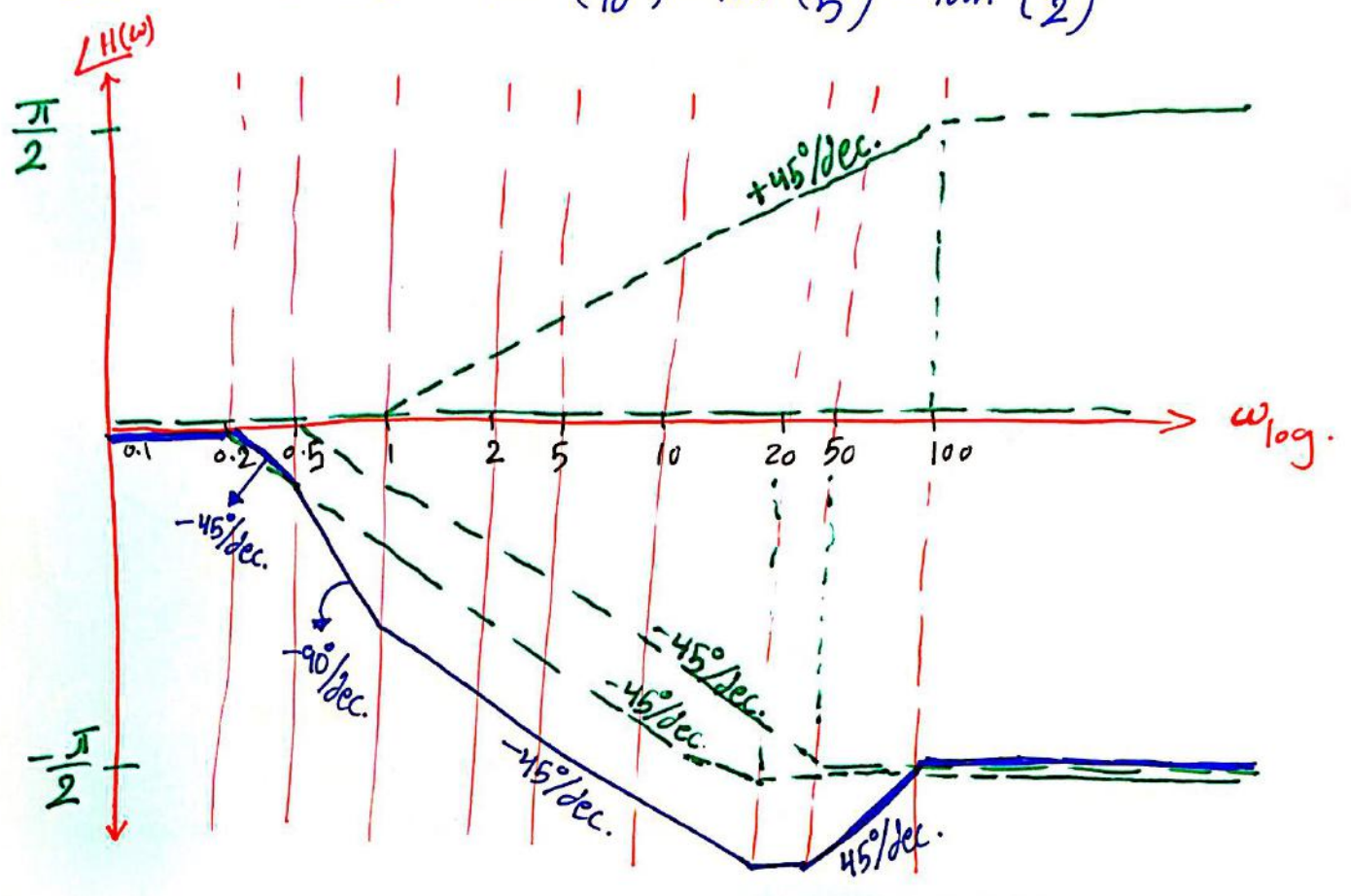
$$\angle H(\omega) = 0 + 0 + \tan^{-1}\left(\frac{\omega}{10}\right) - \tan^{-1}\left(\frac{\omega}{5}\right) - \tan^{-1}\left(\frac{\omega}{2}\right)$$



End of Material.

Best
of
Luck.

Electrical Circuits II

1

* Summary *

* CHAPTER (10):

* for the capacitor:

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

$$v_c(t) = \frac{1}{C} \int_0^t i_c(t') dt' + v_c(0^-)$$

* the current leads the voltage.

* for the inductor:

$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$i_L(t) = \frac{1}{L} \int_0^t v_L(t') dt' + i_L(0^-)$$

* the voltage leads the current.

* Converting from phasor to time domain:

⊗ the amplitude must be positive and peak value.

* Converting from time domain to phasor:

① Amplitude must be (+ve).

② it must be a cosine function.

* CHAPTER (11):

* instantaneous power:

$$P(t) = v(t) \cdot i(t)$$

$$P(t) = \frac{V_m I_m}{2} [\cos(2\omega t + \theta_v + \theta_i) + \cos(\theta_v - \theta_i)]$$

* Average Power:

$$P = \frac{1}{T} \int_0^T P(t) dt$$

* just the resistance has an average power.

$$P_{avg} = \frac{V_m I_m}{2} \text{ (in R)}$$

$$P_{avg} = \text{Zero (in L \& C)}$$

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \text{ (in any element)}$$

$$P_{avg} \text{ (R)} = \frac{1}{2} V_m I_m = \frac{V_m^2}{2R} = \frac{1}{2} I_m^2 R$$

* Maximum Power Transfer:


happens when: $Z_{th} = Z_L^*$

if power is maximized:

$$P_{avg}|_{load} = \frac{V_{th}^2}{8R}$$

* for multiple signals & multiple frequencies:

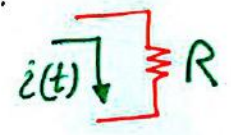
$$i(t) = I_{m1} \sin \omega_1 t + I_{m2} \cos \omega_2 t + I_{m3} \sin \omega_3 t + \dots$$



$$P_{avg} = \frac{1}{2} I_{m1}^2 R + \frac{1}{2} I_{m2}^2 R + \frac{1}{2} I_{m3}^2 R + \dots$$
$$P_{avg} = \frac{V_{m1}^2}{2R} + \frac{V_{m2}^2}{2R} + \frac{V_{m3}^2}{2R} + \dots$$

* RMS:
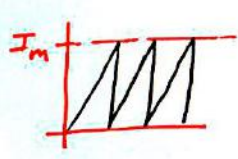
$$V_{eff} = V_{rms} = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt} \Rightarrow \text{in general.}$$



$$I_{rms} = \frac{I_m}{\sqrt{3}}$$

\Rightarrow for ST waveform.

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

\Rightarrow for a sinusoidal signal.

\Rightarrow for a resistor:

$$P_{avg} = V_{rms} I_{rms} = V_{rms}^2 / R = I_{rms}^2 R$$

if there is multiple frequencies:

$$P_{avg} = (I_{rms1}^2 + I_{rms2}^2 + I_{rms3}^2 + \dots) R$$

* Power factor:

$$PF = \cos(\theta_V - \theta_I)$$

Leading if $\theta_V - \theta_I \Rightarrow (-ve)$.
Lagging if $\theta_V - \theta_I \Rightarrow (+ve)$.

equal 1
for resistance.

equal zero
for pure inductance or capacitance.

* Complex Power: (Assume RMS values)

$S = V I^* = \frac{V^2}{Z^*} = I^2 Z$	⇒	Complex Power (VA)
$ S = V I $	⇒	Apparent Power (VA)
$P = V I \cos(\theta_V - \theta_I)$	⇒	Real/Average Power (W)
$Q = V I \sin(\theta_V - \theta_I)$	⇒	Reactive Power (VAR)

* Adding capacitor to a ckt to give us new Pf:

we find P from the old Pf since it will be always constant then find Q_1 Then Q_2 from $Q_2 = P * \tan(\cos^{-1}(Pf_{new}))$

⇒ $Q_c = Q_2 - Q_1$

⇒ $C = \frac{|Q_c|}{|V_{rms}|^2 \omega}$

* RMS value for multiple signals:

$$V_{rms} = \sqrt{(V_{rms1})^2 + (V_{rms2})^2 + \dots}$$

✱ CHAPTER (12):

* in Balanced systems:

if the load is Δ -connected:

$$\begin{aligned} V_{LL} &= V_{phase} \\ I_L &= \sqrt{3} I_p \angle -30^\circ \end{aligned} \quad \dots(1)$$

if the load is Y-connected:

$$\begin{aligned} V_{LL} &= \sqrt{3} V_{LN} \angle +30^\circ \\ I_L &= I_p \end{aligned} \quad \dots(2)$$

$Z_\Delta = 3 Z_Y$ $\dots(3)$

* Always in Balanced-systems: convert to Y-Y and use the single phase ckt ⇒ will be the easiest way to solve.

* In UnBalanced systems: DON'T use the relations in Box (1) & (2) & (3)

* Always the unbalanced system: \Rightarrow unbalanced in the load
 (source is always balanced)
 $\hookrightarrow V_{ab} = \sqrt{3} V_{an} \angle +30^\circ$ (use it always)

* in Balanced system:
 if there is a line (with or without impedance) \Rightarrow connected with n & N
 \Rightarrow we don't care to it, it has NO effect.
 $I_a + I_b + I_c = 0 \Rightarrow$ always in balanced-system.

* in Unbalanced system: (Three Cases)

① if just only a line (without impedance) connected to n & N
 $\Rightarrow I_a + I_b + I_c = I_{Nn}$ & $V_n = V_N = 0$

② if it is line (with impedance) $\Rightarrow I_a + I_b + I_c = I_{Nn}$
 $V_n = 0, V_N \neq 0$
 $\Rightarrow V_N = Z_{line} * I_{Nn}$

③ if No line between n & N $\Rightarrow V_N \neq 0, I_a + I_b + I_c = 0$

* Power in 3phase system:

$P_\Delta = P_Y = 3 V_p I_p \cos(\theta_v - \theta_i)$	$S_\Delta = S_Y = 3 V_p I_p^*$
$Q_\Delta = Q_Y = 3 V_p I_p \sin(\theta_v - \theta_i)$	$ S_\Delta = S_Y = \sqrt{3} V_L I_L $

* Losses in the 3phase system:

$$S_{losses} = S_{source} - S_{load}$$

$$S_{losses} = 3 |I_L|^2 Z_{T.L}$$

* Wattmeter mesurments:

\Rightarrow Determine the voltage (V) & the current (I) that measured by this wattmeter then:
 $P = |V| |I| \cos(\theta_v - \theta_i)$

* if 3-wattmeters used: $P_{Total} = P_1 + P_2 + P_3$

* In Two-Wattmeters method:

$P_T = P_1 + P_2$ $Q_T = \sqrt{3}(P_2 - P_1)$ $S_T = P_T + jQ_T$

$Pf = \cos \theta$ $\theta = \tan^{-1} \left(\frac{\sqrt{3}(P_2 - P_1)}{P_1 + P_2} \right)$

✱ CHAPTER (13):

✱ Linear Transformer:

⇒ Virtual source: we put it between the dot & the coil

* Choosing the polarities:

if the current enter the dot ⇒ take it (+ve) for the other dot.
 if " " leaves " " ⇒ take it (-ve) " " " "

* Energy stored:

$W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 (\pm) M I_1 I_2$

(-) if one current leaves & the other enters.

(+) if both currents leaving or entering the dots.

* Coupling Coefficient: $K = \frac{M}{\sqrt{L_1 L_2}}$

* For linear transformer with current entering in primary & leaving in secondary:

$Z_{11} = R_1 + j\omega L_1$ + any other impedances in primary.

$Z_{22} = R_2 + j\omega L_2 + Z_L$ + any other impedances in secondary.

$Z_{in} = Z_{11} + \frac{(\omega M)^2}{Z_{22}}$

Reflected Impedance = $\frac{(\omega M)^2}{Z_{22}}$

⇒ you can find I_1 & I_2 easily from:

$$I_1 = V_s / Z_{in}$$


for I_2 : ⇒

$$I_2 = \frac{j\omega M}{Z_{22}} I_1$$


if both currents entering the dot here you have to multiply I_2 by (-1) if you use this way.

* T-equivalent ckt:

(Both currents entering or leaving)

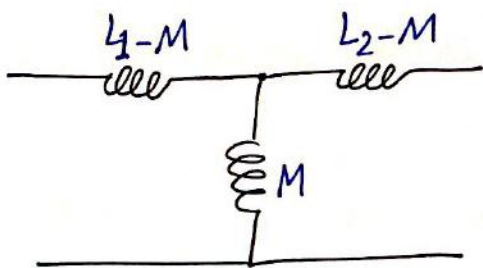


(one current enter and the other leave)

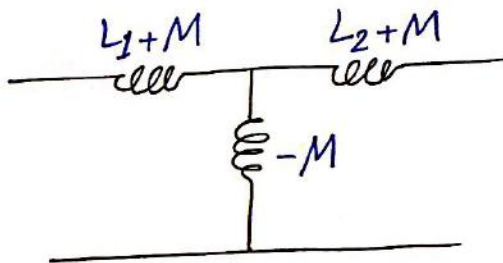


* π-equivalent ckt:

(Both currents enter or leave)

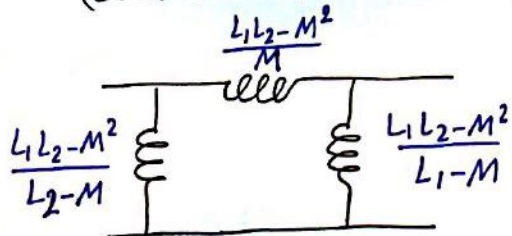

(one current enter & other leave)

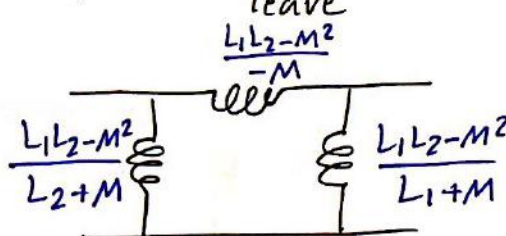

* We use T & π just if there is a connection between the primary & the secondary

** Ideal Transformer:

$$a \text{ or } n = \frac{N_2}{N_1} = \frac{V_2}{V_1} = \frac{I_1}{I_2}$$

for currents:
if the currents entering or leaving the dots together (-ve) n
otherwise (+ve) n


always n (+ve)
for $\frac{N_2}{N_1}$

for voltages:
if V_1, V_2 both (+ve) or both (-ve) ⇒ (+ve) n
otherwise (-ve) n.

* Complex Power:

$$S_{\text{primary}} = S_{\text{secondary}} = V_1 I_1^* = V_2 I_2^*$$

* Reflection:

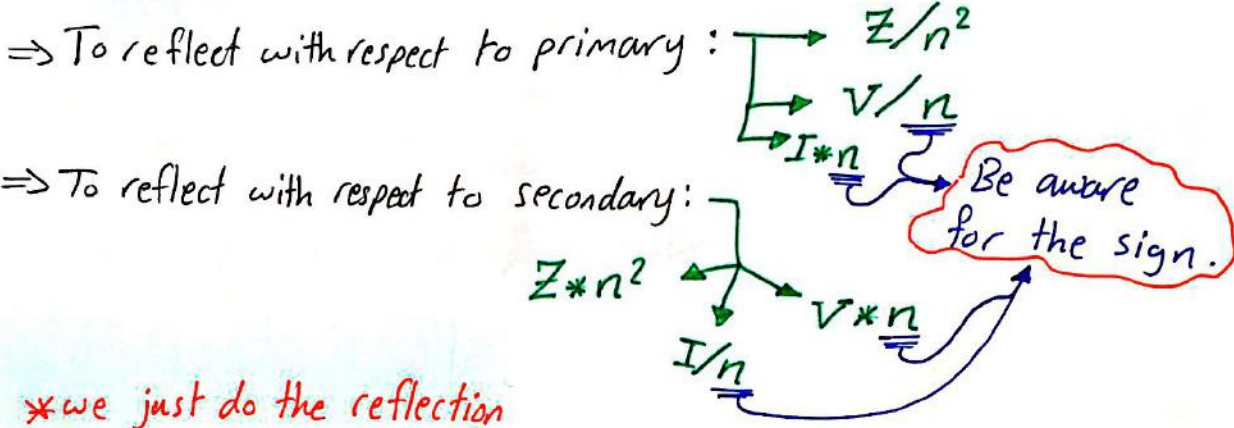

* we just do the reflection if there is NO connection between primary & secondary. Otherwise, use mesh & nodal.

✱ CHAPTER (14):

* Common Relations for series & Parallel Resonance:

$$\beta = \frac{\omega_0}{Q_0}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

$$\omega_{1,2} = \omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0}\right)^2} \mp \frac{1}{2Q_0} \right]$$

* Approximate:

$$\omega_{1,2} = \omega_0 \mp \frac{1}{2}\beta$$

$$\omega_0 = \frac{1}{2}(\omega_1 + \omega_2)$$

$$N = \frac{\omega - \omega_0}{\frac{1}{2}\beta}$$


* Series Resonance:

$$Q_0 = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

$$|V_L(\omega_0)| = |V_C(\omega_0)| = V Q_0$$

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$Z_{\text{app}} = R(1 + jN)$$

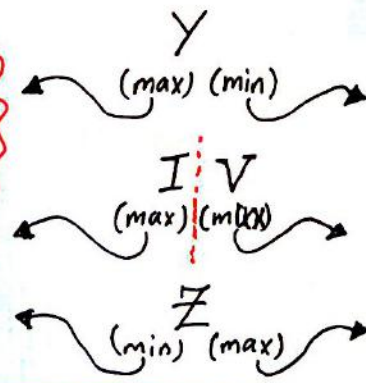



* Parallel Resonance:

$$Q_0 = \omega_0 RC = \frac{R}{\omega_0 L}$$

$$|I_L(\omega_0)| = |I_C(\omega_0)| = I Q_0$$

$$Y = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$$

$$Y_{\text{app}} = \frac{1}{R}(1 + jN)$$

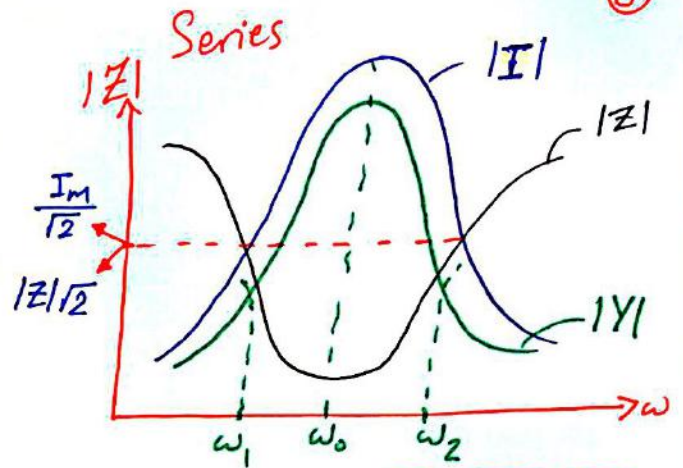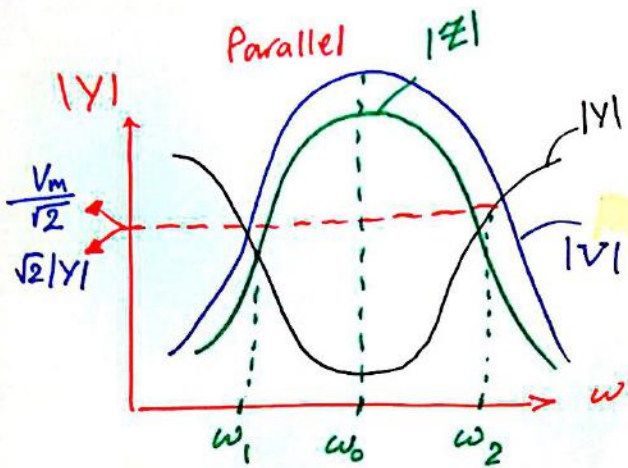

***if you find $P(\omega_0)$ then $P(\omega_1) = P(\omega_2) = \frac{1}{2} P(\omega_0)$

* Other Resonance Forms:

KEY: To find ω_0 just choose what is easy to deal with Z or Y then find the equivalent & put the imaginary part = 0

* Transfer function: $\frac{\text{output}}{\text{input}}$

* Filters:

* Low pass filter: RC ckt \Rightarrow output on C.
 RL ckt \Rightarrow output on R.
 other ckt \Rightarrow make $|H_v(\omega_c)| = \frac{1}{\sqrt{2}}$
 Then find ω_c .

$\omega_c = \frac{1}{RC}$

$\omega_c = \frac{R}{L}$

* High pass filter: RL ckt \Rightarrow output on L.
 RC ckt \Rightarrow output on R.
 other ckt \Rightarrow put $|H_v(\omega_c)| = \frac{1}{\sqrt{2}}$
 Then find ω_c .

$\omega_c = \frac{R}{L}$

$\omega_c = \frac{1}{RC}$

* Band pass filter: RLC ckt \Rightarrow output on R. $\Rightarrow \omega_0$ & ω_1 & ω_2 as in resonance.

* Band stop filter: RLC ckt \Rightarrow output on (L & C) $\Rightarrow \omega_0$ & ω_1 & ω_2 as in resonance.


* Bode Plot: → could be zero or pole.

⇒ standard form:


$$H(\omega) = \frac{K (j\omega)^{\pm 1} \left[1 + \frac{j\omega}{Z_1} \right]}{\left[1 + \frac{j\omega}{P_1} \right]}$$

→ Zero @ Z_1
→ Pole @ P_1
Constant.

⇒ Drawing $H_V(\omega)$:

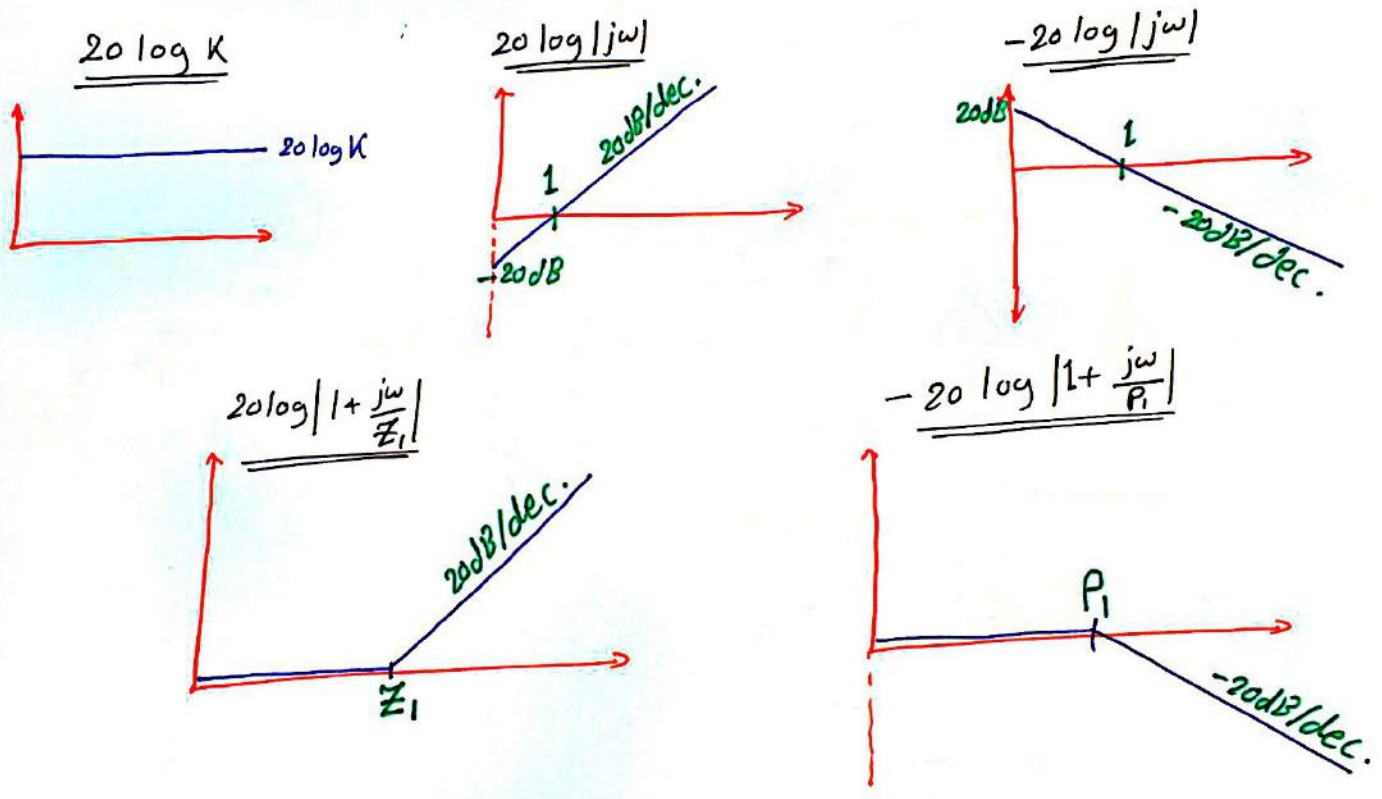

⇒ Drawing $\angle H_V(\omega)$:

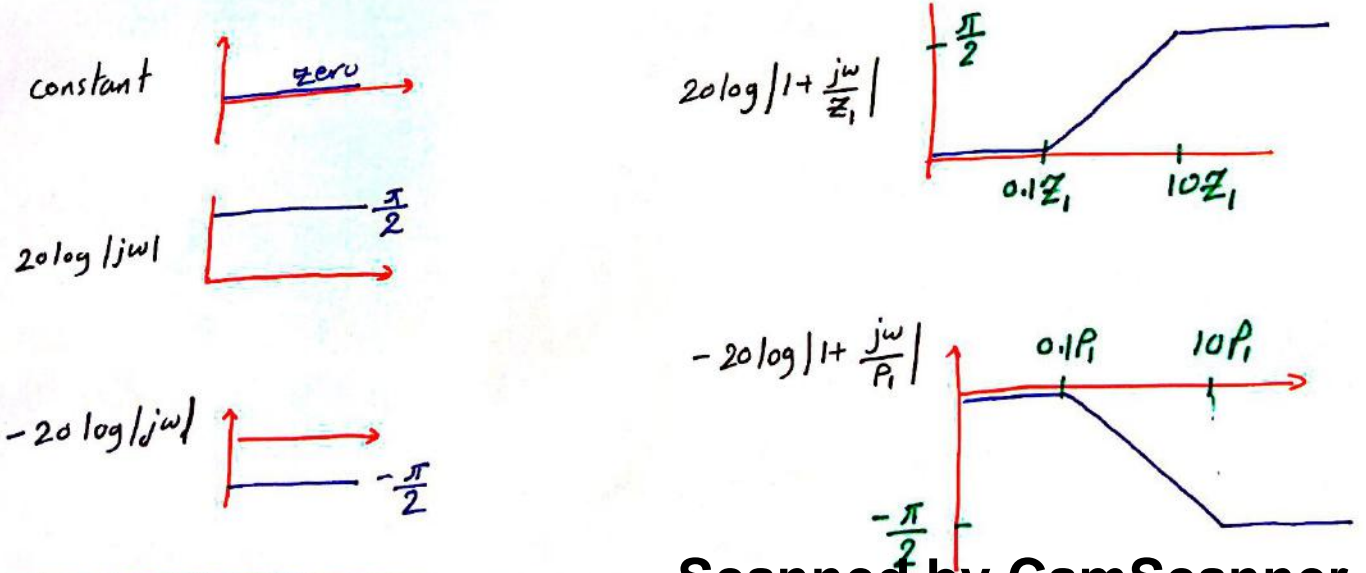


✱ CHAPTER (19):


✱ Z-parameters:

* $I_2 = 0$: $Z_{11} = \frac{V_1}{I_1}$
 * $I_1 = 0$: $Z_{22} = \frac{V_2}{I_2}$
 $Z_{21} = \frac{V_2}{I_1}$ $Z_{12} = \frac{V_1}{I_2}$

* equivalent ckt for 2-port network:

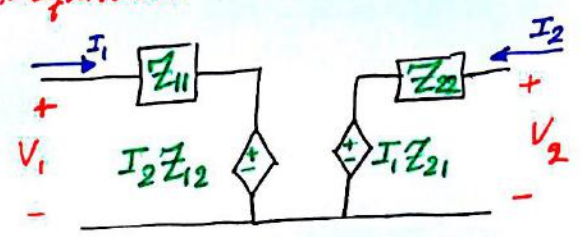


* special case: (reciprocal)

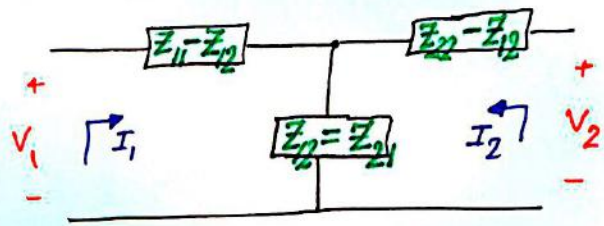


✱ Y-parameters:

* $V_2 = 0$: $Y_{11} = \frac{I_1}{V_1}$
 * $V_1 = 0$: $Y_{22} = \frac{I_2}{V_2}$
 $Y_{21} = \frac{I_2}{V_1}$ $Y_{12} = \frac{I_1}{V_2}$

* equivalent ckt for 2-port network:

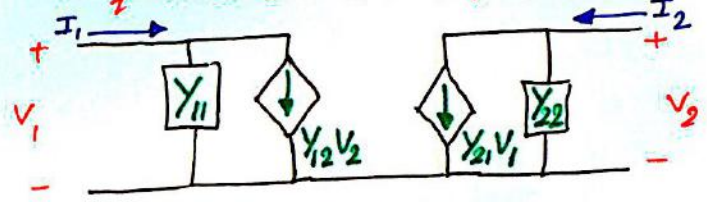

* special case: (reciprocal)

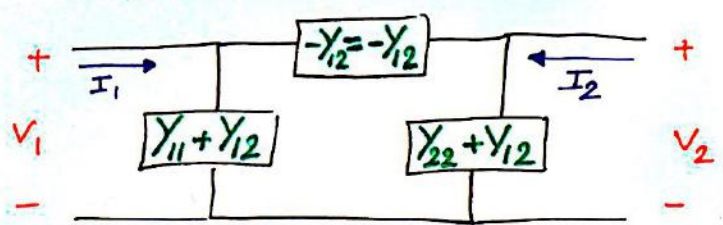

* Z_{in} & Z_{out} :

$Z_{in} = \frac{V_1}{I_1}$

$Z_{out} = Z_{22} - \frac{Z_{12} Z_{21}}{Z_{11} + Z_g}$

GOOD

LUCK

