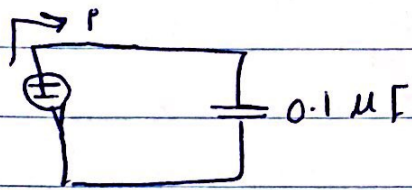


① Calculate $i_c(t)$ when $v_c(t) = 5(1 - e^{t/10^{-6}})$
and $C = 0.1 \mu F$



$$i_c(t) = C \frac{dv_c(t)}{dt} = 0.1 \times 10^{-6} \times \frac{d}{dt} 5(1 - e^{t/10^{-6}})$$

$$= 0.1 \times 10^{-6} (5 + e^{-t/10^{-6}})$$


② Calculate the inductor voltage when
 $i_L(t) = 20t e^{-2t}$ and $L = 0.1 H$



$$v_L(t) = L \frac{di_L(t)}{dt} = 0.1 [20e^{-2t} - 40t e^{-2t}]$$

$$= 2e^{-2t} - 4t e^{-2t} \text{ volt}$$

13/9/2018

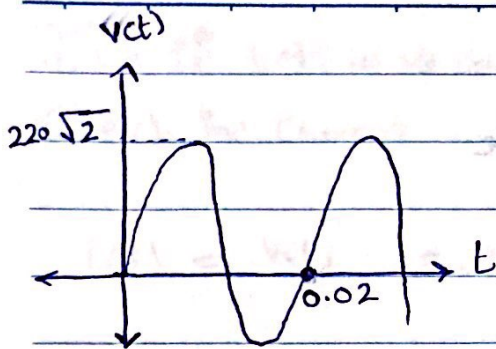

$f = 50 \text{ Hz}$

$T = \frac{1}{f} = \frac{1}{50}$


$v(t) = 220\sqrt{2} \sin(\omega t + 0) \equiv 220\sqrt{2} \cos(\omega t + 0) \quad R=5$

$i(t) = 44\sqrt{2} \sin(\omega t + 0) \quad R=2$

$i(t) = 110\sqrt{2} \sin(\omega t + 0) \quad L = 0.1 \text{ L}$

$i(t) = 10 \cos(\omega t - \frac{\pi}{6})$

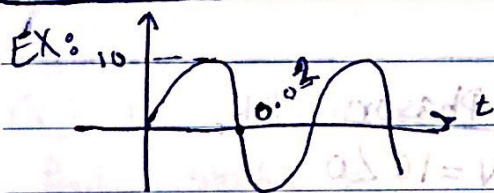$v(t) = 132 \times 10^{-3} \sqrt{2} \sin(\omega t + 0)$




$t = 0 \rightarrow 0$

$t = 0.015 \rightarrow -10$

$t = 0.05 \rightarrow 10$

$t = 0.02 \rightarrow 0$

Phasor:

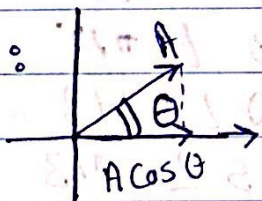




The real value of a phasor is the projection on x-axis

*We will be using $[\cos]$.

$e^{j\theta} = \cos\theta + j \sin\theta$

$\text{Re} \{ e^{j\theta} \} = \cos\theta$

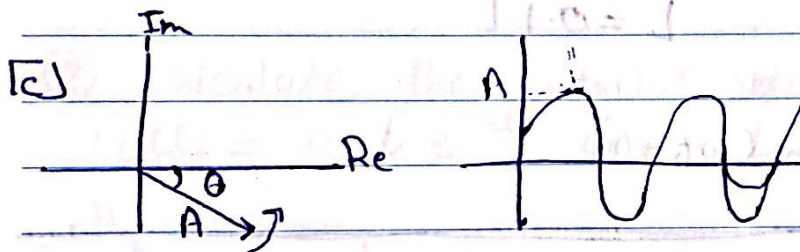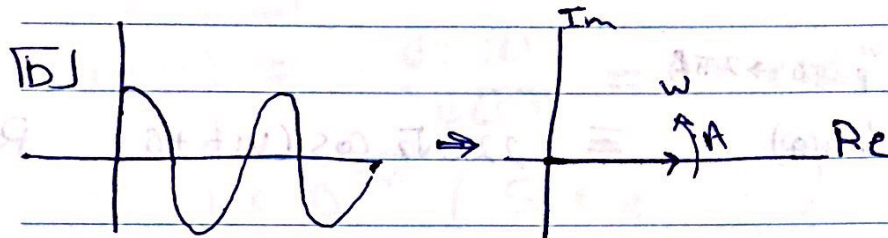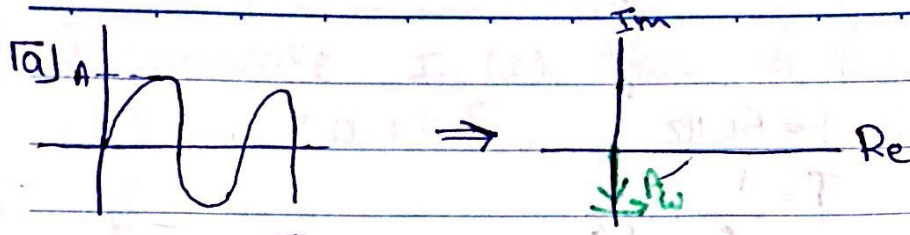$\text{Im} \{ e^{j\theta} \} = \sin\theta$





<u>Time</u>	<u>Phasor</u>
$v(t) = 10 \cos(\omega t)$	$V = 10 \angle 0$
$v(t) = 5 \cos(\omega t - \pi/3)$	$V = 5 \angle -\pi/3$
$i(t) = 3 \cos(\omega t + \pi/4)$	$I = 3 \angle \pi/4$
$v(t) = 10 \sin(\omega t)$	$V = 10 \angle -\pi/2$
$i(t) = 5 \sin(\omega t + \pi/3)$	$I = 5 \angle -\pi/3$

<u>Time</u>	<u>Phasor</u>
R	R
L	$j\omega L$
$v_L(t) = L \frac{di(t)}{dt}$	$V_L = j\omega L I$
C	$1/j\omega C$
$i_C(t) = C \frac{dv_C(t)}{dt}$	$I = j\omega C V$

[EX] if $v(t) = 10 \cos \omega t$, $\omega = 1$, $R = 10$, Find θ
 Sketch the current

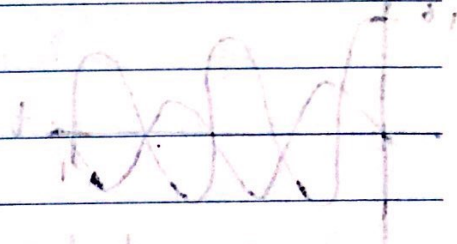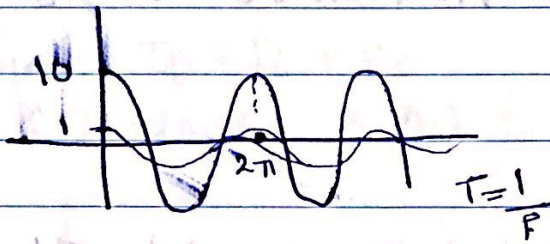
$$i(t) = \frac{v(t)}{R} = \cos \omega t \quad P = \frac{W}{2\pi}$$




- How to differentiate between the leading and lagging?
 → check 2 rising or falling edges and check which one reaches the x-axis first

[EX] if $v(t) = 10 \cos(\omega t)$, $\omega = 1$, $C = 0.1$
 Find & sketch $v(t)$
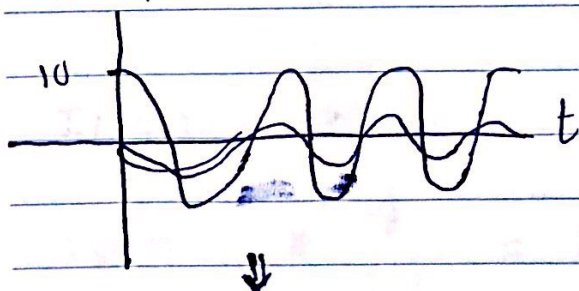
$$i_c(t) = C \frac{dv_c(t)}{dt} = -0.1 * 10 * \sin \omega t = -\sin \omega t$$



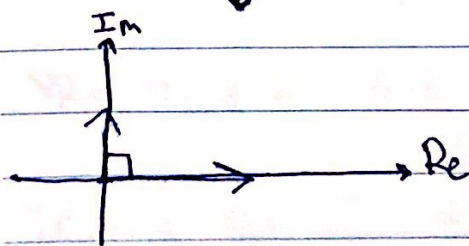in the capacitor, the current leads the voltage by $\pi/2$




Ex] Let $v(t) = 10 \cos \omega t$, $\omega = 1$, $L = 10$


Find & sketch $i(t)$

$$v(t) = L \frac{di(t)}{dt} \quad , \quad i(t) = \frac{1}{L} \int_0^t v(\tau) d\tau$$
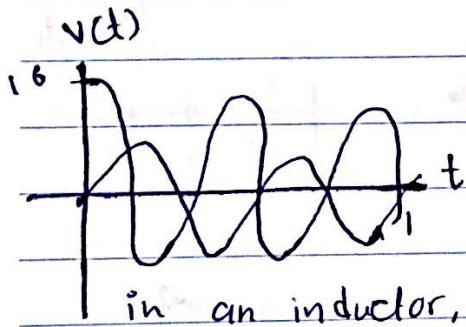
$$= 0.1 \times 10 \times \sin \omega t = \sin \omega t$$




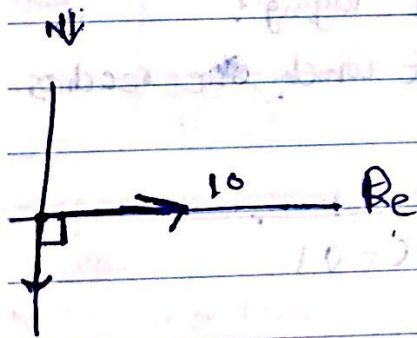in an inductor, the voltage leads the current by $\pi/2$




23/9/2018

EX] Draw all Phasors

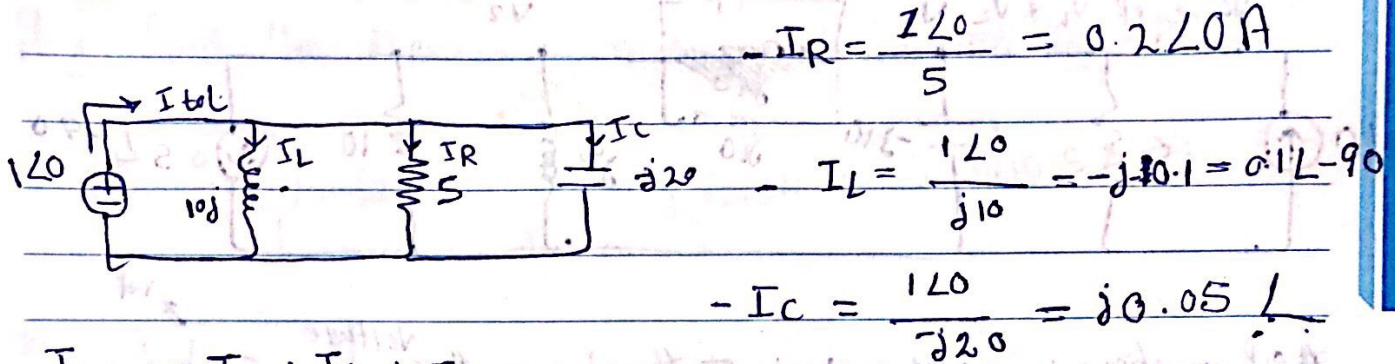


$$I_{\text{Total}} = I_R + I_L + I_C$$
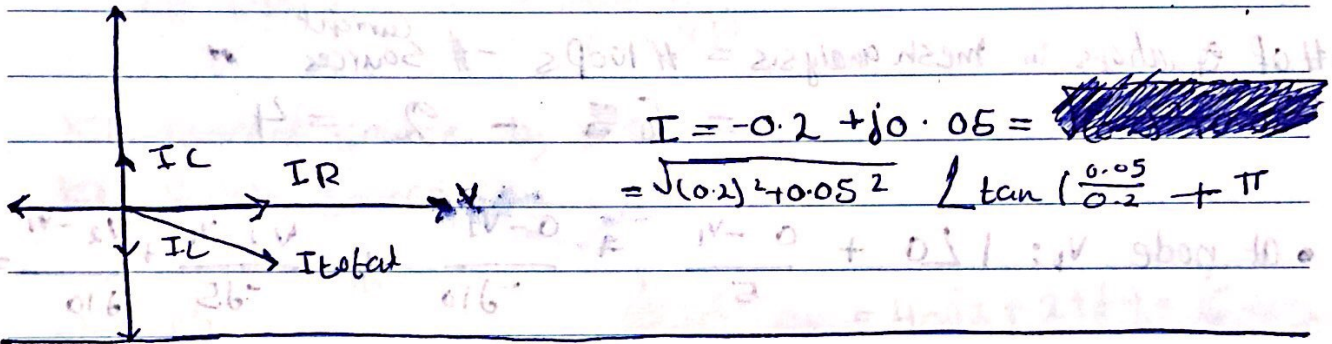
$$= 0.2 - j0.05 \approx 0.2 \angle -14^\circ$$



EX] Draw all Phasors

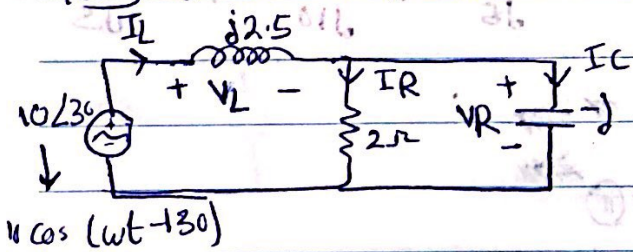


$$I_L = I_R + I_C$$

$$I_R = I_L \times \frac{-j}{2-j} = 2.56 \angle -110^\circ$$

$$V_R = I_R \times R = 5.2 \angle -110^\circ \quad \left\{ \begin{array}{l} V_C = V_R \\ V_L = j2.5 \times I_L = V_S - V_R \\ = 14.3 \angle 43.25^\circ \end{array} \right.$$

$$I_C = I_L - I_R = \frac{V_C}{-j} = 5.12 \angle -20^\circ$$

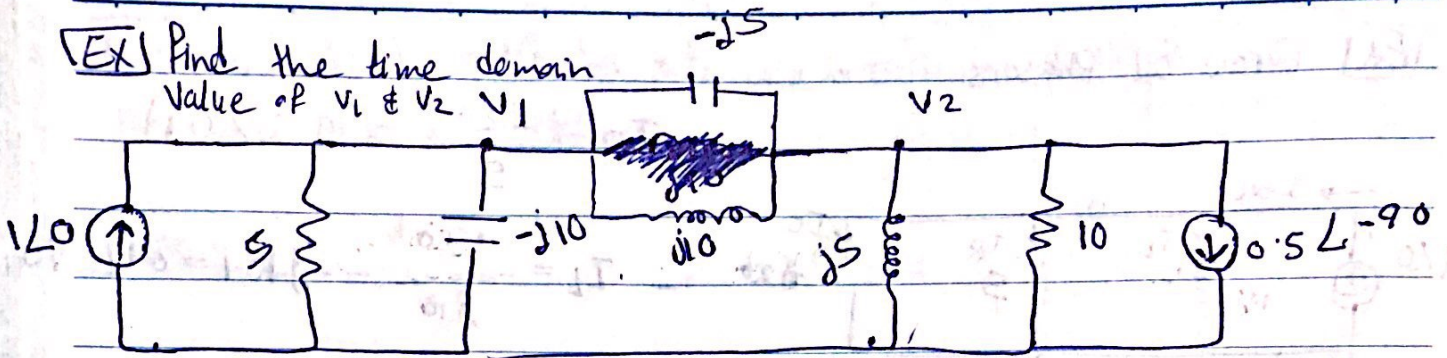EX) Find the time domain value of v_1 & v_2



$$\begin{aligned} \# \text{ of equations in nodal analysis} &= \# \text{ nodes} - \# \text{ voltage sources} - 1 \\ &= 3 - 0 - 1 = 2 \end{aligned}$$

$$\begin{aligned} \# \text{ of equations in mesh analysis} &= \# \text{ loops} - \# \text{ current sources} \\ &= 6 - 2 = 4 \end{aligned}$$

$$\bullet \text{ at node } v_1: 120 + \frac{0 - v_1}{5} + \frac{0 - v_1}{-j10} + \frac{v_2 - v_1}{-j5} + \frac{v_2 - v_1}{j10} = 0$$

$$\bullet \text{ at node } v_2: -0.5 \angle -90 + \frac{0 - v_2}{10} + \frac{v_2}{j5} + \frac{v_1 - v_2}{j10} + \frac{v_1 - v_2}{-j5} = 0$$

$$v_1 = 1 - j2 = \sqrt{5} \angle \tan^{-1} \frac{-2}{1}$$



$$v_2 = -2 + j4 = \sqrt{20} \angle \tan^{-1} \frac{4}{-2} + \pi$$

$$v_1(t) = 2.24 \cos(\omega t - 63.4)$$



$$v_2(t) = 4.47 \cos(\omega t + 116)$$

25/9/2018

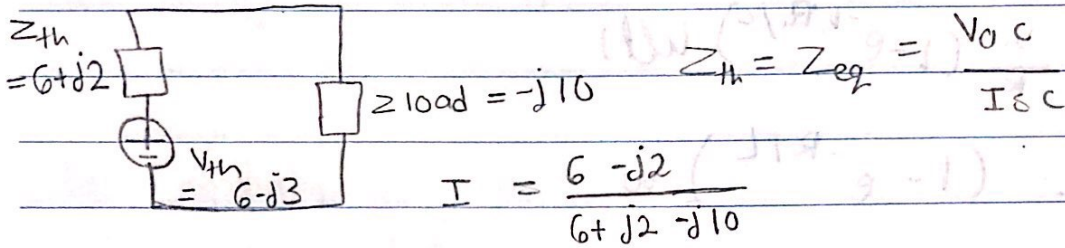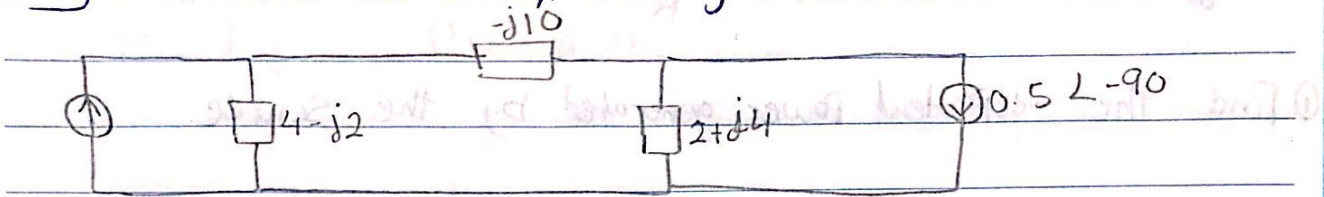[Ex] Find the thevinin eq seen by the $(-j10)$ element



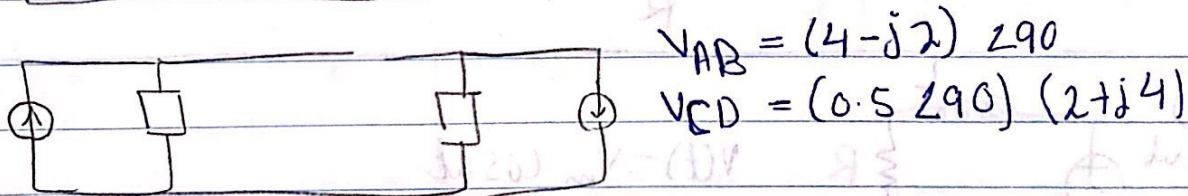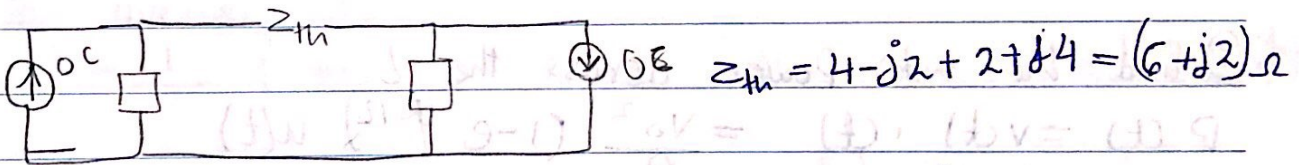Kill current source by $0 \cdot \infty$
 Kill Voltage source by S.C



* Instantaneous P


$$P(t) = v(t) I(t) = \frac{v(t)^2}{R} = I(t)^2 R$$

$$L = v(t) \text{ and } i(t)$$

$$P(t) = v(t) I(t) = \frac{L di(t)}{dt} * i(t) = v(t) * \frac{1}{L} \int_0^t v(\tau) d\tau$$

~~$v(t)$~~

[Ex]

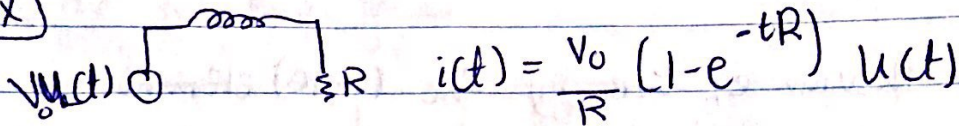

① Find the independent Power generated by the source

$$P_{ct} = v_{ct} i(t)$$
$$= V_0 u(t) * \frac{V_0}{R} (1 - e^{-tR/L}) u(t)$$

$$P(t) = \frac{V_0^2}{R} (1 - e^{-R/L}) w$$


② Find instantaneous p across the resistor:

$$P_{ct} = I(t) v_{ct} = I^2(t) R = \frac{V_0^2}{R} (1 - e^{-tR/L})^2 R u(t)$$

③ Find the inst. Power across the L

$$P_{ct} = v_{ct} i(t) = \frac{V_0^2}{R} (1 - e^{-tR/L}) u(t)$$

[Ex]

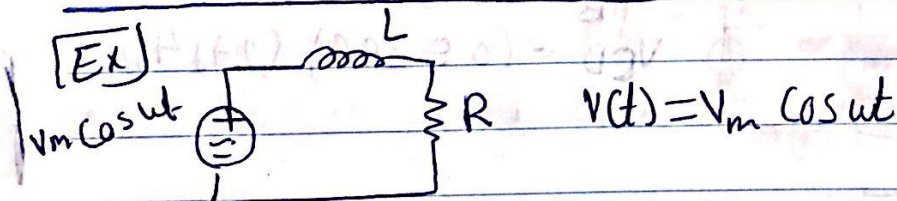

Find the ins. power by the source

$$P_{ct} = v_{ct} i(t) = V_m \cos wt * I_m \cos (wt + \theta)$$
$$= \frac{V_m I_m}{2} [\cos (2wt + \theta) + \cos(\theta)]$$

$$\cos x \cos y = \frac{1}{2} [\cos (x+y) + \cos (x-y)]$$

• Average Power: (a) accurate (b) representation

$$P = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} P(t) dt$$

$$P_{avg} = \frac{1}{T} \int_0^T P(t) dt$$

let suppose / any elements

$$v(t) = V_m \cos(\omega t + \theta)$$

$$i(t) = I_m \cos(\omega t + \phi)$$

The average power:

$$P = \frac{1}{T} \int_0^T v(t) i(t) dt = \frac{1}{T} \int_0^T V_m I_m \cos(\omega t + \theta) \cos(\omega t + \phi) dt$$

$$= \frac{1}{T} \int_0^T \frac{V_m I_m}{2} [\cos(2\omega t + \theta + \phi) + \cos(\theta - \phi)] dt$$

$$= \frac{1}{T} \frac{V_m I_m}{2} \int_0^T \cos(2\omega t + \theta + \phi) dt + \frac{1}{T} \left(\frac{V_m I_m}{2} \cos(\theta - \phi) \right) \int_0^T dt$$

$$= \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(\theta - \phi) dt$$

27/19/2018

* For sinusoidal signals:

$$P_{avg} = \frac{V_m - I_m}{2} \cos(\theta - \phi)$$

[EX] if $v(t) = 4 \cos(\frac{\pi}{4} t)$ and $Z = 2 \angle -60^\circ$
Find the average $v = 4 \angle 0^\circ$?

$$I = \frac{V}{Z} = \frac{4 \angle 0^\circ}{2 \angle -60^\circ} = 2 \angle -60^\circ = 2 \cos(\frac{\pi}{4} t - 60^\circ)$$

$$P_{avg} = \frac{4 \times 2}{2} \cos(\theta + 60^\circ) = 2 \text{ W}$$

$$p(t) = v(t) i(t)$$

$$= 4 \cos(\frac{\pi}{4} t) \times 2 \cos(\frac{\pi}{4} t - 60^\circ) = 4 [\cos(\frac{\pi}{2} t - 60^\circ + \cos(60^\circ))]$$
$$= 2 + 4 \cos(\frac{\pi}{2} t - 60^\circ)$$


* For a pure resistive loads

$$P_{avg} = \frac{V_m - I_m}{2} = \frac{V_m^2}{2R} = \frac{1}{2} I_m^2 R \quad \text{real average power}$$

شکل حقیقی

* For a L and C : $P_{avg} = 0$ شکل صفر

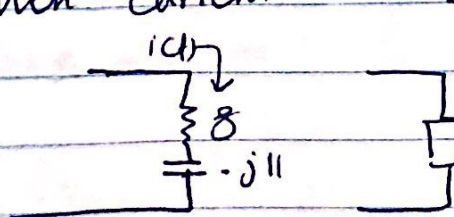
[EX] Find the average real power absorbed by $Z = 8 - j11$
when current $I = 3 + j4$ access through it



$$i = (3 + j4) \text{ A} = \sqrt{3^2 + 4^2} \angle \tan^{-1} \frac{4}{3}$$

$$P = \frac{1}{2} I_m^2 R = \frac{1}{2} \times 5^2 \times 8 = 100 \text{ watt}$$

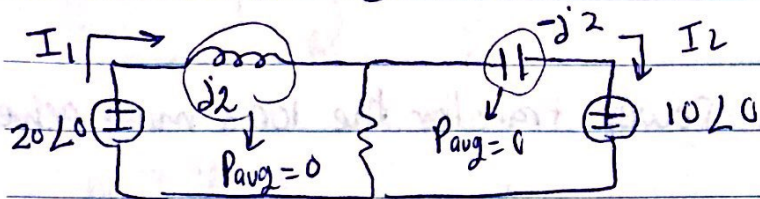EX) Find the real avg. power consumed / generated from elements or sources



Nodal analysis:

$$\frac{20 \angle 0 - V_0}{j2} + \frac{-V_0}{2} + \frac{10 - V_0}{-j2} = 0$$

$$V_0 = 10 \angle -90 \rightarrow V_0 = -j10 \text{ V}$$

$$P_{avg} (W) = \frac{1}{2} \frac{V_m^2}{2} = \frac{1}{2} \times \frac{10^2}{2} = 25$$


$$I_r = \frac{20 \angle 0 - 10 \angle -90}{-j10} = 11.18 \angle 63.43$$

$$P_{avg} = \frac{20 \times 11.18}{2} \cos(0 + 63.43) = 50$$

$$I_2 = \frac{10 \angle -90 - 10 \angle 0}{-j10} = 7.07 \angle -45$$

$$P_{avg} = \frac{1}{2} \times 10 \times 7.07 \cos(0 + 45) = 25 \text{ watt (dissipated)}$$

* maximum power transfer:

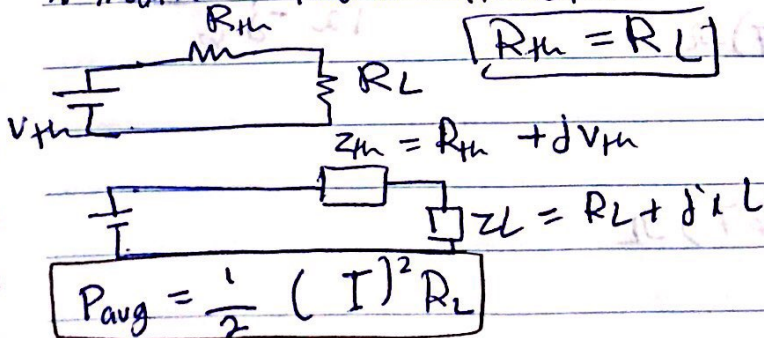

$$I = \frac{V_{th}}{R_{th} + Z_L}$$


$$I = \frac{V_{th}}{\sqrt{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}}$$

$$\angle \phi_{th} - \tan^{-1} \left(\frac{X_{th} + X_L}{R_{th} + R_L} \right)$$

$$\frac{\partial P_{avg}}{\partial R_L} \Rightarrow R_L = R_{th} \quad \frac{\partial P_{avg}}{\partial X_L} \Rightarrow X_L = -X_{th}$$

* conclusion for maximum power transfer the load must achieve $Z_L = Z_{th}^*$
 $I = 0$ $L+ \rightarrow L-$

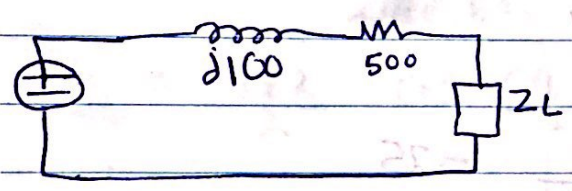
[Ex] Find the value of ~~the~~ Z_L that maximized the maximum Power transfer



$$Z_L = Z_{th}^*$$


$$Z_L = 500 - j100$$

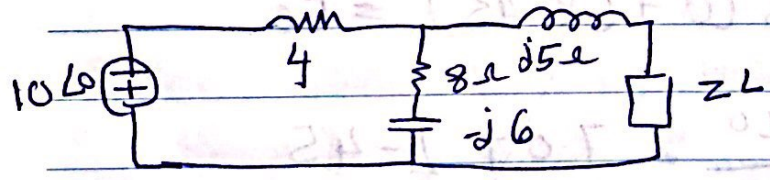[Ex] Determine the load impedance Z_L that maximized the average real power & find the power value



$$Z_L = Z_{th}^*$$
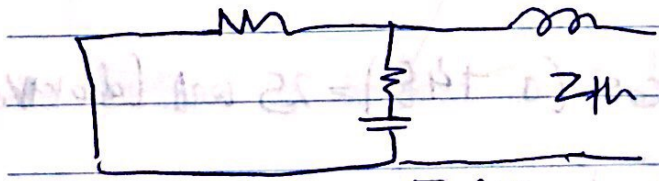
$$Z_{th} = Z_{eq} \text{ after killing sources}$$




$$Z_{th} = j5 + [4 \parallel (8 - j6)] = j5 + \frac{4(8 - j6)}{12 - j6}$$


$$= (2.933 + j4.467) \Omega$$

$$Z_L = (2.933 - j4.467) \Omega$$

$$Z_{th} = 2.933 + j4.467$$

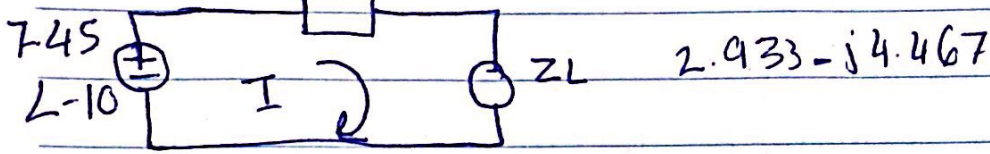

$$V_{th} = V_{oc}$$

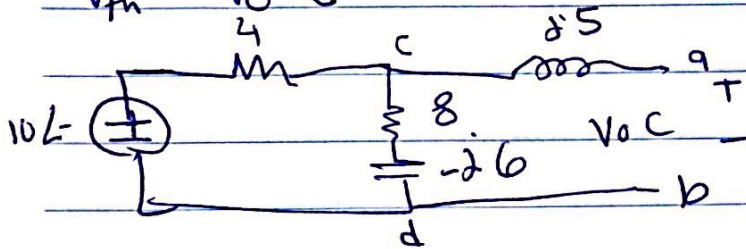

$$V_{ab} = V_{cd} = \frac{8 - j6}{12 - j6} \times 10 \angle 0$$

$$P_{avg} = \frac{1}{2} \times I^2 \times 2.933$$

$$I = \frac{7.45 \angle -10.3}{2.933 \times 2} = 1.27 = 1.27 \angle -10.3$$

$$P_{avg} = \frac{1}{2} (1.27)^2 \times 2.933 = 2.36$$

inolt = V(

20/9/2018

* In general:


$$- P_{avg} \rightarrow P(t) = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$

$$P = \frac{1}{T} \int_0^T P(t) dt$$

$\hookrightarrow = i(t) * v(t)$

$$- P_{inst} \rightarrow P(t) = \frac{1}{2} V_m I_m \cos(\theta - \phi) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta + \phi)$$

* Source with multiple Freq:

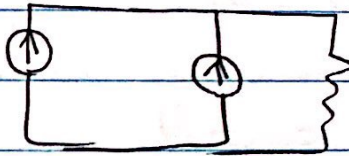

[Ex] $i(t) = 3 \sin 2t + 4 \sin 10t$
 $R = 1$, Find P_{avg}

$$P_{avg} = \frac{1}{T} \int_0^T P(t) dt = \frac{1}{T} \int_0^T i^2(t) * R dt = \frac{1}{T} \int_0^T (3 \sin 2t + 4 \sin 10t)^2 dt$$

$$= \frac{1}{T} \int_0^T 9 \sin^2 2t + 24 \sin 2t \sin 10t + 16 \sin^2 10t dt$$

$$= \frac{1}{T} \int_0^T \left(9 * \frac{1}{2} + 16 * \frac{1}{2} \right) dt = \frac{1}{2} [9 + 16] = 12.5$$

* For Sinoidal signals with multiple Frequencies

$$i(t) = I_{m1} \cos \omega_1 t + I_{m2} \cos \omega_2 t + \dots + I_{mn} \cos \omega_n t$$

$$P_{avg} = \frac{1}{R} [I_{m1}^2 + I_{m2}^2 + \dots + I_{mn}^2]$$

$$OR = \frac{1}{2} \frac{V_{m1}^2 + V_{m2}^2 + \dots + V_{mn}^2}{R}$$

Ex] ① $i(t) = 2 \cos 10t - 3 \cos 20t$, $R = 4$, find P_{avg}

$$P_{avg} = \frac{1}{2} \times 4 \times (4+9) = 26 \text{ W}$$

② $v(t) = 3 \cos \omega_1 t + 4 \sin \omega_2 t$, $R = 2$, find P_{avg}

$$P_{avg} = \frac{1}{2} \times \frac{(9+16)}{2} = \frac{25}{2} = 6.25 \text{ W}$$

③ $i(t) = 3 \cos 10t - 5 \cos 10t$, $R = 1$, find P_{avg}
 $= -2 \cos 10t$

$$P_{avg} = \frac{1}{2} \times (2)^2 \times 1 = 2 \text{ W}$$

④ $i(t) = 5 + 4 \cos \omega t$, $R = 1$, find P_{avg}

$$P_{avg} = (5)^2 + \frac{1}{2} \times 4^2 \times 1 = 33 \text{ W}$$

note: DC power $\rightarrow (I^2 R)$ [no $\frac{1}{2}$ in DC]

AC power $\rightarrow \frac{1}{2} I^2 R$ or $\frac{1}{2} \frac{V^2}{R}$

⑤ $v(t) = 3 \cos \omega t + 4 \sin \omega t$, $R = 2$, $P_{avg}?$

$$= 3 \angle 0 + 4 \angle -90 = 3 - j4 \Rightarrow 5 \angle -53$$


$$P_{avg} = \frac{1}{2} \frac{V^2}{R} = \frac{1}{2} \frac{(25)}{2} = 6.25 \text{ W}$$

⑥ $v(t) = 3 \cos \omega t + 4 \cos(\omega t - \pi/3)$


$$= 3 \angle 0 + 4 \angle -\pi/3 = 5 - j3.5 \Rightarrow 6.1 \angle -35$$

$$P_{avg} = \frac{1}{2} \times \frac{(6.1)^2}{R}$$


* Effective Values:

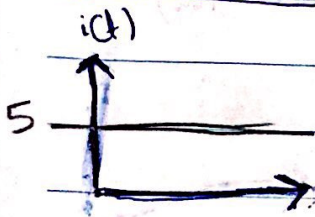



$$P_{avg} = 5^2 R$$

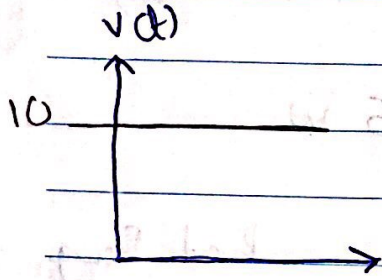


$$P_{avg} = 10^2 / R$$

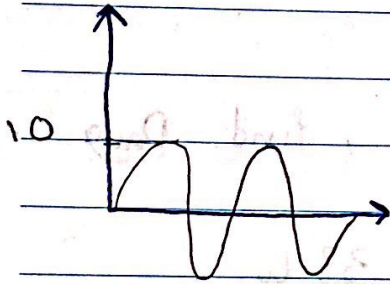


$$P_{avg} = 10^2 / 2R$$

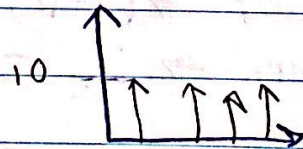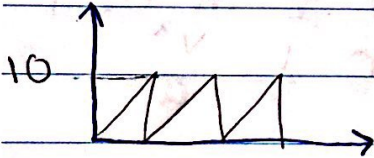


$$P_{avg} \neq \frac{10^2}{2R}$$

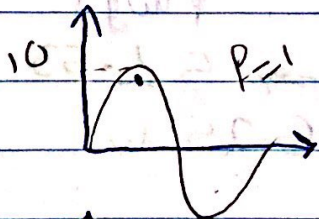

$$P_{avg} = \frac{10^2}{2R}$$

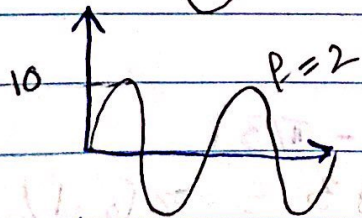

$$P_{avg} = \frac{10^2}{2R}$$

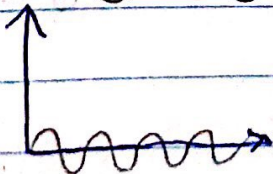


$$P_{avg} = \frac{1}{2} R$$

* Find the RMS (effective) value of:

$$i(t) = I_m \cos(\omega t + \phi)$$

$$I_{RMS} = I_{eff} = \sqrt{\frac{1}{T} \int_0^T I^2 \cos^2(\omega t + \phi) dt}$$
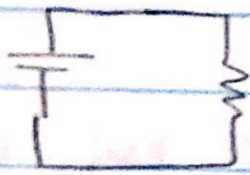
$$= \sqrt{\frac{1}{T} \int_0^T \frac{I_m^2}{2} dt} = \frac{I_m}{\sqrt{2}}$$




$$P = \frac{V_{DC}}{2}$$

$$P = \frac{1}{T} \int_0^T \frac{v^2(t)}{R} dt$$



$$\frac{V_{DC}^2}{R} = \frac{1}{T} \int_0^T \frac{v^2(t)}{R} dt$$
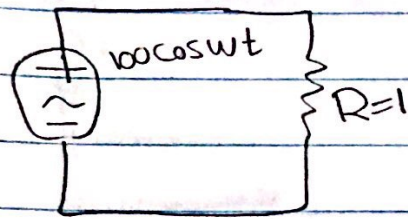
$$V_{eff} = V_{DC} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$



$$P_{avg} = 5000 \text{ W} \quad \frac{V_{DC}^2}{R=1} = 5000$$

$$V_{DC} = \sqrt{5000} = 70.7$$

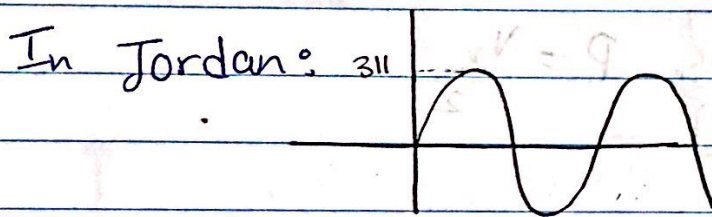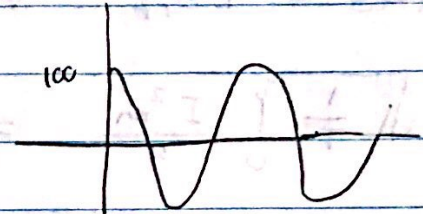

- For a sinusoidal signal:

$$P_{avg} = \frac{I_m V_m}{2} \cos(\theta - \phi) = I_{rms} V_{rms} \cos(\theta - \phi)$$

- For a resistor:

$$P_{avg} = \frac{V_m I_m}{2} = \frac{V_m^2}{2R} = \frac{1}{2} I_m^2 R$$

$$= V_{rms} I_{rms} = \frac{V_{rms}^2}{2} = I_{rms}^2 R$$

* Effective value: $V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$



• For sinusoidal:

$$V_{rms} = V_m / \sqrt{2}$$

$$I_{rms} = I_{Peak} / \sqrt{2}$$

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi) = V_{rms} I_{rms} \cos(\theta - \phi)$$

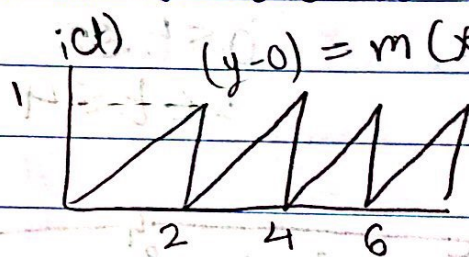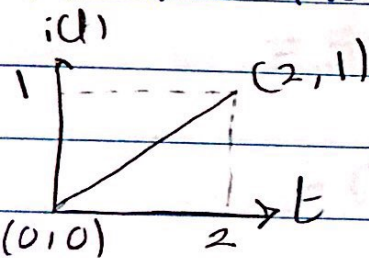Ex: Find the avg power delivered to (5 Ω) resistor



$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi) = I_{rms}^2 R$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} \quad (T=2)$$

$$i(t) = \frac{1}{2} t \quad 0 \leq t \leq 2$$

$$I_{rms} = \sqrt{\frac{1}{2} \int_0^2 \left(\frac{1}{2} t\right)^2 dt} = \sqrt{\frac{1}{2} \int_0^2 \frac{1}{4} t^2 dt}$$

$$= \sqrt{\frac{1}{2} \left(\frac{1}{12} t^3\right)} = \frac{1}{\sqrt{3}} \text{ A}$$

$$P_{avg} = 5 * \frac{1}{3} \text{ W}$$

• For sawtooth functions:


$$V_{rms} = V_m / \sqrt{3} \quad , \quad I_{rms} = I_m / \sqrt{3}$$

[Ex] Find the rms values:

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$T = 4$$

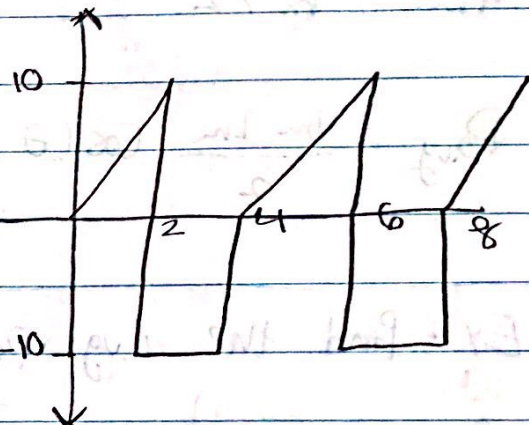
$$v(t) = \begin{cases} 5t & 0 \leq t \leq 2 \\ -10 & 2 \leq t \leq 4 \end{cases}$$



$$V_{rms} = \sqrt{\frac{1}{4} \left(\int_0^2 25t^2 dt \right) + \int_2^4 100 dt}$$


$$= \sqrt{\frac{1}{4} \left(\frac{25}{3} t^3 \Big|_0^2 + 100(2) \right)} = 8.165 \text{ V}$$

Examples to find RMS:

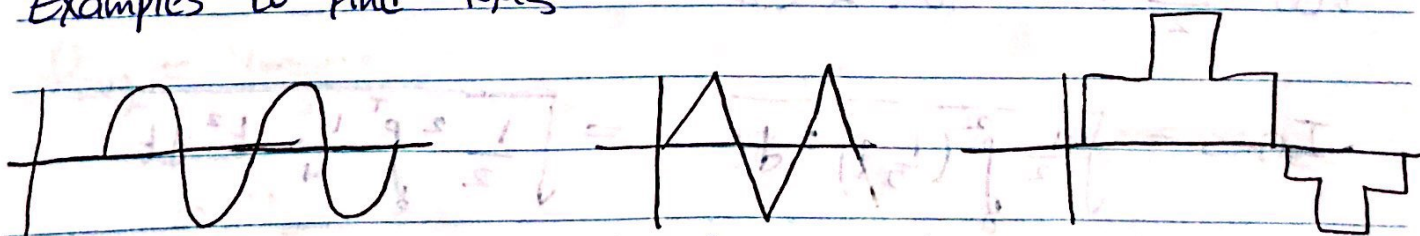

* Source with multiple freq: $v(t) = 3 \cos \omega_1 t + 4 \cos \omega_2 t$, find rms
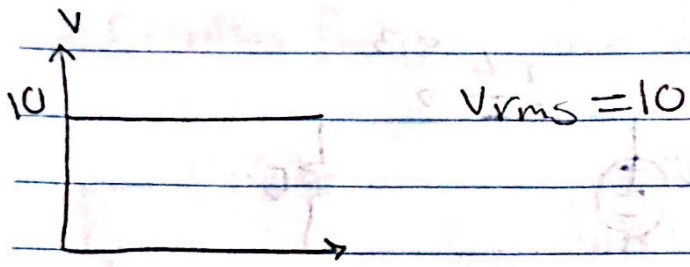
$$V_{rms} = \sqrt{(V_{rms1})^2 + (V_{rms2})^2 + \dots} = \sqrt{\left(\frac{3}{\sqrt{2}}\right)^2 + \left(\frac{4}{\sqrt{2}}\right)^2}$$



$$i(t) = 5 + 4 \sin(\omega t - \pi/3) \quad \text{Find } I_{\text{rms}}$$

$$v(t) = 5 \cos \omega t + 3 \cos(\omega t - \pi/3)$$


$$= 5 \angle 0 + 3 \angle -\pi/3$$

$$= 5 + j0 + 3 \cos(-\pi/3) + j3 \sin(-\pi/3) =$$


$$= 6.5 - j \frac{3\sqrt{3}}{2} = \sqrt{(6.5)^2 + \left(\frac{3\sqrt{3}}{2}\right)^2} \angle \tan^{-1}\left(\frac{\frac{3\sqrt{3}}{2}}{6.5}\right)$$

$$\boxed{V_{\text{rms}} = \frac{V_{\text{Peak}}}{\sqrt{2}}}$$

* Power Factor

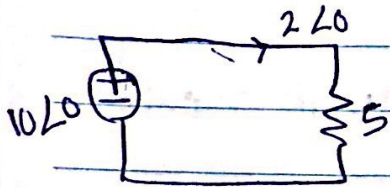
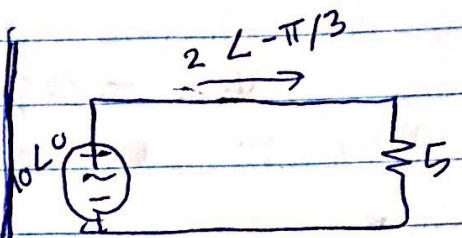
$$P_{avg} = \frac{V_m I_m}{2} = \frac{10 \times 2}{2} = 10W$$



$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi) = \frac{10 \times 2}{2} \cos(0 - \pi/3) = 5W$$


The Power Factor represents the loss in the circuit

$$PF = \frac{\text{Real Power}}{\text{apparent power}} = \frac{V_{rms} I_{rms} \cos(\theta - \phi)}{V_{rms} I_{rms}} = \cos(\theta - \phi)$$

$$0 \leq PF = \cos(\theta - \phi) \leq 1, \quad [\text{For } R \quad \cos(\theta - \phi) = 1, \quad PF = 1]$$

$$\text{For } L/C \quad \cos(\theta - \phi) = 0, \quad PF = 0$$

L & R

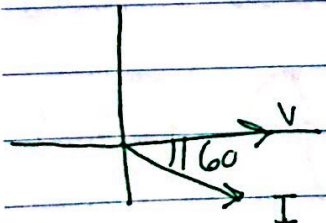


$$PF = \cos(0 + 60) = 0.5$$

lagging

(I lags V) → inductive load

C & R

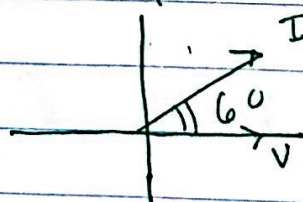


$$PF = \cos(0 - 60) = +0.5$$

Leading


(I leads V) → capacitive load

* Example: Find the source PF

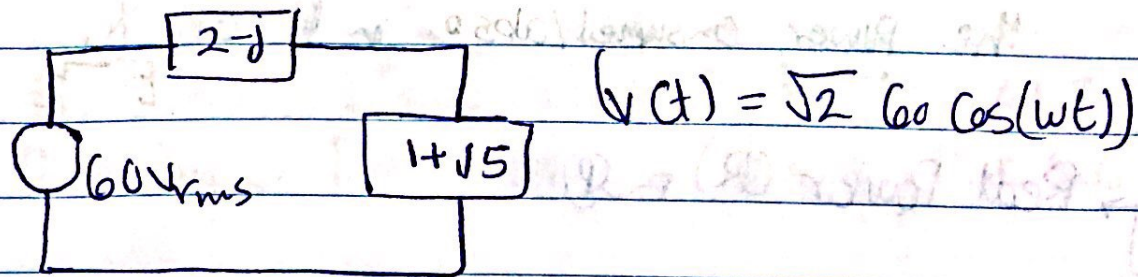

• $PF_{\text{source}} = \cos(\theta - \phi) = \cos(0 - 53.13) = 0.6$ lagging (I lags V)

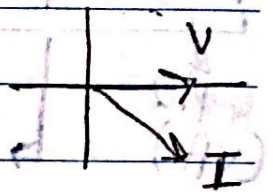• $I = \frac{60 \angle 0}{2 - j + 1 + j5} = 12 \angle -53.13 \text{ Arms}$



$P_{\text{avg}} = (2 - j) = (12)^2 * 2$

$P_{\text{avg}} = (1 + j5) = (12)^2 * 1$

4/10/2018

*Complex Power: This concept is introduced to represent the power consumed/stored in R or X.

⑤ → complex }
→ Real Power (R) $\Rightarrow \text{P}$
→ Reactive Power (L, C) $\Rightarrow \text{Q}$

$$S = P + jQ$$

Complex (VA)

→ Power (real Power (W))
→ Reactive Power (VAR) volt ampere reactive

$$\Rightarrow x = 5 \cos \theta$$

$$z = 5 e^{j\theta} = 5(\cos \theta + j \sin \theta)$$

$$x = \operatorname{Re}\{z\}$$

$$P = |V_{\text{rms}}| |I_{\text{rms}}| \cos(\theta - \phi)$$

$$e^{j(\theta - \phi)} = \cos(\theta - \phi) + j \sin(\theta - \phi)$$

$$= |V_{\text{rms}}| |I_{\text{rms}}| \operatorname{Re}\{e^{j(\theta - \phi)}\}$$

$$\cos(\theta - \phi) = \operatorname{Re}\{e^{j(\theta - \phi)}\}$$

$$= \operatorname{Re}\{|V_{\text{rms}}| |I_{\text{rms}}| e^{j(\theta - \phi)}\}$$

$$P = \operatorname{Re}\{S\}, \quad Q = \operatorname{Im}\{S\}$$

$$= \operatorname{Re}\{V_{\text{rms}} e^{j\theta} \# I_{\text{rms}} e^{-j\phi}\}$$

$$= \operatorname{Re}\{V \# I^*\}$$

$$S = \frac{1}{2} V_m I_m^*$$

$$S = V I^*$$

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$

• Suppose $V_{rms} = 10 \angle 30$

$$I_{rms} = 5 \angle 20$$

$$S = V_{rms} I_{rms}^* = 10 \angle 30 * 5 \angle -20 = 50 \angle 10 \text{ VA}$$

$$P = V_{rms} I_{rms} \cos(\theta - \phi) = 10 * 5 \cos(30 - 20)$$

• Suppose: Given Peak Values

$$V = 10 \angle 30, \quad I = 5 \angle 20$$

$$S = \frac{1}{2} V I^* = \frac{1}{2} * 10 \angle 30 * 5 \angle -20 = 25 \angle 10 \text{ VA}$$

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi) = \frac{1}{2} * 10 * 5 \cos(10)$$

• Suppose: $v(t) = 10 \cos(\omega t + 30)$

$$i(t) = 5 \cos(\omega t + 20)$$

$$P \rightarrow \text{Re}\{S\}, \quad Q \rightarrow \text{Im}\{S\}$$

$$S = V I^*$$

$$= |V_{rms}| \angle \theta \quad I_{rms} \angle -\theta$$

$$= |V_{rms}| |I_{rms}| \angle \theta - \theta$$

$$= |V_{rms}| |I_{rms}| e^{j\theta - \theta}$$


$$= |V_{rms}| |I_{rms}| (\cos(\theta - \theta) + j \sin(\theta - \theta))$$

$$= |V_{rms}| |I_{rms}| (\cos \theta - \theta) + j |V_{rms}| |I_{rms}| \sin(\theta - \theta)$$


$$S = P + jQ$$

$$P = |V_{rms}| |I_{rms}| \cos(\theta - \phi) \quad \text{W}$$

$$Q = |V_{rms}| |I_{rms}| \sin(\theta - \phi) \quad \text{VAR}$$

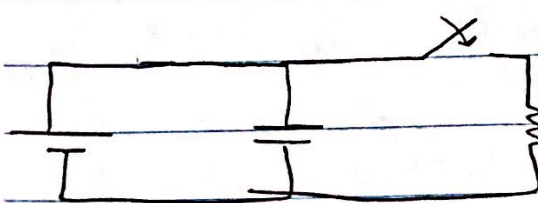

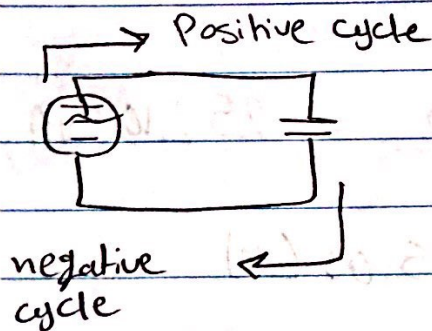P : real Power (heat in R)
 Q : Rate of change in stored energy
 caused for produce em waves



$$Z = R + jX$$

$$Z = \sqrt{R^2 + X^2} \angle \tan^{-1} \frac{X}{R}$$

$$X = |Z| \sin \theta, \quad R = |Z| \cos \theta$$

$$S = P + jQ$$

$$|S| = \sqrt{P^2 + Q^2} \angle \tan^{-1} Q/P$$

$$P = |S| \cos \theta$$


$$Q = |S| \sin \theta$$

Complex power is a phasor
(mag + angle)

Apparent Power: $|S| \rightarrow \text{VA}$

$$|S| = |V_{rms}| |I_{rms}|$$

Example :

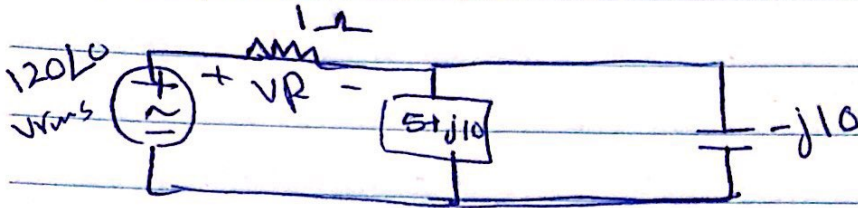

$$S = I^* V$$

$$I = \frac{120 \angle 0}{1 + \frac{(5 + j10) \parallel (-j10)}$$


$$I = \frac{120 \angle 0}{1 + \frac{100 - j5}{*}} = 5.16 \angle 25.46 \text{ A}$$

$$V_R = I R = (5.16 \angle 25.46) * I \text{ volt}$$

$$S(1\Omega) = V I^* = 5.16 \angle 25.46 * 5.16 \angle -25.46$$
$$= 26.6 \angle 0 = 266 + j0 \text{ VA}$$

• Example:

$$S = V I^k$$

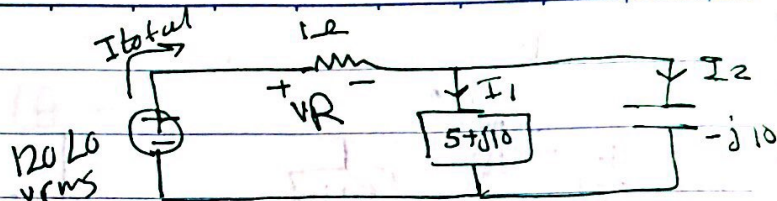

$$I = \frac{120 \angle 0}{1 + (5 + j10) \parallel (-j10)}$$

$$V_R = I R = (516 \angle 25.46) * I \text{ Volt}$$

$$S(LR) = V I = 516 \angle 25.46 * 5.16 \angle 25.46 = 26.2 \angle 0 = 266 + j0 \text{ VA}$$

For capacitor

$$I_2 = \frac{5 + j10}{5} * I_{total} = 11.53 \angle 88.9^\circ \text{ A}$$

$$V(-j10) = -j10 * I_2 = 115.3 \angle -1.1 \text{ V}$$

$$S = 115.3 \angle -1.1 * 11.53 \angle 88.9 = 1333.1 \angle -90 \text{ VA} = 0 - j1333 \text{ VA} = -j1333 \text{ VA}$$

For inductor

$$I_2 = I_{tot} - I_2 = 10.31 \angle -64.53 \text{ A}$$

$$V = V_{capacitor} = 115.3 \angle -1.1 \text{ V}$$

$$S = 115.3 \angle -1.1 * 10.31 \angle 64.53 = 531.5 + j1063 \text{ VA}$$

$$S'(\text{source}) = VI^* = 120 \angle 0^\circ * 5.16 \angle -25.46^\circ = 558 - j226 \text{ VA}$$

- Capacitor is ~~is~~ generated for ~~reactive~~ reactive power
- Inductor Consumed for reactive power
- Source \rightarrow Generated for real power
 \rightarrow ~~Consumed~~ for reactive power
- Resistor Consumed real Power

\ominus Generated


\oplus Consumed

-j1331 generated reactive power (For capacitor)

+j1063 Consumed reactive power (For inductor)


* PF correction:

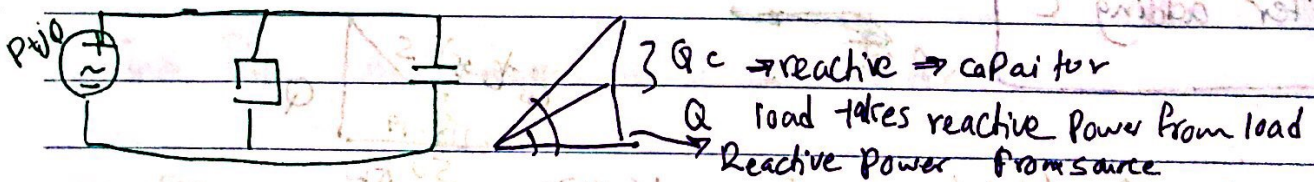Increasing the PF by installing a capacitive element in the circuit
 \Rightarrow should not affect the load voltage or current ($PF = \cos(\theta - \phi)$)



A Load of 50 kW with 0.8 lagging PF is supplied by a 230 V_{rms} source

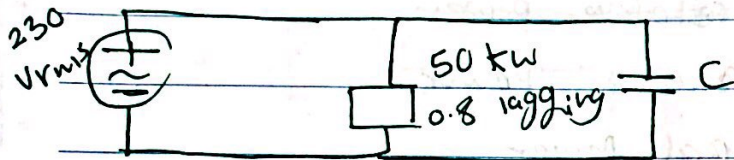it is required to increase the PF = 0.95 lagging



Add capacitor in parallel

Before adding C


$$P = S \cos 36.9 \quad \left. \begin{array}{l} \\ \tan 36.9 = Q/P \end{array} \right\} \begin{array}{l} Q = 37.5 \text{ kVAR} \\ S = 50 \end{array}$$

$$I_s = I_L \Rightarrow P = V_{rms} I_{rms} PF$$


$$50 \times 10^3 = 230 \times I \times 0.8$$

$$I = 271.74$$

After adding C

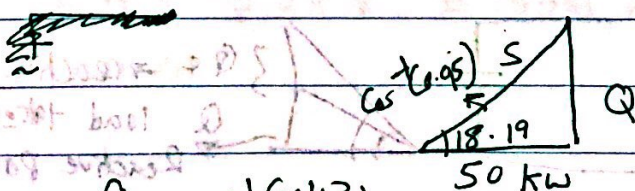

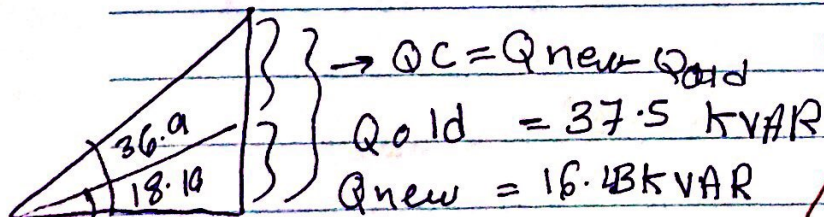
$$\tan 18.19 = \frac{Q_{new}}{50 \times 10^3}, \quad Q_{new} = 16.43 \text{ kVAR}$$



$$Q_C = -21.07 \text{ kVAR}$$

$$|Q_C| = 21.07 \text{ kVAR}$$

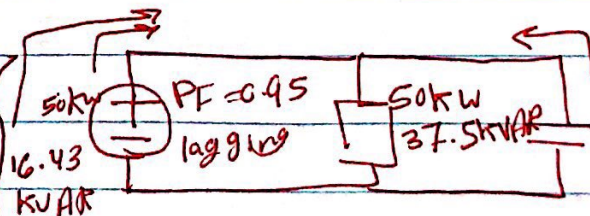

$$I_s \neq I_L$$

$$I_s = I_L + I_C$$

$$Q = |V_{Rms}| |I_{Rms}| \sin(\theta - \phi)$$

$$|I_C| = \frac{Q_C}{V_{rms}} = \frac{21.07 \times 10^3}{230}$$

$$|I_C| = 91.6 \text{ A}, \quad I_C = 91.6 \angle 90^\circ \text{ A}$$


$$Q_C = V_C I_C = \frac{V_C^2}{|X_C|} = I_C^2 X_C$$

$$|Q_C| = \frac{V_C^2}{X_C} = \omega C V_C^2$$

$$C = |Q_C| / \omega V_C^2 = 21.07 \times 10^3 / (2\pi \times 50) \times (230)^2 = 1.26 \mu\text{F}$$

$$I_S = 271.4 \angle -36.9^\circ + 91.6 \angle 90^\circ = 228.78 \angle -18.9^\circ$$

• Example:

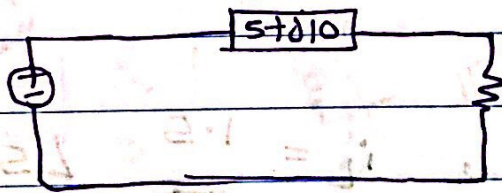

Find R_L that maximize power transfer

$$R_L = |Z_{th}| = \sqrt{5^2 + 10^2} = \sqrt{125}$$

• Example: Find the PF and P for the load


$$i(t) = 4 \cos(100\pi t + 10)$$

$$v(t) = 120 \cos(100\pi t - 20)$$

$$PF = (-20 - 10) = 0.866 \text{ leading}$$

$$P = \frac{120 \times 4}{2} \cos(-30)$$

* Example

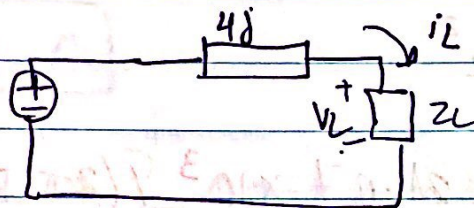

$$V_L(t) = 60 \cos(\omega t - 10)$$

$$i_L(t) = 1.5 \cos(\omega t + 50)$$

Find S_L & load PF

$$V_L = \frac{60}{\sqrt{2}} \angle -10$$

$$i_L = \frac{1.5}{\sqrt{2}} \angle 50$$

$$S_L = V I^* = 45 \angle -60 \text{ VA}$$

$$\text{Load PF} = \cos(\theta_{V_L} - \theta_{i_L}) = \cos(-10 - 50) = 0.5 \text{ leading}$$




$$V_S = V_L + (i_L)(1+j) = 42.0 \angle -8 \text{ V}$$

$$PF(\text{source}) = \cos(-8 - 50) = 0.53 \text{ leading}$$

CH 12 Poly Phase system

- How do we generate electricity


- Faraday : $V = -N \frac{d\phi}{dt}$

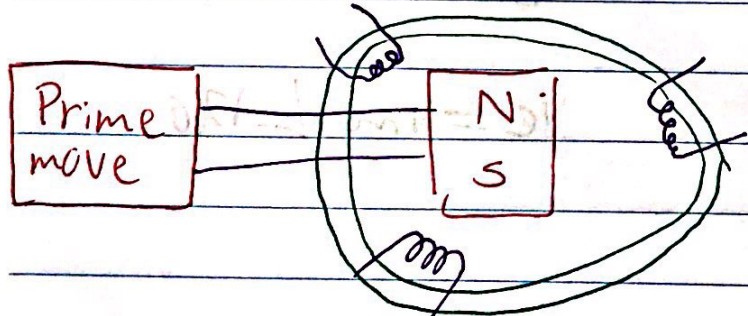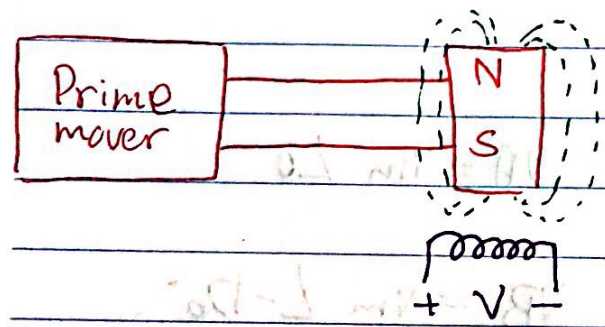
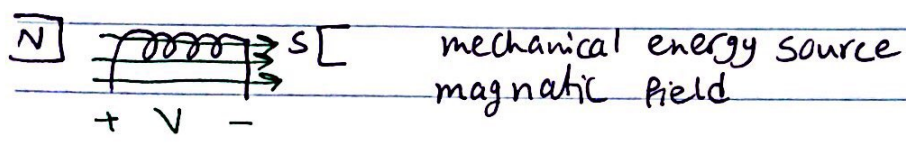


Three Phase system

~~2 loads (capacitor)~~

$|VA| = |VB| = |VC| = N \times VA \sin \omega t$
different Phase

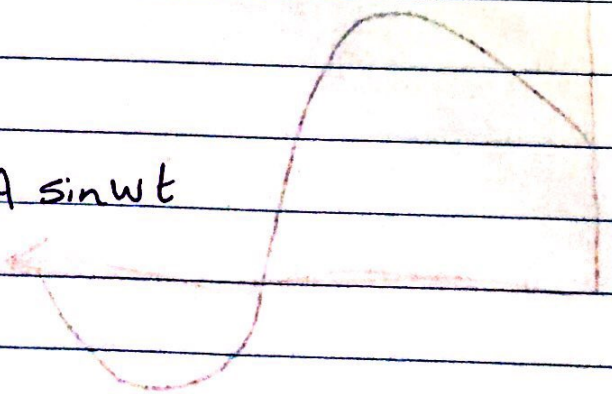

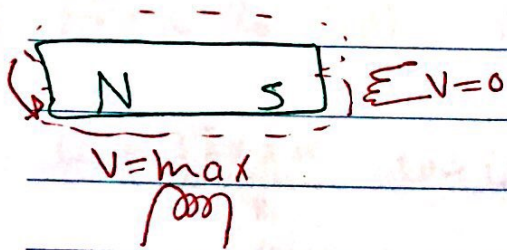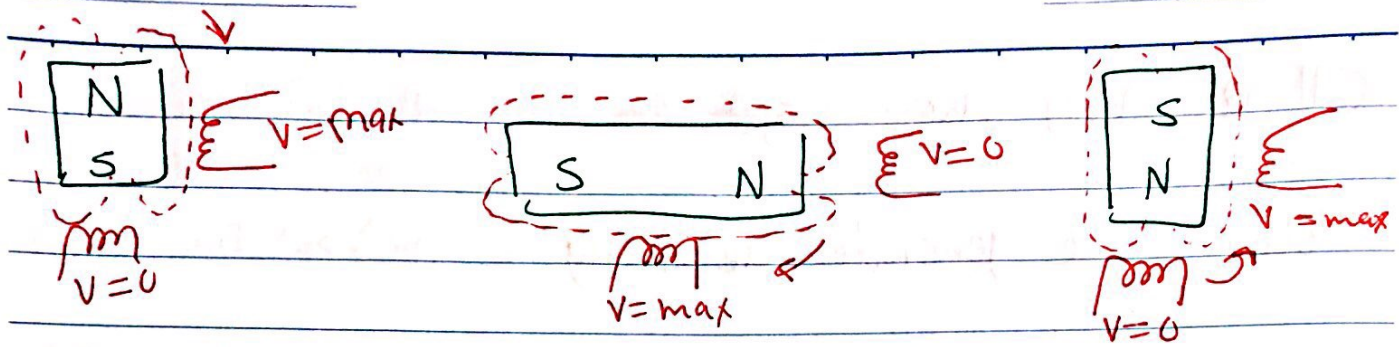

* In General :

$$V_A = V_m \cos(\omega t)$$


$$V_A = V_m \cos 0$$

$$V_B = V_m \cos(\omega t - 120^\circ)$$

$$V_B = V_m \cos -120^\circ$$

$$V_C = V_m \cos(\omega t - 240^\circ)$$

$$V_C = V_m \cos 120^\circ$$

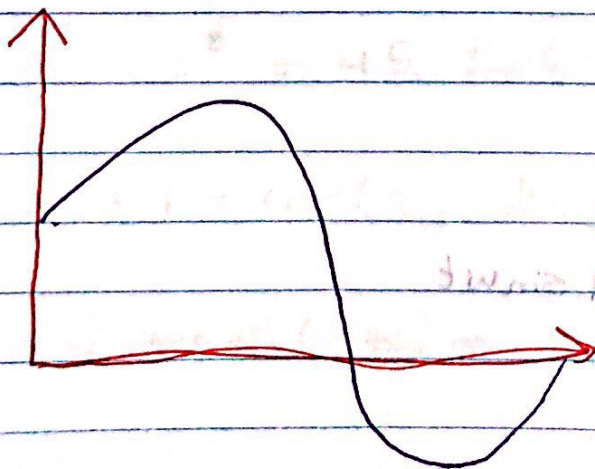

14/10/2018

balanced
Y-Y connected systems

* The voltage across the load in Y-connected load is line-neutral voltage, also called phase to neutral voltages

* A load can be connected between two lines (phases) & the voltage across this load is then (line-line voltage) or (phase-phase) voltage & can be calculated as follows

$$V_{AB} = V_{AN} - V_{BN} = V_m \angle 0 - V_m \angle -120$$

$$= V_m - V_m \cos(-120) - j V_m \sin(-120)$$

$$= V_m + \frac{1}{2} V_m + j \frac{\sqrt{3}}{2} V_m = \frac{3}{2} V_m + j \frac{\sqrt{3}}{2} V_m$$

$$= \sqrt{3} V_m \left[\frac{\sqrt{3}}{2} + j \frac{1}{2} \right] = \sqrt{3} V_m \left[\cos 30 + j \sin 30 \right]$$

$$= \sqrt{3} V_m \angle 30^\circ$$

$$V_{BC} = V_{BN} - V_{CN} = V_m \angle -120 - V_m \angle 120$$

$$= V_m \cos(-120) + j V_m \sin(-120) - V_m \cos(120) - j V_m \sin(120)$$

$$= -j \sqrt{3} V_m = \sqrt{3} V_m \angle -90^\circ$$


$$V_{CA} = V_{CN} - V_{AN} = V_m \angle 120 - V_m \angle 0$$

$$= V_m \cos 120 + j V_m \sin 120 - V_m = \frac{1}{2} V_m + j \frac{\sqrt{3}}{2} V_m - V_m$$

$$= \frac{-3}{2} V_m + j \frac{\sqrt{3}}{2} V_m = \sqrt{3} V_m \left[\frac{-\sqrt{3}}{2} + j \frac{1}{2} \right]$$

$$= \sqrt{3} V_m \left[\cos 150 + j \sin 150 \right] = \sqrt{3} V_m \angle 150^\circ$$

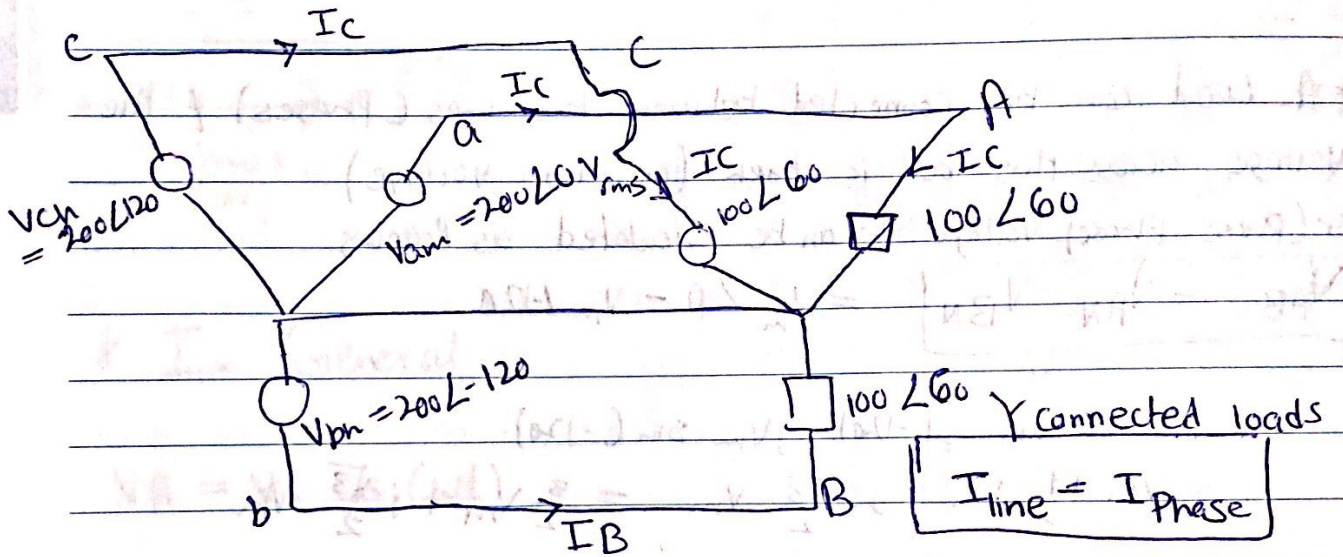Ex) For a γ - γ connected balanced system in the figure
 Find the phase & line currents & the total active power
 absorbed by the load 30



Find the Phase-Phase voltages

$$V_{AB} = \sqrt{3} V_{an} \angle 30^\circ = 200\sqrt{3} \angle 30^\circ$$

$$V_{BC} = \sqrt{3} V_{bn} \angle 30^\circ = 200\sqrt{3} \angle -90^\circ$$

$$V_{CA} = \sqrt{3} V_{cn} \angle 30^\circ = 200\sqrt{3} \angle 150^\circ$$

Phase Current = Line Current

$$I_a = \frac{V_{an}}{Z_Y} = \frac{200\angle 0^\circ}{100\angle 60^\circ} = 2\angle -60^\circ \text{ Arms}$$

$$I_b = 2\angle -180^\circ \text{ Arms}$$

$$I_c = 2\angle 60^\circ \text{ Arms}$$

~~Find~~ *

$$*P_{total} = P_A + P_B + P_C$$

$$\bullet P_A = V_{AN} I_A \cos(\theta) \rightarrow \theta_{V_m} - \theta_I$$

$$= 200 \times 2 \times \cos(30 + 60) = 200 \text{ W}$$


$$\bullet P_B = V_{BN} I_B \cos(\theta) \rightarrow \theta_{V_m} - \theta_I$$

$$= 200 \times 2 \times \cos(-120 + 180) = 200 \text{ W}$$

$$\bullet P_C = V_{CN} \times I_C = 200 \text{ W}$$

$$P_{total} = 600 \text{ W}$$

16/10/2018

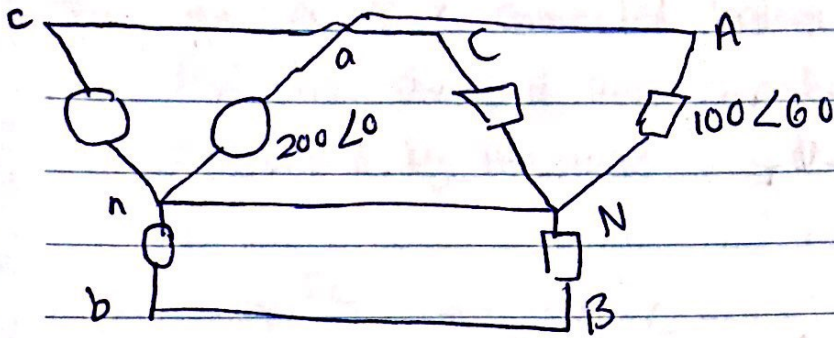

$$P = P_A + P_B + P_C = 600 \text{ W}$$

$$P_{\text{tot}}(t) = P_A(t) + P_B(t) + P_C(t)$$

$$V_{AN} = 200 \angle 0 \rightarrow V_A(t) = 200 \sqrt{2} \cos(\omega t)$$

$$V_{BN} = 200 \angle -120 \rightarrow V_B(t) = 200 \sqrt{2} \cos(\omega t - 120)$$

$$V_{CN} = 200 \sqrt{2} \cos(\omega t + 120)$$

$$i_A(t) = 2\sqrt{2} \cos(\omega t - 60)$$

$$i_B(t) = 2\sqrt{2} \cos(\omega t - 180)$$

$$i_C(t) = 2\sqrt{2} \cos(\omega t + 60)$$

$$P_A(t) = V_{AN}(t) i_A(t) = 800 [\cos(\omega t) \cos(\omega t - 60)]$$

$$= \frac{800}{2} [\cos(2\omega t - 60) + \cos(60)]$$

$$= 200 + 400 \cos(2\omega t - 60) \text{ W}$$

$$P_B(t) = V_{BN}(t) i_B(t) = 800 \cos(\omega t - 120) \cos(\omega t - 180)$$

$$= 200 + 400 \cos(2\omega t + 60) \text{ W}$$

$$P_C(t) = V_{CN}(t) i_C(t) = 800 \cos(\omega t + 120) \cos(\omega t + 60)$$

$$= \frac{800}{2} [\cos(2\omega t + 180) + \cos(60)] = 200 + 400 \cos(2\omega t + 180) \text{ W}$$



$$P_{\text{tot}} = P_A(t) + P_B(t) + P_C(t) = \cancel{600 + 400 \cos(2\omega t - 60)} + \cancel{400 \cos(2\omega t + 60)} + 400 \cos(2\omega t + 180) \text{ W}$$

$$= 600 + 400 \cos(2\omega t - 60) + 400 \cos(2\omega t + 60) + 400 \cos(2\omega t + 180) \text{ W}$$

$$W_T = VI = P$$

$$P_{\text{total}} = 600 \text{ W}$$

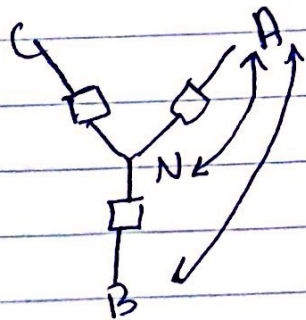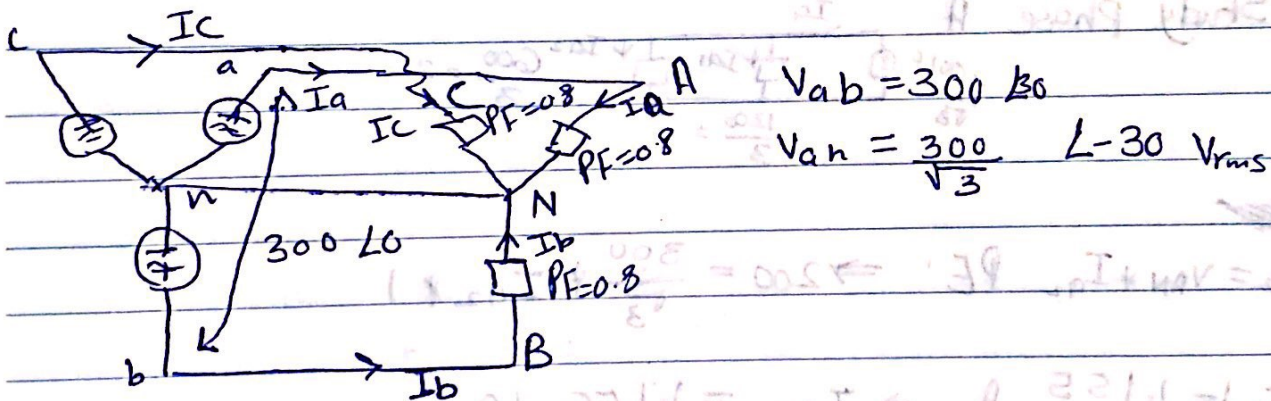Ex] A balanced 3 ϕ system with $V_{ab} = 300 \angle 30^\circ \text{ V}$ & ~~supplying~~ supplying a balanced Y-connected load with 1200 W @ a leading PF of 0.8, find the line currents & the Pre-phase load impedance



$$V_{ab} = \sqrt{3} V_{an} \angle 30^\circ \quad (\text{Y connected}) \quad V_{LL} = \sqrt{3} V_{LN} \angle 30^\circ$$

$$P_A = V_{AN} I_a \cos(\phi_{V_{AN}} - \phi_{I_a}) = V_{AN} I_a \text{ PF}$$

$$400 = \frac{300}{\sqrt{3}} * |I_a| * 0.8$$


$$|I_a| = 2.89 \text{ A}_{\text{rms}}, \quad I_a = 2.89 \angle +\cos^{-1}(0.8) = 2.89 \angle 36.9^\circ \text{ A}$$

I leading V

$$I_{\text{line (a)}} = 2.89 \angle 36.9^\circ$$


$$Z_L = \frac{V_{AN}}{I_A} = \frac{300}{\sqrt{3}} \angle 0^\circ = 60 \angle -36.9^\circ \Omega$$

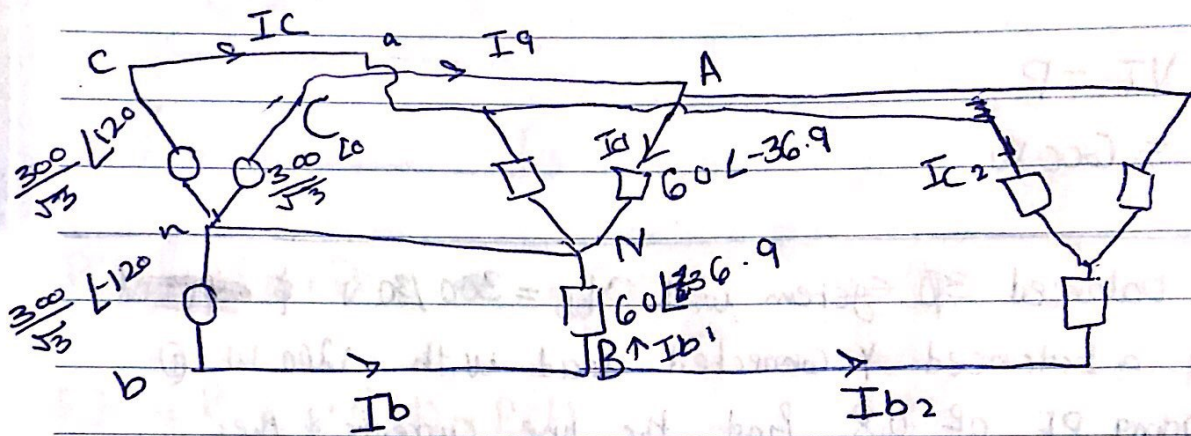Ex) A balanced 600 W Y-connected load is added in Parallel to the previous system, find the new line current



* Single Phase equivalent circuit

→ Study phase A

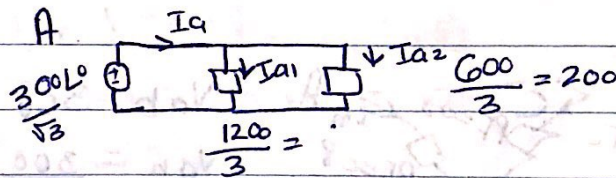

~~A~~

$$P_{A2} = V_{AN} * I_{a2} \quad PE \Rightarrow 200 = \frac{300}{\sqrt{3}} * I_{a2} * 1$$

$$|I_{a2}| = 1.155 \text{ A} \Rightarrow I_{a2} = 1.155 \angle 0$$

$$\begin{aligned} I_a &= I_{a1} + I_{a2} \\ &= 2.89 \angle 26.9 + 1.155 \angle 0 \\ &= 3.87 \angle 26.6 \text{ A} \end{aligned}$$

The real power supplied by the source is

$$P_A = V_s I_s \cos(\theta - \phi_{I_s}) = \frac{300}{\sqrt{3}} * 3.87 \cos(0 - 26.6) = 600 \text{ W}$$

$$\text{Total Source Power} = 1800 \text{ W}$$

$$P_{3\phi} = P_{1\phi}$$