



☀ Switch off your mobile. No advanced calculators, Tablets or mobile phones are allowed.
 ☀ Hand over your exam sheets with your scratch paper.
 ☀ Show work and write the final answer units inside the box to get credit on problems.
 ☀ Answer all problems directly on the exam paper.
 ☀ Feel free to use the calculator in each problem's solution work.
 ☀ Please keep ☺, ☺ & ☺. Don't ☹, ☹, ☹ & ☹. Take your ☺ & enjoy yourself.


Q1-(10Pis) On the last blank page, solve each part separately. Then write the answer in the following table:

- For the circuit shown, If the conditions for maximum power transfer exist, Determine the:

a- Value of Z_L . $Z_L = Z_{in}^*$ $\frac{60\sqrt{2}V_{rms}}{Z-1}$

b- Source current I_S . $I_S = \frac{V_{rms}}{Z-1}$ $I = \frac{V}{Z}$

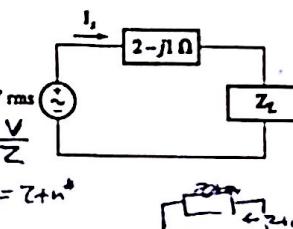c- Efficiency (η). ($\eta = P_{out}/P_{input}$) $P_{out} = V_{rms}I_{rms}$ $Z_L = Z_{in}^*$



~~$Z_L = (2 + j)^{-1} \Omega$~~

~~$I_S = 15 A$~~

~~$\eta =$~~


- In the circuit, $v(t) = 4 \cos(t)$ V,

$C_1 = 1\text{mF}$, $C_2 = 2\text{mF}$, $C_3 = 3\text{mF}$, $Z_1 = \frac{4 - j \cdot 1000}{-500j}$

- Determine the: a- Current of C_2 .

- b- Instantaneous power of C_2 .
c- Total average power (P).
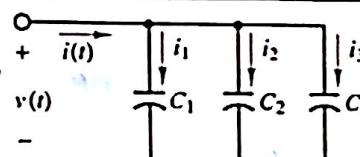
$$P_{avg} = V(t) \cdot i(t) = 4 \cos(t) \cdot \frac{1}{2} \cdot 4 \cos(t) = 8 \cos^2(t)$$



~~$i_2(t) = 1.33 A$~~


~~$P_2(t) = \frac{1}{2} \times 4 \times$~~

~~$P =$~~

- For the given computer central processing unit (CPU) clock waveform, find the:

- a- Average (DC) value.
b- Effective (rms) value.
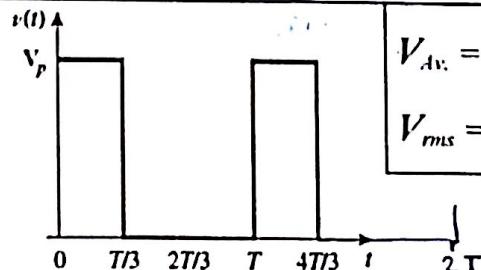
$$T = T \int_0^{T/3} \frac{1}{T} \int_0^t V_p^2 dt = \frac{V_p^2 t}{3}$$



~~$V_{av.} =$~~


~~$V_{rms} = \frac{V_p}{\sqrt{3}}$~~

Describe the sinusoidal signal in:

- a- Time domain $i(t)$.
b- Euler's form I_E .
c- Phasor form I .

Then Find the:

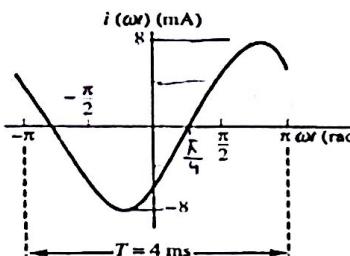- d- Peak-Peak current I_{pp} .
e- Root mean square value I_{rms} .
f- Frequency f .



~~$i(t) = 8 \sin(500\pi t - \frac{\pi}{4}) \text{ mA}$~~

~~$I_E = 8 e^{-j1500\pi t - \frac{\pi}{4}} \text{ mA}$~~

~~$I = 8 \angle -135^\circ \text{ mA}$~~

~~$I_{pp} = 16 \text{ mA}$~~

~~$I_{rms} = 5.657 \text{ mA}$~~

~~$f = 250 \text{ Hz}$~~

Find the phasor of:

$$v = 5 \cos(j2)$$

~~$V = 5 \angle 180^\circ$~~

Describe the phasor form of:

$$v_s(t) = 7 \cos(10t + 60^\circ) + 4 \sin(50t + 45^\circ)$$

~~$V_s =$~~

6)

Q2-I-(6pts) In the circuit shown, Take: $L = 0.5 \text{ H}$, $R = 10 \text{ k}\Omega$,
 $V_{S1}(t) = 10 \cos(31.4t) \text{ V}$, $V_{S2}(t) = 1.2 \sin(2.5 \times 10^6 t + 30^\circ) \text{ V}$.


a- Name the proper method to solve this problem.

b- Determine $i(t)$.

c- Determine $v_{out}(t)$.

d- Determine the average power P_{out} .

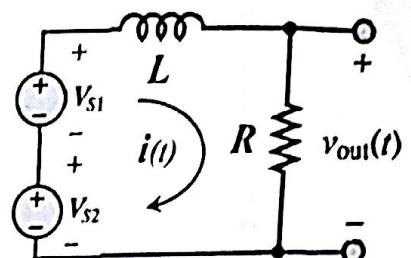e- Discuss $v_{out}(t)$ and P_{out} , respect to the frequency.



e- b)


$$i(t) = \frac{10 \cdot 10}{10000 + 15.7j} = 9.99 \times 10^{-4} \angle -0.9^\circ \text{ A}$$

$$\begin{aligned} v_{out} &= 10 \cdot 10 \angle -0.9^\circ \\ &= 10 \angle -0.9^\circ \\ P_{out} &= \frac{1}{2} \times 10 \times 9.99 \times 10^{-4} \\ &= \frac{1}{200} \omega = 5 \times 10^{-3} \end{aligned}$$

$$i''(t) = \frac{1.2 \angle -60^\circ}{10^4 + 1.25 \times 10^6 j} = 9.6 \times 10^{-7} \angle -149.5^\circ$$

$$v''(t) = 1.2 \angle -60^\circ \times \frac{10^4}{10^4 + 1.25 \times 10^6 j} = 9.6 \times 10^{-3} \angle -149.5^\circ$$
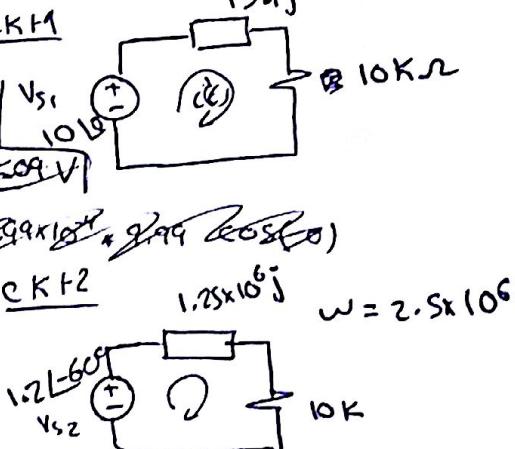
$$L = j\omega L \quad 15.7j \quad \omega = 31.4$$



$$\begin{aligned} P_{out}'' &= \frac{1}{2} V_m \sin(\omega t) \cos(\theta) \\ &= 1.602 \times 10^{-9} \\ &= 5.76 \times 10^{-7} \text{ W} \end{aligned}$$

$$P_{out} = \frac{1}{2} V_m \sin(\omega t) \cos(\theta)$$

a- Superposition method

b- $i(t) = i'(t) + i''(t) = 9.99 \times 10^{-4} \angle -0.9^\circ + 9.6 \times 10^{-7} \angle -149.5^\circ = 9.98 \times 10^{-4} \angle -0.12^\circ \text{ A}$

c- $v_{out}(t) = v_{out}'(t) + v_{out}''(t) = 10 \angle -0.9^\circ + 9.6 \times 10^{-3} \angle -149.5^\circ = 9.99 \angle -0.12^\circ \text{ V}$

d- $P_{out} = P_{out}' + P_{out}'' = 5 \times 10^{-3} + 5.76 \times 10^{-7} \approx 5 \times 10^{-3} \text{ W}$


e- The frequency is a major factor in them

درجات الحرارة

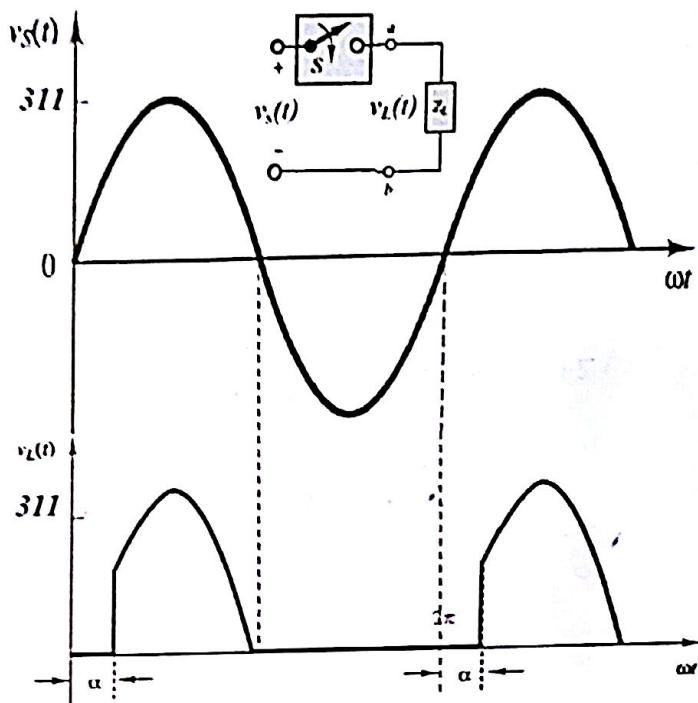
Q2-II-٤٣) For the sinusoidal controlled system, the input function is:
 $v_s(t) = 311 \sin(314t)$. If the switch (S) is OFF at time from $[0 \text{ to } \alpha]$ and at $(\pi \text{ to } 2\pi + \alpha)$, and ON from $(\alpha \text{ to } \pi)$. Find the:

- a- Average voltage of v_s .
- b- rms voltage of v_s .
- c- Average voltage of v_L .
- d- rms voltage of v_L .

[Hint: $\sin^2(x) = \frac{1}{2}(1 - \cos(2x))$]



POWER UNIT


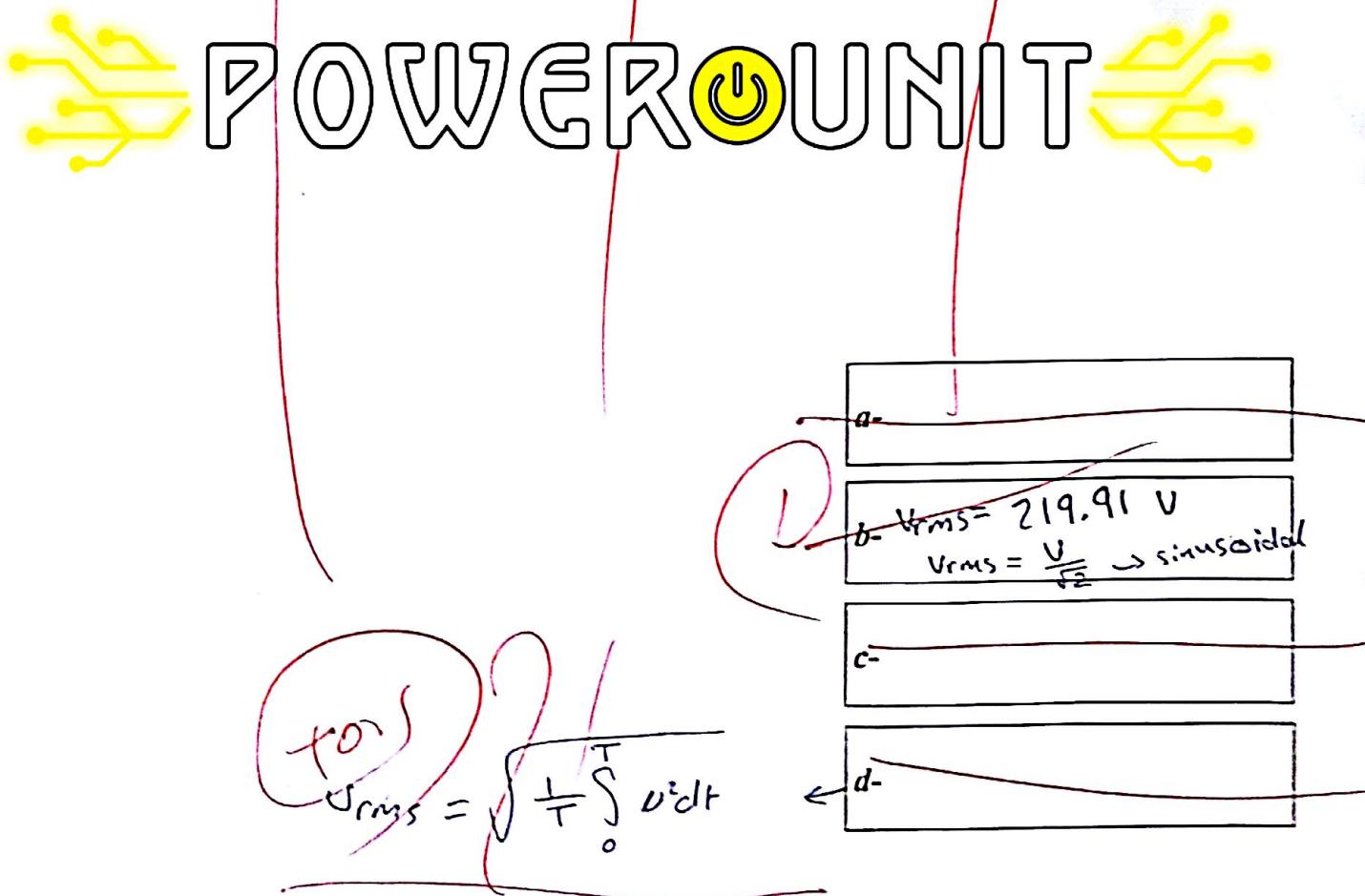


قام المعلم وفي التجيل
كاد يكون رسولاً!
أعلم أشرف أو أجل من الذي
ينبني وينشئ أنفساً وعقلولاً؟

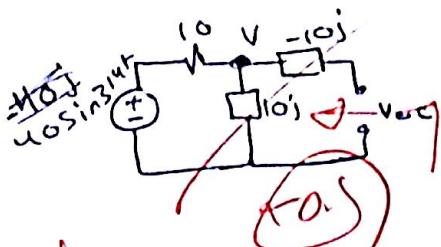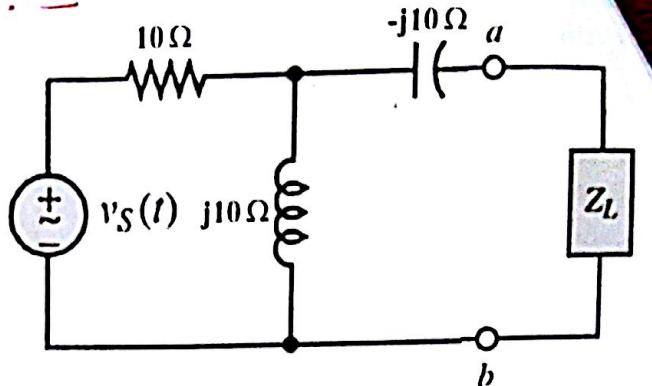Q3 (SP10)

- In the circuit shown, $v_s(t) = 40 \sin(314t)$.
- Find, Sketch, and Label the Thevenin equivalent circuit as seen from terminals $a - b$. Then find the:
 - Load current at $Z_L = 6 + j8 \Omega$.
 - Value of Z_L for max. power transfer.
 - Value of $Z_L = R_L$ (Z_L replace by a pure resistive) for max. power transfer.

$$a) Z_{Th} = -10j + \frac{10 \times 10j}{10 + 10j}$$



POWERUNIT

1

$$Z_{Th} = (5 - 5j) \Omega$$

$$V_{Th} = ?$$

Sketch


b-

c-

d-

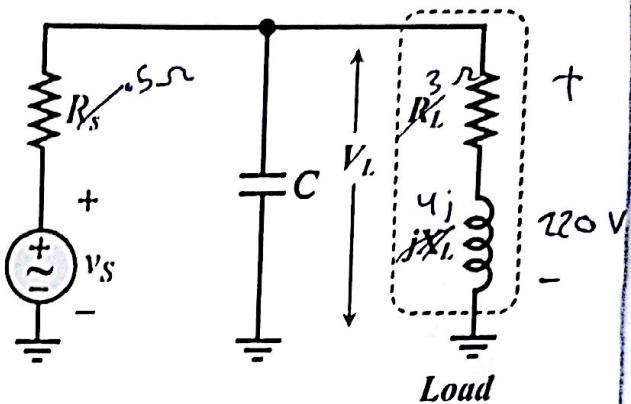
Q4-(17m) The circuit shown, represents an induction motor equivalent circuit. Take: $R_s = 0.5\Omega$, $R_L = 3\Omega$, $X_L = 4\Omega$, $V_{L\text{rms}} = 220\angle 0^\circ \text{ V}$, $\omega = 314 \text{ rad/s}$. Without connecting the capacitor C , Determine the:

- a- Load Current in phasor form.
- b- Complex power S of the load.
- c- Sketch and label the power triangle of the load.
- d- Losses Power in R_s .
- e- Efficiency (η).
- With C connected, Determine the:
- f- C value, if the power factor is to be corrected (improved) to (0.98) lagging.
- g- Losses Power in R_s .
- h- Efficiency (η).



$$a) I_L = \frac{220}{3+4j} = 44 \angle -53.13^\circ \text{ A}$$

ct

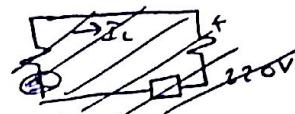

$$b) S = \frac{1}{2} I_m V_m \cos(\theta_v - \theta_i) + \frac{1}{2} I_m V_m \sin(\theta_v - \theta_i) j$$

$$= \frac{1}{2} \times 44 \times 220 \times \cos(53.1)$$



~~$$d) P_{loss} = \frac{1}{2} I_m^2 R$$~~

~~$$e) C = \frac{Q_c}{\omega v_r m_s}$$~~

Phasor
44 $\angle -53.13^\circ$

+ time

$$a) I_E = 44 \cos(314t - 53.13) \text{ A}$$

$$b) S = 2906 + 3870.5j \text{ VA}$$

~~$$d) P_{loss} = 484 \text{ W}$$~~

~~$$e) \text{Efficiency} = \frac{P_{out}}{P_{in}} = \frac{2906}{3870.5} = 0.75$$~~

