

46

University of Jordan
Faculty of Engineering & Technology
Electrical Engineering Department
First Semester 2014-2015

EE091212: Electric Circuits II
 First Exam
 29/10/2014
 Time: 75 Minutes

Student Name: ~~Abdullah Alkhatib~~ **Student ID:** ~~1010101010~~ **Section #**

Mark the correct answer for each of the following statements.

SHOW YOUR CALCULATIONS IN THE SPACE PROVIDED

QUESTION #	ANSWER			
1.	<input checked="" type="radio"/> a	b	c	d
2.	a	b	<input checked="" type="radio"/> c	d
3.	a	b	<input checked="" type="radio"/> c	d
4.	a	<input checked="" type="radio"/> b	c	d
5.	a	b	<input checked="" type="radio"/> c	d
6.	a	b	c	<input checked="" type="radio"/> d
7.	<input checked="" type="radio"/> a	b	c	d
8.	a	b	<input checked="" type="radio"/> c	d
9.	<input checked="" type="radio"/> a	b	c	d
10.	a	<input checked="" type="radio"/> b	c	d
11.	a	b	<input checked="" type="radio"/> c	d
12.	<input checked="" type="radio"/> a	b	c	d
13.	a	<input checked="" type="radio"/> b	c	d
14.	a	b	c	<input checked="" type="radio"/> d
15.	a	<input checked="" type="radio"/> b	c	d
16.	a	b	c	<input checked="" type="radio"/> d
17.	<input checked="" type="radio"/> a	b	c	d
18.	a	<input checked="" type="radio"/> b	c	d
19.	a	b	<input checked="" type="radio"/> c	d
20.	a	b	c	<input checked="" type="radio"/> d
21.	<input checked="" type="radio"/> a	b	c	d
22.	a	<input checked="" type="radio"/> b	c	d
23.	a	b	<input checked="" type="radio"/> c	d
24.	a	<input checked="" type="radio"/> b	c	d
25.	<input checked="" type="radio"/> a	b	c	d
26.	a	<input checked="" type="radio"/> b	c	d
27.	a	b	c	<input checked="" type="radio"/> d

20

Instructors: Dr. Nabeel Tawalbeh
 Dr. Eyad A. Feilat

Questions 1-3

In Fig. 1, $v(t) = v_{dc}(t) + v_1(t) + v_2(t) + v_3(t)$. Answer questions 1-3.

1. the average voltage V_{dc} is _____ V.
 - (a) 0.0
 - b. 30
 - c. 25
 - d. 54.77
2. the effective voltage V_{eff} is _____ V.
 - a. 28.28
 - b. 70.71
 - (c) 38.73
 - d. 54.77
3. if $v(t)$ appears across a $10\text{-}\Omega$ resistor, the average power dissipated is _____ W.
 - a. 150
 - b. 300
 - (c) 1000
 - d. 80

$\frac{v_{max} + v_{min}}{2} = V_{avg}$

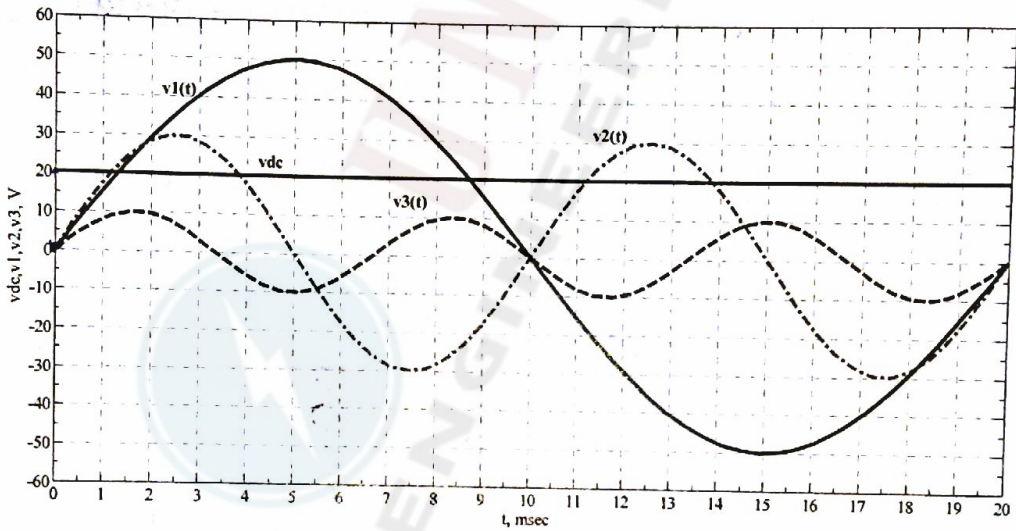


Fig.1

$\frac{1}{T} \int_0^T v(t) dt$

Questions 4-9

Figure 2 shows the voltage $v(t)$ applied to a load and its absorbed instantaneous power $p(t)$. If the load composed of resistive R and reactive X elements in series. Answer questions 4-9.

4. the voltage amplitude V_m is _____ V.
 a. 7.07 **b. 10** c. 14.14 d. 5

5. the frequency, f , of the voltage waveform is _____ Hz.
 a. 20 b. 40 **c. 50** d. 100

6. the average power P drawn by the load is _____ W.
 a. 60 **b. 40** c. 30 **d. 20**

7. the current amplitude I_m is _____ A.
a. 4 b. 8 c. 6 d. 12

8. the phase shift θ between $v(t)$ and $i(t)$ is _____.
 a. 0° b. 30° **c. 60°** d. 45°

9. The instantaneous power $p(t)$ is given by _____ A.
a. $20 + 40 \cos(200\pi t - 60^\circ)$ b. $40 + 40 \sin(100\pi t + 30^\circ)$
 c. $80 \sin(100\pi t + 30^\circ)$ d. $80 \cos(200\pi t + 60^\circ)$

$$P_{avg} = \frac{V_m I_m}{2}$$

$$P_{avg} = \frac{V_m I_m}{2} \times \cos \theta$$

$$40 = \frac{40 \times 4}{2} \times \cos \theta$$

$$40 = 80 \times \cos \theta$$

$$\cos \theta = \frac{40}{80} = \frac{1}{2}$$


$$\theta = 60^\circ$$

$$60 + 20 = \frac{80 \times 20}{2}$$

$$80 = 80$$

$$V_{pp} = 80$$

$$V_p = 40$$

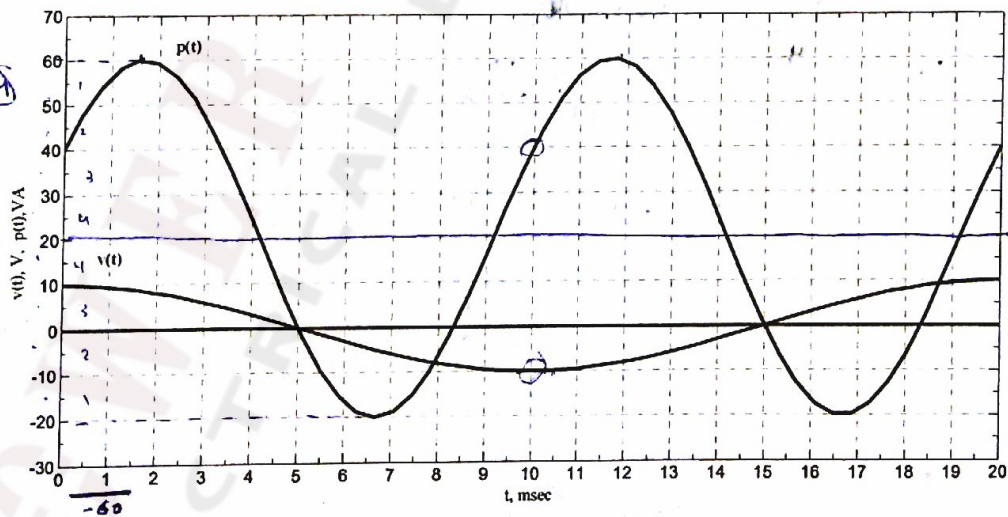

$$\frac{1}{20 \times 10^{-3}} = \frac{1}{T} \quad \omega = 50$$

$$P_m = V_m I_m \cos \theta$$

$$40 = 40 \times 4 \times \cos \theta$$

$$\cos \theta = \frac{1}{2} \quad \theta = 60^\circ$$

$$P_{avg} = \frac{V_m I_m}{2} \cos \theta = \frac{40 \times 4}{2} \times \frac{1}{2} = 40$$

Fig. 2

Questions 10-14

For the circuit shown in Fig.3, $v_s(t) = 10\sin(100\pi t)$ A and the load impedance Z_L is adjusted to absorb the maximum average power. Answer questions 10-14.

10. the complex impedance Z_L which absorbs maximum power is _____ Ω .
 a. $2.4\angle 36.9^\circ$ **b. $2.4\angle -36.9^\circ$** c. $1.78\angle -53.5^\circ$ d. $1.78\angle +53.5^\circ$
11. the maximum power P_{max} absorbed by the load is _____ W.
 a. 24 ~~b. 30~~ **c. 75** d. 37.5
12. the reactive power supplied by the source Q_s is _____ VAR.
a. 28.125 b. -28.125 c. 0.0 d. -56.25
13. the power factor at the source is _____.
 a. 1.0 **b. 0.8 lagging** c. 0.8 leading d. 0.6 lagging
14. If the load impedance is replaced by a pure resistive load R_L , the value of R_L which absorbs maximum power is _____ Ω .
 a. 1.92 ~~b. 3~~ **c. 2.4** d. 5

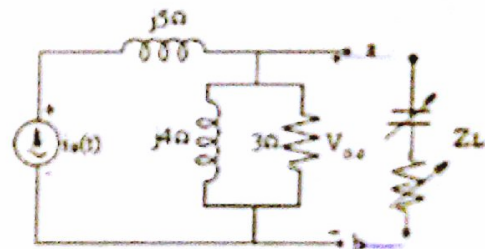


Fig.3

10/0

$$V_{30} = \frac{I_{30} \cdot Z_{in}}{Z_s}$$

$$\frac{V_{30}^2}{4Z_{in}} = I_{30}^2 \cdot 4Z_{in}$$



$$1.92 = 6.44i$$

$$Z_{in} = Z_L \cdot \frac{P_{max}}{P_s} = \frac{I_{30}^2 \cdot e}{I^2} \cdot \frac{V_{30}^2}{4Z_{in}}$$

$$Z_{in} = Z_L$$

$$\frac{1}{30} = \frac{1}{40}$$

Questions 15-16

For the circuit shown in Fig.4, an inductive load of 12 kVA operates at $V_L = 240 \angle 0^\circ V_{rms}$ and 0.60 power factor lagging. If the source frequency $\omega = 314$ rad/s, answer questions 15-16.

15. the real and reactive power taken by the load P_L are _____ kVA.

- a. $12 + j9.6$ **b. $7.2 + j9.6$** c. $12 + j7.2$ d. $9.6 + j7.2$

$P = S \cos \theta$
 $Q = S \sin \theta$
 $I^2 \times R$

16. the magnitude of the source current $|I_s|$ is _____ A.

- a. 62.5 b. 20 c. 30 **d. 50**

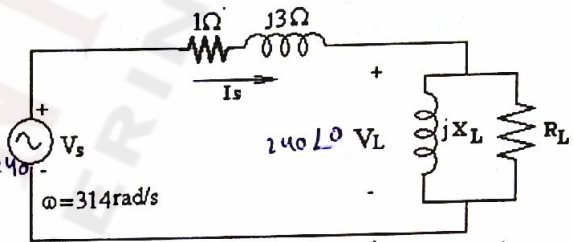


Fig. Q4

Questions 17-19 (ABET/Outcomes a)

If a capacitor is connected in parallel with load of Fig.4 to improve the overall power factor to 0.95 lagging, answer questions 17-19.

17. the reactive power supplied by the capacitor Q_C is _____ kVAR.

- a. 9.6** b. 12 c. 7.2 d. 2.4

18. the size of the capacitor C is approximately _____ μF .

- a. 400 **b. 530** c. 550 d. 690

19. the magnitude of the source current $|I_s|$ after adding the capacitor is _____ A.

- a. 47.5 b. 30 **c. 31.6** d. 50

$Q_c = P_{avg} (\tan \theta_{old} - \tan \theta_{new})$

$\omega = 2\pi f$
 $P_{avg} = V_s I_s$
 $I_s^2 = \frac{P}{R}$

$I_s (1 + j3) + 240$
 $|I_s| =$
 $\frac{P}{R} = \frac{I_s^2 R}{R} =$

$31.6 = \frac{240}{1 + j3}$

$P = U \times$

$7.2k = 240 \times I_L \times 0.95$




$Q_C = V_{eff}^2 \omega C$

Questions 20-22


For the circuit shown in Fig. Q5, answer questions 20-22.

20. the total real power P_{tot} and total reactive power Q_{tot} absorbed by the three loads are _____ VA.
 a. $1400+j400$ b. $800-j400$ c. $800+j400$ **d. $1400-j400$**
21. the overall load power factor pf is _____.
a. 0.961 leading b. 0.894 lagging c. 0.894 leading d. 0.961 lagging
22. the total real and reactive power (P_{tot}, Q_{tot}) supplied by the source are _____ VA.
 a. $1400+j440$ **b. $1400-j360$** c. $800-j440$ d. $800+j360$

$PF = \cos \theta$

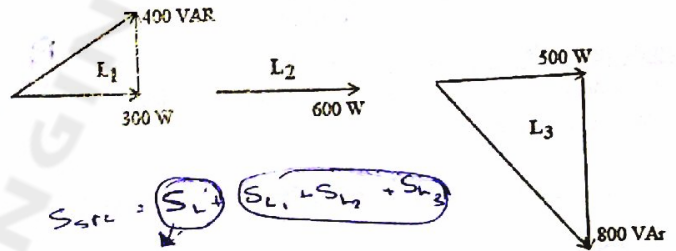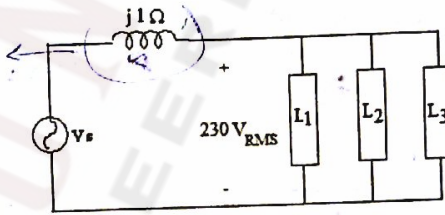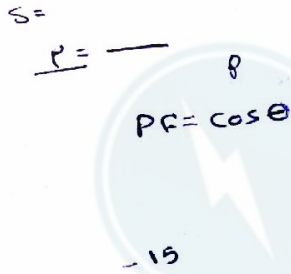

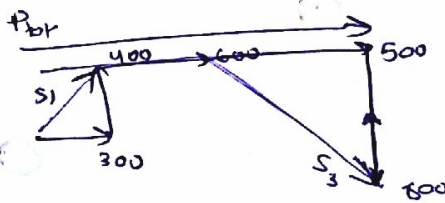$S_{src} = S_{L1} + S_{L2} + S_{L3}$
 $300 + 600 + 500$
 1400



$S_{TOT} = V \times I^*$
 P
 1400

Fig. Q5

Questions 23-27

A balanced three-phase *abc* sequence Y-connected source is connected to a balanced Y-connected load through a transmission line with an impedance of $j1 \Omega$ per phase as shown in Fig.6. The load consumes 8.64 kVA at 0.8 pf lagging. Given the line-to-line voltage $V_{CB} = 208 \angle 90^\circ$ V_{rms} at the load terminals, answer questions 23-27.


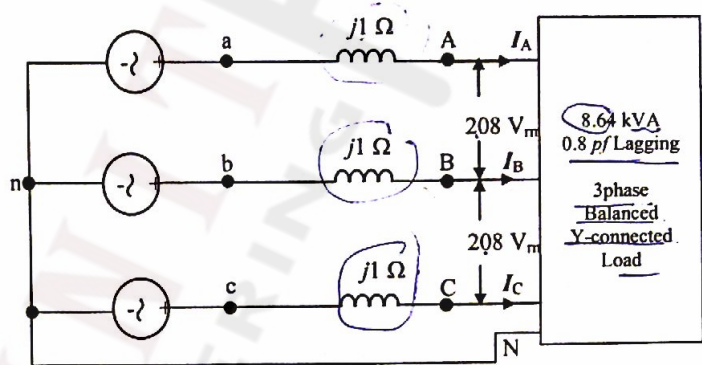
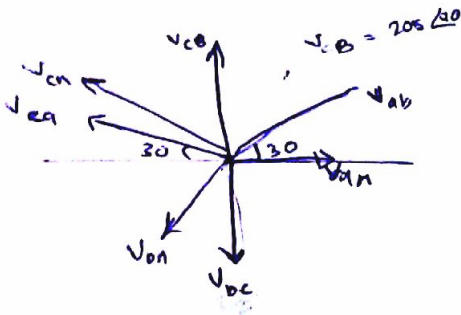


Fig. Q6

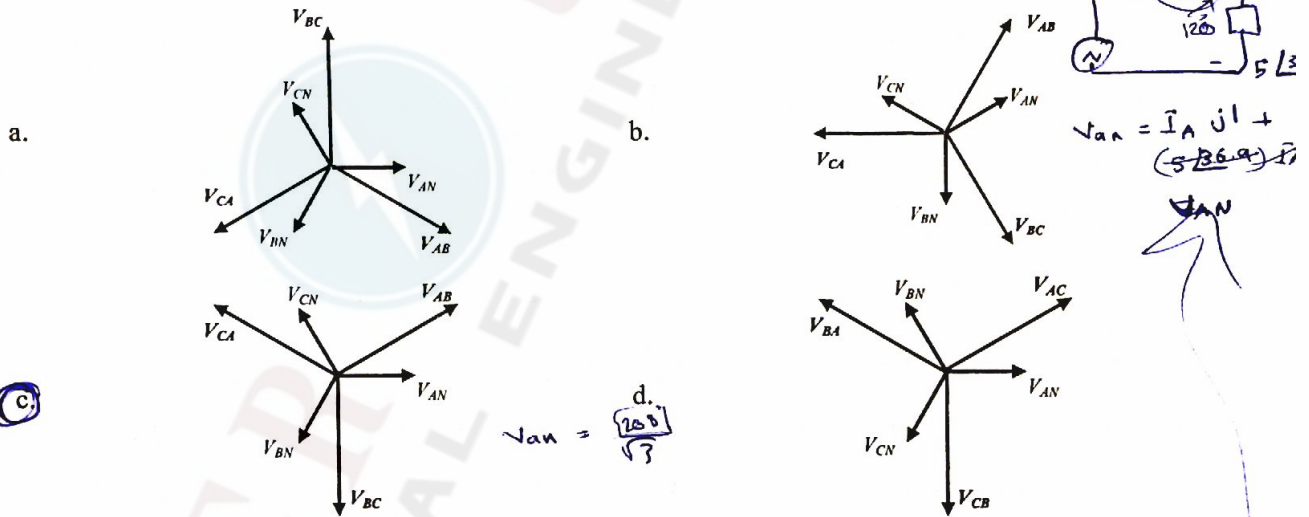23. the phasor diagram showing the load phase and line voltages is shown in Fig. ().



24. The load phase voltage V_{AN} is given as _____ V_{rms}.

- a. $V_{AN} = 208 \angle 30^\circ$ **(b)** $V_{AN} = 120 \angle 0^\circ$ c. $V_{AN} = 120 \angle -30^\circ$ d. $V_{AN} = 208 \angle -30^\circ$

25. the phasor current I_A is given as _____ A_{rms}.

- (a)** $I_A = 24 \angle -36.9^\circ$ b. $I_A = 41.6 \angle -53.1^\circ$ **(c)** $I_A = 24 \angle 36.9^\circ$ d. $I_A = 41.6 \angle 53.1^\circ$

26. the load impedance per phase Z_Y is _____ Ω .

- a. $Z_Y = 5 \angle -36.9^\circ$ **(b)** $Z_Y = 5 \angle 36.9^\circ$ c. $Z_Y = 8.66 \angle 53.1^\circ$ d. $Z_Y = 8.66 \angle 36.9^\circ$

27. the magnitude of the source voltage $|V_{an}|$ is _____ V_{rms}.

- a. $V_{an} = 232 \angle 30^\circ$ b. $V_{an} = 144 \angle 0^\circ$ c. $V_{an} = 122.4 \angle 11.3^\circ$ **(d)** $V_{an} = 135.8 \angle 8.1^\circ$

Handwritten calculations and notes:

- 8.64×10^4
- $120 \angle$
- $P = 3 V_L \times I_L \cos \theta$
- $6912 = 3 V_L \times I_L \cos \theta$
- $6912 = 3 V_L \times I_L \times 0.8$
- $6912 = 2.4 V_L I_L$
- $V_L I_L = 2880$
- $V_L = 120 \angle$
- $I_L = 24 \angle -36.9^\circ$
- $Z_Y = 5 \angle 36.9^\circ$
- $V_{an} = 135.8 \angle 8.1^\circ$
- Good Luck!**