



Instructors:	Dr. Omar Ghezawi	<input checked="" type="checkbox"/>	11
	Dr. Yanal Faouri	<input type="checkbox"/>	

Electrical Circuits (1) (EE211)

First Exam


2nd Term, 2015-2016

March 13th, 2016. ⌚ 15:00 – 15:50

Problem 1: (5 points)

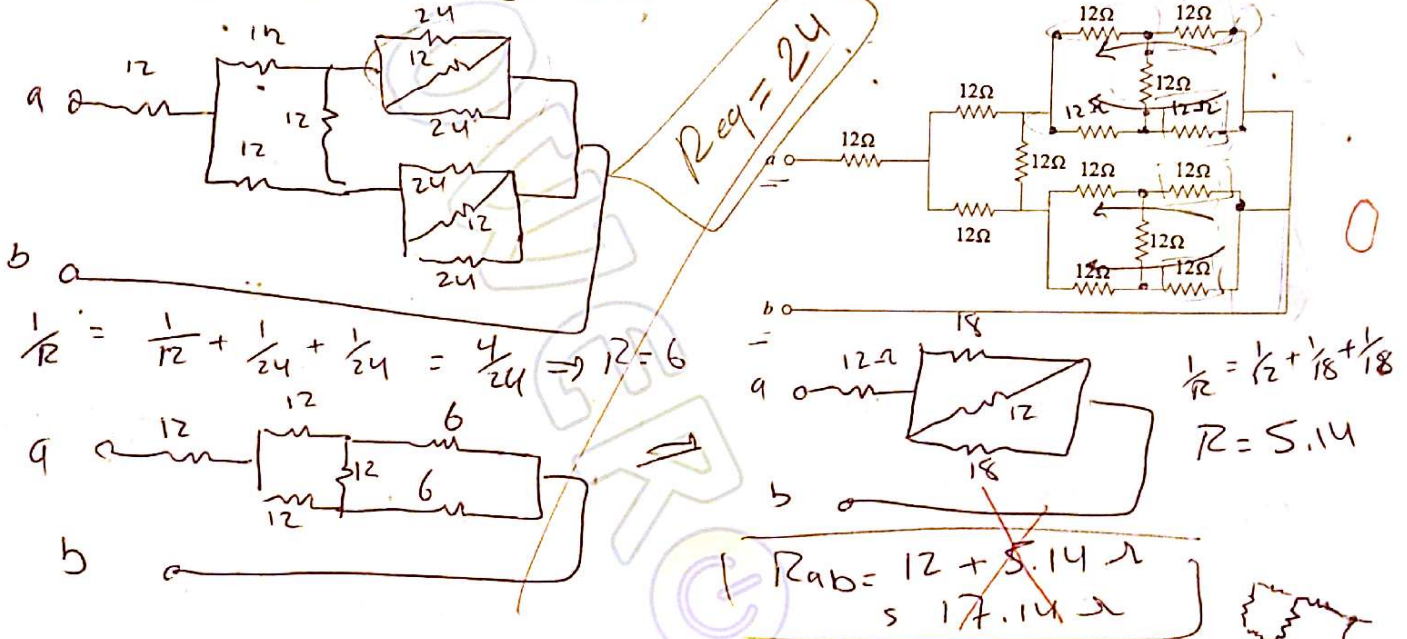a) Find the equivalent resistor (R_{ab}) in the four-way power divider circuit.

(Hint: Before attempting to solve; examine the circuit carefully, redraw, look for patterns and symmetry. You should get an integer answer)



b) Two delicate devices are rated as shown in Fig. 2.142. Find the values of the resistors and needed to power the devices using a 24-V battery.

(Hint: force the fuse to work to its maximum limit)

@ Device 2:

$$P = V \times I$$

$$I_2 = \frac{P}{V} = \frac{480 \times 10^{-3}}{24} = 0.02 \text{ Ampere}$$

@ Device 1: $I_1 = \frac{P}{V} = \frac{45 \times 10^{-3}}{9} = 5 \times 10^{-3} \text{ Ampere}$

By KVL @ Loop (1)

$$-V_2 + I_1 R_1 + V_1 = 0$$



$$-24 + 5 \times 10^{-3} \times R_1 + 9 = 0$$

$$\Rightarrow R_1 = \frac{15}{5 \times 10^{-3}} = 3 \text{ k}\Omega$$

$$V_{R_2} = V_1 = 9 \text{ Volts (By KVL) Loop (2)}$$

~~By KVL for loop 3:~~

~~-24~~

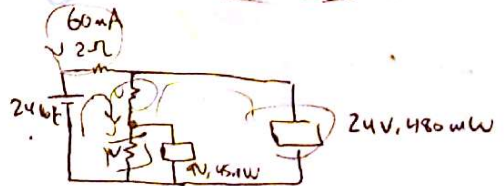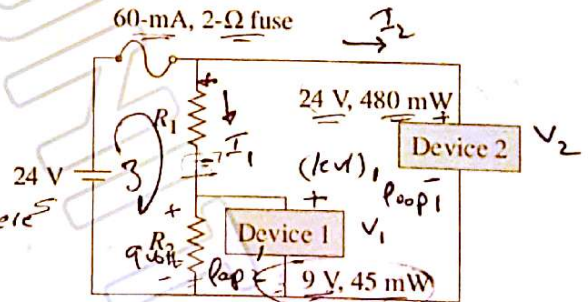

By KVL (loop 1 & 2)

$$I_1 R_1 + I_2 R_2 = 24$$


$$R_2 = \frac{V}{I} =$$

$$R_1 = 375$$

$$R_2 = 257.14$$

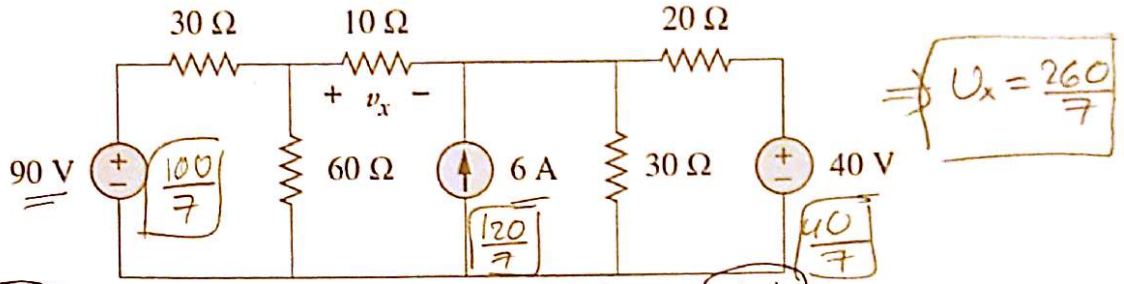Problem 2: (5 points)


Use superposition to obtain v_x in the circuit shown.




@ Source 90 Volt:


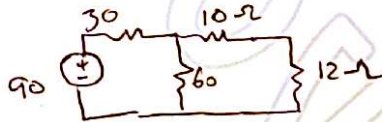
$$R_{20} // R_{30} \Rightarrow \frac{20 \times 30}{20 + 30} = 12 \Omega$$


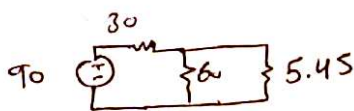
$$R_{12} // R_{10} \Rightarrow \frac{12 \times 10}{10 + 12} = 5.45 \Omega$$




$$R_{5.45} // R_{60} \Rightarrow \frac{60 \times 5.45}{60 + 5.45} = 5 \Omega$$



$$I_1 = \frac{90}{30 + 5} = \frac{90}{35} = 2.571 \text{ Ampere}$$
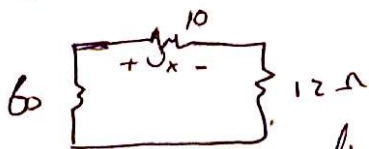
$$V_{@ 5 \Omega} = I \times R = 2.571 \times 5 = 12.857 \text{ Volt} = \text{Voltage @ } 60 \Omega$$




By voltage division


$$v_x' = V_T \frac{10}{10 + 12} = 12.857 \frac{10}{22}$$

$$v_x' = 5.844 \text{ Volt}$$

@ Source 6 A

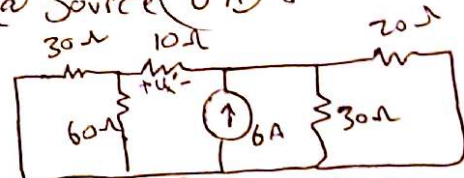
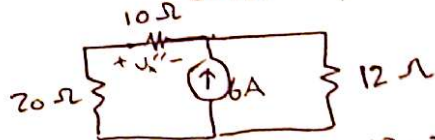
$$R_{30} // R_{60} = \frac{30 \times 60}{30 + 60} = 20 \Omega$$



$$R_{10} \text{ Series with } R_{20} \Rightarrow 10 + 20 = 30 \Omega$$

By current division


$$I_1 = I_T \frac{R_{12}}{R_{12} + R_{30}}$$

$$I_1 = 6 \times \frac{12}{12 + 30} = 3.4285 \text{ Ampere}$$

$$\text{Voltage @ } 10 \Omega = v_x'' = I_1 R_{10}$$

$$v_x'' = 3.4285 \times 10 = 34.28 \text{ Volt}$$

@ Source 40 volt:

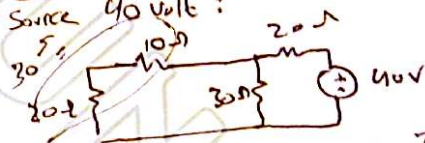

$$\frac{30 \times 30}{60} = 15 \Omega$$

$$I = \frac{40}{20 + 15} = 1.14 \text{ Ampere}$$

$$V_{15} = 1.14 \times 15 = 17.14 \text{ Volt}$$


By voltage division:

$$v_x''' = 17.14 \times \frac{10}{10 + 20} = 5.714 \text{ Volt}$$

$$\begin{aligned} \therefore v_x &= v_x' + v_x'' + v_x''' \\ &= 5.844 + 34.28 + 5.714 \\ &= 45.838 \text{ Volt} \end{aligned}$$

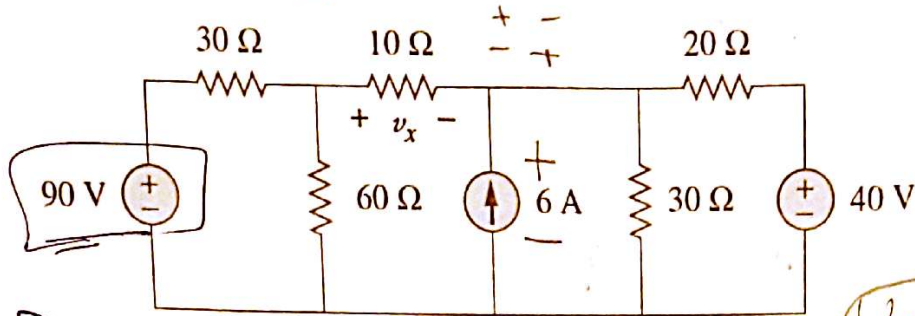
Problem 3: (5 points)

Use source transformation to obtain v_x in the circuit shown.







$V_x = I_x R_x$

$V_x = \frac{60}{7}$

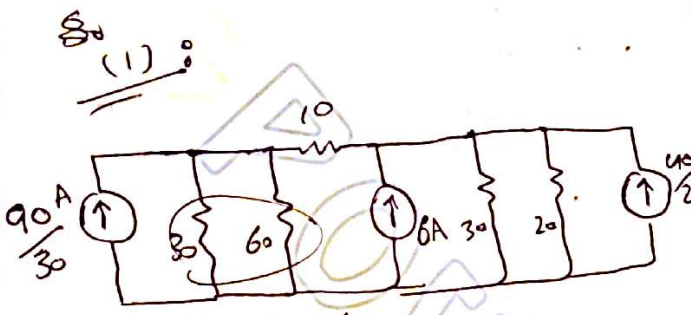


$30 \parallel 60 \Rightarrow \frac{30 \times 60}{30 + 60} = 20 \Omega$

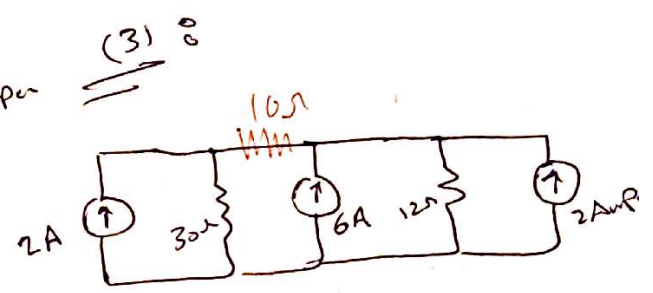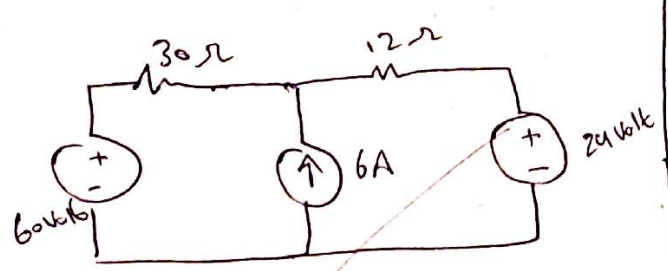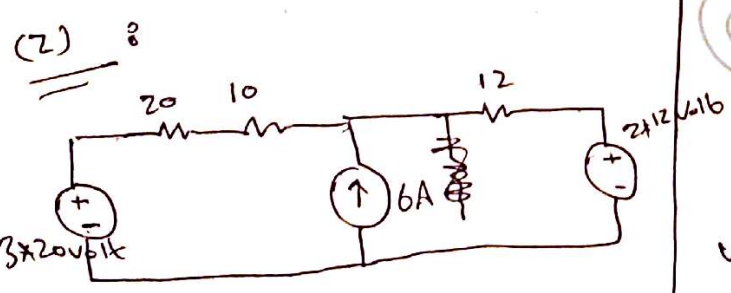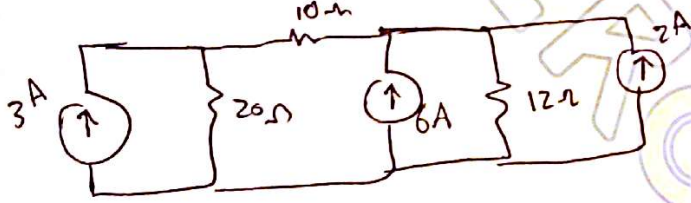$30 \parallel 20 \Rightarrow \frac{30 \times 20}{30 + 20} = 12 \Omega$



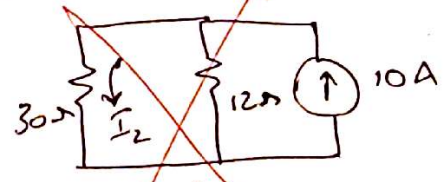$\Sigma \uparrow = 6 + 2 + 2 = 10 \text{ Amperes}$



By current division:

$I_2 = 10 \times \frac{12}{12 + 30}$


$I_2 = 10 \times \frac{12}{42} = 2.85714$

$V_x = V @ 10\Omega = I_2 \times R_{10}$
 $= 2.85714 \times 10$

$V_x = 28.5714 \text{ Volt}$

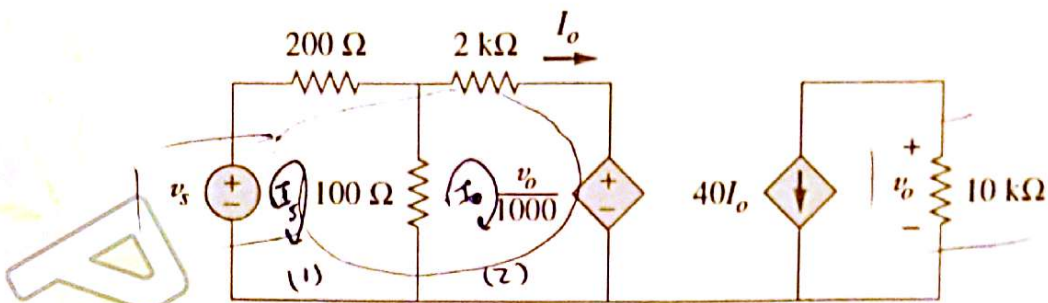Problem 4: (5 points)

Determine the gain $\frac{V_o}{V_s}$ of the transistor amplifier circuit.
 (Note that some resistor values are given in $k\Omega$)



$\frac{V_o}{V_s} \Rightarrow$ gain

$\therefore V_o = I \cdot R_{10k\Omega}$

$= -40 I_o \cdot 10 k\Omega$

$V_o = -400 \cdot 10^3 I_o \dots (3)$

\Rightarrow we divided it for 2 circuits

By Mesh :

(1): $-V_s + 200 I_s + 100 (I_s - I_o) = 0$ ✓ ~~(1)~~

$-V_s + 200 I_s + 100 I_s - 100 I_o = 0$ ~~(1)~~

$-V_s + 300 I_s - 100 I_o = 0 \dots (1)$

(2): $\frac{V_o}{1000} + 100 (I_o - I_s) + 2 k\Omega I_o = 0$

$\frac{V_o}{1000} + 100 I_o - 100 I_s + 2000 I_o = 0$

$\frac{V_o}{1000} + 2100 I_o - 100 I_s = 0 \dots (2)$

~~$\frac{2100 I_o}{1000} = 100 I_s$~~ $100 I_s = \frac{V_o}{1000} + \frac{2100 (400 \cdot 10^3) V_o \cdot 1000}{1000}$

$I_s = \frac{V_o}{100 \cdot 1000} (1 + 2100 \cdot 400 \cdot 10^3 + 1000) = 8400 V_o$

$-V_s + 300 \cdot 8400 V_o - 100 \left(\frac{V_o}{400 \cdot 10^3} \right) = 0$

$V_s = 2520 k\Omega V_o - 0.25 \cdot 10^{-3} V_o$

$\frac{V_s}{1} = V_o (2520 \cdot 10^3 - 0.25 \cdot 10^{-3}) \Rightarrow$

$\frac{V_o}{V_s} \approx \frac{1}{2520 \cdot 10^3}$

Solve $V_o/V_s = -80$
3.5