



Circuits I


Summer 017



Dr. **Y**anal **F**auori



By: **H**amza **A**bedrabbo

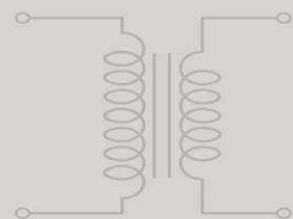

Powerunit-ju.com

Circuits 1

Summer OIT
Dr. Yanal

4/6, lect

*ch1:

Charge: Q or q


↳ +ve charge

↳ -ve charge

$$1e^- = -1.6 \times 10^{-19} \text{ C}$$


$$\text{Proton} = 1.6 \times 10^{-19} \text{ C}$$

~~Current is the flow of charge~~

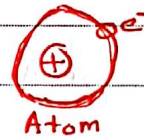

Current: I or i (A)

↳ charge in motion

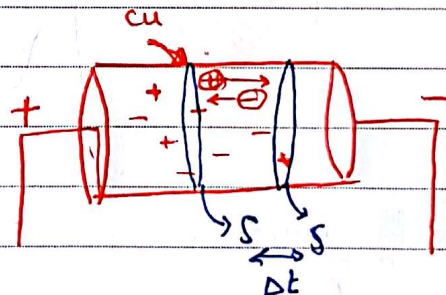

In Uniform
surfaces

$$i = \frac{\Delta q}{\Delta t} \rightarrow \text{[C/s]} \text{ [A]}$$

Ampere \equiv C/s \rightarrow columbia
second

In General
~~surfaces~~ case

$$i = \frac{dq}{dt}$$



* I is in the direction of +ve Q .

* Convention:

Capital letters: I, V, Q, P

for quantities that don't change with time

Example:

$Q = 4 C, I = 5 A, V = -2 V$

Small letters: q or $q(t), i$ or $i(t)$


for general case

either change or not change with time

Example

$i = 4 A$


$i = 4 \cos t$

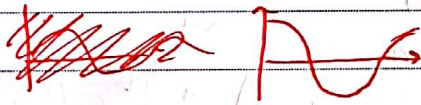


* Types of current:

1) DC

$I = 5 A$

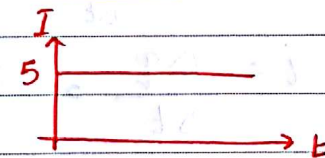


4) Damped sinusoidal current

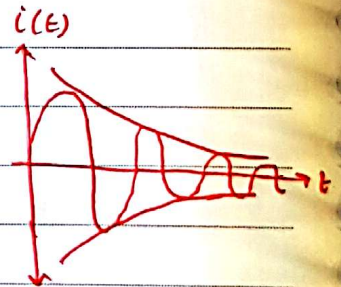



2) AC

$i = 5 \sin t$

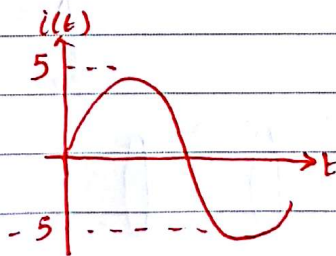

3) exponentially decaying

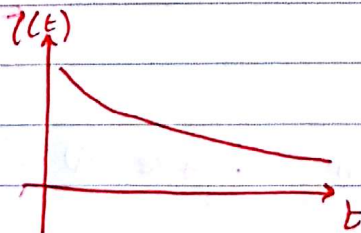

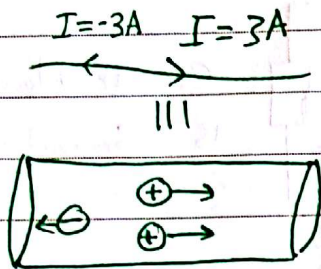

Ex: $i(t) = \begin{cases} 5e^{4t} \text{ A}, & t < 0 \\ 5e^{-4t} \text{ A}, & t > 0 \end{cases}$

Find the total +ve charge crossed from left to right during $[-0.25, 0.25]$ s

$$i = \frac{dq}{dt} \Rightarrow \int dq = \int i dt$$


$$q = \int_{-0.25}^{0.25} i(t) dt = \int_{-0.25}^0 5e^{4t} dt + \int_0^{0.25} 5e^{-4t} dt \text{ C}$$

$$= 1.58 \text{ C}$$

* Voltage : V or v





Unit is Volt (V)

↳ Potential difference.

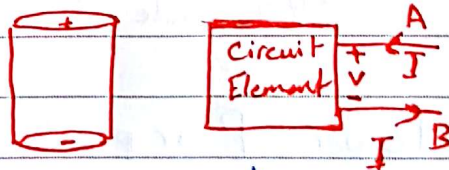


$$\text{Voltage} = \frac{\text{work}}{\text{Charge}}$$
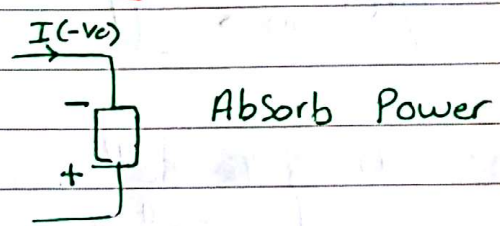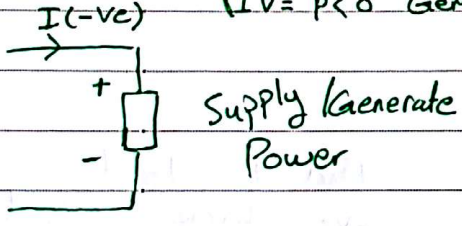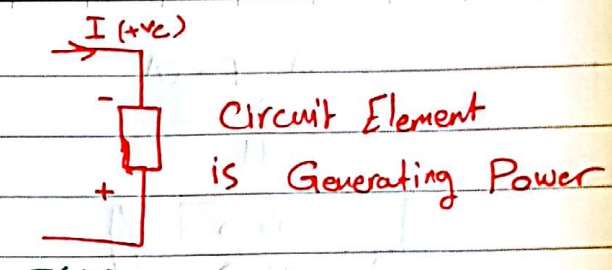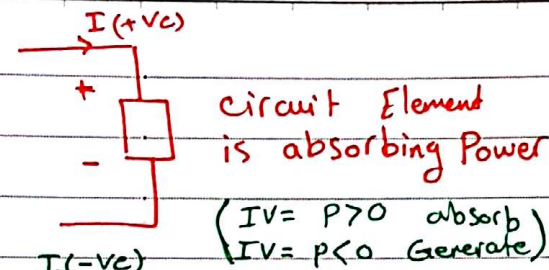
$$1 \text{ Volt} = 1 \text{ Joule} / \text{Coulomb}$$



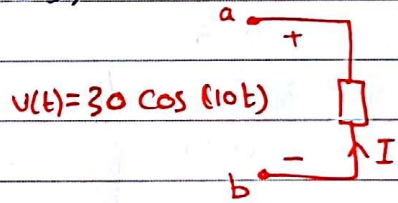Ex: what is the Energy required to move 3C from (a) to (b) during $(t=6s)$






$$\begin{aligned}
 W &= V * Q \\
 &= 30 \cos(10t) \Big|_{t=0}^{t=6} * 3 \\
 &= 90 \cos(60^\circ) \\
 &= 45 \text{ Joule}
 \end{aligned}$$


* Power : P or p

$$P = \frac{\text{work}}{\text{time}} = \frac{W}{t} \quad \text{J/s or watt}$$
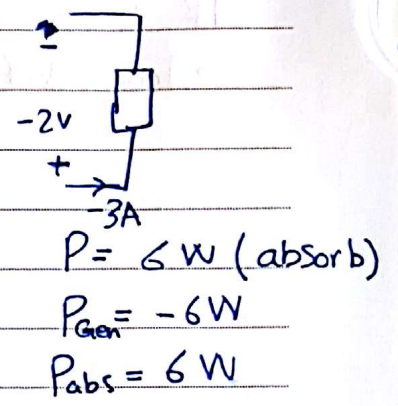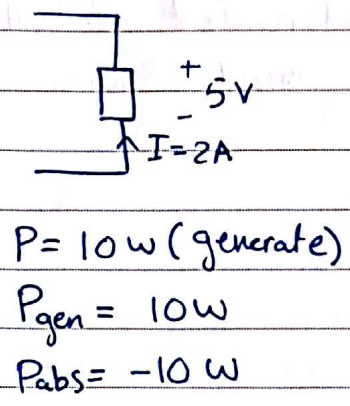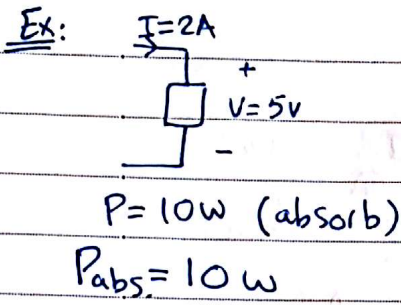
$$P = \frac{dw}{dt} * \frac{dq}{dq} = \frac{dw}{dq} * \frac{dq}{dt} = VI$$



* $P_{\text{Gen}} = -P_{\text{Abs}}$

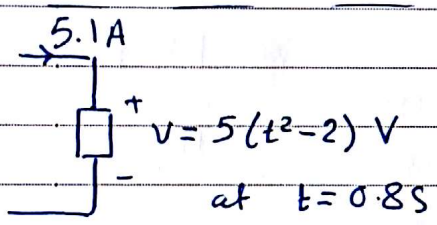


$P = 5.1 \times 5(0.8^2 - 2)\text{W}$ (Generate)

* Types of Circuit Elements:

IF $V \propto i \Rightarrow$ Resistance

IF $V \propto \frac{di}{dt} \Rightarrow$ Inductance

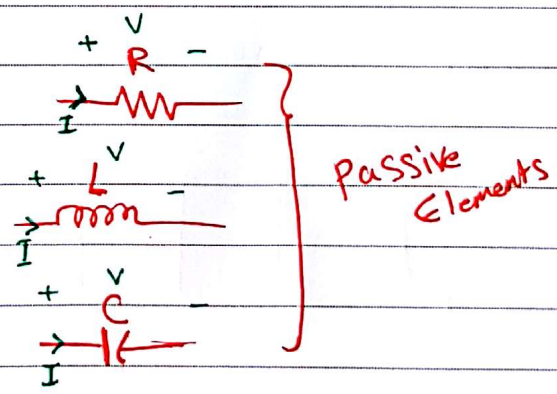
IF $V \propto \int i dt \Rightarrow$ Capacitance




these elements absorb power. called passive elements

C, L are also called storing devices.


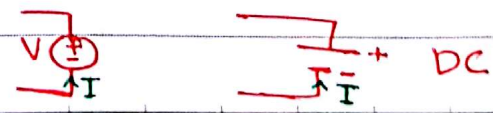
IF V is independent of current
 \rightarrow Independent Voltage Source.



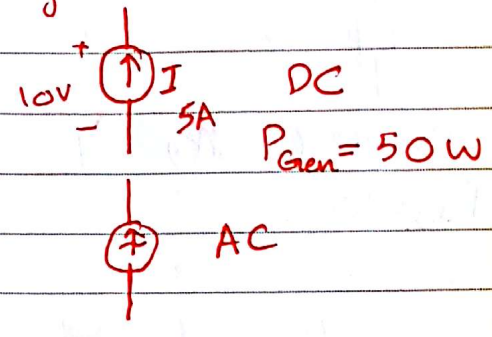If i is independent of Voltage
→ Independent Current Source




* Dependent Sources

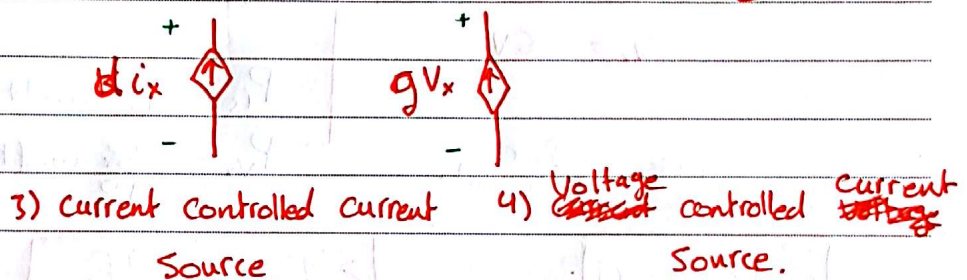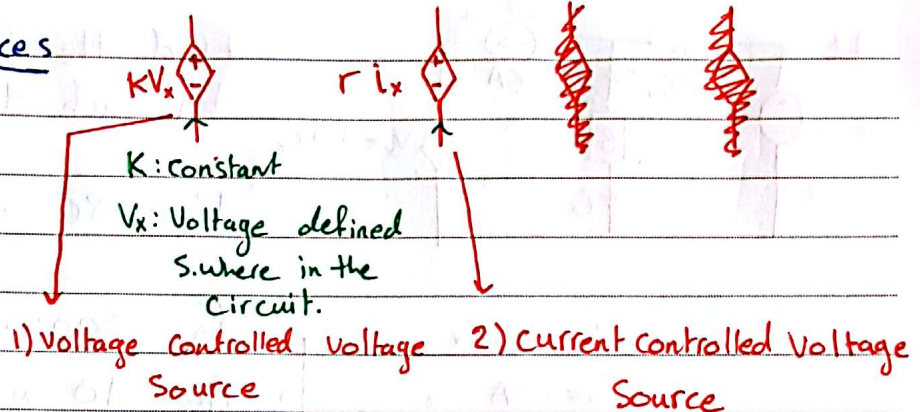


k, d, g are all constants

k, d [Unitless] / r [ohm Ω] / g [Seimens $S \equiv \Omega^{-1}$]

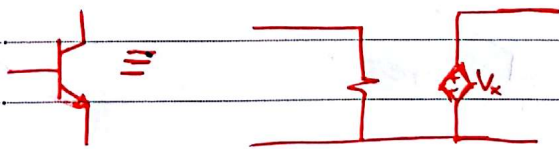Note
* You'll see Dependent Sources in Electronics, such as Transistors




* Ex:

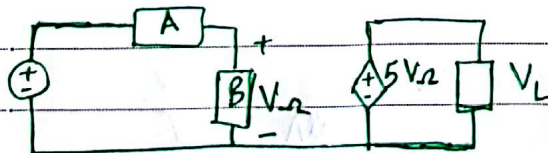

find V_L if $V_r = 3V$??

$V_L = 5 V_r$ (Parallel)

$V_L = 15 V$

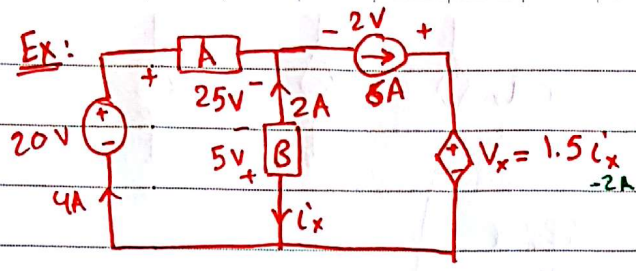

Find the Power Generated by each element??

$P_{V_s} = 80 \text{ watt}$

$P_A = -100 \text{ watt}$

$P_B = -10 \text{ watt}$

$P_{i_s} = 12 \text{ watt}$

$P_{V_x} = \cancel{20} \text{ watt}$
18

$V_x = 1.5 i_x$

$i_x = -2A$


$V_x = -6V$

this is for all circuit.

$\sum P_{Gen} = 0$



$\sum P_{Gen} = \sum P_{Loss}$

* Ohm's law

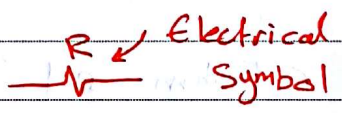

$V \propto i$, $V = iR$, $R \equiv \text{Resistor}$, $R = \frac{V}{I}$

$\frac{V}{A} \equiv \Omega$

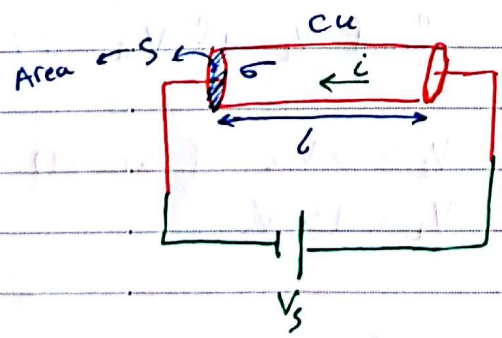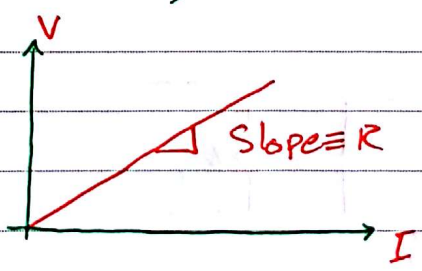

$R = \frac{l}{\sigma A} = \frac{V}{I}$

σ : conductivity $\equiv \frac{1}{\rho}$ [Ω/m]
[S/m]

ρ : Resistivity [Ω/m]

$$P = VI, \quad V = IR, \quad I = \frac{V}{R}$$

$$P = I^2 R = \frac{V^2}{R} \quad \text{Joule's law}$$

$$R = \frac{V}{I}, \quad G = \frac{I}{V} = \frac{1}{R} \quad [r^{-1}, S, \Omega]$$

$G \equiv$ Conductance.


$$I = GV$$

$$P = GV^2 = I^2/G$$


* Ex: if $V = 2 \sin(100t) \text{ V}$
 $R = 10 \Omega$



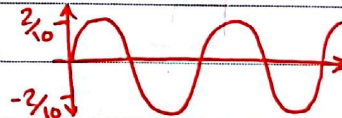
$$i = \frac{2}{10} \sin(100t) \text{ A}$$


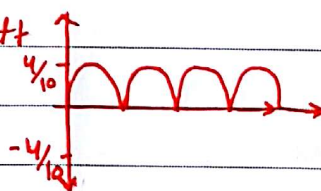
$$P = \frac{4}{10} \sin^2(100t) \text{ watt}$$



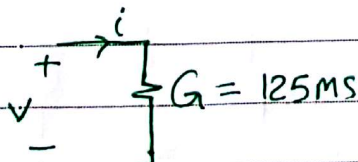Ex: if $P_{abs} = 200 \text{ mW}$, find V ??




$$\text{Sol: } V = \pm \sqrt{\frac{P}{G}} = \pm \sqrt{\frac{200}{125}}$$

$$V = \oplus 1.26 \text{ V}$$

~~since~~ ~~absor~~ according to current sign.

* Open & Short Circuit.


Open Circuit ($R = \infty$)

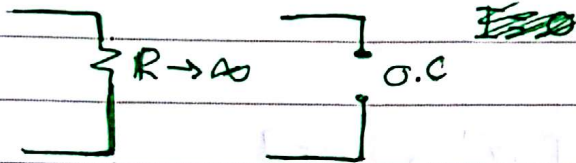

$$I = \frac{V}{R} = \frac{V}{\infty} = \text{zero A}$$


$$I_{o.c} = \text{zero}$$

Short Circuit ($R = 0$)

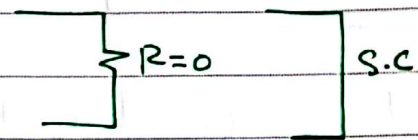

$$V = IR = I(0) = \text{zero V}$$


$$V_{o.c} = \text{zero}$$

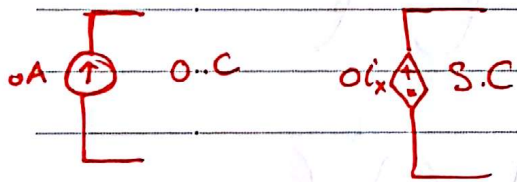

~~C~~

Ch2: Voltage & current laws.

* Node, Branch, Path, loop, Mesh

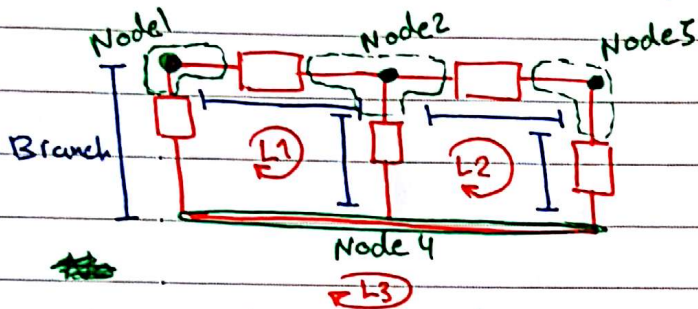

This circuit contains
4 Nodes, 5 branches, 3 loops
, 2 Meshes


Node \equiv Connection between two Circuit Elements

Branch \equiv Node - element - Node


~~Path~~ Path \equiv Start from a Node and go to another ^{node}

loop \equiv Start from a Node and return to it.

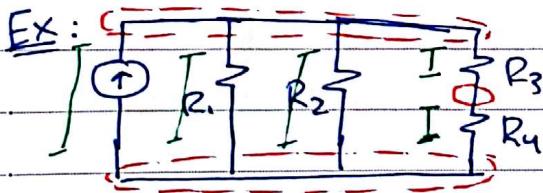Mesh \equiv loop that does not contain another loop.



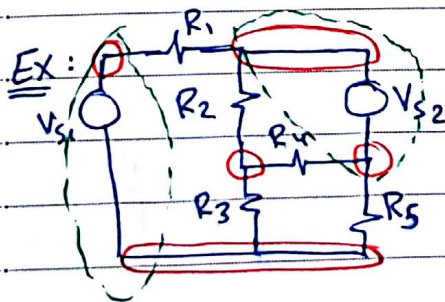3 Nodes, 5 branches, 6 loops, ~~2~~ 3 Meshes




5 Nodes, 7 Branches, 7 loops
3 Meshes

Supernode \equiv V_s between 2 Nodes


* Kirchoff's laws

* Kirchoff's current law (KCL)

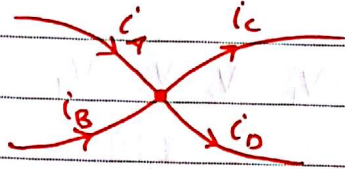

$$\sum I_{\text{entering}} = \sum I_{\text{leaving}}$$

$$i_A + i_B = i_C + i_D \Rightarrow i_A + i_B - i_C - i_D = \text{Zero}$$

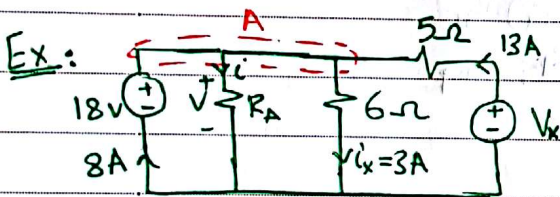find R_A ??

$$V = 18V$$

Apply KCL @ Node A


$$13 + 8 = i + 3$$

$$i = 18A$$

$$R_A = \frac{V}{i}$$

$$= \frac{18}{18} = 1\Omega$$

$$R_A = 1\Omega$$

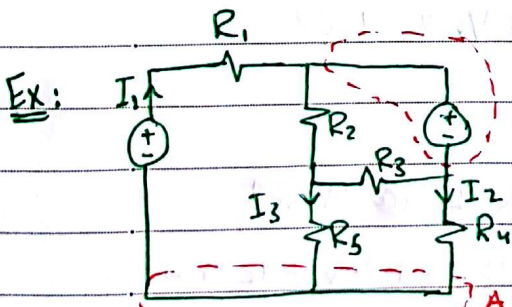

$$I_3 = 2A$$


$$I_2 = 0A$$

Apply KCL @ Node A

$$I_1 = I_2 + I_3 \Rightarrow I_1 = 2A$$


* Kirchoff's Voltage laws (KVL)

$$\sum V = 0$$

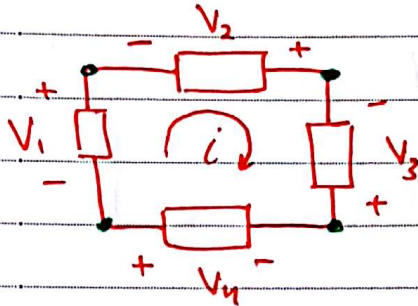

$$-V_1 - V_2 - V_3 - V_4 = \text{Zero}$$

$$V_1 + V_2 + V_3 + V_4 = \text{Zero}$$

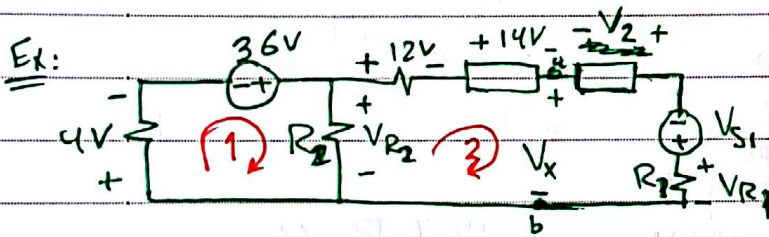


Find $V_x, V_{R2} ??$

KVL @ Mesh 1

$$+4 - 36 + V_{R2} = 0 \Rightarrow V_{R2} = 32 \text{ Volt}$$

KVL @ Mesh 2
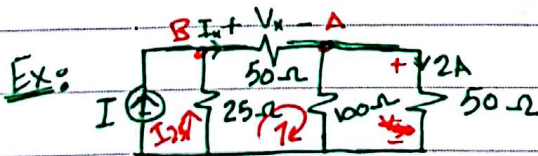
$$-32 + 12 + 14 + V_x = 0 \Rightarrow V_x = 6 \text{ Volt}$$



Find V_x & $I ??$

$$V_{50\Omega} = 2 * 50 = 100 \text{ V}$$

$$V_{50\Omega} = V_{100\Omega} = 100 \text{ V}$$

KCL @ Node A

$$I_x = I_{100\Omega} + I_{50\Omega}$$

$$I_x = 3 \text{ A} \rightarrow V_x = 150 \text{ V}$$

KVL @ Mesh 1

$$25I_{25} + V_x + 100 = 0$$


$$I_{25\Omega} = \frac{-250}{25} = -10 \text{ A}$$

KCL @ Node B

$$I = I_x + I_{25} = 3 - 10 = -7 \text{ A}$$

$$I = 13 \text{ A}$$

* The Single loop circuit:

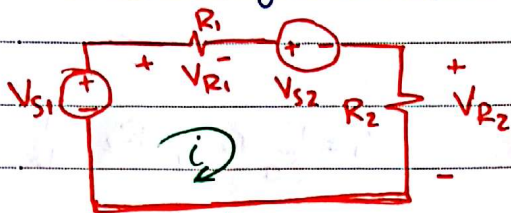

Apply KVL:


$$-V_{S1} + V_{R1} + V_{S2} + V_{R2} = 0$$

$$V_{R1} = iR_1$$

$$V_{R2} = iR_2$$

$$-V_{S1} + iR_1 + V_{S2} + iR_2 = 0$$
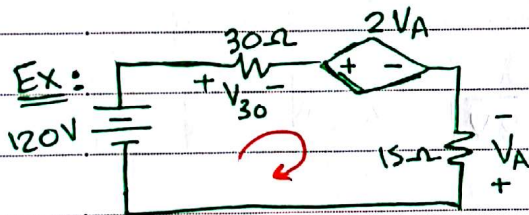
$$i = \frac{V_{S1} - V_{S2}}{R_1 + R_2}$$



Find the Power Absorbed by each element??

Apply KVL

$$-120 + V_{30} + 2VA - V_A = 0$$

$$-120 + V_{30} + V_A = 0$$

$$V_{30} = 30i, \quad V_A = -15i$$

$$-120 + 30i - 15i = 0$$

$$i = 8A$$

P_{abs}

$$P_{120V} = -960 \text{ watt}$$


$$P_{30\Omega} = 30(8)^2 = 1920 \text{ watt}$$

$$P = i^2 R$$

$$P_{2VA} = 2(-15(8))(8) = -1920 \text{ watt}$$

$$P_{15\Omega} = (8)^2 \cdot 15 = 960 \text{ watt}$$

* The Single Node Pair circuit :-

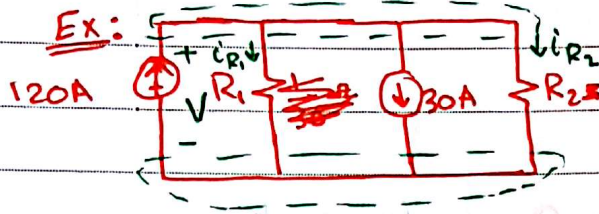

$$R_1 = \frac{1}{30} \Omega, \quad R_2 = \frac{1}{15} \Omega$$

Find Power Absorbed by each element

KCL @ upper Node



$$i_{R1} = \frac{V}{R_1}$$

$$120A = i_{R1} + 30A + i_{R2} \quad \left| \quad i_{R2} = \frac{V}{R_2} \right.$$

$$90 = \frac{V}{R_1} + \frac{V}{R_2}$$

$$90 = 30V + 15V \Rightarrow \boxed{V = 2V}$$

P_{abs}

$$P_{120A} = -120 \cdot 2 = -240 \text{ watt}$$


$$P_{R1} = \frac{(2)^2}{R_1} = \frac{4}{120} \text{ watt}$$

$$P = \frac{V^2}{R}$$

$$P_{R2} = \frac{(2)^2}{R_2} = \frac{4}{15} \text{ watt}$$

$$P_{30A} = 30 \cdot 2 = 60 \text{ watt}$$

Ex:

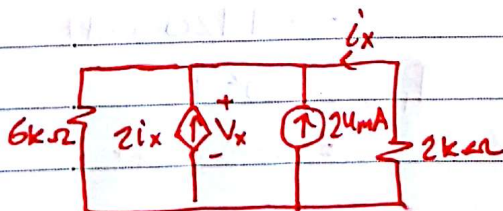


Find V & P_{gen} 24mA ??

Answers:

$$V = 14.4V, \quad P_{\text{gen } 24mA} = 345.6 \text{ mW}$$

* Series & Parallel combinations:

→ Parallel

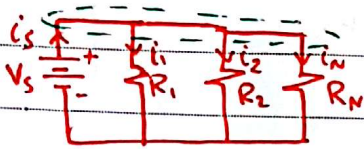


KCL @ upper Node

$$i_s = i_1 + i_2 + \dots + i_N$$

$$i_s = \frac{V_s}{R_1} + \frac{V_s}{R_2} + \dots + \frac{V_s}{R_N}$$

$$i_s = V_s \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right)$$
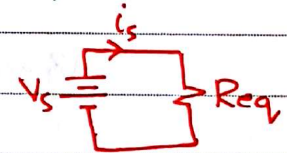
$$R_{eq} = \frac{V_s}{i_s} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$




2 Resistors in Parallel

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$G_{eq} = \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

→ Series

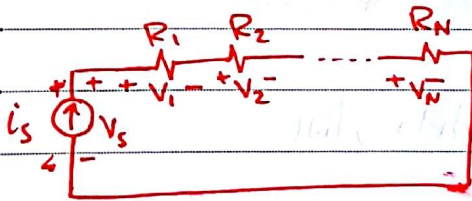

KVL

$$-V_s + V_1 + V_2 + \dots + V_N = 0$$


$$V_s = V_1 + V_2 + \dots + V_N$$

$$= i_s (R_1 + R_2 + \dots + R_N)$$

$$\frac{V_s}{i_s} = R_1 + R_2 + \dots + R_N$$

$$R_{eq} = R_1 + R_2 + \dots + R_N$$

Ex:

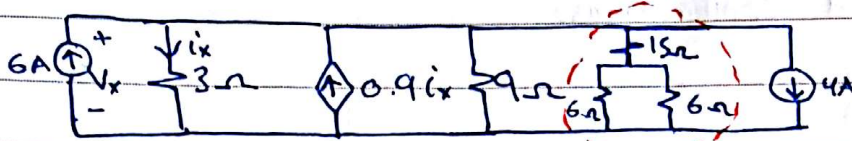


Find $P_{gen\ 6A}$, $P_{gen\ 4A}$, V_x , i_x

$$6\Omega \parallel 6\Omega \rightarrow R_{eq1} = \frac{6 \cdot 6}{12} = 3\Omega$$

$$3\Omega \parallel 15\Omega \rightarrow R_{eq2} = 18\Omega$$
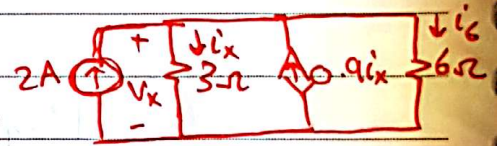
$$18\Omega \parallel 9\Omega \rightarrow R_{eq3} = \frac{18 \cdot 9}{27} = 6\Omega$$



KCL @ upper Node

$$i_x = \frac{V_x}{3}$$

$$i_6 = \frac{V_x}{6}$$

$$2 + 0.9i_x = V_x \left(\frac{1}{3} + \frac{1}{6} \right)$$

$$2 + \frac{9^3}{10} \frac{V_x}{3} = V_x \left(\frac{1}{3} + \frac{1}{6} \right)$$

$$2 + 0.3V_x = \frac{1}{2}V_x$$

$$0.2V_x = 2 \Rightarrow V_x = 10 \text{ Volt}$$

$$\rightarrow i_x = \frac{10}{3} \text{ A}$$

$$P_{gen\ 6A} = 60 \text{ watt}$$


6A

التيار داخل في السالب

$$P_{gen\ 4A} = -40 \text{ watt}$$


4A

التيار داخل في الموجب

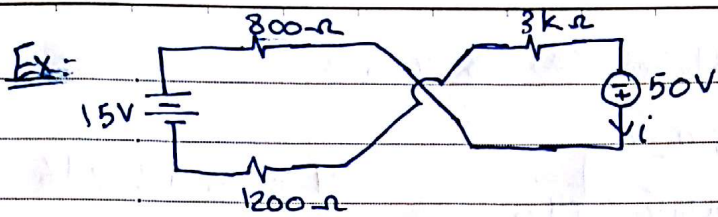

find i ??


Redraw the circuit

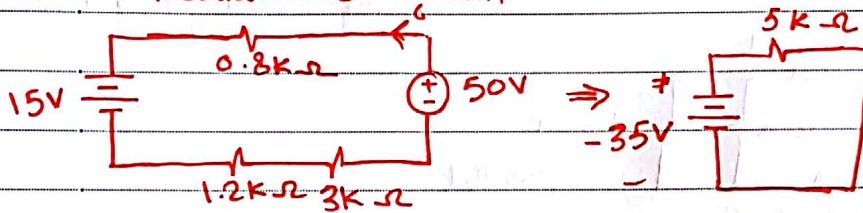

KVL

$$-35 + 5i = 0$$

$$i = \frac{35}{5} = 7A$$

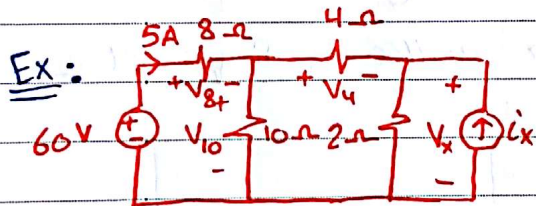

Find V_x, i_x ??


$$V_8 = 5(8) = 40V \quad ; \quad 100 = V_4 + V_x$$

$$V_{10} = V_8 + 60$$

$$V_{10} = 100V$$

$$V_x = 8V, \quad i_x = 1A$$


Ex: Find R_{eq} between (a) & (c)

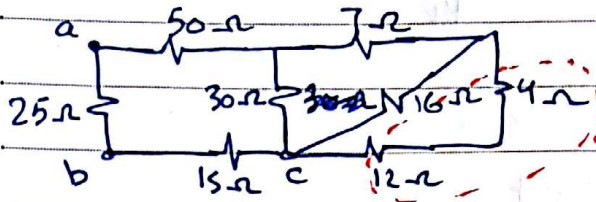

4 Series 12 \Rightarrow 16



16 || 16 \Rightarrow 8

8 Series 7 \Rightarrow 15

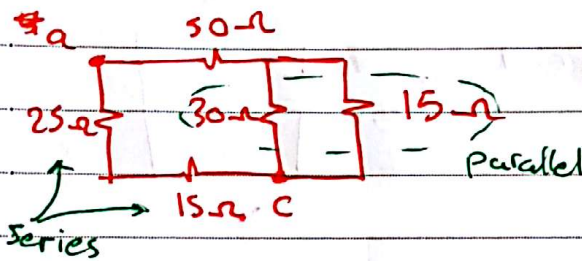

15 || 30 \Rightarrow 10 Ω

25 || 15 \Rightarrow 40 Ω

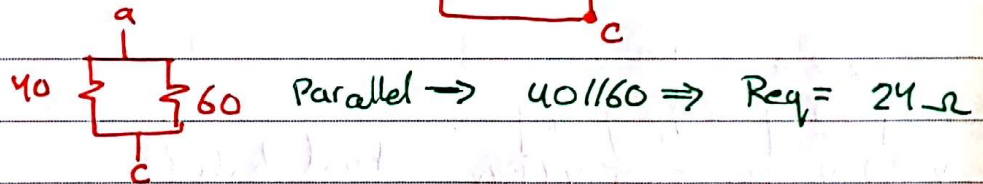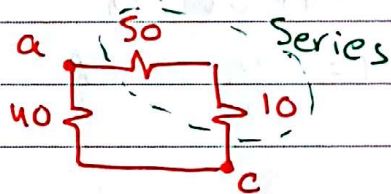


~~Resistive~~

Ex: Find R_{eq} between (a) & (b)

$R_{eq} = 18.75 \Omega$

* Voltage & current division

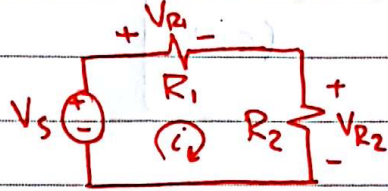⇒ Voltage divider rule (VDR) "Only for Series Elements"



KVL

$$-V_s + V_{R1} + V_{R2} = 0 \quad ; \quad V_{R1} = iR_1 \rightarrow i = \frac{V_{R1}}{R_1}$$

$$V_s = iR_1 + iR_2$$

$$V_s = i(R_1 + R_2)$$

$$V_s = i$$


$$\frac{V_s}{R_1 + R_2}$$

$$V_{R2} = iR_2 \rightarrow i = \frac{V_{R2}}{R_2}$$

$$* \frac{V_{R1}}{R_1} = \frac{V_s}{R_1 + R_2} \Rightarrow V_{R1} = V_s \frac{R_1}{R_1 + R_2}$$

$$* \frac{V_{R2}}{R_2} = \frac{V_s}{R_1 + R_2} \Rightarrow V_{R2} = V_s \frac{R_2}{R_1 + R_2}$$

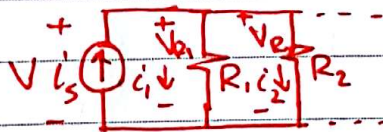⇒ current divider rule ~~VDR~~ (CDR) "only for Parallel Elements"



KCL @ upper Node

$$i_s = i_1 + i_2 + \dots$$

$$i_s = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$V = i_s \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$i_1 = \frac{V_{R1}}{R_1} \rightarrow V_{R1} = i_1 R_1$$

$$i_2 = \frac{V_{R2}}{R_2} \rightarrow V_{R2} = i_2 R_2$$

$$V = V_{R1} = V_{R2}$$


$$i_1 R_1 = i_s \frac{R_1 R_2}{R_1 + R_2} \Rightarrow i_1 = i_s \frac{R_2}{R_1 + R_2}, \quad i_2 = i_s \frac{R_1}{R_1 + R_2}$$

(21)

* for N elements

$$i_k = \frac{R_{eq}}{R_k} \cdot i_s \quad (\text{CDR})$$
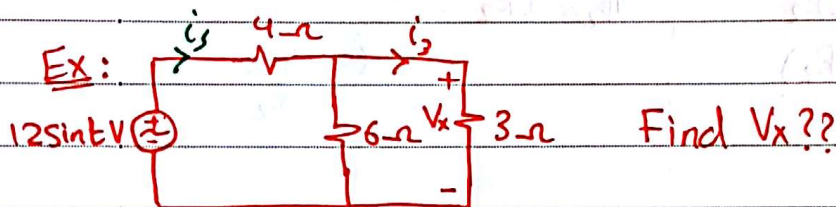
$$V_k = \frac{R_k}{R_{eq}} \cdot V_s \quad (\text{VDR})$$




$$i_s = \frac{12 \sin t}{R_{eq}} = 2 \sin t \quad ; \quad R_{eq} = \frac{3 \cdot 6}{3+6} + 4 = 6 \Omega$$

$$R_{eq} = \frac{3 \cdot 6}{3+6} + 4 = 6$$

$$i_3 = i_s \cdot \frac{6}{3+6}$$

$$i_3 =$$

$$V_x = 3 \cdot i_3$$

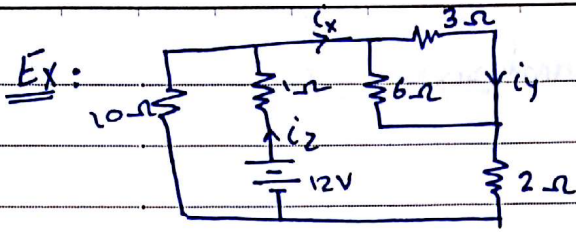

find i_x, i_y, i_z ??


Simplify the ckt

$$R_{eq} = [(3 \parallel 6 + 2) \parallel 10] + 1 \Rightarrow R_{eq} = \frac{27}{7} \Omega$$

$$4 \parallel 10$$


$$i_z = \frac{12}{27/7}$$

$$i_z = \frac{28}{9} \text{ A}$$

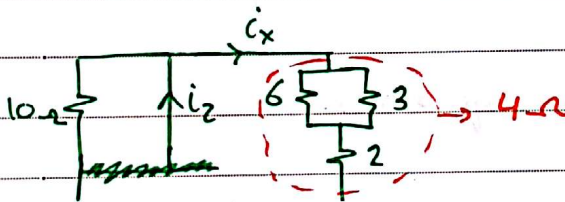


$$i_x = i_z \cdot \frac{10}{10+4} \Rightarrow i_x = \frac{20}{9} \text{ A}$$

(CDR)

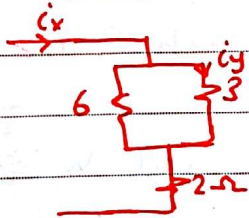

$$i_y = i_x \cdot \frac{6}{3+6} \Rightarrow i_y = \frac{40}{27} \text{ A}$$

(CDR)

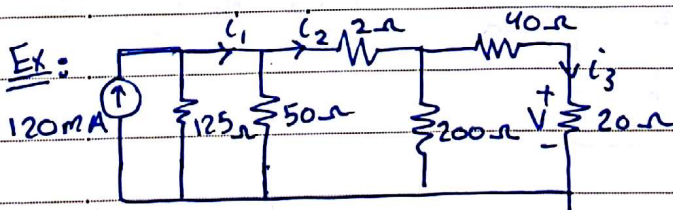

find i_1, i_2, V ??

Solutions: $i_1 = 100 \text{ mA}$

$i_2 = 50 \text{ mA}$

~~i_3~~

$V = 0.8 \text{ V}$

Ch 3: Nodal & Mesh Analysis.

* Nodal Analysis:

* Procedure:-


1) Assume a ckt with N -nodes

Choose one node as a reference.

then write kcl equation for the remaining $(N-1)$ nodes and rename the nodes as V_1, V_2, \dots, V_{N-1}

2) Solve the $N-1$ equations.

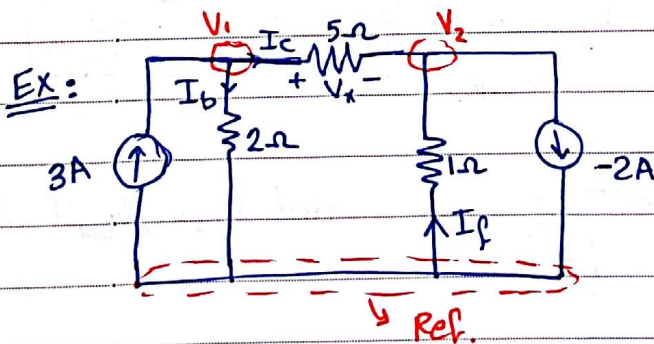3) If a voltage source exists in a circuit, you can form a Super Node, thus reducing the ~~no.~~ of eq.s by 1 for each source, and a replacement eqn should be written for each source.



Find V_x, I_b, I_f using Nodal Analysis??

~~use~~ Kcl eqn @ Node 1

$$-3 + I_b + I_c = 0$$

$$\frac{V_1}{2} + \frac{V_1 - V_2}{5} - 3 = 0 \quad \text{--- ①}$$

$$V_1 \left(\frac{1}{2} + \frac{1}{5} \right) + V_2 \left(-\frac{1}{5} \right) - 3 = 0 \quad \text{--- ①}$$

$$I_b = \frac{V_1 - 0}{2}$$

$$I_c = \frac{V_1 - V_2}{5}$$

KCL @ Node 2

$$-2 + \frac{V_2}{1} + \frac{V_2 - V_1}{5} = 0$$

$$\boxed{-2 + V_2 \left(1 + \frac{1}{5}\right) + V_1 \left(-\frac{1}{5}\right) = 0} \quad \text{--- ②}$$

You can solve eqns ① & ② by الحزب والتعويض

$$0.7V_1 - 0.2V_2 = 3$$


$$-0.2V_1 + 1.2V_2 = 2$$

$$\Rightarrow \left\{ \begin{array}{l} V_1 = \frac{3 + 0.2V_2}{0.7} \end{array} \right.$$

$$\boxed{V_1 = 5V}, \quad \boxed{V_2 = 2.5V}$$

$$V_x = V_1 - V_2 = 2.5V, \quad I_b = \frac{V_1}{2} = 2.5A, \quad I_f = \frac{-V_2}{1} = -2.5A$$

Ex:

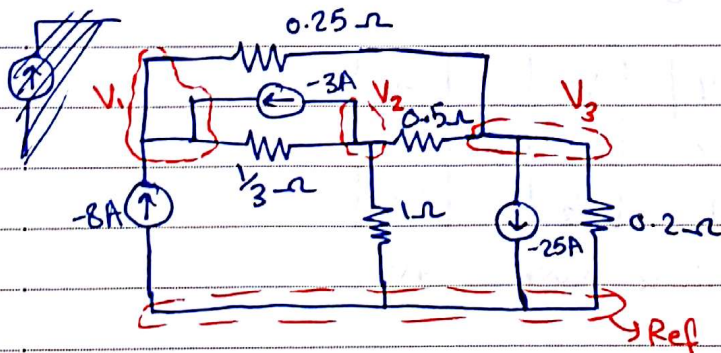

Find the Nodal Voltages ??

* 3 kcl eqns.

* kcl @ Node 1

$$8 + 3 + \frac{V_1 - V_2}{1/3} + \frac{V_1 - V_3}{0.25}$$

$$\boxed{V_1(3 + 4) + V_2(-3) + V_3(-4) = -11} \quad \text{--- ①}$$

* KCL @ Node 2

$$\frac{V_2}{1} + -3 + \frac{V_2 - V_1}{\frac{1}{3}} + \frac{V_2 - V_3}{0.5} = 0$$

$$\boxed{V_1(-3) + V_2(1 + 3 + 2) + V_3(-2) = 3} \quad \text{--- (2)}$$

* KCL @ Node 3

$$-25 + \frac{V_3}{0.2} + \frac{V_3 - V_2}{0.5} + \frac{V_3 - V_1}{0.25} = 0$$


$$\boxed{V_1(-4) + V_2(-2) + V_3(5 + 2 + 4) = 25} \quad \text{--- (3)}$$

Solve using matrix

$$\begin{bmatrix} 7 & -3 & -4 \\ -3 & 6 & -2 \\ -4 & -2 & 11 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -11 \\ 3 \\ 25 \end{bmatrix}$$

↳ these must be +ve.

Ex:

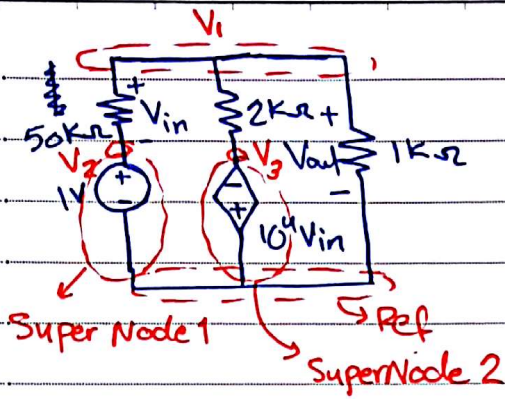

Find the Node to Ref Voltages

KCL @ Node 1

$$\frac{V_1 - V_2}{50} + \frac{V_1 - V_3}{2} + \frac{V_1}{1} = 0$$

$$\frac{V_1 - 1}{50} + \frac{V_1 - (-10^4(V_1 - V_2))}{2} + \frac{V_1}{1} = 0$$

$$V_2 = 1V$$

$$V_3 = -10^4 V_1$$

$$V_{in} = V_1 - V_2$$

$$V_1 \left(\frac{1}{50} + \frac{1+10^4}{2} + 1 \right) = \frac{1}{50} + \frac{10^4}{2} \Rightarrow V_1 = 0.9997V$$

$$V_3 = -10^4(V_1 - 1)$$

$$V_3 = 2.999V$$

$$V_{out} = V_2$$

Resolve with the Ref bottom Node


$$V_1 = 102.52V, V_2 = -63. V$$

$$Ref \leftarrow V_3 = 36.52V$$

$$V_1 = 66V$$

$$V_2 = -100V$$

Ex:

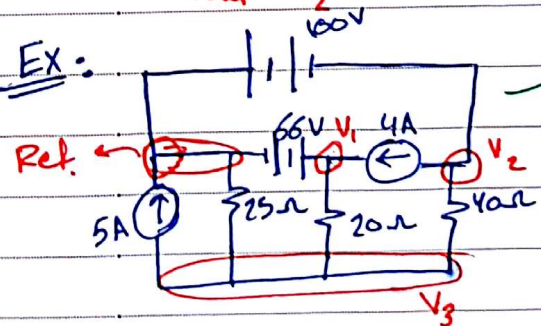

KCL @ Node 3

$$5 + \frac{V_3}{25} + \frac{V_3 - V_1}{20} + \frac{V_3 - V_2}{40} = 0$$

$$V_3 = -36.52V$$

$$\leftarrow V_3 \left(\frac{1}{25} + \frac{1}{20} + \frac{1}{40} \right) = -5 + \frac{66}{20} + \frac{100}{40}$$


* Mesh Analysis

Only applied for a planar circuits

Procedure:

- ① Assume a circuit with M -meshes
Assign a mesh current inside each mesh i_1, i_2, \dots, i_m .
- ② write KVL eq.s for each Mesh (M -eq.s)
- ③ Solve M -eq.s, to find M -unknown
- ④ if a circuit contains a current source, create a Super Mesh for each current (by applying KVL around the larger loop formed by the branches that are not common to the meshes).
- ⊗ KVL eq. not needed if the current source is \perp on the \downarrow of the circuit.
parameter

Ex: Find the Mesh currents.

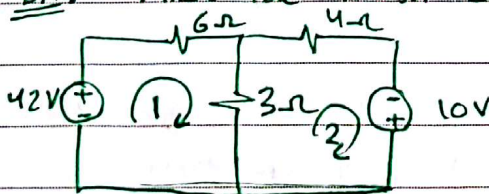

$$i_1 = 6A$$

$$i_2 = 4A$$

$$\text{KVL eq. for Mesh-1}$$

$$\rightarrow -42 + 6i_1 + 3(i_1 - i_2) = 0$$


$$\boxed{9i_1 - 3i_2 = 42} \quad \text{--- (1)}$$

$$\text{KVL eq. for Mesh-2}$$

$$3(i_2 - i_1) + 4i_2 - 10 = 0$$

$$\boxed{7i_2 - 3i_1 = 10} \quad \text{--- (2)}$$

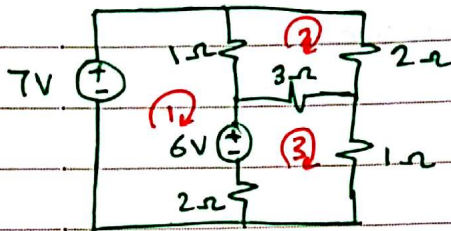Ex: Use Mesh analysis to find the Mesh currents.



KVL eq. for Mesh 1

$$-7 + 1(i_1 - i_2) + 6 + 2(i_1 - i_3)$$

$$\textcircled{1} \quad 3i_1 - i_2 - 2i_3 = 1$$

KVL eq. for Mesh 2

$$1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$$

$$\textcircled{2} \quad -i_1 + 6i_2 - 3i_3 = 0$$

KVL eq. for Mesh 3


$$2(i_3 - i_1) - 6 + 3(i_3 - i_2) + i_3$$

$$\textcircled{3} \quad -2i_1 - 3i_2 + 6i_3 = 6$$

$$i_1 = 3A$$

$$i_2 = 2A$$

$$i_3 = 3A$$

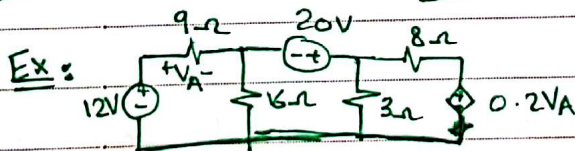


$$i_1 = 2.621A$$

$$i_2 = 3.265A$$

$$i_3 = 0.462A$$

Ex: Find the three Mesh currents & V_x

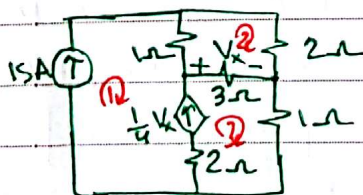

$i_1 = 15A \rightarrow$ Super Node

KVL eq. @ Mesh 2

$$1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3)$$

$$-15 + 6i_2 - 3i_3 = 0$$

$$\textcircled{1} \quad 6i_2 - 3i_3 = 15$$

KVL eq. @ Mesh 3

$$3(i_3 - i_2) + i_3 + 2(i_3 - i_2)$$

$$i_3 - i_1 = \frac{1}{9} V_x$$

$$V_x = 3(i_3 - i_2)$$

$$i_3 - 15 = \frac{1}{9} V_x$$

$$i_3 - 15 = \frac{3}{9} (i_3 - i_2)$$

$$\frac{2}{3} i_3 + \frac{1}{3} i_2 = 15 \quad \text{--- (2)}$$

by eq.s ① & ②


$$i_1 = 15A$$

$$i_2 = 11A$$

$$i_3 = 17A$$

$$V_x = 18V$$

Ex:

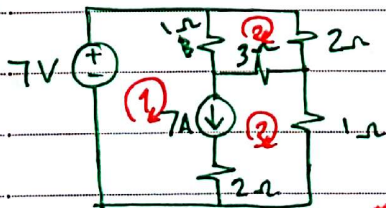

Find the Mesh Currents.

Super Mesh

$$i_1 - i_3 = 7A \quad \text{--- (1)}$$

~~Mesh~~ KVL eq. @ Super Mesh 1,3

$$-7 + 1(i_1 - i_2) + 3(i_3 - i_2) + 3i_3 = 0$$

$$i_1 - 4i_2 + 3i_3 = 7 \quad \text{--- (2)}$$

KVL eq. @ Mesh 2

$$1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$$


$$i_1 = 9A$$

$$i_2 = 2.5A$$

$$i_3 = 2A$$

$$-i_1 + 6i_2 - 3i_3 = 0 \quad \text{--- (3)}$$

* Nodal v.s Mesh Analysis

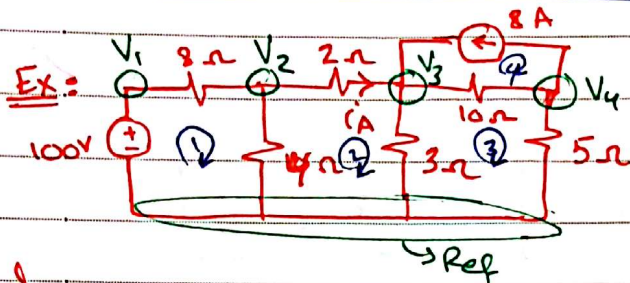

Find i_A ??

Nodal

$$V_1 = 100V$$

Node 2

$$\frac{V_2 - 100}{8} + \frac{V_2}{4} + \frac{V_2 - V_3}{2} = 0$$

Node 3

$$\frac{V_3 - V_2}{2} + \frac{V_3}{3} + \frac{V_3 - V_4}{10} = 8$$

Node 4

$$\frac{V_4 - V_3}{10} + \frac{8}{5} V_4 + 8 = 0$$

$$V_2 = 25.89V$$

$$V_3 = 20.31V$$

$$V_4 = 19.89V$$

$$i_A = \frac{V_2 - V_3}{2} = 2.79A$$

Mesh

Mesh 1

$$-100 + 8i_1 + 4(i_1 - i_2) = 0$$

Mesh 2

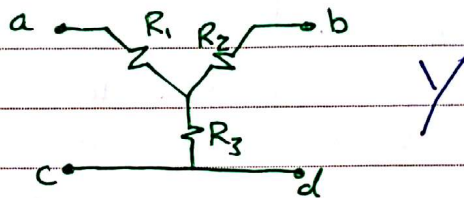
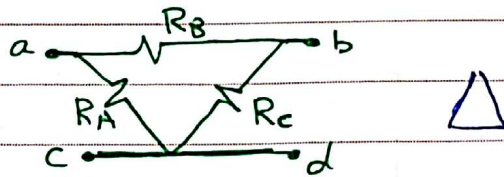
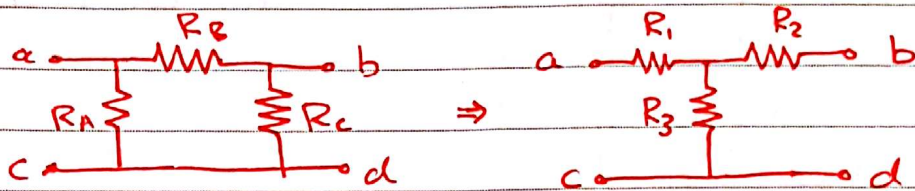
$$4(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$$

Mesh 3

$$3(i_3 - i_2) + 10(i_3 + 8) + 5i_3 = 0$$

$$i_4 = 8A$$

Delta to Wye Conversion:

 $Y \rightarrow \Delta$ R_1, R_2, R_3 known

$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$


$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

 $\Delta \rightarrow Y$ R_A, R_B, R_C known

$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$


$$R_2 = \frac{R_B R_C}{R_A + R_B + R_C}$$
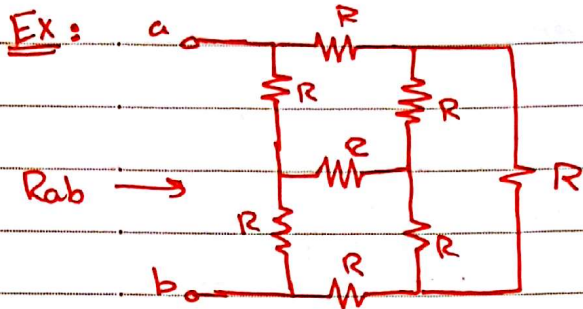
$$R_3 = \frac{R_A R_C}{R_A + R_B + R_C}$$




$R = 10 \Omega$
All R's are 10Ω


$R_{ab} \rightarrow$

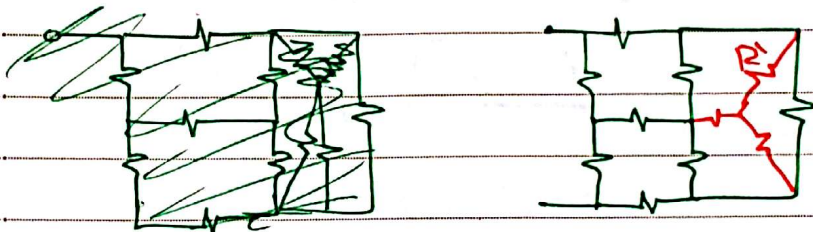
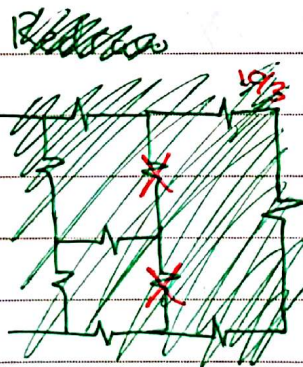
$$R' = \frac{10 \cdot 10 + 20 \cdot 10}{10 + 10 + 10} = \frac{10}{3}$$



* Redraw

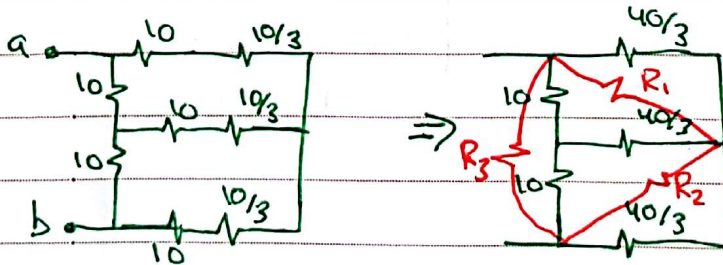


$$R_1 = \frac{10 \cdot \frac{40}{3} + 10 \cdot \frac{40}{3} + 10 \cdot 10}{10}, \quad R_2 = \frac{10 \cdot \frac{40}{3} + 10 \cdot \frac{40}{3} + 10 \cdot 10}{\frac{40}{3}}$$

$$R_2 = R_1$$

$$R_1 = R_2 =$$

~~Another method of solving~~


Another way to solve this ckt

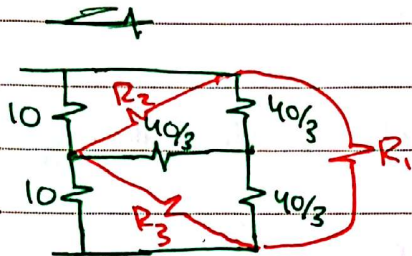


$$R_1 = R_2 = R_3 = \frac{(40/3 \cdot 40/3) + 3}{40/3}$$

$$R_1 = R_2 = R_3 = 40 \Omega$$

Redraw

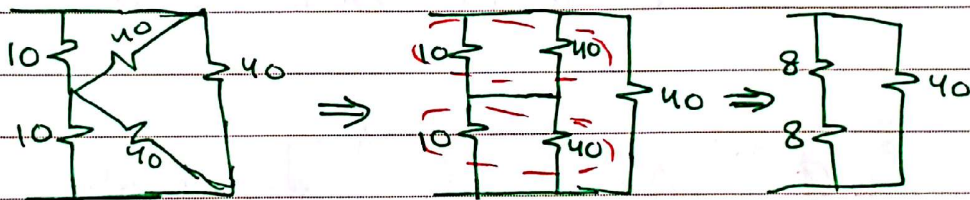
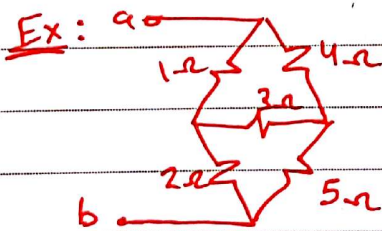
$$40 \parallel 16 \Rightarrow R_{ab} = 11.43 \Omega$$



$$R_{ab} = 1.74 \Omega$$


Ch.4 Useful Circuit Analysis techniques.

* Linearity & Superposition


any linear circuit consists of the following

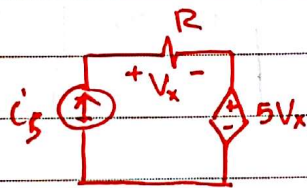- 1) Independent Sources. (Forcing function)
- 2) Linear dependent Sources. $\diamond AV_x$
- 3) Linear passive circuit elements.

\hookrightarrow the loads must all be resistive.




Linear

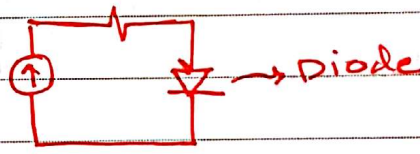

Non-linear

* Superposition

Ex: Find i_x using S.P

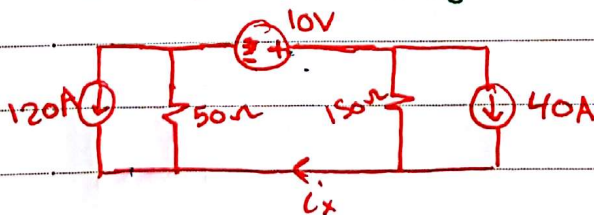


S.P: only one independent source should be active at a time.

* To kill a Source

- If the Source is Voltage Source replace it with Short circuit.

- If the Source is Current Source replace it with open circuit.

For 120A only

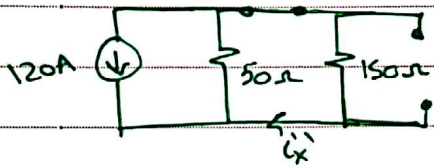


i_x'
by current Divide rule

$$i_x' = -120 \cdot \frac{50}{200}$$

$$i_x' = -30 \text{ A}$$

for 40A only

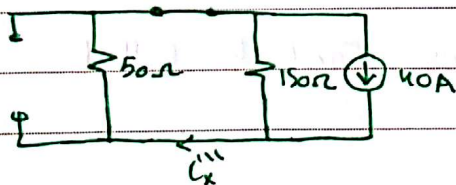


i_x''
by CDR

$$i_x'' = 40 \cdot \frac{150}{200}$$

$$i_x'' = 30 \text{ A}$$

for 10V only

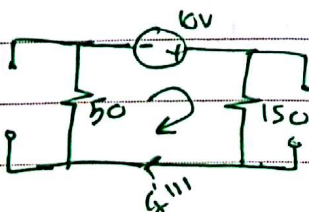


i_x'''
KVL

$$i_x''' = \frac{10}{200}$$



$$i_x''' = 50 \text{ mA}$$
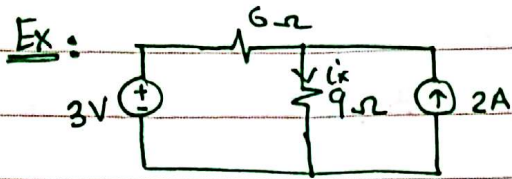
$$i_x = i_x' + i_x'' + i_x''' = 50 \text{ mA}$$



Find i_x Using S.P

$$i_x = 1A$$

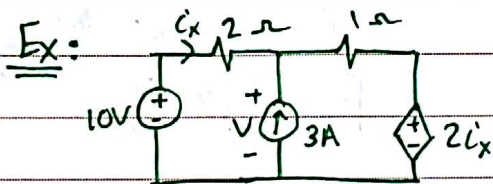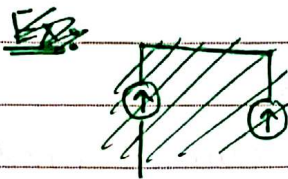


Find i_x & V using S.P.

~~Independent~~

* Independent Sources can't be killed.

① for 10V only

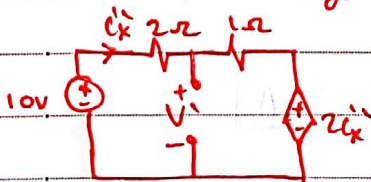

KVL


$$i_x = \frac{10 - 2i_x}{3}$$

$$i_x = 2A$$

$$V' = 10 - 2i_x$$

$$V' = 6V$$

② for 3A only

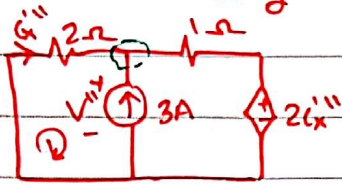

kcl @ upper node

$$\frac{V''}{2} + \frac{V'' - 2i_x''}{1} = 3$$

$$\boxed{\frac{3}{2}V'' - 2i_x'' = 3} \text{ --- ①}$$

kvl @ Mesh 1

$$\boxed{V'' - 2i_x'' = 0} \text{ --- ②}$$



~~V = 6V~~ V''


$$V = V' + V''$$

$$i_x = i_x' + i_x''$$


* S.P can't be applied for non-linear elements, sources or quantities such as Power.

* Source Transformation:

* Ideal Voltage Source

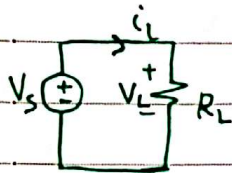


* Practical Voltage Source

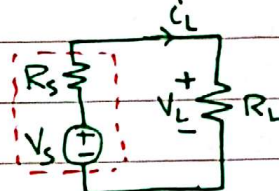

KVL : $-V_s + i_L R_s + V_L = 0$


$V_L = V_s - i_L R_s$

$V_L = 0 \Rightarrow i_L R_s = V_s$

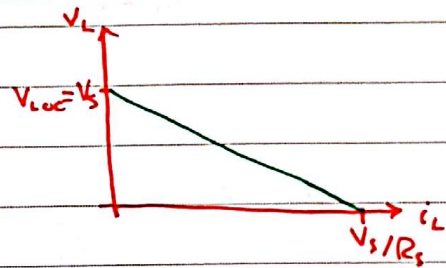


If $I_L = 0 \rightarrow$ o.c

$V_L = V_s = V_{Loc}$

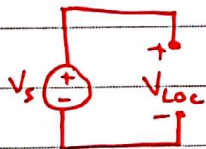

If $V_L = 0 \Rightarrow$ s.c

$i_L = \frac{V_s}{R_s} = i_{Loc}$

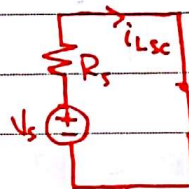


If $R_s = R_L$


$V_L = V_s \cdot \frac{R_L}{R_s + R_L}$

at $R_s = R_L \Rightarrow V_L = V_s / 2$

* Ideal current Source

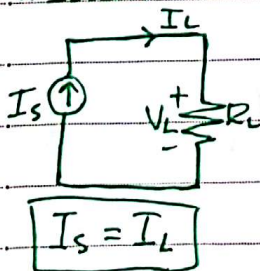

* Practical current Source

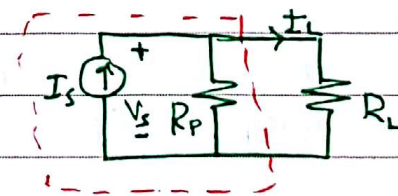

$I_L = I_s \frac{R_p}{R_p + R_L}$, $V_L = V_s$

$I_L = I_s - \frac{V_s}{R_p}$


(39)

~~$I_L = I_s - \frac{V_L}{R_p}$~~

$$I_L = I_s - \frac{V_L}{R_p}$$

at $V_L = 0 \Rightarrow V_s = 0 \Rightarrow$ S.C $\rightarrow V_L = V_s$
 $\rightarrow R_L = 0$

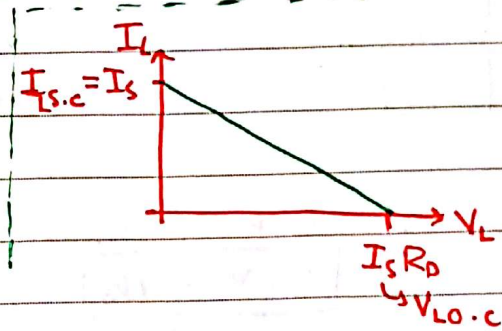
at $I_L = 0 \Rightarrow$ O.C $I_{s.c} = I_s$
 $\rightarrow R_L = \infty$



$$I_L = I_s \frac{R_p}{R_p + R_L}$$

\gg i.f $R_p = R_L$
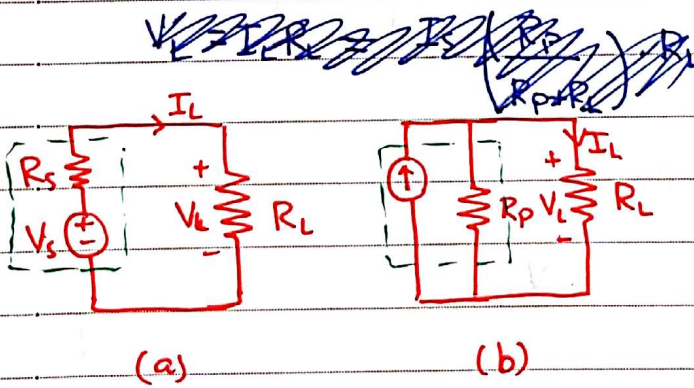
$$I_L = I_s \frac{R_p}{R_p + R_p} = I_s / 2$$




$$V_L = I_L R_L$$

(a) $V_L = \frac{V_s}{R_s + R_p} R_L$ equal (b) $V_L = I_s \left(\frac{R_p}{R_p + R_L} \right) R_L$


* $R_s = R_p$

$\Rightarrow V_s = I_s R_s = I_s R_p$

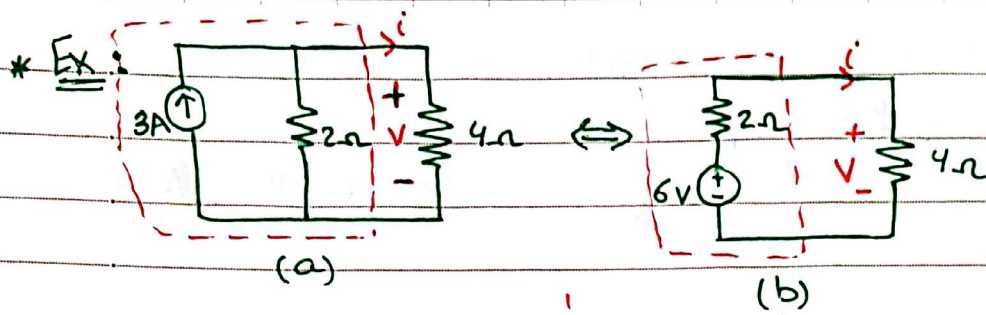


$i = \frac{3(2)}{6} = 1A$ (CDB) $i = \frac{6}{6} = 1A$ (KVL)

$V = 4V$ $V = 4V$
 $P = 4W$ $P = 4W$

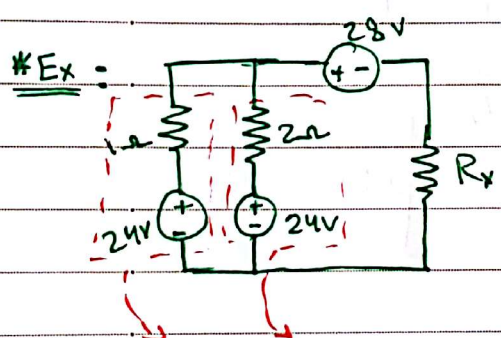

Find R_x
 that absorb 5w ??
 "using S.T"

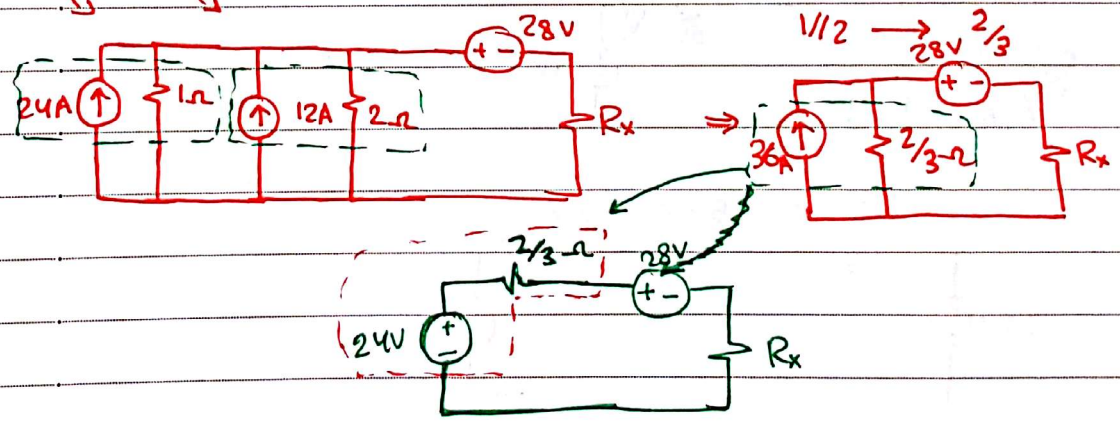

KVL eq

$-24 + \frac{2}{3}I + 28 + IR_x = 0$


$I^2 R_x = 5W$ → from R_x absorb 5w

$(\frac{2}{3} + R_x)I = -4$ --- ①

from ①, ② we find eqs





$R_x = 1.587\Omega$
 $R_x = 0.28\Omega$ → both are the solution, if one is negative ⇒ neglected

* Ex: Find I_x using S.T

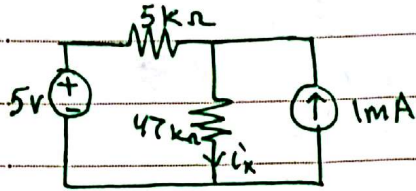

$$I_x = 0.192 \text{ mA}$$

Ex: Find I, V_x using S.T

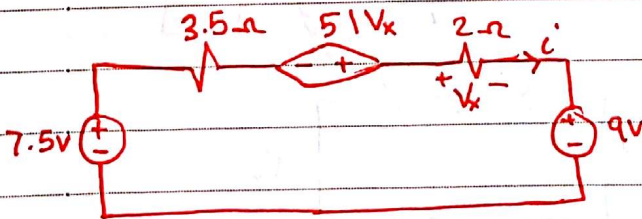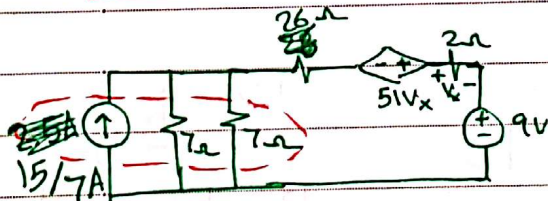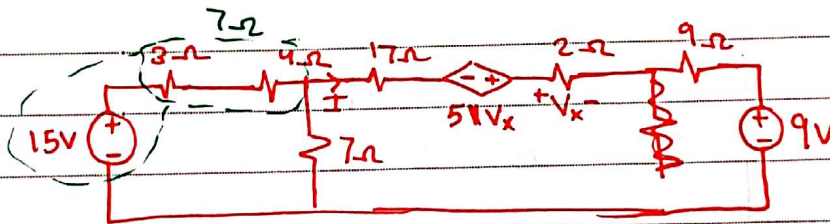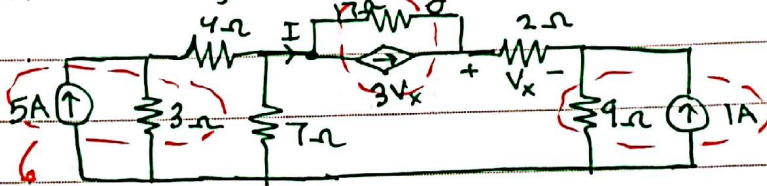

KVL

$$-7.5 + 3.5i - 5I_x + 2i + 9 = 0 \Rightarrow 5.5i - 5I_x = -1.5 \quad \text{--- (1)}$$

$$V_x = 2i \quad \text{--- (2)}$$

$$V_x = 42.56 \text{ mV}$$

$$i = 21.28 \text{ mA}$$

(42)

لغون العبد


* Thevenin & Norton's equivalents:

>> If a variable load exists in the circuit

>> If you are interested in a partial of the circuit

→

→ Applied for linear circuits.

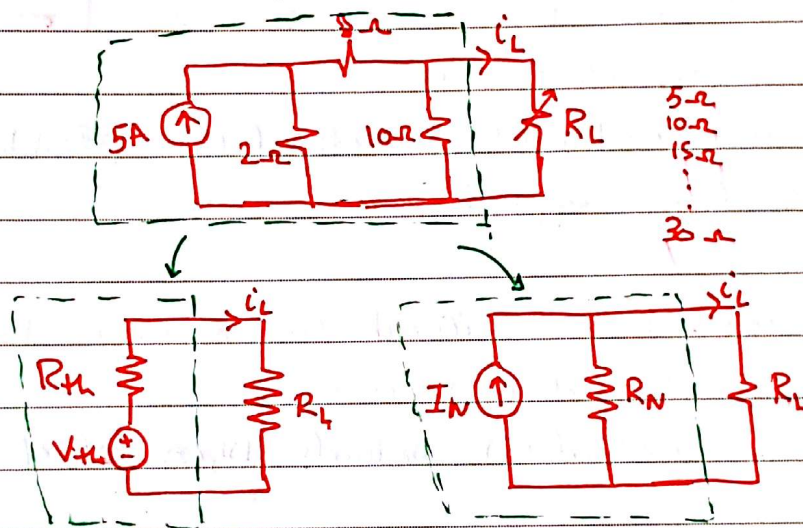

$$R_{th} = R_N$$

$$V_{th} = I_N R_N$$

$$I_N = \frac{V_{th}}{R_{th}}$$

* methods to find thevenin's or Norton's equivalent:

1) R_{th} & V_{th} or R_N & I_N

2) V_{oc} & I_{sc}


3) $V_{test} = 1V$ or $I_{test} = 1A$

* When to use these methods??



Case 1: If a circuit contains only Resistors and V, I Sources.

Use method (1), but methods (2) & (3) are possible.

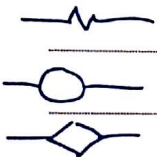

Case 2: If a circuit contains Resistors, V, I Sources & V, I dependent Sources.


Use method (2), method (3) possible, method (1) can't be applied.



Case 3: If a circuit contains only Resistors & V, I dependent Sources.

Use method (3), methods (1), (2) can't be applied.

* Ex: Find the Thevenin's

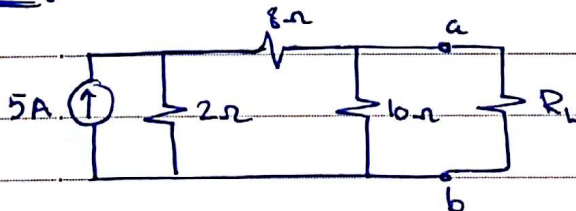

* R_{th}

Disconnect R_L , then Kill the Sources.




$$R_{th} = 10 \parallel (8+2)$$



$$R_{th} = 5 \Omega$$

* V_{th} Disconnect R_L , then find V_{oc} .


$$V_{th} = V_{oc}$$

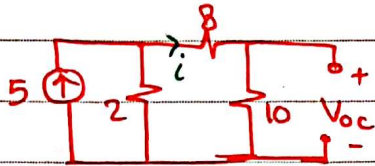
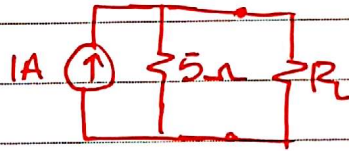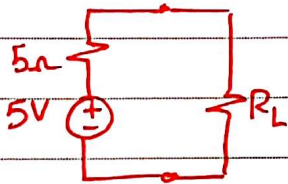
$$i = 5 \times \frac{2}{20} = \frac{1}{2} \text{ A}, \quad V_{oc} = 10 \times \frac{1}{2} = 5 \text{ V}$$



Ex:

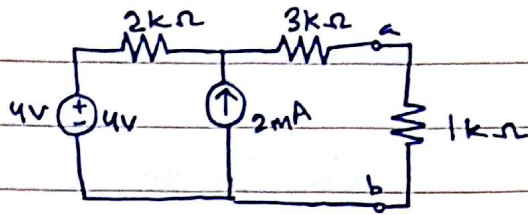

Find thevenin's (on method (1))

~~Remove~~ between a & b


1) Remove R_L

2) Kill the sources to find R_{th}

3) Place O.C if thevenin's eq. (find V_{oc})


= S.C if Norton's eq. (find i_{sc})

Solve by thevenin

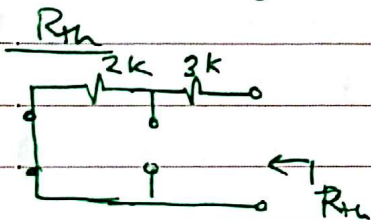

$$R_{th} = 2k + 3k = 5k\Omega$$

$$R_{th} = 5k\Omega$$

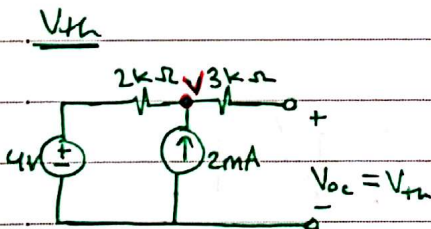


$$V = V_{oc} = V_{th}$$

*Solve by Nodal


$$\frac{V-4}{2k} = 2 \Rightarrow V = 8V$$

$$V_{th} = 8V$$


thevenin eq.

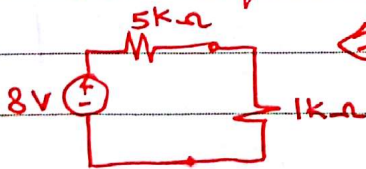

Norton's eq.

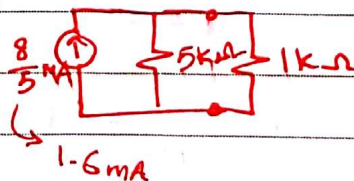

Resolve by Norton

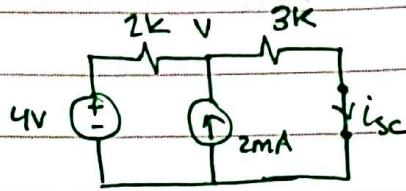


$$i_{sc} = \frac{V}{3k}$$

Solve by Nodal

$$\frac{V-4}{2} + \frac{V}{3} = 2 \Rightarrow V =$$
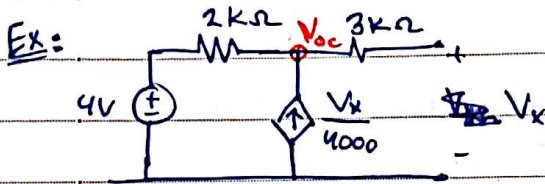
$$i_{sc} = \frac{V}{3k} = 1.6 \text{ mA}$$



find thevenin's eq. between the terminals.
(on method (2))

$$R_{th} = \frac{V_{oc}}{i_{sc}} = \frac{V_{th}}{i_N}$$

$$\frac{V_{oc}}{V_{oc} = V_x}$$



$$\frac{i_{sc}}{i_{sc}}$$



by Nodal

$$\frac{V_x - 4}{2000} = \frac{V_x}{4000}$$

$$2V_x - 8 = V_x$$

$$V_x = 8V$$

$$V_{th} = V_{o.c} = V_x = 8V$$


$V_x = 0$, so dependent i_s is o.c



$$i_{sc} = \frac{4}{5} = 0.8 \text{ mA}$$
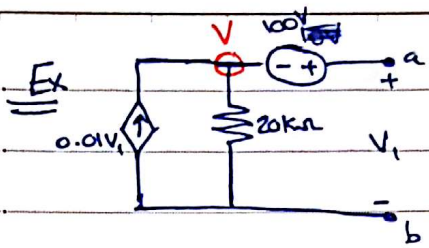
$$R_{th} = R_N = \frac{V_{th}}{i_N} = 10k\Omega$$






Find thevenin's eq. between a & b.

Voc, isc

Voc

$V_1 = V_{oc}$

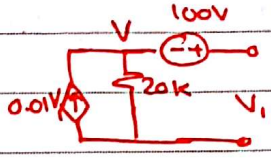

~~Method~~


Nodal

$V = V_1 - 100$ --- ①


$\frac{V}{20k} = 0.01V_1$ --- ②

$V_1 = V_{oc} = \frac{-100}{199} V = -502.5 mV$

isc

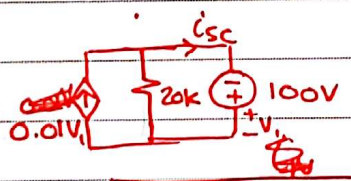


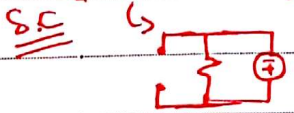$V_1 = 0 \Rightarrow I_{sc} = \frac{100}{20k} = 5 mA$




$R_{th} = R_N = \frac{V_{th}}{I_N} = \frac{-502.5}{5} = -100.5 \Omega$

Ex on method (3)

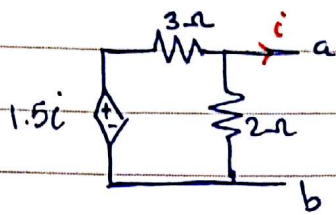

Find Thevenin's eq.

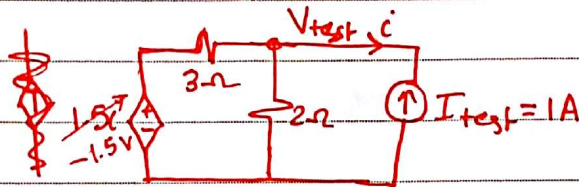- ① Assume ~~V_{test}~~ $V_{test} = 1V$ or $i_{test} = 1A$
- ② find i_{test} or V_{test}
- ③ $R_{th} = \frac{V_{test}}{i_{test}}$




$i = -1A$, V_{test} by Nodal


$$\frac{V - (-1.5)}{3} + \frac{V}{2} = 1 \Rightarrow \boxed{V_{test} = 0.6V}$$

$$\boxed{R_{th} = 0.6 \Omega} \rightarrow \frac{V_{test}}{i_{test}}$$

Thevenin eq.

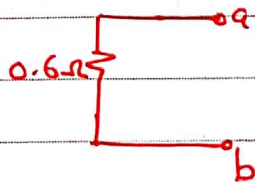


Ex:

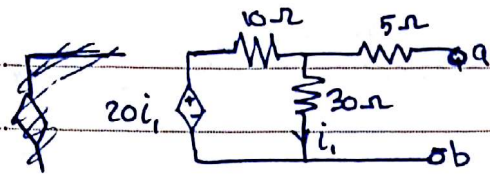

Find Thevenin's eq.

assume $V_{test} = 1V$

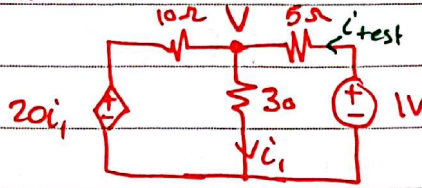

by Nodal

$$\frac{V-1}{5} + \frac{V-20i_1}{10} + \frac{V}{30} = 0 \quad \text{--- (1)}$$


$$i_1 = \frac{V}{30} \quad \text{--- (2)}$$

$$V = 0.75V$$

we find i_{test} ~~test~~ ~~test~~ ~~test~~ ~~test~~ ~~test~~


$$\Rightarrow i_{test} = \frac{1-V}{5} = 50mA$$

Thevenin's eq.

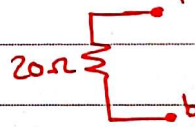

$$R_{th} = \frac{0.75}{50mA} = 20\Omega$$

* Maximum Power Transfer:

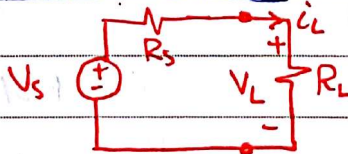

$$P_L = V_L \cdot i_L = i_L^2 \cdot R_L, \quad i_L = \frac{V_s}{R_s + R_L}$$

$$P_L = \frac{V_s^2}{(R_s + R_L)^2} \cdot R_L$$

$$P_L \text{ max ??} \Rightarrow \frac{dP_L}{dR_L} = 0$$

~~$$\frac{dP_L}{dR_L} = \frac{V_s^2 R_L}{(R_s + R_L)^2}$$~~


$$\frac{dP_L}{dR_L} = \frac{(R_S + R_L)^2 V_S^2 - V_S^2 R_L (2(R_S + R_L))}{(R_S + R_L)^4} = 0$$

$$\Rightarrow (R_S + R_L)^2 V_S^2 = V_S^2 2R_L (R_S + R_L)$$

$$R_S^2 + 2R_L R_S + R_L^2 = 2R_L R_S + 2R_L^2$$

* $R_S = R_L$ for max Power Transfer

* i.e

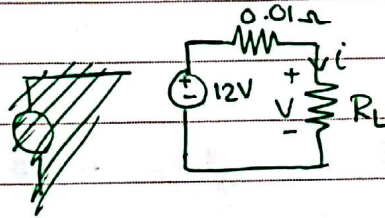

$$R_L = 0.01$$


$$i = \frac{12}{2(0.01)} \Rightarrow i = 600$$

$$V = 6V \quad (\text{VDR})$$

≠

$$P_{L\max} = \frac{V_L^2}{R_L} = \frac{36}{0.01} = 3.6 \text{ kW}$$

* i.e

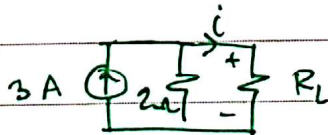


$$i = 3 \cdot \frac{2}{2 + R_L}$$

$$R_L = 2 \Omega$$

$$i = 4.5 \text{ A}$$

$$P_{L\max} = i^2 R = 4.5 \text{ kW}$$

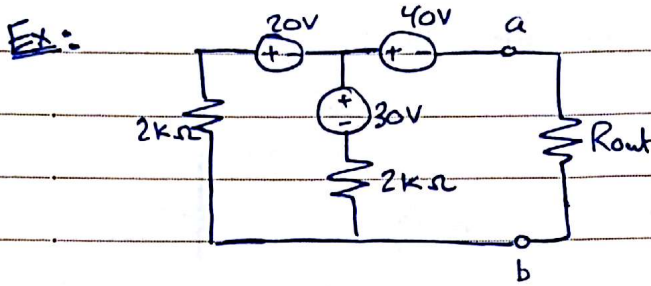


- a) Find P_{out} if $R_{out} = 3k\Omega$
- b) Find R_{out} that will absorb Maximum Power Transfer
- c) Find R_{out} if $P_{out} = 20mW$

We solve by Thevenin (method 1)


~~But find this~~

R_{th} (Remove R_{out} , kill the sources)

$R_{th} = 2 // 2 = 1k\Omega$

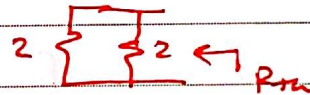

V_{th} (Remove R_{out} , find V_{oc})

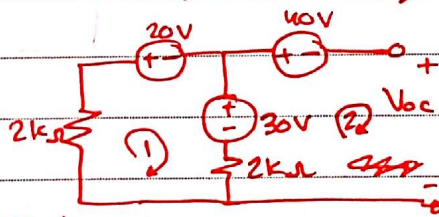

KVL @ Mesh 1

~~But find this~~

$+30 + 2i + 2i + 20 = 0$

$i = -\frac{50}{4} mA$


KVL @ Mesh 2

$+40 + V_{oc} - 2i - 30 = 0$

$V_{oc} = -10 - \frac{-100}{4}$

$V_{oc} = -35V$

$V_{th} = -35V$, $R_{th} = 1k\Omega$

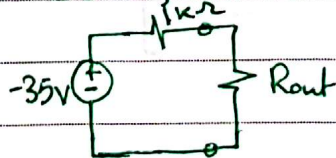


a) $P_{out} = i^2 R_{out} = \frac{V^2}{R_{out}} = \frac{(-35)^2}{1+3} = \frac{(-35 + \frac{3}{1+3})^2}{3}$

$P_{out} = 239.69mW$

b) $R_{out} \text{ (max Power)} = R_{th} = 1k\Omega$

c) $R_{out} = \frac{V^2}{P_{out}}$

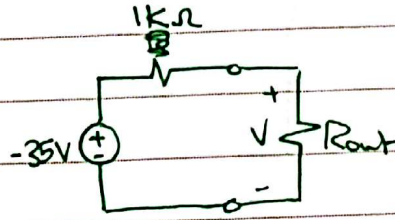


~~V = -35 * R_out / (R_out + 1)~~

$R_{out} = \frac{(-35)^2}{20m} \left(\frac{R_{out}}{R_{out}+1} \right)^2 \Rightarrow \begin{cases} R_{out} = 59.2k\Omega \\ R_{out} = 16.88k\Omega \end{cases}$

$\frac{R_{out}(R_{out}+1)^2}{(R_{out})^2} = \frac{(-35)^2}{20m}$

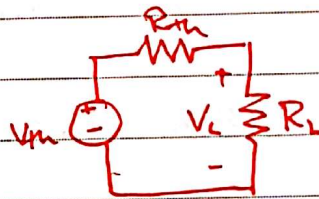* $P_{max} = \frac{V_L^2}{R_L}$, $R_L = R_{th}$



~~$V_L = V_{th} * \frac{R_L}{R_L + R_{th}}$~~

$V_L = V_{th} * \frac{R_L}{R_L + R_{th}}$, $P_{max} = \frac{\left(V_{th} * \frac{R_L}{R_L + R_{th}} \right)^2}{R_L}$

~~Process~~

$P_{max} = \frac{V_{th}^2 R_L^2}{4R_L^2 R_L}$

$P_{max} = \frac{V_{th}^2}{4R_{th}}$


Ch6: Capacitors & Inductors:

* They are storing elements.

* Capacitors:

$$v \propto \int i dt \Rightarrow \boxed{V = \frac{1}{C} \int i dt}$$

C: capacitor

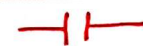

$$V = \frac{1}{C} \int i dt$$




$$dV = \frac{1}{C} i dt$$

$$\boxed{i = \frac{C dv}{dt}}, \quad i = \frac{dq}{dt}$$

$$\frac{dq}{dt} = \frac{C dv}{dt}$$

$$\boxed{C = \frac{Q}{V}}$$

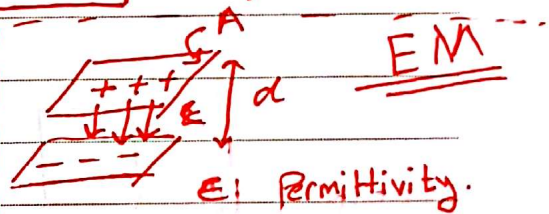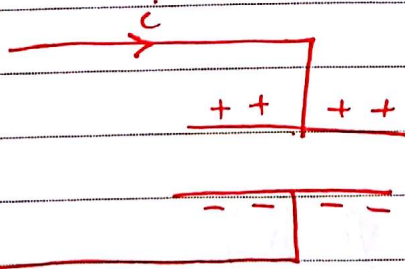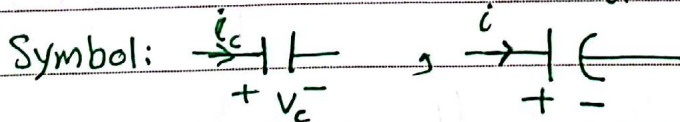Unit is Farad [F] or $\left[\frac{C}{V}\right]$



$$\epsilon = \epsilon_0 \epsilon_r$$

ϵ_0 : Permittivity for Air

ϵ_r : Relative Permittivity.

$$C = \frac{\epsilon A}{d} [F]$$

1F is a very big capacitor.

$C \rightarrow \mu F, nF, pF$



In Circuit lab



$$i = C \frac{dv}{dt}$$

if $V = \text{constant}$ or $V = 0$

$i = \text{zero}$ (open circuit)
to DC

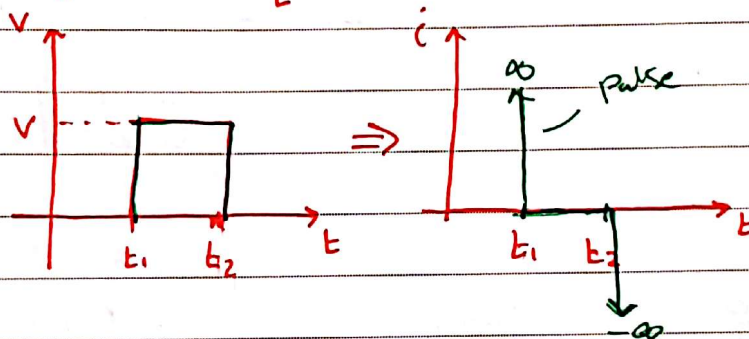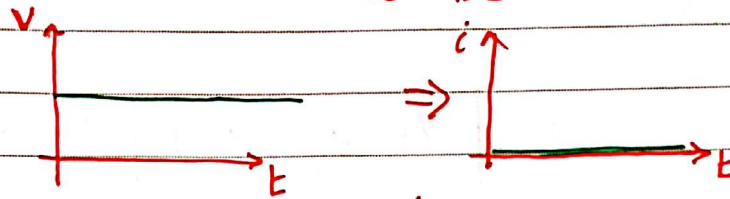

* Energy Stored in a Capacitor:

$w_c(t)$ or w_c

* $w_c(t) = \text{Power} \times \text{time}$.

$$P_c(t) = V \cdot i = V C \frac{dv}{dt}$$

$$w_c(t) = \int_{-\infty}^{t_0} P_c(t) dt$$

$$w_c = \frac{1}{2} C V^2$$

$$w_c(t) = \int_{-\infty}^{t_0} V C \frac{dv}{dt} dt$$


$$w_c(t) = \frac{1}{2} C V^2 \Big|_{-\infty}^{t_0}$$

$$= \frac{1}{2} C (V^2(t_0) - \overset{\text{zero}}{V^2(-\infty)})$$

$$w_c(t) = \frac{1}{2} C V^2(t_0)$$

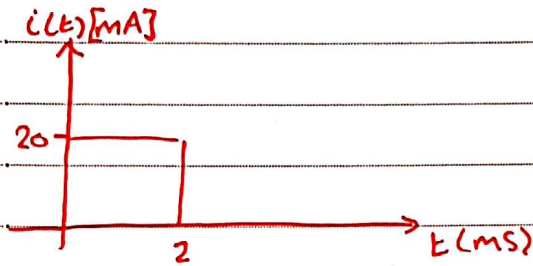(55)

*Ex: Find $V_c(t)$ & $w_c(t)$ if $C = 5\mu F$ & $i(t)$ is shown



$$V_c(t) = \frac{1}{C} \int_{-\infty}^{t} i(t) dt$$

~~scribbled out text~~

* $V_c(t)$

for $t \leq 0$

~~scribbled out text~~

$$V_c(t) = \frac{1}{C} \int_{-\infty}^0 i(t) dt = \text{zero}$$

for $0 \leq t < 2$

$$V_c(t) = \frac{1}{C} \left(\int_{-\infty}^0 i(t) dt + \int_0^t i(t) dt \right)$$


$$= \frac{1}{5\mu} \int_0^t 20 \text{ m} dt \Rightarrow \boxed{V_c(t) = 8t \text{ V}} \quad V_c(t) = 4000t \text{ V}, 0 \leq t < 2 \text{ ms}$$

for $2 \leq t$

$$V_c(t) = \frac{1}{C} \left(\int_{-\infty}^0 + \int_0^2 + \int_2^t i(t) dt \right)$$

$$V_c(t) = 8 \text{ Volt}, 2 \leq t$$
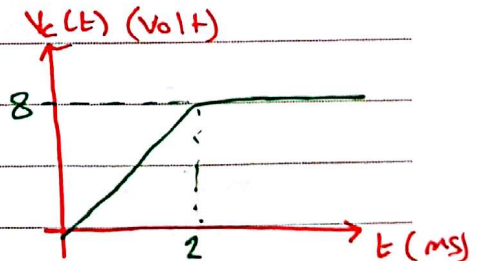
$$V_c(t) = \begin{cases} \text{zero}, & t \leq 0 \\ 4000t, & 0 < t < 2 \text{ ms} \\ 8, & 2 \text{ ms} \leq t \end{cases}$$




* $W_c(t)$

$$W_c(t) = \frac{1}{2} C V_c^2(t)$$

~~$\frac{1}{2} C t$~~

$$W_c(t) = \begin{cases} \text{zero}, & t \leq 0 \\ 40t^2, & 0 < t < 2\text{ms} \\ 160\mu, & 2\text{ms} \leq t \end{cases} \quad [\text{Joule}]$$

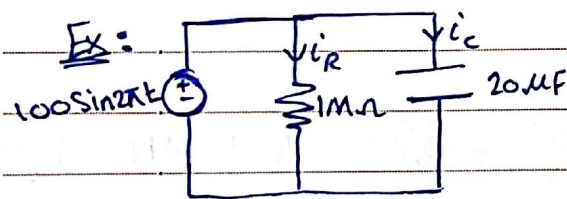$\frac{1}{2} C (200)^2$ ←
 $\frac{1}{2} C (4000t)^2$ ←
 $\frac{1}{2} C (8)^2$ ←



Find $W_c(t)_{\max}$, $W_R(t)$
in $0 < t \leq 0.5\text{s}$

$$W_c(t) = \frac{1}{2} C V_c^2(t)$$

$$= \frac{1}{2} \cdot 20 \cdot 10^{-6} \cdot 10^4 \sin^2 2\pi t$$

$$= 0.1 \sin^2 2\pi t \quad \text{Joule}$$


this is
max
value
for
sin

$$W_c(t)_{\max} = 0.1 \text{ J} = 100 \text{ mJ}$$

$$\sin 2\pi t = 1$$

$$2\pi t = \frac{\pi}{2}$$

$$t = \frac{1}{4} \text{ s}$$

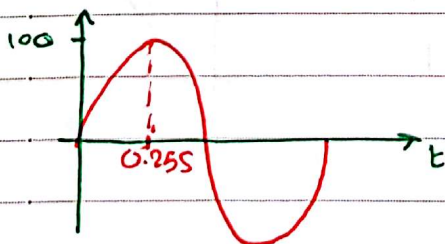

$$W_R(t) = P_R t \quad \left| \quad P_R(t) = \frac{V^2(t)}{R} = \frac{10^4 \sin^2(2\pi t)}{10^6} \right.$$

$$P_R(t) = 10^{-2} \sin^2 2\pi t \text{ Watt}$$

$$W_R(t) = \int P_R(t) dt$$

$$= \int_0^{0.5} P_R(t) dt = \int_0^{0.5} 10^{-2} \left(\frac{1}{2} (1 - \cos 4\pi t) \right) dt$$

$$= \frac{10^{-2}}{2} \left(t - \frac{\sin 4\pi t}{4\pi} \right) \Big|_0^{0.5}$$

$$= \frac{10^{-2}}{2} \left(\frac{1}{2} - 0 \right)$$

$$= \frac{10^{-2}}{4} = \frac{1}{400} \text{ J} = 2.5 \text{ mJ}$$

loss in charging capacitor

* The Inductor:

$$V \propto \frac{di}{dt}$$


$$V = L \frac{di}{dt}, \quad i = \int \frac{dv}{dt}$$

L : Inductance (H). ohm

if i is constant or zero

$$\Rightarrow V = 0 \text{ (S.C)}$$

Inductor is Short Circuit to DC

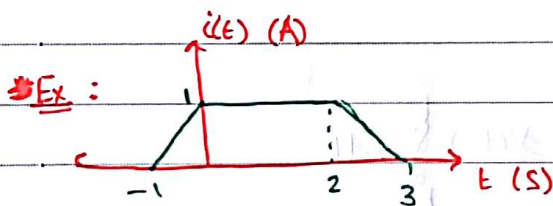

if $L = 3H$, find $V_L(t)$??

$$V_L(t) = L \frac{di}{dt}$$


$$t < -1 \Rightarrow i = 0, V = 0$$

$$-1 < t < 0 \Rightarrow V = 3 \frac{(1-0)}{(0-(-1))} = 3$$


$$0 < t < 2 \Rightarrow V = 0$$

$$2 < t < 3 \Rightarrow V = 3 \frac{(0-1)}{3-2}, V = -3$$


$$3 < t \Rightarrow V = 0$$

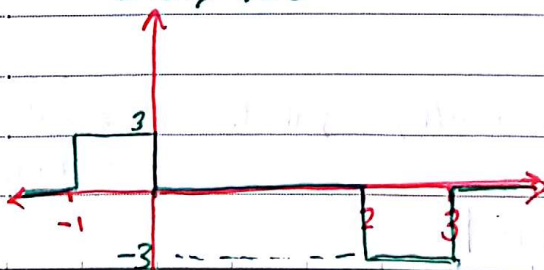

(5A)

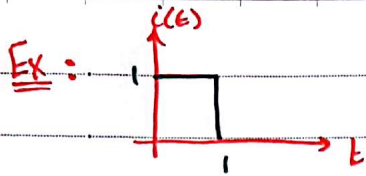

find $V_L(t) ??$

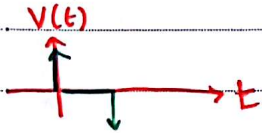

$$V = L \frac{di}{dt}$$

$$\int_{t_0}^t V dt = \int_{i(t_0)}^{i(t)} L di \quad \text{at } t = t_0 \Rightarrow i = i(t_0)$$

~~$$L(i(t) - i(t_0)) = \int_{t_0}^t V dt$$~~

$$i(t) = \frac{1}{L} \int_{t_0}^t V dt + i(t_0) \quad ; \text{ if } t_0 \rightarrow \infty \Rightarrow i(t_0) = 0$$

~~...~~

* Energy Stored

$$W_L(t) = P_L * t$$

$$P_L = V * i = i \left(L \frac{di}{dt} \right)$$

$$W_L(t) = \frac{1}{2} L i(t)^2$$

$$W_L(t) = \int_{t_0}^t P_L(t) dt$$

$$= \int_{t_0}^t i L \frac{di}{dt} dt + W(t_0) \quad ; \text{ if } t_0 \rightarrow \infty \Rightarrow W(t_0) = 0$$

$$\Rightarrow i(t_0) = 0$$

~~$$\frac{1}{2} L i^2$$~~

$$= \frac{1}{2} L i^2 \Big|_{t_0}^t$$

(60)

Ex: if $v_L(t) = 6 \cos 5t$ V, $L = 2$ H & $i(t = -\frac{\pi}{2}) = 1$ A
 find $i_L(t)$??

$$i_L(t) = \frac{1}{L} \int_{t_0}^t v_L(t) dt + i(t_0)$$

$$i_L(t) = \left(\frac{1}{2} \int_{-\frac{\pi}{2}}^t 6 \cos 5t dt \right) + 1$$

~~$\frac{1}{2} \int \cos 5t$~~


$$= \frac{1}{2} \left(\frac{6}{5} \sin 5t \Big|_{-\frac{\pi}{2}}^t \right) + 1$$

$$= \frac{6}{10} (\sin 5t + 1) + 1$$

$$i_L(t) = 0.6 \sin 5t + 1.6 \text{ A}$$

$$W_L(t) = \frac{1}{2} (2) (0.6 \sin 5t + 1.6)^2$$

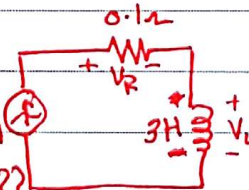Ex: Find $W_L(t)$ & $W_R(t)$ ~~max~~
 $W_R(t)$ during charging & $W_L(t)$ during discharging of the inductor??



$$W_L(t) = \frac{1}{2} L i^2(t)$$

$$= \frac{1}{2} (3) (12 \sin \frac{\pi}{6} t)^2$$

$$= 216 \sin^2 \frac{\pi}{6} t \rightarrow \text{for max } \frac{\pi}{6} t = \frac{\pi}{2} \Rightarrow t = 3 \text{ s}$$

* $W_L(t) = 216 \text{ J at } t = 3 \text{ s}$

$W_R(t)$ during charging & Discharging of the Inductor

~~$W_R(t) =$~~ $0 < t < 6 \rightarrow 3S \text{ Charge, } 3S \text{ Discharge.}$

$$W_R(t) = \int_0^6 P_R(t) dt$$

$$P_R(t) = V \cdot i = \frac{V^2}{R} = i^2 \cdot R$$

$$= 14.4 \sin^2 \frac{\pi}{6} t \text{ W}$$

$$W_R(t) = \int_0^6 14.4 \sin^2 \frac{\pi}{6} t dt$$

$$= 14.4 \int_0^6 \frac{1}{2} (1 - \cos \frac{\pi}{3} t) dt$$


$$= 7.2 (6 - \cos \frac{\pi}{3} t \Big|_0^6)$$

$$W_R(t) = 43.2 \text{ Joule}$$

\rightarrow losses

* Inductance & Capacitance Combinations :

→ Series Inductance:

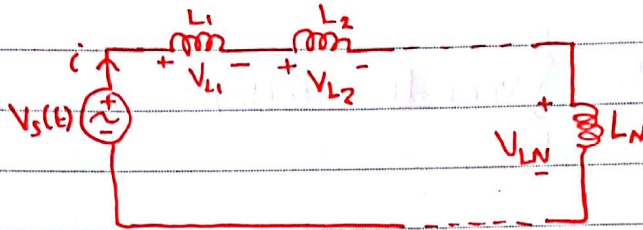


$$\sum_{k=1}^N \overset{\text{KVL}}{V_k} \Rightarrow -V_s + V_{L_1} + V_{L_2} + \dots + V_{L_N} = 0$$

$$0 = -V_s + L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_N \frac{di}{dt}$$

$$V_s = (L_1 + L_2 + \dots + L_N) \frac{di}{dt}$$

$$\boxed{L_{eq} = L_1 + L_2 + \dots + L_N} \text{ in Series}$$

→ Parallel Inductance:

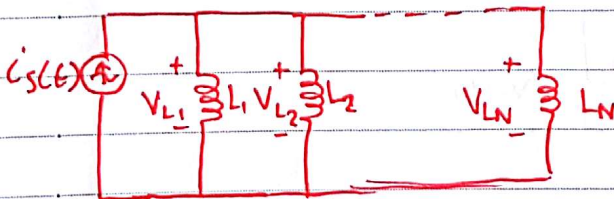

$$\underline{\text{KCL}} \Rightarrow i_s(t) = i_1 + i_2 + \dots + i_N$$

$$i_s(t) = \frac{1}{L_1} \int_{t_0}^t V(t) dt + i_1(t_0)$$

$$+ \frac{1}{L_2} \int_{t_0}^t V(t) dt + i_2(t_0)$$

$$\dots + \frac{1}{L_N} \int_{t_0}^t V(t) dt + i_N(t_0)$$

$$i_s(t) = \left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_N} \right) \int_{t_0}^t v(t) dt + i_s(t_0)$$

$$i_s(t) = \frac{1}{L_{eq}} \int_{t_0}^t v(t) dt + i_s(t_0)$$

~~Leq~~


$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$

$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}} \quad \text{In Parallel}$$

for 2 Inductances

$$L_{eq} = \frac{L_1 \cdot L_2}{L_1 + L_2}$$

→ Capacitance In Series

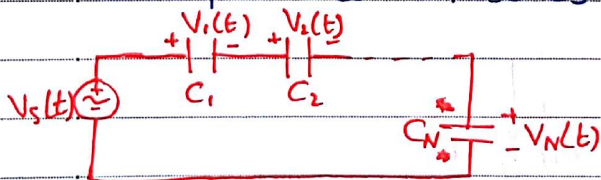

KVL

$$v_s(t) = v_1(t) + v_2(t) + \dots + v_N(t)$$

$$v_s(t) = \frac{1}{C_1} \int i(t) dt + \cancel{V(t_0)} V(t_0)$$

$$+ \frac{1}{C_2} \int i(t) dt + V(t_0)$$

$$\vdots$$

$$+ \frac{1}{C_N} \int i(t) dt + V(t_0)$$


(64)

$$V_s(t) = \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right) \int i(t) dt + i_s(t_0)$$

$$V_s(t) = \frac{1}{C_{eq}} \int i(t) dt + i_s(t_0)$$

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}} \quad \text{In Series}$$

→ Capacitance in parallel

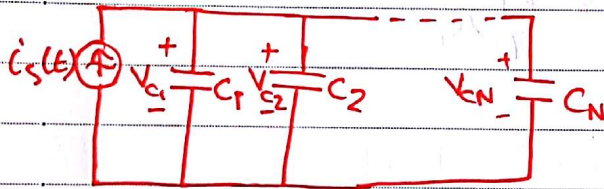

$$\text{KCL} \Rightarrow i_s(t) = i_1 + i_2 + \dots + i_N$$


$$i_s(t) = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt}$$

$$i_s(t) = (C_1 + C_2 + \dots + C_N) \frac{dv}{dt}$$

$$i_s(t) = C_{eq} \frac{dv}{dt}$$

$$C_{eq} = C_1 + C_2 + \dots + C_N \quad \text{In Parallel}$$


Ex: Find C_{eq} between a & b ??

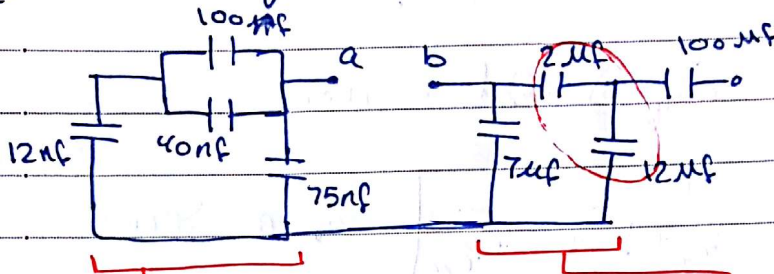

$$\begin{aligned}
 & * 2 \mu F + 12 \mu F \rightarrow \frac{2 \cdot 12}{14} = \frac{12}{7} \\
 & 7 \parallel \frac{12}{7} \rightarrow \frac{61}{7} \mu F \\
 & \rightarrow 100 \parallel 40 \rightarrow 140 nF \\
 & \rightarrow 140 + 12 \rightarrow \frac{140 \cdot 12}{152} = 11 nF \\
 & \rightarrow 11 \parallel 75 \rightarrow 86 nF
 \end{aligned}$$


$$\frac{61}{7} \mu + 86 n \rightarrow \frac{\frac{61}{7} * 86 \mu \cdot n}{\frac{61}{7} \mu + 86 n} \Rightarrow C_{eq} = 35.2 nF$$

~~$C_{eq} = 86 nF$~~

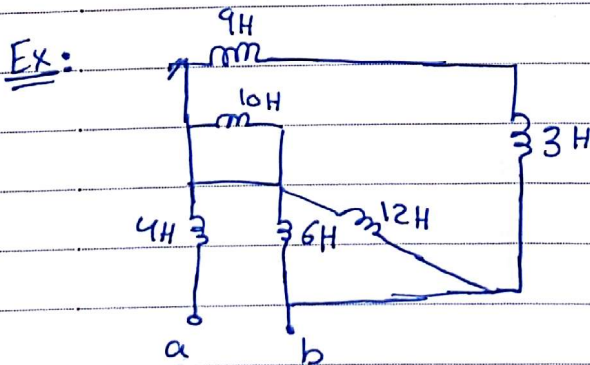



$$L_{eq} = 7H$$

*Simplify :

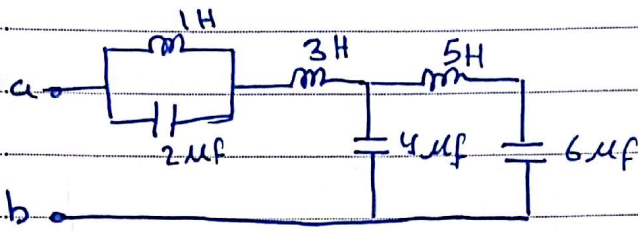


⇒ This can not be simplified.

* Ex: Simplify

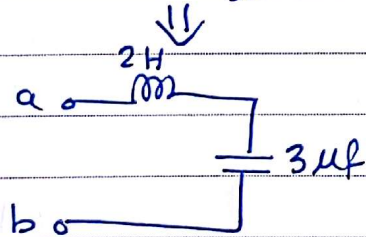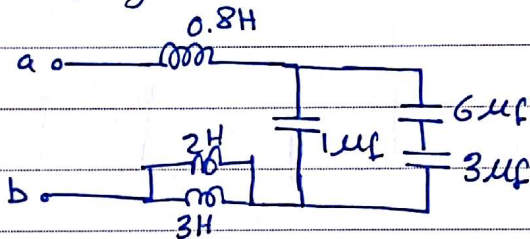

* Consequences of Linearity:

Ex: write the Nodal equations:

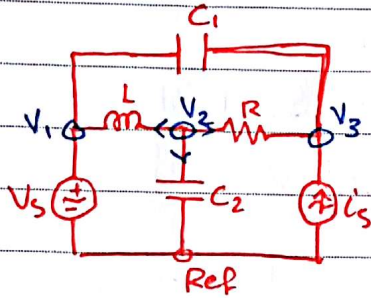

$i_L(t_0)$
 $V_{C1}(t_0)$
 $V_{C2}(t_0)$ } → Should be give

$V_1 = V_s$

KCL @ Node 2

$$\frac{V_2 - V_3}{R} + \left(\frac{1}{L} \int_{t_0}^t (V_2 - V_1) dt + i_L(t_0) \right) + C_2 \frac{dV_2}{dt} = 0$$

KCL @ Node 3

$$-i_s + \frac{V_3 - V_2}{R} + C_1 \frac{d(V_3 - V_1)}{dt}$$

Linear Integro differential equations

$$V_L = L \frac{di}{dt}$$

So linear
 $\rightarrow KV_L = KL \frac{di}{dt}$

$$i = \frac{1}{L} \int v(t) dt + i(t_0)$$

So linear
 $Ki = \frac{K}{L} \int v(t) dt + Ki(t_0)$

Simplify


~~$\frac{V_2}{R} + \frac{1}{L} \int_{t_0}^t v_2 dt + i_L(t_0)$~~

$$\frac{-1}{L} \int_{t_0}^t v_1 dt + \frac{V_2}{R} + \frac{1}{L} \int_{t_0}^t v_2 dt + C_2 \frac{dV_2}{dt} - \frac{V_3}{R} = -i_L(t_0) \quad \text{--- ①}$$

~~scribbles~~

$$-C_1 \frac{dV_1}{dt} + \frac{-V_2}{R} + \frac{V_3}{R} + C_1 \frac{dV_3}{dt} = i_s \quad \text{--- ②}$$

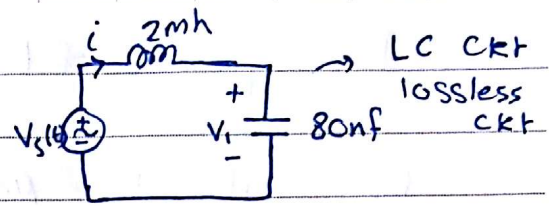*Ex: If $V_c(t) = 4 \cos 10^5 t$ V
 Find $V_s(t)$??



$$i = C \frac{dV_c(t)}{dt}$$

$$= 80 \times 10^{-9} (-4 \times 10^5 \sin 10^5 t)$$

$$i = -32 \sin 10^5 t \text{ mA}$$

$$V_L = L \frac{di}{dt}$$

$$= 2 \times 10^{-3} (-32 \times 10^5 \cos 10^5 t \times 10^{-3})$$

$$V_L(t) = -6.4 \cos 10^5 t \text{ V}$$

KVL:

$$-V_s(t) + V_L(t) + V_c(t) = 0$$

$$V_s(t) = V_L(t) + V_c(t)$$

$$V_s(t) = -2.4 \cos(10^5 t) \text{ V}$$

*Duality:

two circuits are dual if Nodal eqs for one circuit is similar to Mesh eqs. of the other circuit.

Dual


$$V \leftrightarrow I$$

$$R \leftrightarrow \frac{1}{R}$$

$$L \leftrightarrow C$$

$$\text{Series} \leftrightarrow \text{Parallel}$$

Ex: Write the mesh eq.s

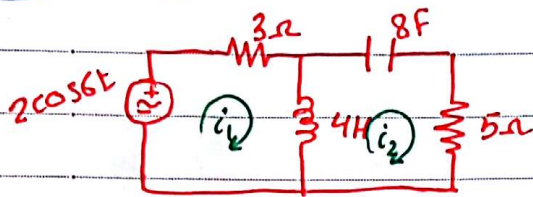

$$V_C(t_0) = 10V$$

$$i_L(t_0) = 0A$$

$$(1) \quad -2 \cos 6t + 3i_1 + 4 \frac{d(i_1 - i_2)}{dt} = 0$$

$$(2) \quad 4 \frac{d(i_2 - i_1)}{dt} + \frac{1}{8} \int_{t_0}^t i_2(t) dt + V_C(t_0) + 5i_2 = 0$$

$$3i_1 + 4 \frac{di_1}{dt} - 4 \frac{di_2}{dt} = 2 \cos 6t \quad \text{--- (1)}$$


$$-4 \frac{di_1}{dt} + 5i_2 + 4 \frac{di_2}{dt} + \frac{1}{8} \int_{t_0}^t i_2(t) dt = -10 \quad \text{--- (2)}$$

Find the Dual Circuit

$$3V_1 + 4 \frac{dV_1}{dt} - 4 \frac{dV_2}{dt} = 2 \cos 6t \quad \text{--- (1)}$$

$$-4 \frac{dV_1}{dt} + 5V_2 + 4 \frac{dV_2}{dt} + \frac{1}{8} \int_{t_0}^t V_2(t) dt = -10 \quad \text{--- (2)}$$

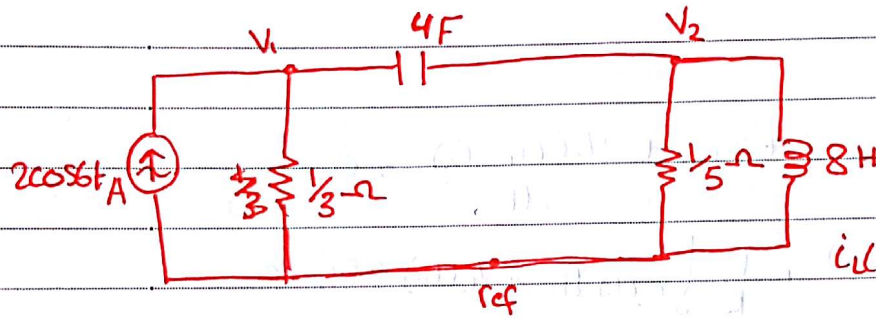Draw the Dual Circuit
two methods
method (1): from eqs.



$\Omega \leftrightarrow \Sigma$
 $L \leftrightarrow C$
 $V \leftrightarrow I$
Series \leftrightarrow Parallel


$$\frac{1}{L} \int v dt$$

$$C \frac{dv}{dt}$$


$$L \frac{di}{dt}$$

$$\frac{1}{C} \int i dt$$




method (2): From circuit

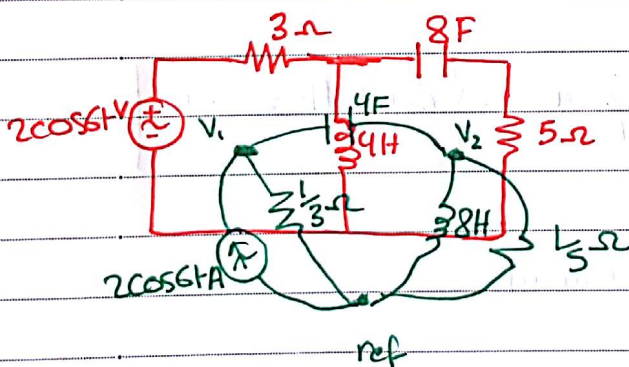

Redraw Redraw

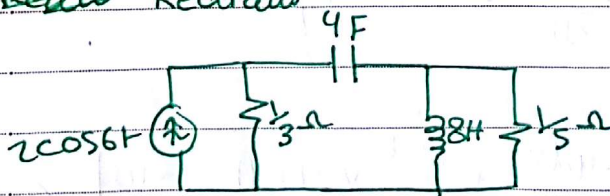

Ex: Draw the Dual Circuits

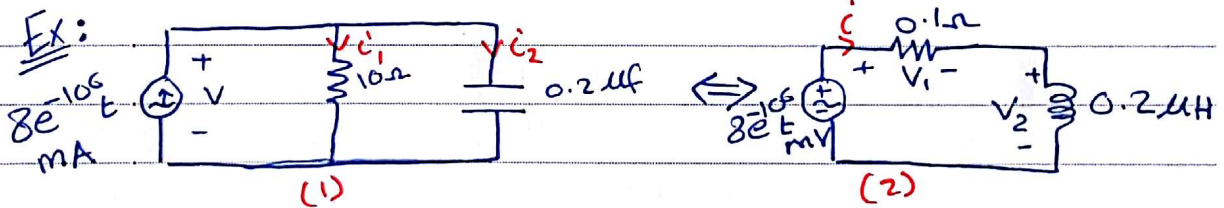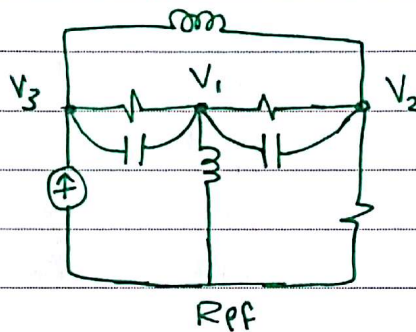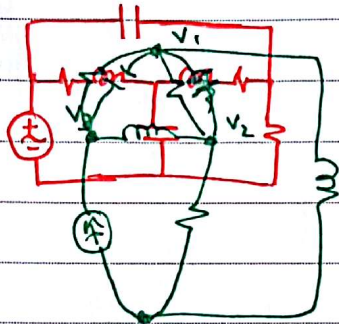

Find V_1, V_2 , and i if 2 circuits are dual ??
and $v = -80e^{-10t}$ mV

$$i_1 = v_1 \Rightarrow i_1 = v_1, \quad i_2 = v_2$$

(2) (1) (1) (2) (1) (2)

~~Handwritten scribbles~~ $i = -80e^{-10t}$ mA


$$\begin{aligned} i_1 &= -8e^{-10t} \text{ mA} \\ i_2 &= 16e^{-10t} \text{ mA} \\ v_1 &= -8e^{-10t} \text{ mV} \\ v_2 &= 16e^{-10t} \text{ mV} \end{aligned}$$

(72)

CH.7: Basic RL & RC circuits

-RL Circuits

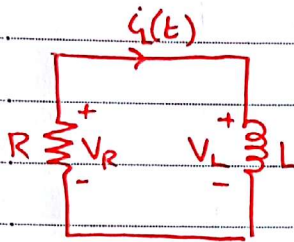- Series
 - Source free
 - Driven
- Parallel
 - Source free
 - Driven



$$i_L(t_0) = I_0$$

KVL:

$$-V_R + V_L = 0$$

$+iR + L \frac{di}{dt} = 0 \rightarrow$ linear homogeneous first order
Differential equation

$$\frac{di(t)}{dt} + \frac{R}{L} i(t) = 0$$

$$\int_{I_0}^{i(t)} \frac{di(t)}{i(t)} = \int_{t_0}^t -\frac{R}{L} dt$$


$$\ln\left(\frac{i(t)}{I_0}\right) = -\frac{R}{L}(t-t_0)$$

$$i(t) = I_0 e^{-\frac{R}{L}(t-t_0)}$$

If $t_0 = 0$

$$i(t) = I_0 e^{-\frac{R}{L}t}$$

Decaying exponential

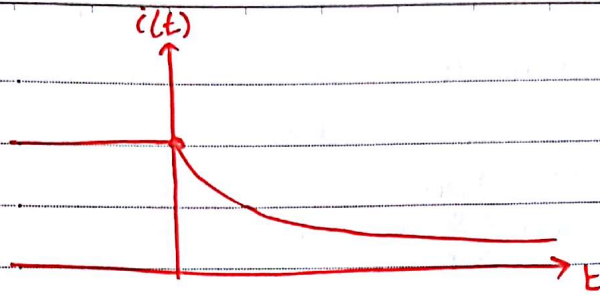

discharging of the inductor
(Dissipated by the series
resistance).

* Power Dissipated:

$$P_R(t) = i^2(t) R$$

$$= I_0^2 e^{-\frac{2R}{L}t} \cdot R \quad \text{Watt}$$

$$W_R(t) = \int_0^{\infty} P_R(t) dt \quad (t=0)$$

$$= \int_0^{\infty} I_0^2 R e^{-\frac{2R}{L}t} dt$$


$$= I_0^2 R \left(-\frac{L}{2R} e^{-\frac{2R}{L}t} \Big|_0^{\infty} \right)$$

~~$$= I_0^2 R \cdot L$$~~


$$= \frac{I_0^2 L}{2} (0 - (-1))$$

$$W_R(t) = \frac{1}{2} L I_0^2 = -W_L(t)$$

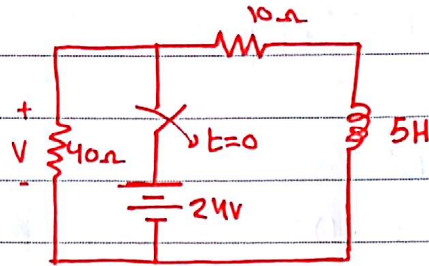*Ex: Find the current through the 5H at $t=200\text{ms}$



1) for $t < 0$, $t = 0^-$

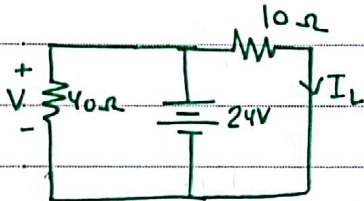


$$i_L(0^-) = \frac{24}{10} = 2.4\text{A}$$

$$i_L(0^+) = i_L(0^-) = i_L(0) = 2.4\text{A}$$

* Because current is not allowed to change suddenly across the inductor.

$$i_L(0) = 2.4\text{A}$$

2) for $t > 0$

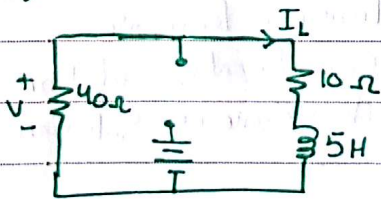

\Rightarrow



Series RL Circuit

$$i_L(t) = I_0 R e^{-\frac{R}{L}t}$$

$$I_0 = i_L(0) = 2.4\text{A}$$

$$i_L(t) = 2.4 e^{-10t} \text{ A} \rightarrow i_L(200\text{ms}) = 2.4 e^{-10 \times (200 \times 10^{-3})}$$

$$i_L(200\text{ms}) = 2.4 e^{-2} \text{ A}$$

$$V = -40I = -40(2.4)e^{-10t} \text{ V}$$

$$V = -96 e^{-10t} \text{ V}$$

$$V = -96 e^{-2} \text{ V}$$

(75)

$$P_R(t) = I_L^2 R$$

$$= (2.4)^2 e^{-20t} (50)$$

$$P_R(t) = 288 e^{-20t} \text{ watt}$$

$$W_L(t) = \frac{1}{2} L I_0^2$$

$$= \frac{1}{2} (5) (2.4)^2$$

$$W_L(t) = 14.4 \text{ J}$$


$$W_R(t) = \int_0^{\infty} P_R(t) dt$$

Switch \rightarrow

$$= \int_0^{\infty} 288 e^{-20t} dt = \frac{288}{-20} e^{-20t} \Big|_0^{\infty}$$

$$W_R(t) = -14.4 \text{ J}$$

$$W_L(t) = -W_R(t)$$

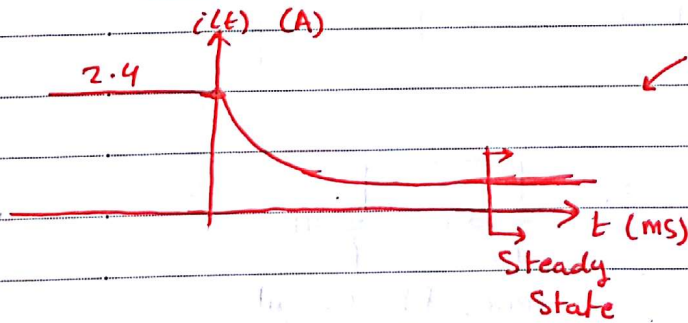

Natural Response.
 Transient Response.
 Complementary Solution
 homogeneous Solution

Define $\tau \equiv$ time Constant

$$i(t) = I_0 e^{-R/L t} = I_0 e^{-t/\tau}$$

$$\boxed{\tau = \frac{L}{R}} \text{ for RL Circuits in Seconds.}$$

at $t = \tau$ $\tau = \frac{5}{50} = 0.1 \text{ms}$

$$i(\tau) = I_0 e^{-\tau/\tau} = I_0 e^{-1}, \quad (e^{-1} = 0.368)$$

$$\boxed{i(\tau) = 0.368 I_0}$$

at $t = \tau \rightarrow$ Current drop from I_0 to $0.368 I_0$
Reduction by 36.8%.

$$e^{-1} \approx 36.8\%$$

$$e^{-2} \approx 14\%$$


$$e^{-3} \approx 5\%$$

$$e^{-4} \approx 1.8\%$$

$$e^{-5} \approx 0.67\%$$

Steady State begins after (5τ)
because the current drops to less
than 1% from its initial condition.
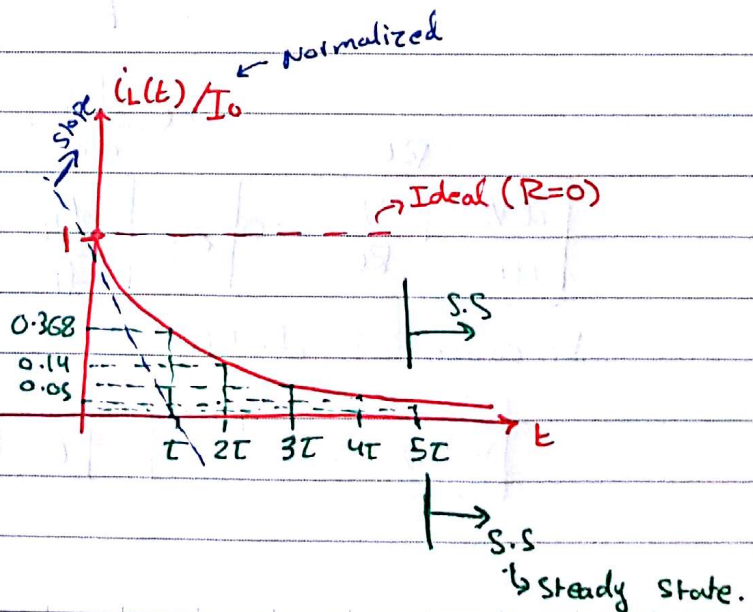
$$i_L(t) = I_0 e^{-t/\tau}$$
$$\frac{i_L(t)}{I_0} = e^{-t/\tau}$$



$$d\left(\frac{i_L(t)}{I_0}\right) = e^{-t/\tau} dt$$

$$= -\frac{1}{\tau} e^{-t/\tau}$$

at $t=0$

$$-\frac{1}{\tau} = -\frac{R}{L}$$

derivative \equiv Slope


$$\tau \uparrow, \frac{L}{R} \uparrow, L \uparrow, R \downarrow$$

$\tau \uparrow$ better

$\tau \equiv$ Discharging JI ~~for~~ ~~time~~

* Source free ~~series~~ RC Circuits.

Parallel ~~find~~ $V_C(t)$

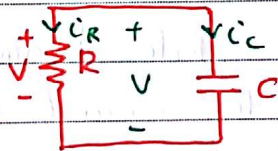

KCL @ upper Node

$$i_R + i_C = 0$$

$$\frac{V_C}{R} + C \frac{dV_C}{dt} = 0$$

$$C \frac{dV_C}{dt} = -\frac{V_C}{R}$$

$$\boxed{\frac{dV_C}{dt} + \frac{V_C}{RC} = 0} \iff \boxed{\frac{di_L}{dt} + \frac{R}{L} i_L(t) = 0}$$

because of duality

$$\boxed{V_C(t) = V_0 e^{-t/\tau}}$$

$$\boxed{\tau = RC}$$

KVL

$$-V_R + V_C = 0$$

$$iR + \frac{1}{C} \int_{t_0}^t i(t) dt + V(t_0) = 0$$

$$R \frac{di}{dt} + \frac{1}{C} i(t) = 0$$


$$\frac{di}{dt} + \frac{1}{RC} i(t) = 0 \Rightarrow \boxed{i(t) = I_0 e^{-t/\tau}}, \quad \boxed{\tau = RC}$$

(79)
E4


* Parallel RC circuits

$$V(t) = V_0 e^{-t/\tau}, \quad \tau = RC$$

Ex: Find V at $t = 200 \mu s$

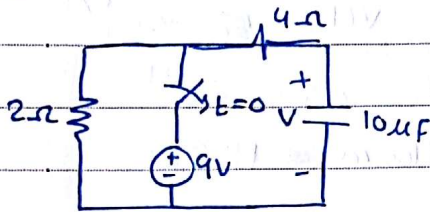


for $t < 0, t = 0^-$

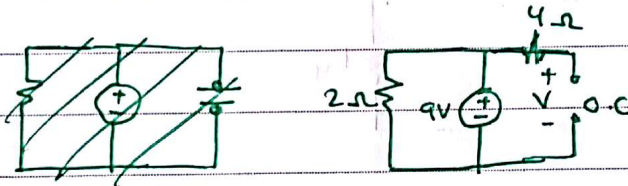

~~$V(0^-)$~~

$$V(0^-) = 9V = V(0^+)$$

for $t > 0, t = 0^+$

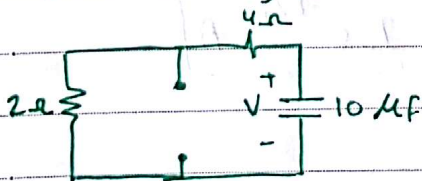

$$V(t) = V_0 e^{-t/\tau} \\ = 9e^{-t/60}$$

$$\tau = RC = 60 \mu s$$

$$V(200 \mu s) = 9e^{-200/60}$$

$$= 321.1 \text{ mV}$$


$$\frac{0.321}{9} * 100\% = 3.57\%$$

$$> 3\tau$$

$$3\tau = 180 \mu s$$

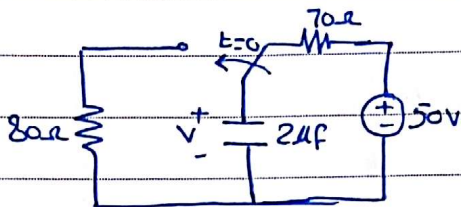(80)

Ex: Find $V(t)$, $V(0^-) = V(0^+) = V(0)$
 & $V(160\mu s)$??




$$V(0^-) = V(0^+) = V(0) = 50V$$

$$V(t) = 50e^{-t/(160 \times 10^{-6})}$$

$$V(160\mu s) = 50e^{-1}$$

$$V(160\mu s) = 18.39V$$

* General RL Circuits

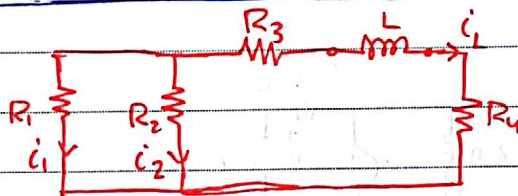

$$\tau = \frac{L_{eq}}{R_{eq}} = \frac{L_{eq}}{R_{th}}$$

$$R_{eq} = R_1 // R_2 + R_3 + R_4$$

$$\tau = \frac{L}{R_{eq}}, \quad i_L(t) = I_0 e^{-t/\tau} \text{ A}$$

$$i_L(0^-) = i_L(0^+)$$


$$i_L(t) = i_L(0^+) e^{-t/\tau}$$

$i_L(0^+) \neq i_L(0^-)$ across a Resistor


at $t=0$ $i_L(0^+) = -I_0 \left(\frac{R_2}{R_1 + R_2} \right)$

$$i_L(t) = -I_0 \left(\frac{R_2}{R_1 + R_2} \right) e^{-t/\tau}$$

*Ex: Find i_1 & i_L

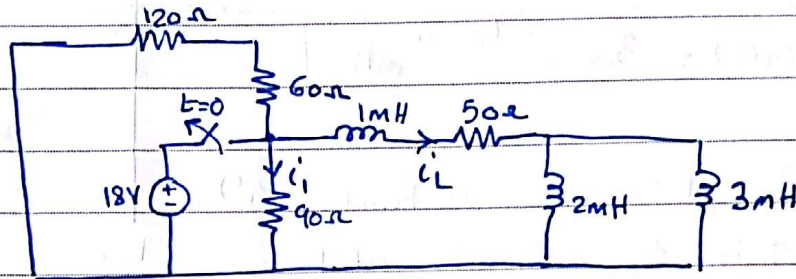


1) For $t < 0$ or $t = 0^-$

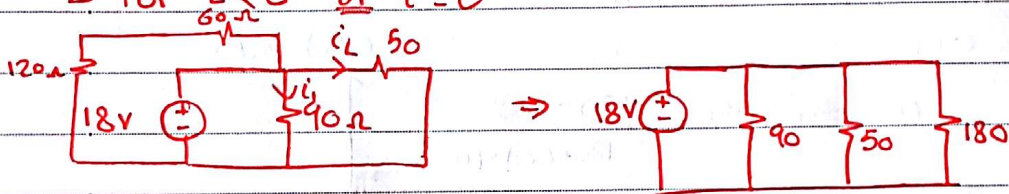

$$i_1(0^-) = \frac{18}{90} = 200 \text{ mA} \neq i_1(0^+)$$

~~$$i_L(0^-) = \frac{18}{50} = 360 \text{ mA} = i_L(0^+)$$~~

2) for $t > 0$ or $t = 0^+$

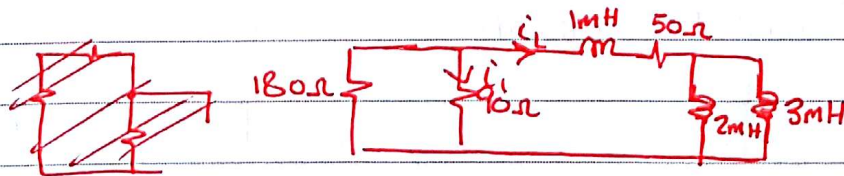

→ Source free circuit


$$R_{eq} = (180 \parallel 90) + 50 = 110 \Omega$$

$$L_{eq} = (2\text{m} \parallel 3\text{m}) + 1\text{m} = 2.2\text{mH}$$

$$\tau = \frac{L_{eq}}{R_{eq}} = 20 \mu\text{s}$$

$$i_L(t) = I_0 e^{-t/\tau}$$

$$i_L(t) = 360 e^{-t/20\mu} \text{ mA}$$

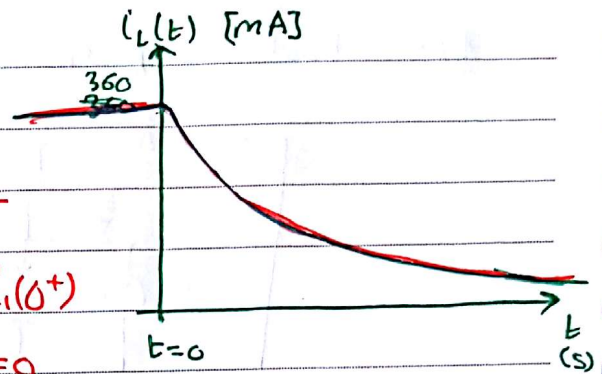

For $t=0^+$ to find $i_1(0^+)$

→ Solve the circuit at $t=0$


$$i_L(0^+) = 360 \text{ mA}$$

COR:

$$i_1(0^+) = -i_L(0^+) \times \frac{120 + 60}{120 + 60 + 90}$$

$$i_1(0^+) = -240 \text{ mA}$$
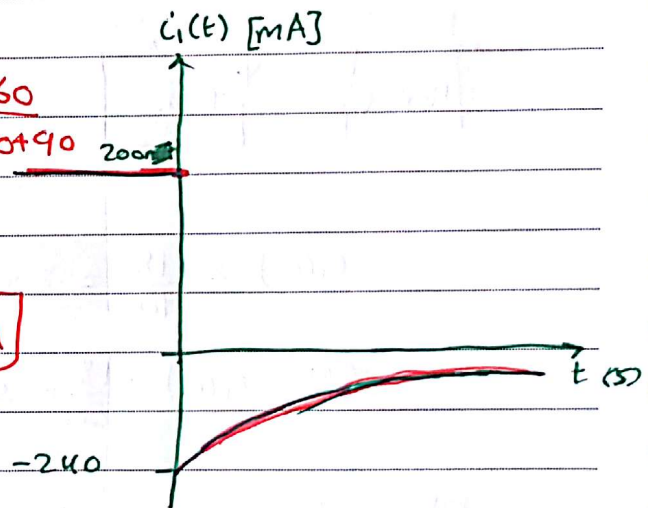
$$i_1(t) = -240 e^{-t/20\mu} \text{ mA}$$




* General RC circuits


~~Ex~~

* General RC Circuits

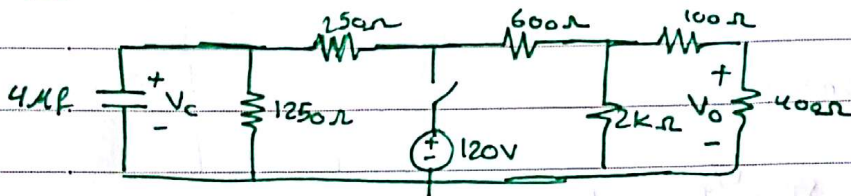Ex: find V_c & V_o at $t=0^-$, $t=0^+$, $t=1.3\text{ms}$



For $t < 0$, $t=0^-$

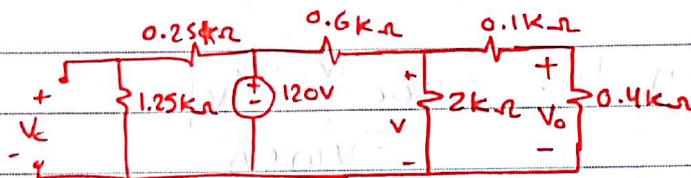


$$V_c = 120 \times \frac{1.25\text{k}}{1.5\text{k}}, \quad V_c(0^-) = 100\text{V} = V_c(0^+)$$

~~Vo~~

$$V = 120 \times \frac{2 \parallel 0.5}{2 \parallel 0.5 + 0.6} = 120 \times \frac{400}{1000}$$

$$V_o = V \times \frac{0.4}{0.5}, \quad V_o(0^-) = 38.4\text{V} \neq V_o(0^+)$$

for $t > 0$, $t=0^+$

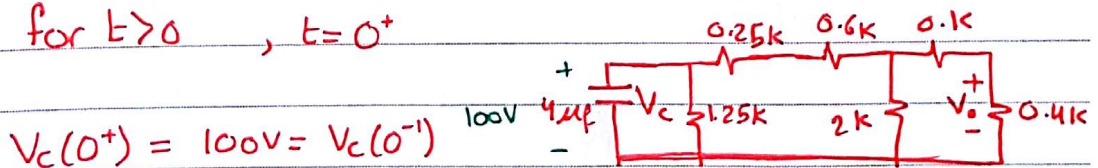

$$V_c(0^+) = 100\text{V} = V_c(0^-)$$

$V_o(0^+)$, Solve at $t=0$

$$V_o(0^+) + V_{0.1\text{k}\Omega} = 100 \times \frac{2 \parallel 0.5}{2 \parallel 0.5 + 0.85} = V_x$$

$$V_o(0^+) = V_x \times \frac{0.4}{0.5}$$

$$V_o(0^+) = 25.6\text{V}$$

(84)

$$\tau = R_{eq} \cdot C$$

$$R_{eq} = 1250 // 1250 = 625 \Omega$$

$$\tau = 2.5 \text{ ms}$$


~~$$V_c(t) = V_c(0^+) e^{-t/\tau} = 100 e^{-t/2.5 \text{ ms}}$$~~

$$V_c(t) = V_c(0^+) e^{-t/\tau} = 100 e^{-t/2.5 \text{ ms}} \text{ V}$$

$$V_o(t) = V_o(0^+) e^{-t/\tau} = 25.6 e^{-t/2.5 \text{ ms}} \text{ V}$$

$$V_c(1.3 \text{ ms}) = 59.45 \text{ V}$$
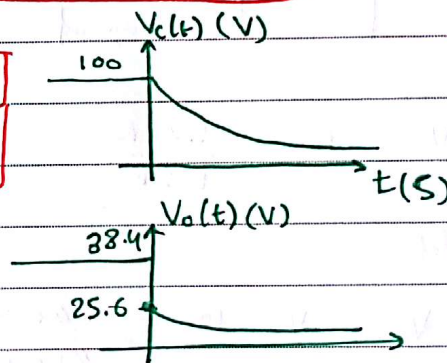
$$V_o(1.3 \text{ ms}) = 15.22 \text{ V}$$




Ex:



Find $V_c(t)$ if $V_c(0^-) = 2V$

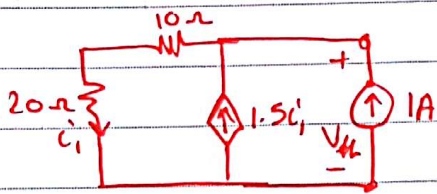* Using Thevenin's method (3) [Remove C & add $I_s = 1A$ Test]



~~$R_{th} = \dots$~~

$R_{th} = \frac{V_{test}}{1}$

Using Nod

$i_1 = V_{th}/30$

$1 + 1.5 \left(\frac{V_{th}}{30} \right) = \frac{V_{th}}{30} \Rightarrow V_{th} = -60V$


$R_{th} = -\frac{60}{1} = -60 \Omega$

$\tau = R_{th} \cdot C = (-60)(1\mu)$

$\tau = -60\mu s$


$V_c(t) = V_0 e^{-t/\tau}$
 $= 2 e^{-t/-60\mu}$

$V_c(t) = 2 e^{t/60\mu} V$

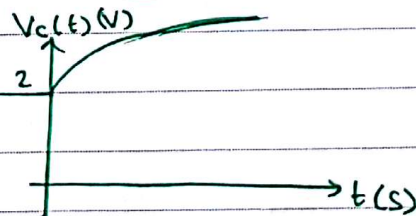

* This is an unstable circuit, circuit increase without limit.

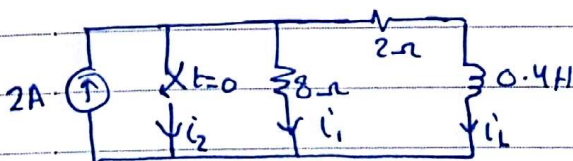Ex: Find i_L, i_1, i_2 for all $t, t=0^-, 0^+, \text{ any } t$



$i_L(0^-) = i_L(0^+) = 1.08 A$

$i_1(0^-) = 0.4A, i_1(0^+) = 0A$

$i_2(0^-) = 0, i_2(0^+) = 0.4A$

$i_L(t) = 1.6 e^{-t/0.2} A$

$i_1(t) = 0 A$


$i_2(t) = 2 - 1.6 e^{-t/0.2} A$

(86)

$\tau = 0.25$


* Unit Step functions:

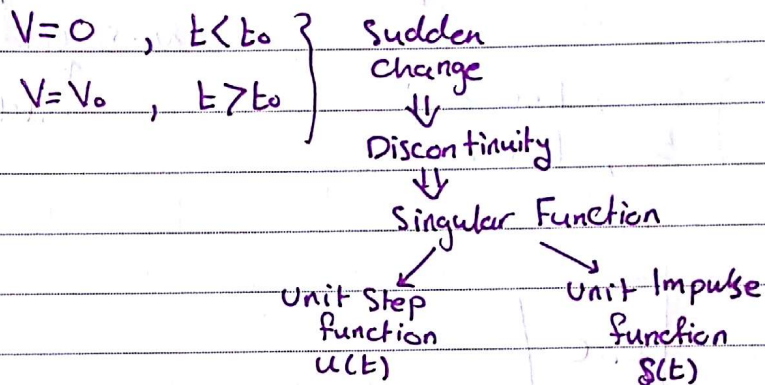If a Source is Suddenly Inserted in a Circuit at $t = t_0$




* $u(t)$
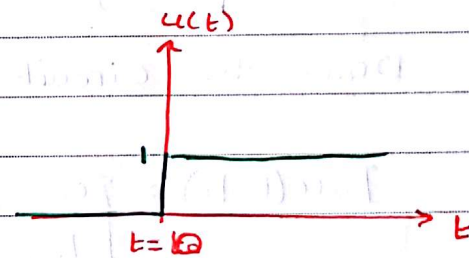
$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$




* $\delta(t)$
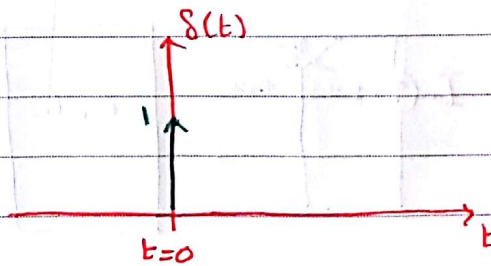
$$\delta(t) = \begin{cases} 0, & t < 0 \\ 1, & t = 0 \\ 0, & t > 0 \end{cases}$$




* $u(t-t_0)$
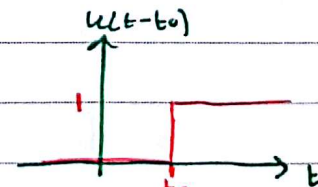
$$u(t-t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$




* $\delta(t-t_0)$
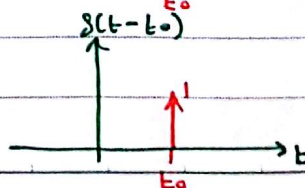
$$\delta(t-t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t = t_0 \\ 0, & t > t_0 \end{cases}$$



(87)


* Physical Sources & $u(t)$

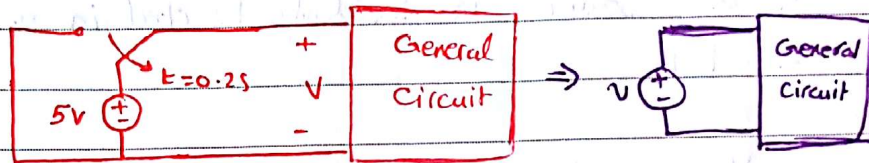

$$v = \begin{cases} 0, & t < 0.2 \\ 5, & t > 0.2 \end{cases}$$


$$v = 5 u(t - 0.2)$$

↑
Switch

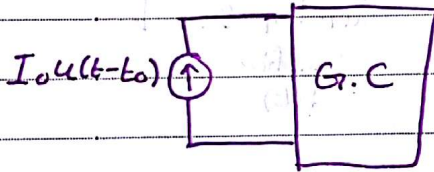


Draw the circuit with a Switch.
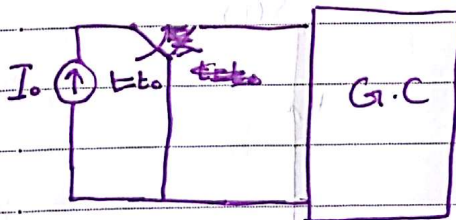
$$I_0 u(t - t_0) = \begin{cases} 0, & t < t_0 \\ I_0, & t > t_0 \end{cases}$$







*The Rectangular Pulse Function:

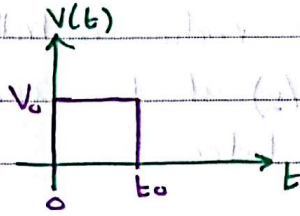

$$V(t) = \begin{cases} 0, & t < 0 \\ V_0, & 0 \leq t < t_0 \\ 0, & t > t_0 \end{cases}$$

~~$V(t) = u(t) - u(t - t_0)$~~

$V(t) = V_0 u(t) - V_0 u(t - t_0)$

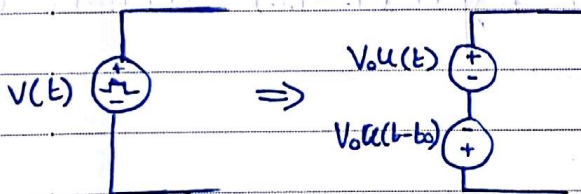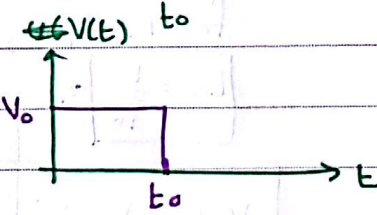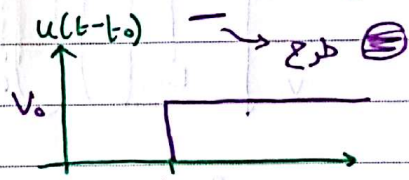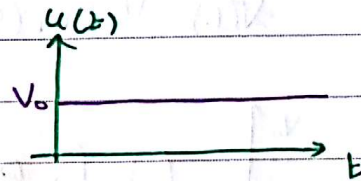


If a Sinusoidal Source ($V_m \sin \omega t$) is connected suddenly to a network at $t = t_0$, then

~~$V(t) = 0$~~


$$V(t) = \begin{cases} 0, & t < t_0 \\ V_m \sin \omega t, & t > t_0 \end{cases}$$

$V(t) = V_m \sin \omega t u(t - t_0)$

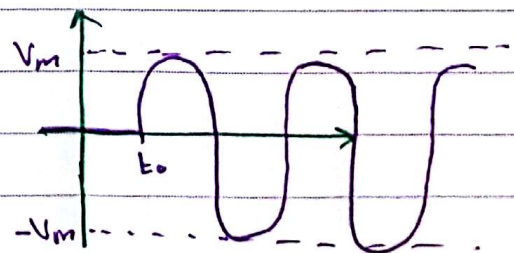

Ex: If a burst of energy need to be applied from the transmitter to a radio-controlled car operating at 47 MHz (295 Mrad/s) at t_0 and turn off the source ~~at~~ 70 ns later


~~$V(t) = V_0 \sin(295 \times 10^6 t)$~~

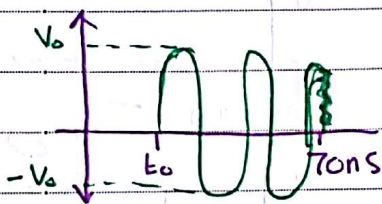

$f_0 = 47 \text{ MHz}$, $\omega = 2\pi f$ ~~$\Rightarrow 2\pi$~~ $\omega =$


$t_0 = \frac{1}{f_0}$ \Leftarrow

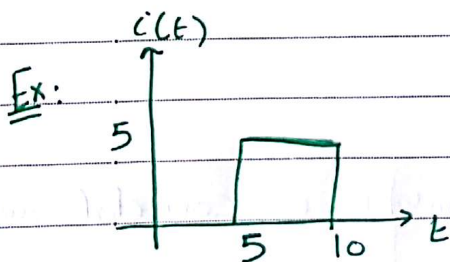$V(t) = V_0 \sin(295 \times 10^6 t) [u(t - t_0) - u(t - t_0 - 70 \times 10^{-9})]$



$c(t) = 5 u(t - 5) - 5 u(t - 10)$


* Driven RL Circuit
Series

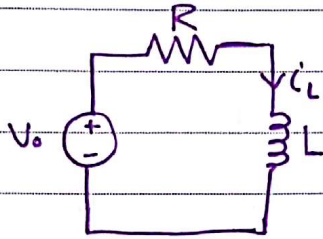

The source exists in the circuit


For $t > 5\tau$

Inductor will act as a short circuit

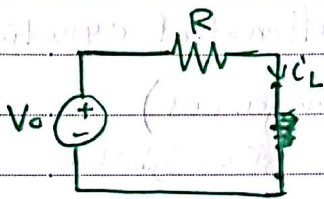


$$i_L = \frac{V_0}{R} \text{ for } t > 5\tau$$
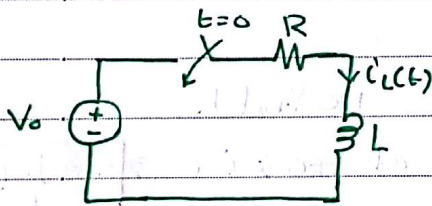
$$i_{\infty} = \frac{V_0}{R} \Rightarrow \infty \rightarrow t > 5\tau$$



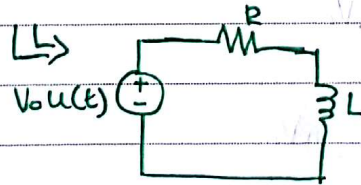
$$V = \begin{cases} 0, & t < 0 \\ V_0, & t \geq 0 \end{cases} = V_0 u(t)$$



$$i_L(0^-) = i_L(0^+) = i_L(0)$$

for $t < 0 \Rightarrow V = 0 \Rightarrow i_L(0^-) = 0 = i_L(0^+) = i_L(0)$

for $t > 0 \rightarrow i_L(0) = 0$

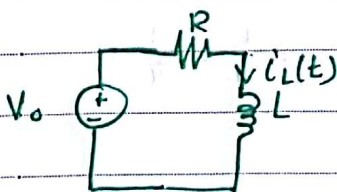

KVL:

$$-V_0 + IR + L \frac{di}{dt} = 0$$

$$L \frac{di}{dt} + iR = V_0$$

$$L \frac{di}{dt} = V_0 - iR \leadsto \text{Linear differential equation}$$

(Not Homogeneous)

* الطرف الثاني لا يساوي صفر *

$$\int \frac{L di}{V_0 - iR} = \int dt$$

$$\frac{L}{-R} \ln(V_0 - iR) = t + k$$

we find k

$$\text{at } t=0 \Rightarrow i=0 \Rightarrow k = -\frac{L}{R} \ln V_0$$

$$\frac{L}{-R} \ln(V_0 - iR) = t - \frac{L}{R} \ln V_0$$

~~$$\ln(V_0 - iR) = t + \frac{R}{L} t + \ln V_0$$~~

~~$$\ln(V_0 - iR) = t + \frac{R}{L} t + \ln V_0$$~~

$$-\frac{L}{R} (\ln(V_0 - iR) - \ln V_0) = t$$

$$\ln \left(\frac{V_0 - iR}{V_0} \right) = -\frac{R}{L} t, \quad \frac{R}{L} = \frac{1}{\tau}$$


$$\frac{V_0 - iR}{V_0} = e^{-t/\tau}$$

$$V_0 - iR = V_0 e^{-t/\tau}$$

$$i(t) = \frac{V_0}{R} - \frac{V_0}{R} e^{-t/\tau}, \quad \tau = \frac{L}{R}$$


Solution for Driven Series RL circuit

$$\Rightarrow i(0) = 0$$

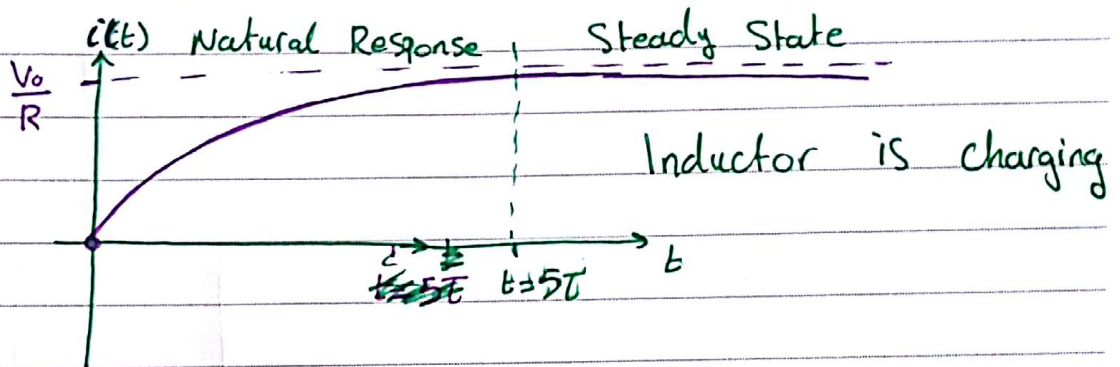

Steady State \equiv Forcing function \equiv Particular Solution

* Driven RL Circuits Series

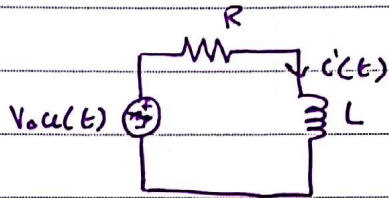

$$v_0 u(t) = \begin{cases} 0, & t < 0 \\ v_0, & t > 0 \end{cases}$$

$$i(0^-) = I_0 = i(0^+) = i(0)$$

$$\text{KVL}_{t > 0} \quad -v_0 + Ri + L \frac{di}{dt} = 0$$

$$L \frac{di}{dt} = v_0 - Ri$$

$$\int \frac{L di}{v_0 - Ri} = \int dt$$

$$\boxed{-\frac{L}{R} \ln(v_0 - Ri) = t + k}$$

To find k $i(0) = I_0 \Rightarrow t=0 \Rightarrow i = I_0$

$$\boxed{k = -\frac{L}{R} \ln(v_0 - RI_0)}$$

$$-\frac{L}{R} \ln(v_0 - Ri) = t - \frac{L}{R} \ln(v_0 - RI_0)$$

$$-\frac{L}{R} (\ln(v_0 - Ri) - \ln(v_0 - RI_0)) = t$$

$$\ln \left(\frac{v_0 - Ri}{v_0 - RI_0} \right) = -\frac{tR}{L}$$


$$v_0 - Ri = (v_0 - RI_0) e^{-\frac{tR}{L}}$$

$$R i(t) = \frac{V_0}{R} - (V_0 - RI_0) e^{-t/\tau}, \quad \tau = \frac{L}{R}$$

$$i(t) = \frac{V_0}{R} - \left(\frac{V_0}{R} - I_0 \right) e^{-t/\tau}$$

at $t = \infty \Rightarrow (t > 5\tau)$


$L \rightarrow$ S.C

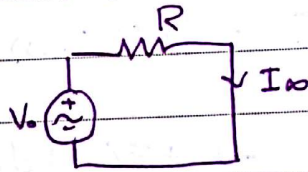


$$I_\infty = \frac{V_0}{R}$$

$$i(t) = I_\infty - (I_\infty - I_0) e^{-t/\tau}$$
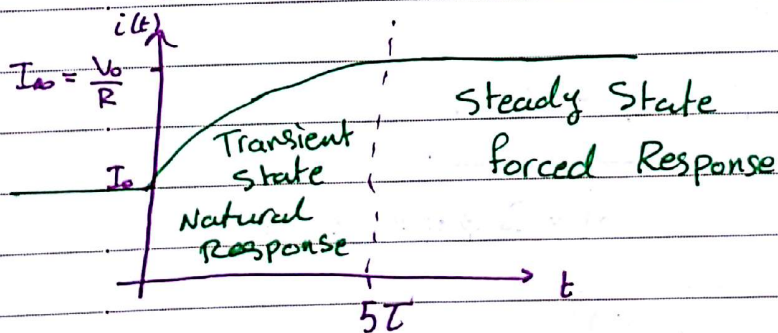
$$i(t) = I_\infty + (I_0 - I_\infty) e^{-t/\tau}$$




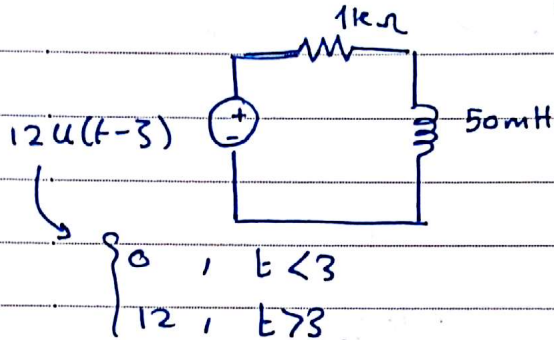Ex: Find $i(t)$ for $t=0^-$, 3^- , 3^+ and $100\mu s$ after the source changes value.




~~for $t < 3$~~

for $t < 3$

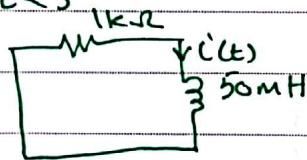

$$i(3^-) = 0 = i(3^+) = i(3)$$

for $t > 3$

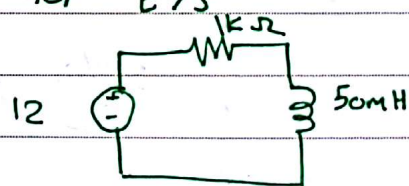

$$I_{\infty} = 12mA$$

$$T = \frac{L}{R} = \frac{50 \times 10^{-3}}{1 \times 10^3} = 50\mu s$$

$$i(t) = I_{\infty} + (I_0 - I_{\infty}) e^{-t/T}$$

$$i(t) = 12 + (0 - 12) e^{-t/50\mu s} \text{ mA}$$

$$i(t) = 12(1 - e^{-t/50\mu s}) \text{ mA}, t > 3$$


~~$i(3.0001) = 12(1 - e^{-3.0001/50\mu s})$~~

$$i(3.0001) = 10.38 \text{ mA}$$


$$i(t) = \begin{cases} 0 & , t < 3 \\ 12(1 - e^{-t/50\mu s}) \text{ mA} & , t > 3 \\ 12 \text{ mA} & , t = \infty \end{cases}$$

$$i(t) = 12(1 - e^{-t/50\mu}) u(t-3) \text{ mA}$$


for all t

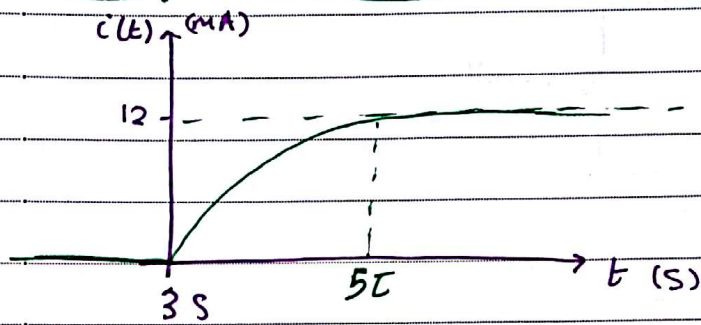

Ex: find $i(t)$ for all t

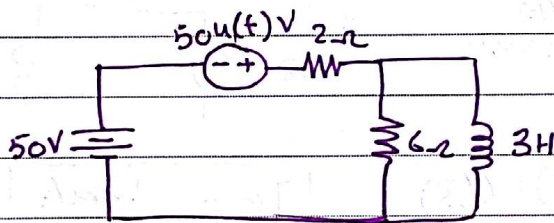


for $t < 0$

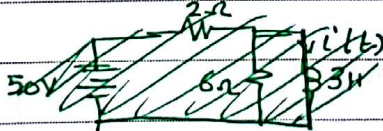

$L \rightarrow$ Short circuit

$$I_0 = i(0^-) = i(0^+) = \frac{50}{2} = 25 \text{ A}$$

for $t > 0$

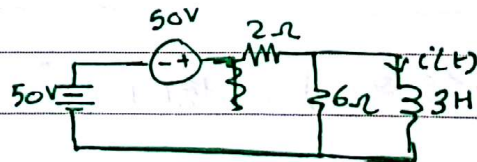

$I_0 \rightarrow$

$$I_0 = \frac{100}{2} = 50 \text{ A}$$




$I_0 = 25A$, $I_{\infty} = 50A$, now we find $i(t)$
for $t > 0$

$$i(t) = I_{\infty} + (I_0 - I_{\infty})e^{-t/\tau}$$

find $\tau = \frac{L}{R_{th}} \rightarrow$ seen from inductor
 $= \frac{3}{6/2} = 2 \text{ Sec}$

$$\tau = 2 \text{ Sec}$$

Thevenin's eq.

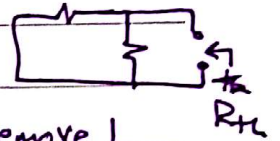

- ① Remove L
- ② kill Sources

$$i(t) = 50 + (25 - 50)e^{-t/2} \text{ A}$$

$$i(t) = 50 - 25e^{-t/2} \text{ A}, t > 0$$


for all t

~~$i(t) = 25 + (25 - (50 - 25))e^{-t/2} u(t)$~~
 ~~$i(t) = 25 + (25 - (50 - 25))e^{-t/2} u(t)$~~


$$i(t) = 25 + (25 - (50 - 25))e^{-t/2} u(t)$$

~~Eq:~~


Ex: find $i(t)$ for all t

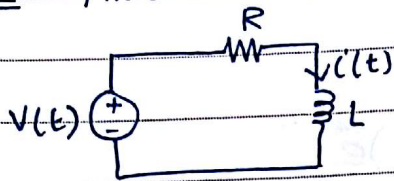


where

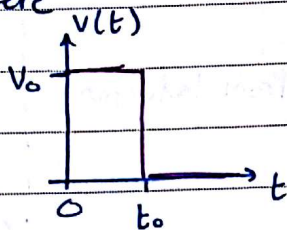

$$v(t) = V_0 u(t) - V_0 u(t - t_0)$$

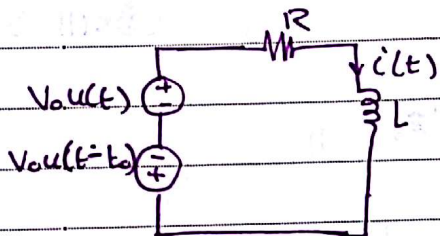


for $t < 0$

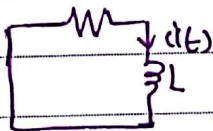

$$i(0^-) = i(0^+) = I_0 = 0 \text{ A}$$

for $0 < t < t_0$

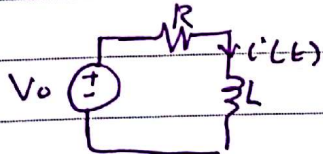


$$I_{\infty} = \frac{V_0}{R}, \quad \tau = \frac{L}{R}$$

$$i(t) = \frac{V_0}{R} - \left(\frac{V_0}{R} - 0\right) e^{-t/\tau}$$

$$i(t) = \frac{V_0}{R} (1 - e^{-t/\tau}) \text{ A}, \quad \text{for } 0 < t < t_0$$

for $t > t_0 \rightarrow$ we need $i(t_0^-) \neq i(t_0^+)$
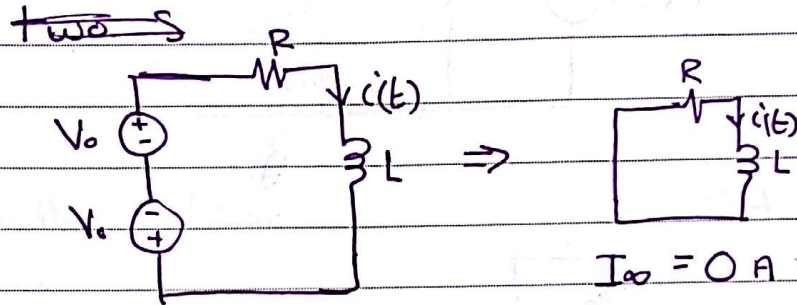
$$i(t_0) = \frac{V_0}{R} (1 - e^{-t_0/\tau}) = i(t_0^-) = i(t_0^+)$$



~~$$i(t) = 0 - (0 - I_0) e^{-t/\tau}$$~~

~~$$i(t) = i(t_0) e^{-t/\tau}, t > t_0$$~~


$$i(t) = 0 - (0 - i(t_0)) e^{-(t-t_0)/\tau}$$

$$i(t) = \left(\frac{V_0}{R} - \frac{V_0}{R} e^{-t_0/\tau} \right) e^{-(t-t_0)/\tau}, t > t_0$$

~~$$i(t) = \frac{V_0}{R} - \frac{V_0}{R} e^{-(t_0/\tau)} e^{-t_0}$$~~

$$i(t) = \left(\frac{V_0}{R} - \frac{V_0}{R} e^{-t_0/\tau} \right) e^{-(t-t_0)/\tau} \cdot u(t-t_0)$$

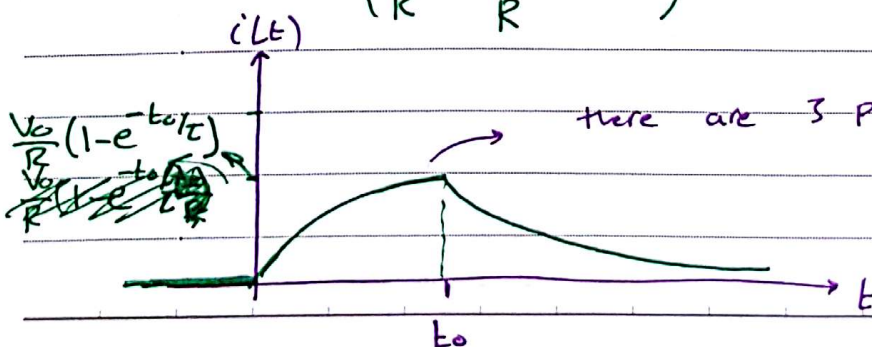
$$+ \left(\frac{V_0}{R} - \frac{V_0}{R} e^{-t/\tau} \right) u(t) - \left(\frac{V_0}{R} - \frac{V_0}{R} e^{-t/\tau} \right) u(t-t_0)$$



there are 3 possibilities either ① $t_0 > 5\tau$


② $t_0 < 5\tau$

③ $t_0 = 5\tau$

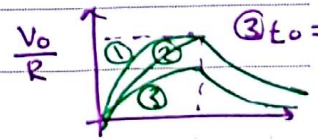


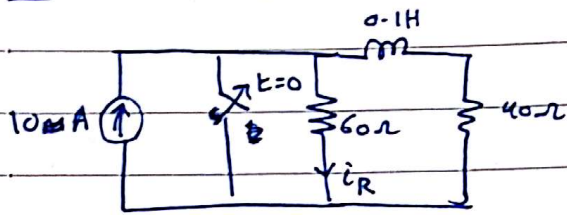(100)

Ex: find $i_R(t)$ at $t=0^-, 0^+, \infty, 1.5\text{ms}$




for $t < 0$

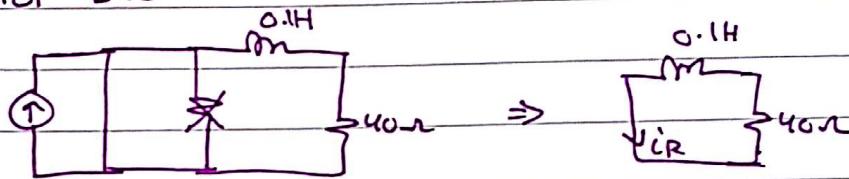

$$i_L(0^-) = i_L(0^+) = 0$$

$$i_R(0^-) = -i_L(0^-) = 0 \neq i_R(0^+)$$

for $t > 0$

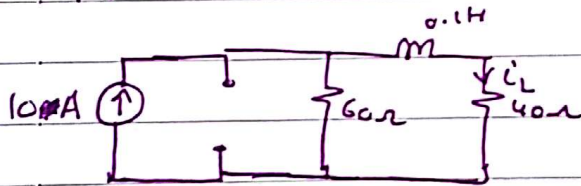

$$R_{th} = 60 + 40 = 100 \Omega$$

$$\tau = \frac{0.1}{100} = 1\text{ms}$$

$$i_{L\infty} = 10 \cdot \frac{60}{100} = 6\text{mA}$$

$$i_{L\infty} = \frac{10 \cdot 60}{100} = 6\text{A}$$

$$i_L(t) = 6 - (6e^{-t/1\text{ms}})\text{A}, \quad t > 0$$

$$i_R = 10 - i_L(t)$$


$$= 10 - (6 - 6e^{-t/1\text{ms}})\text{A}$$

$$i_R(t) = 4 + 6e^{-t/1\text{ms}}\text{A}, \quad t > 0$$

$$i_{R\infty} = 10 \cdot \frac{40}{100} = 4\text{A}$$

$$i_R(1.5\text{ms}) = 5.34\text{mA}$$

* Driven RC Circuits
 Parallel

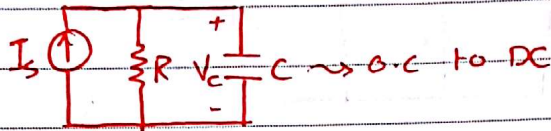


by Duality

$$V_c(t) = V_{\infty} - (V_{\infty} - V_0) e^{-t/\tau} \text{ V}$$


$$\tau = RC$$

$$V_{\infty} = I_s R$$

Ex: Find $V_c(t)$ & $i(t)$

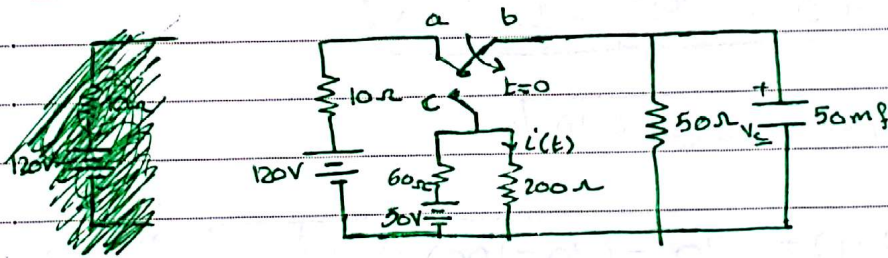

For $t < 0$

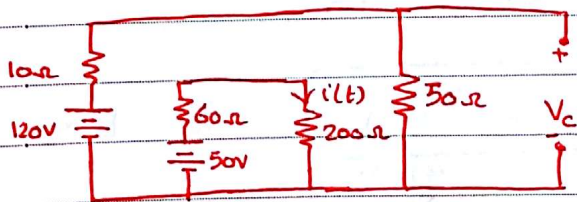


$$V_c(0^-) = 120 \times \frac{50}{60} = 100\text{V} = V_c(0^+) = V_c(0)$$

$$i_c(0^-) = \frac{50}{260} = 0.1923\text{A} \neq i_c(0^+)$$

for $t > 0$

$V_c(0) = 100V$

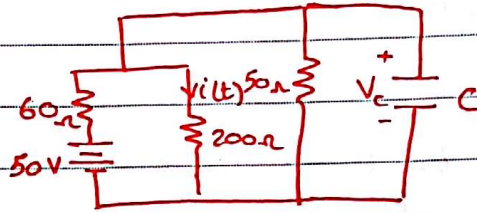

~~$V_{c(0)} = 50 \cdot \frac{200}{200+50}$~~

$V_{c(0)} = 50 \cdot \frac{200 \parallel 50}{200 \parallel 50 + 60}$

$= 50 \cdot \frac{40}{40+60}$

$V_{c(0)} = 20V$

$\frac{200 \cdot 50}{200+50}$

$200 \parallel 50 \rightarrow 40 \Omega$

$40 \parallel 60 \rightarrow \frac{40 \cdot 60}{40+60} = 24$

$i(0^+) = \frac{100}{200} = \frac{1}{2} A = 0.5A$


$i_{\infty} = \frac{20}{200} = 0.1A$

$V_c(t) = 20 - (20 - 100) e^{-t/1.2} V$ for $t > 0$


$\tau = RC = 24 \times 50 \times 10^{-3} = 1.2$

$R_{eq} = 200 \parallel 50 \parallel 60 = 24 \Omega$

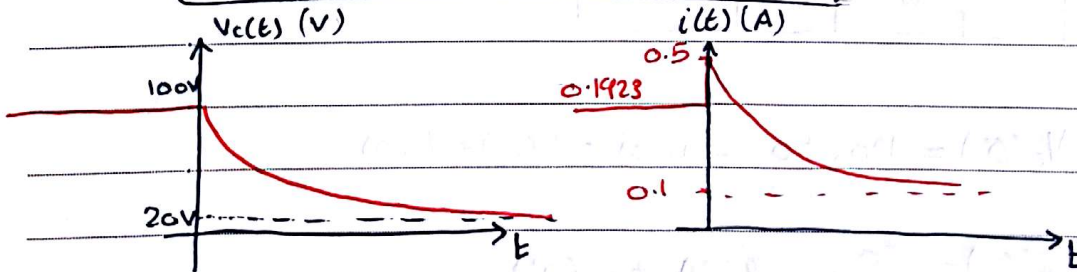
$i(t) = 0.1 - (0.1 - 0.5) e^{-t/1.2} A$ for $t > 0$



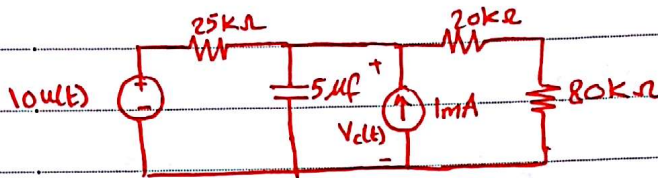*Ex: Find $V_c(t)$, for all t
and at $t = 0.08s$




For $t < 0$

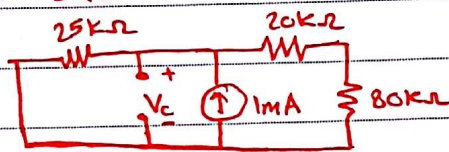

$$V_c(0^-) = \left(1 \times 10^{-3} + \frac{100 \times 10^3}{125 \times 10^3} \right) \times 25 \times 10^3$$


$$V_c(0^-) = 20V = V_c(0^+) = V_c(0)$$

For $t > 0$

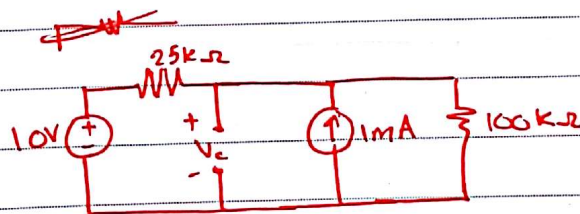


Norton's eq.
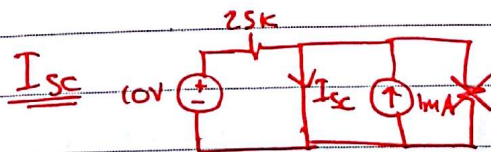
$$R_N = 25 \parallel 80 \Rightarrow = 20k\Omega$$



$$I_{sc} = 1m + \frac{10}{25k}$$

$$I_{sc} = 1.4mA$$

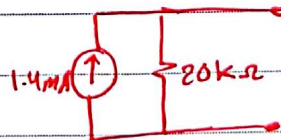

$$V_{th} = 28V = V_{oc}$$

$$V_c(t) = 28 - (28 - 20)e^{-t/0.1} \text{ V}$$

$$\tau = R_N \times C = 0.15$$

$$V_c(0.08) = 24.4 \text{ V}$$

لوقت السكون