

Name: محمد عبد الرحمن
محمد عبد الله

sec#: 1

ID# 0144364

Serial #:

Section 1
Dr. Mohammed Abuelha

Section 3
Dr. Eyad Feilat


Section 4
Mohammed Abuelhaj

13.5

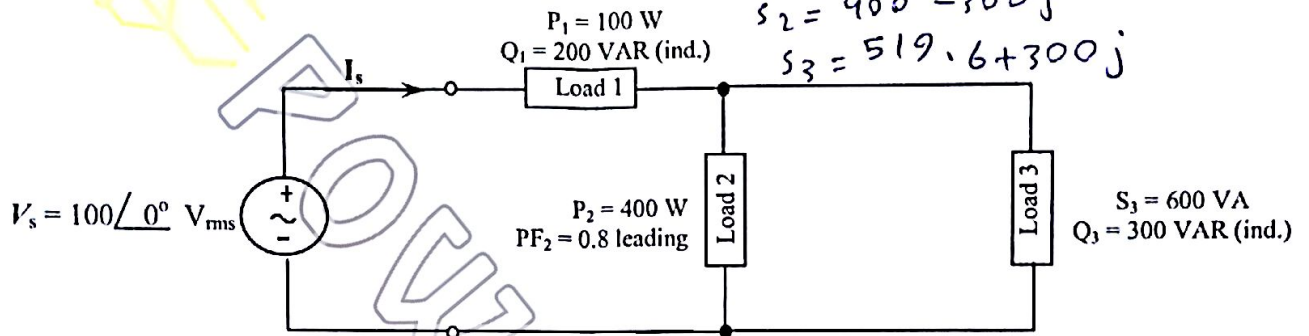Questions 1 (5 points)

The circuit shown below consists of three loads in a series-parallel connection, with each of the loads defined as indicated. Find:

- The overall real, reactive and complex power supplied by the source, P_s , Q_s , and S_s .
- The overall source power factor, PF_s .
- The source phasor current, I_s .



$S_1 = 100 + 200j$
 $S_2 = 400 - 300j$
 $S_3 = 519.6 + 300j$

P_s	Q_s	S_s	PF_s	I_s
1019.6	200 VAR	1019.6 + 200j	0.9813	$I_s = 10.4 \angle -11.1^\circ \text{ A}_{rms}$

$S_s = 1019.6 + 200j \text{ VA}$

$S = V_{rms} I_{rms}^*$
 $I_{rms} = 10.39$


$S = V_{rms} I_{rms}^*$

$I_{rms} = 10.4 \angle -11.1^\circ$

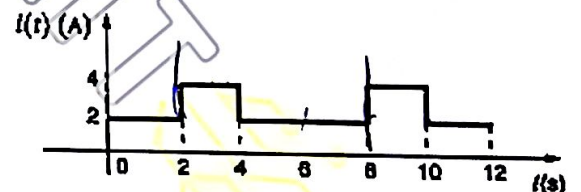Question 2 (3 points)

The current waveform shown below is flowing through a 4-Ω resistor. Compute

- the frequency of the signal, f .
- the effective values (rms) current I_{rms} ,
- average power delivered to the resistor, P_{avg} .



f	I_{rms}	P_{avg}
$\frac{1}{6} \text{ Hz}$	$2\sqrt{2}$	32

$i(t) = \begin{cases} 4, & 2 < t < 4 \\ 2, & 4 < t < 8 \end{cases}$
 $P_{avg} = I_{rms}^2 R$

$I_{rms}^2 = \frac{1}{T} \left(\int_2^4 16 dt + \int_4^8 4 dt \right)$
 $= \frac{1}{6} (16(2) + 4(4))$

$f = \frac{1}{T} = \frac{1}{6}$

$T = 6$

$f = \frac{1}{6}$

$T = 6$

Questions 3 (3 points)

A load with 0.8 lagging PF absorbs 60 W from a 100 V, 60 Hz power line. It is required to correct the power factor to 0.9 lagging. Find:

- The old and new line current,
- The value of the element (R, L, or C) to be added to achieve the required PF correction.

I_{old}	I_{new}	Value of the element
1.06 $\angle -36.86^\circ$	0.972 $\angle -25.8^\circ$	$C = 8.449 \mu F$

1.5

$PF_1 = 0.8 \quad \theta_1 = 36.86$

$S = 60 + 45j$

$V = 100V$

$f = 60Hz$

$PF_2 = 0.9 \quad \theta_2 = 25.84$

$S_2 = 60 + 29j$

$S = \frac{1}{2} V_{RMS} I^*_{RMS}$

$I^*_{RMS} = \frac{60 + 45j}{100/\sqrt{2}} = 1.06 \angle -36.86$

$I_{RMS} = 1.06 \angle -36.86$

$C = \frac{P (\tan \theta_1 - \tan \theta_2)}{\omega V_{RMS}^2} = \frac{60 (\tan(36.86) - \tan(25.84))}{2\pi \cdot 60 \cdot (100/\sqrt{2})^2}$

Questions 4 (3 points)

The 60-Hz line current of a 3-phase balanced, abc sequence Y-Y system is 2 A_{rms}. Each phase impedance Z consists of a 30-Ω resistance connected in series with a 106-mH inductance. Find:

- The magnitudes of phase and line voltages of the load, $|V_{ph}|$ and $|V_{LL}|$.
- The total real, reactive, and apparent power absorbed by 3-phase load, P_L , Q_L and S_L .
- The power factor of the load, PF.

1.5

$ V_{ph} $	$ V_{LL} $	P_L	Q_L	$ S_L $	PF
100	$\sqrt{3} \cdot 100$ 173.2	200W	266.667	333.33	0.6

$f = 60 \quad I_L = 2A_{rms}$

$Z_Y = 30 \Omega + 40j = 50 \angle 53.13$

$|V_{ph}| = I_L Z_Y \quad pf =$

$P_L = |I_L|^2 R_Y$

=

106mH
 $j\omega L = j 2\pi \times 60 \times 106 \times 10^{-3}$
 $= 39.96 j$
 $\approx 40 j$

Question 5 (3 points)

For the circuit shown below

a.	Find, draw and label the Thevenin equivalent circuit as seen from terminals a-b.	$V_{th} = 7.07 \angle 15^\circ$ $Z_{th} = 8 - 8j$
b.	If the load impedance $Z_L = 3 + j4 \Omega$, find the load current, I_L .	$I_L = 0.604 \angle 34.9^\circ$
c.	If Z_L is adjusted till maximum power is transferred, find Z_L which absorbs maximum power, and find the value of the maximum power, P_{max} .	$Z_L = 8 + 8j$ $P_{max} = \frac{ V_{th} ^2}{8R_{th}} = 0.781$

$$Z_{th} = -j8 \parallel (8 + j8)$$

$$Z_{th} = \frac{-8j(8 + j8)}{8}$$



$$Z_{th} = 8 - 8j$$

$$V_{th} = 5 \angle -30^\circ \left(\frac{8 + j8}{8} \right)$$

$$= 7.07 \angle 15^\circ$$

$$Z_L = 3 + j4$$

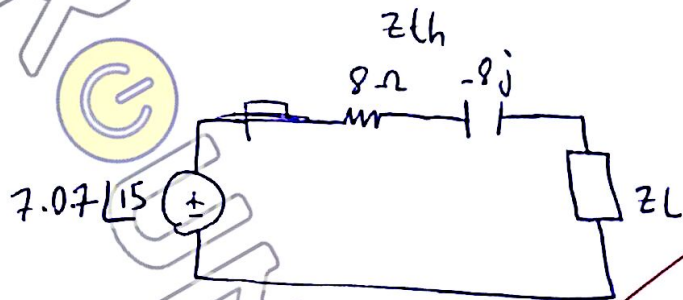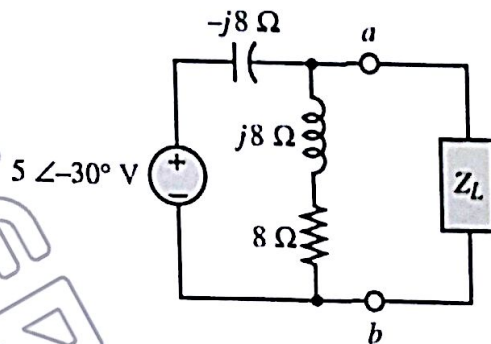
$$I_L = \frac{V_{th}}{Z_L + Z_{th}} = \frac{7.07 \angle 15^\circ}{3 + j4 + 8 - 8j} =$$



Questions 6 (3 points)

In the Figure shown below, $v(t) = v_{dc}(t) + v_1(t) + v_2(t) + v_3(t)$. Answer questions 6.1-6.3.

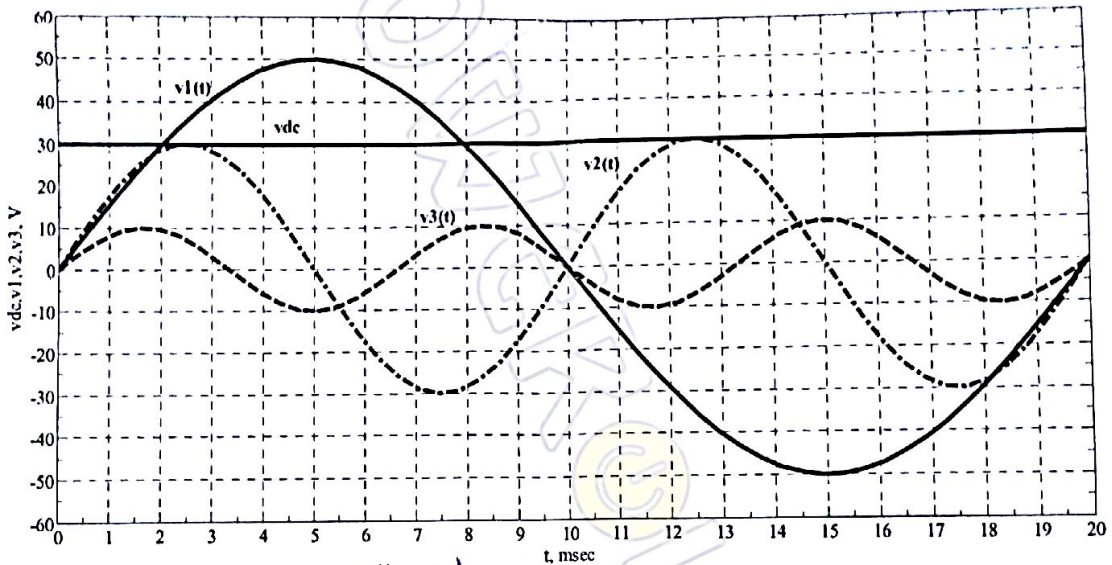- 6.1 the average voltage V_{dc} is 0 V.
- 6.2 the effective voltage V_{eff} is 71.83 V. $P_{avg} = \frac{(V_{eff})^2}{R}$
- 6.3 if $v(t)$ appears across a $10\text{-}\Omega$ resistor, the average power dissipated is 515.95 W.



$v_{dc}(t) = 30$
 $v_1(t) = 50 \sin(\omega t + \theta)$
 $v_2(t) = 30 \sin(\omega t + \theta)$
 $v_3(t) = 10 \sin(\omega t + \theta)$

$$V_{eff}^2 = \sqrt{\frac{2500}{2} + \frac{900}{2} + \frac{100}{2}}$$

$$V_{eff} = 41.83 + V_{dc} = 41.83 + 30 = 71.83$$

Name: _____ sec#: _____ ID# _____ Serial #: _____

Section 1
Dr. Mohammed Abuelhaj


Section 3
Dr. Eyad Fellat

Section 4
Mohammed Abuelhaj

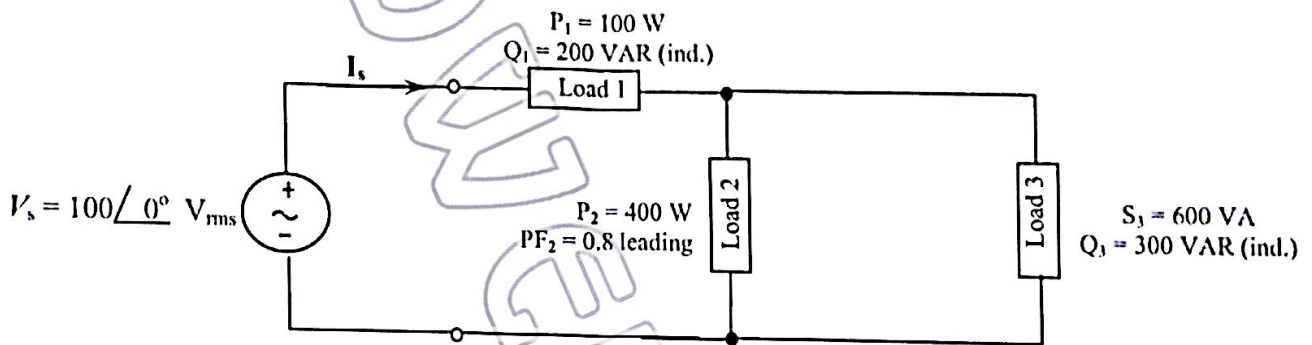Questions 1 (5 points)

The circuit shown below consists of three loads in a series-parallel connection, with each of the loads defined as indicated. Find:

- The overall real, reactive and complex power supplied by the source, P_s , Q_s , and S_s .
- The overall source power factor, PF_s .
- The source phasor current, I_s .




P_s	Q_s	S_s	PF_s	I_s
1019.6 W	200 VAR	1019.6+j200 $S_s = 1039\angle 11.1^\circ$ VA	0.981 lagging	$I_s = 10.39\angle -11.1^\circ$ A

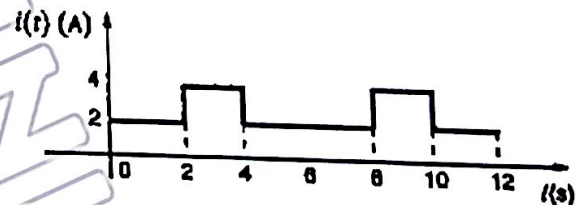Question 2 (3 points)

The current waveform shown below is flowing through

- a 4-Ω resistor. Compute
- the frequency of the signal, f .
- the effective values (rms) current I_{rms} ,
- average power delivered to the resistor, P_{avg} .



f	I_{rms}	P_{avg}
1/6 Hz	$\sqrt{8}$ A _{rms}	32 W

Questions 3 (3 points)

A load with 0.8 lagging PF absorbs 60 W from a 100 V (peak), 60 Hz power line. It is required to correct the power factor to 0.9 lagging. Find:

- The old and new line current,
- The value of the element (R , L , or C) to be added to achieve the required PF correction.

I_{old}	I_{new}	Value of the element
$I_{old} = 1.5\angle -36.9^\circ$ A	$I_{new} = 1.33\angle -25.8^\circ$ A	C= 8.512×10^{-06} F 8.512 μF