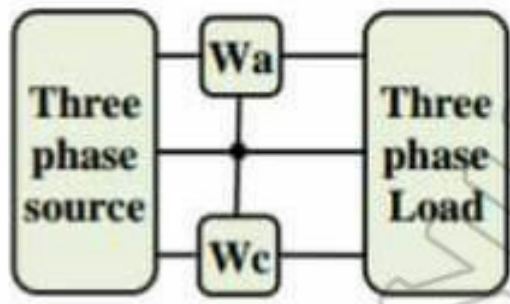


- 🔌 Switch off your mobile. **No** advanced calculators, Tablets or mobile phones are allowed.
- 👤 Hand over your exam sheets with your scratch paper.
- ⚙ Show **work** and **write** the **final** answer & **units** inside the **box**, to get credit on problems.
- ✍ Answer **all** problems directly on the exam sheet **only**.
- 📄 Feel free to use the blank space on the exam sheets for scratch work.
- 👉 Please keep 😊, 🙌 & 🧐. **Don't** 🙄, 🤔, 🤔, 🤔 & 😞. Take your 🕒 & enjoy yourself.

Q1-(16Pts) Solve each part separately.


(ABET outcome (a) Assessment)

- The readings of the shown wattmeters are:
- $W_a = 1500 \text{ W}$.
- $W_c = 2200 \text{ W}$. - Determine the:
 - Total active power.
 - Total reactive power.
 - Power Factor.
 - Type of the load, Resistive, Inductive or Capacitive.




$P_T =$
 $Q_T =$
 $P.F =$
 Type =

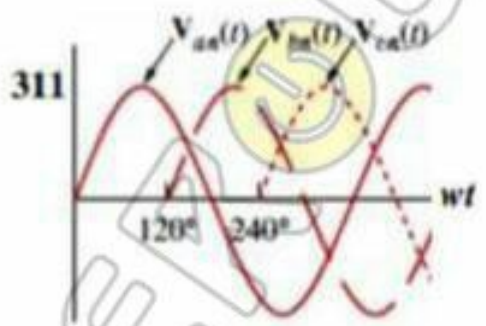- The shown signals for a three-phase system Y-Y connection.
- $i_a(t) = 7.071 \sin(314t - 60^\circ) \text{ A}$.
- a- Write time-varying $v_{an}(t)$.
- b- Write time-varying $v_{ab}(t)$.
- Then Determine the:
 - c- Total instantaneous power $p(t)$.
 - d- Total average power P .
 - e- Total pulsating (time varying) power $P_{puls}(t)$.




$v_{an}(t) =$
 $v_{ab}(t) =$
 $p(t) =$
 $P =$
 $P_{puls}(t) =$

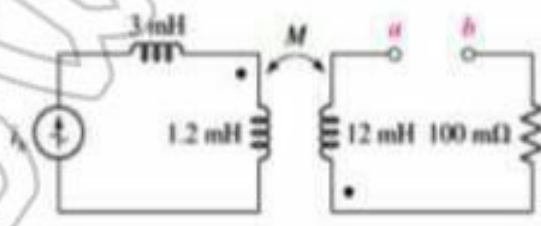- In the circuit, $k=0.75$, if $i_s(t) = 10 \cos(200t) \text{ A}$.
- Determine the:
 - a- Mutual Inductance M .
 - b- V_{ab} voltage $v_{ab}(t)$.
 - c- Max. stored energy W .



$M =$
 $v_{ab}(t) =$
 $W =$

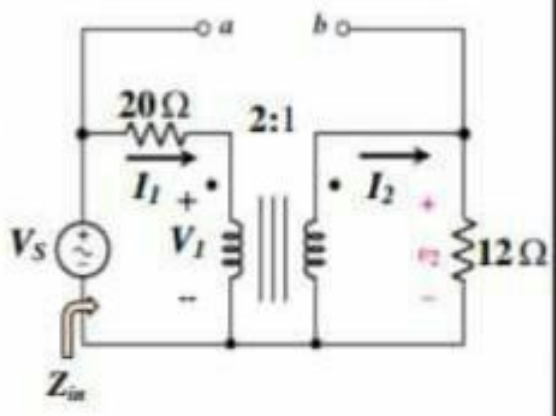- In the circuit, $V_s = 220 \text{ V}_{rms}$.
- Find the:
 - Input impedance seen by the source Z_{in} , I_1 , V_1 , I_2 , V_2 , V_{ab} , and the total dissipated power P_T .




$Z_{in} =$
 $I_1 =$
 $V_1 =$
 $I_2 =$
 $V_2 =$
 $V_{ab} =$
 $P_T =$

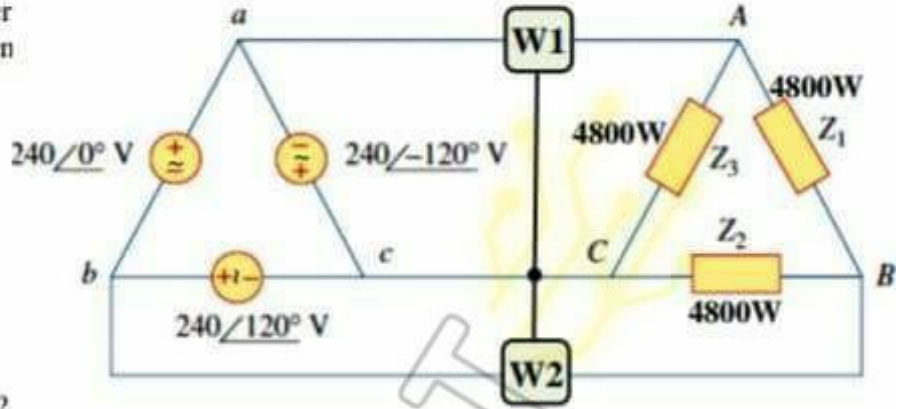Q2-(8pts) I- In the circuit shown, consider a balanced 3-phase system, given voltage in rms, $Z_1=Z_2=Z_3=R$.

Determine the:

- a- R .
- b- I_{AB} , I_{BC} , and I_{CA} .
- c- I_{aA} , I_{bB} , I_{cC} .
- d- Wattmeter reading of: $W1$, $W2$.
- e- The PF can be corrected, if yes what is the type of element.
- f- Is the reading of $(W1 + W2)$ equals to the total power? Why?



$R =$

$I_{AB} =$

$I_{BC} =$

$I_{CA} =$

$I_{aA} =$

$I_{bB} =$

$I_{cC} =$

$W1 =$

$W2 =$


Type:

f-

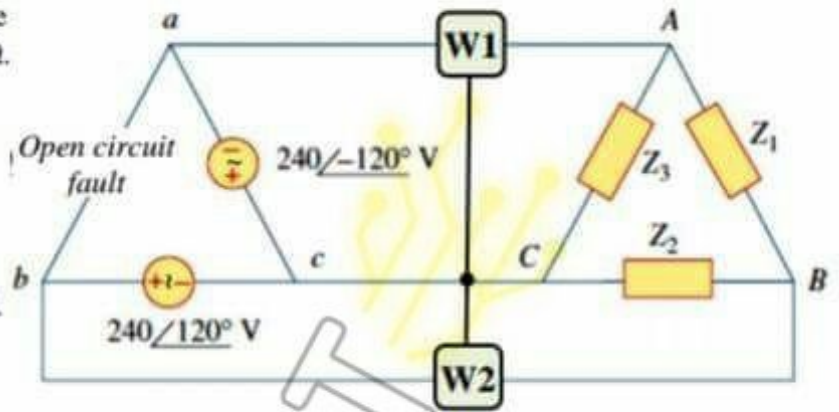Q2-(8Pts) II- In the circuit shown, the voltage in rms, assume $Z_1=Z_2=Z_3=R=12\Omega$. Consider an *open circuit fault* at source *ab* (V_{ab} opened).

Determine the:

- a- I_{AB} , I_{BC} , and I_{CA} .
- b- I_{aA} , I_{bB} , and I_{cC} .
- c- Wattmeter reading of: **W1**, **W2**.
- d- System is balanced or Unbalanced.
- e- What is the advantage of the DELTA connection source?



$$I_{AB} =$$

$$I_{BC} =$$

$$I_{CA} =$$

$$I_{aA} =$$

$$I_{bB} =$$

$$I_{cC} =$$

$$W1 =$$


$$W2 =$$

d-

e-

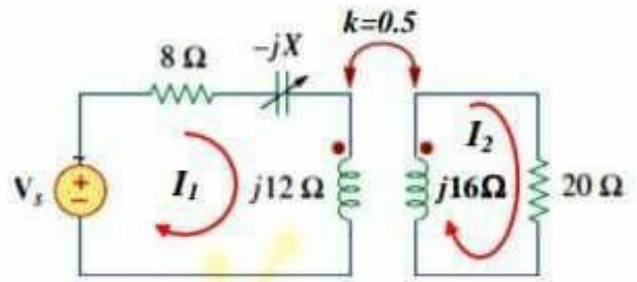Q3-(12Pts) In the shown circuit, $V_s = 100$ Vrms.

- a- Find the mutual impedance ($j\omega M$).
- b- Write the mesh current equations in **matrix** form.
- c- Draw and label the **T** equivalent circuit only for the coupled coils.
- d- Find the value of X that will give maximum power transfer to the 20Ω load.
- e- Find I_1 and I_2 .



a-
 $j\omega M =$

b-

c-


d-
 $X =$

e-
 $I_1 =$
 $I_2 =$

4-(6Pts) I- A transformer is used to match the different impedance systems with each others, A computer/electrical/mechatronics engineer want to couple a coaxial cable with BNC socket to UTP cable with RJ-45 socket as shown in the figure, the used transformer is an **ideal**, **determine** the:



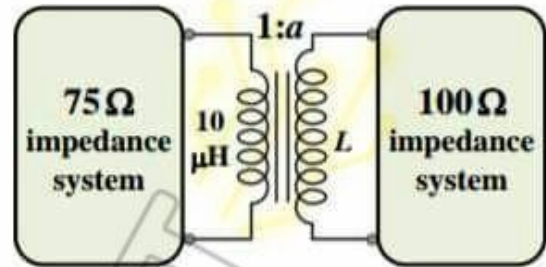- a- Required turns ratio (a) for maximum energy power transfer.
- b- Inductance L value in 100-ohm side.




a-
 $a =$

b-
 $L =$

4-(10Pts) II- In the shown circuit, the transformer is an **ideal**,
 $v_s(t) = 10 \cos(2t)$ V. **determine** the following:

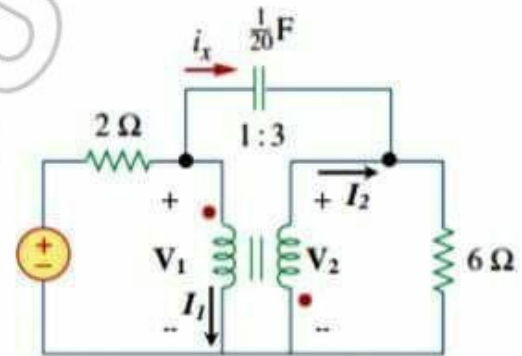- a- Primary voltage and current V_1, I_1 .
- b- Secondary voltage and current V_2, I_2 .
- c- Feedback current i_x .



a-
 $V_1 =$
 $I_1 =$

b-
 $V_2 =$
 $I_2 =$

c-
 $i_x =$