

SECOND EXAM

08/12/2014

NAME: _____

Please write in arabic, your name, ID#, and Seat# section



Power Unit

Part A


Problem1 [9 marks]: The circuit shown below is energized by a voltage source with $v(t) = 200\sqrt{2} \cos(100\pi t) V$.

$\omega = 100\pi$

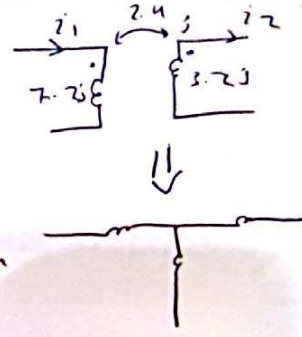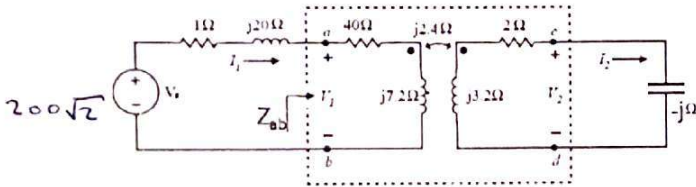
- a) Find the impedance seen from terminals a&b (Z_{ab}).
- b) Find I_1, V_1, V_2 and I_2
- c) If the reactance of $-j\Omega$ is replaced with an adjustable resistance R_L to maximize the power transfer, find the value of the resistance R_L .
- d) Find the energy stored in the magnetic coupled circuit at $t = 12ms$.



① $Z_{ab} \Rightarrow$

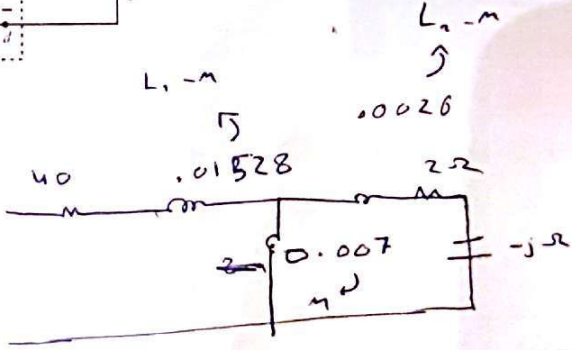

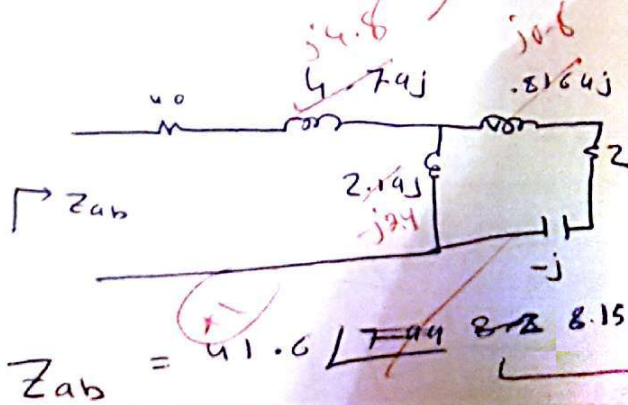$L_1 = 2.3 \cdot 10^{-2} \text{ H}$
 $L_2 = 0.0102 \text{ H}$
 $M = 7.0433 \cdot 10^{-3} \text{ H}$



$I_1 = 5.72 \angle -31.4^\circ \text{ A}$
 $I_2 = 2.95 \angle 23.1^\circ \text{ A}$
 $V_1 = 238.5 \angle -14.8^\circ \text{ V}$
 $V_2 = 2.46 \angle 4.6^\circ \text{ V}$

② $Z_{ab} = 1 + 20j$
 تلف الصفحه


including (-j2)

Power Unit

NAME: 8 - 9130 0132805 سورى
 Please write in arabic, your name, ID#, and Seat# section

Problem2 [7 marks]: For the circuit shown below,

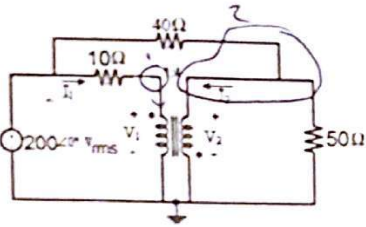- a) Find I_1, V_1, V_2 and I_2
- b) Find the power dissipated in the 40Ω resistor.



317

$$\frac{N_1}{10} - \frac{200}{10} + I_1 = 0 \quad \text{--- (1)}$$

$$\frac{N_2}{50} - \frac{200}{50} + I_2 + \frac{V_2}{50} = 0 \quad \text{--- (2)}$$

$$N_2 = -4N_1 \quad \text{--- (3)}$$

$$I_2 = \frac{1}{5} I_1 \quad \text{--- (4)}$$

$$\frac{N_1}{10} - \frac{200}{10} + I_1 = 0 \Rightarrow \boxed{V_1 + 10 I_1 = 200} \quad \text{--- (1)}$$

$$\frac{-4N_1}{50} - \frac{200}{50} + \frac{1}{5} I_1 + \frac{-4N_1}{50} = 0$$

$$\frac{-N_1}{10} + \frac{1}{5} I_1 - \frac{4}{50} N_1 = 5 \Rightarrow \boxed{N_1 \left(\frac{-1}{10} - \frac{4}{50} \right) + \frac{1}{5} I_1 = 5} \quad \text{--- (2)}$$

$$\begin{bmatrix} \frac{-1}{10} & \frac{1}{5} \\ 1 & 0 \end{bmatrix} \begin{bmatrix} N_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 5 \\ 200 \end{bmatrix}$$

$$N_1 = -64.5 \text{ V} \quad I_1 = 26.45 \text{ A}$$

$$V_2 = 258 \text{ V} \quad I_2 = 5.29 \text{ A}$$

$$D = (-.18 \cdot 10) - \frac{1}{5} = -1.55$$

$$\text{Power} = \frac{(N_2 - 200)^2}{50} = \boxed{84.1 \text{ W}}$$

$$D_x = 2000 - \frac{5}{4} = 1987.75$$

$$N_1 = -64.5 \text{ V}$$

$$D_y = -200 \cdot 4 \Rightarrow I_1 = 48 \text{ A}$$

Power Unit


NAME: _____

Please write in arabic, your name, ID#, and Seat# section

Part B

Problem 3 [8 marks]: For the circuit shown below:

- Find $Z(s) = \frac{V(s)}{I(s)}$ for the circuit shown.
- Find the poles and zeros of $Z(s)$.
- Sketch $|Z_m(s)|$ versus s , if $s = \sigma + j0$.
- If $v(t) = 25e^{-2t} u(t)$, find the complete response $i(t)$, $t \geq 0$.

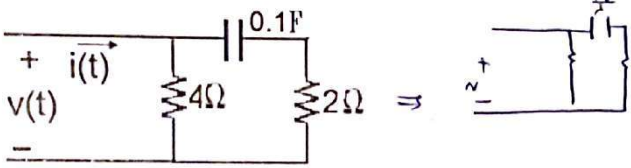

$$\textcircled{a} \left(\frac{10}{s} + 2 \right) // 4$$

$$\Rightarrow \frac{10 + 2s}{s} // 4$$

$$\frac{\frac{40 + 8s}{s}}{\frac{10 + 2s + 4s}{s}} = \frac{40 + 8s}{10 + 6s}$$

$$\Rightarrow \boxed{\frac{20 + 4s}{5 + 3s}} = Z(s)$$

$$V(s) = I(s) + Z(s)$$


$$\textcircled{a} \boxed{Z(s) = H(s) = \frac{V(s)}{I(s)}}$$

$$\textcircled{b} Z(s) = \frac{20 + 4s}{5 + 3s}$$

$Z(s)$ have zeros \textcircled{a} $-5 = s$
 $Z(s)$ have poles \textcircled{b} $s = -\frac{5}{3}$

$$\textcircled{b} \boxed{\text{Zero} = -5 \quad \text{pole} = -\frac{5}{3}}$$
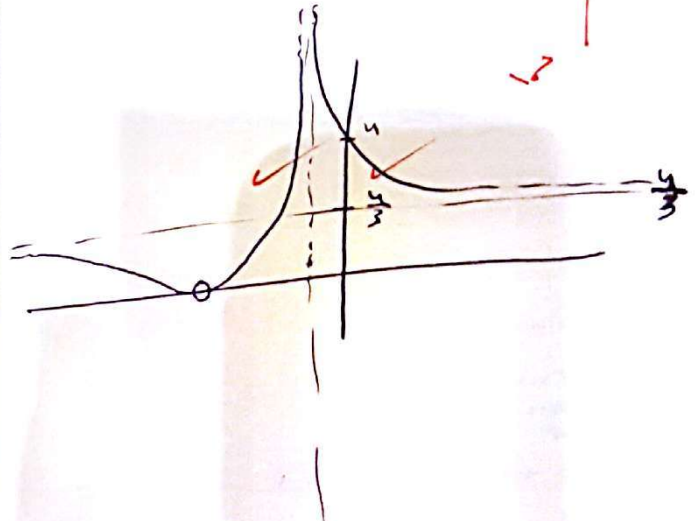
$$\textcircled{c} Z(s) = \frac{20 + 4s}{5 + 3s}$$



$$\textcircled{d} v(t) = 25e^{-2t} u(t) \quad \boxed{s = -2}$$

$$I(s) = \frac{V(s)}{Z(s)} \Rightarrow I_{nat.} + I_{forc.}$$

$$I_{forc.} \Rightarrow H(-2) \cdot V \Rightarrow \boxed{-12 + 25e^{-2t}}$$

$$I_{nat.} = A e^{-\frac{5}{3}t}$$

$$I(0) = \frac{25}{4}$$

$$A = \frac{25}{4}$$

$$= 6.25$$

$$I = 6.25 e^{-\frac{5}{3}t} + -12 + 25e^{-2t}$$

NAME:

Please write in arabic, your name, ID#, and $\frac{Seat\#}{section}$



Problem 4) [8 marks]: The balanced load in the figure shown below is fed from a balanced three-phase system having $V_{ba} = 230 \angle 30^\circ V_{rms}$ and positive phase sequence. Draw the phasor diagram, then find:

- the reading of each wattmeter W_1 and W_2 .
- the total active and reactive power drawn by the load in terms of the wattmeters readings.
- the power factor in terms of wattmeters readings.

المعطى
المعطى

$$V_{ab} = 230 \angle 210$$

$$V_{an} = 132.8 \angle 180$$

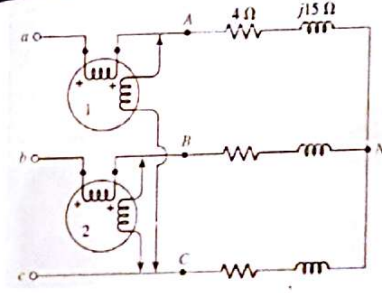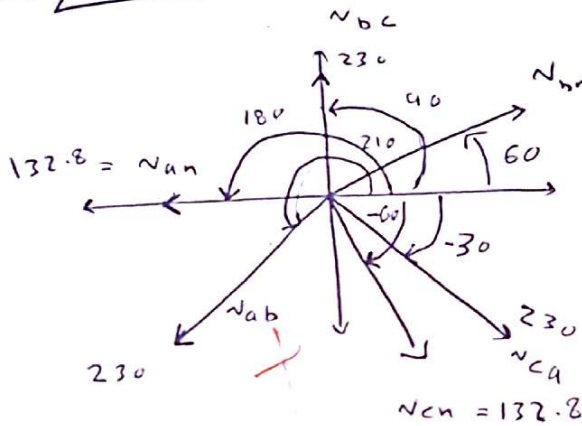

$$\begin{aligned} N_{ab} &= 230 \angle 210 & N_{an} &= 132.8 \angle 180 \\ N_{bc} &= 230 \angle 40 & N_{bn} &= 132.8 \angle 60 \\ N_{ca} &= 230 \angle -30 & N_{cn} &= 132.8 \angle -60 \end{aligned}$$

a) w_1 :

$$P_A = I_{aA} \cdot V_{AC} \cos(\theta_v - \theta_i)$$

$$N_{AC} = 230 \angle 150 \Leftrightarrow -N_{CA}$$

$$I_{aA} = \frac{N_{an}}{4 + 15j} \Rightarrow \frac{132.8 \angle 180}{4 + 15j} = 8.5 \angle 104.9$$

$$\begin{aligned} \text{So } P_A = w_1 &= 8.5 \cdot 230 \cos(150 - 104.9) \\ &= 1382.4 \text{ W} \end{aligned}$$

$$w_2: P_B = I_{bB} \cdot V_{BC} \cos(\theta_v - \theta_i)$$

$$N_{BC} = 230 \angle 40$$

$$I_{bB} = \frac{132.8 \angle 60}{4 + 15j} = 8.5 \angle -15$$

$$\begin{aligned} P_B = w_2 &= 8.5 \cdot 230 \cdot \cos(105) \\ &= -505.9 \text{ W} \end{aligned}$$

$$\begin{aligned} S_A &= 132.8 \angle 180 + (8.5 \angle 104.9) \\ &= 292.15 + 1090.3j \\ S_{Load} &= 3386.4 \angle 75 \\ &= 876.5 + 3271j \end{aligned}$$

$$\begin{aligned} PF &= \cos(75) \\ &= 0.2598 \text{ lag.} \end{aligned}$$

$$Z_{ab} = \left(\frac{40}{4 + 20j} + 7.2j \right) + \frac{(100 + 314 + .007)^2}{3.2j + 2 + R}$$

$$Z_{ab} = \frac{\left(\frac{40}{4 + 20j} + 7.2j \right) (3.2j + 2 + R) + (100 + 314 + .007)^2}{3.2j + 2 + R}$$

$$Z_{ab} = \frac{(40 + 7.2j)(3.2j + 2 + R) + (314 + .007)^2}{3.2j + 2 + R}$$

$$Z_{ab} = \frac{4.83 + 153.4 \angle 68^\circ + 406 \frac{10 R}{3.2j + 2 + R}}{(2 + 3.2j) + R}$$

$$Z_{ab} = (1 + 20j)^4$$



R should \Rightarrow $Z_{ab} = 1 - 20j$ $\Rightarrow R = 2.05 \Omega$

a) $i_1 = 5.72 \cos(100\pi t + -31.4)$

$i_2 = 4.6 \cos(100\pi t + 10.87)$

$L_1 = .02$ $L_2 = .01$ $M = .007$

$$E = \frac{1}{2} + .02 + \left[5.72 \cos(314 + .012 - 31.4) \right]^2$$

$$+ \frac{1}{2} + .01 + \left[4.6 \cos(314 + .012 + 10.87) \right]^2$$

\oplus \ominus $.007 + 5.72 + 4.6 + \cos(314 + .012 + 10.87)$
 $\cos(314 + .012 - 31.4)$

$\Rightarrow .513 \angle \left(\frac{1}{2} \right) + 2.5$

$$(1 - 20j) (2 + 3.2j) R = \frac{155.3 \angle 66.3}{155.3 \angle 66.3} + (406 \angle 10) R$$

$$R = \frac{155.3 \angle 66.3}{[(1 - 20j)(2 + 3.2j)]}$$

$$\textcircled{3} \rightarrow \vec{S}_A = V_{AC} \cdot \vec{I}_{aA}^* \Rightarrow 230 \angle 150 + 8.5 \angle -104.9$$

$$1455 \angle 45$$

$$\vec{S}_B = V_{BC} \cdot \vec{I}_{bB}^* \Rightarrow 230 \angle 90 + 8.5 \angle 15 = 1455 \angle 105$$

$$\vec{S}_{\text{tot}} = 3386.159 \angle 75$$

*in terms of
W-reading*

$$\textcircled{4} \cos(75) \text{ p.f.} \Rightarrow 0.2584 \text{ p.f.}$$