

# Diode Circuits Analysis

## ■ Graphical Method


- The intersection of the diode and the resistor current equations is calculated
- 👍 Gives good understanding to the circuit operation
- 👍 Time consuming
- 👍 Not suitable for large circuits

## ■ Analytical Method

- Both diode and resistor current equations are solved simultaneously or iteratively
- 👍 Faster than graphical method
- 👍 More accurate
- 👍 Time consuming
- 👍 Not suitable for large circuits
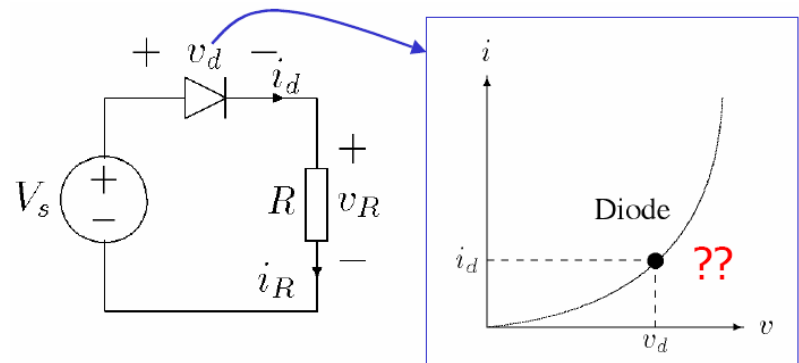
## ■ Diode Models

- Piecewise-linear diode model is used to replace the diode
- 👍 Least time consuming method
- 👍 Suitable for larger circuits
- 👍 Accuracy depends on the used model



A simple diode circuit.

## Diode Current Equation

$$I_D = I_S \left( e^{\frac{V_D}{nV_T}} - 1 \right)$$

## Resistor Current Equation


$$I_R = \frac{V_S - V_D}{R}$$

# Graphical Method

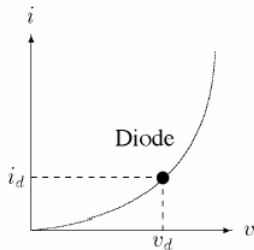
## Step 1 : Locating the Operating Points

We know

① the operating point ( $v_d, i_d$ ) is somewhere on the diode characteristic curve



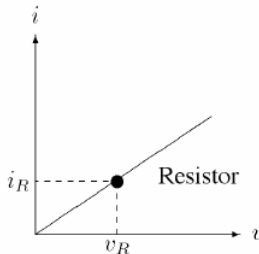
② the operating point ( $v_R, i_R$ ) is somewhere on the resistor characteristic curve


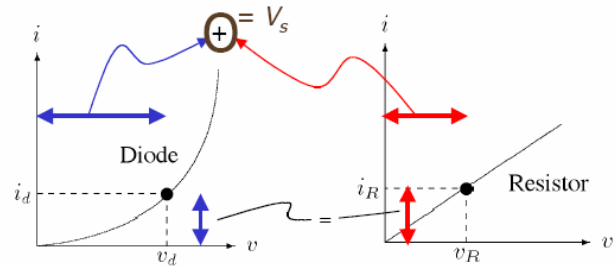
## Step 2 : KVL & KCL Constraints


We also know

from KCL :  $i_d = i_R$  AND from KVL :  $v_d + v_R = V_s$



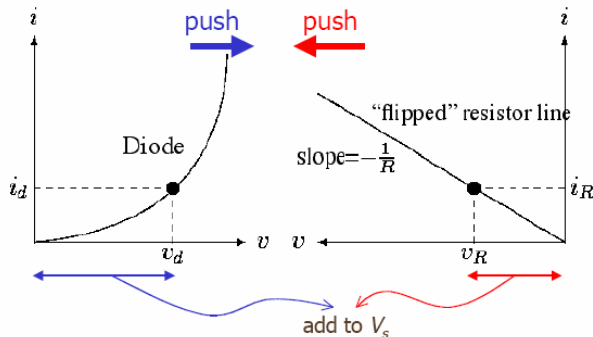
## Step 3 : Enforcing KVL & KCL

Method: flip the resistor curve horizontally; and push the two curves together horizontally until the y-axes are  $V_s$  apart.



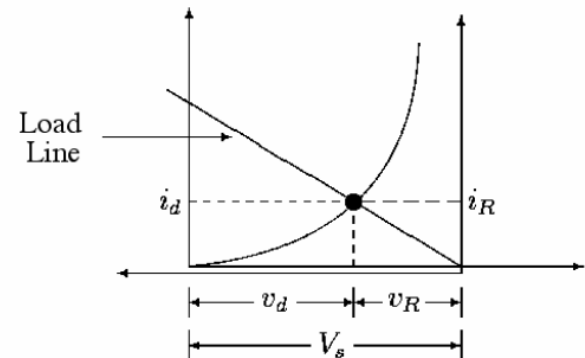
## Solution

The flipped resistor line is called the LOAD LINE.




# Graphical Method (cont.)


## General Problem

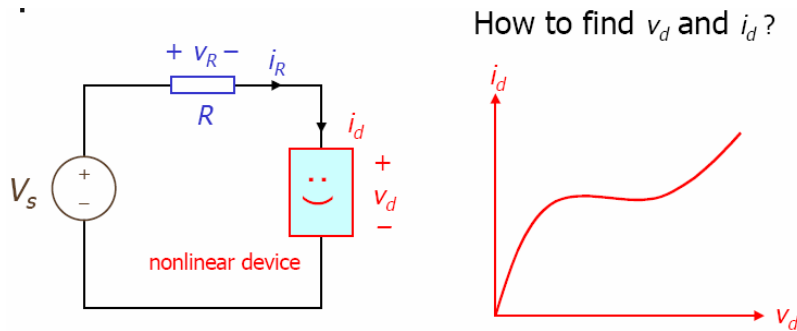

## Basic Load Line Construction

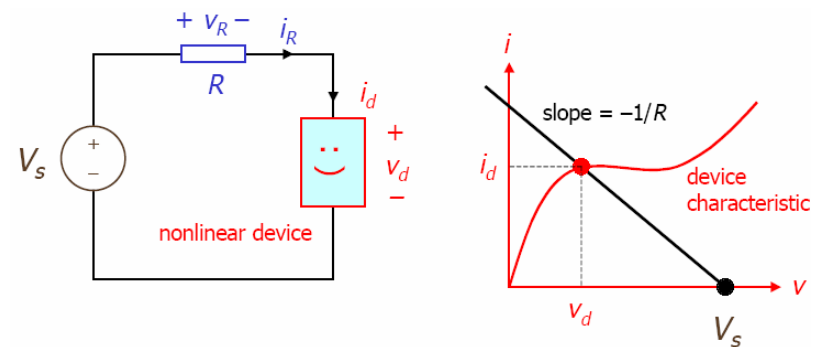


## Alternative Construction

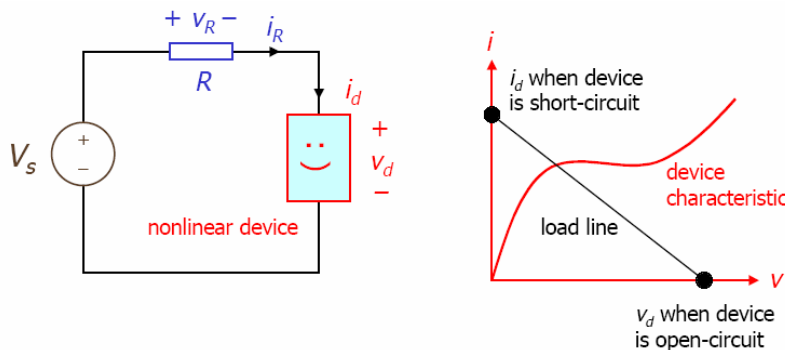

- 👍 Gives good understanding to the circuit operation
- 👎 Not suitable for large circuits

# Graphical Method (Example)

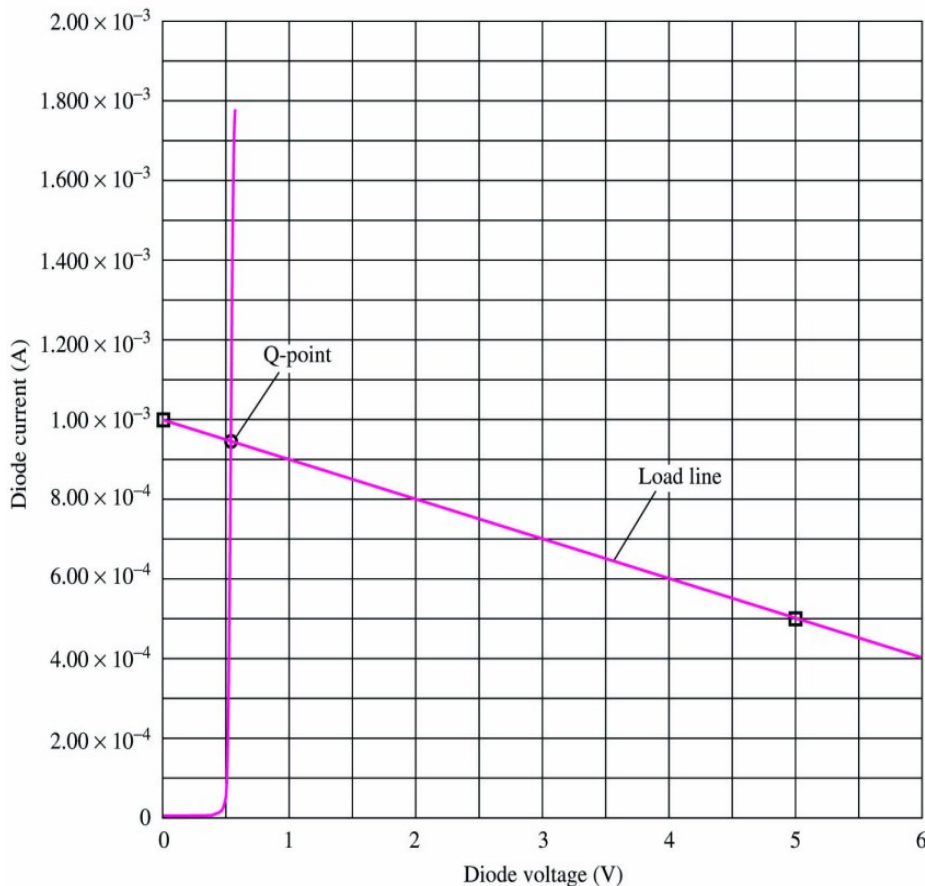

**Problem:** Find Q-point

**Given data:**  $V_S = 10$  V,  $R = 10$  k $\Omega$ .

**Analysis:**

To define the load line we use,

$$V_D = 0$$

$$V_D = 5$$
 V,  $I_D = 0.5$  mA

These points and the resulting load line are plotted. Q-point is given by the intersection of the load line and the diode characteristic:

**Q-point = (0.95 mA, 0.6 V)**

# Analytical Method

Example:

$$I_s = 10^{-15} \text{ A}, n=1, V_s = 5 \text{ V}, R = 1\text{K}$$

Step 1:

$$\text{Assume } V_D = V_{D0} = 0.7\text{V}$$

$$I_{D1} = (V_s - V_{D0}) / R = 4.3 \text{ m.A}$$

$$V_{D1} = 0.025 \ln(I_{D1} / I_s) = 0.7272 \text{ V}$$


Step 2:

$$I_{D2} = (V_s - V_{D1}) / R = 4.2728 \text{ m.A}$$

$$V_{D2} = 0.025 \ln(I_{D2} / I_s) = 0.7271 \text{ V}$$

Exact Value:
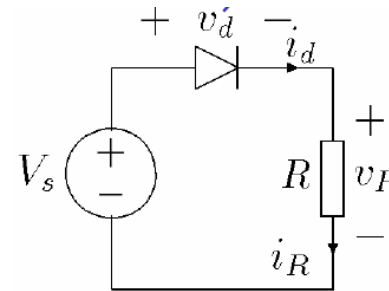
$$I_D = 4.2729 \text{ m.A}, V_D = 0.7271 \text{ V}$$




Diode Current Equation



$$I_D = I_s \left( e^{\frac{V_D}{nV_T}} - 1 \right)$$

Resistor Current Equation

$$I_R = \frac{V_s - V_D}{R}$$

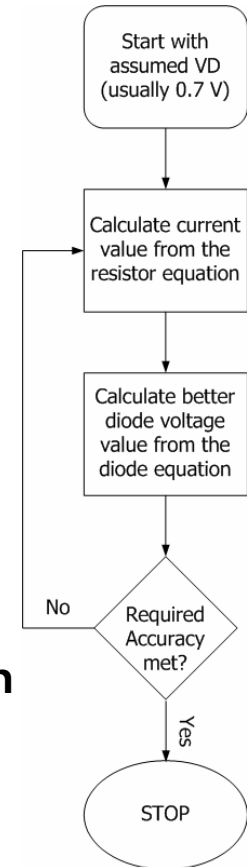


# Diode Models

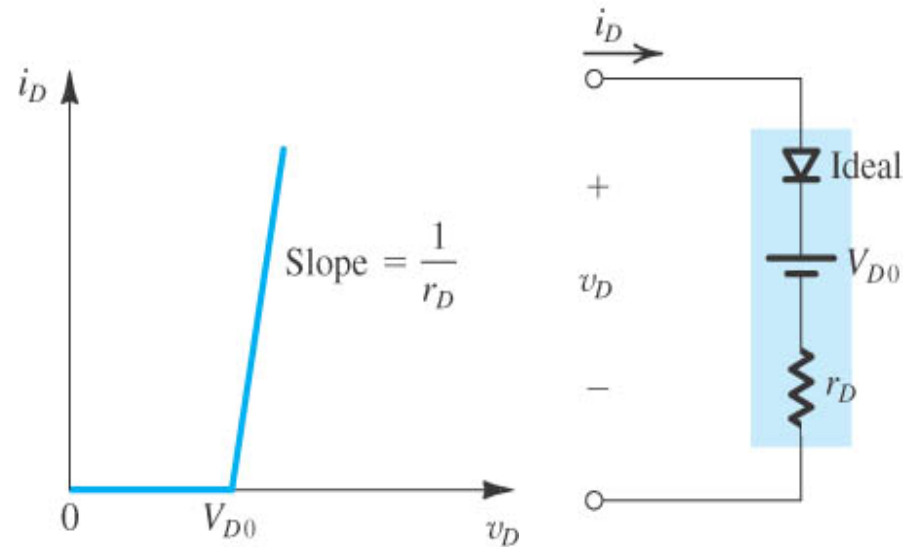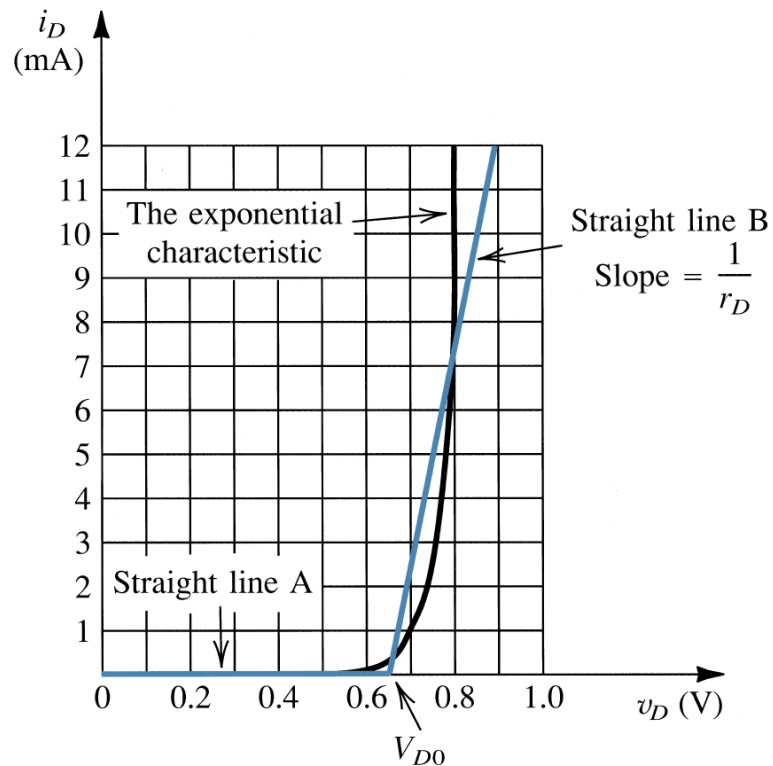


Piecewise-linear model of the diode forward characteristic and its equivalent circuit representation.

Approximating the diode forward characteristic with two straight lines.

# Diode Models (cont.)

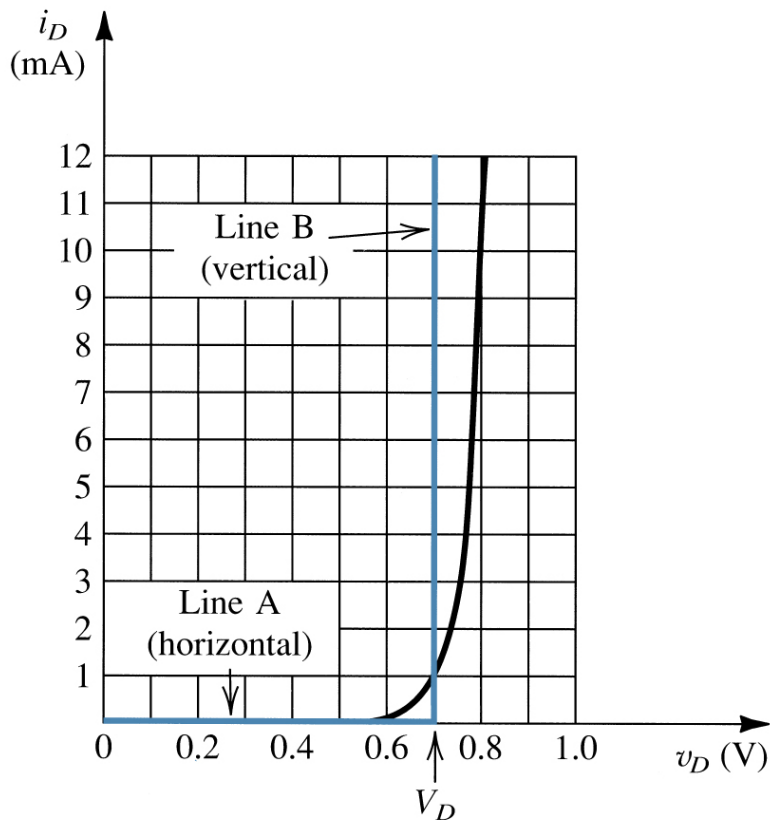

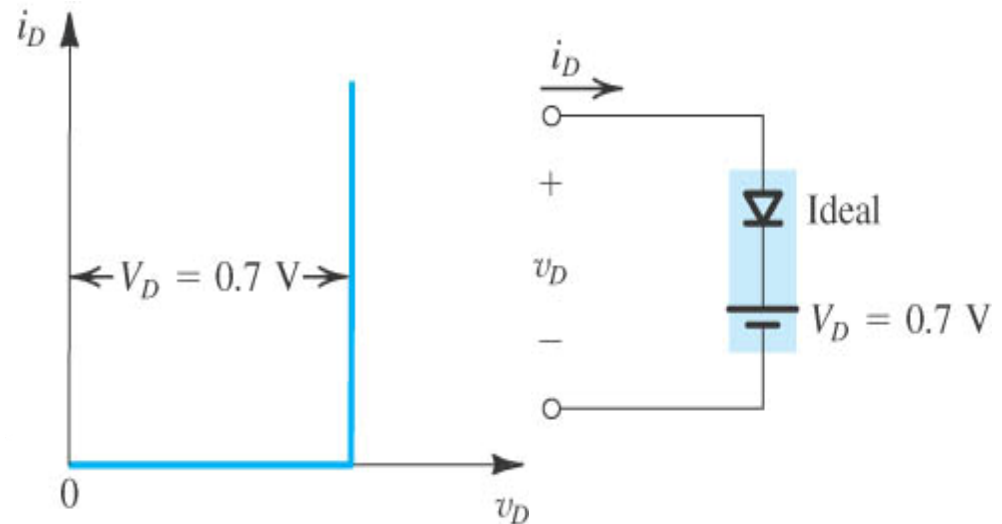Development of the constant-voltage-drop model of the diode forward characteristics. A vertical straight line (b) is used to approximate the fast-rising exponential.




The constant-voltage-drop model of the diode forward characteristic and its equivalent circuit representation.

**Also Ideal diode model may be used which means short circuit in the forward direction and open circuit in the reverse direction.**
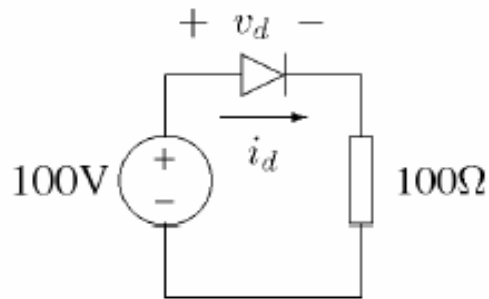
# Which Model to Use?

The choice depends on the external voltage magnitudes.




Ideal model:

$$i_d = 100/100 = 1 \text{ A}$$

With 0.7V drop:
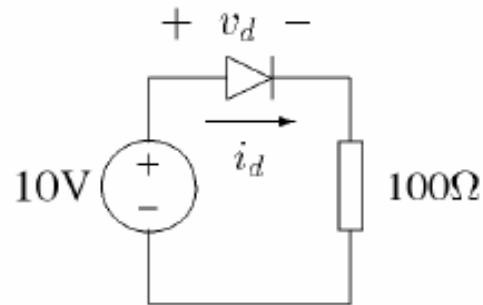
$$i_d = (100 - 0.7)/100 \\ = 0.997 \text{ A}$$




Ideal model:

$$i_d = 10/100 = 100 \text{ mA}$$

With 0.7V drop:
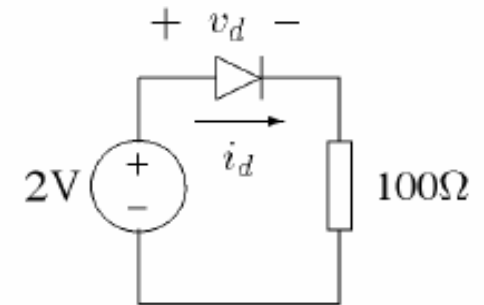
$$i_d = (10 - 0.7)/100 \\ = 93 \text{ mA}$$



Ideal model:

$$i_d = 2/100 = 20 \text{ mA}$$

With 0.7V drop:

$$i_d = (2 - 0.7)/100 \\ = 13 \text{ mA}$$





# Analysis using Diode Models

---


Diode is assumed to be either ON or OFF.

Analysis is conducted as follows:

1. Select diode model.
2. Identify anode and cathode of diode and label  $v_D$  and  $i_D$ .
3. Guess diode's region of operation from circuit.
4. Analyze circuit using diode model appropriate for assumed operating region.
5. Check results to check consistency with assumptions.  
(For forward assumption check that  $i_D > 0$ , for reverse biased check that  $v_D < V_{D0}$  or zero for ideal diode model)
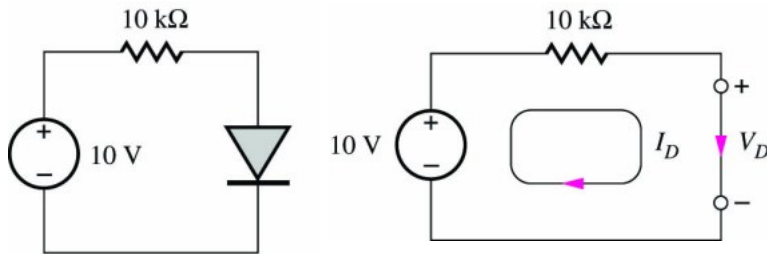
# Analysis using Ideal Model for Diode: Example

Find the Q-Point ( $I_D$ ,  $V_D$ ) for the following diodes assuming ideal diode model.




Since source is forcing positive current through diode assume diode is on.

$$I_D = \frac{(10 - 0)V}{10k\Omega} = 1mA$$

$\therefore I_D \geq 0$  our assumption is right.

**Q-point is(1 mA, 0V)**

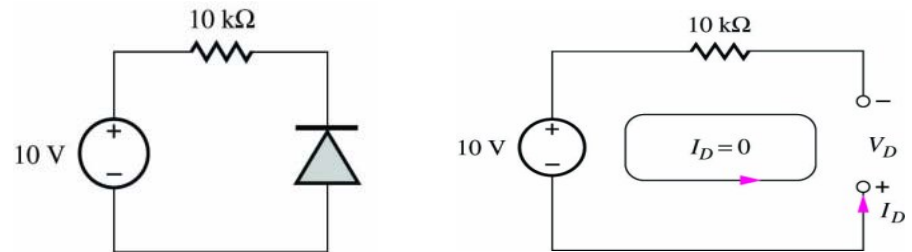

Since source is forcing current backward through diode assume diode is off. Hence  $I_D = 0$ . Loop equation is:



$$10 + V_D + 10^4 I_D = 0$$

$\therefore V_D = -10V$  our assumption is right.

**Q-point is (0, -10 V)**

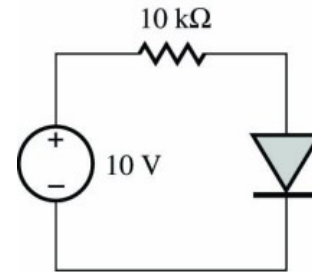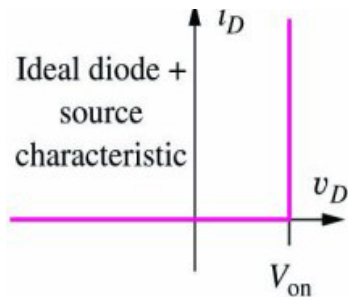
# Analysis using Constant Voltage Drop Model for Diode

Find the Q-Point ( $I_D$ ,  $V_D$ ) for the following diode assuming CVD, with  $V_{D0}=0.6V$ .



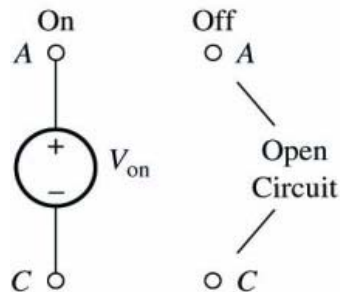
## Analysis:

Since 10V source is forcing positive current through diode assume diode is on.



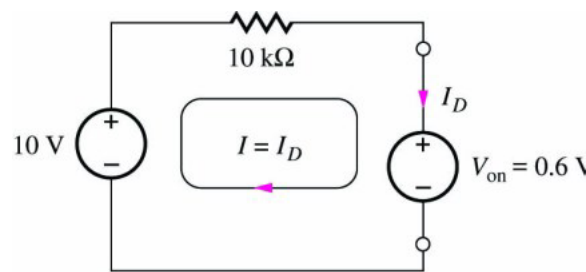$V_D = V_{on}$  for  $i_D > 0$  and  
 $i_D = 0$  for  $V_D < V_{on}$ .




$$I_D = \frac{(10 - V_{on})V}{10k\Omega}$$

$$= \frac{(10 - 0.6)V}{10k\Omega} = 0.94\text{mA}$$

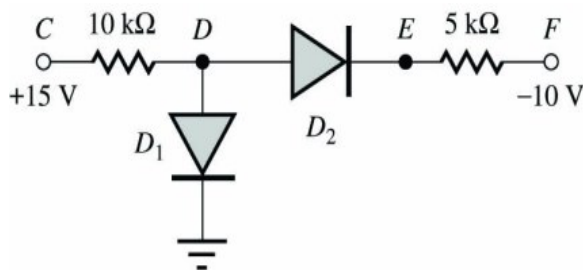
# Two-Diode Circuit Analysis

Find the Q-Point ( $I_D$ ,  $V_D$ ) for the following diodes assuming ideal diode model.



**Analysis:** Since 15V source is forcing positive current through  $D_1$  and  $D_2$  and -10V source is forcing positive current through  $D_2$ , assume both diodes are on.

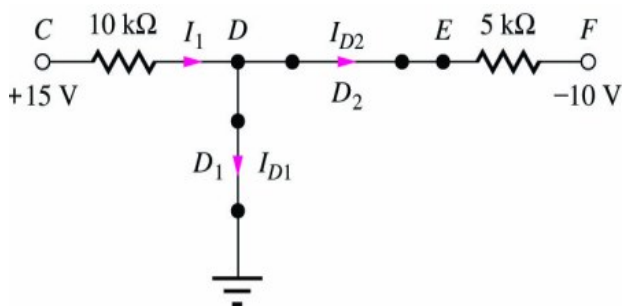Since voltage at node  $D$  is zero due to short circuit of ideal diode  $D_1$ ,




$$I_1 = \frac{(15 - 0)V}{10\text{k}\Omega} = 1.50\text{mA} \quad I_{D2} = \frac{0 - (-10)V}{5\text{k}\Omega} = 2.00\text{mA}$$

$$I_1 = I_{D1} + I_{D2} \quad \therefore I_{D1} = 1.5 - 2 = -0.50\text{mA}$$

Q-points are (-0.5 mA, 0 V) and (2.0 mA, 0 V)

But,  $I_{D1} < 0$  is not allowed by diode, so try again.

# Two-Diode Circuit Analysis (cont.)

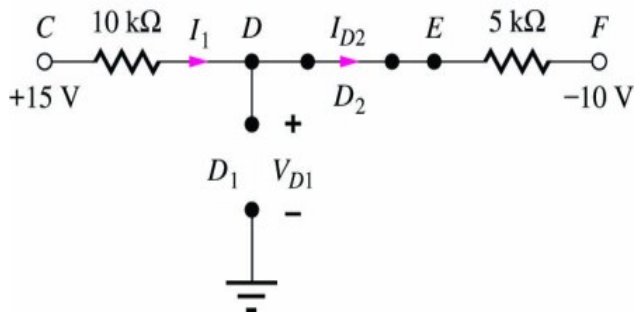

Since current in  $D_2$  but that in  $D_1$  is invalid, the second guess is  $D_1$  off and  $D_2$  on.

Since current in  $D_1$  is zero,  $I_{D2} = I_1$ ,

$$15 - 10,000I_1 - 5,000I_{D2} - (-10) = 0$$

$$\therefore I_1 = \frac{25\text{V}}{15,000\Omega} = 1.67\text{mA}$$

$$V_{D1} = 15 - 10,000I_1 = 15 - 16.7 = -1.67\text{V}$$

**Q-points are  $D_1$  : (0 mA, -1.67 V):off**

**$D_2$  : (1.67 mA, 0 V) :on**