



Name (in Arabic)

Student No.

عمر عباس

0094338

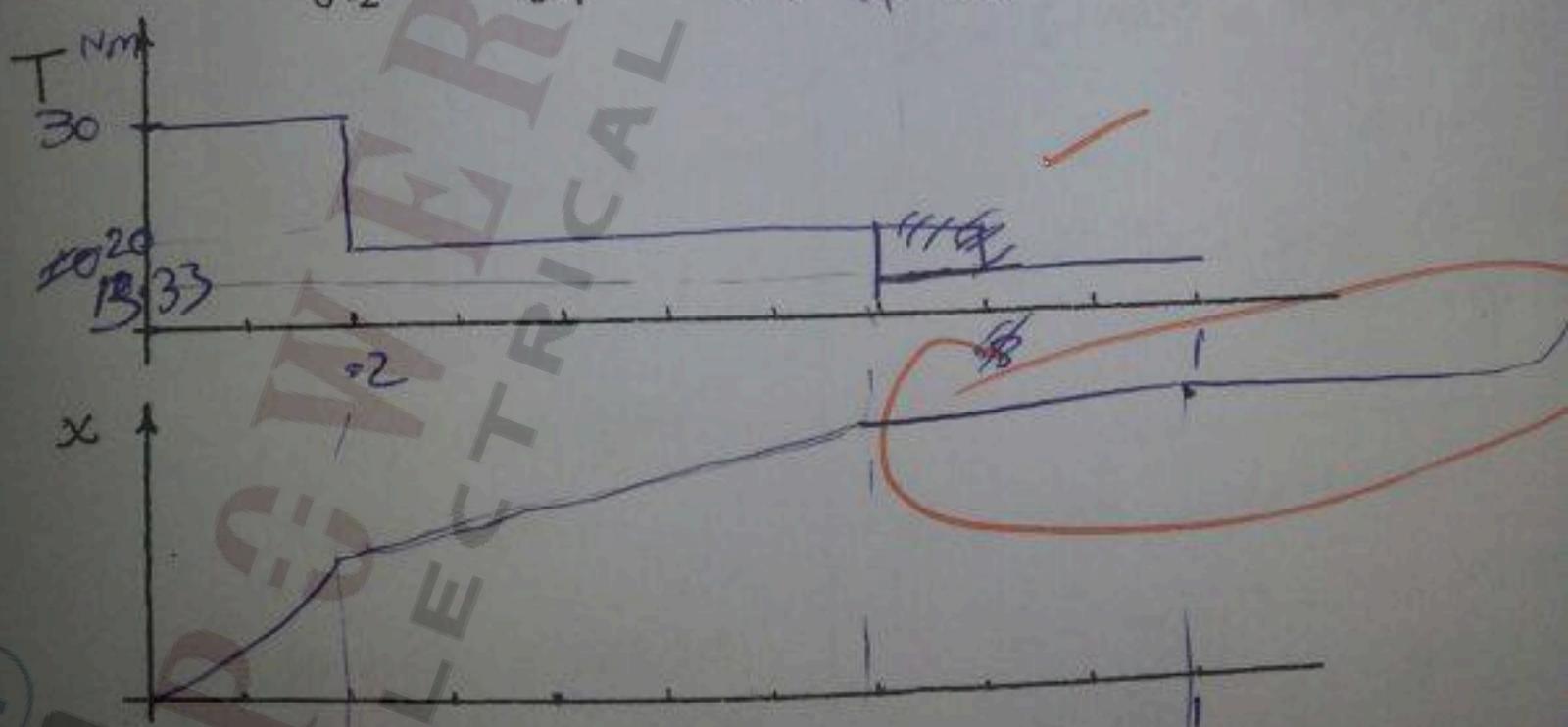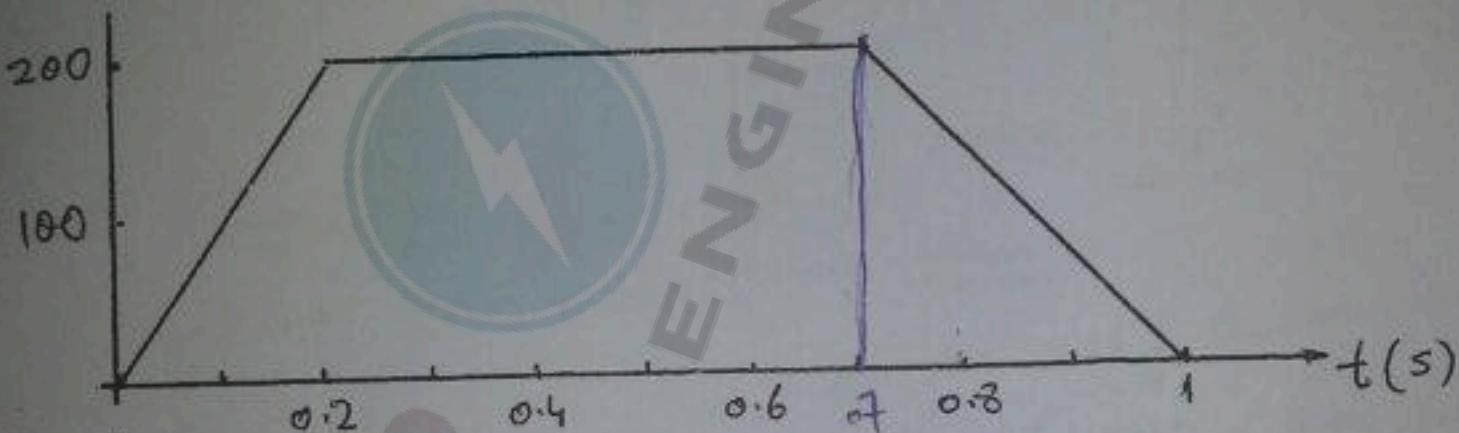1. Given the speed variation with time for certain load. Draw the variation of the Torque and position with time. Given that the constant torque is 20Nm and the motor load inertia  $J = 0.01 \text{ kgm}^2$ . 4marks



$$T_e = T_L + J \frac{d\omega}{dt}$$

$$t = 0 \rightarrow \omega = 0$$

$$\left| \begin{array}{l} \text{for } t = 1 \rightarrow \omega \\ \omega = 0 \end{array} \right. \Rightarrow T_e = T_L = 20$$

3. A 300 V dc shunt motor drives a certain load at a speed of 1000 rpm. The armature resistance =  $0.5\Omega$  and the field current = 2A. The motor draws a total current of 82A.
- The load torque is proportional to square of the speed. The speed control for this motor is performed by field current control. Calculate the field current to drive the load at 1200rpm. What is the value of the armature current then?

$$U_T = 300 \text{ V}$$


$$n_1 = 1000 \text{ rpm}$$

$$R_A = 0.5 \Omega$$

$$I_F = 2 \text{ A}$$

$$T_L = k n^2$$

6marks

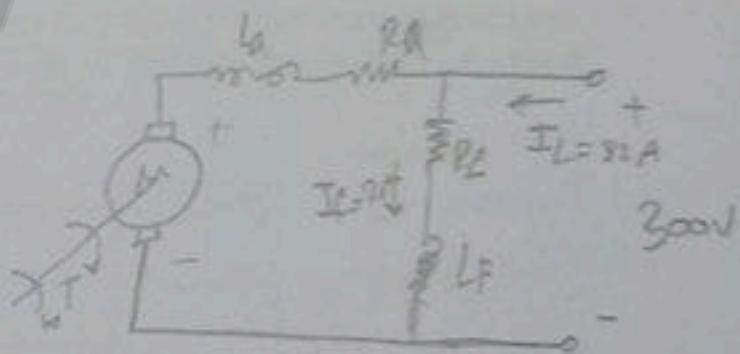

\* Find  $I_{F_2}$  at  $n_2 = 1200 \text{ rpm}$

$$I_{A_1} = I_L - I_{F_1} = 82 - 2 = 80 \text{ A}$$

$$V_T = E_{A_1} + I_{A_1} R_A$$

$$E_{A_1} = 300 - (80) \times 0.5 = 260 \text{ V}$$

$$T = k \Phi I_A$$

$$T = k \omega^2$$

L

4. A dc. Separately excited motor is driving a load torque composed of two components as given in the equation:

$$T = 25 + 0.1 \omega^2$$

The armature circuit of the motor is connected to a full-wave, ac/dc SCR converter. The input voltage to the converter is 300V (rms). The armature resistance of the motor is 5 Ω, and the field constant ( $k\phi$ ) is 2.5 V sec. Assume that the armature current is always continuous. Calculate the range of the triggering angle to operate the motor at a speed range of 0 to 600 rpm.

$$\text{at } \omega_m = \frac{600 \pi}{60} = 62.9 \text{ rad/sec.}$$

6marks

$$\alpha = \cos^{-1} \left[ \frac{T}{2IR_{av}} \right] (R_a + I_{av} R_a + k\phi)$$

$$\alpha = \cos^{-1} \left[ \frac{\bar{T}}{2 \cdot 5 \cdot 300} \right] (0.5 * (25 + 10))$$

$$\alpha = \cos^{-1} \left( 3.7 \times 10^{-3} \right) (0.5 * (168.26))$$

$$\alpha = 26.73^\circ \text{ for } \omega = 62.9$$

$$\text{for } \omega = 0$$

$$\alpha = \cos^{-1} \left[ \frac{\bar{T}}{2 \cdot 5 \cdot 300} \right] \left[ 0.5 \left( \frac{25}{2.5} \right) \right]$$

Q3  $I_a = 82 - 8 = 80 \text{ A}$   $\rightarrow E_a = 300 - 80 \left(\frac{1}{2}\right) \approx 260 \text{ volt}$

$$T = K\phi I_a \Rightarrow \frac{I_{F_2}}{I_{F_1}} \frac{I_{a_2}}{I_{a_1}} = \left(\frac{n_2}{n_1}\right)^2$$

$$\left(\frac{1200}{1000}\right)^2 = \frac{I_{F_2} I_{a_2}}{I_{F_1} I_{a_1} \rightarrow 80} \Rightarrow E_a = K\phi w$$

$$\frac{E_{a_2}}{260} = \frac{I_{F_2}}{2} * \frac{1200}{1000} \quad \cancel{E_{a_2}} /$$

$$E_{a_2} = 300 - E_{a_2} \left(\frac{1}{5}\right) \Rightarrow I_{a_2} = 1.39 \text{ A}$$

$$I_{a_2} = 165 \text{ A} \quad X$$

4. A dc. Separately excited motor is driving a load torque composed of two components as given in the equation:

$$T = 25 + 0.1 \omega^2$$

The armature circuit of the motor is connected to a full-wave ac/dc SC II converter. The input voltage to the converter is 200V rms. The armature resistance of the motor is 0.5 Ω, and the field constant ( $k\phi$ ) is 2.5 V/deg. Assume that the armature current is always continuous. Calculate the range of the triggering angle to operate the motor at a speed range of 0 to 600 rpm.

marks

for  $\alpha = 0^\circ$

$1\phi = 9.5 \text{ V/deg}$

continuous Inv

6

$$T_2 = k\phi I_A$$

$$\text{at } n_1 = 0$$

$$T_1 = 25 + 0.1 \times 0^2 = 25 \text{ N-m}$$

$$I_{A1} = \frac{T}{k\phi} = \frac{25}{2.5} = 10 \text{ A}$$

$$E_{A1} = k\phi \omega_1 = 2.5 \times 62.83 = 157.1 \text{ V}$$

$$2 \text{ Units} \quad \cos(\alpha) = \frac{E_{A1}}{240} = \frac{157.1}{240} = 0.6541$$

$$\frac{2 \times 200 \sqrt{2}}{\pi} \cos(\alpha) > 0.6541 \times 10$$

$$270.1 \cos(\alpha) = 2.2 \times 10$$

$$\cos^{-1}\left(\frac{2.2}{270.1}\right) = 82.93^\circ$$

$$I_{A2} = \frac{T_2}{k\phi} = \frac{419.3}{2.5} = 167.72 \text{ A}$$

$$E_{A2} = k\phi \omega_2 = 2.5 \times 62.83 = 157.1 \text{ V}$$

$$\frac{2 \times 200 \sqrt{2}}{\pi} \cos(\alpha) = 157.1 + 0.5 \times 167.72$$

$$270.1 \cos(\alpha) = 241.06$$


$$\alpha = \cos^{-1}\left(\frac{241.06}{270.1}\right) = 26.31^\circ$$

range of α

$$(26.31^\circ - 82.93^\circ)$$

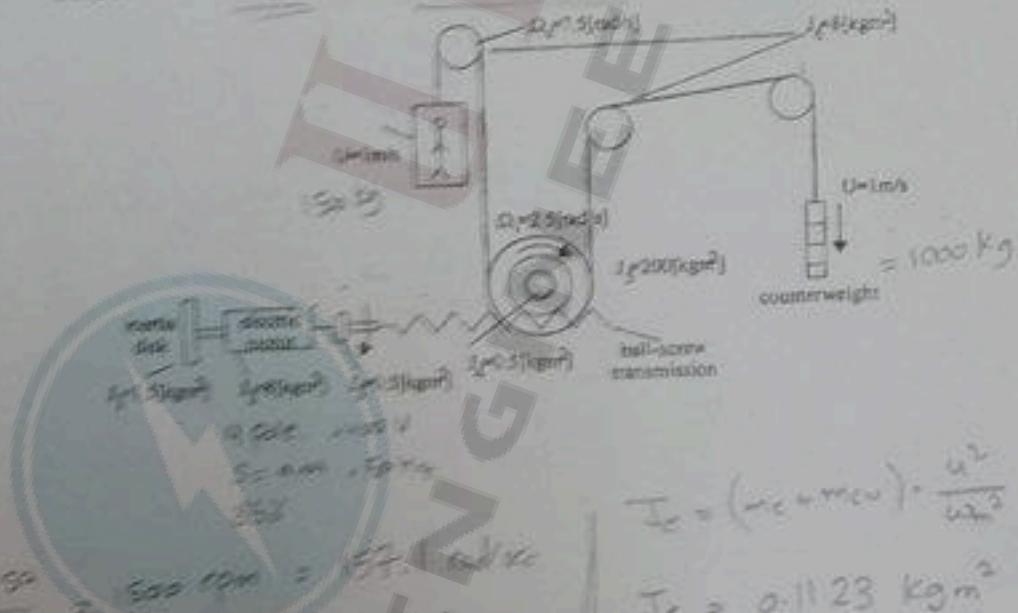2. The figure below shows an elevator drive with multiple mechanical transmission and counterweight. The motor is a 4 pole motor operating at a slip of 0.05 and an efficiency of 85% from a 3-phase supply of 400V, 50 Hz. The counterweight = 1000Kg and the elevator load is 1500kg. 5marks

Calculate the torque and the electromagnetic power without counterweight.



$$T_{em} = (m \cdot g \cdot r) \cdot \frac{\omega^2}{\omega_m^2} = \frac{(1500 + 1000) \times 9.81}{(149.2)^2}$$

$$T_{em} = 0.1123 \text{ kgm}^2$$

$$T_{em} = J_m + J_c = 0.05 + 0.1123 = 0.1623 \text{ kgm}^2$$

$$\Sigma T = \alpha \sum J$$

$$T_{em} \cdot \omega_m \cdot \eta = m \cdot g \cdot r$$

$$T_{em} = \frac{1500 \times 9.81 \times 1}{149.2 \times 0.85} = 116.03 \text{ N.m}$$

$$P_{em} = T_{em} \cdot \omega_m = 116.03 \times 149.2 =$$

$$P_{em} = 17311.576 \text{ W}$$

$$4975 - 128V_i' + .092V_i'^2 + 863V_i' - .125V_i'^2 \\ - .033V_i'^2 - 4.17V_i' + 443.5 \\ - 63.18 - j89.2$$

Torque  
↑

5. A 3-phase, 400V, 50Hz, 6-poles, induction motor is driving a constant load of 80Nm. The parameters of the motor are:

$$R_{TH} = R_1 = 0.5\Omega \quad R_2 = 0.3\Omega \quad X_{TH} = 2\Omega \quad X_2 = 2\Omega \quad N_1/N_2 = 2$$

7marks

- (i) Calculate the magnitude of the injected voltage that will reduce the motor speed to 700 rpm

$$\frac{120fs}{P} = \frac{120(50)}{6} = 1000 \text{ rpm}$$

new speed.

$$\frac{n_s - n}{n_s} = \frac{1000 - 700}{1000} = .3$$

$$(2) * 2^2 = 8 \text{ } \sim$$

$$(.3) * (2)^2 = 1.2 \text{ } \sim$$

$$3 + 2 = 10 \text{ } \sim$$

$$T_d = \frac{3}{S \times S} \left[ (I_2')^2 * R_2 + V_i' I_2' \cos \theta \right]$$

$$80 = \frac{3}{.3 * \left( \frac{2\pi * 1000}{60} \right)} \left[ (I_2')^2 * (1.2) + V_i' I_2' \cos \theta \right]$$

$$I_2' = \frac{\left[ 230.94 - \frac{V_i'}{.3} \right] * .3}{10.97} * .3$$

$$I_2' = \frac{\left[ 69.28 - \frac{V_i'}{3.29} \right]}{3.29}$$

$$80 = \frac{3}{10\pi} \left[ \left( \frac{69.28 - V_i'}{3.29} \right) * 1.2 + V_i' \right]^2$$

$$= 3 \left[ 4801.1 - 138.58V_i' + V_i'^2 \right] + \sqrt{\frac{69.28 - V_i'}{3.29}}$$

A 300 V dc shunt motor drives a certain load at a speed of 1000 rpm. The arm resistance =  $0.5\Omega$  and the field current = 2A. The motor draws a total current of  $I_f + I_a$ . The load torque is proportional to square of the speed. The speed control for motor is performed by field current control. Calculate the field current to drive load at 1200 rpm. What is the value of the armature current then?

6marks

$$I_f,$$

$$32 - 2 = 80A.$$

A.

$$= K\phi_1 I_{a1}$$

$$= K\phi_1 (80)$$

$$\propto \phi_1 I_{a2}$$

$$(1000 \text{ rpm})^2$$

$$\rightarrow (1200)^2$$

$$\frac{\phi_1}{\phi_2} \frac{n_1}{n_2} = \frac{V - I_{a1}}{V - I_{a2}}$$

$$\frac{\phi_1}{\phi_2} = \frac{n_2}{n_1} \left[ \frac{300 - I_{a1}}{300 - I_{a2}} \right]$$

$$\frac{\phi_1}{\phi_2} = \frac{1200}{1000} \left[ \frac{300 - I_{a1}}{300 - I_{a2}} \right]$$

$$\frac{\phi_1}{\phi_2} = K_2 \frac{31}{300}$$

see table 10.1

(Ass)

a. @ operating point 1  $\rightarrow T = 40 = \frac{V^2 s_1}{s_1(\omega_1) R_1}$

$$\rightarrow \frac{120P}{P} = \frac{120 \times 60}{4} = 1800 \text{ rpm} \rightarrow n_1 = \frac{1800}{60} = 30 \text{ rad/s}$$

$$\approx 40 = \frac{(480)^2 s_1}{188.5 \times 0.3} \rightarrow s_1 \approx 0.01 \quad (\approx 0.0001) \rightarrow I_m = \frac{V s_1}{\sqrt{3} R_2} = \frac{480 \times 0.01}{\sqrt{3} \times 0.3} = 9.237 \text{ A}$$

b. @ operating point 2  $\rightarrow I_m = \frac{V}{\sqrt{3} X_{eq}} = \frac{480}{\sqrt{3} \times 12} = 23.09 \text{ A}$

c. @ operating point 3  $\rightarrow I_m = \frac{V}{\sqrt{3} X_{eq}} = 23.09 \text{ A}$

d. @ operating point 4  $\rightarrow T = \frac{V^2 R_2}{s_2(-\omega_2) X_{eq}^2} = \frac{(480)^2 \times 0.3}{11 (-188.5)(12)^2} = -2.546 \text{ NM}$

e. @ operating point 5  $\rightarrow T_B = T_1 = 40 = \frac{V^2 s_2}{(-\omega_2) R_2} \rightarrow s_2 = \frac{40 (-\omega_2) (R_2)}{V^2} \approx -0.01 \text{ (rad/s)}$


f.  $T_B = T_1 = 40 \text{ NM}$

g.  $n = n_s(1 - s_2) = 1800(1 + 0.01) = 1818 \text{ rpm}$


6. Sketch the relationship of torque speed for

2marks


2

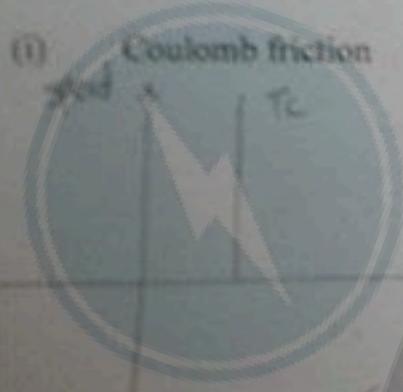

(i) Coulomb friction

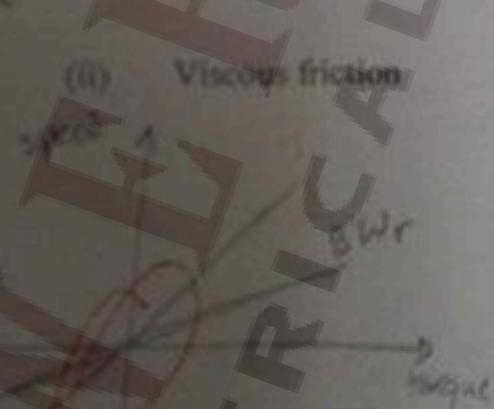

(ii) Viscous friction

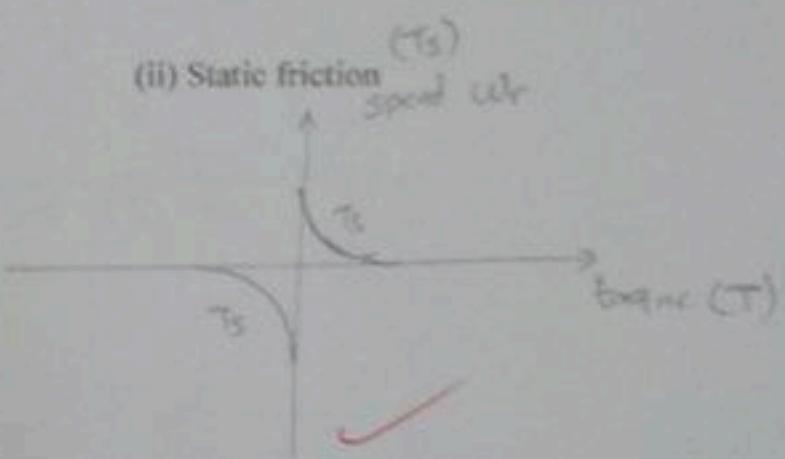

(ii) Static friction

(iv) Windage friction

