

208

Question 1 (4 pts)

A 50 Ohm T.L. is terminated in a load with impedance $(100 + j 50)$ Ohm. Find reflection coefficient and VSWR

4

$$Z_0 = 50 \Omega \quad Z_L = 100 + j50 \Omega \quad Z_n = \frac{100 + j50}{50} = 2 + j1$$

$$F = \frac{Z_n - 1}{Z_n + 1} = \frac{2 + j1 - 1}{2 + j1 + 1} = \frac{1 + j1}{3 + j1} = 0.447 \angle 26.565^\circ$$

$$S = \frac{1 + |F|}{1 - |F|} = \frac{1 + 0.447}{1 - 0.447} = 2.616$$

Question 2 (4 pts)

A slotted line with 50 Ohm characteristic impedance is terminated with an unknown load. It was found that $VSWR = 3$, distance between the two minimas = 30 cm, and first minima at 12 cm from load. Compute load impedance

4

$$Z_0 = 50 \Omega \quad S = 3 \quad d = 30 \text{ cm} \quad d_{min} = 12 \text{ cm}$$


$$S = \frac{1 + |F|}{1 - |F|} \quad S - |F|S = |F| + 1 \quad |F| = \frac{S - 1}{S + 1} = \frac{2}{4} = 0.5$$

$$\frac{\lambda}{2} = 30 \text{ cm} \quad \lambda = 60 \text{ cm}$$

$$\theta_r = 2\beta d_{min} = 2\pi(2n+1)$$

$$\theta_r = 2 \times \frac{2\pi}{60 \times 10^{-2}} \times 12 \times 10^{-2} = 2\pi = -36$$

$$F = 0.5 \angle -36$$

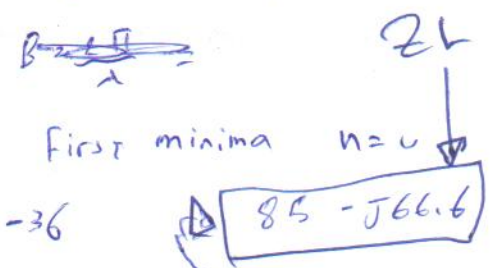

$$F = \frac{Z_n - 1}{Z_n + 1} \quad F(Z_n + 1) = Z_n - 1 \quad Z_n F + F = Z_n - 1$$

$$Z_n = \frac{1 + F}{F - 1} = \frac{1 + 0.5 \angle -36}{0.5 \angle -36 - 1} \quad Z_L = 2n Z_0 = 2.16 \angle -38 = 2.16 \times 50 = 108 \angle -38$$

$$Z_L = 85 - j66.6$$

دسته اولی

Question 3 (6 pts)

Given $\Gamma = 0.5 \exp(j 60)$, and $\lambda = 24$ cm. find the location of first minima and maxima


$F = 0.5 e^{j60}$ $|F| = 0.5$ $\theta r = 60$ $\lambda = 24$

① $n=0$ $d_{min} = \frac{\theta r \lambda}{4\pi} + \frac{(2n+1)\lambda}{4} = \frac{\frac{\pi}{3} \times 24 \times 10^{-2}}{4\pi} + \frac{24 \times 10^{-2}}{4} = 8 \text{ cm}$

② $n=0$ $d_{max} = \frac{\theta r \lambda}{4\pi} + \frac{n\lambda}{2} = \frac{\frac{\pi}{3} \times 24 \times 10^{-2}}{4\pi} + 0 = 2 \text{ cm}$

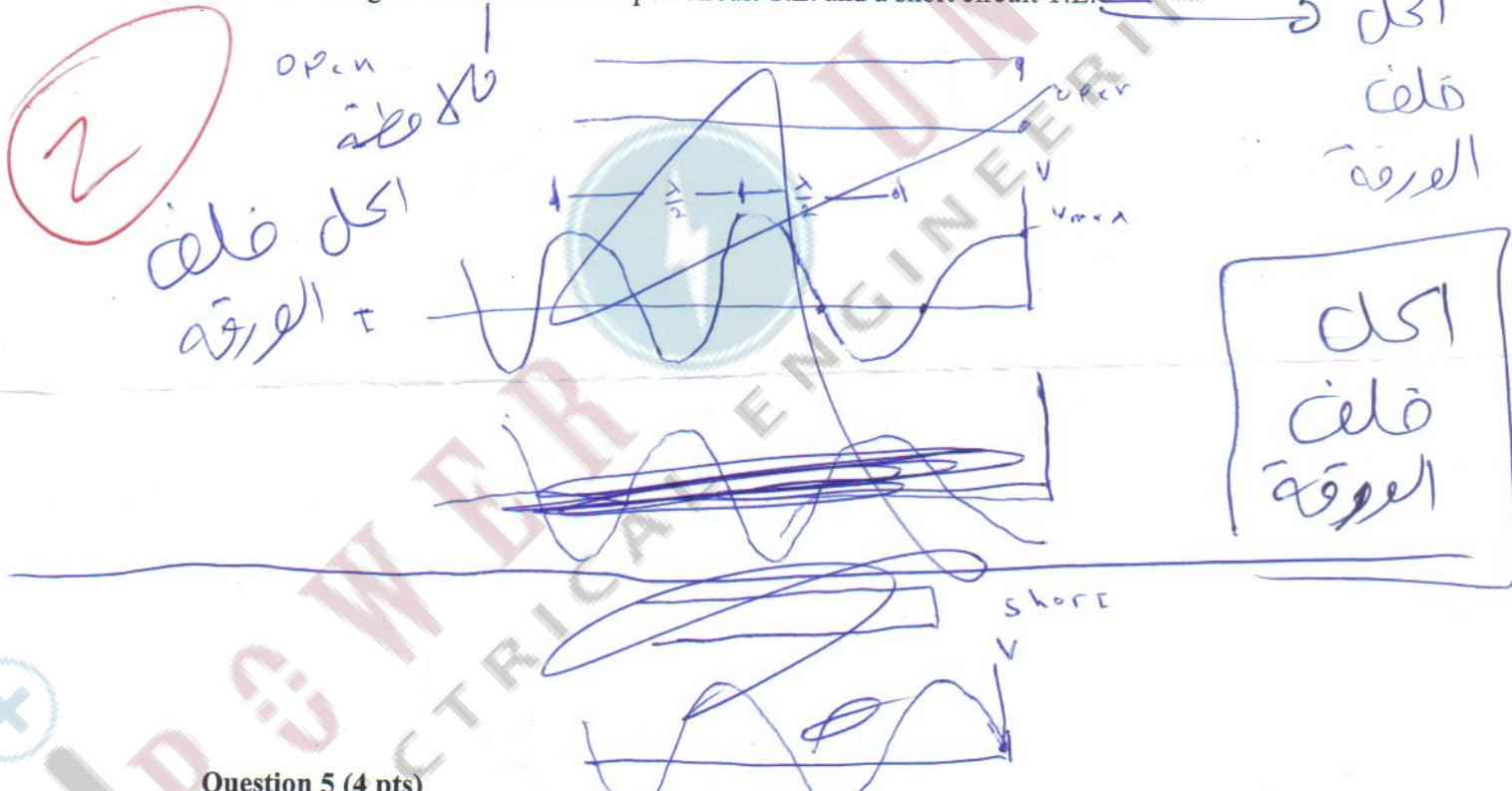
Question 4 (4 pts)

Plot the voltage and current on an open circuit T.L. and a short circuit T.L.



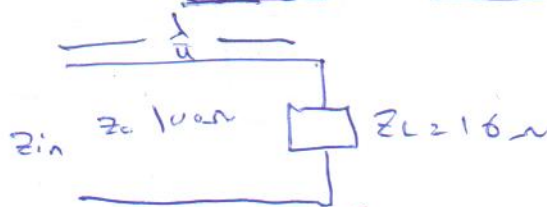Question 5 (4 pts)

Use a quarter wavelength transformer to match a load of 16 Ohm to a T.L. of 100 Ohm





$Z_{in} = Z_0 \left(\frac{Z_L + j Z_0 \tan(\beta L)}{Z_0 + j Z_L \tan(\beta L)} \right)$

$Z_0 = \sqrt{Z_{in} Z_L}$




$Z_{in} = \frac{(100)^2}{16} = 625 \Omega$

To happen matching the value of Z_{in} must be equal 625

Question (a)

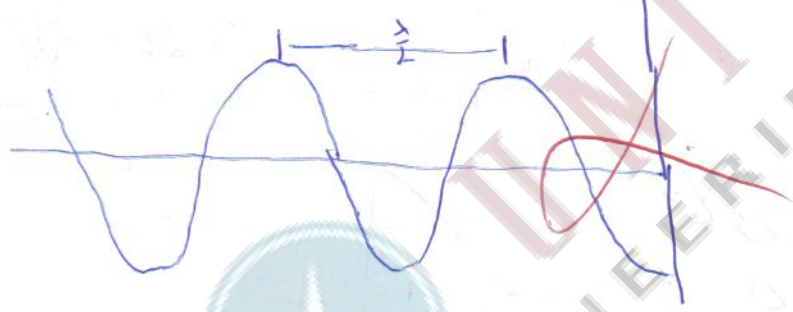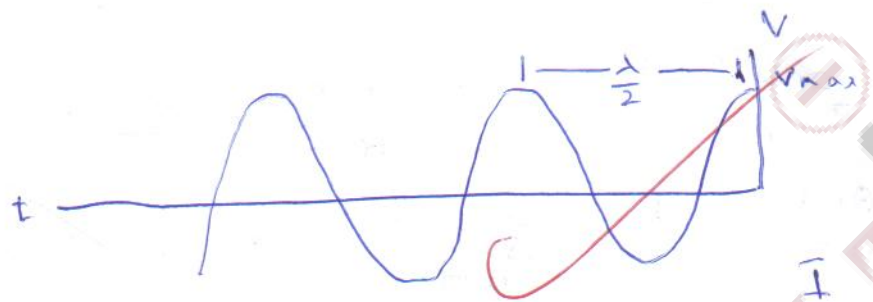

Short

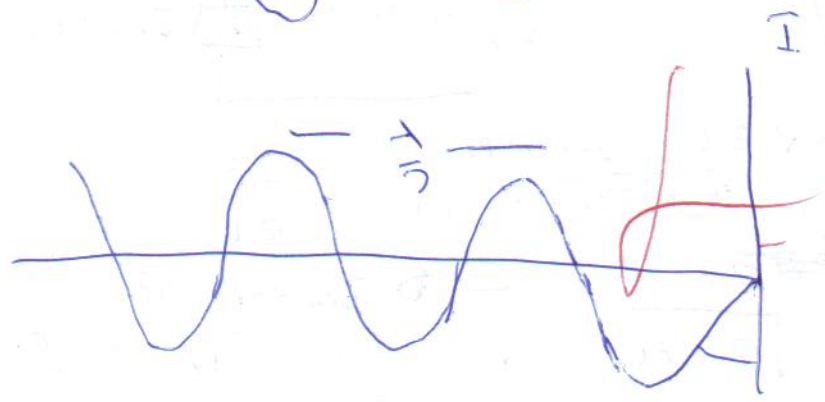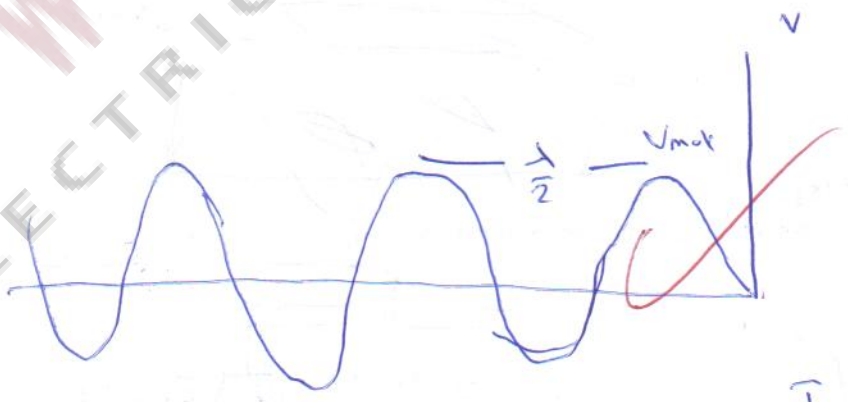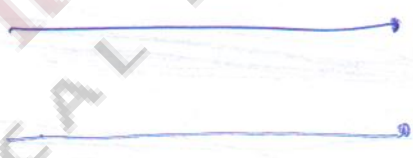

Question 6 (10 pts)


A load of impedance $(25 - j 50)$ Ohm is connected to a 50 Ohm T.L. Use a short circuit stub to perform matching using the Smith Chart.

① we find $Z_n = \frac{25 - j 50}{50} = 0.5 - j 1$

② $Y_n = \frac{1}{Z_n} = \frac{1}{0.5 - j 1} = 0.4 + j 0.8$

③ we perform Y_n on Smith chart

④ we move to $1 + jx$ to find value of x

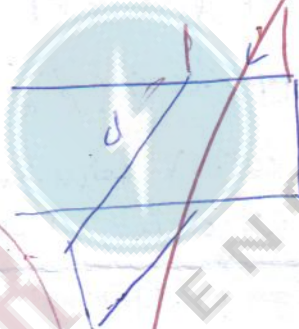

now we find L_A, L_B

$L_A = 0.063 \lambda$

$L_B = 0.207 \lambda$

we choose

$L_A = 0.063 \lambda$

less cost

now we find $d??$

$d_A = \text{stub impedance} = \pm j 1.58$

$d_A = 0.089 \lambda$

$d_B = 0.409 \lambda$

Question 7 (2 pts)

A 1.05 GHz generator with $v_g(t) = 10 \sin(\omega t + 30)$, with impedance of 10 Ohm is connected by a T.L. with 50 Ohm impedance and terminated in a load of $(100 + j 50)$ Ohm. The phase velocity is 0.7 c. Find $v(z,t)$ and $i(z,t)$ on line



V_{in} $0.7c = 6 \times 10^8 \rightarrow \lambda = \frac{0.7 \times 3 \times 10^8}{1.05 \times 10^9} = 0.2$ $\lambda = 0.2$

$\beta L = \frac{2\pi}{\lambda} = \frac{2\pi}{0.2} = 1800$ $\beta L =$

$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan(\beta L)}{Z_0 + jZ_L \tan(\beta L)} = Z_L = 100 + j50$

$V_g(t) = 10 \sin(\omega t + 30) = 10 \cos(\omega t - 60)$

$V_g = 10 \angle -60$

voltage divider

$V_{in} = \frac{Z_{in} \times 10 \angle -60}{Z_{in} + Z_g} = 9.256 e^{-j57.87}$

$V^+ = V_{in} \left(\frac{e^{j\beta z} + F e^{-j\beta z}}{e^{j\beta z} + F e^{-j\beta z}} \right) = 9.256 \angle -57.87 \left(\frac{e^{j\beta z} + F e^{-j\beta z}}{e^{j\beta z} + F e^{-j\beta z}} \right)$

$F = \frac{Z_L - Z_0}{Z_L + Z_0} = 0.852 \angle 4.61$

$V^+ = 9.256 \angle -57.87 (1 + F) = 17 \angle -55.75$

$V(z,t) = v^+ (e^{j\omega t - \beta z} + F e^{-j\omega t + \beta z}) = 17 \angle -55.75 \left(e^{j\omega t - \beta z} + \frac{0.852 e^{j\omega t + \beta z}}{F} \right)$

$= 17 \cos(\omega t - \beta z - 55.75) + 14.482 \cos(2.1\pi \times 10^9 t - \beta z - 51.6)$

$I(z,t) = 1.7 \cos(\omega t - \beta z - 55.75) - 1.448 \cos(2.1\pi \times 10^9 t - \beta z - 51.6)$

$2\pi f = 2.1\pi \text{ GHz}$

Question 8 (2 pts)

Use the incident voltage and current waves on a T.L. to find an expression for the incident power on the T.L.

$P_i = \frac{1}{2} \text{Real} (V_i I_i^*)$

$P_i = \frac{1}{2} \text{Real} (V_i \times I_i^*)$

$V_i(z) = V^+ e^{-\beta z}$

$I_i(z) = \frac{V^+}{Z_0} e^{-\beta z}$

$P_i = \frac{1}{2} \text{Real} \left(\frac{V^+}{Z_0} e^{-\beta z} e^{\beta z} \right) = \frac{V^+{}^2}{2Z_0}$

$\frac{V^+{}^2}{2Z_0}$

Power for incident

The Complete Smith Chart

Black Magic Design

