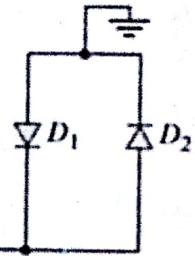


Question 1

a) The parameters for both D_1 and D_2 in the circuit shown are $V_D = 1.7V$ and $r_f = 20 \Omega$. The current in each diode is to be limited to $15mA$ when $V_I = \pm 9V$. Determine the value of R given that the breakdown voltage for each diode is $100V$ and $r_z = 30 \Omega$.



$$V_D = 1.7V$$

$$r_f = 20 \Omega$$

$$r_z = 30 \Omega$$





$$I_D = 15mA$$

$$R + r_f = \frac{V_I - V_D}{I} \Rightarrow R + 20 = \frac{9 - 1.7}{15 \times 10^{-3}} = R + 20$$

$$R + 20 = \frac{8.7}{15 \times 10^{-3}} \Rightarrow R + 20 = 48 \Omega$$

$$\boxed{R = 466.6 \Omega}$$

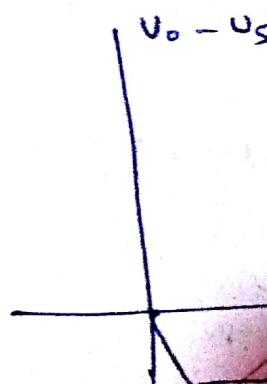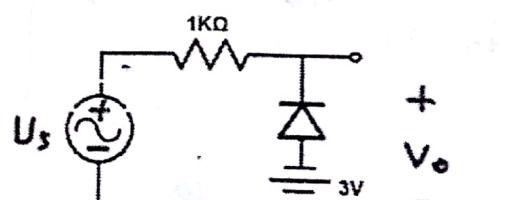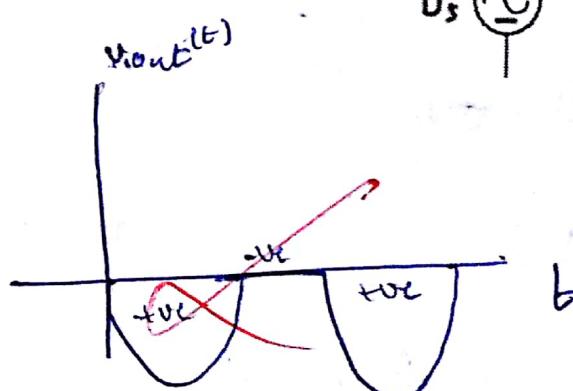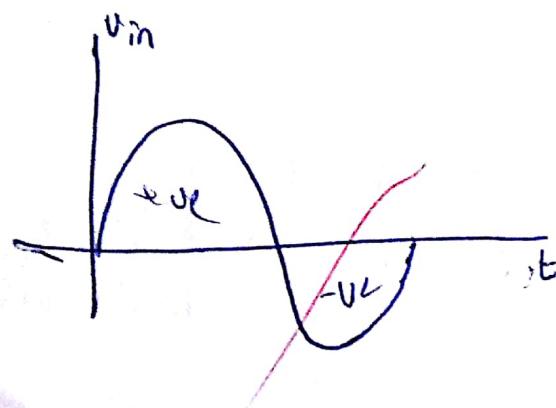b) Given the circuit shown where $v_s = 9 \sin(\omega t)$. Sketch $v_o(t)$ and the $v_o - v_s$ characteristic.



	ups min	I_L Max
Min		
Max		

Question 2


a) Consider the Zener diode circuit shown. Let $V_1 = 60V$, $R_i = 150 \Omega$, and $V_Z = 16V$. Assume $r_z = 0 \Omega$. The power rating of the diode is 4 W and the minimum diode current is to be 5 mA.

(a) Determine the range of load currents.

$$I_L = \frac{V_Z}{R_L}$$

$$I_Z = \frac{V_B - V_Z - I_L}{R_Z}$$

$$V_Z = V_L = 16V$$

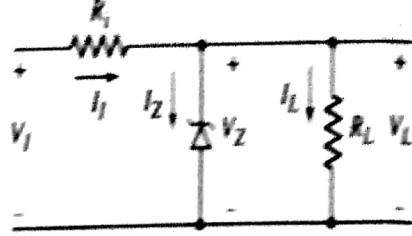

$$P = 4W$$

$$P_Z = I_Z V_Z$$

$$\frac{4}{16} = I_Z \frac{16}{16}$$

$$I_Z = 0.25A$$

$$I_{\text{min}} = \frac{V_{B\text{ min}} - V_Z}{R_i} - I_{L\text{ max}}$$

$$\frac{60 - 16}{150} - 0.25 = 0.43A$$

(b) Determine the range of load resistance.

$$V_L = 16V \rightarrow V_L = I_L R_L$$

$$R_L = \frac{16}{0.43} = 37.20 \Omega$$

1.5

b) The cut-in voltage of each diode in the circuit shown is 0.7V. Determine I_{D1} , I_{D2} , and I_{D3} . Use the assumption that all diodes are ON.



assume $D_3 \rightarrow \text{off}$

D_1, ON

D_2, ON

loop ①
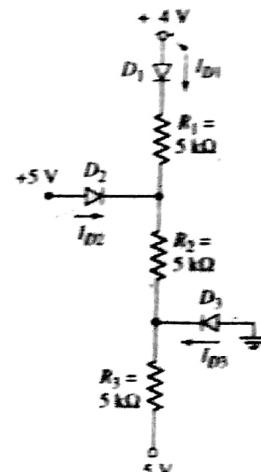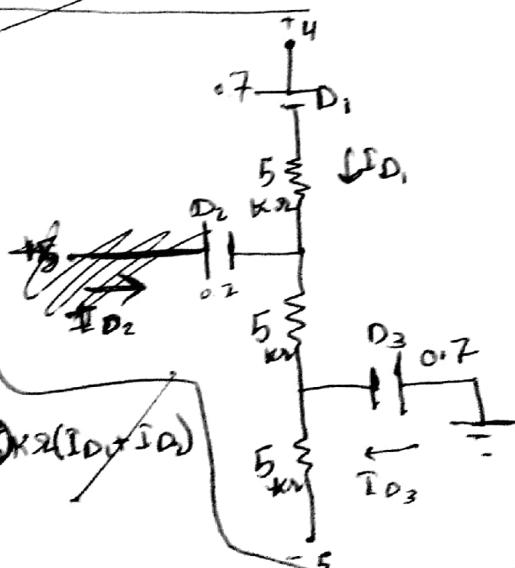
$$-4 + 0.7 + I_{D1}(5k\Omega) + 10k\Omega(I_{D2} + I_{D3}) = 0$$



2.5

loop ②

$$-5 + 0.7 + 10k\Omega(I_{D1} + I_{D2}) = 0$$

$$10k\Omega(I_{D1} + I_{D2}) = 9.3$$

loop ③

$$1 + I_{D1}(5k\Omega) = 0$$

$$I_{D1} = \frac{1}{5k\Omega} = -0.2mA \quad (\text{incorrect})$$


Assumption incorrect
so D_3 is

$$-0.2 + I_{D2} = 0.93$$

$$I_{D2} = 1.13mA \quad (\text{correct})$$

Question 3

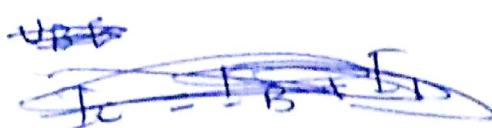a) consider the circuit shown where $\beta = 120$, and $V_{BEON} = 0.7V$. Calculate R_C , and I_C .



~~NEET~~


$$I_C = \frac{\beta}{\beta + 1} * I_E$$

$$I_C = 1.84 \text{ mA}$$

$$V_{BE} + I_E R_E - 10 = 0$$

$$5K I_E = 10 - 0.7$$

$$I_E = 1.86 \text{ mA}$$

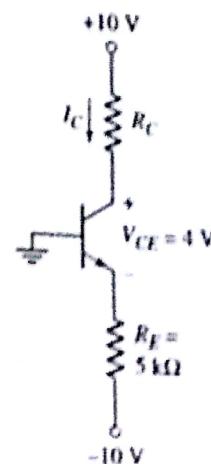

$$-10 + I_C R_C + 4 + I_E R_E - 10 = 0$$

$$1.84 \text{ mA} * R_C + 1.86 \text{ mA} * 5K = 10$$

$$R_C = \frac{6.7}{1.84 \text{ mA}} = 3641.21 \Omega$$

3.

b) consider the circuit shown where $\beta = 120$, and $V_{BEON} = 0.7V$. Calculate V_C , and I_B .

~~$I_E = I_C + I_B$~~

$$\beta B \cdot R_B + V_{BE} + I_E R_E = V_C \neq 0$$

$$20K I_B + 0.7 + 2K I_E = 0$$

$$3 + I_E 10K + V_{CE} + I_E R_E = 0$$


$$20K I_B + 0.7 + 2K(\beta + 1) I_B = 0$$

~~$20K (\beta + 1) I_B = -0.7$~~

$$20K I_B + 2K I_B = -0.7$$




$$26K I_B = -0.7$$

~~$I_B = 374.28 \text{ A}$~~

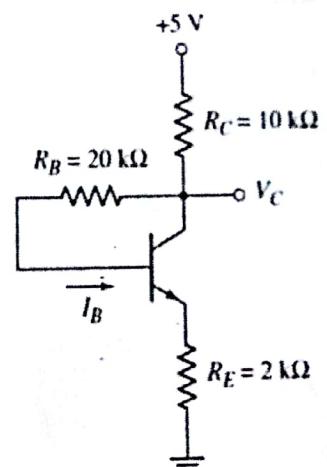

use the event

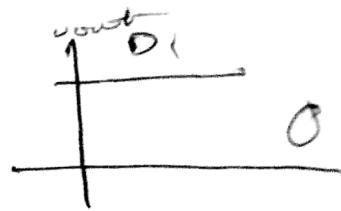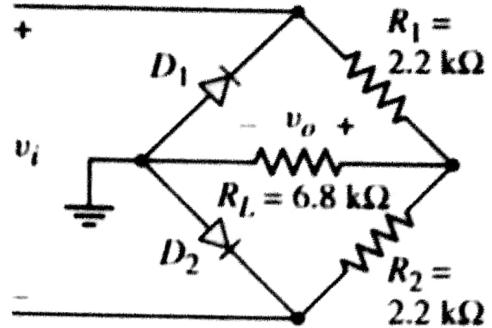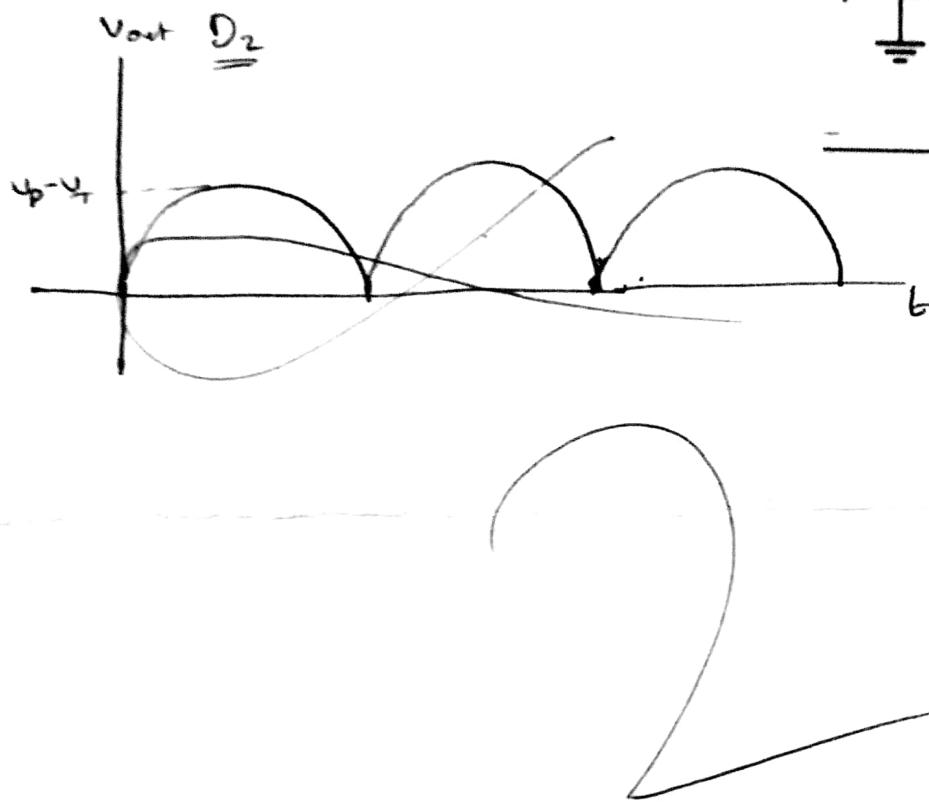package , Sketch v_o versus
 v_i is a sine wave of 10
assume $V_T = 0.7V$



Find

any circuit simulation package to

$$I_B = ?$$


$$I_C = ?$$

$$\text{V}_{CE} = ?$$

$$I_B = 0.01 \times$$

$$I_C = 0.01, 901 \mu A$$

$$V_{CE} = 3.36 V$$

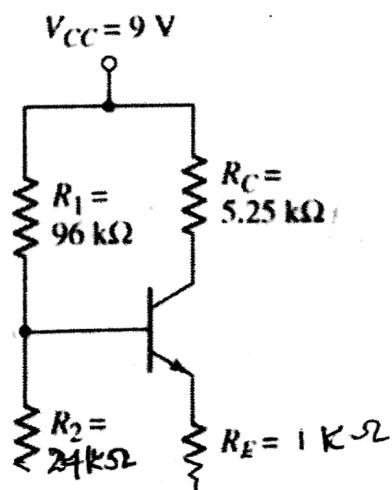

2