

Electronics 1

Dr. Raad Alzubi

POWER UNIT

By: Salah Hamayel
Spring 16


Types of materials: - (depends on electric conductivity not heat)

- ① Conductors e.g. Copper
- ② Insulators e.g. wood
- ③ Semiconductors e.g. Silicon (Si), Germanium (Ge)

* Valence electrons: (الإلكترونات الخارجة)

the electron on the outer most shell and the number of these electrons determine the chemical activity of the material

"يا كاشي أيضاً قديونك لادع مني ابدا"

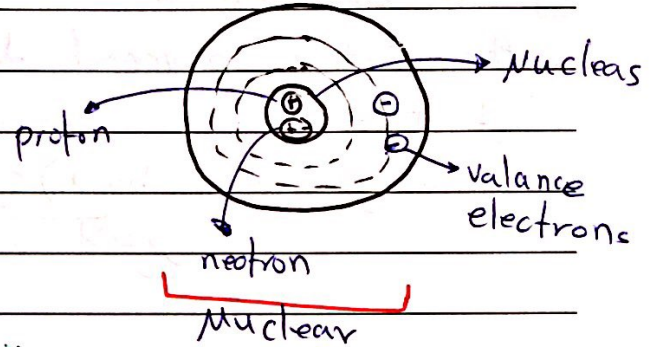

* sample of periodic table

III	IV	V
B	C	
Al	Si	P → phosphorus
G	Ge	As → Arsenic


Annotations above the table: '3 valance' points to III, '4 valance' points to IV, and '5 valance electrons' points to V.

- to make current to flow we have :-

- ① there should be free electrons to move.
- ② Force to move the electron "Electric Field".

[A] Conductor :-

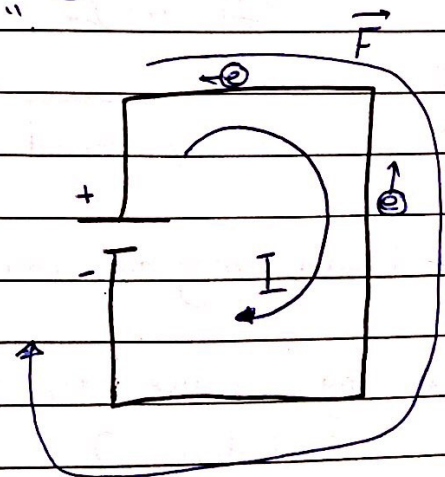- Contain free electron
- if we applied electric field to the material then the valance electrons will move, " " and the current will flow, " note that the current is flowing on the opposite direction of electron movement "



B Insulators:-


- if we appl. ind electric field to the material then the valance electrons will not move, so no current will flow.

C Semi conductors:-

- the electrons movement depends on temp.


at $T=0$ kelven

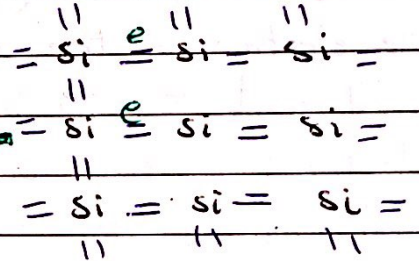ترتبط بروابط تساهمية (covalent bonds) التي تتشكل بين الالكترونات المتجاورة




at $T > 0$ kelven

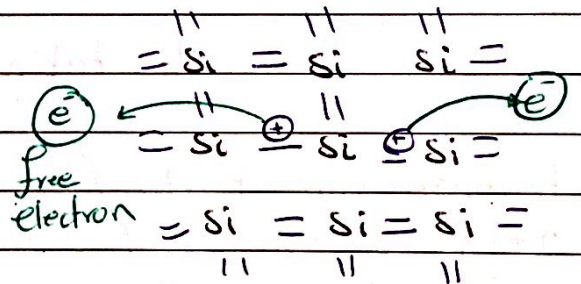* we name the places which the electron leave as "holes" which have a positive charge.



*** energy bands**

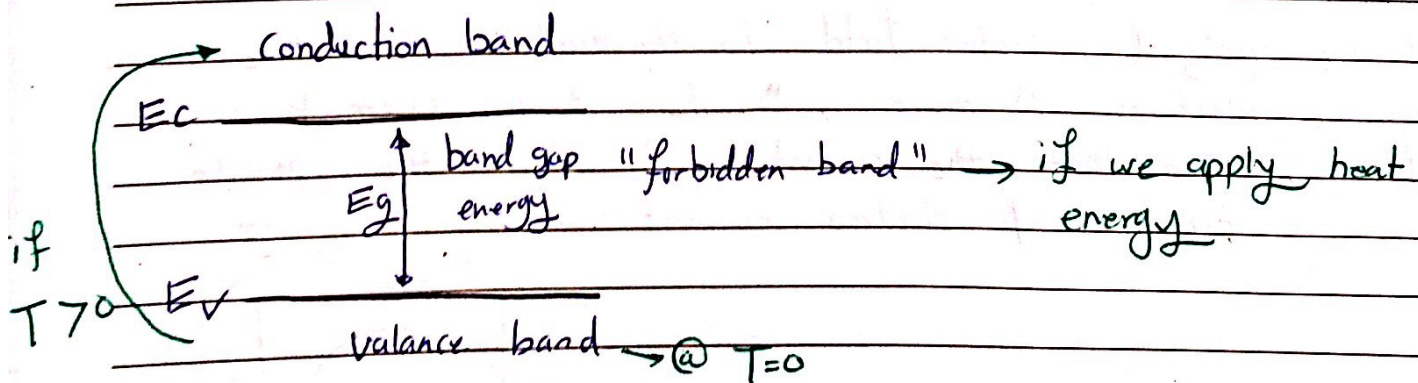

* Diodes may not run will at low/high temperatures.

* why we use the semi-conductors if we can use the conductors ??

Concentration : عدد الإلكترونات الحرة لكل ذرة، صيغة مكتوبة

Semiconductors

Types of semiconductors :-

① Intrinsic semiconductor (pure) e.g. Si, Ge

② extrinsic semiconductor (doped) e.g. pure s.c + impurity
Si + As

A - intrinsic semiconductor (pure silicon or Ge)

- at $T=0 \rightarrow 0$ carriers (0 free electrons, 0 free holes)

at $T > 0$ * free electrons = * free holes

$$n_i = \beta T^{\frac{3}{2}} e^{\left(\frac{-E_g}{2kT}\right)}$$

concentration of free electrons
or free holes since it's equal
(* electrons/cm³)

n_i : intrinsic carrier concentration, T : temp in kelvin (K)

E_g : bandgap energy (eV), k : Boltzmann's constant ($86 \times 10^{-6} \frac{eV}{K}$)

β : coefficient related to the type of semiconductor.

B - extrinsic semiconductors (doped semiconductors)

- they are materials containing impurity atoms

* types of extrinsic semiconductors are on the next page 😊

4/2/2015


Dr. Ra'ad AL-Zoabi

wednesday

① donor impurity (e.g phosphors)

↳ 5 valance electrons

$T > 0K$

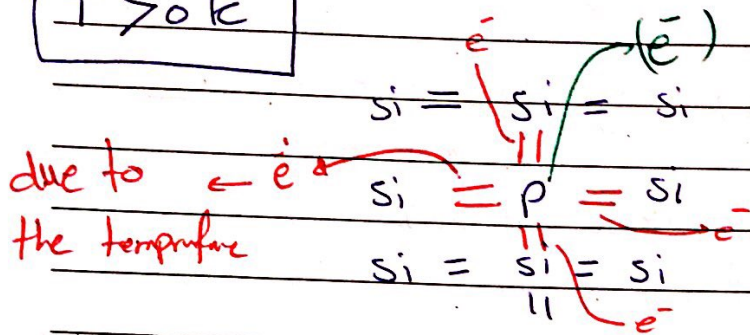


* there would be a free electrons ^{n_f} due to increasing the (T), so it would make holes behind it, after doping (p), an extra (e) we will have.

Concentration of free electrons $>$ concentration of free holes
 $n_0 > p_0$

⇒ n-type semiconductor material
(majority carries are electrons)

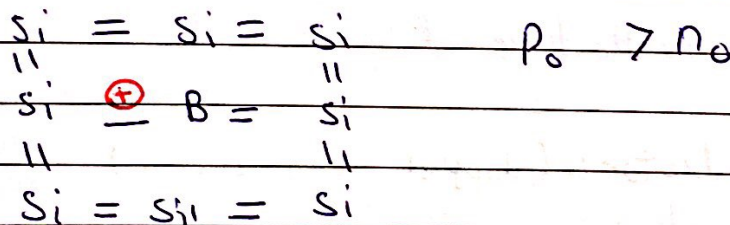② acceptor impurity (e.g, Boron ⇒ 3 valance electrons)



⇒ p-type semiconductor material
(majority carries are protons)

* to control the concentration of free electrons and holes we use the doping process.

* $n_0 p_0 = n_i^2$ ⇒ Always holds

$n_i \Rightarrow$ تركيز الإلكترونات في لمادة متساوية في كماداتها
 n_i

$N_d \rightarrow$ تركيز الإلكترونات في المادة المضافة
 P

$n_0 \Rightarrow$ تركيز الإلكترونات للمادة المضافة N_d + المادة الأصلية n_i

* if the donor concentration (N_d) is much greater than the intrinsic concentration, ($N_d \gg n_i$), then

$$n_0 \approx N_d \Rightarrow p_0 = \frac{n_i^2}{N_d}$$

* if the acceptor concentration (N_a) is much greater than the intrinsic concentration, then ($N_a \gg n_i$)

$$p_0 \approx N_a \Rightarrow n_0 = \frac{n_i^2}{N_a}$$

* Concentration of electrons or holes / cm^3

Drift and Diffusion currents:-

The two basic processes that cause the carriers to move are:-

1] Drift process: which is the movement caused by electric field.

2] Diffusion process: " " " " " by variations in the concentrations (due to non-homogeneous doping)


Drift current density:-

1] n-type

the minus sign indicates that the electron movement is opposite to electric field

$$\vec{V}_{dn} = -\mu_n \vec{E}$$

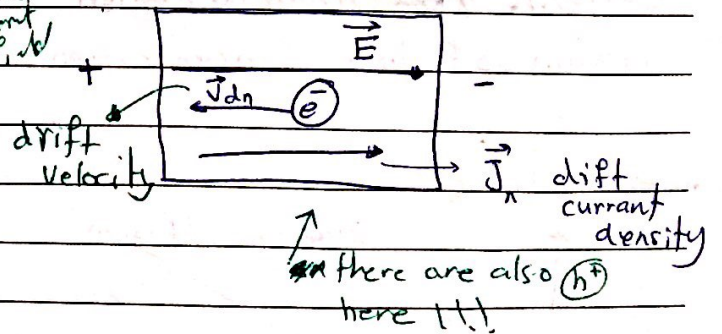electron mobility ($\text{cm}^2/\text{V.s}$)
 constant



$$\vec{J}_n = -en_0 \vec{V}_{dn} \Rightarrow \vec{J}_n = -en_0 (-\mu_n \vec{E})$$

$$\vec{J}_n = +en_0 \mu_n \vec{E}$$

$e = 1.6 \times 10^{-19}$ (electron charge)

$$\vec{J} \equiv (\text{A}/\text{cm}^2)$$


$$n_0 = n_i + N_d$$

$$p_0 = p_i + N_a$$

2] P-type

$$\vec{V}_{dp} = + \mu_p \vec{E}$$

mobility of holes.

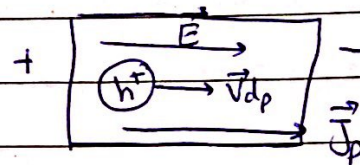

↑ there is e^- also
On this type!!

$$\vec{J}_p = +e p_0 \vec{V}_{dp} = +e p_0 \mu_p \vec{E}$$

* Total drift current in any material :-

$$\vec{J}_{total} = e n_0 \mu_n \vec{E} + e p_0 \mu_p \vec{E}$$

$$\vec{J} = (e n_0 \mu_n + e p_0 \mu_p) \vec{E}$$


$$\vec{J} = \underbrace{\sigma}_{\text{conductivity } (\frac{1}{\Omega \cdot \text{cm}})} \vec{E} \Rightarrow \vec{J} = \frac{1}{\underbrace{\rho}_{\text{resistivity } (\Omega \cdot \text{cm})}} \vec{E}$$

* Solve the example on the book *

B] Diffusion current density

Current flow from a region of high concentration to a region of low concentration

n-type

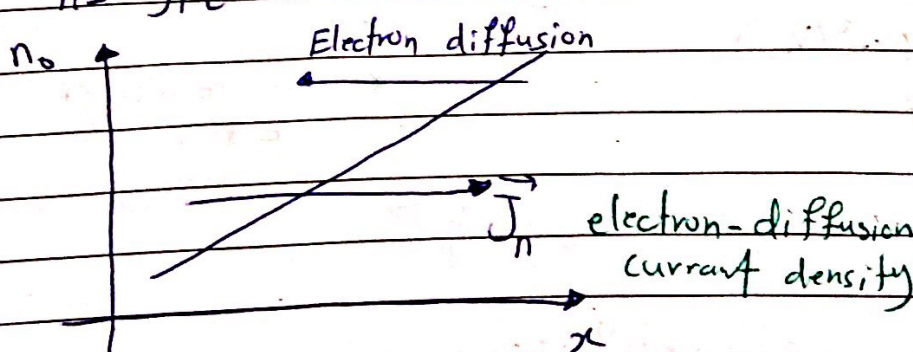


$$\vec{J}_n = e D_n \frac{dn_0}{dx}$$

electron diffusion coefficient (cm^2/sec)

Sunday

Revision:-

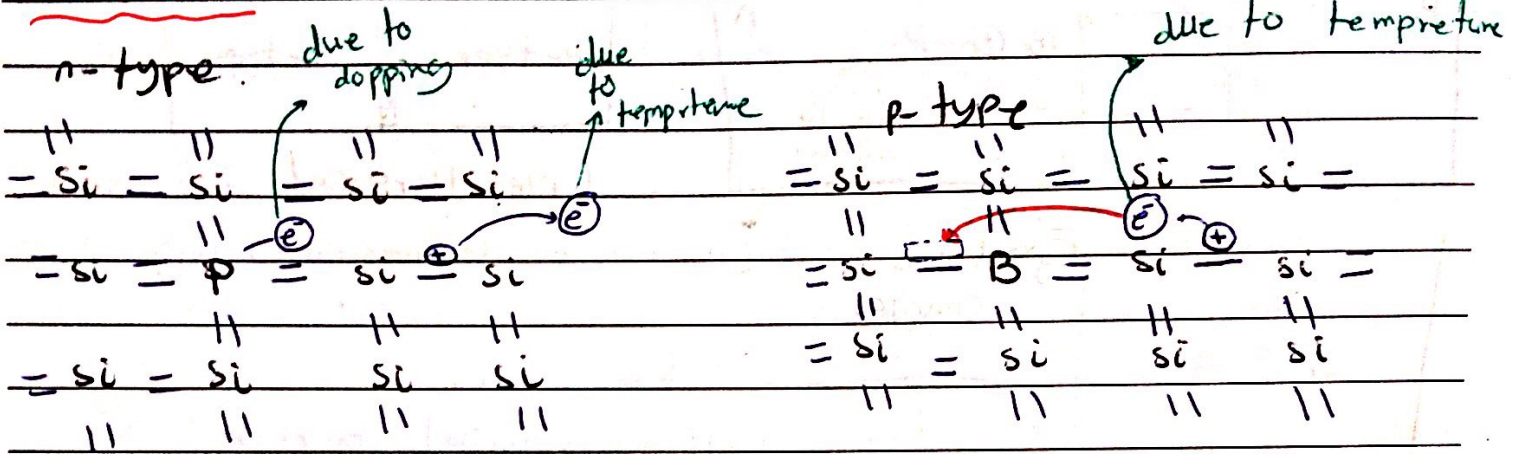

* e⁻ > * holes

* holes > * electrons


على الكبريت الحر الساخن ارتفاع درجة الحرارة
 على مكان الزاوية للفقوة من الزاوية (B) مع (Si)

*Continue to diffusion current:-

P-type

hole diffusion coefficient

$$\vec{J}_p = -e D_p \frac{dp_0}{dx}$$

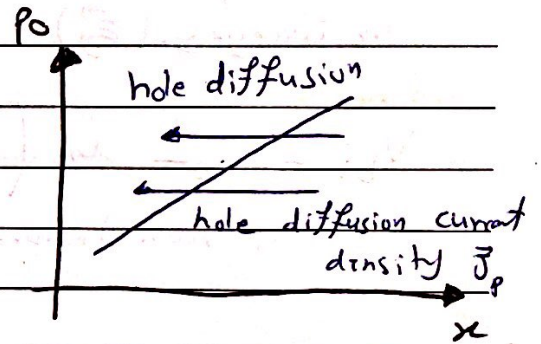


$$\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = \frac{kT}{e} = 0.026V \text{ (at room } T \text{ "300 K")}$$

(Einstein relation)

Thermal Voltage

* Drift and diffusion current are related through (Einstein relation)

* The pn junction :

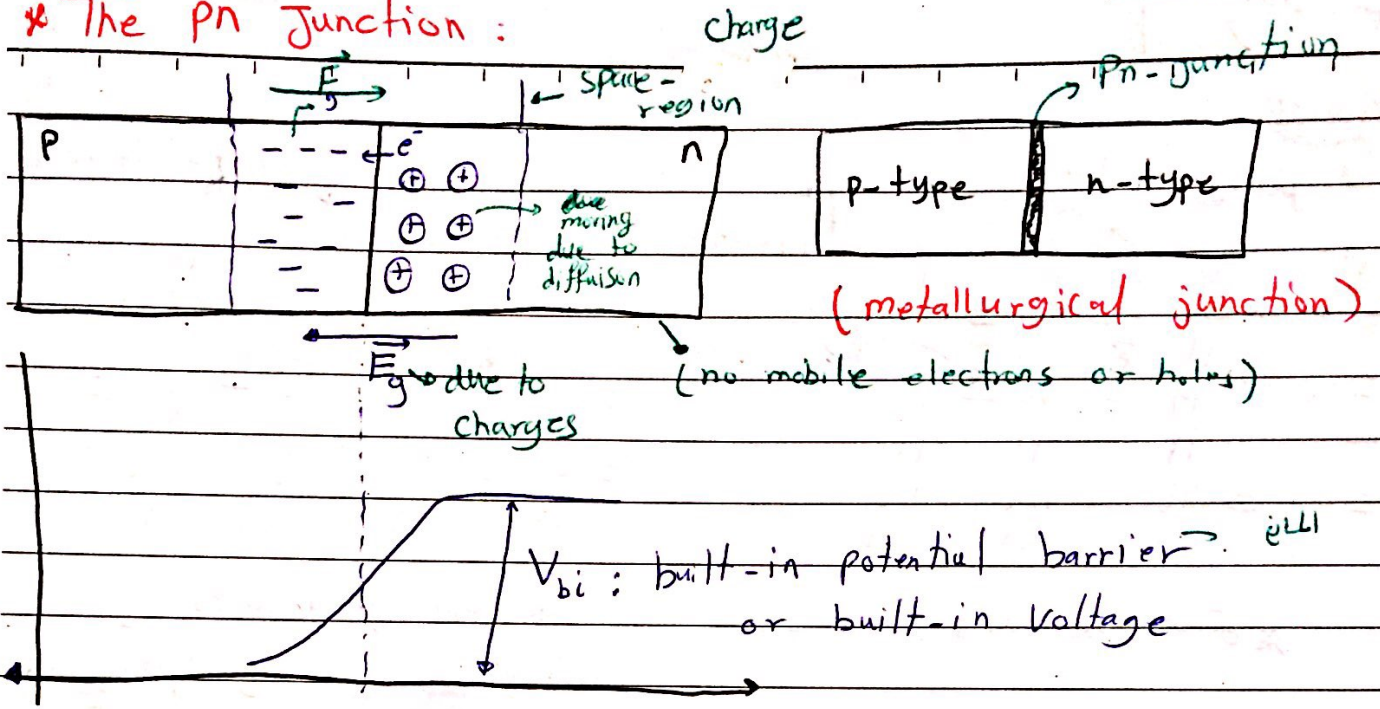

* the electrons and holes will stop moving when the diffusion force equal to the force due to electric field generated from the charges. (E_g)


$$V_{bi} = \frac{KT}{e} \ln \left(\frac{N_a N_d}{n_i^2} \right) = V_T \ln \left(\frac{N_a N_d}{n_i^2} \right) \approx 0.026V$$

at room temperature

Note:- Thermal equilibrium occurs when the force produced by the electric field and the force produced by the densities gradient exactly balance.


* Reverse-biased pn junction :-

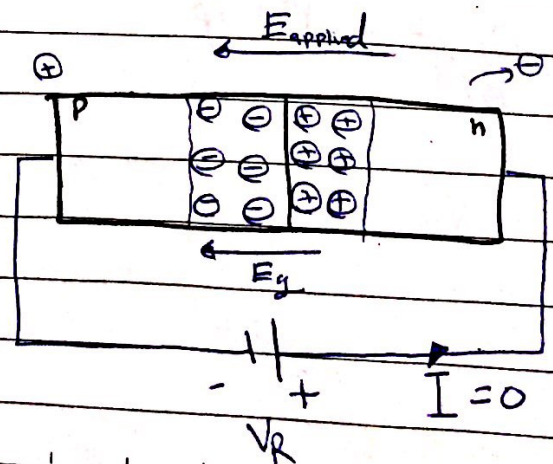* Since $E_{applied}$ will help the E_g to Resist moving charges, so no current will move here



* E_g and $E_{applied}$ in the same direction

2/2/2016 | Dr. Raed AL-Zabi
Tuesday | pn-junction

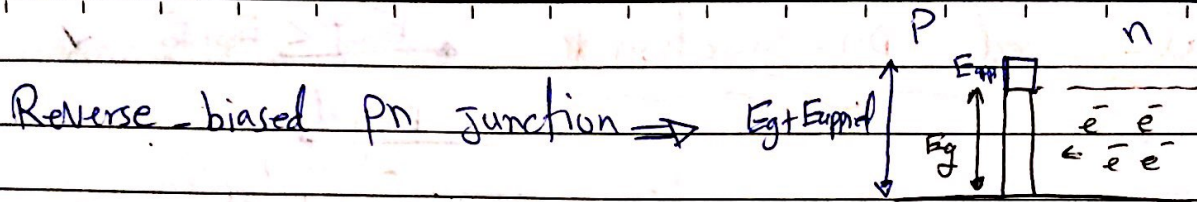

* junction capacitance or depletion layer " $C_j = C_{j0} \left(1 + \frac{V_R}{V_{bi}}\right)^{-1/2}$ "
junction capacitance at $V_R = 0$

* So, the pn-junction can be used as variable capacitor controlled by V_R (reverse-biased voltage source)


* Junctions fabricated specifically for this purpose are called Varactor diodes

* The voltages in the circuits that contain diodes cannot change at zero-time, due to junction capacitance "since if we change it in zero-time we going to have infinite current"

* If V_R is increased to a very high value, the Electric field ($E_{applied}$) will increase also. At some point (breakdown point) will occur and a reverse bias current will be generated.

* Forward-biased pn-junction *

$E_{net} < E_{app} + E_g$

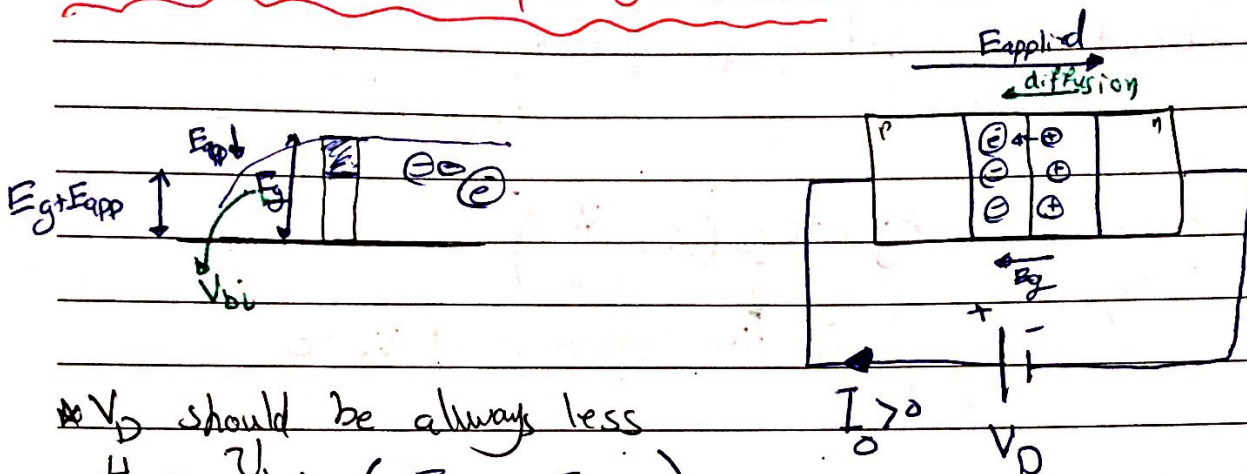

V_D should be always less than V_{bi} ($E_g > E_{app}$)

$I_D > 0$

electrons

* When the E_{app} reverse E_g , so the electrons will continue to move from $n \rightarrow p$, which make current to flow from $p \rightarrow n$ due to diffusion

* $I_D = I_s \left[e^{\frac{V_D}{nV_T}} - 1 \right]$


reverse-bias saturation current ($10^{-15} - 10^{-13} A$)

V_T : thermal voltage ($V_T = 0.026 V$ at room temperature 300K)

n : emission coefficient or ideality factor ($1 \leq n \leq 2$)

* V_{bi} فرق الجهد اللامي لكل V_{bi} نقل وبالتالي يجعل الإلكترونات تتحرك


this current could burn the junction

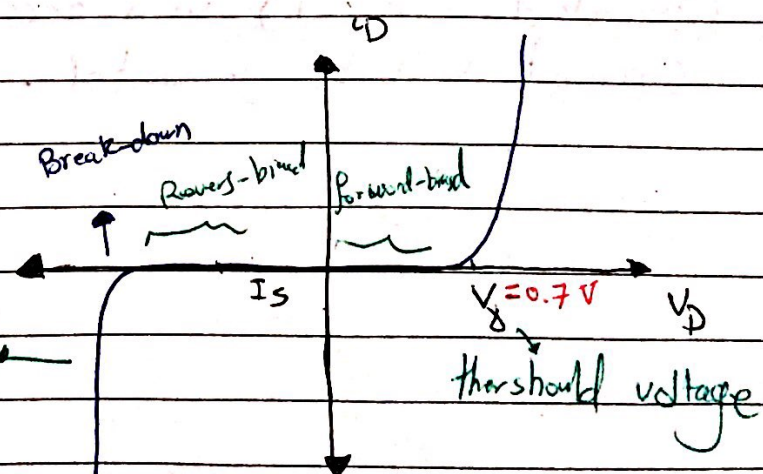

Example:

if $V_s = -3V$

Reverse-bias region

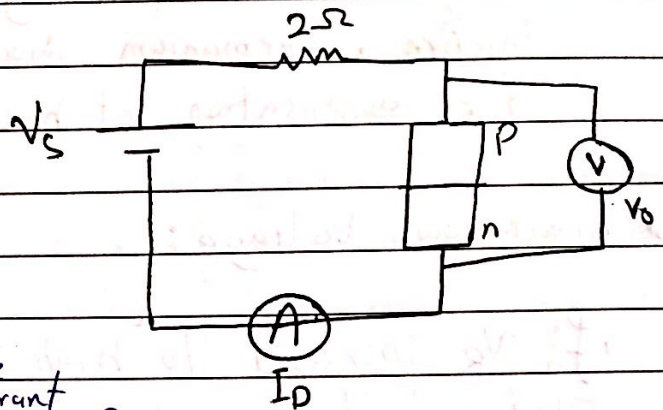

$I_D = 0$, $V_D = -3V$ → Since no current flow through R

if $V_s = 0V$

$I_D = 0$, $V_D = 0$

if $V_s = 0.5V$

$I_D = 0$, $V_D = 0.5V$




if $V_s = 0.9V$

$V_D = 0.7V$, $I_D = 0.1A$ → $-0.9 + 2I_D + 0.7 = 0$
 always on p-n junction

KVL

* pn junction Diode :-

* Temperature effect

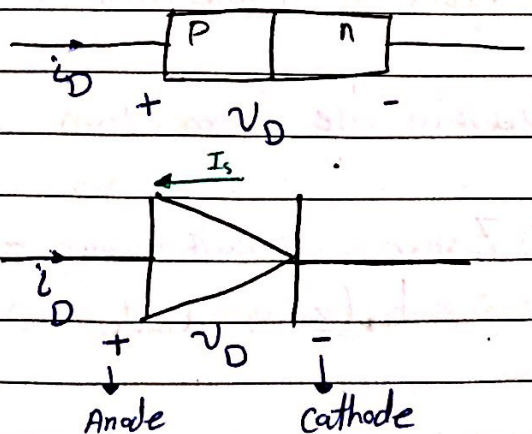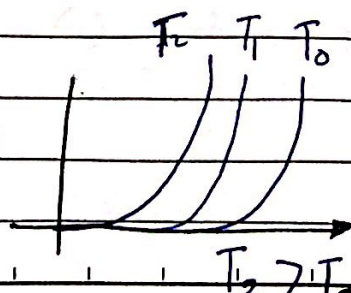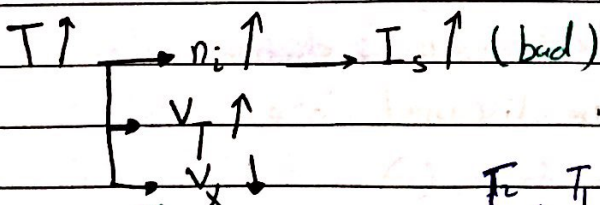


Note: In germanium, n_i is large, so large value of I_s .
Therefore, germanium diodes are highly impractical for application at high temperature.

* breakdown voltage:

if V_R increased to a high value, then the generated electric field may become large enough such that covalent bonds are broken and electrons and holes are created.

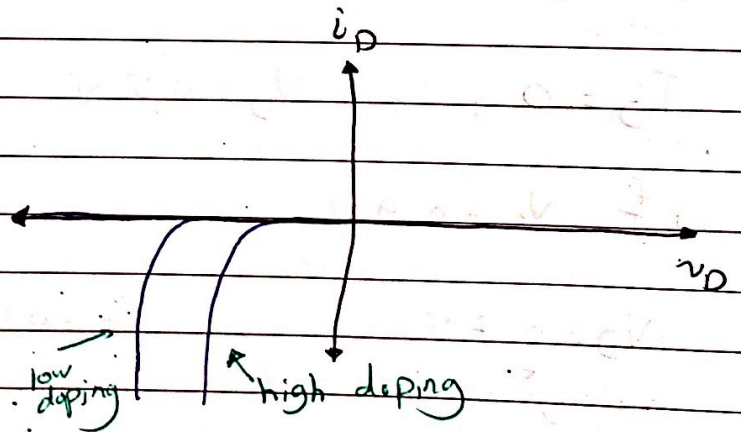then a large reverse bias current will flow and this current may dissipate a power on the diode which may damage the diode.





* types of breakdown :-

① avalanche breakdown \rightarrow leads to damaging the diode
(due to accidents of electrons)

② Zener breakdown \rightarrow will be discussed later.


\rightarrow (Zener diode will not be damaged)

14/2/2016 | Dr. Ra'ed Al-Zoabi
 Sunday | * switching transient :-

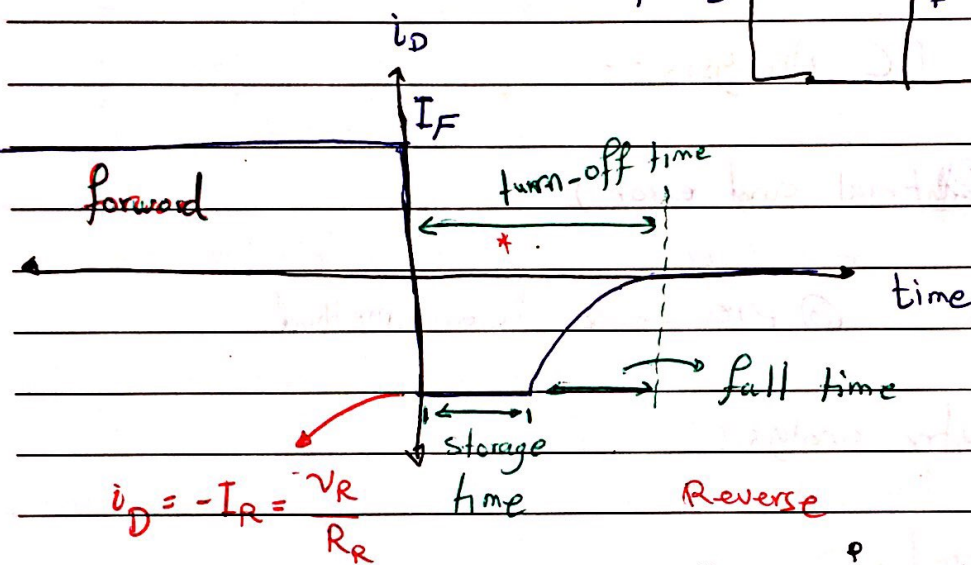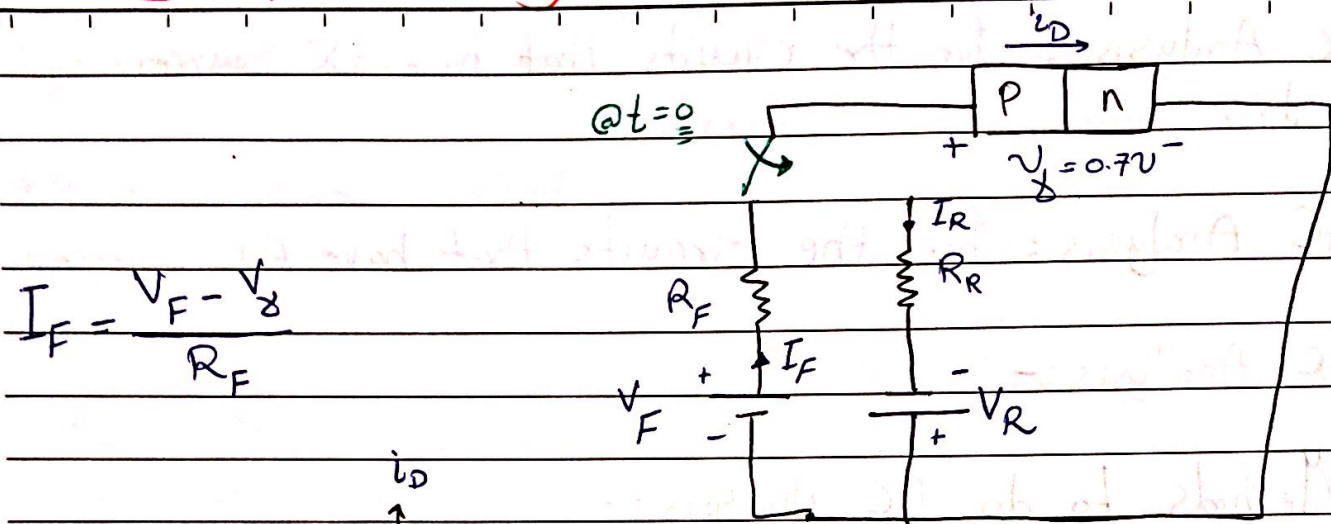

→ note that the current on the diode changed instantaneously not the voltage!!

concentration of minority carriers

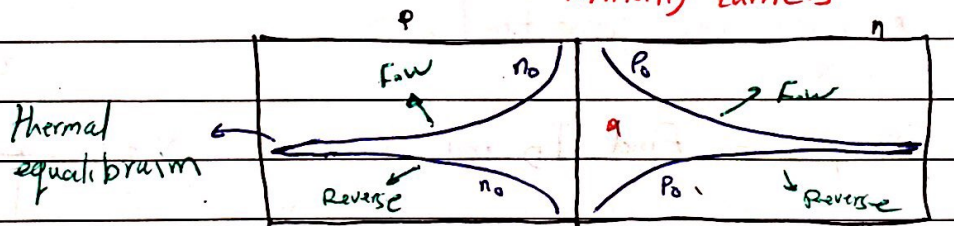

⇒ switching speed of diodes & transistors in digital circuits affects the speed of computer.

* Analysis of Diodes circuits:-

① DC Analysis: for the circuits that have DC Sources and/or large AC sources:

② AC Analysis: for the circuits that have ^{small} AC sources.

* DC Analysis:-

* Methods to do DC Analysis:-

① Iteration (Trial and error)


② graphical method ③ piece-wise linear method

④ Computer analysis

* Iteration method :-

Example:- Find I_D and V_D

$V_s = 5V$

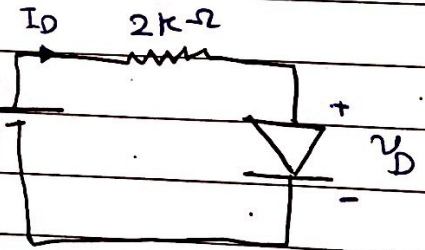

Sol: we know that $i_D = I_s \left[e^{\frac{V_D}{nV_T}} - 1 \right]$ ①

and Given: $I_s = 10^{-13} A$, $n=1$, $V_T = 0.026 V$

⇒ from the circuit KVL: $-5 + (2 \times 10^3) I_D + V_D = 0$ ②

From equation ① and ② $5 = 10^{-13} \times 2 \times 10^3 \left[e^{\frac{V_D}{0.026}} - 1 \right] + V_D$


⇒ try $V_D = 0.6V \Rightarrow 5 \stackrel{?}{=} 2.7$ wrong solution

⇒ try $V_D = 0.65V \Rightarrow 5 \stackrel{?}{=} 15.1$ wrong solution

⇒ try $V_D = 0.619V \Rightarrow 5 \stackrel{?}{=} 4.99V$ correct solution ✓


$V_D = 0.619 \text{ V}$ so $I_D = 2.19 \text{ mA}$

* using graphical method

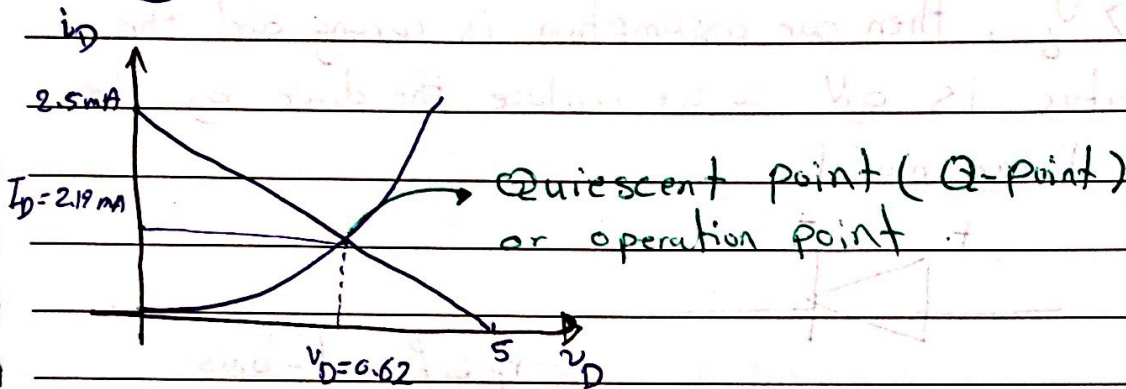

Note: equation $\frac{2}{5}$ is ^{the} called load Line

③ piecewise Linear method :-

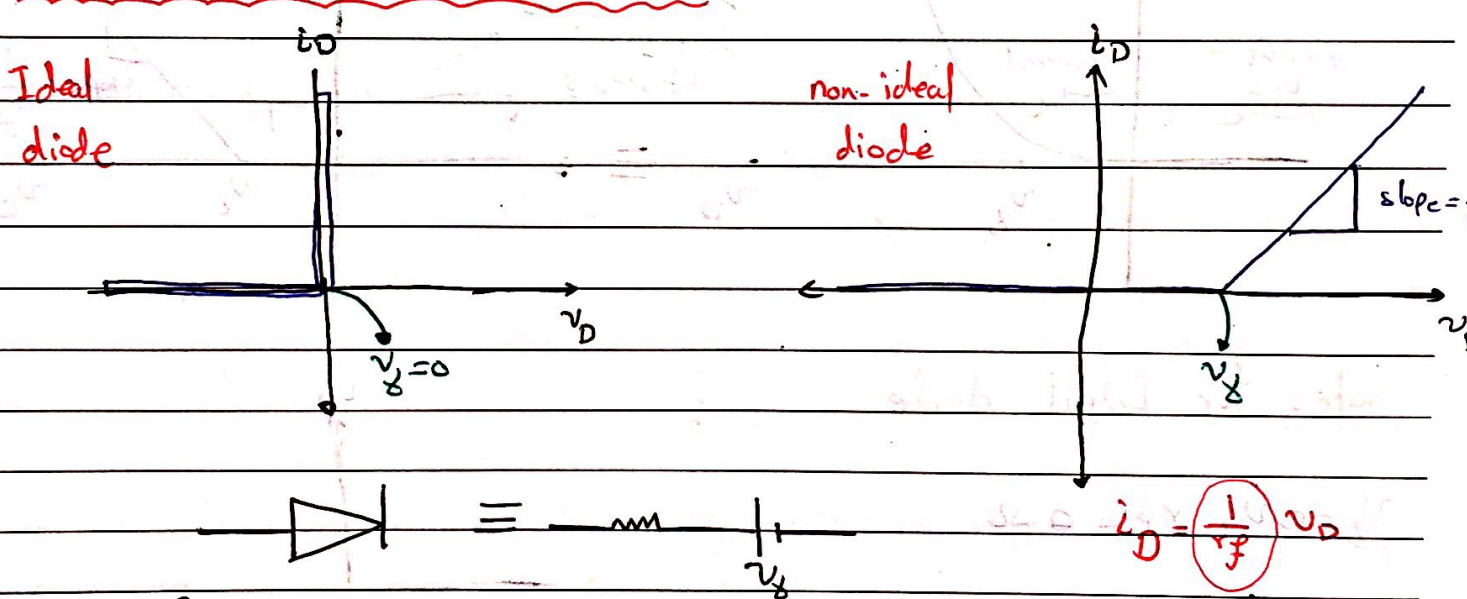

steps of solving :-


step 1: assume that the diode is off (reverse-biased) so replace the diode by open circuit

step 2: find v_D


16/2/2016 | Dr. Raed Al-Zoabi
 Tuesday | continue to steps of solving.

step 3: 1* if $v_D < v_g$, then our assumption is correct and the diode is off, $I_D = 0A$, $v_D =$ the value found on step 2.

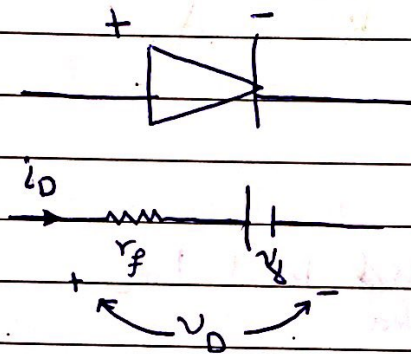2* if $v_D > v_g$, then our assumption is wrong and the diode status is on so we replace the diode by the following linear model.




r_f : forward-bias resistance.

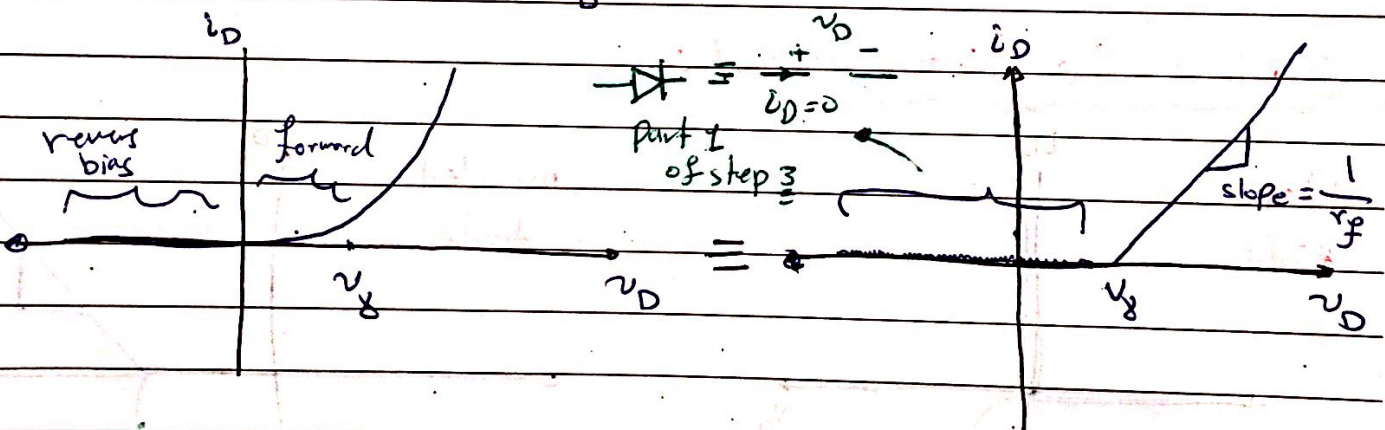

Note: for Ideal diode

$$v_g = 0V, r_f = 0\Omega$$

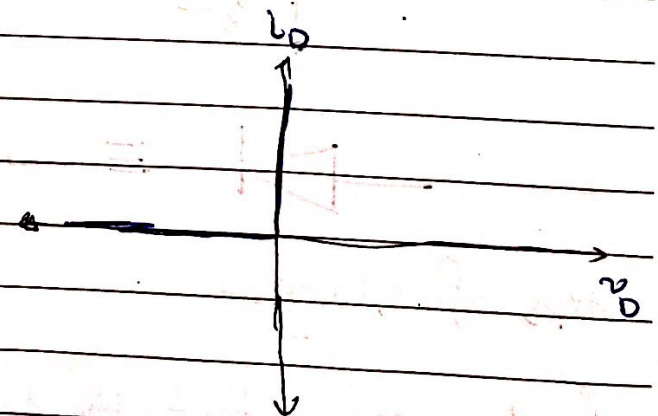
so, the diode is open circuit or short circuit.




Ex: Given, $V_g = 0.6\text{V}$, $r_f = 10\Omega$, find

a) the status of the diode.

b) I_D and v_D , P_D

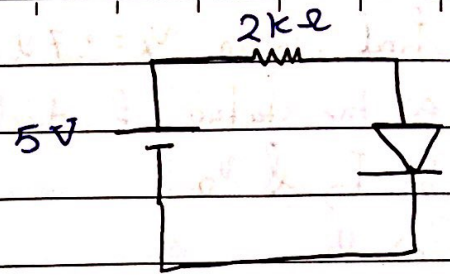


Sol: step 1

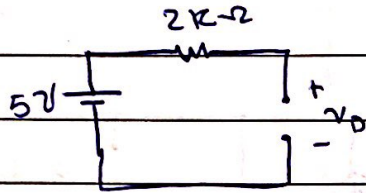

Step 2: find $v_D \Rightarrow v_D = 5\text{V}$

Step 3: check $\Rightarrow v_D < V_g$ No, so wrong assumption!

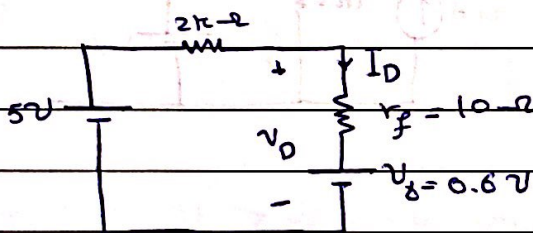\therefore The status of the diode is ON (forward-bias)



find I_D :- KVL: $-5 + 2 \times 10^3 I_D + 10 I_D + 0.6 = 0$

$$I_D = 2.19\text{mA}$$

$$\Rightarrow v_D = 0.6 + 10 * I_D \Rightarrow v_D = 0.622\text{V}$$


$$\Rightarrow P_D = I_D v_D = 1.36\text{mW}$$

Ex: find, Given $V_D = 0.7V$, $r_f = 0.2$

a) the status of diode


b) I_D & V_D

c) V_o

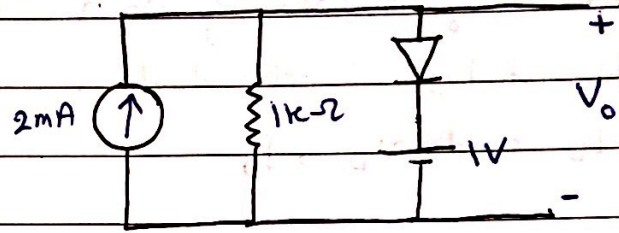

Solution:- step 1:

step 2: $V_D = 2 - 1 = 1V$

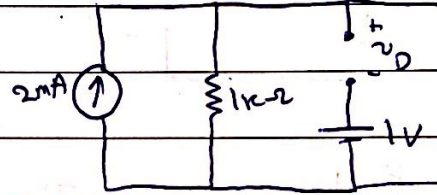


step 3: $V_D < V_D \Rightarrow$ No (wrong assumption)

so a) the diode is ON


$$\therefore V_D = 0.7V$$

$$I_D = 2mA - \frac{1.7}{1 \times 10^3} = 0.3mA$$


$$V_o = 1.7V$$

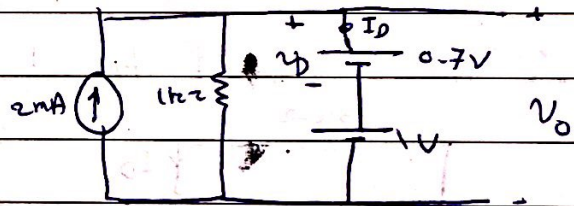

Ex: $V_f = 0.6V$, $r_f = 0\Omega$

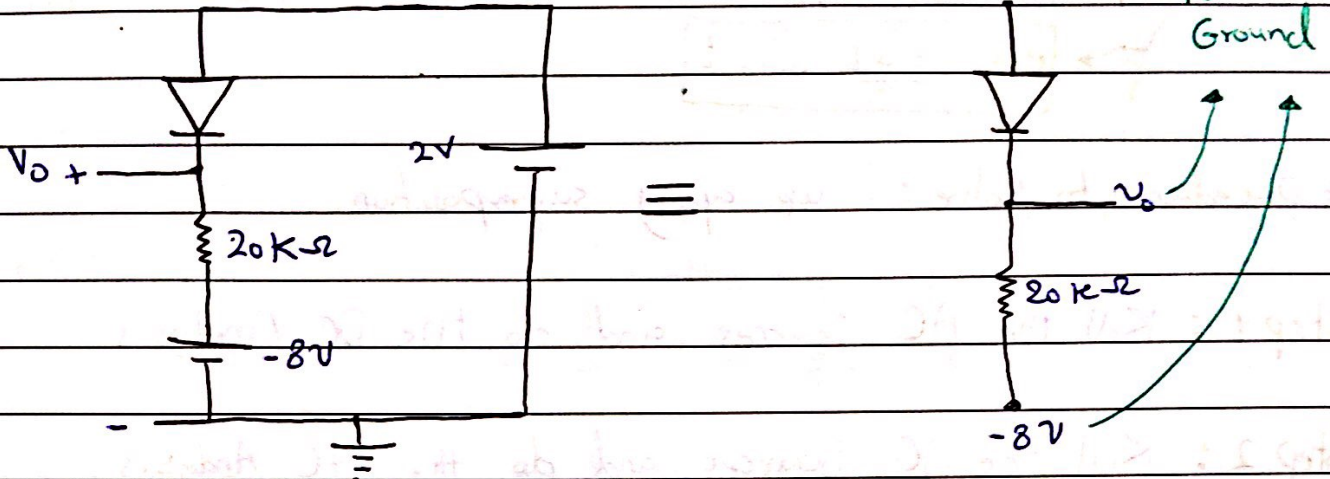

Sol: step 1:

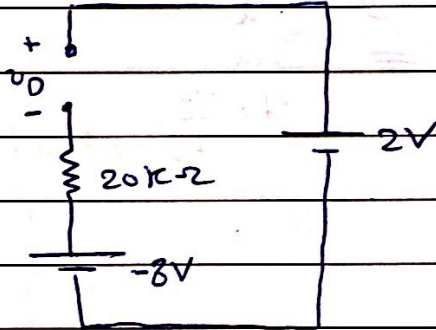

step 2: $2 - V_D + 2 = 0$

$$V_D = 1.0V$$

step 3: $V_D > V_f \rightarrow$ the diode is ON


$$\Rightarrow -V_D - 0.6 + 2 = 0$$

$$V_D = 1.4V$$

$$\Rightarrow 0.6 + 20I_D - 8 - 2 = 0$$

$$* I_D = \frac{9.4}{20} = 0.47mA$$

$$* V_D = 0.6V$$

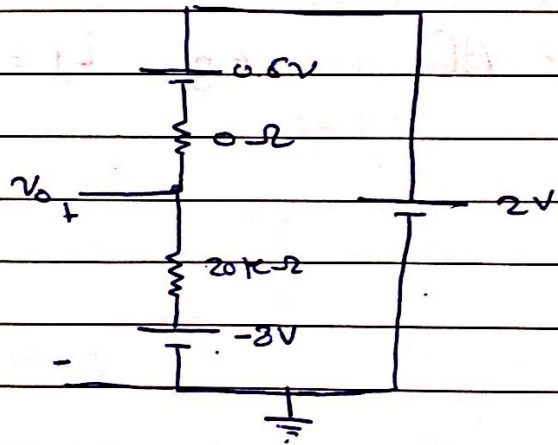

18/2/2016 | Dr. Ra'ed AL-Zoubi
Thursday | * AC Analysis

* We apply the AC Analysis if the circuit has DC sources and small AC sources

↳ e.g. $0.01 \sin \omega t$

* procedure to solve: we apply superposition

step 1: Kill the AC sources and do the DC Analysis.

step 2: Kill the DC sources and do the AC Analysis.

⇒ replace the diode by r_d



≡ r_d

$r_d = \frac{V_T}{I_D}$ → found on step 1

Note: -

I_D : DC e.g., $I_D = 5A$


i_D : AC + DC e.g., $i_D = 5 + 4 \sin \omega t$ A

i_d : AC e.g., $i_d = 3 \cos \omega t$ A

r_d (for small ac sources we replace the diode by Resistor which equal $r_d = \frac{v_T}{I_D \rightarrow DC}$)


big letters sine (AC+DC) sources

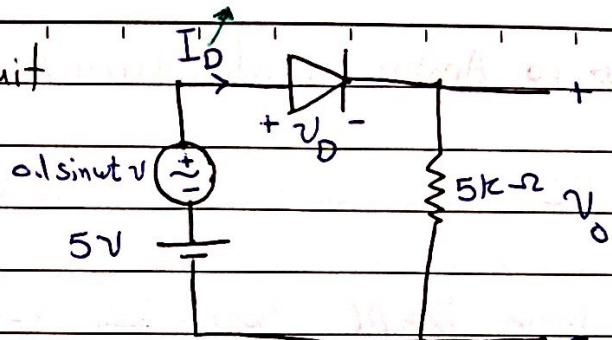Ex: find v_o in the following circuit
given $v_g = 0.6V$, $v_T = 0.026V$



Solution:


* step 1:

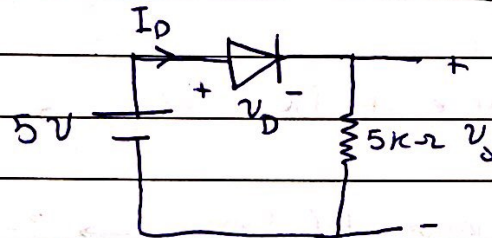

DC circuit

⇒ 3-step solution

step A:

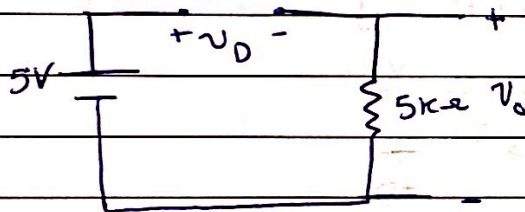


step B:

$$v_D = 5V$$

step C:

$$v_D > v_g \Rightarrow \text{yes}$$

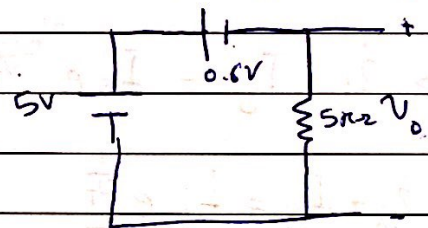

$$KVL: -5 + 0.6 + 5I_D = 0$$


$$I_D = 0.88 \text{ mA}$$

$$v_o = 5I_D = 4.4 \text{ V}$$

step 2: $r_d = \frac{v_T}{I_D} = \frac{0.026}{0.88 \text{ mA}} = 0.0295 \text{ k}\Omega$

$$KVL: -0.1 \sin \omega t + (0.6295 \text{ k}\Omega) i_d + (5 \text{ k}\Omega) i_d = 0$$
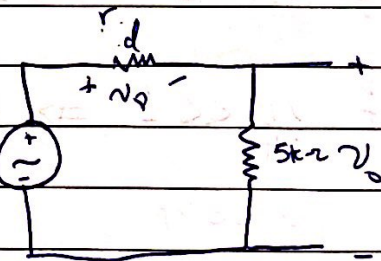
$$i_d = 19.9 \sin \omega t \text{ }\mu\text{A}$$



$$\Rightarrow v_o = 5 i_d = 0.0995 \sin \omega t \text{ V}$$

finally add the two voltages (from AC and DC): $v_o = 4.4 + 0.0995 \sin \omega t \text{ V}$

$$i_D = I_D + i_d = 0.88 \text{ mA} + 19.9 \sin \omega t \text{ }\mu\text{A}$$

$$v_D = V_D + v_d = 0.6 + 0.0295 i_d$$

→ to Analyse diode circuits:

① DC Source only → 3-step solution

② large AC source ^{only} → 3-step solution

③ small AC source + DC sources → AC analysis

④ DC sources + large AC sources → 3-step solution

* mathematical Analysis :-

$$i_D = I_s \left[e^{\frac{v_D}{nV_T}} - 1 \right] \Rightarrow i_D \approx I_s \left[e^{\frac{v_D}{V_T}} \right] \quad \text{assume } n=1$$

$$\Rightarrow i_D + I_D = I_s e^{\frac{v_D + V_D}{V_T}} \Rightarrow i_D + I_D = I_s e^{\frac{v_D}{V_T}} e^{\frac{V_D}{V_T}}$$

$$\Rightarrow i_D + I_D = I_D e^{\frac{v_D}{V_T}}$$

→ we know from Taylor series: $e^{\theta} = \frac{\theta^0}{0!} + \frac{\theta^1}{1!} + \frac{\theta^2}{2!} + \frac{\theta^3}{3!} + \dots$

$$\text{if } \theta \ll 1 \quad e^{\theta} \approx 1 + \theta$$

$$\text{if } \frac{v_D}{V_T} \ll 1 \Rightarrow e^{\frac{v_D}{V_T}} = 1 + \frac{v_D}{V_T}$$

$v_D \ll V_T$

$$i_D + I_D = I_D \left(1 + \frac{v_D}{V_T} \right) \Rightarrow i_D + I_D = I_D + I_D \frac{v_D}{V_T}$$

$$i_D = \frac{I_D}{V_T} v_D$$

\downarrow
 $\frac{1}{r_d}$

$$\Rightarrow \left\{ \begin{array}{l} \text{Remember } V = R I \\ v_D = \left[\frac{V_T}{I_D} \right] i_D \\ \rightarrow r_d \end{array} \right.$$


21/2/2016

Dr. Ra'ed AL-Zoabi

Sunday

* Some types of Diodes:-

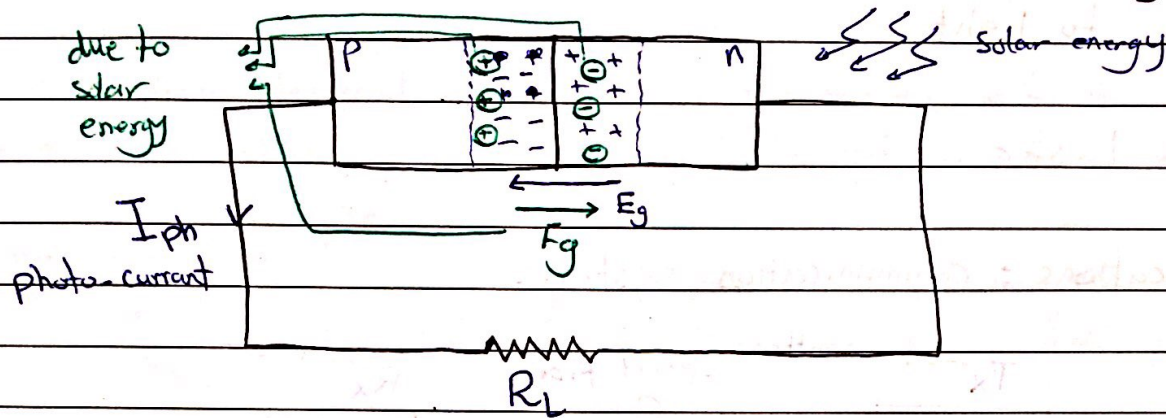1) Solar cell: Converts solar energy to electric energy.




* Made from: Si, GaAs, or III-V compound.

* Applications: 1) Calculator 2) race cars
3) space vehicles & satellites.

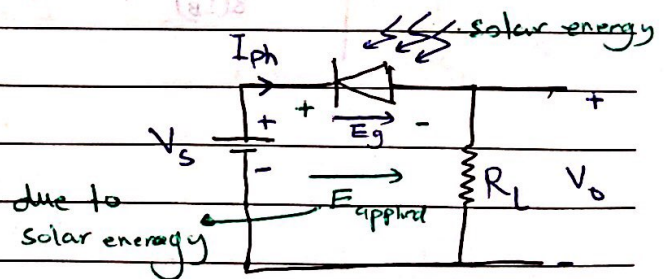2) photo-diode: small solar-cell.

⇒ I_{ph} is small, so it is not sufficient to turn-on a certain load so, we use it for controlling.


⇒ we connect the photo-diode as reverse-bias in the circuit.





3] LED: (Light emitting diode): converts electric energy to light

* e.g: Laser

* applications: communication systems.

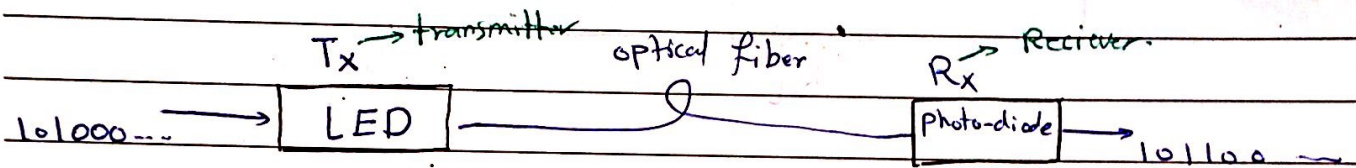

4] Schottky Barrier diode:

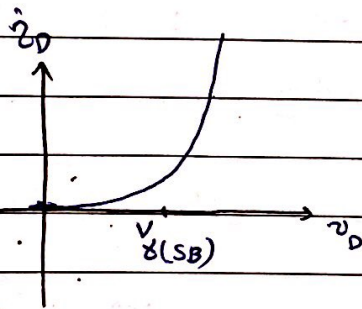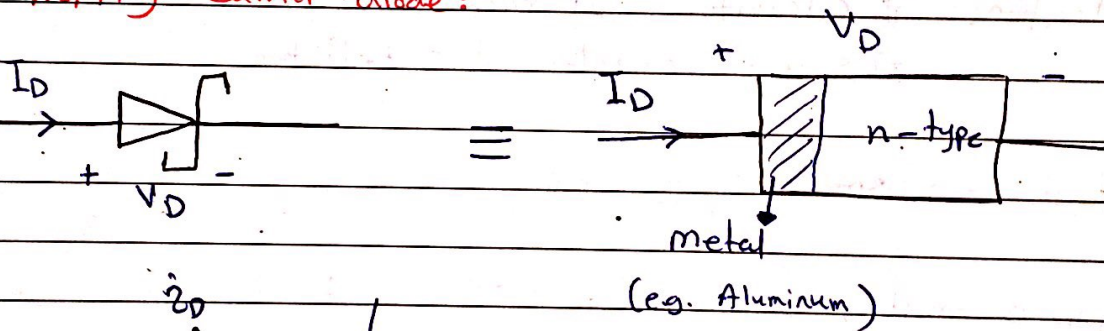

$$\Rightarrow I_s(\text{SB}) > I_s(\text{Pn})$$


Schottky diode
p-n junction diode

$$\Rightarrow V_\gamma(\text{CSB}) < V_\gamma(\text{Pn})$$

\Rightarrow switching time is very small in (SB) ≈ 0 (advantage)


5] Zener diode:

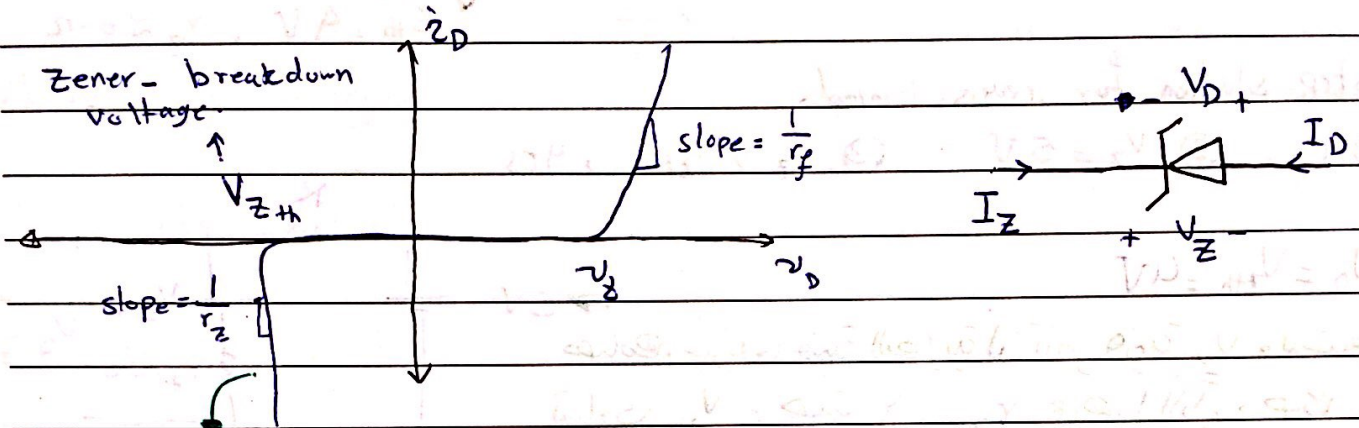It is a diode designed to exploit the advantage of the fixed break-down voltage. So, we can use it to get a reference voltage.




This curve is sharper $* r_f > r_z$, $* r_z$: Very small value than V_Z

* on Forward-bias:

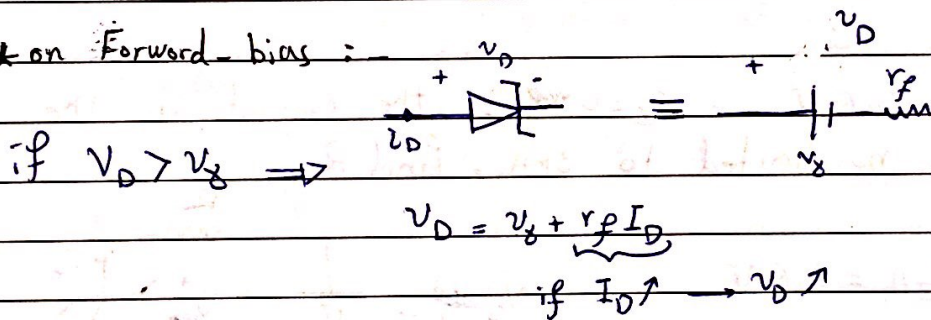

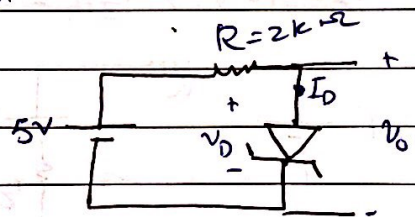
Example: given that $V_g = 0.7V$, $r_f = 10\Omega$



Sol: 3-step solution: ① O.C

② $V_D = 5V$

③ $V_D > V_g$

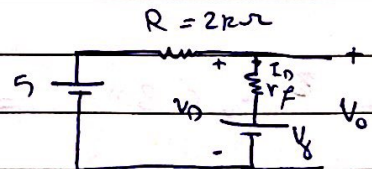

$$V_D = V_g + I_D r_f$$

$$I_D = \frac{5 - 0.7}{2k + 10}$$


Here in the example we will use the current to make it not exceed the power rating.

* on Reverse biased:

Example:-

3-step solution


- ① O.C ② $V_D = -5V$ ③ $V_D < V_Z$, off

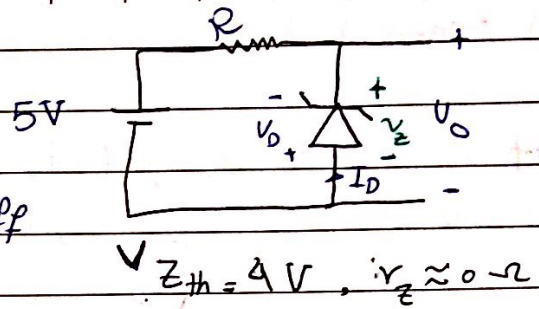

3-step solution for reverse biased.

- ① O.C ② $V_Z = 5V$ ③ $V_Z > V_{Zth}$, YES



$V_D = V_{Zth} = 4V$

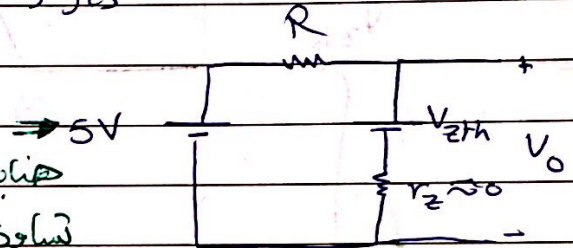

هنا كما غيرنا في قيمة البطارية لأن تنقص قيمة V_D ويستبقى
 تساوياً V_{Zth} ، حيث أن r_Z في هذا التآثر صفر
 صغرى وتقرن قيمتان الصغر ، وهذه أحر أهم
 استنتاجات هذا النوع من الدايودات ، لأننا نعطينا مرجع
 ثابت لفرق الجهد V_D

Ex: given $V_{Zth} = 5.6V$, $r_Z = 0 \Omega$, the current in the diode is to be limited to 3mA , find R

Sol: $V_Z = 10V > V_{Zth} = 5.6V$

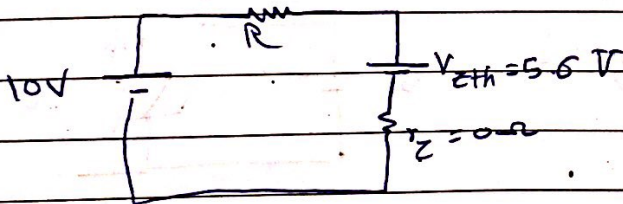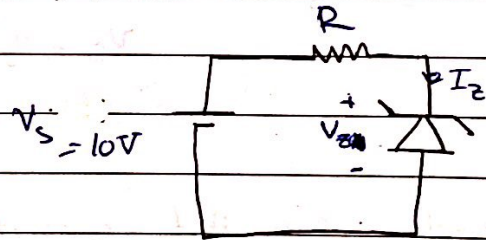

$I_Z < 3mA \Rightarrow \frac{10 - 5.6}{R} < 3mA \Rightarrow R > 1.47 k\Omega$

power on Zener diode = $I_Z V_Z = (3 \times 10^{-3})(5.6) = 16.8 mW$

* The Zener diode must be able to dissipate 16.8 mW of power without being damaged. (note that even we replace the diode by power supply , we did that for mathematical aims , but it doesn't supply power , it is a passive element)

on Jordan the frequency of the power rate : 50Hz and 220 V (rms)
 " Saudi Arabia " " " " " : 60 Hz and 120 V (rms)

***Diodes Circuits:-**

① AC to DC signals converter:

- ↳ rectifier circuit.
- ↳ Voltage regulator circuit.
- ↳ filter circuit.


② Battery charger.

③ Clipper circuit.

④ Clamper circuit.





⑤ logic circuit.

AC-to DC converter:-

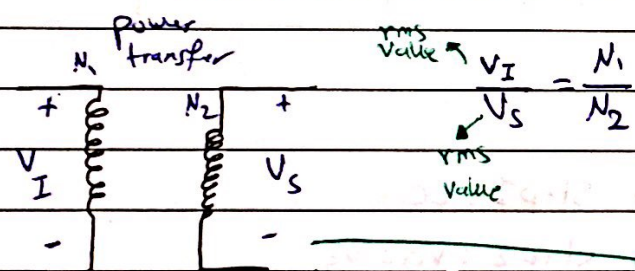

$$V_I(rms) = \frac{V_{mI}}{\sqrt{2}}$$

$$V_S(rms) = \frac{V_{mS}}{\sqrt{2}}$$

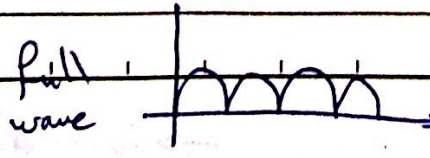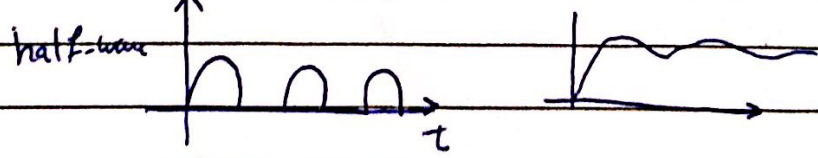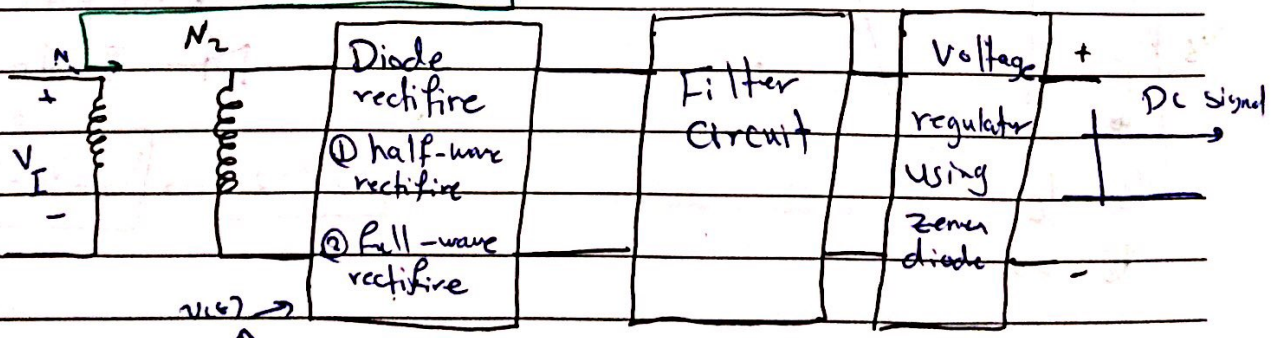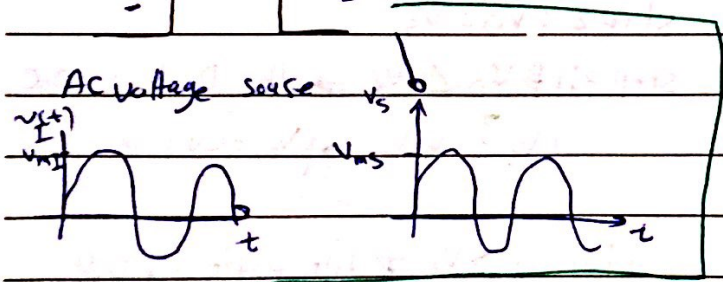

* Rectifier circuits:-


① Half-wave rectifier circuit (H.w) ↗ Half-wave

② Full-wave rectifier circuit (F.w) ↗ Full-wave

↳ AT center-tapped F.w

↳ BI Bridge F.w

* Half-wave rectifier circuit:-

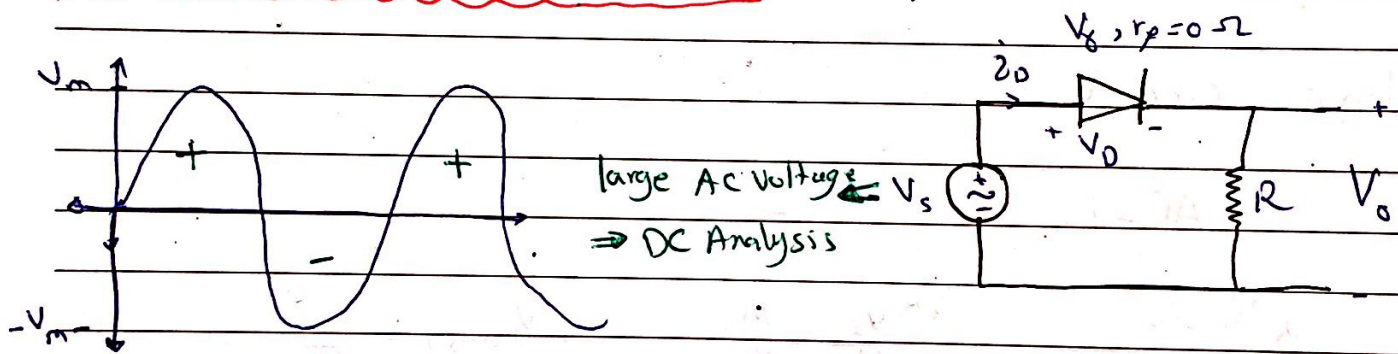

* For the cycle \int^+ \Rightarrow step 1: o.c

step 2: $V_o = V_s$


step 3: if $V_o < V_g \Rightarrow$ the Diode is o.c


$V_s < V_g \Rightarrow V_o = 0V$

if $V_o > V_g \Rightarrow$ the Diode is o.n



$V_s > V_g \Rightarrow V_o = V_s - V_g$

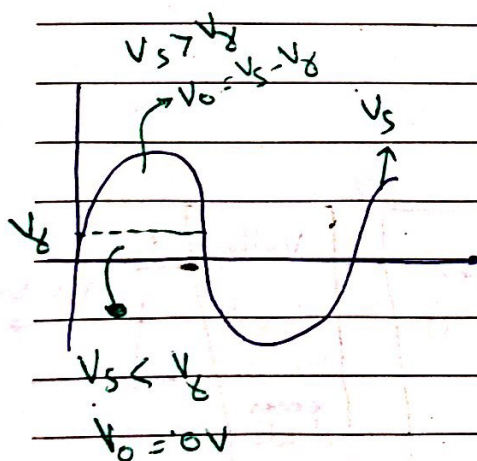


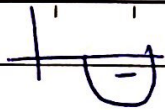* for -ve cycle :- 




step 1 : o.c

step 2 : $V_D = V_S$

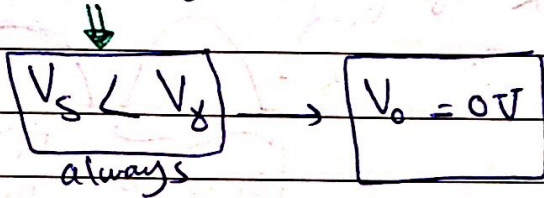step 3: if $V_D < V_g \rightarrow$ Diode is off




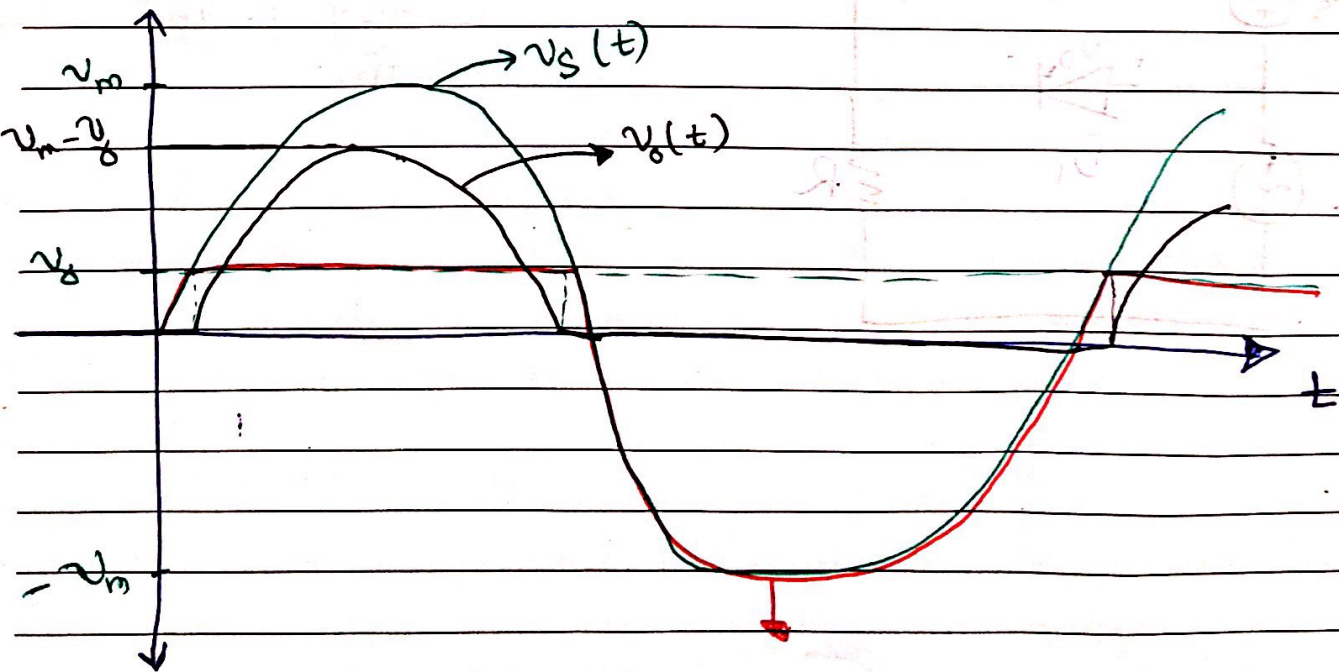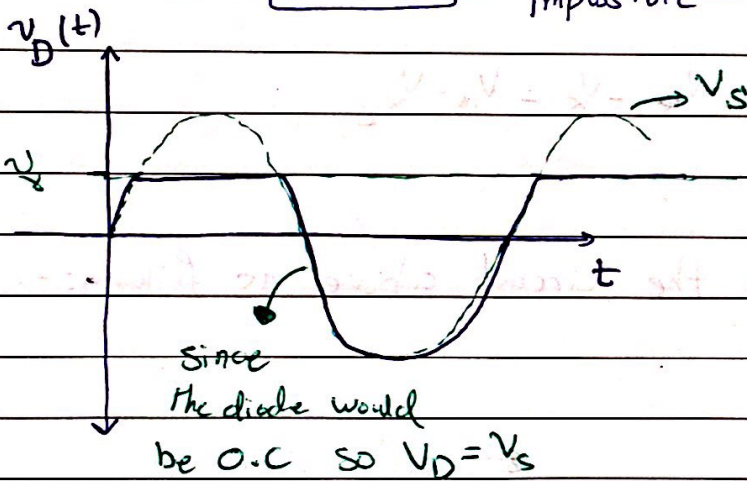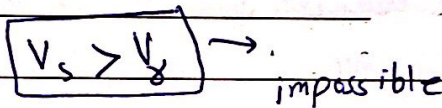if $V_D > V_g \rightarrow V_o = V_S - V_g$



Full-wave rectifier circuit:-


① Center-trapped F.w

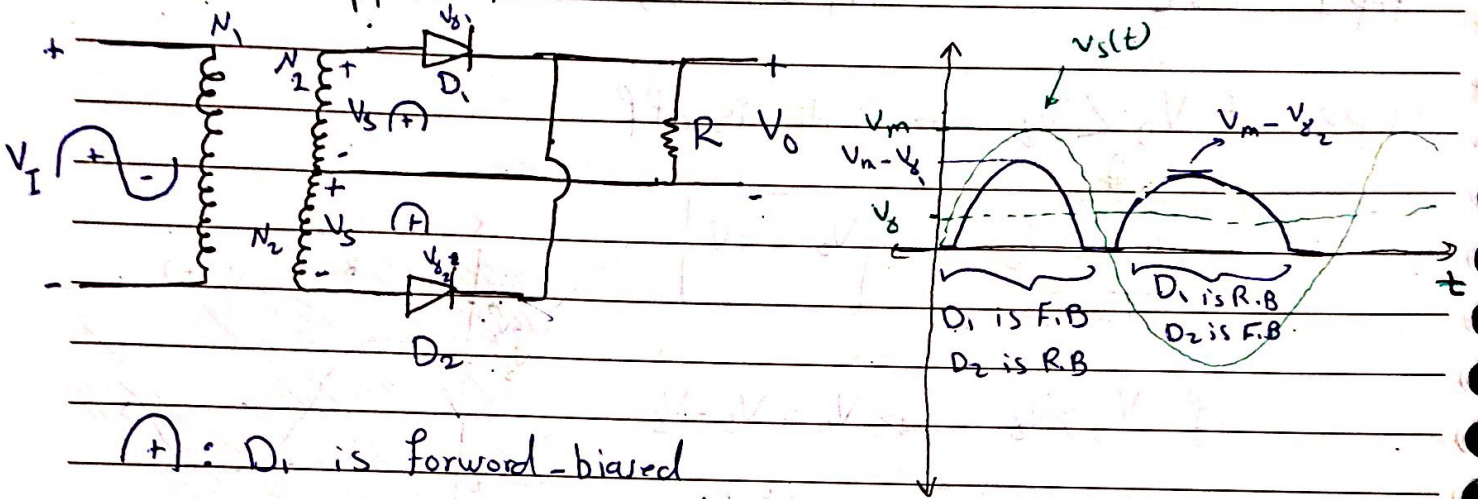

(+) : D_1 is forward-biased
 D_2 is reverse biased

(-) : $V_8 + V_8 + V_5 = 0 \Rightarrow V_0 = -V_5 - V_8 = V_m - V_{D2}$

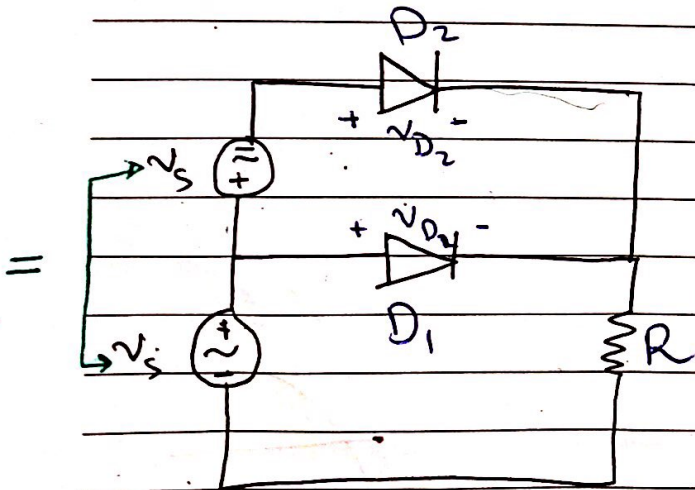→ you can imagine the circuit above as following:-




← this circuit is easy to deal with.

Sunday



Dr. Raed Al-Zaabi

28/2/2016

2] Full-wave Bridge rectifier:-

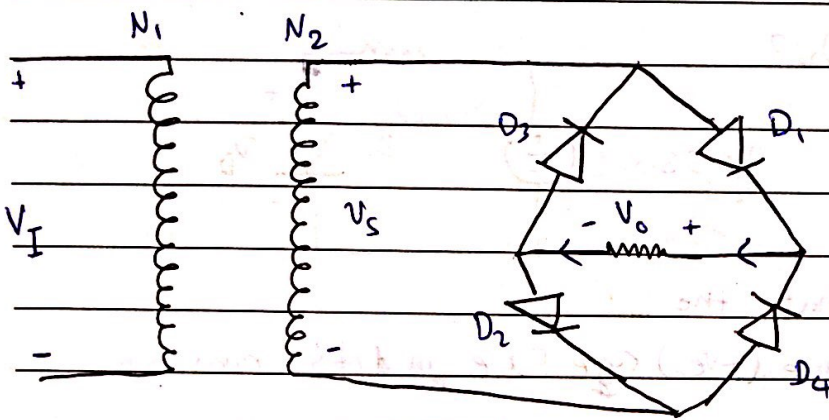

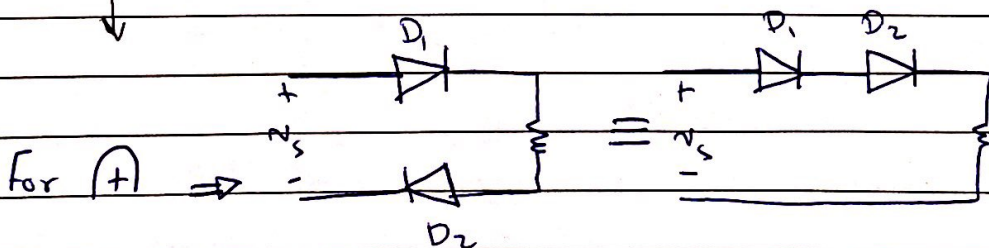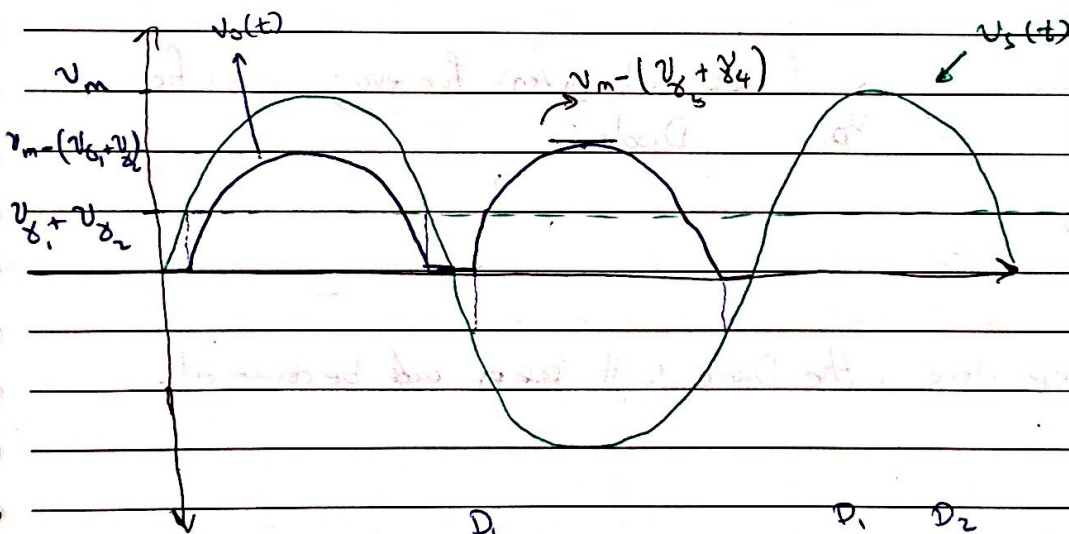for (+) \Rightarrow D_1 & D_2 Forward biased
 D_3 & D_4 Reverse biased




For (-) \Rightarrow D_3 & D_4 is Forward biased

D_1 & D_2 is Reverse biased



* PIV: Peak-inverse voltage of a diode :-

Ex: what is the PIV for D_1 ?

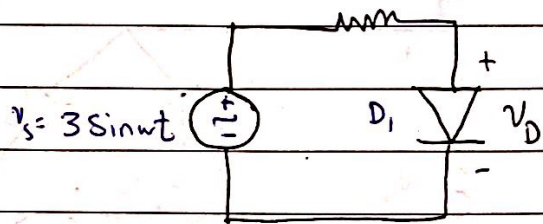

Solution:- first I assume that the source at the reverse (-ve) cycle in its maximum value


$$KVL \Rightarrow -(-3) - PIV = 0$$

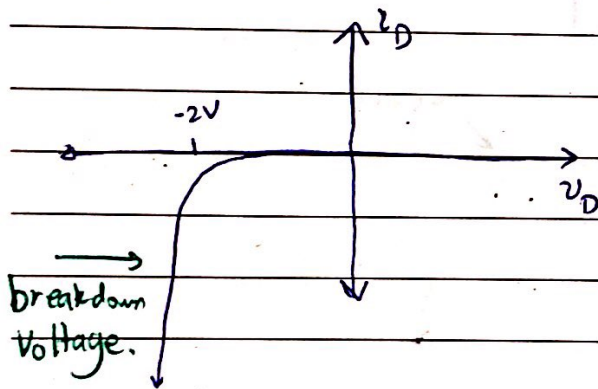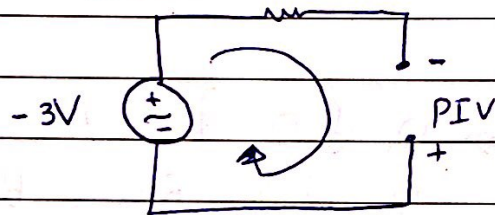


will given for every specific Diode.

in our case here, the Diode will be damaged.

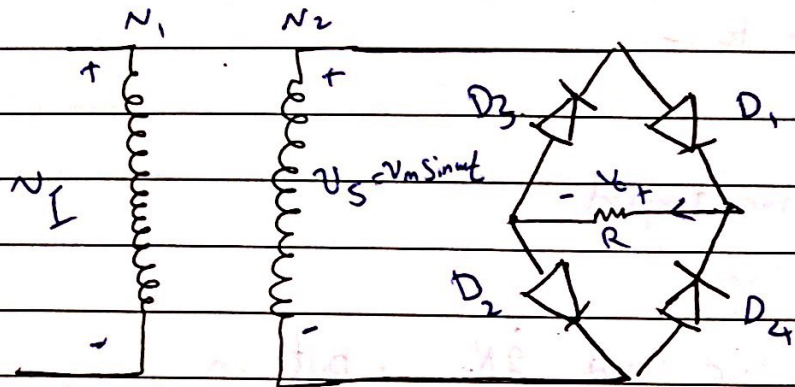Ex: Find PIV for D_1 in F.W rectifier circuit.



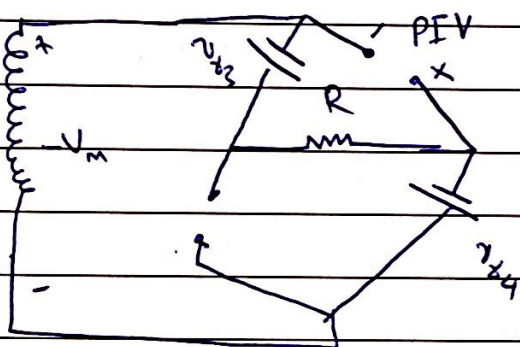Solution: assume we are at the (ive) cycle at maximum value




$$KVL: -(-v_m) - PIV - v_{D4} = 0$$

$$PIV = v_m - v_{D4}$$

PIV: The maximum reverse-voltage will affect the diode.

Ex:

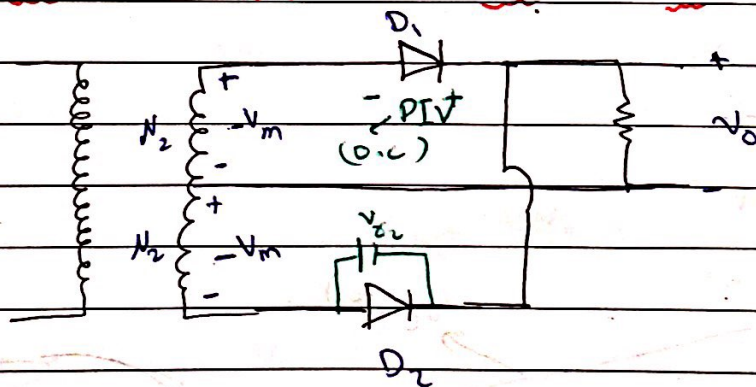


$$-(-v_m) - (-v_m) - PIV - v_{D2} = 0 \Rightarrow PIV = 2v_m - v_{D2}$$

* Usually the Bridge rectifier circuit is used more than the center-tapped circuit due to:-


① $PIV_{\text{Bridge}} < PIV_{\text{center-tapped}}$

② in the center tapped, we need $2N_2$, but in the bridge we need only N_2 , so in the center-tapped more cost and large sizes.


* Filter circuit:-

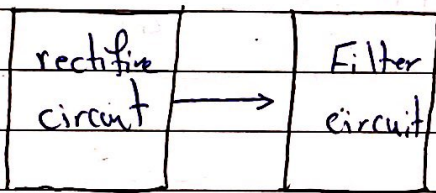

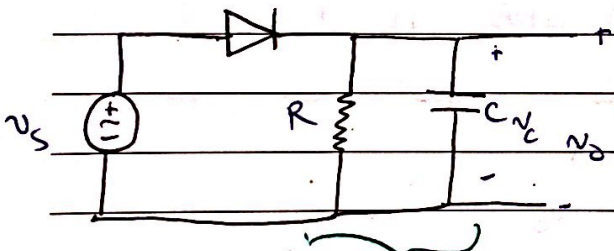Example: assume $V_s = 20V$, $r_f = 1\Omega$





Filter circuit

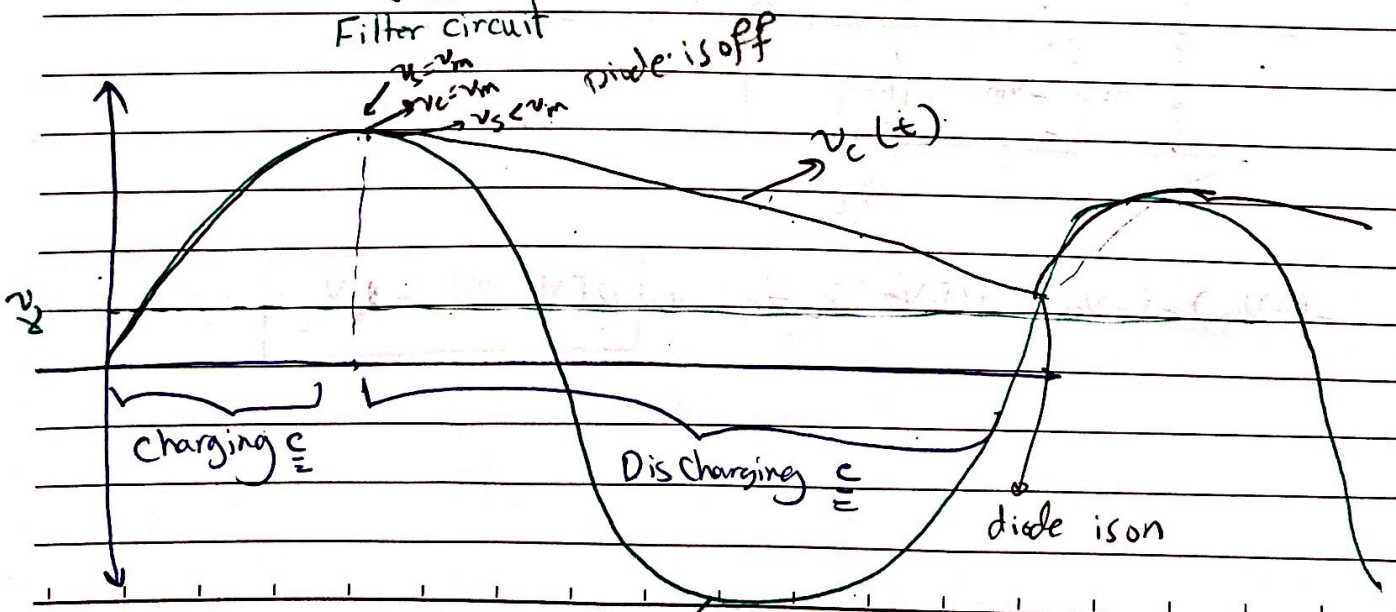

Tuesday

Dr. Raed AL-Zabi

11/3/2016

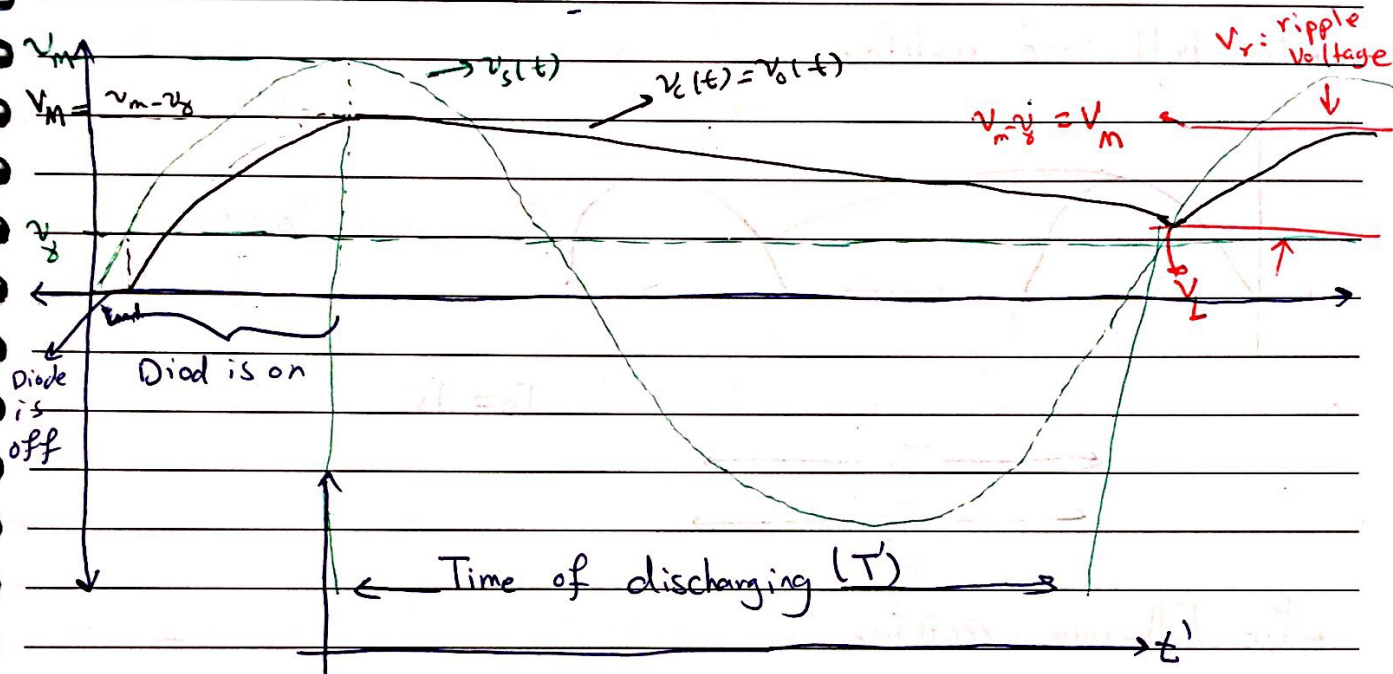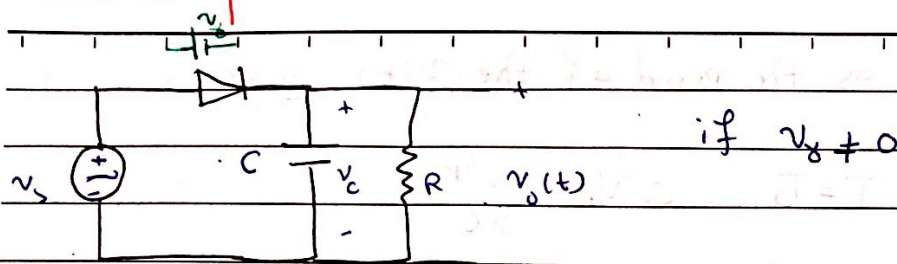

$$* V_r = V_m - V_L \Rightarrow V_m = V_m - V_L$$

* due to the free RC circuit, $v_o(t) = v_c(t) = V_m e^{-\frac{t'}{RC}}$

* $v_o(t) = V_m e^{-\frac{t'}{RC}}$, τ : time constant

$$* V_L = v_o(t' = T') = V_m e^{-\frac{T'}{RC}}$$

$$\Rightarrow V_r = V_m - V_m e^{-\frac{T'}{RC}} = V_m (1 - e^{-\frac{T'}{RC}})$$

* We want by design to minimize V_r . This can be done by make $e^{-\frac{T'}{RC}} \approx 1$, so we need $T' \ll RC$ ($\frac{T'}{RC}$ very small)

but if $\frac{T'}{RC}$ is very small, (by Taylor series): $e^{-\frac{T'}{RC}} \approx 1 - \frac{T'}{RC}$


$$V_r = V_m (1 - (1 - \frac{T'}{RC})) = \boxed{V_r = \frac{V_m T'}{RC}}$$

Five Apple


* if we define T_p as the period of the $v(t)$ signal

→ We can assume $T' = T_p \quad \therefore V_r = \frac{V_m T_p}{RC}$

* for half-wave rectifier

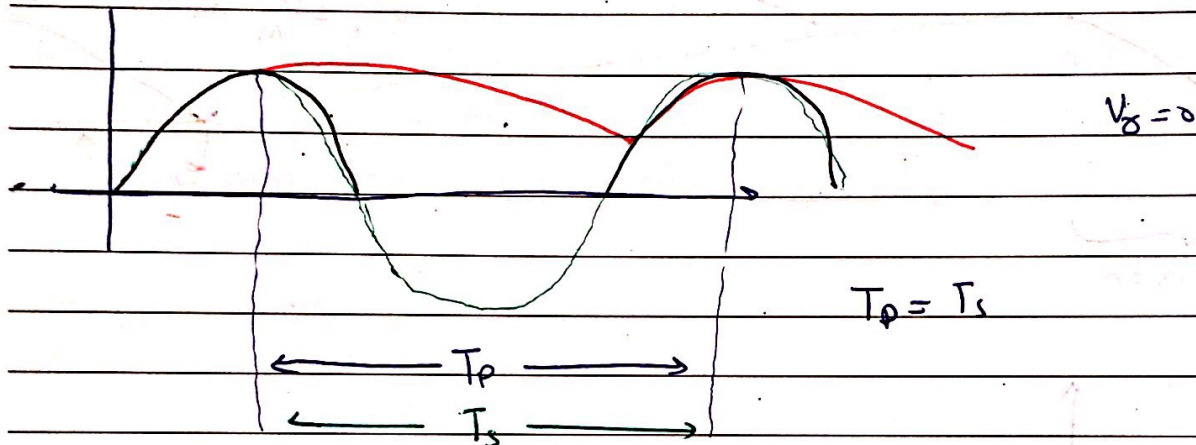

* for Full-wave rectifier

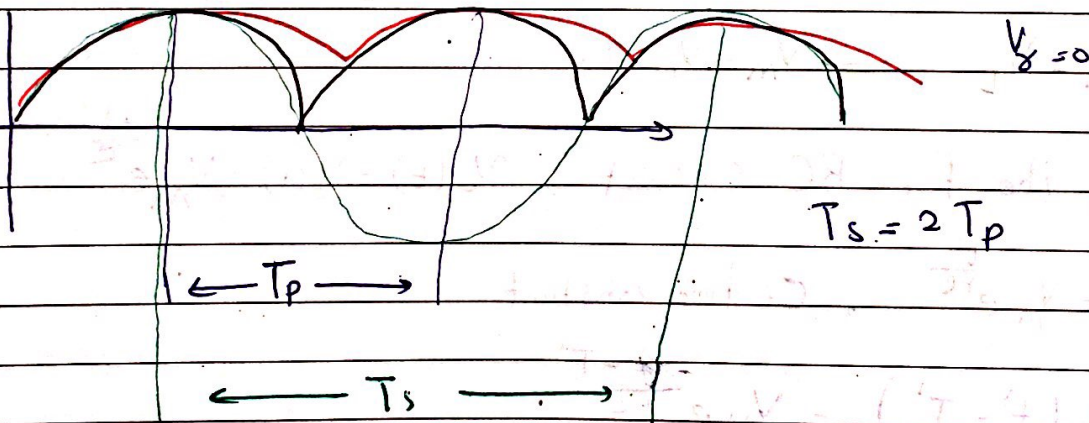

$$V_r = \frac{V_m T_p}{RC}$$

, for half-wave:

$$\Rightarrow V_m = V_m - V_g \quad \Rightarrow T_p = T_s = \frac{1}{f_s}$$

$$\Rightarrow V_r = \frac{(V_m - V_g)}{f_s RC}$$

V_M : The maximum voltage which the output will have.

For Full-wave :- \Rightarrow Bridge

$$V_M = V_m - 2V_d \quad \Rightarrow \quad T_p = \frac{T_s}{2} = \frac{1}{2f_s}$$

$$V_r = \frac{V_m - 2V_d}{2f_s RC}$$

\leftarrow The smallest V_r which is the best for design

\rightarrow Center-trapped

$$V_M = V_m - V_d \quad \Rightarrow \quad T_p = \frac{T_s}{2} = \frac{1}{2f_s}$$

$$V_r = \frac{V_m - V_d}{2f_s RC}$$

Use full relation :- \Rightarrow half-wave without filter :-


$$V_{dc} = \frac{V_m}{\pi}$$

average




\rightarrow Full-wave without filter :-

$$V_{dc} = \frac{2V_m}{\pi}$$

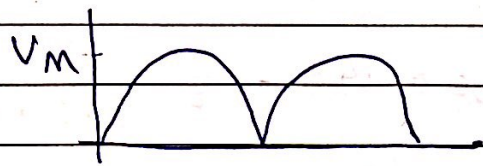


\rightarrow half-wave with filter :-

$$V_{dc} = V_m - \frac{1}{2}V_r$$

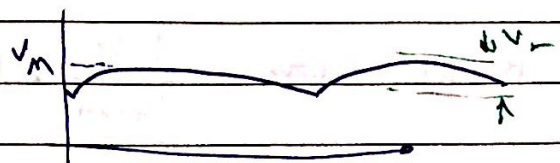


\rightarrow Full-wave with filter :-

$$V_{dc} = V_m - \frac{1}{2}V_r$$

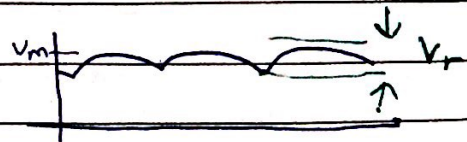

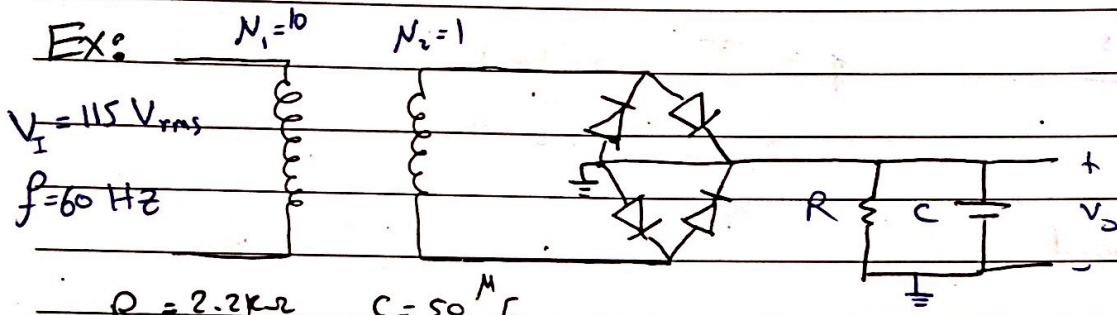* ripple factor % $\Rightarrow = \frac{V_r}{V_{DC} \text{ with filter}} \times 100\%$



$R = 2.2k\Omega$ $C = 50 \mu F$
 $V_f = 0.7V$ Find ripple factor.

Sol: ripple factor $\Rightarrow \frac{V_r}{V_{DC}}$

$\Rightarrow V_{DC} = V_m - \frac{1}{2} \frac{V_m}{f_s RC} \Rightarrow V_m = V_{DC} + \frac{1}{2} \frac{V_m}{f_s RC}$

$V_{S(rms)} = V_{I(rms)} \frac{N_2}{N_1} = 115 \times \frac{1}{10} = 11.5V$

$\therefore V_m = V_{S(rms)} \sqrt{2} = 16.3V$

$f_s = f_I = 60Hz$

$\therefore V_{DC} = 14.9 - \frac{1}{2} \frac{14.9}{2 \times 60 \times 2.2 \times 10^3 \times 50 \times 10^{-6}} = 14.34V$


$\therefore V_r = \frac{V_m}{2f_s RC} = 1.13V$

Ripple factor = $\frac{1.13}{14.34} \times 100\% \Rightarrow$

$= 8\% \Rightarrow$ كذا كانه اصبحت كان الفلتر اخرج

Sunday
6/3/2016

Dr. Raed AL-Zoubi

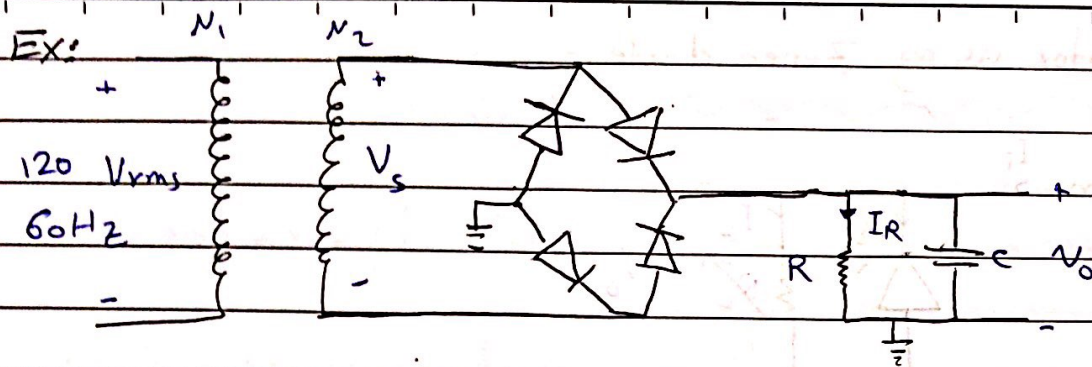

$$V_M = 12 \text{ V (max. output voltage } V_o(\text{max}))$$

$$V_r \leq 5\% V_M, \quad V_g = 0.7 \text{ V}, \quad I_{R(\text{max})} = 120 \text{ mA}$$

Find, $R, C, \frac{N_1}{N_2}$

$$\text{Sol: } V_M = V_m - 2V_g \Rightarrow \frac{V_{I(\text{rms})}}{V_{s(\text{rms})}} = \frac{N_1}{N_2}$$

$$V_m = V_M + 2V_g = 12 + 2(0.7) = 13.4 \text{ V}$$

$$\frac{120}{13.4/\sqrt{2}} = \frac{N_1}{N_2} = 12.67$$

$$I_{R(\text{max})} = \frac{V_M}{R} \Rightarrow R = 100 \Omega$$

$$V_r = \frac{V_M}{2fRC}$$


$$V_{r(\text{max})} = \frac{V_M}{2fRC_{\text{min}}}$$

$$\frac{(5)(12)}{100} = \frac{12}{(2)(60)(100) C_{\text{min}}}$$

$$C_{\text{min}} = 1667 \mu\text{F}$$

$$C > 1667 \mu\text{F}$$

* Voltage regulator using Zener diode:-

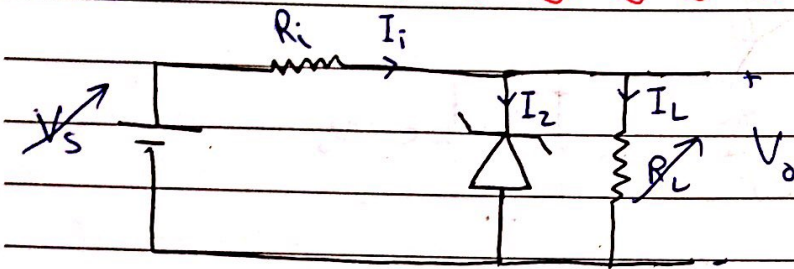

⇒ In this circuit, we want V_o to be a fixed value even the R_L or load V_L is changed

* Assume $r_z = 0 \Omega$

⇒ R_i is used to protect the Zener (to limit I_z)

$$\Rightarrow R_i = \frac{V_s - V_{zth}}{I_i} \quad \Rightarrow R_i = \frac{V_s - V_{zth}}{I_z + I_L}$$

$$\Rightarrow \boxed{I_z = \frac{V_s - V_{zth}}{R_i} - I_L} \quad \Rightarrow \boxed{I_L = \frac{V_{zth}}{R_L}}$$

⇒ We know that:-

① $I_{z(min)}$ when $I_{L(max)}$ and $V_{s(min)}$

② $I_{z(max)}$ when $I_{L(min)}$ and $V_{s(max)}$

$$\therefore R_i = \frac{V_{s(min)} - V_{zth}}{I_{z(min)} + I_{L(max)}} \quad \text{①}$$

$$R_i = \frac{V_{s(max)} - V_{zth}}{I_{z(max)} + I_{L(min)}} \quad \text{②}$$

Equation ① = Equation ②

$$(V_{s(\min)} - V_{zth}) (I_{z(\max)} + I_{L(\min)}) = (V_{s(\max)} - V_{zth}) (I_{z(\min)} + I_{L(\max)})$$

usually, $I_{z(\min)} \approx 0.1 I_{z(\max)}$


and we know: $V_{s(\min)}$, $V_{s(\max)}$, $I_{L(\min)}$, $I_{L(\max)}$, V_{zth}

$$I_{z(\max)} = \frac{I_{L(\max)} [V_{s(\max)} - V_{zth}] - I_{L(\min)} [V_{s(\min)} - V_{zth}]}{V_{s(\min)} - 0.9 V_{zth} - 0.1 V_{s(\max)}}$$

Then we use ② to find R

Ex: Design a voltage regulator to power a Car Radio at $V_L = 9V$ from an automobile battery whose voltage may vary between (11 - 13.6 V), The current in the radio will vary between (0 (off) 100 mA (full volume)) Assume $r_z = 0$

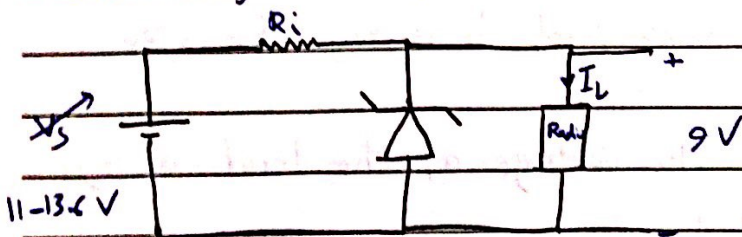Sol: Design means: select a Zener diode (V_{zth}) ($P_{z(\max)}$) $\rightarrow I_{z(\max)} \times V_{z(\max)}$



$\Rightarrow V_{zth}$ should equal 9V.

$$\Rightarrow I_{z(\max)} = \frac{100 \times 10^{-3} [13.6 - 9] - 0 [11 - 9]}{11 - (0.9)(9) - (0.1)(13.6)}$$

$$= 300 \text{ mA}$$

\Rightarrow power rating for the selected Zener diode should

$$be = (300 \times 10^{-3})(9) = 2.7 \text{ watt}$$


→ Continue to previous example:-

$$R_i = \frac{V_{s(\max)} - V_{zth}}{I_z(\max) + I_L(\min)} = 15.3 \Omega$$

$$P_{R_i(\max)} = I_{i(\max)}^2 \times R_i = \frac{(V_{s(\max)} - V_{zth})^2}{R_i} = 1.4 \text{ watt}$$

* For non-ideal Zener diode ($r_z > 0 \Omega$), V_z will be

$$V_z = V_{zth} + I_z r_z$$

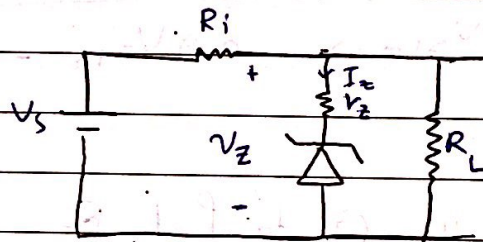

To consider the effect of r_z , we find

① Source regulation = $\frac{\Delta V_L}{\Delta V_s} \times 100\%$ (at fixed R_L)

② load regulation = $\frac{V_L(\text{no load}) - V_L(\text{Full load})}{V_L(\text{Full load})} \times 100\%$ (at fixed V_s)

* For Ideal Zener diode the source and load regulations = Zero.

Since on Ideal Zener diode the voltage at the load always constant $V_L = V_{zth}$, so $\Delta V_L = 0$.

* load regulation :- هو مقدار التغير في خرج الجهد عند وجود الحمل (التيار) عند التغير في الجهد الكهربي
كسبة مئوية

8/3/2016 | Dr. Raed AL Zoabi

Tuesday


EX: for the last example "Radio design example", if $r_z = 2 \Omega$
find the source and load regulations.

Sol: source regulation = $\frac{\Delta V_L}{\Delta V_s} * 100\%$ (at a fixed R_L)

→ assume $R_L = \infty$ (open circuit), $I_L = 0A$

* if $V_s = 13.6V$
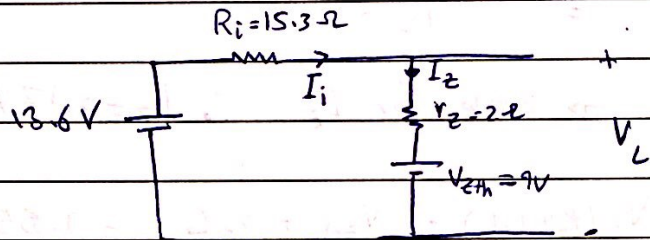
$$I_i = I_z = \frac{V_s - 9}{R_i + r_z} = 0.2659 A$$



$$\therefore V_L = V_{Zth} + r_z I_z = 9.532 V$$

* if $V_s = 11V$

$$I_i = I_z = \frac{V_s - 9}{R_i + r_z} = 0.1159 \text{ Ampere}$$

$$V_L = V_{Zth} + r_z I_z = 9.231 V$$

$$\therefore \text{Source regulation} = \frac{9.532 - 9.231}{13.6 - 11} * 100\%$$

$$= 11.6\%$$

← كلما كان اقل كلما كان افضل

$$\therefore \text{load regulation} = \frac{V_L(I_L=0A) - V_L(I_{L,max})}{V_L(I_{L,max})} \quad (\text{at a fixed } V_s)$$

Let $V_s = 13.6V$ (or $11V$ no difference)

if $I_L = 0A \Rightarrow V_L = 9.532 V$
(no load)

if $I_L = 100 mA \Rightarrow V_L(\text{full load}) = V_{Zth} + r_z I_z$

→ Continue to previous example

$$V_L = V_{zth} + r_z I_z$$

(full load)

but $I_z = I_i - I_L = \frac{V_s - (I_z r_z + V_{zth})}{R_i} - I_L$


$$I_z = \frac{13.6 - (2I_z + 9)}{15.3} - 0.1$$

→ solve for $I_z \therefore I_z = 0.1775 \text{ A}$


$$V_L (\text{full load}) = V_{zth} + r_z I_z = 9.355 \text{ V}$$

→ load regulation = $\frac{9.532 - 9.355}{9.355} \times 100\%$
 $= 1.89\%$

* The final form of (AC → DC) circuit: -

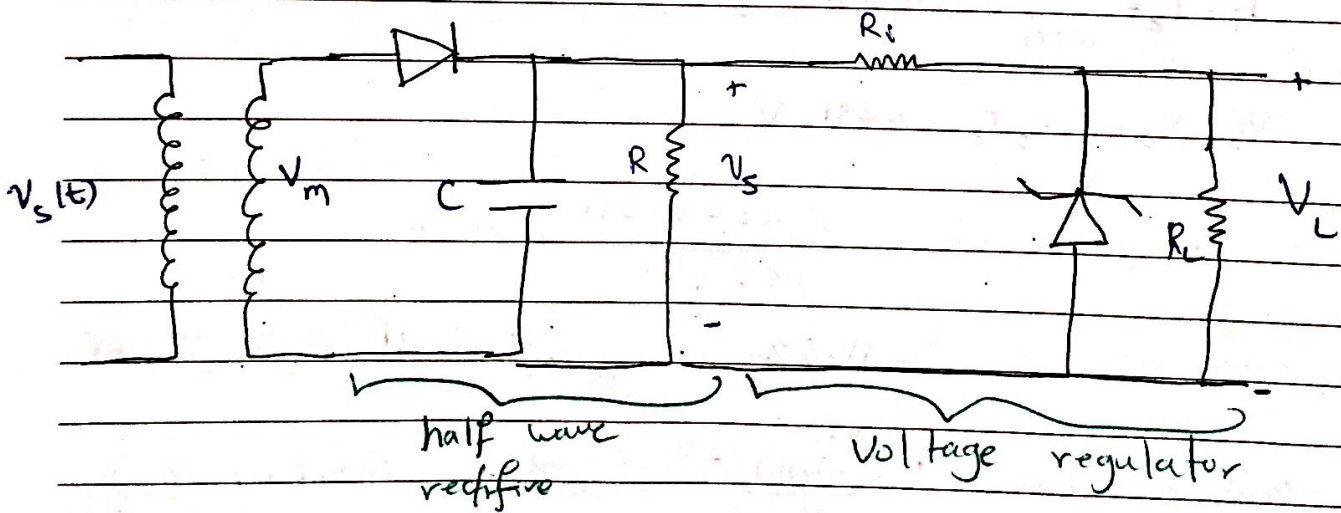

* Battery Charger:-

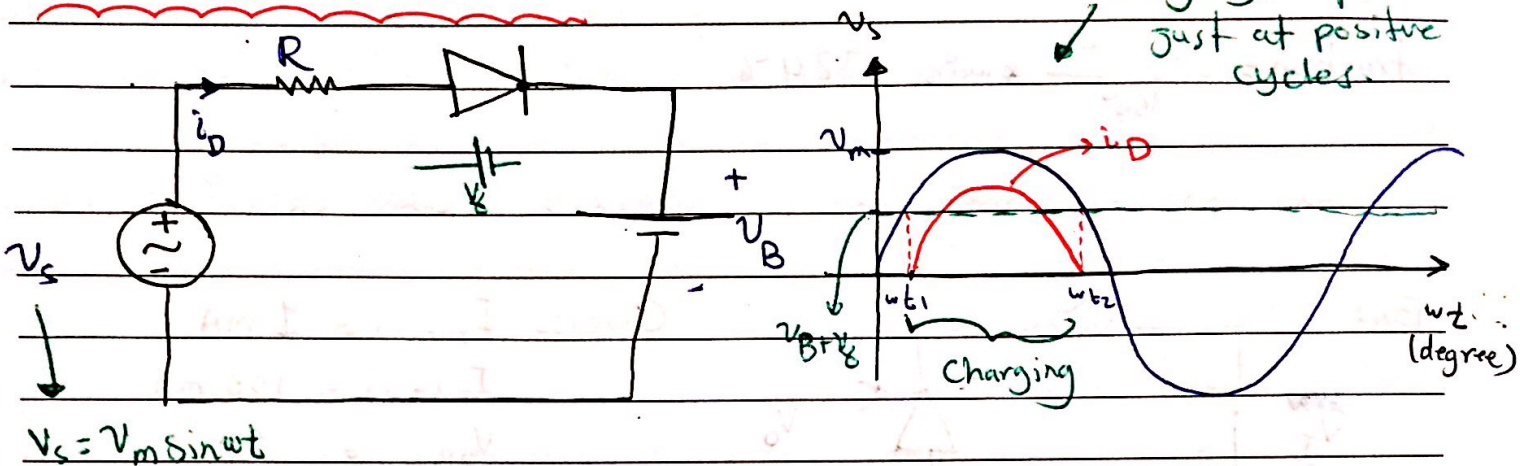

⇒ Diode is ON, if $v_s - V_B > V_g$, $v_s > V_g + V_B$

↓
Charging process
 $i_D > 0$

Example:- if $V_B = 12 \text{ V}$, $R = 100 \Omega$, $V_g = 0.6 \text{ V}$, $v_s(t) = 24 \sin \omega t$.

- Determine:
- (a) the peak diode current.
 - (b) the maximum reverse bias diode voltage (PIV).
 - (c) the fraction of the cycle over which the diode is conducting.

Sol: a) KVL: $-v_s + Ri_D + V_g + V_B = 0 \Rightarrow i_{D(\max)} = \frac{v_{s(\max)} - (V_g + V_B)}{R} = 114 \text{ mA}$

b) PIV = $v_s + V_B = 36 \text{ V}$


c) fraction = $\frac{\omega t_2 - \omega t_1}{360^\circ} \times 100\%$
the full cycle of the v_s

$\omega t_1 = ? \rightarrow v_s|_{\omega t_1} = V_g + V_B \Rightarrow 24 \sin(\omega t_1) = 12.6 \Rightarrow \omega t_1 = \sin^{-1}\left(\frac{12.6}{24}\right) = 31.7^\circ$

$$\Rightarrow \omega_2 t = 180^\circ - 31.7^\circ = 148.3^\circ \quad (\text{by symmetry})$$

$$\text{fraction} = \frac{\omega_2 - \omega_1}{360^\circ} \times 100\% = 32.4\%$$

Ex:

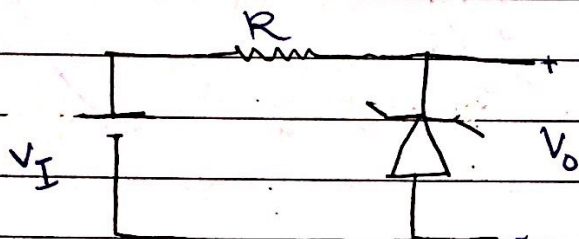

Given: $I_{z(\min)} = 1 \text{ mA}$

$I_{z(\max)} = 126 \text{ mA}$

$V_{zth} = 5.1 \text{ V}$

$r_z = 7 \Omega$

$R = 100 \Omega$

a) Find the range of V_I where the Zener diode works as regulator

b) Find the source regulation.

Sol: a) if $I_z = I_{z(\min)}$ $\Rightarrow -V_{I(\min)} + R I_{z(\min)} + r_z I_{z(\min)} + V_{zth} = 0$
 $\Rightarrow V_{I(\min)} = 5.207 \text{ V}$

if $I_z = I_{z(\max)}$ $\Rightarrow -V_{I(\max)} + R I_{z(\max)} + r_z I_{z(\max)} + V_{zth} = 0$
 $\Rightarrow V_{I(\max)} = 26.072 \text{ V}$

So $5.207 \text{ V} \leq V_I \leq 26.072 \text{ V}$

b) Source regulation = $\frac{\Delta V_O}{\Delta V_I} \times 100\%$

$\Rightarrow I_{z(\min)} \Rightarrow V_L = r_z I_{z(\min)} + V_{zth} = 5.107 \text{ V}$


$\Rightarrow I_{z(\max)} \Rightarrow V_L = r_z I_{z(\max)} + V_{zth} = 6.472 \text{ V}$

Source regulation = $\frac{6.472 - 5.107}{26.072 - 5.207} \times 100\% = 6.5\%$

* Clipper circuits (limiter circuit):-

→ clip portions of a signal.


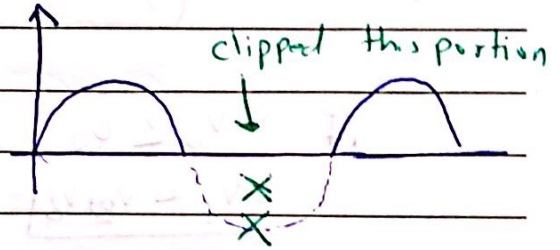
Ex: half-wave rectifier circuit is a clipper circuit



* applications:-


limit the voltage at the input of an electronic circuit so as to prevent breakdown of the transistors and diodes in the circuit.

Example:-

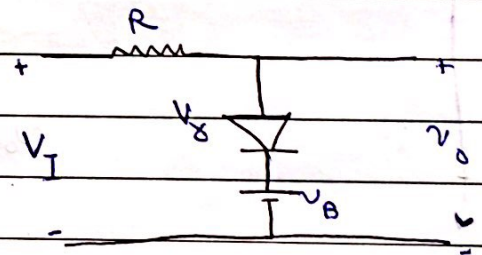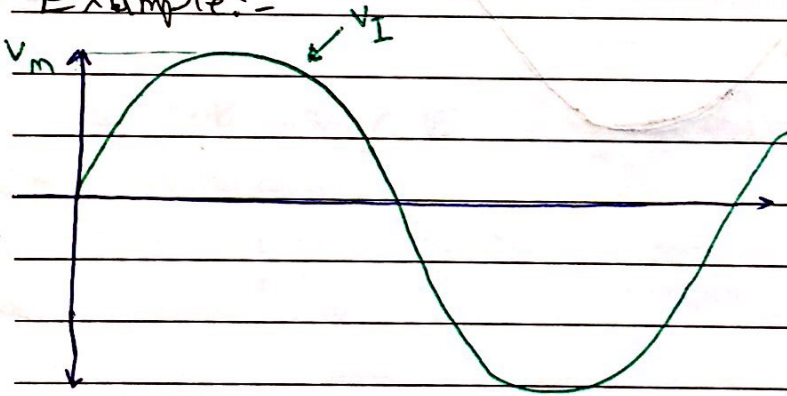

Solve use 3-step solution :-

① the diode is open circuit

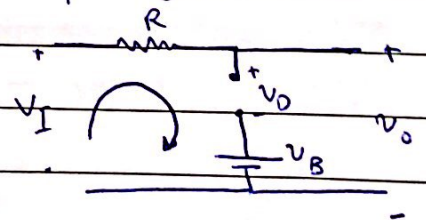

$$② \quad V_I + V_D + V_B = 0$$

$$V_D = V_I - V_B$$


→ continue to previous example.

③ check if $V_D > V_g \rightarrow$ Diode is ON

$$V_I - V_B > V_g$$

$$V_I > V_g + V_B$$


$$\therefore V_o = V_B + V_g$$

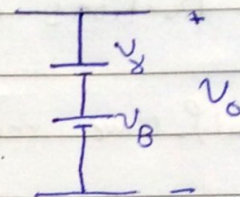

if $V_D < V_g \rightarrow$ Diode is off


$$V_I < V_B + V_g$$

$$\therefore V_o = V_I$$

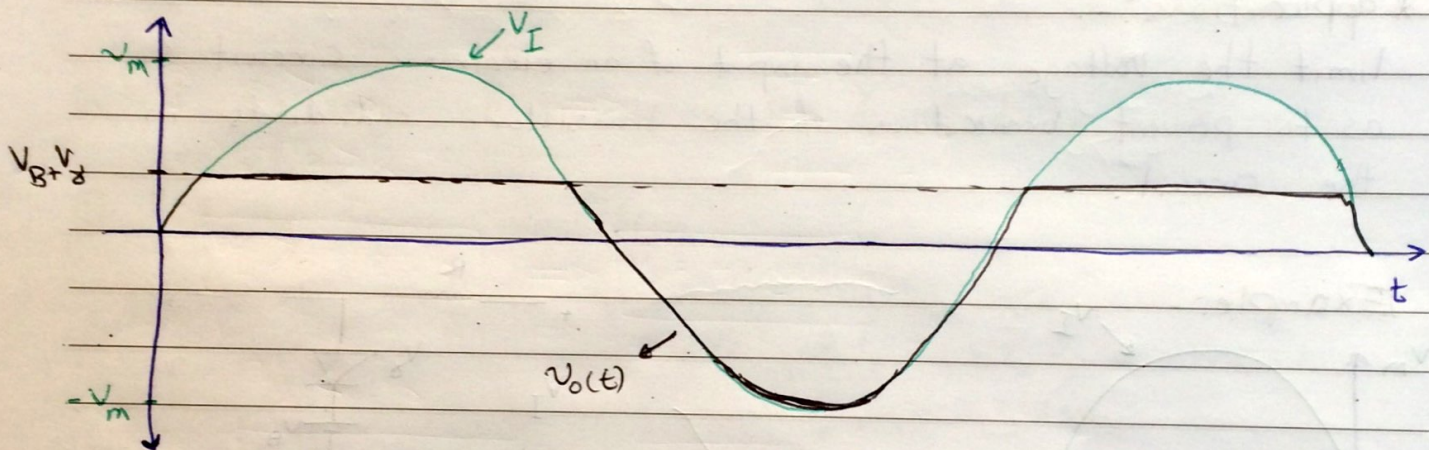


followed \Rightarrow

Five Apple

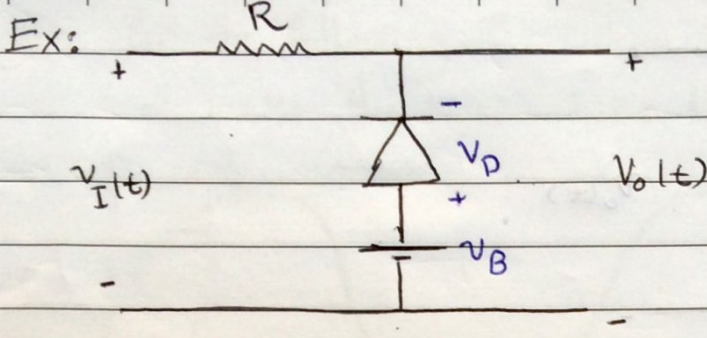

Sol: ① assume the diode is open circuit

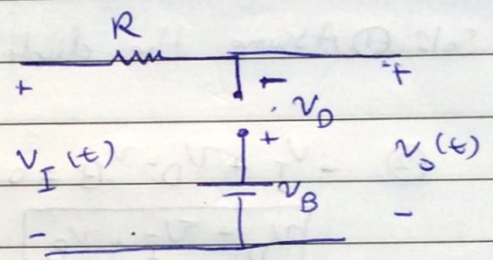

② $-v_I - v_D + v_B = 0$
 $v_D = -v_I + v_B$


③ if $v_D > v_s \Rightarrow$

$-v_I + v_B > v_s$

$v_I < v_B - v_s \Rightarrow \therefore v_O = v_B - v_s$


if $v_D < v_s \Rightarrow v_O = v_I$

$v_I > v_B - v_s$

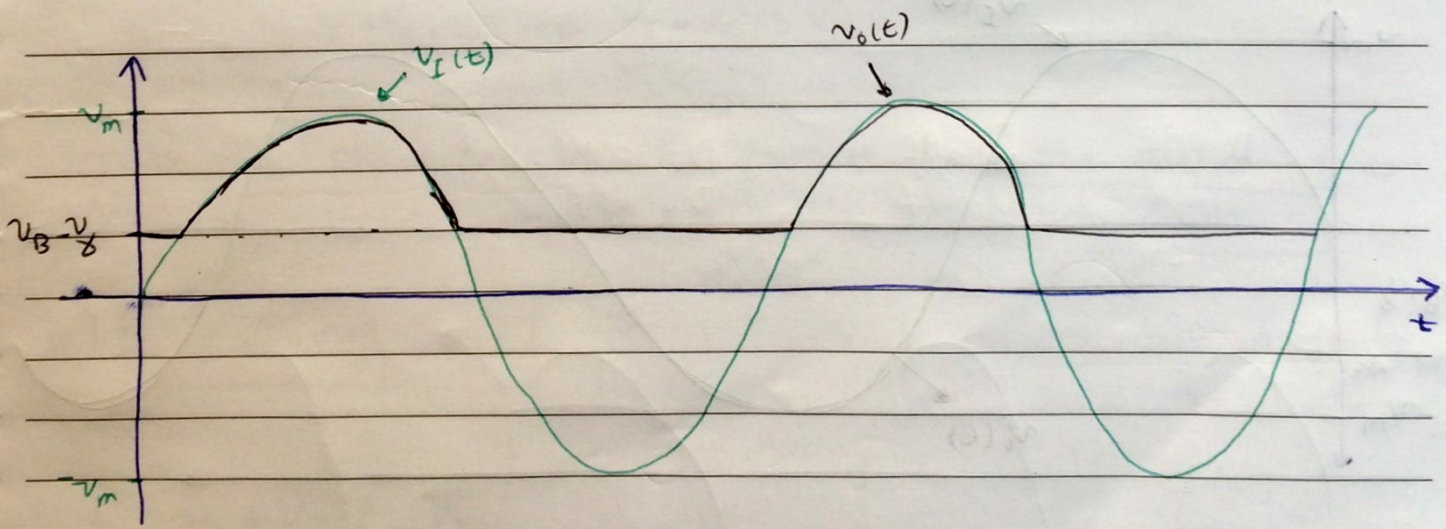


* try to draw v_o vs $v_I(t)$

Example:-

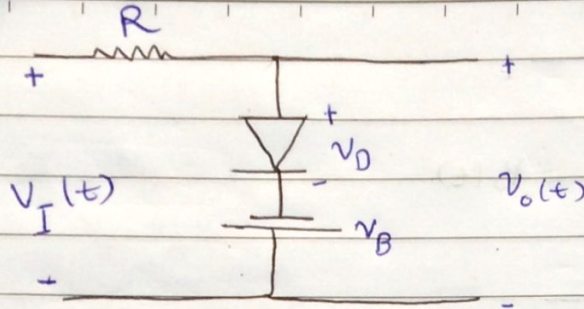

Sol: ① Assume the diode is open circuit

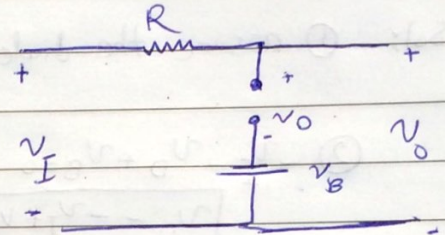


② $-v_I + v_D - v_B = 0$

$v_D = v_I + v_B$

③ $v_D > v_s$

$v_I + v_B > v_s$

\Rightarrow

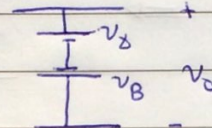


$v_I > -v_B + v_s$

$\Rightarrow v_o = -v_B + v_s$



$v_D < v_s$

$v_I < -v_B + v_s$

$\Rightarrow v_o = v_I$

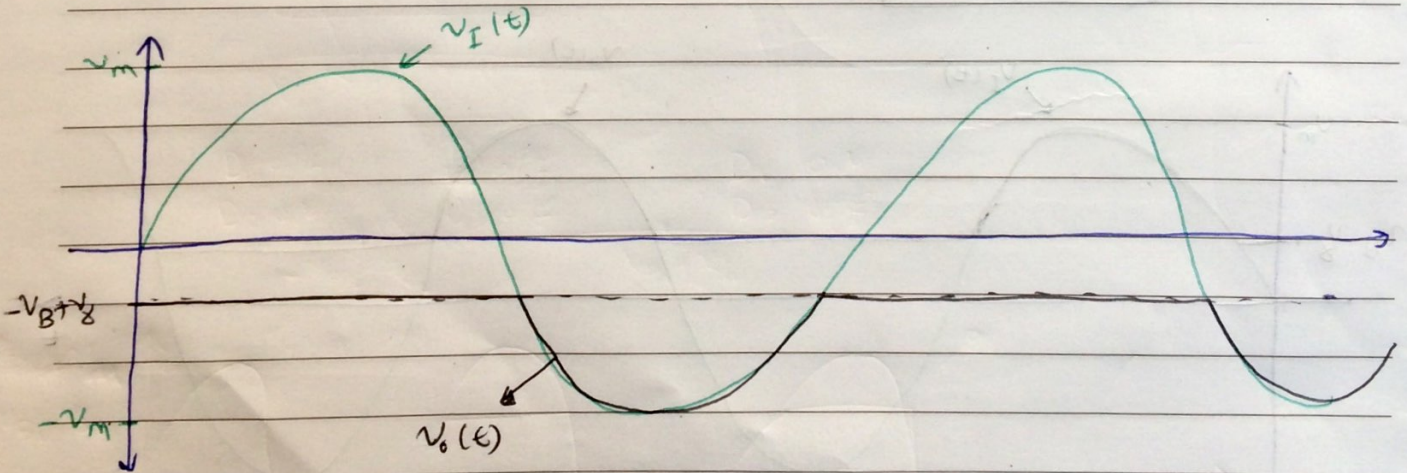

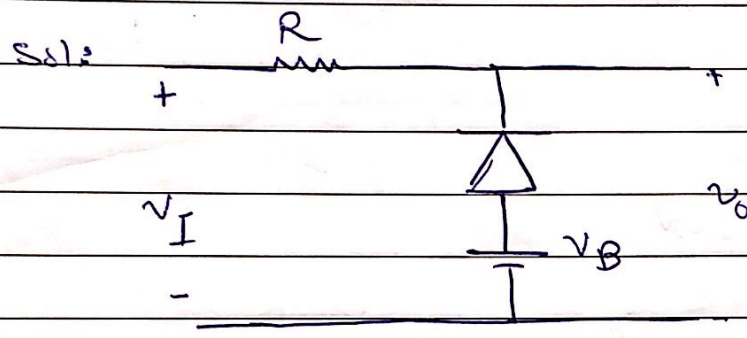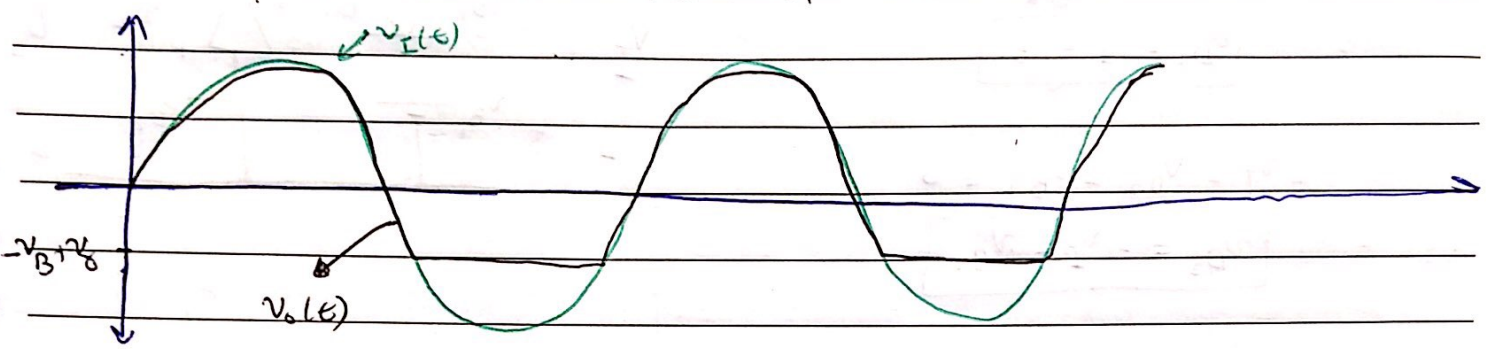Ex: for the following graph find the (clipper circuit) which will make the $v_o(t)$ like that



← By trying !!!
or solve it in reverse way!


Ex: ① O.C

② $-V_I + V_{D1} + V_{B1} = 0$

$V_{D1} = V_I - V_{B1}$

$-V_I - V_{D2} - V_{B2} = 0$

$V_{D2} = -V_I - V_{B2}$

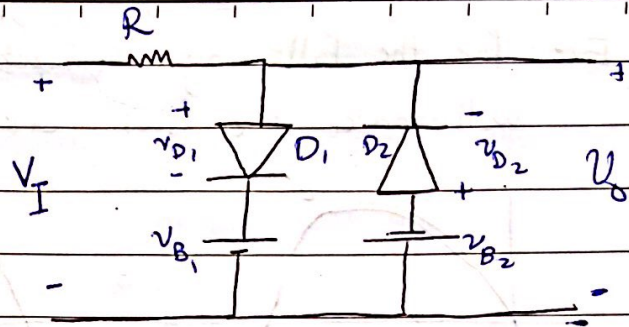

③ if $V_{D1} > V_{B1} \Rightarrow D_1$ is ON

$V_I - V_{B1} > V_{B1}$

$V_I > 2V_{B1} \rightarrow D_1$ is ON



$V_I < 2V_{B1} \rightarrow D_1$ is off

if $V_{D2} > V_{B2} \Rightarrow D_2$ is ON

$-V_I - V_{B2} > V_{B2}$

$V_I < -2V_{B2} \rightarrow D_2$ is ON



$V_I > -2V_{B2} \rightarrow D_2$ is off

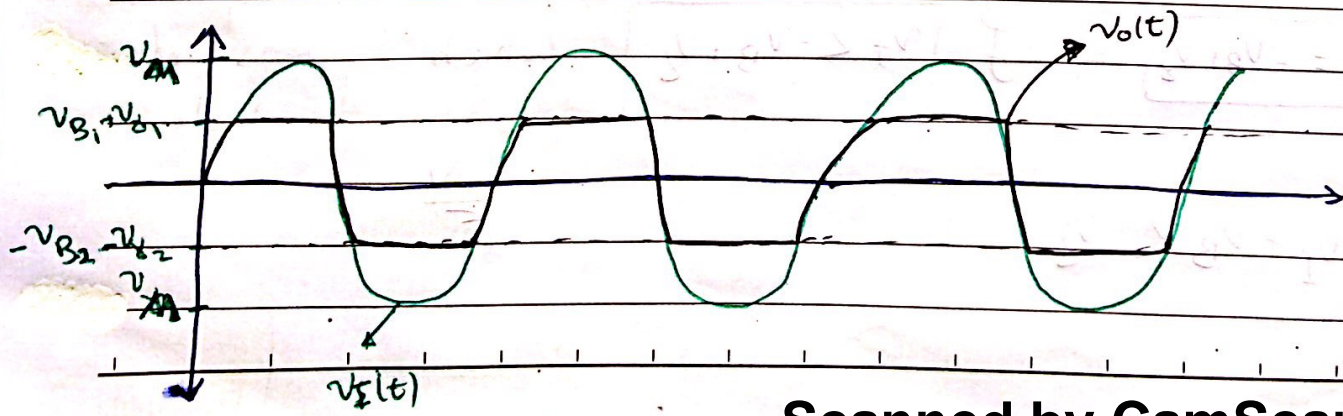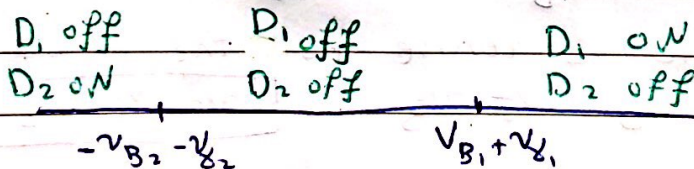

13/3/2016 | Dr. Raed AL-Zaabi
 Sunday | Continue to clipper circuit.

Ex:

Solution:- ① Diode is off (open circuit)

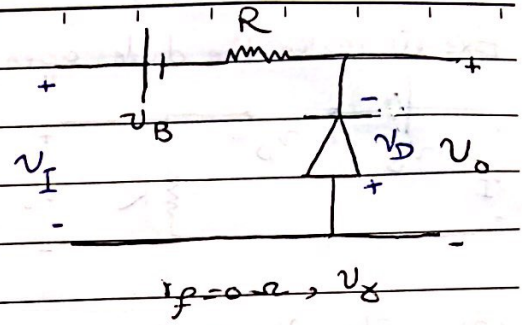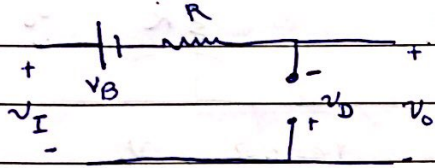


$$\textcircled{2} -v_I + v_B - v_o = 0 \Rightarrow v_o = -v_I + v_B$$

③ Check: if $v_o > v_\gamma \Rightarrow -v_I + v_B > v_\gamma \Rightarrow v_B - v_\gamma > v_I$
 Diode is on



$$\therefore v_o = -v_\gamma$$

④ if $v_o < v_\gamma \Rightarrow v_B - v_\gamma < v_I \Rightarrow$ Diode is off
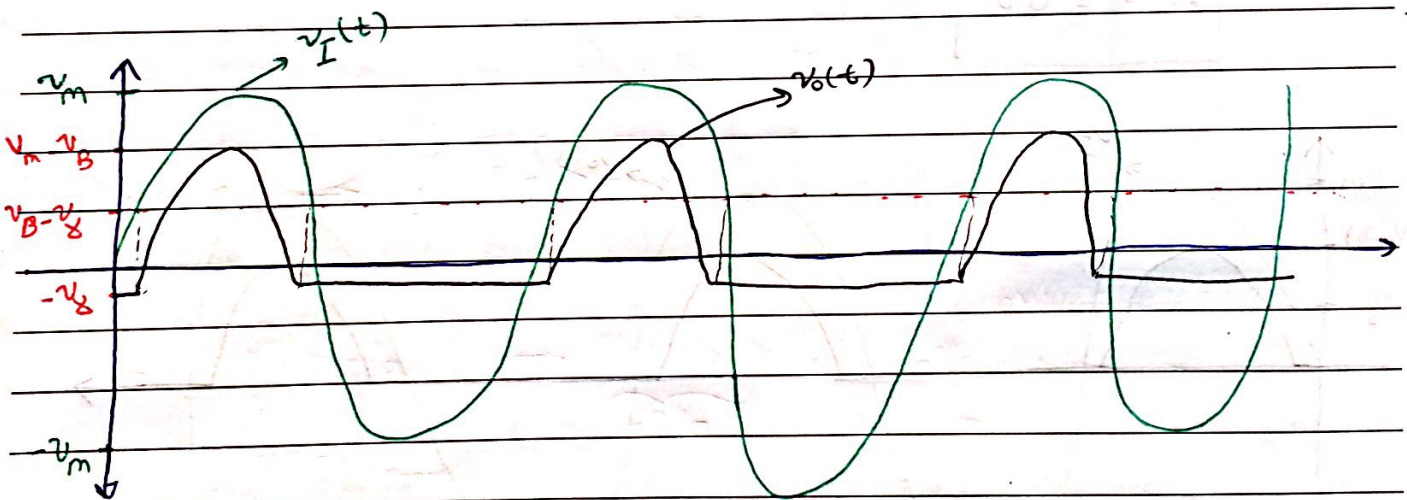
$$\text{KVL: } -v_I + v_B + v_o = 0 \Rightarrow v_o = v_I - v_B$$



Ex: ① make the diode open circuit

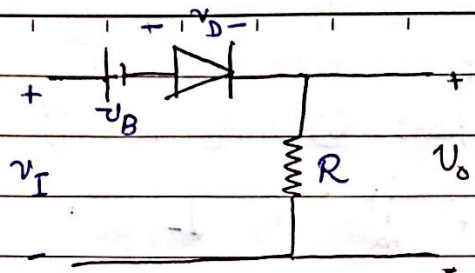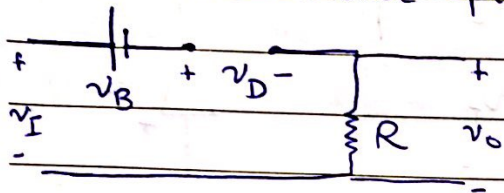


$$r_f = 0, v_s$$

② $-v_I + v_B + v_D = 0 \rightarrow v_D = v_I - v_B$

③ check: if $v_D > v_s \rightarrow v_I - v_B > v_s \Rightarrow v_I > v_s + v_B$
 Diode is ON


KVL: $-v_I + v_B + v_s + v_o = 0$

$$v_o = v_I - (v_B + v_s)$$


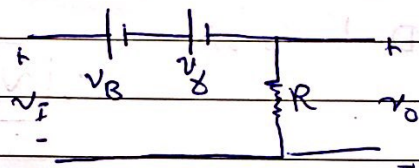


if $v_D < v_s \rightarrow v_I < v_s + v_B \rightarrow$ Diode is off

$$\therefore v_o = 0V$$

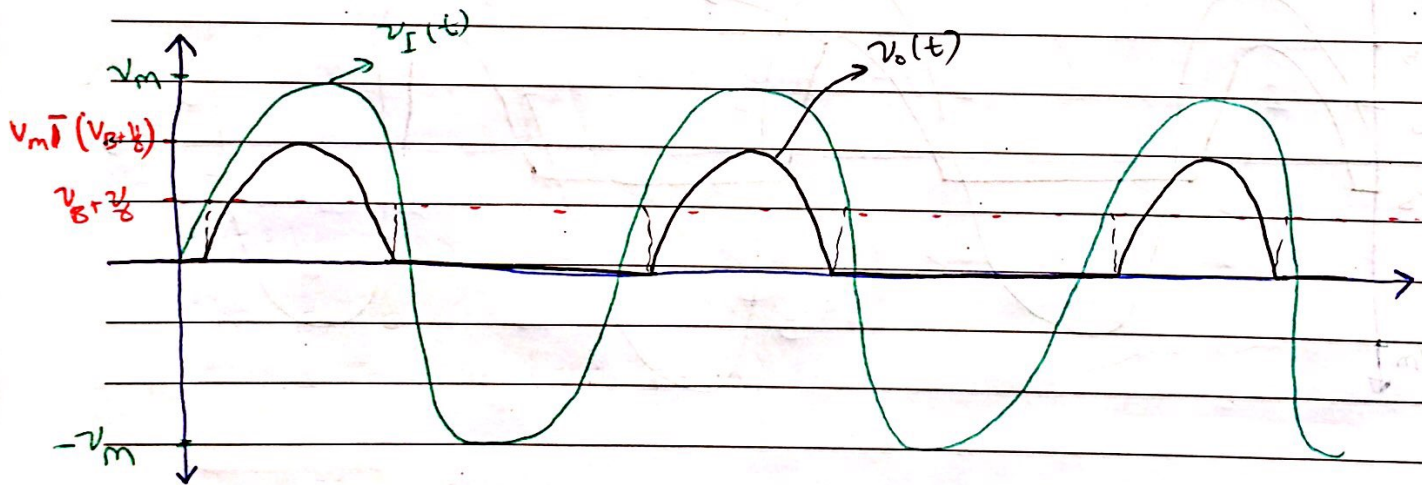


Ex:

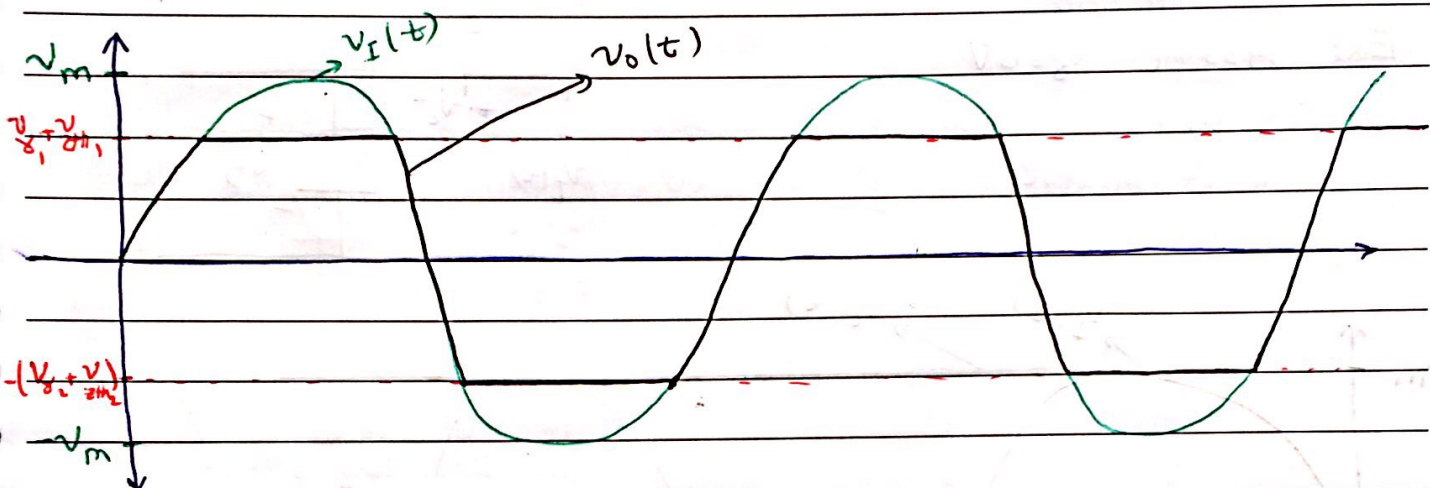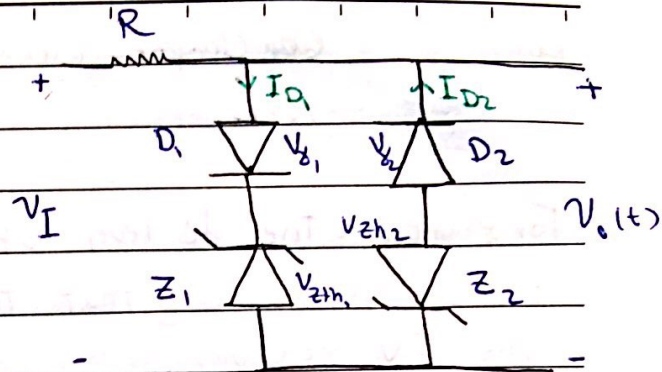

* at the positive cycle (+), D_2 is off, and D_1, Z_1 is off until $v_I > v_{D1} + v_{Z1}$.



* at the negative cycle (-), D_1 is always off, and D_2, Z_2 is off until $|v_I| > |v_{D2} + v_{Z2}| \Rightarrow v_I < -(v_{D2} + v_{Z2})$

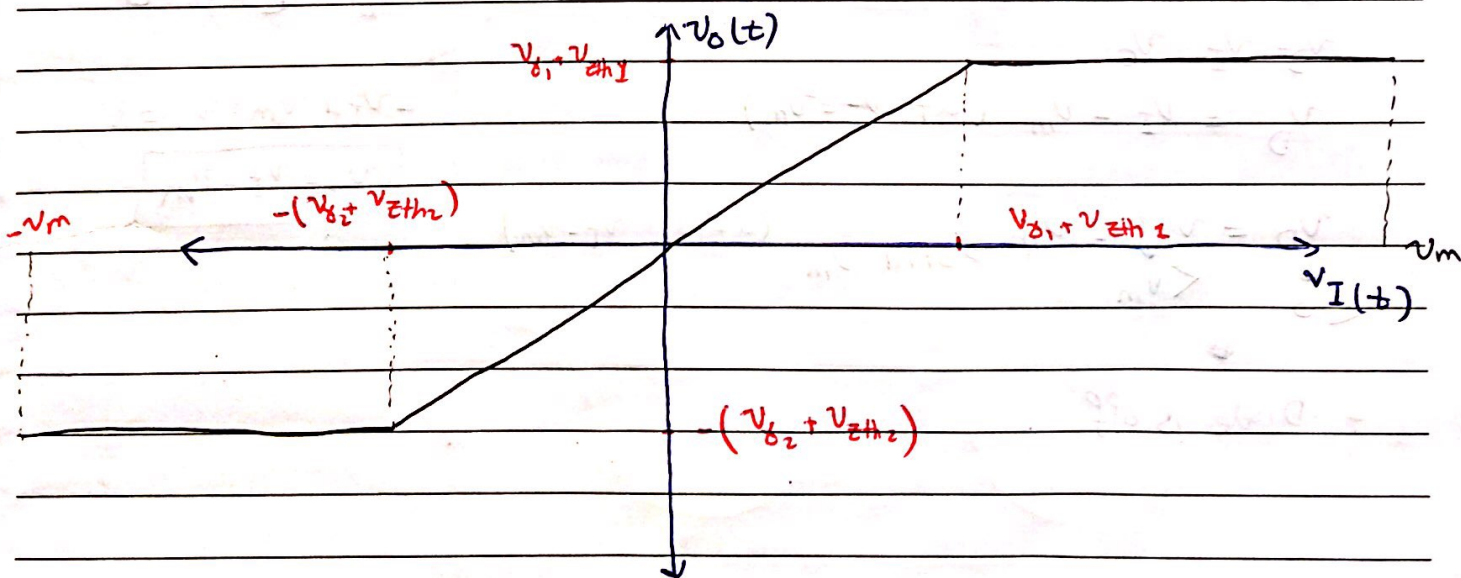

Definition: - clamper circuit shift the DC voltage level of the input signal.

For example:- the dc level of a TV signal may be lost during transmission so that the dc level must be restored at the TV receiver.

Ex: Assume $v_c = 0V$

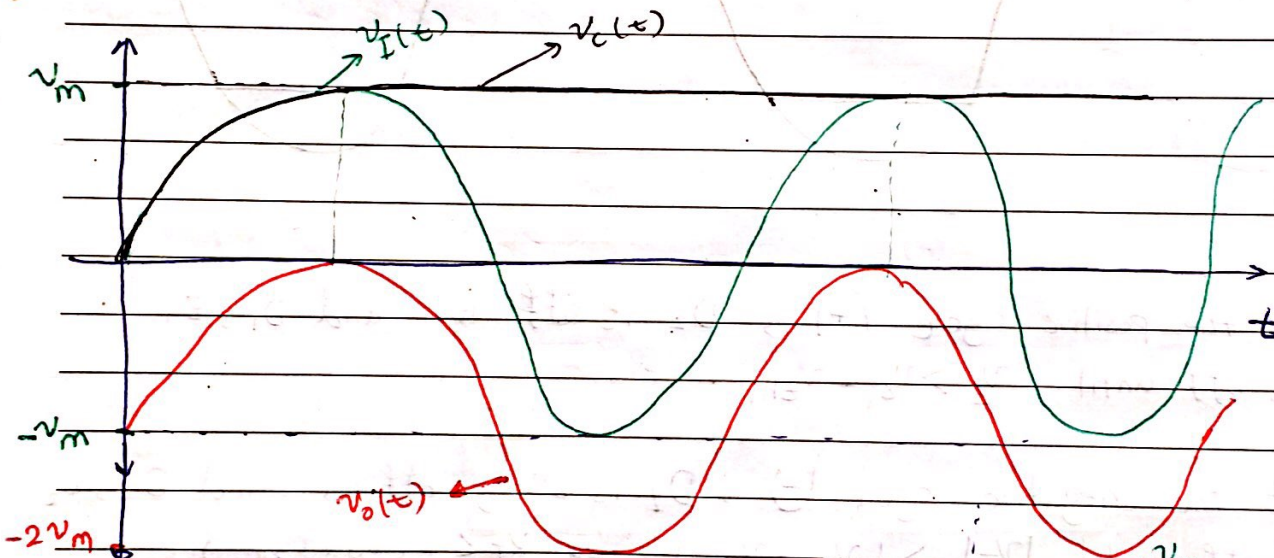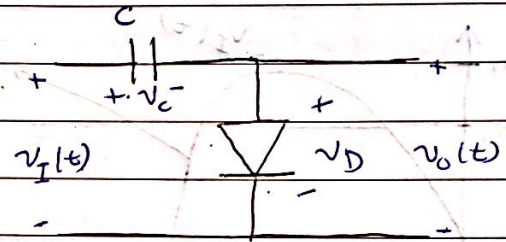

$$-v_I + v_c + v_o = 0$$

$$v_D = v_I - v_c$$

$$v_D = v_I - v_m \quad (\text{at } v_I = v_m)$$

$$v_D = v_I - v_m \rightarrow \text{still } v_m \quad (\text{after } v_I = v_m)$$

< 0

↓

Diode is off

$$-v_I + v_m + v_o = 0$$

$$-v_I + v_m + v_o = 0$$

$$v_o = v_I - v_m$$

How to solve these kind of problems..

Step (0): Calculate $V_{c(max)}$ and replace the capacitor by a voltage source $v_{c(max)}$

Step (1): repeat the 3-step solution as we did before.

* solving the previous example with these steps:-

Step (0): $-V_I + v_c = 0 \Rightarrow v_c = V_I \Rightarrow v_{c(max)} = V_{I(max)} = v_m$

Step (1): A - Assume diode is o.c

B - $-v_I + v_m + v_D = 0$


$$v_D = v_I - v_m$$

C - Check:- if $v_D > v_s$
 \Rightarrow Diode is ON

$$v_D > v_s \Rightarrow v_I - v_m > 0 \Rightarrow v_I > v_m \rightarrow \text{impossible} \\ \Rightarrow v_D = 0V$$

if $v_D < v_s$
 \Rightarrow Diode is off
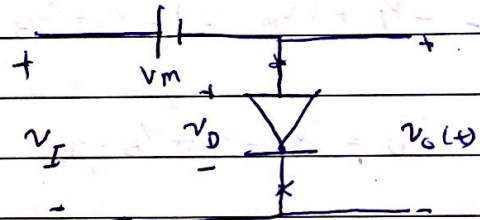
$$v_I - v_m < 0 \Rightarrow v_I \leq v_m \Rightarrow \text{always} \\ \Rightarrow v_D = v_I - v_m$$



* charging process happens when there is current (Diode on)


Ex:

Step (0) : $-v_I + v_C + v_B = 0$

$v_C = v_I - v_B$

$v_{C(max)} = v_{I(max)} - v_B$


$v_{C(max)} = v_m - v_B$

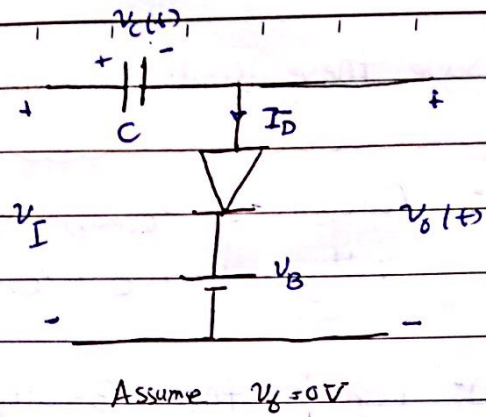

Step (1) :- A-O.C

B- $-v_I + (v_m - v_B) + v_D + v_B = 0$

$v_D = v_I - v_m + v_B - v_B$

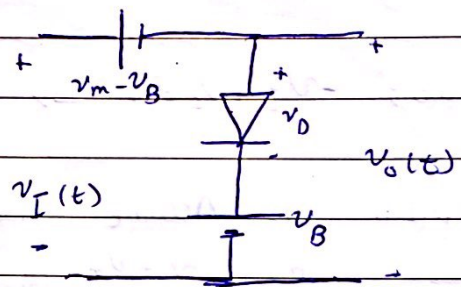

check :- if $v_D > v_B$ \Rightarrow Diode is on

$v_I - v_m > 0$


$v_I > v_m \rightarrow$ impossible $\rightarrow v_O = 0V$

if $v_D < v_B$ \Rightarrow Diode is off

$v_I < v_m$

$v_O = v_I - (v_m - v_B)$

$v_O = v_I - v_m + v_B$

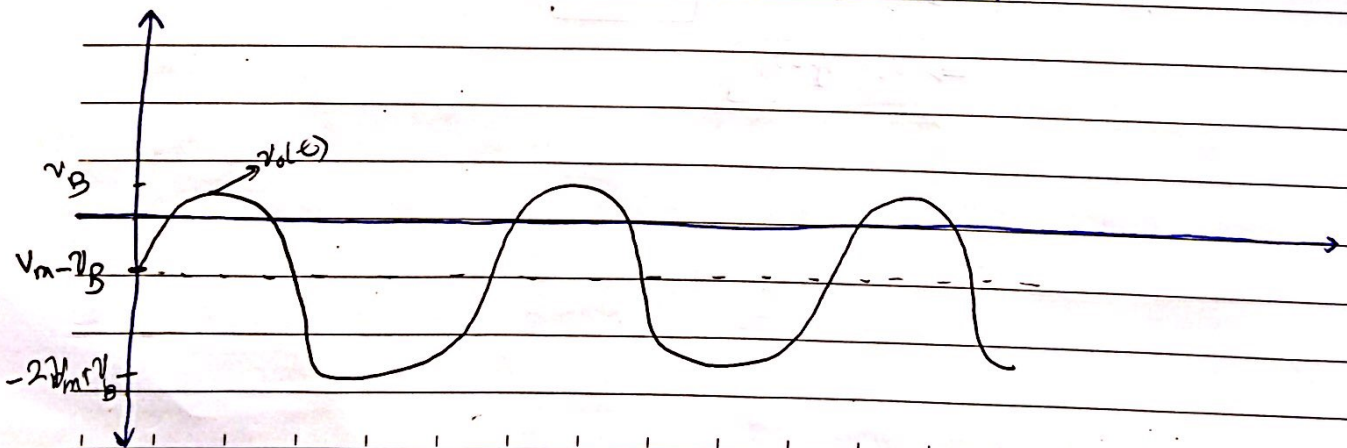

sunday

24/3/2016

حل الامتحان الأول

Q₁: $T = 300K$, $x = 0 \text{ cm} \Rightarrow n_0 = 10^{15} \text{ cm}^{-3}$
 $x = 5 \text{ cm} \Rightarrow n_0 = 5 \times 10^{15} \text{ cm}^{-3}$
 drift $J_n = 100 \text{ mA/cm}^2$

Sol: 1) Diffusion D_n : $\frac{D_n}{\mu_n} = 0.026 \rightarrow D_n = 39$



2) Diffusion $J_n = e D_n \frac{dn}{dx} = (1.6 \times 10^{-19} \text{ A}) (39) \left(\frac{5 \times 10^{15} - 10^{15}}{5 - 0} \right)$

$J_n = 0.0049 \text{ A/cm}^2$

3) \vec{E} at $x = 5 \text{ cm}$, $\vec{J}_n = en \mu_n \vec{E}$ (drift)
 $\vec{E} = 0.0833 \text{ A/cm}$

4) $V = -\mu_n \vec{E} = -124.95$

Q₂:

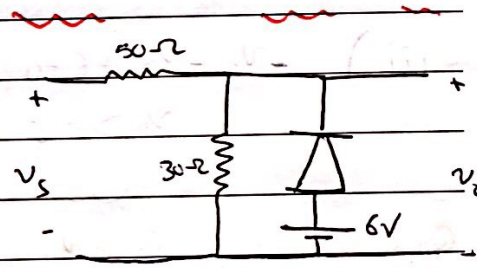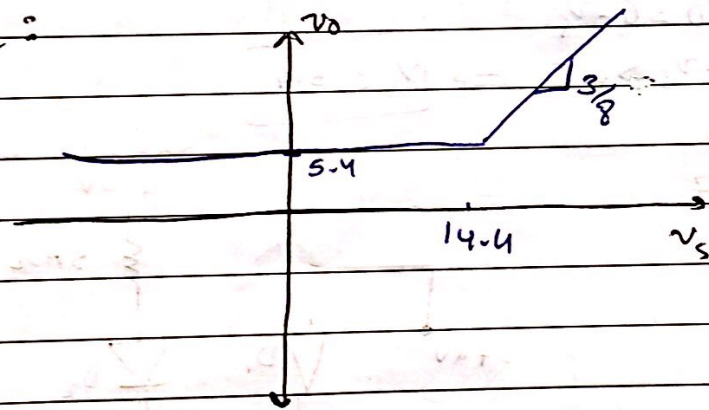

1) o.c, 2) $v_{3\Omega} = v_s \frac{30}{30+50} = \frac{3}{8} v_s$
 $v_D = 6 - \frac{3}{8} v_s$

3) if $v_o > 0.6$ Diode is on $\Rightarrow v_o = 5.4 \text{ V}$
 $6 - \frac{3}{8} v_s > 0.6 \Rightarrow v_s < 14.4$


if $v_s > 14.4 \Rightarrow$ Diode is off

$v_o = \frac{3}{8} v_s$

حل الامتحان الأول

Q3: $V_s = 3.8V$, $V_f = 0.6V$, $r_f = 10\Omega$

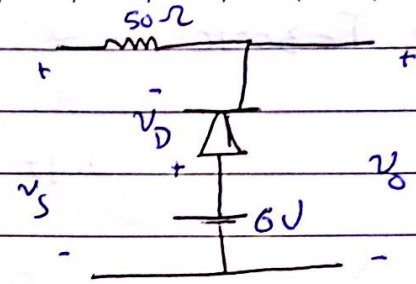
i) 3-step solution \rightarrow Diode is on



$$-6 + 0.6 + 10I_D + 50I_D + 3.5 = 0$$

$$I_D = 0.0267A$$
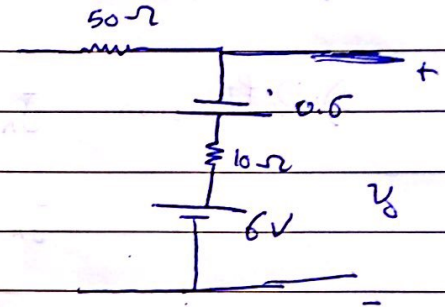
$$V_o = 6 - 0.6 - (10)(0.0267) = 5.133V$$



ii) $V_s = 10$ snwt, $V_f = 0.6V$, $r_f = 0\Omega$

$$-V_s + P_{IV} + 6 = 0 \Rightarrow PIV = V_s - 6 = 10 - 6 = 4V$$


iii) $-V_s - V_D + 6 = 0 \Rightarrow V_D = 6 - V_s$

$$V_D > 0.6 \Rightarrow 6 - V_s > 0.6 \Rightarrow V_s < 5.4$$

Q4: Diode 2 is on $V_f = 0.7$

Sol: 3-step solution

Step 1, 2) $V_D = 4 - V_x$

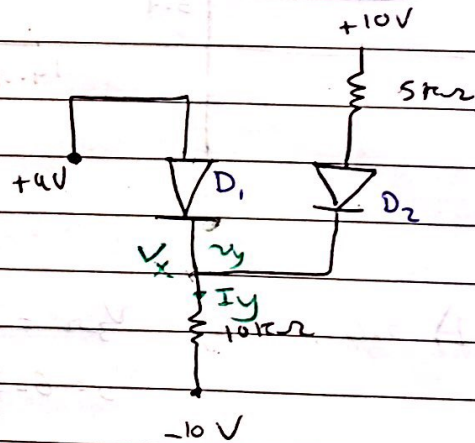

$$-10 + 5I_x + 0.7 + 10I_y - 10 = 0$$

$$I_x = 1.2867mA$$

$$-V_x + 10I_x = 10 = 0 \Rightarrow V_x = 2.8670V$$


$$V_{D1} = 1.133 > 0.7 \Rightarrow \text{Diode is on}$$

$$\Rightarrow -4 + 0.7 - 0.7 + V = 0 \Rightarrow V = 4V \quad | \quad -4 + 0.7 + V_y = 0 \Rightarrow V_y = 3.3V$$

$$I_y = \frac{3.3 + 10}{10} = \frac{16 - 0.7 - 3.3}{5} = 0.13mA$$

حل الامتحان الأول

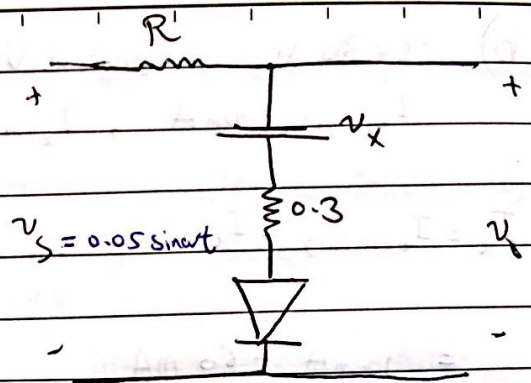Q5) $r_f = 10 \Omega$, $i_D = 0.5 + 0.05 \sin \omega t$




Sol: for AC Analysis

$$r_d = \frac{v_T}{I_D} = \frac{0.026}{0.5} = 0.052 \Omega$$

$$\rightarrow -v_s + R i_D + 0.3 i_D + r_d i_D = 0$$


$$R = 0.048 \Omega$$

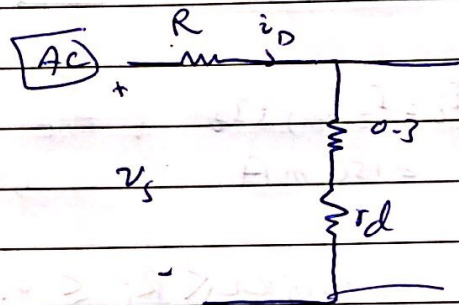


for DC Analysis

$$R I_D - v_x + 0.3 I_D + 0.7 + r_d I_D = 0$$

$$v_x = 6.1740 \text{ V}$$

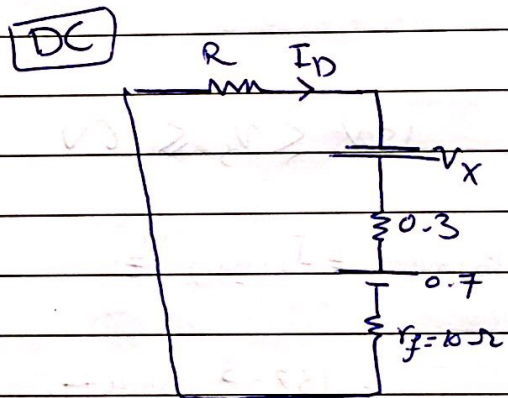

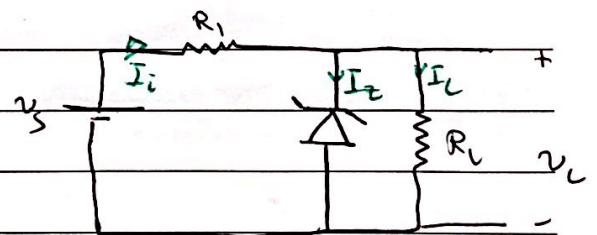Q6) a) $P_{max} = I_{z(max)} v_z$
 $= I_{z(max)} [v_{zth} + r_z I_z]$
 $640 \text{ m} = 6 I_z + 4 I_z^2$
 $I_{z(max)} = 100 \text{ mA}$



$$v_s = 3 \text{ V}, v_{zth} = 6 \text{ V}, r_z = 4 \Omega$$

$$P_{max} = 640 \text{ mWatt}$$

b) $v_s = 3 \text{ V}, v_{zth} = 6 \text{ V}, r_z = 0 \Omega$

حل الامتحان الأول

$$b) V_s = 30 \text{ V}, V_{z1k} = 6 \text{ V}, V_z = 0 \Omega, R_L = 100 \Omega$$
$$I_{z(\min)} = 10 \text{ mA}, I_{z(\max)} = 90 \text{ mA}$$

$$I_i = I_{z(\min)} + I_L \Rightarrow I_L = \frac{6}{100} \text{ mA} \rightarrow \text{constant}$$

$$= 10 \text{ mA} + 60 \text{ mA}$$

$$= 70 \text{ mA}$$

$$\rightarrow R_i = \frac{30 - 6}{70} = \frac{24}{70} \text{ k}\Omega$$

$$I_i = I_{z(\max)} + I_L$$

$$= 150 \text{ mA}$$

$$\rightarrow R_i = \frac{30 - 6}{150} = \frac{24}{150} \text{ k}\Omega$$

$$0.16 \text{ k}\Omega \leq R_i \leq 0.2425 \text{ k}\Omega$$

$$c) 15 \text{ V} \leq V_s \leq 18 \text{ V}, 200 \Omega \leq R_L \leq 600 \Omega$$

$$P_{z(\max)} = I_{z(\max)} V_z$$



$$\rightarrow I_{z(\max)} =$$

$$= 157.5 \text{ mWatt}$$

$$= 26.25 \text{ mA}$$

Tuesday / Dr. Raied Al-Zoabi
 22/3/2015 } continue to clamper circuit

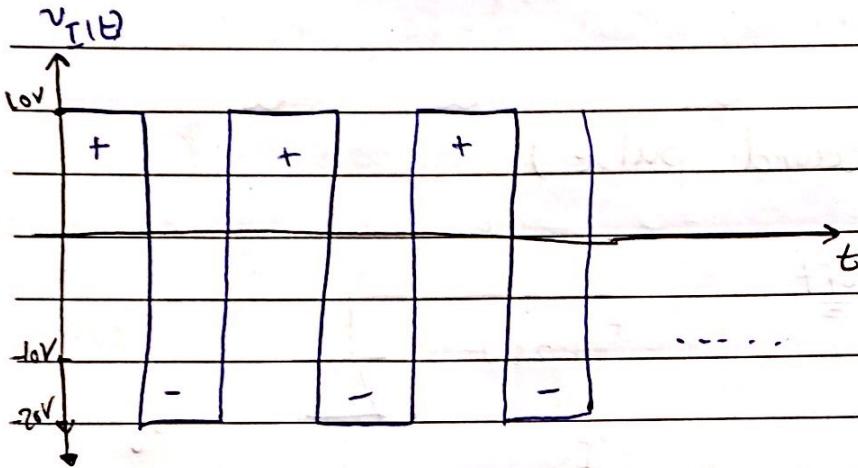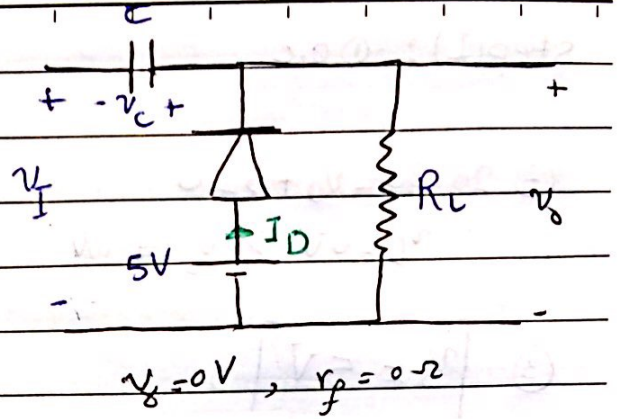EX: Assume $R_L \approx \infty$ to neglect the discharging of the capacitor



transient state

Sol: for $V_I = 10V$ (first pulse) $\Rightarrow V_C = 0V$

$$-10 + V_C - V_D + 5 = 0 \Rightarrow V_D = -5V$$

$\therefore V_D < V_B \Rightarrow$ the Diode is off $\Rightarrow V_o = V_I = 10V$

for $V_I = -20V \Rightarrow$ ① o.c ② $20 + V_C - V_D + 5 \Rightarrow V_D = 25V$

$V_D > V_B \Rightarrow$ Diode is on replace the Diode by $V_B = 0$

\therefore Charging process.

step (2): Find $V_C \Rightarrow -5 + V_C + (-20) = 0 \Rightarrow V_C = 25V$

$$V_C = 25V$$


Replace the capacitor

step(1): ① o.c

② $20 - 25 - v_D + 5 = 0$

$v_D = 0V > V_f \Rightarrow \text{off}$

③ $v_o = 5V$

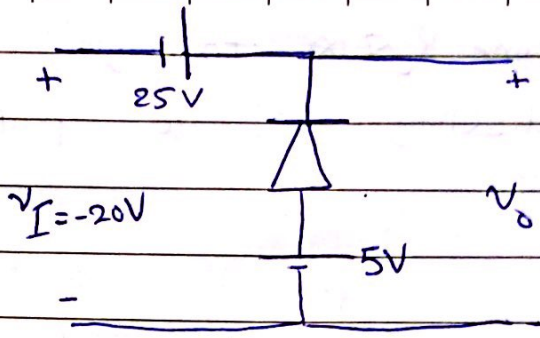


if $v_I = 10V$ (the second pulse)

* Since the Diode is off


$-v_I - 25 + v_o = 0$

$v_o = 10 + 25 = 35V$

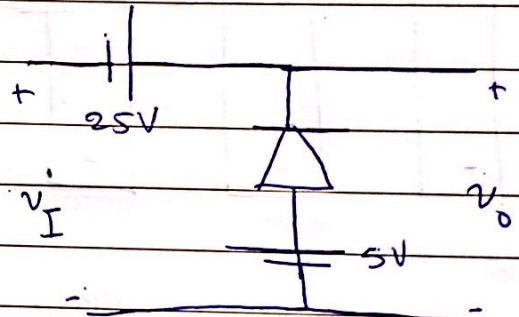

if $v_I = -20V \Rightarrow v_o = 5V$


and continue the same sequence.

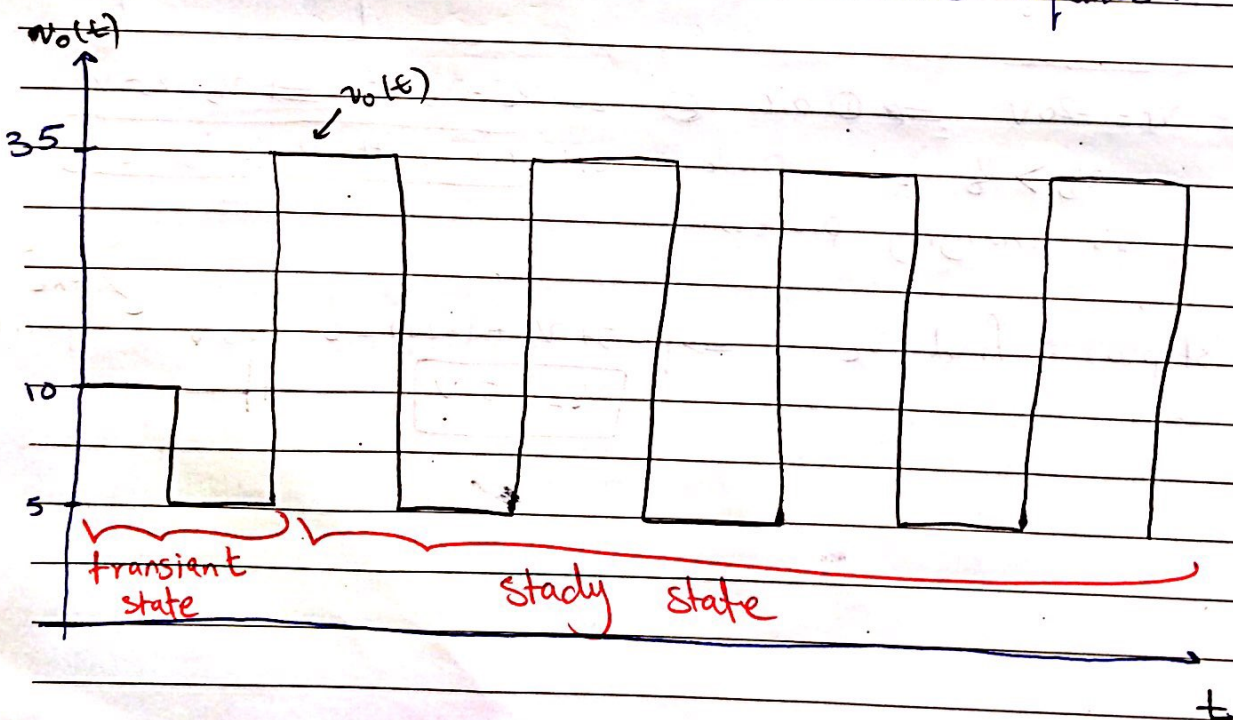

* Multiple diode circuits:-




1) assume Diode is ON

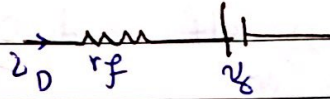

2) find i_D 3) if $i_D > 0 \Rightarrow$ Diode is ON and our assumption is \equiv

4) if $i_D < 0 \Rightarrow$ Diode is off and our assumption not correct.

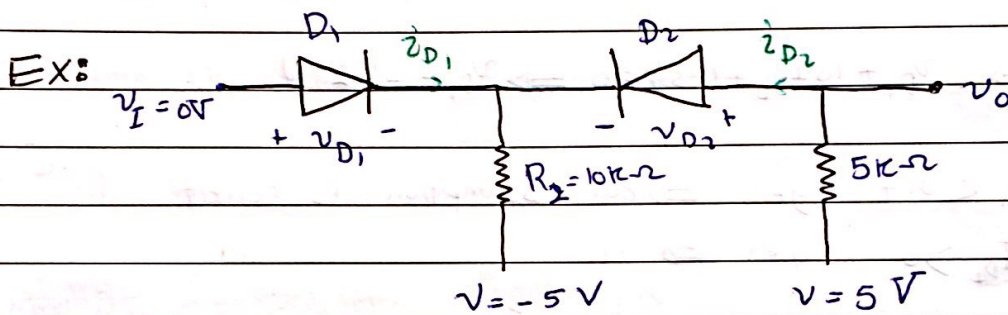

find 1) status of both diodes 2) v_O

* Solution: 1) Assume D_1 is off and D_2 is off

2) find v_{D1} and v_{D2}

$$v_{D1} = 5V$$

3) Check $v_{D1} < v_g$, No \Rightarrow wrong assumption

Since we assumed the diode is off.

\rightarrow followed

→ continue to previous example:-

→ the second assumption:-

3-step
solution

1) assume D_1 is off and D_2 is ON

$$V_{D_2} = 0.7V$$

2) find V_{D_1} and I_{D_2}

$$-5 + 5I_{D_2} + 0.7 + 10I_{D_2} + (-5) = 0 \Rightarrow I_{D_2} = 0.62 \text{ mA} > 0 \checkmark$$

$$\text{find } V_{D_1} \Rightarrow V_{D_1} + 10I_{D_2} + (-5) = 0 \Rightarrow V_{D_1} = -1.2V$$

3) check $V_{D_1} < 0.7$ yes \Rightarrow our assumption is correct

$I_{D_2} > 0$ yes \Rightarrow " " " "

so D_1 is off and D_2 is ON

to find V_o $-5 + 5I_{D_2} + V_o = 0$

$$V_o = 1.9V$$

Ex:


3-step solution (first assumption)

① Assume D_1 is off & D_2 is off

② find v_{D_1} & v_{D_2}



③ $15V > 0.7V$ ∴ wrong assumption

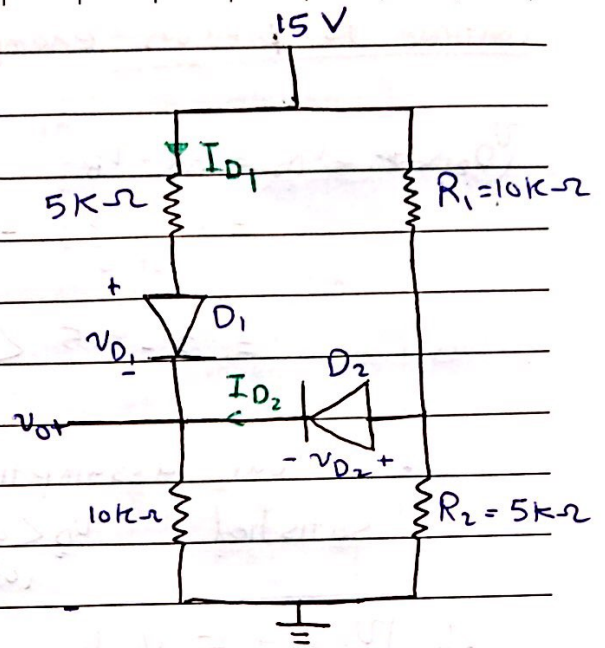

3-step solution (second assumption)

① Assume D_1 is off & D_2 is on

given $v_{D_1} = v_{D_2} = 0.7V$

↓ easier for solving


② find v_{D_1} & I_{D_2}

mesh 1: $0.7 + 10I_1 + 5(I_1 - I_2) = 0$ ①

mesh 2: $-15 + 10I_2 + 5(I_1 - I_2) = 0$ ②

* after solving this system

$I_1 = 0.32 \text{ mA} = I_{D_2} > 0$

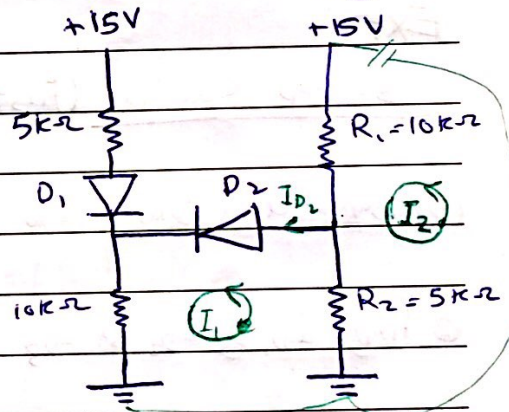

⇒ $v_{D_1} = 15 - 10 * I_{D_2} = 15 - 3.2 > 0.7$ ∴ wrong assumption


3-step solution (third assumption)

① Assume D_1 is on & D_2 is off

② find I_{D_1} & v_{D_2}

KVL: $-15 + 5I_{D_1} + 0.7 + 10I_{D_1} = 0$

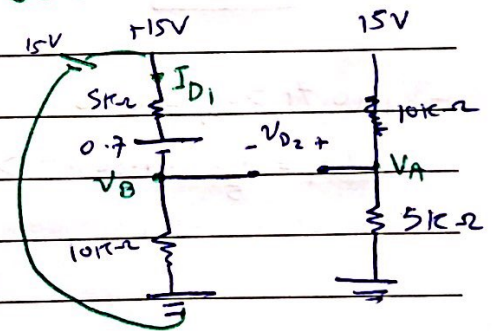$I_{D_1} = 0.45 \text{ mA} > 0$ correct ✓



Continue to previous example (third assumption)

$$V_{D_2} \Rightarrow V_{D_2} = V_A - V_B$$

$$= \frac{-(15)(5)}{5+10} - (0.45)(10)$$

$$= 5 - 4.5 < 0.7 \quad \text{Yes} \checkmark$$

\therefore So our assumption is correct since it's satisfied $V_D < 0.7$ & $I_D > 0$
(off) $V_{D_1} (0.7V)$


$$V_0 = 9.5 \text{ V}$$

Ex:

3-step solution (first assumption)

① Assume all Diodes on

② Find I_{D_1} & I_{D_2} & I_{D_3}

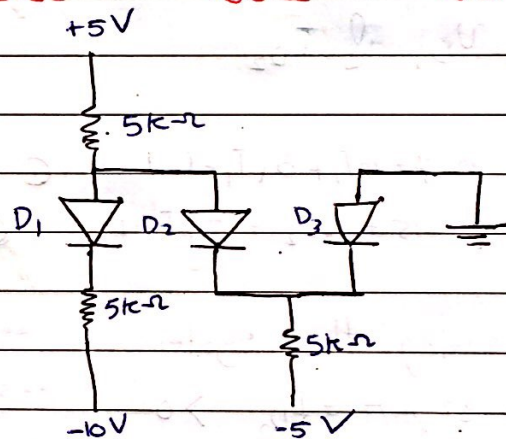


$$I_{D_1} \Rightarrow -V_A + 0.7 - 0.7 = 0$$

$$V_{D_1} = V_{D_2} = V_{D_3} = 0.7 \text{ V}$$

$$V_A = 0 \text{ V}$$

$$-V_A + 0.7 + 5I_{D_1} - 10 = 0$$
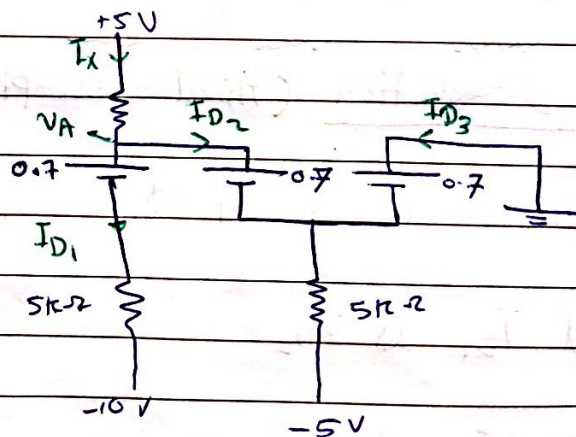
$$I_{D_1} = \frac{9.3}{5} = 1.86 \text{ mA} > 0 \quad \text{Yes} \checkmark$$



$$I_{D_2} \Rightarrow I_{D_2} = I_x - I_1$$

$$= \frac{5-0}{5} - 1.86 < 0 \quad \therefore \text{wrong assumption}$$

3-step solution (second Assumption)

① Assume D_1 is on & D_2 is off & D_3 is on

② find I_{D_1} & V_{D_2} & I_{D_3}

$$I_{D_3} \Rightarrow 0.7 + 5I_{D_3} - 5 = 0$$

$$I_{D_3} = \frac{4.3}{5} > 0 \quad \checkmark$$


$$I_{D_1} \Rightarrow -5 + 5I_{D_1} + 0.7 + 5I_{D_1} - 10 = 0$$

$$I_{D_1} = \frac{14.3}{10} = 1.43 \text{ mA} > 0 \quad \checkmark$$


$$V_{D_2} \Rightarrow -V_{D_2} + 0.7 + 5I_{D_1} - 10 + 5 + 5(-I_{D_3}) = 0$$

$$V_{D_2} = 0.7 + 5(1.43 \text{ m}) - 10 + 5 - 5\left(\frac{4.3}{5} \text{ m}\right) =$$
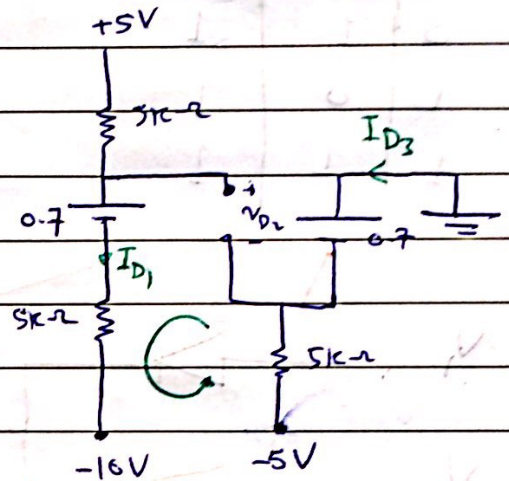
$$V_{D_2} = -1.45 \text{ V} < 0.7 \text{ V} \quad \therefore \text{correct assumption}$$




Sunday | Dr. Raed AL-Zoabi
 27/3/2016 | Diode logic circuit

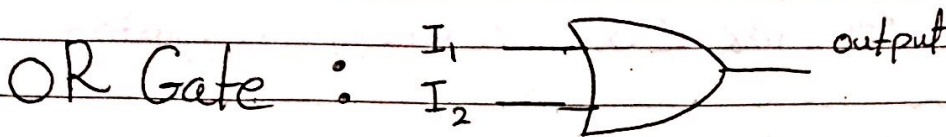

I_1	I_2	output
0	0	0
0	1	1
1	0	1
1	1	1

1: voltage $> 2.5V$

0: voltage $< 2.5V$

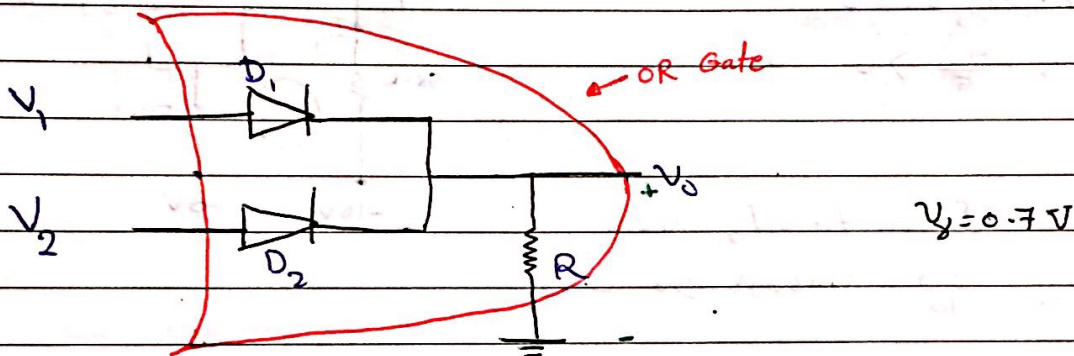


$V_1 (V)$	$V_2 (V)$	D_1	D_2	V_0	logic
0	0	off	off	0V	0
5	0	ON	off	4.3V	1
0	5	off	ON	4.3V	1
5	5	ON	ON	4.3V	1


→ try to Design the NOR Gate 😊

(not OR)

→ followed

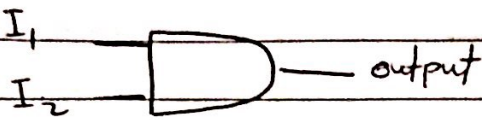
AND Gate : 

I_1	I_2	output
0	0	0
0	1	0
1	0	0
1	1	1

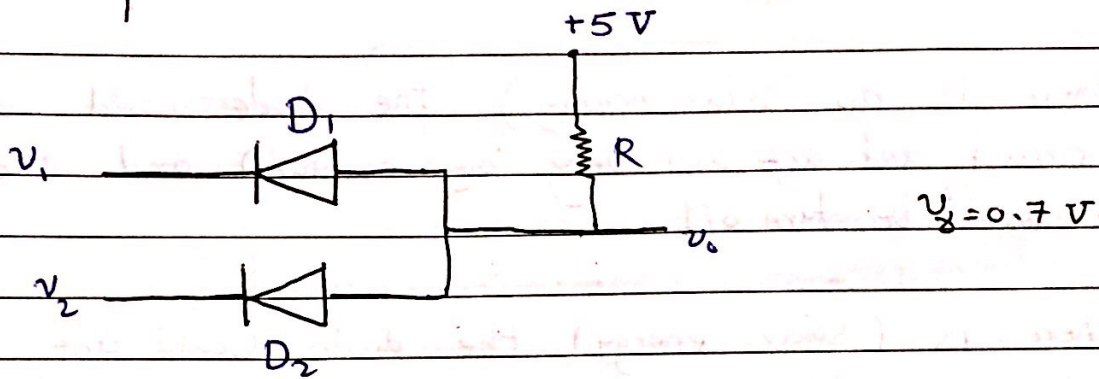

$V_1 (V)$	$V_2 (V)$	D_1	D_2	V_0	logic
0	0	ON	ON	0.7V	0
0	5	ON	off	0.7V	0
5	0	off	ON	0.7V	0
5	5	off	off	5V	1


* Photo diode circuit:-

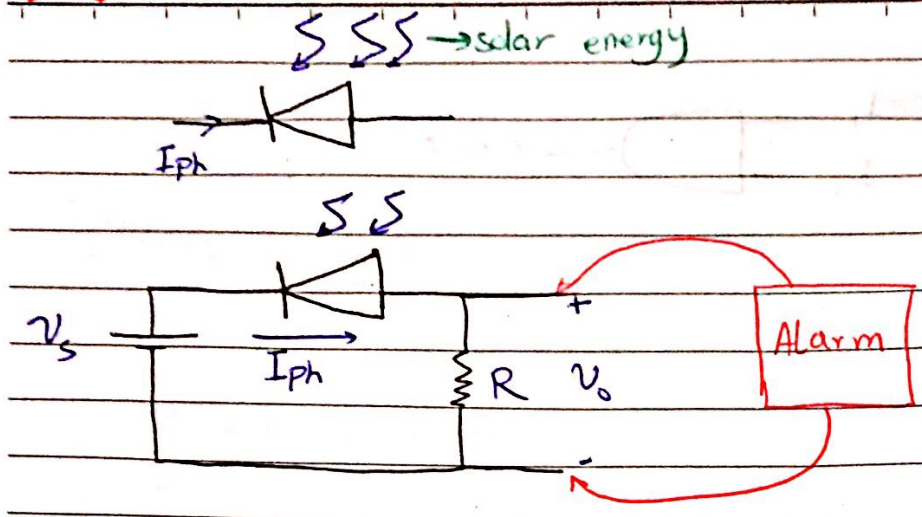

* if there is no (solar energy) the diode would be open circuit and act as (very big resistor) and the alarm would be turn off.

* if there is (solar energy) the diode would act as (short circuit) and will let the current to flow and the alarm would be turned on.

LED Circuit? - (seven-segment display)

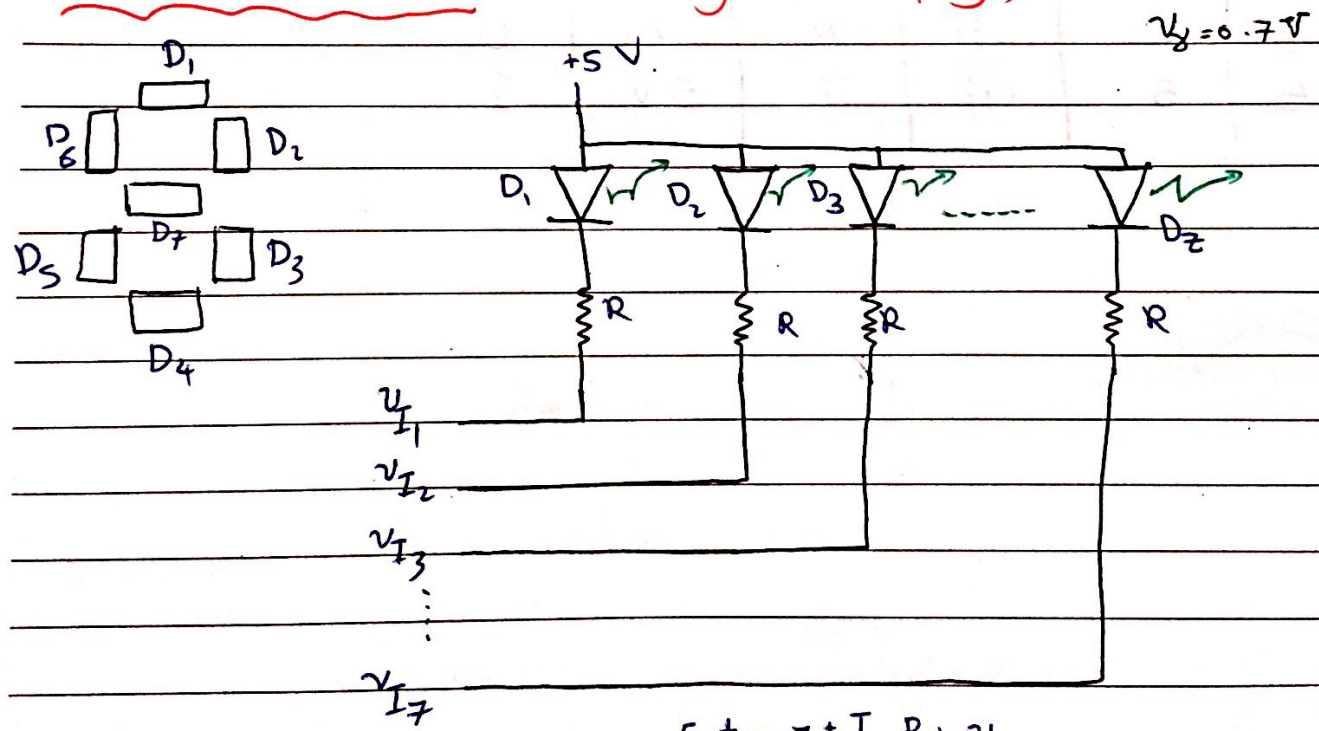

to find the current
to limited to power
Rating

$$-5 + 0.7 + I_D R + V_f = 0$$

$$I_D = \frac{5 + 0.7 - V_f}{R}$$



* Transistor :-

main types :-

① Bipolar Junction Transistor (BJT)


② Field Effect Transistor (FET)

* BJT :-

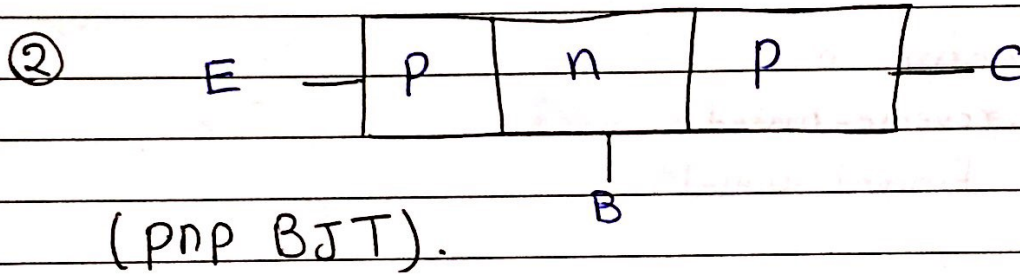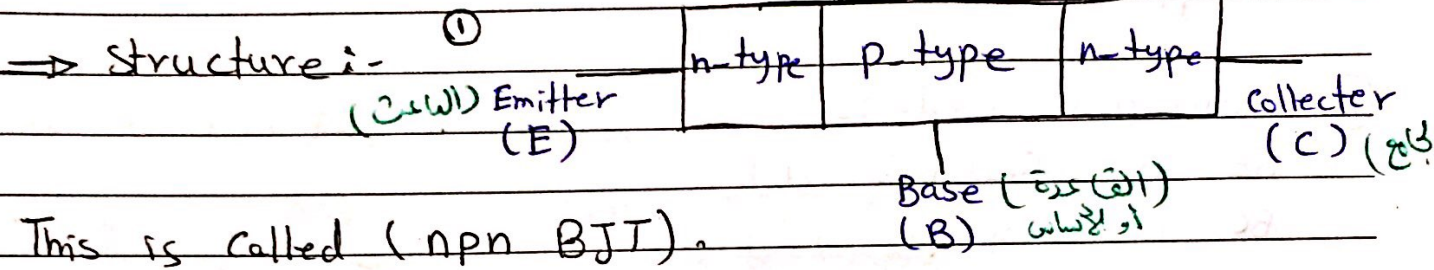

⇒ Symbols :-


nnp ⇒

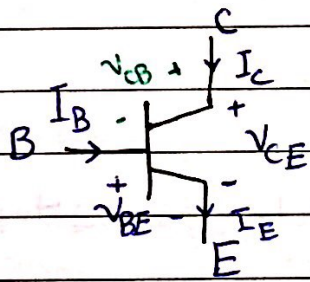

$$I_E = I_B + I_C$$

$$V_{CB} = V_{CE} - V_{BE}$$

pnp ⇒

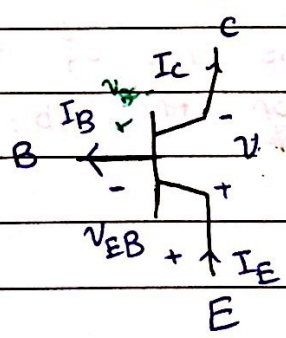

$$I_E = I_B + I_C$$

$$V_{BC} = V_{EC} - V_{EB}$$

* 2 junctions \rightarrow 4 modes of operation.

* Modes of operation for BJT:-

① Forward-active mode:- (active mode)

BE junction is forward-biased.

BC " " Reverse-biased.

(Sometime, we say that the transistor is in the forward-active region)

* application: Amplifiers.

② Saturation mode:-

BE is F.W (Forward).

BC is F.W (Forward).

* application: switch.

③ Inverse-active mode:-

BE is reverse-biased.


BC is Forward-biased.

④ cut off mode.

BE is reverse-biased.

BC " " " "

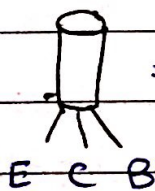* in this mode $\rightarrow I_B = I_C = I_E = 0$ Amperes



\Rightarrow the shape of transistor on the lab.

* Current relationships :- (for npn & pnp)

$\Rightarrow I_E = I_B + I_C$

$\Rightarrow I_C = \beta I_B$ mA \rightarrow mA

β : is the common-emitter current gain and it is a key parameter of the BJT (given in the Data-sheet)

$50 \leq \beta \leq 300$
unitless


$\Rightarrow I_E = I_B + \beta I_B \rightarrow I_E = (1 + \beta) I_B$

$\Rightarrow I_E = \frac{I_C}{\beta} + I_C \rightarrow I_E = \left(\frac{1 + \beta}{\beta} \right) I_C$

$I_C = \left(\frac{\beta}{1 + \beta} \right) I_E$



$I_C = \alpha I_E$ α : common-base current gain.
 \downarrow
 ≈ 0.999

* Current-Voltage characteristics:-


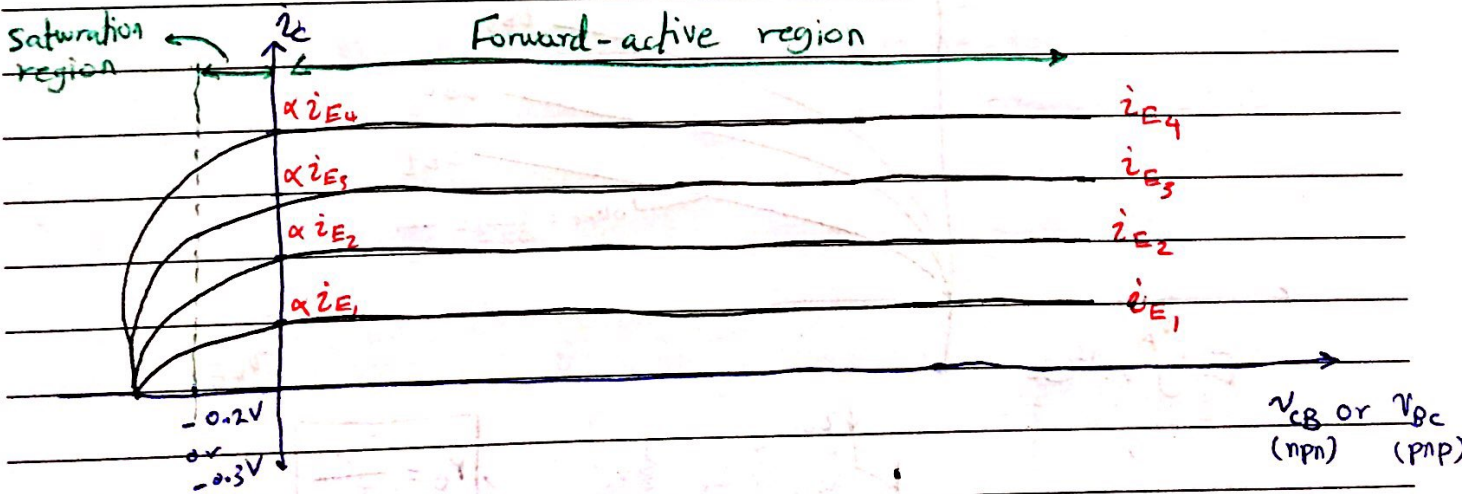


Thursday | Dr. Raed Al-Zoabi
31/3/2016

→ for the ^{previous} graph:-

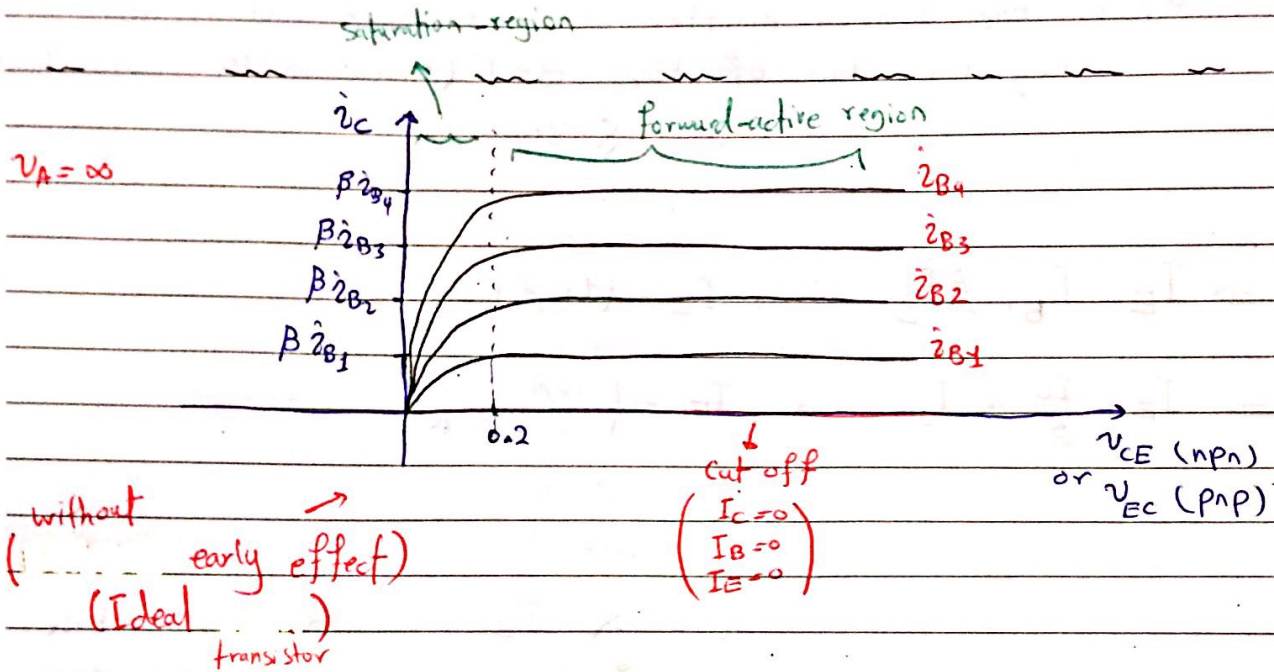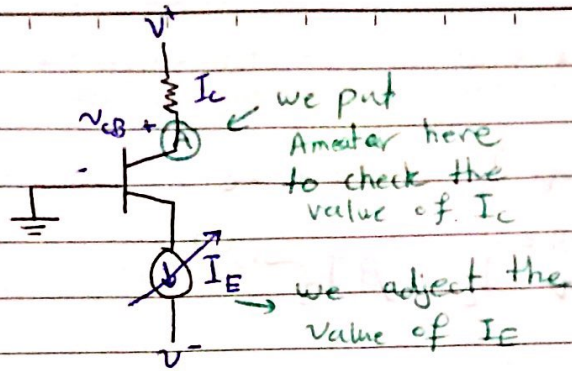

(with early effect)

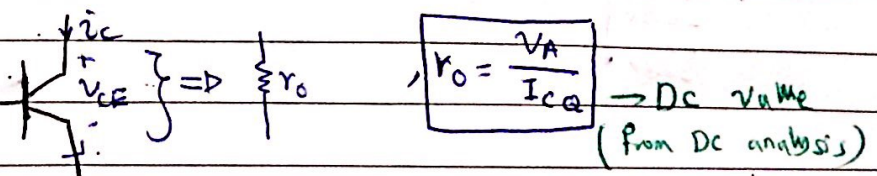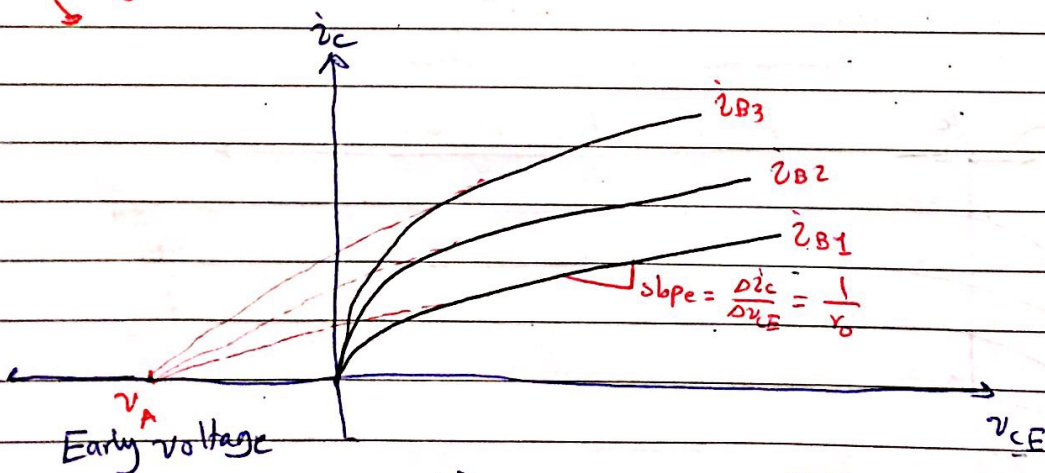

→ without early effect :-

$$I_B = I_S \left(e^{\frac{V_{BE}}{V_T}} - 1 \right)$$

$$I_B \approx I_S e^{\frac{V_{BE}}{V_T}}$$

$$\therefore I_C = \beta I_S e^{\frac{V_{BE}}{V_T}}$$

independent
on V_{CE}

reverse saturation
current

→ with early effect:

$$I_C = \beta I_S e^{\frac{V_{BE}}{V_T}} \left(1 + \frac{V_{CE}}{V_A} \right)$$

depends
on V_{CE}

$$* r_o = \frac{V_A}{I_{CQ}}$$


→ used also on AC analysis.

DC value


(from DC analysis of the circuit)

منسرب
* Leakage currents :-

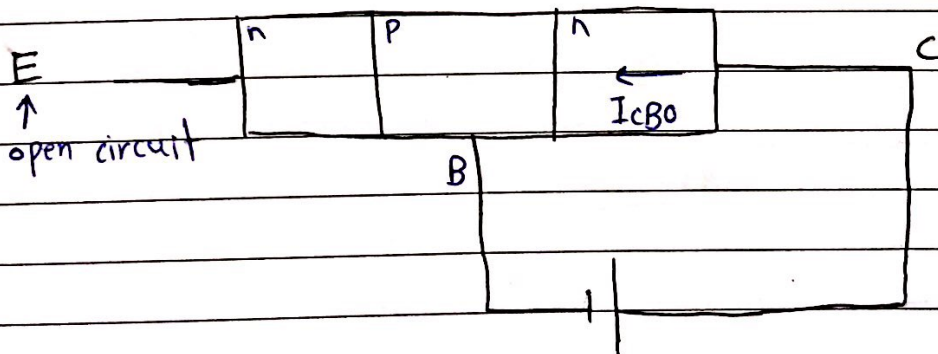I_{CBO} : is the collector leakage current in the common base configuration when the emitter is open circuit




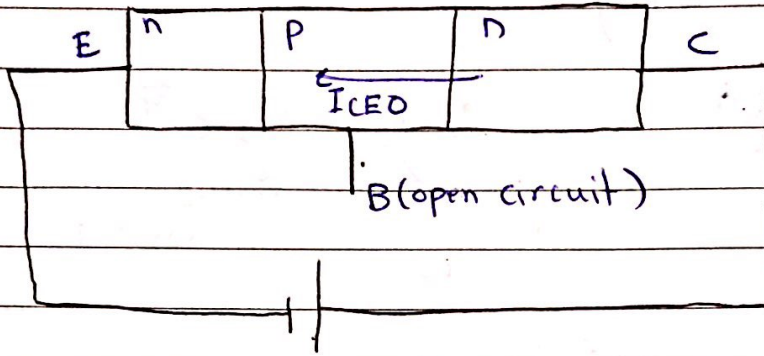I_{CEO} : is the emitter leakage current when the Base is open circuit.




$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} = \beta I_{CBO}$$

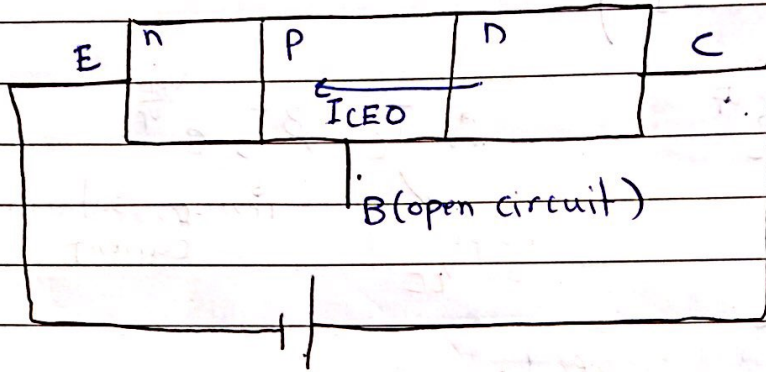I_{CEO} is the emitter leakage current when the Base is open circuit.




$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} = \beta I_{CBO}$$

* Break-down voltages:-

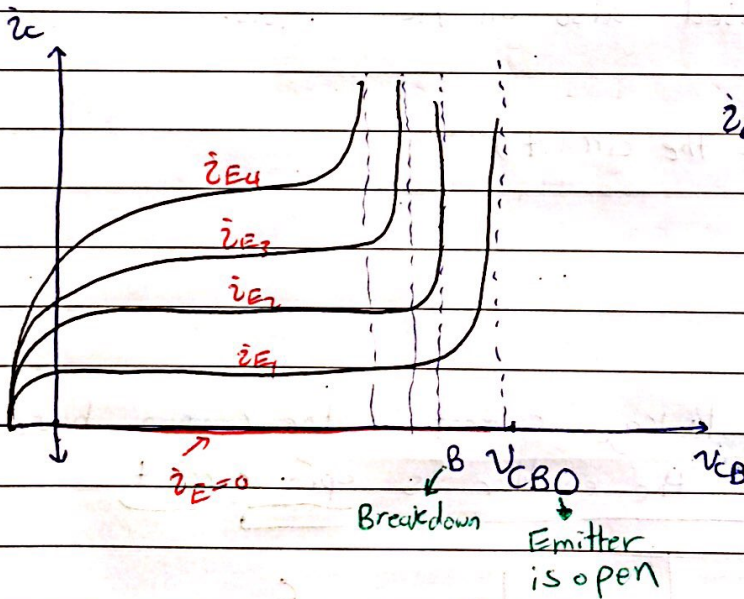

$$V_{E4} > V_{E3} > V_{E2} > V_{E1} > V_{E0}$$
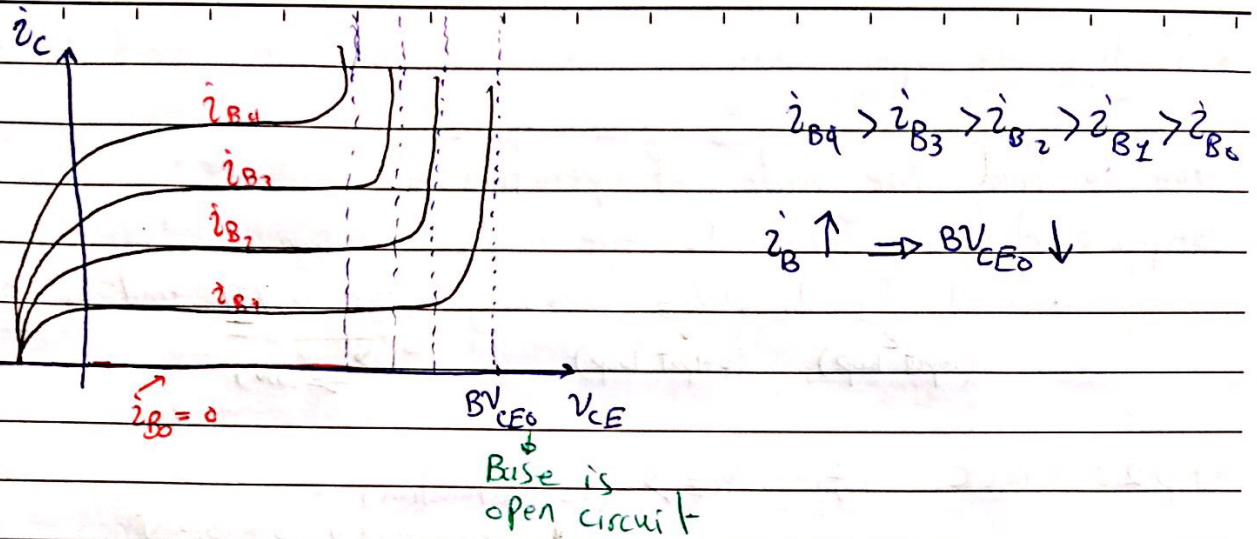
$$V_E \uparrow \Rightarrow V_{CBO} \downarrow$$



* $BV_{CEO} = \frac{BV_{CBO}}{\sqrt{\beta}}$, n is an empirical constant usually in the range of 3 to 6

* DC analysis of BJT circuit:-

we will study the following topics:-

- ① modes of operation.
- ② load-line and Q-point values. ($I_c \propto V_{EC}$)
- ③ Voltage transfer characteristic ($V_o \propto V_I$)
- ④ Biasing (controlling the Q-point position)
- ⑤ Applications of BJT:-
 - A] switch (small size & high speed & no need of maintenance)
 - B] Amplifiers.
 - C] logic circuits.

* Modes of operation:

How to find the mode of operation:-

step 1: * Assume forward-active mode.

* Find I_B , I_C , V_{CE} using $V_{BE} = 0.7V$ and $I_C = \beta I_B$
(input loop) (output loop) $V_{BE(ON)}$

step 2: check if $V_{CE} > V_{CE(saturation)}$
 \downarrow given 0.2V or 0.3V
 \therefore our assumption is correct.

step 3: otherwise, assume saturation mode.

\Rightarrow use $V_{BE} = 0.7V$ and $V_{CE} = V_{CE(saturation)}$
 \downarrow \downarrow
 $V_{BE(ON)}$ 0.2V or 0.3V

\Rightarrow find I_B & I_C
(input loop) (output loop)

step 4: check if $I_C < \beta I_B$, then our assumption is correct.

step 5: otherwise, the mode of operation is cut-off
 $I_C = I_B = I_E = 0$


Example: Find the mode of operation Given $V_{CE(sat)} = 0.2 \text{ V}$

$$\beta = 100, \quad V_{BE(on)} = 0.7 \text{ V}$$

Sol: \Rightarrow BJT

\Rightarrow npn

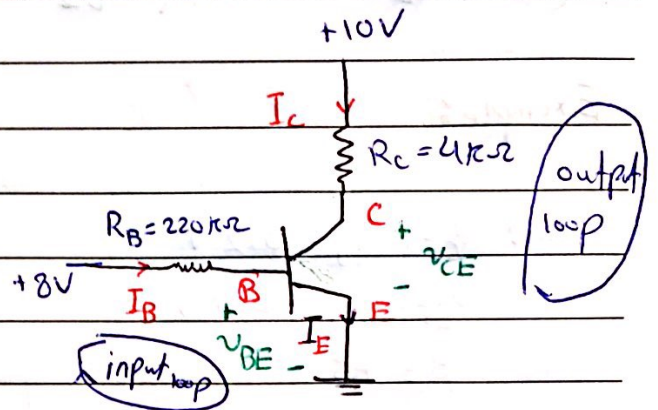\Rightarrow step 1: assume forward-active



input loop: (KVL)

$$-8 + 220 I_B + 0.7 = 0$$

$$\Rightarrow I_B = \frac{8 - 0.7}{220} = 33.2 \mu\text{A}$$

$$\Rightarrow I_C = \beta I_B = 3.32 \text{ mA}$$

output loop: (KVL)

$$-10 + 4 I_C + V_{CE} = 0$$

$$V_{CE} = 10 - 4(3.32) = -3.28 \text{ V}$$

\Rightarrow step 2: check $V_{CE} > V_{CE(sat)}$, No

\therefore our assumption is wrong.

\Rightarrow step 3: assume saturation mode $V_{BE} = 0.7$, $V_{CE} = V_{CE(sat)} = 0.2 \text{ V}$

\Rightarrow input loop: $I_B = 33.2 \mu\text{A}$


\Rightarrow output loop: (KVL) $-10 + 4 I_C + 0.2 = 0 \Rightarrow I_C = \frac{10 - 0.2}{4} = 2.45 \text{ mA}$

\Rightarrow step 4: - $I_C < \beta I_B$, yes: saturation mode.
 $2.45 \text{ mA} \quad 3.32 \text{ mA}$

* load line and Q-point values (Quiescent point) :-
 operation mode
 ($I_C \propto V_{CE}$) (I_{BQ}, I_{CQ}, V_{CEQ})

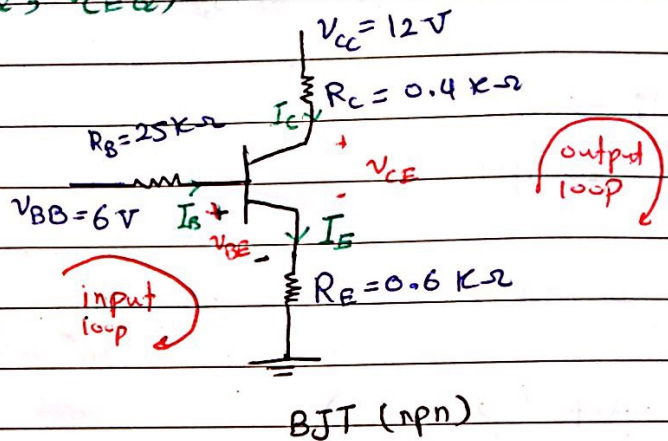Example:

Given: $V_{CE(sat)} = 0.2 V$
 $V_{BE(on)} = 0.7 V$
 $\beta = 75$



BJT (npn)

- Find the mode of operation.
- Find the Q-point values.
- Find and draw the load line.
- Find the power dissipated by transistor.

Sol: a) Step 1: assume F.w ($V_{BE} = V_{BE(on)} = 0.7 V$, $I_C = \beta I_B$)

input loop :-

$$-6 + 25I_B + 0.7 + 0.6 \frac{I_C}{(1+\beta)} = 0 \Rightarrow I_B = 75.1 \mu A$$

$$\Rightarrow I_C = \beta I_B = 5.63 \text{ mA}$$

output loop :-

$$-12 + 0.4 \frac{I_C}{5.63 \text{ mA}} + V_{CE} + 0.6 \frac{I_C}{(1+\beta)} = 0 \Rightarrow V_{CE} = 6.32 V$$

step 2: check $V_{CE} > V_{CE(sat)}$? \Rightarrow yes, the mode of operation is Forward-active

b) $I_{BQ} = 75.1 \mu A$, $I_{CQ} = 5.63 \text{ mA}$, $V_{CEQ} = 6.32 V$

c) load line $I_C \propto V_{CE}$


outloop :-

$$-12 + 0.4 I_C + V_{CE} + 0.6 \frac{I_C}{\alpha} = 0 \Rightarrow -12 + 0.4 I_C + V_{CE} + \frac{0.6 I_C}{\alpha} = 0$$

$$I_C = \alpha I_E$$

$$\alpha = \frac{\beta}{1+\beta} = 0.99$$

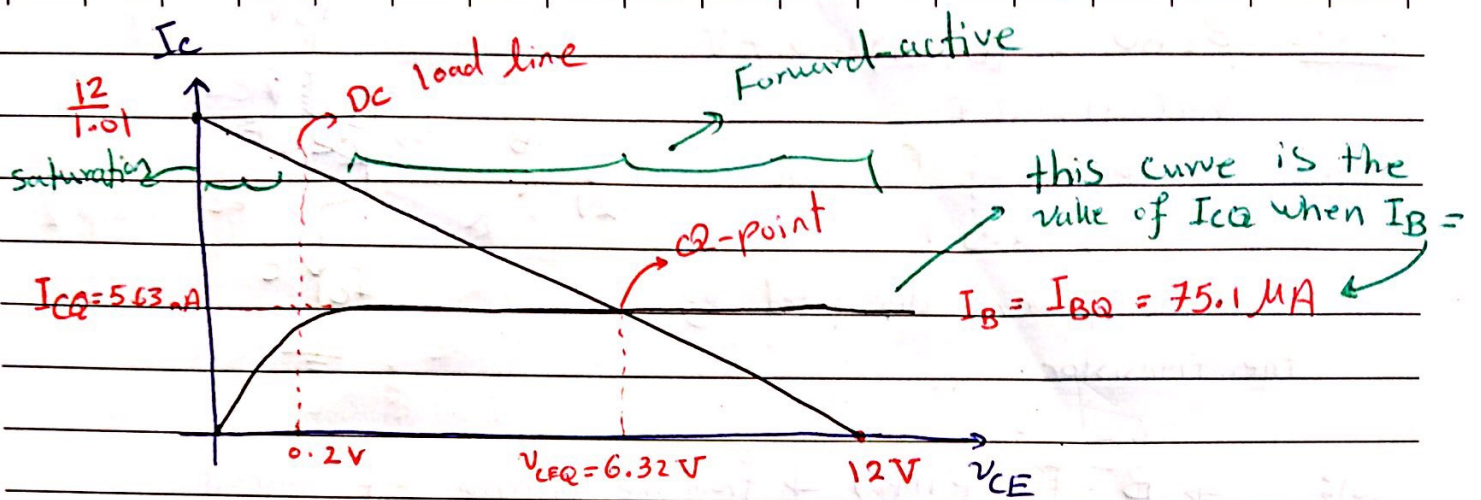$I_C = \frac{12}{1.01} - \frac{V_{CE}}{1.01}$



$$I_c = \frac{12}{1.01} - \frac{V_{CE}}{1.01}$$

slope

→ General KVL for output loop:-

$$-12 + R_c I_c + V_{CE} + \frac{R_E}{\alpha} I_c = 0 \Rightarrow \underbrace{\left(R_c + \frac{R_E}{\alpha} \right)}_{\approx R_c + R_E} I_c = 12 - V_{CE}$$

$$I_c = \frac{12}{R_c + R_E} - \frac{V_{CE}}{R_c + R_E}$$

→ to make Q-point at the saturation region at fixed I_B
we have to increase R_c and/or decrease V_{CC} (from graph)

→ to make Q-point at the saturation region by changing the value of I_B , we can increase V_{BB} and/or decrease R_B

d) the power dissipated on the transistor by this relation

$$P_T = I_B V_{BE} + I_C V_{CE} \Rightarrow P_T \approx I_C V_{CE}$$

$$\approx (5.63 \times 10^{-3})(6.32) = 35.58 \text{ mWatt}$$

Thursday
8/4/2016


Dr. Kaed AL-zoabi

EX:- $\beta = 60$, $V_{EB(on)} = 0.7V$

$V_{EC(sat)} = 0.2V$

a) Find the value of R such that $V_{ECQ} = 2.5V$

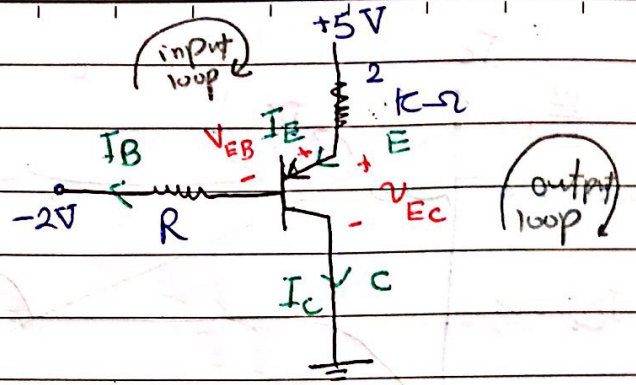b) Find the power dissipated by the transistor.



Sol: \Rightarrow BJT (PNP) \Rightarrow From the direction of current

a) \Rightarrow as $V_{ECQ} > V_{EC(sat)}$ \Rightarrow Forward active mode

\Rightarrow output loop: $-5 + 2I_E + 2.5 = 0$

$I_E = \frac{5 - 2.5}{2 \times 10^3} A = 1.25 mA$

$\therefore I_B = \frac{I_E}{1 + \beta} = 0.0265 mA$

\Rightarrow Input loop: $-5 + 7I_E + 0.7 + RI_B - 2 = 0$

$R = 125 k\Omega$


b) $P_T = I_C V_{EC} = 3.075 mW$ \Rightarrow (ممكن يكون خطا في الأرقام، تأكد!)

c) DC load line :- $I_C \propto V_{EC}$

$-5 + 2I_E + V_{EC} = 0$ (from output loop)


$-5 + \frac{2I_C}{\alpha} + V_{EC} = 0 \Rightarrow \frac{2}{\alpha} I_C = 5 - V_{EC} \Rightarrow I_C = \frac{\alpha}{2} (5 - V_{EC})$

$I_C = 2.47 - 0.49 V_{EC}$

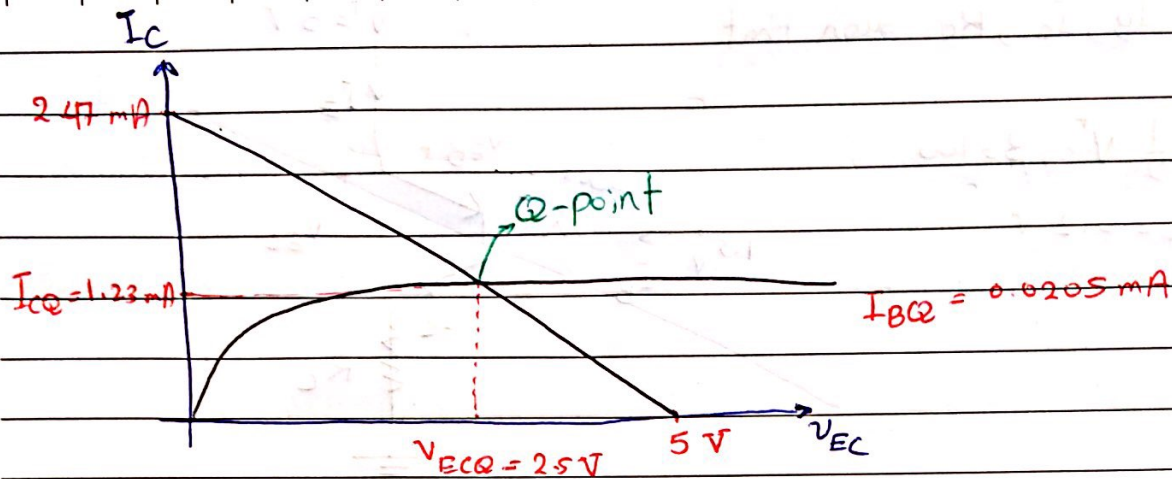

Ex: Find I_B, I_C, I_E, V_{CE}

Given

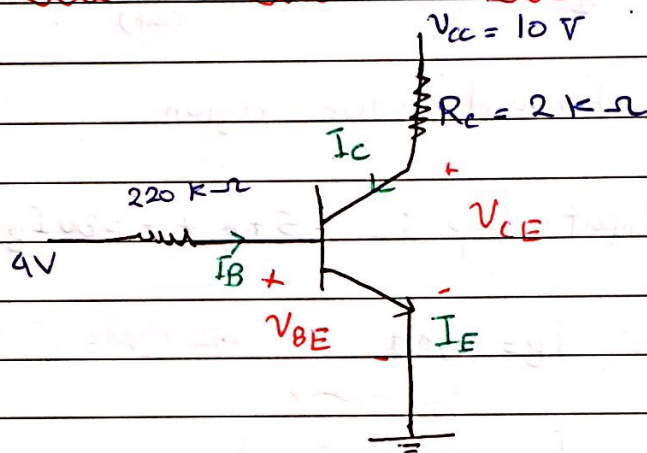

$\beta = 200, V_{BE(\text{on})} = 0.7 \text{ V}$

$V_{CE(\text{sat})} = 0.2 \text{ V}$

Sol: First, we find the mode of operation.

⇒ Assume F.W :-

⇒ Input loop :- $-4 + 220 I_B + 0.7 = 0 \Rightarrow I_B = \frac{4 - 0.7}{220 \times 10^3} = 15 \mu\text{A}$

∴ $I_C = \beta I_B = 3 \text{ mA}$

⇒ output loop :- $-10 + 2 I_C + V_{CE} = 0 \Rightarrow V_{CE} = 4 \text{ V} > V_{CE(\text{sat})}$

∴ since $V_{CE} > V_{CE(\text{sat})}$, Forward-active region (mode)


So, $I_B = 15 \mu\text{A}, I_C = 3 \text{ mA}, I_E = I_C + I_B = 3.015 \text{ mA}$

$V_{CE} = 4 \text{ V}$

EX: Find I_B , I_C , R_C such that

$$V_{EC} = \frac{1}{2} V^+, \beta = 100$$

$$V_{EC} = 0.2 \text{ V}$$

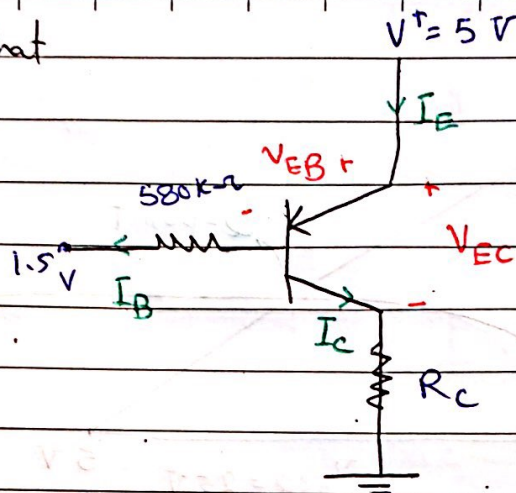

$$\text{Sol: } V_{EC} = \frac{1}{2} \times 5 = 2.5 > V_{EC(\text{sat})}$$

∴ Forward active region

$$\Rightarrow \text{Input loop: } -5 + 0.7 + 580 I_B + 1.5 = 0$$

$$\therefore I_B = 5 \mu\text{A}$$

$$\therefore I_C = \beta I_B = 0.5 \text{ mA}$$

$$\Rightarrow \text{output loop: } -5 + 2.5 + R_C I_C = 0$$

$$\therefore R_C = 5 \text{ k}\Omega$$

11/4/2016
Sunday


Dr. Raed Al-Zoabi

EX:

Find R_c & R_E given that

$$I_{EQ} = 0.5 \text{ mA}, V_{ECQ} = 4 \text{ V}$$
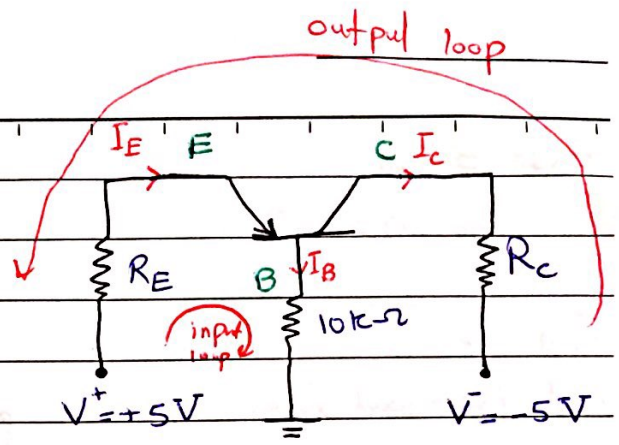
$$\beta = 120, V_{BE(on)} = 0.7 \text{ V}$$



$$\text{Sol: } I_{BQ} = \frac{I_{EQ}}{1 + \beta} = \frac{0.5 \text{ mA}}{121} = 4 \mu\text{A}$$

$$I_{CQ} = \beta I_{BQ} = 0.49 \text{ mA}$$

\therefore since $V_{ECQ} > 0 \Rightarrow$ Forward active


$$\text{Input loop: } -5 + R_E I_E + 0.7 + 10 * I_B = 0$$
$$R_E = 8.52 \text{ k}\Omega$$

$$\text{output loop: } -5 + R_E I_E + V_{EC} + R_C I_C - 5 = 0$$
$$R_C = 3.51 \text{ k}\Omega$$

Ex: $\beta = 100$

$V_{BE(on)} = 0.7 \text{ V}$

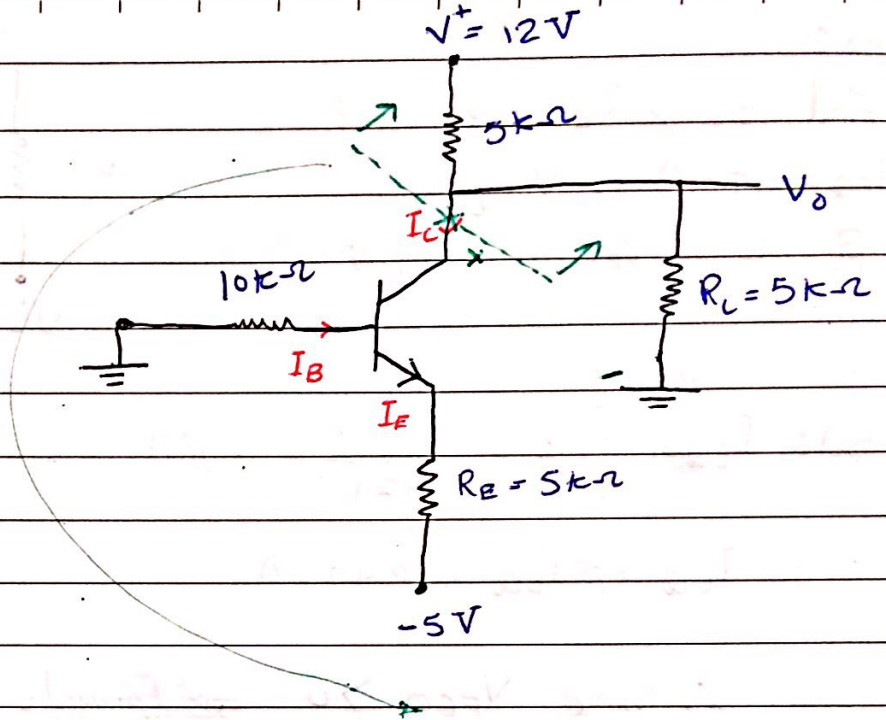Find the Q-point values and the load line.




$V_{th} = V_{oc}$

KVL: $-12 + 5I + 5I = 0$

$I = \frac{12}{10} = 1.2 \text{ mA}$

$V_{th} = V_{oc} = I R_L = 6 \text{ V}$

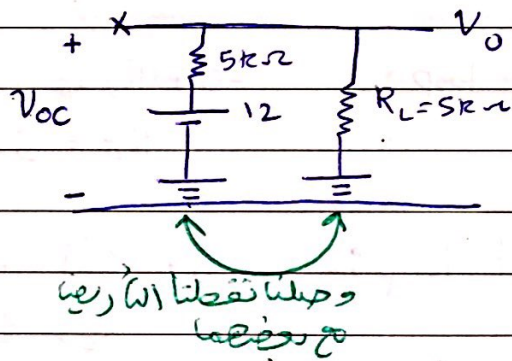

R_{th} , after killing the source

$5 // 5 = 2.5 \text{ k}\Omega$


→ Assume F.w

Input loop: $(1 + \beta) I_B$

$0 + 10 I_B + 0.7 + 5 I_E - 5 = 0$

→ $I_B = 8.35 \text{ mA}$

→ $I_C = \beta I_B = 0.835 \text{ mA}$

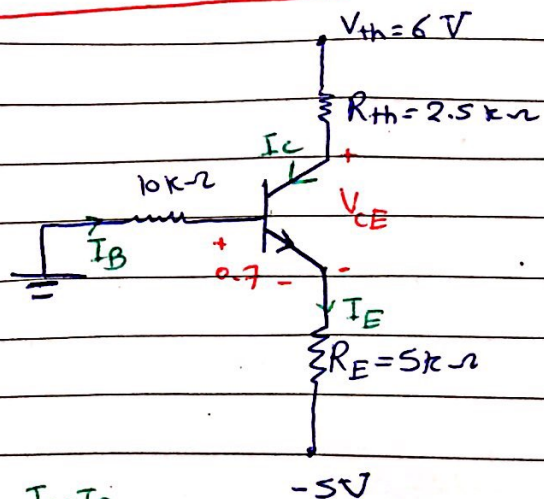

output loop: $-6 + 2.5 I_C + V_{CE} + 5 I_E - 5 = 0$

$V_{CE} = 4.7 \text{ V} > V_{CE(sat)}$ ∴ Forward-active

$$\rightarrow I_{BQ} = 8.35 \mu A, I_{CQ} = 0.835 \text{ mA}, V_{CEQ} = 4.7 \text{ V}$$

\rightarrow load line ($I_C \propto V_{CE}$)

$$-6 + 2.5 I_C + V_{CE} + 5 \frac{I_C}{\alpha} - 0.5 = 0$$


$$I_C = \frac{11}{7.55} - \frac{V_{CE}}{7.55}$$

How to Find the relationship between v_o & v_i

EX: $\beta = 120, V_{BE(on)} = 0.7 \text{ V}$

$V_{CE(sat)} = 0.2 \text{ V}$

$V_A = \infty \rightarrow v_o = \infty$

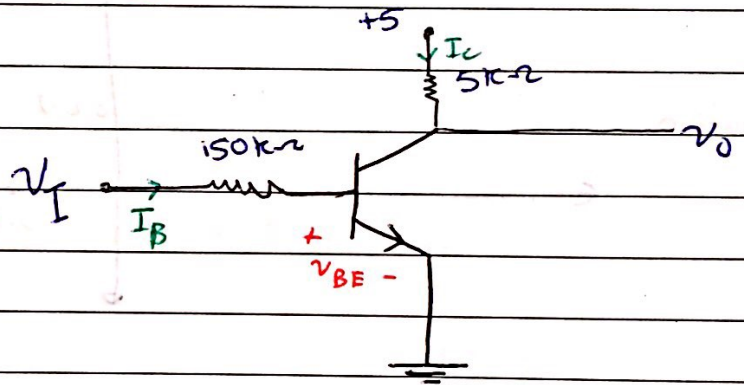

Draw v_o Vs v_i

Sol: \Rightarrow cutoff mode :- $I_C = I_B = I_E = 0 \text{ A} \rightarrow v_o = 5 \text{ V}$

\Rightarrow saturation mode :- $V_{CE} = V_{CE(sat)} = 0.2 \rightarrow v_o = 0.2 \text{ V}$

\Rightarrow Forward-active mode :- $V_{BE} = 0.7 \text{ V}, I_C = \beta I_B$

\rightarrow Input loop:-

$$-v_i + 150 I_B + 0.7 = 0 \Rightarrow I_B = \frac{v_i - 0.7}{150} \text{ mA}$$


$$\Rightarrow I_C = \beta I_B = (120) \frac{v_i - 0.7}{150} \text{ mA}$$

\rightarrow output loop:-


$$-5 + 5 I_C + v_o = 0$$

$$v_o = 5 - 5 I_C$$
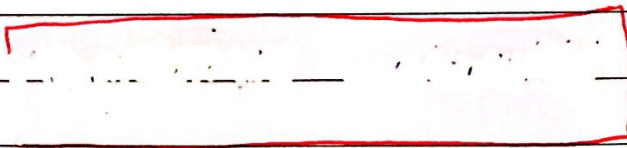
$$v_o = 5 - 5I_c \Rightarrow v_o = 5 - 5 \left(\frac{120}{150} \frac{v_I - 0.7}{150} \right)$$




$$v_o = 7.8 - 4v_I$$

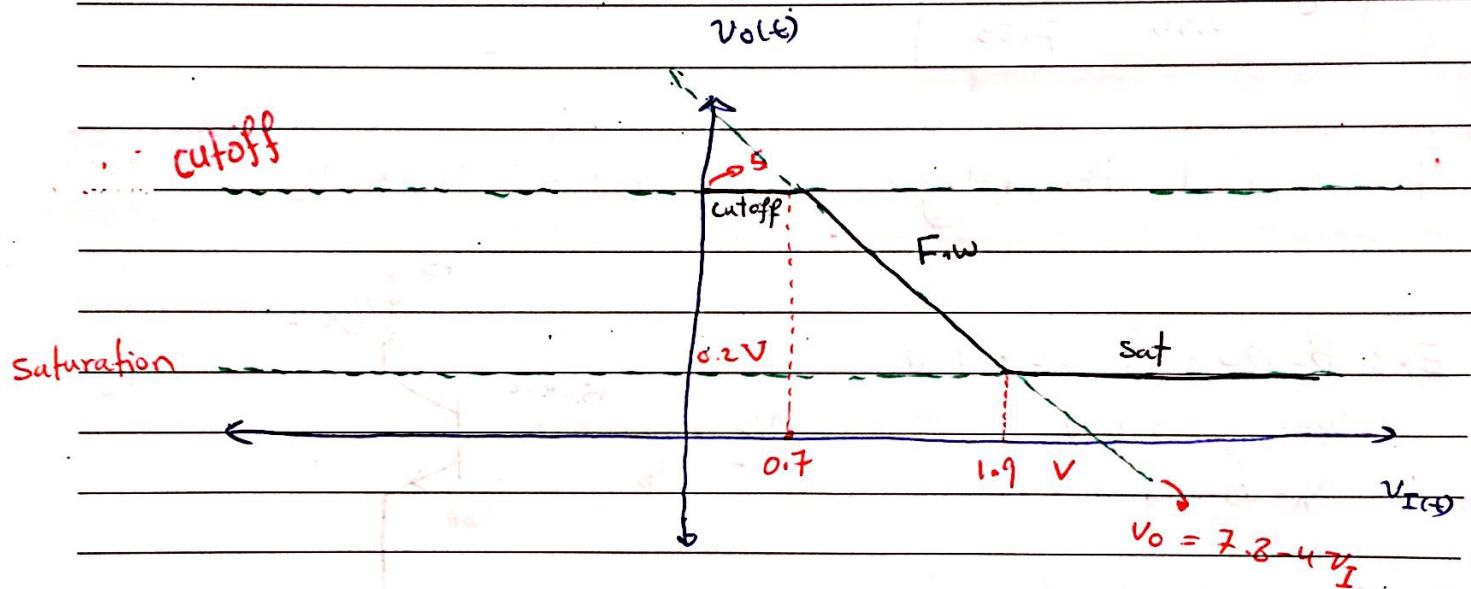

17/4/2016 | Dr. Ra'ed AL-Zoabi
 Sunday

Ex: Draw v_o & v_i

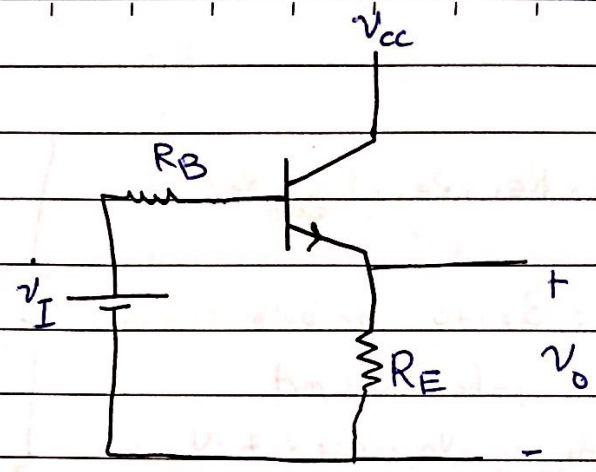

Sol: cut off :- $I_B = I_C = I_E = 0A \Rightarrow v_o = 0V$


Saturation :- $V_{CE} = V_{CE(sat)} \Rightarrow -v_{cc} + V_{CE(sat)} + v_o = 0$
 $v_o = v_{cc} - V_{CE(sat)}$

Forward active mode :-

Input loop :- $-v_i + I_B R_B + 0.7 + (1 + \beta) I_B R_E = 0$

$I_B = \frac{v_i - 0.7}{R_B + (1 + \beta) R_E} \Rightarrow v_o = (1 + \beta) I_B R_E$

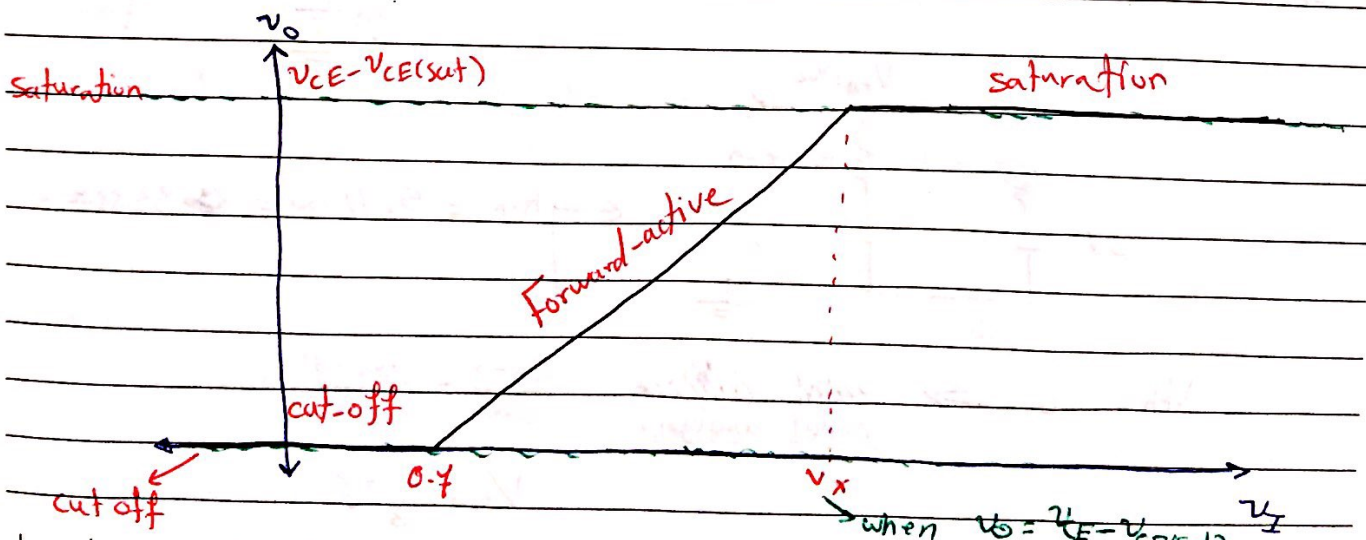$v_o = (1 + \beta) R_E \frac{(v_i - 0.7)}{R_B + (1 + \beta) R_E} = \frac{(1 + \beta) R_E v_i}{R_B + (1 + \beta) R_E} - \frac{(1 + \beta) R_E \cdot 0.7}{R_B + (1 + \beta) R_E}$



Ex:

Find, R_{E1} , R_{E2} , R_{C1}

Given: $\beta = 100$ for both transistors


$I_{C1} = I_{C2} = 0.8 \text{ mA}$

$V_{B1(ON)} = V_{B2(ON)} = 0.7 \text{ V}$


$V_{CE1} = 3.5 \text{ V}$

$V_{CE2} = 2 \text{ V}$



Forward active

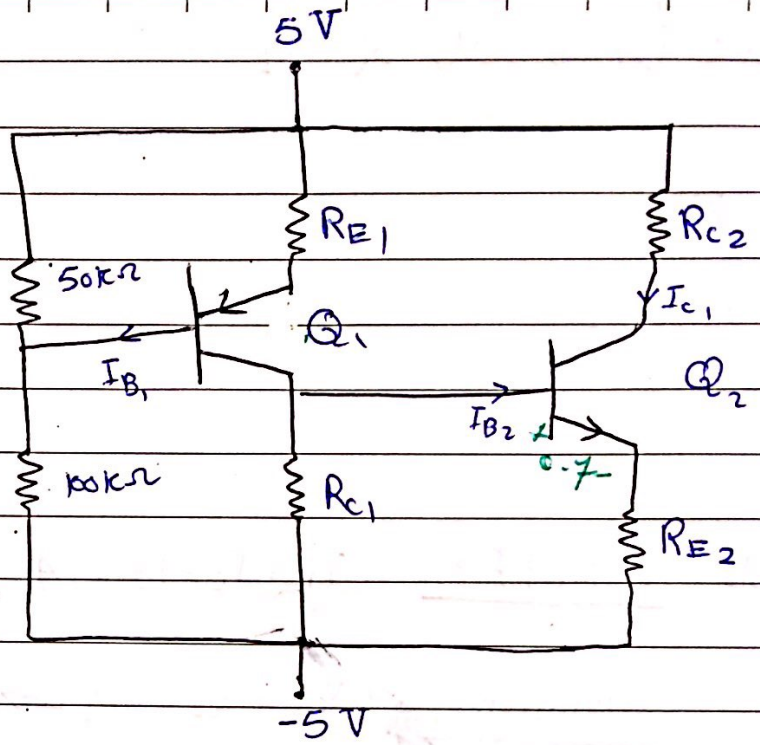

Sol:

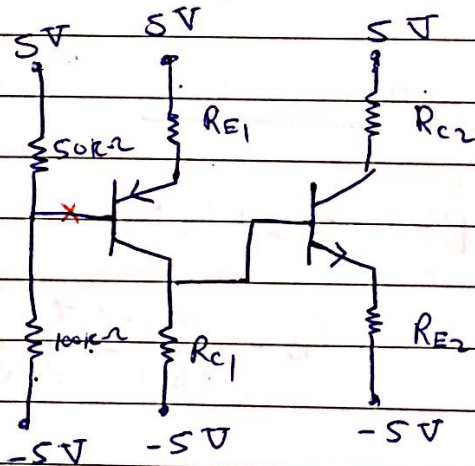

⇒ Find thevenin equivalent at point X

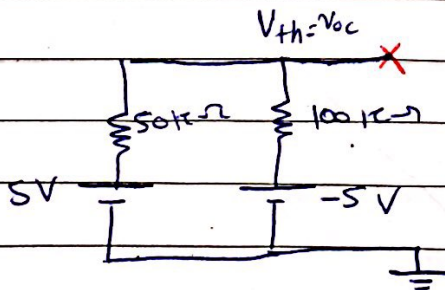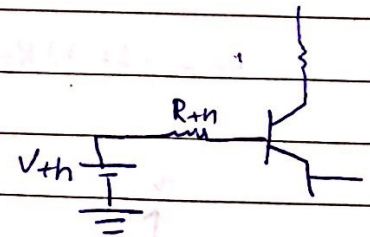


$R_{th} = 50 \parallel 100 = 33.33 \text{ k}\Omega$

$V_{th} = V_{oc} \Rightarrow$

Nodal analysis

$\frac{V_{th} - 5}{50k} + \frac{V_{th} + 5}{100k} = 0$

$V_{th} = \frac{5}{3} \text{ V}$

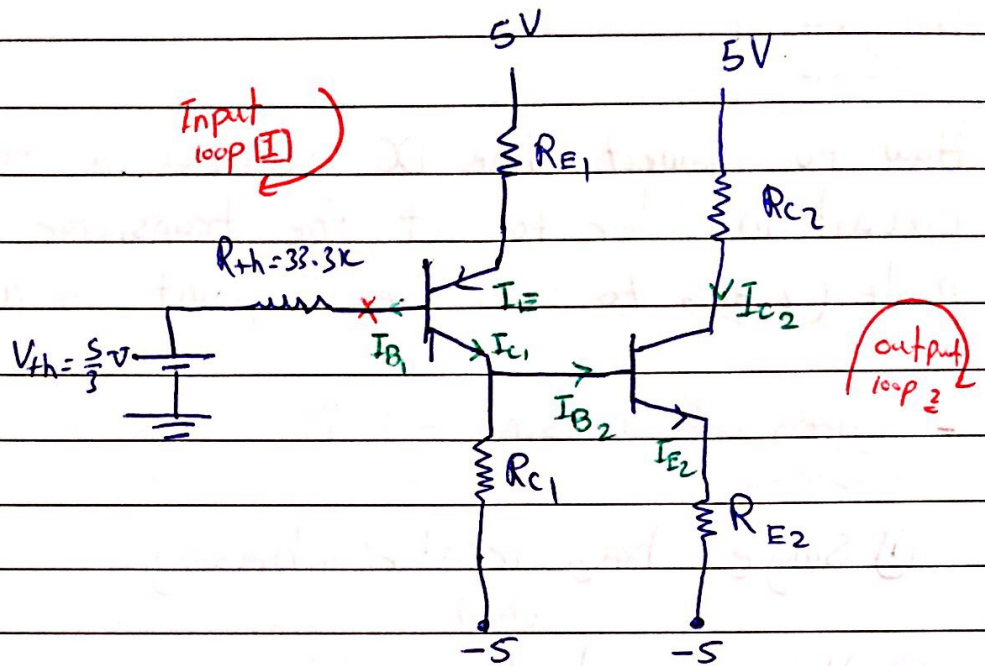

$$I_{B1} = \frac{I_{C1}}{\beta} = 8 \mu A, \quad I_{B2} = \frac{I_{C2}}{\beta} = 8 \mu A, \quad I_{E1} = (1 + \beta) I_{B1} = 0.808 \text{ mA}$$

$$I_{E2} = (1 + \beta) I_{B2} = 0.808 \text{ mA}$$

* Input loop 1 :- $-5 + R_{E1} I_{E1} + 0.7 + 33.33 I_{B1} + V_{th} = 0$

$$R_{E1} = 2.93 \text{ k}\Omega$$

* output loop 1 :- $-5 + I_{E1} R_{E1} + V_{CE1} + (I_{C1} - I_{B2}) R_{C1} - 5 = 0$

$$R_{C1} = 5.215 \text{ k}\Omega$$

* Input loop 2 :- $-(-5) - R_{C1} (I_{C1} - I_{B2}) + 0.7 + I_{E2} R_{E2} - 5 = 0$

$$R_{E2} = 4.25 \text{ k}\Omega$$

* output loop 2 :- $-5 + I_{C2} R_{C2} + V_{CE2} + I_{E2} R_{E2} - 5 = 0$

$$R_{C2} = 3.215 \text{ k}\Omega$$

Biassing:-

⇒ How to connect the DC sources in the transistor circuit in order to set the transistor in a certain mode (i.e., to set the Q-point in a certain region)

- Types of biassing:-



① Single base-resistor biassing.
(R_B)

② Voltage divider biassing.

③ positive and negative biassing.

* Single base-resistor biassing

Ex:

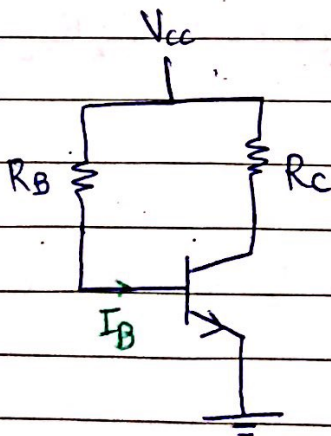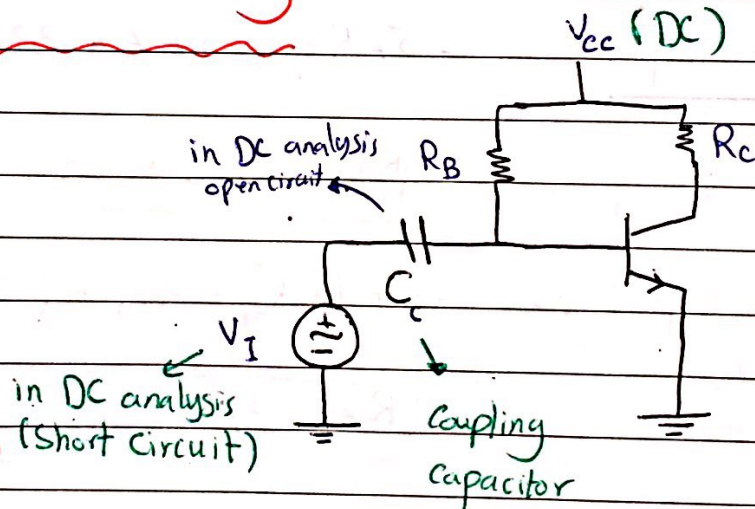

DC

The impedance of the capacitor: $Z_c = \frac{1}{j2\pi f c} = \infty$ (open circuit) at DC $f=0$

* advantages :-

it is simple (one resistor)

* Disadvantages :-

1. R_B has a high value ($M-\Omega$)


2. Q-point is not stable with β (i.e. with temperature)

EX: if $V_{CC} = 12V$, Design a single base-resistor such that $I_{CQ} = 1mA$, $V_{CEQ} = 6V$, $\beta = 100$

Sol: $\Rightarrow R_C = \frac{V_{CC} - V_{CEQ}}{I_{CQ}} = 6K-\Omega$

$\Rightarrow I_{BQ} = \frac{I_{CQ}}{\beta} = 10 \mu A$

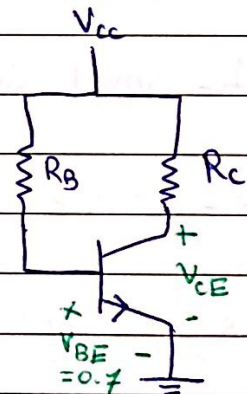$\Rightarrow R_B = \frac{V_{CC} - 0.7}{I_{BQ}} = 1.13 M-\Omega$



\Rightarrow we are going to see the affect of changing the value of β (changing the temperature)

β	50	100	150
I_{CQ}	0.5mA	1mA	1.5mA
V_{CEQ}	9V	6V	3V

I_B (unchanged) = 10 μA

if $\beta = 50 \Rightarrow I_{CQ} = \beta I_B = 0.5mA$


$\Rightarrow V_{CE} = V_{CC} - R_C I_C = 9V$

if $\beta = 150 \Rightarrow I_{CQ} = 1.5mA$

$\Rightarrow V_{CE} = 3V$

* the only affected parameter of changing the temperature is (β).

* Voltage divider Biasing:-

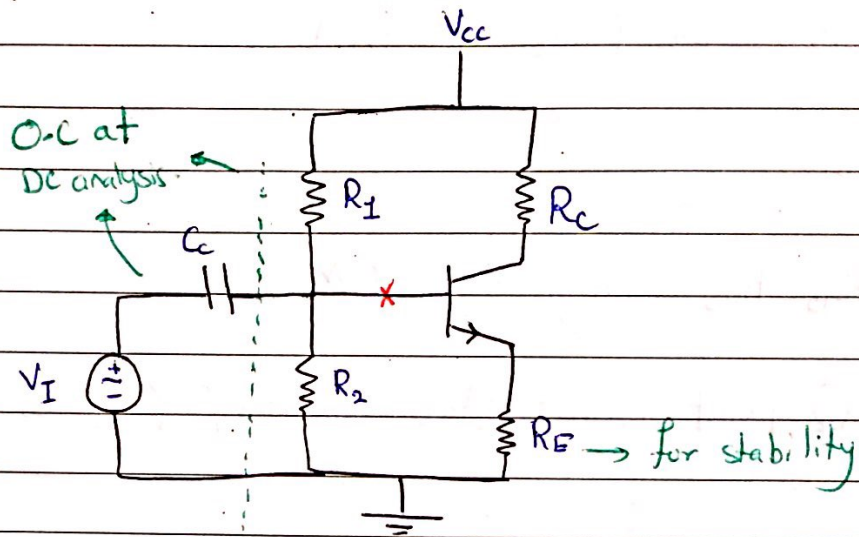


* Advantages:-

1. Small value of resistors (in $K\Omega$).
2. Stable Q-point.

* Disadvantages:-

- 3 resistors instead of one resistor as in type 1.

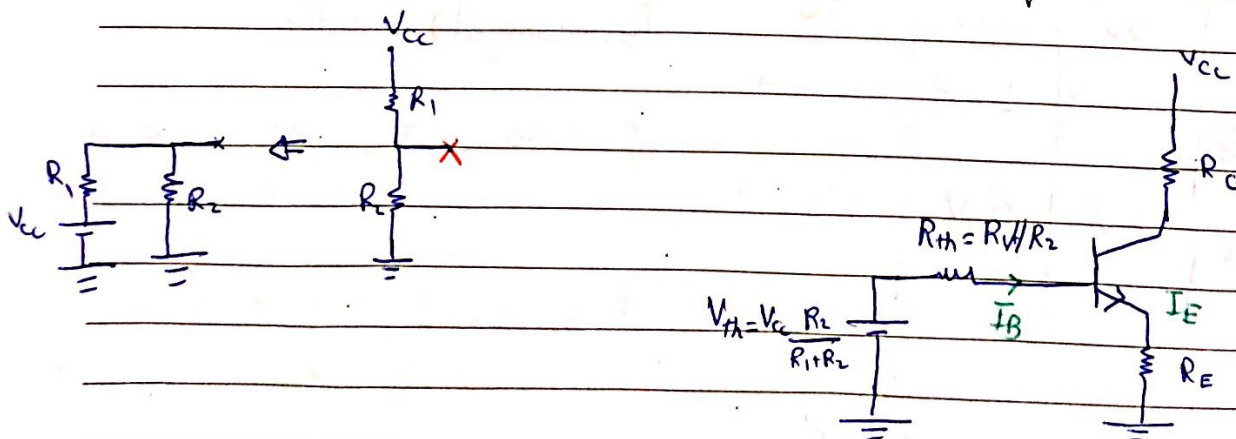⇒ to simplify the circuit we do thevenin equivalent:- (at point x)



⇒ Input loop:-

$$-V_{th} + R_{th}I_B + 0.7 + R_E(1+\beta)I_B = 0$$

$$I_B = \frac{V_{th} - 0.7}{R_{th} + R_E(1+\beta)} \Rightarrow I_C = \beta I_B = \frac{\beta(V_{th} - 0.7)}{R_{th} + (1+\beta)R_E}$$

* to get a stable Q-point (I_C less dependent) on β

$$\text{we need } R_{th} \ll (1+\beta)R_E \Rightarrow I_C \approx \frac{\beta(V_{th} - 0.7)}{(1+\beta)R_E}$$


$$I_C \approx \frac{V_{th} - 0.7}{R_E}$$

as a general rule:-

$$\boxed{R_{th} = 0.1(1+\beta)R_E} \quad \text{stability rule}$$

② Voltage divider Biasing:-

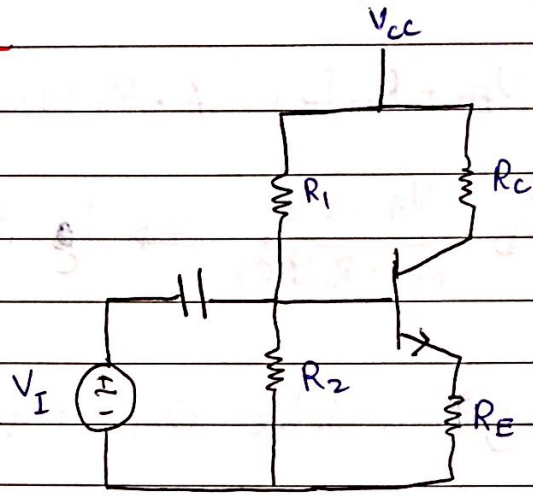EX: $R_1 = 56k\Omega$, $R_2 = 12.2k\Omega$
 $R_C = 2k\Omega$, $R_E = 0.4k\Omega$
 $V_{CC} = 10V$, $V_{BE(on)} = 0.7V$




Find the Q-point values:-

if $\beta = 100$, $\beta = 50$, $\beta = 150$

Sol:

$$R_{th} = R_1 || R_2 = 10k\Omega$$
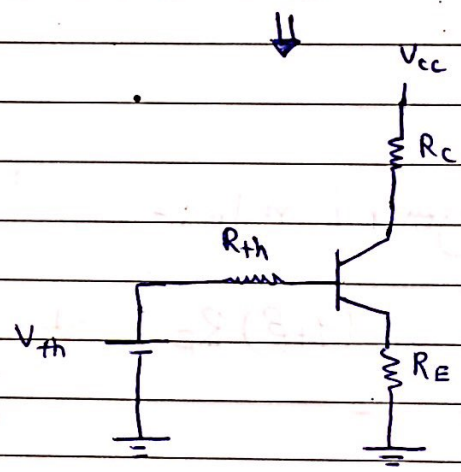
$$V_{th} = V_{CC} \cdot \frac{R_2}{R_1 + R_2} = 1.79V$$



إضافة على السؤال

Stability rule:-

$$R_{th} \ll (1 + \beta) R_E$$

$$10 \ll (1 + 100) \cdot 0.4$$

$$10 \ll 40$$

⇓

$$R_{th} \stackrel{?}{=} 0.1 (1 + \beta) R_E \Rightarrow$$

$$10 \stackrel{?}{=} 4, \text{ No!}$$

⇒ the best choice to get the stability: the maximum of R_E and the minimum of R_{th}

⇒ $I_{BQ} = ?$ Input loop :- $-V_{th} + I_B R_{th} + 0.7 + R_E (1 + \beta) I_B = 0$

$$I_{BQ} = 21.6 \mu A$$

$$\Rightarrow I_{CQ} = \beta I_{BQ} = 2.16 \text{ mA}$$

$$\text{output loop :- } -V_{CC} + I_C R_C + V_{CE} + (1 + \beta) I_B R_E = 0$$


$$V_{CEQ} = 4.81 \text{ V}$$

β	50	100	150
I_{BQ}	35.9 mA	21.6 mA	15.5 mA
I_{CQ}	1.8 mA	2.16 mA	2.32 mA
V_{CEQ}	5.67 V	4.81 V	4.4 V

③ Positive & negative biasing:-

* Advantages :-

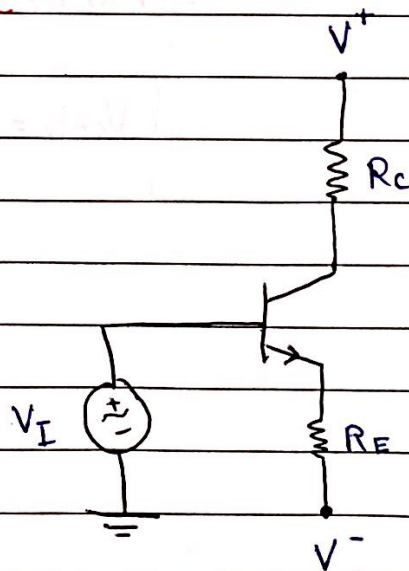- ① no need for coupling capacitor
- ② stable Q-point



Ex:- if $V^+ = 5V$, $V^- = -5V$


$R_C = 1.5K\Omega$, $R_E = 2K\Omega$

$\beta = 100$

Find the Q-point values

Sol: we do a DC analysis

So we make V_I short circuit.

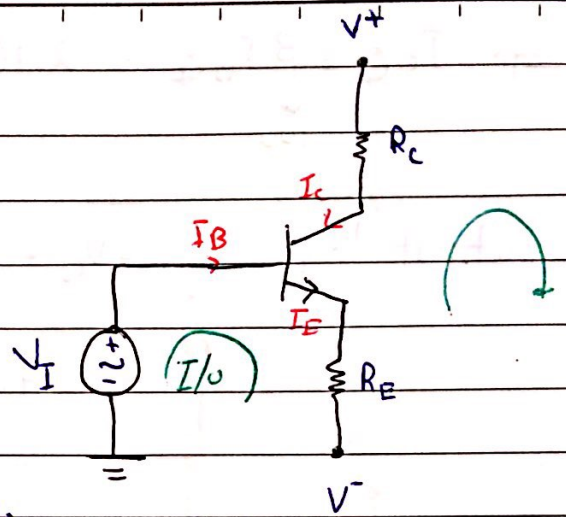

Input loop:- $0 + 0.7 + R_E(1+\beta)I_B + (-5) = 0$

$$\Rightarrow I_{BQ} = \frac{5 - 0.7}{(1+\beta)R_E} = 21.3 \mu A$$

$$\Rightarrow I_{CQ} = \beta I_{BQ} = \frac{\beta(5 - 0.7)}{(1+\beta)R_E} \quad \text{= stable Q-point}$$

$$I_{CQ} = 2.13 \text{ mA}$$

output loop:-


$$-5 + R_C I_{CQ} + V_{CEQ} + R_E I_{EQ} - 5 = 0$$

$$V_{CEQ} = 2.51 \text{ V}$$

حل الامتحان الثاني

Q1 Source regulation

1.5%

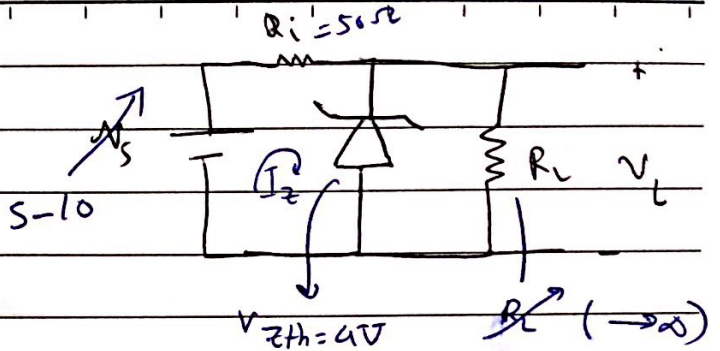

$$\text{Source regulation} = \frac{\Delta V_L}{\Delta V_S} \times 100\%$$

at $R_L \rightarrow \infty$

$$I_Z = \frac{V_S - 4}{50 + r_Z}, \quad V_L = 4 + \frac{r_Z (V_S - 4)}{50 + r_Z}$$


$$\text{if } V_S = 10 \Rightarrow V_L = 4 + \frac{6r_Z}{50 + r_Z}$$

$$\text{if } V_S = 5 \Rightarrow V_L = 4 + \frac{r_Z}{50 + r_Z}$$

$$\frac{\Delta V_L}{\Delta V_S} = \frac{1.5}{100} \Rightarrow \frac{5r_Z}{50 + r_Z} = \frac{1.5}{100} \Rightarrow r_Z = 0.761 \Omega$$

Q2

$r_Z = 0, V_{Zth} = 2, V_S = 0.7$

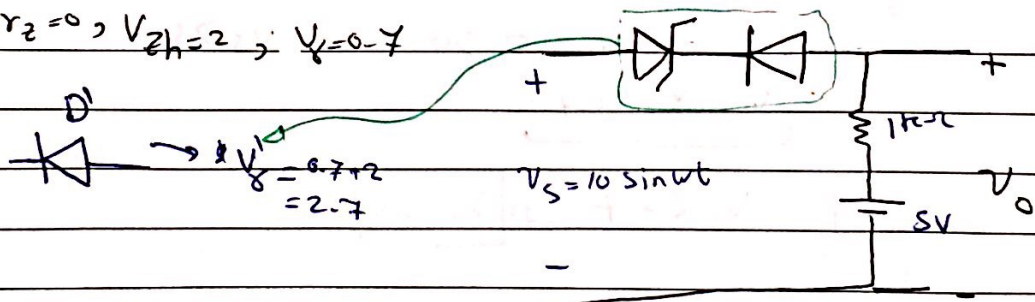

step 1: assume D' is open


$$\text{step 2: } -V_S - V_{D'} + 5 = 0 \Rightarrow V_{D'} = 5 - V_S$$

step 3: $V_{D'} > 2.7 \Rightarrow 5 - V_S > 2.7 \Rightarrow V_S < 2.3$ diode is on


$$V_O = V_S + 3.7$$

if $V_S > 2.3 \Rightarrow$ Diode is off $V_O = 5V$

حل الامتحان الثاني

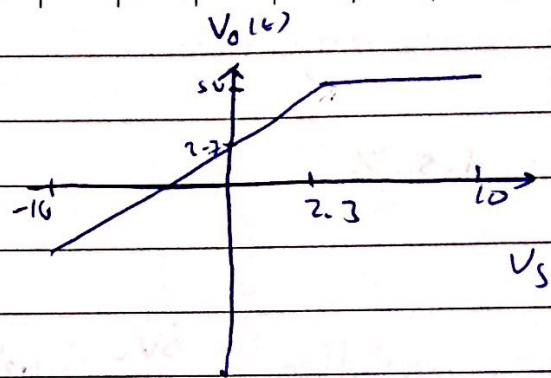

Q3

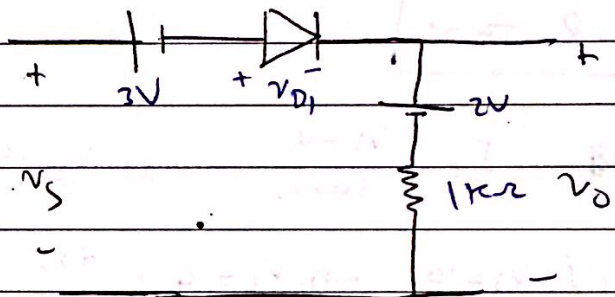

step 1: o/c

step 2 :- $-V_s + 3 + V_{D+2} = 0 \Rightarrow V_D = V_s - 5$

step 3 :- $V_D > 0.7$ Diode is ON

$V_s - 5 > 0.7 \Rightarrow V_s > 5.7$

$V_o = V_s - 3.7$

if $V_s < 5.7 \Rightarrow V_o = 2V$

24/4/2016 | Dr. Raed AL-Zoabi

Sunday

* Basic Applications of transistor:


1] switch

2] logic circuits


3] Amplifier (in Electronics II)

① * switch:-

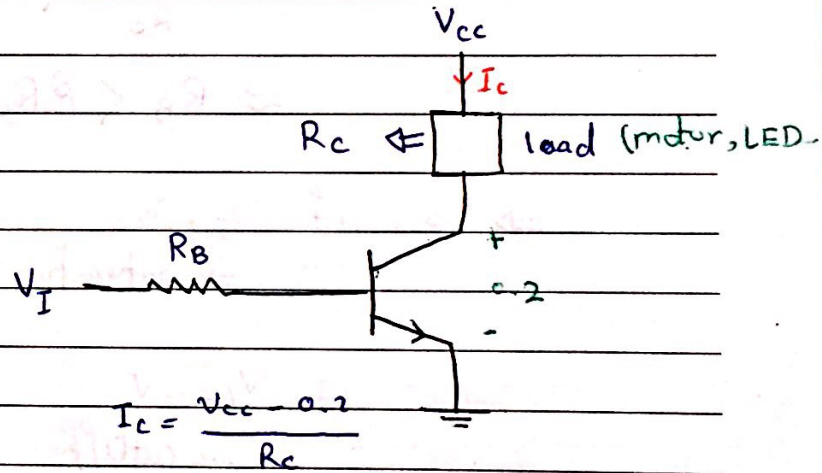⇒ the transistor should be in saturation mode to work as switch, why?




≡ saturation

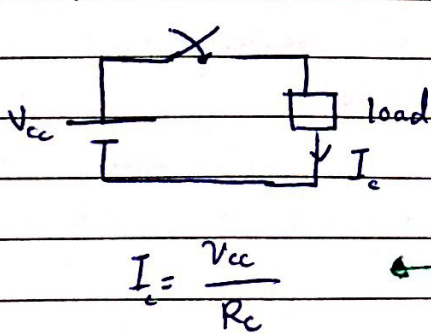

$$\approx \frac{V_{CC}}{R_C}$$

≡ off

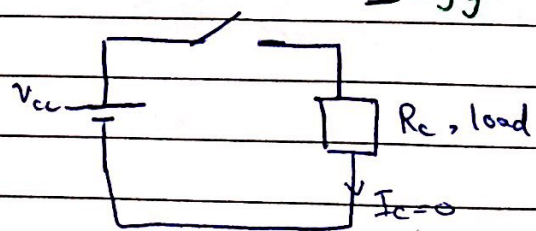

How to select R_B :

In saturation : $V_{CE} = V_{CE(sat)} = 0.2 \text{ V}$

$$I_C < \beta I_B$$



$$\frac{V_{CC} - 0.2}{R_C} < \beta \frac{V_I - 0.7}{R_B}$$

if $V_I = V_{CC}$

$$\approx \frac{V_{CC}}{R_C} < \beta \frac{V_{CC}}{R_B}$$

$$\approx R_B < \beta R_C$$

⇒ So, if $V_I = V_{CC}$

⇒ saturation ⇒ switch ON

if $V_I = 0 \text{ V}$

⇒ cut off ⇒ switch off


Ex: if $\beta = 50$, $V_{CE(sat)} = 0.2 \text{ V}$

LED cut-in voltage $V_y = 1.5 \text{ V}$

The required $I_c = 12 \text{ mA}$

Find R_B & R

Given that $V_I = 0$ or 5 V .

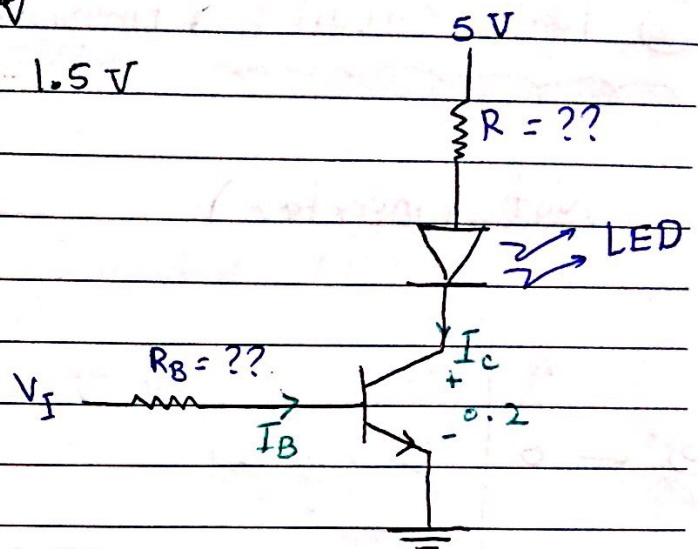

Sol: if $V_I = 0 \text{ V} \Rightarrow$ cutoff $\Rightarrow I_c = 0 \text{ A}$

LED is off

if $V_I = 5 \text{ V} \Rightarrow$ saturation $\Rightarrow V_{CE} = 0.2 \text{ V}$

$$\therefore I_c = \frac{5 - (0.2 + 1.5)}{R} \Rightarrow R = 275 \Omega$$

\downarrow
12 mA

$$\Rightarrow I_c < \beta I_B$$

$$12 \text{ mA} < 50 I_B$$

$$\frac{12}{50} < I_B$$


$$\frac{12}{50} < \frac{5 - 0.7}{R_B}$$

$$R_B < \frac{(4.3)(50)}{12} \Rightarrow R_B < 18 \text{ k}\Omega$$


\Rightarrow we can select any value for R_B such that $R_B < 18 \text{ k}\Omega$

② Logic circuit: (transistor are used as switch)


Not (inverter)

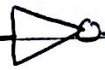

V_I	V_O
0	5
5	0.2

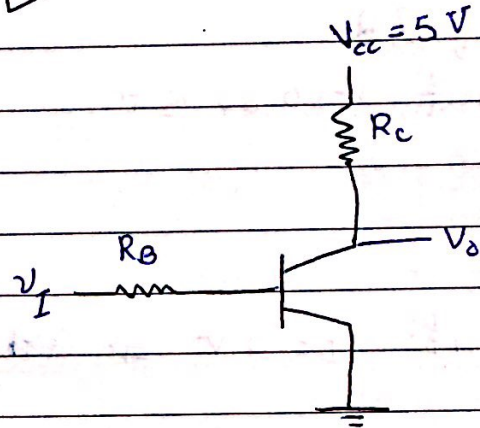

NOR Gate

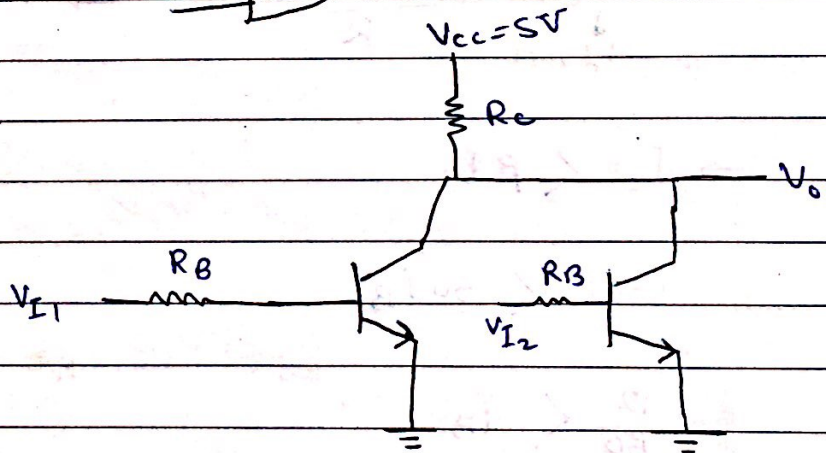

V_{I1}	V_{I2}	V_O
0	0	5
0	5	0.2
5	0	0.2
5	5	0.2

* Field-effect transistor (FET):

Types:-

① MOSFET: metal-oxide-semiconductor FET.

→ NMOSFET: n-channel MOSFET. ┌ enhancement mode
└ depletion mode

→ PMOSFET: p-channel MOSFET. ┌ enhancement mode
└ depletion mode.

→ Complementary MOSFET (CMOS)

Applications:-

Laptops, desktop, calculators, ...

Features
compared with
BJT

- ① small size.
- ② high input impedance.
- ③ low power dissipation.

② JFET: junction FET

→ pn junction FET (pn JFET)

→ Metal-semiconductor FET (MESFET)

⇒ JFETs were developed before MOSFET.


⇒ MOSFET is used more than JFET.

26/4/2016 | Dr. Raed AL-Zoabi
 Tuesday


* MOSFET:

n-channel

p-channel

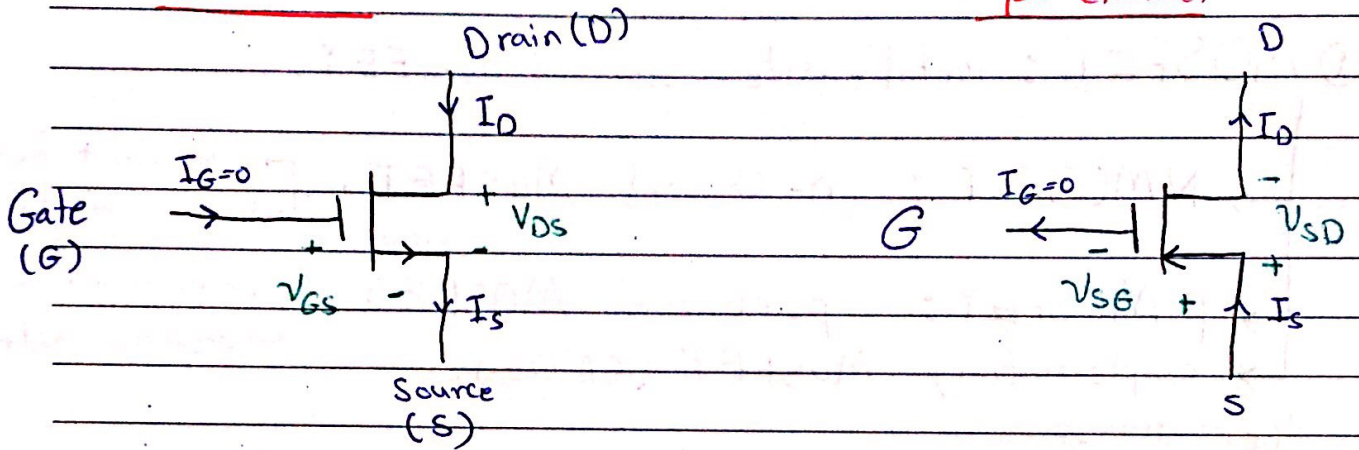

$$I_D = I_S$$

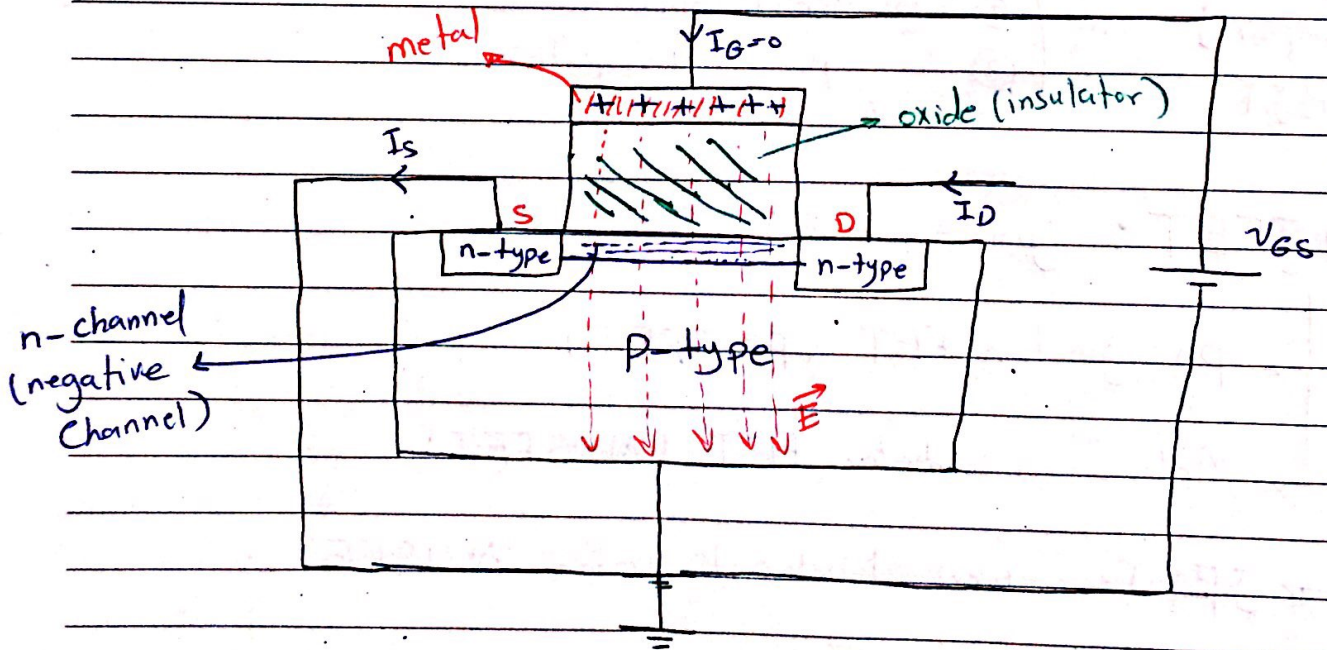

* if $V_{GS} = 0 \Rightarrow$ no $E \Rightarrow$ no n-channel $\Rightarrow I_D = 0$


* if V_{GS} is increased \Rightarrow n-channel is created $\Rightarrow I_D > 0A$

threshold voltage.

* if $V_{GS} \geq V_{TN} \Rightarrow$ then the n-channel will be created $\Rightarrow I_D > 0$

* if $V_{GS} < V_{TN} \Rightarrow I_D = 0$ Ampere.

* Current voltage characteristic :-

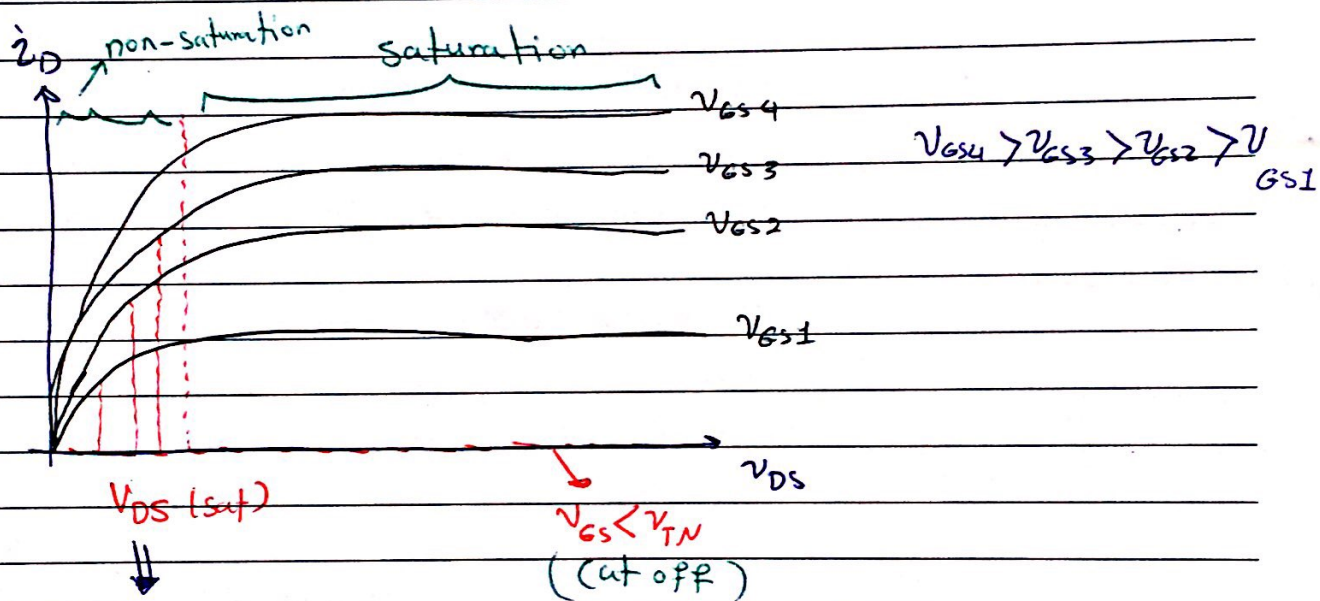

$V_{DS(sat)} = V_{GS} - V_{TN} \Rightarrow$ each curve has its own $V_{DS(sat)}$

Notes :-

Field effect (FET) :-

The phenomenon used to control the conductance of a semiconductor or to control the current in a semiconductor by applying an electric field perpendicular to the surface is called field effect.

⇒ Enhancement mode:- it means that a voltage (V_{GS}) should be applied to create the channel.

- n-channel :- positive V_{GS} should be applied to create channel.
- p-channel :- negative V_{GS} should be applied to create channel.



⇒ depletion mode:-

- n-channel :- V_{GS} should be negative to turn the device off.
- p-channel :- V_{GS} should be positive to turn the device off.



enhancement mode:-

depletion mode:-

1. n-channel

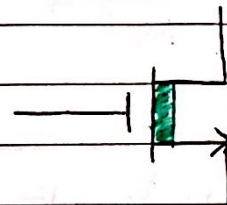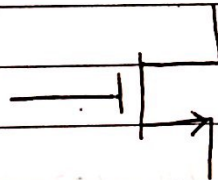


2. p-channel

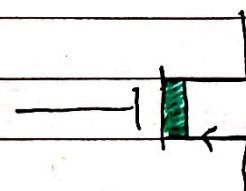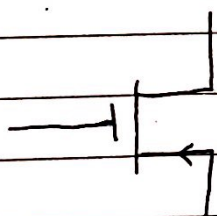


28/4/2016 | Dr. Raed AL-Zoabi
Thursday

* Complementary MOSFET: CMOS

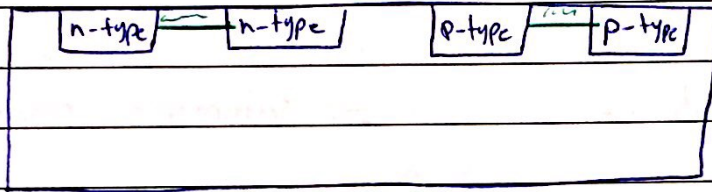CMOS uses both n-channel and p-channel in the same structure.



قناة للتيار السالب

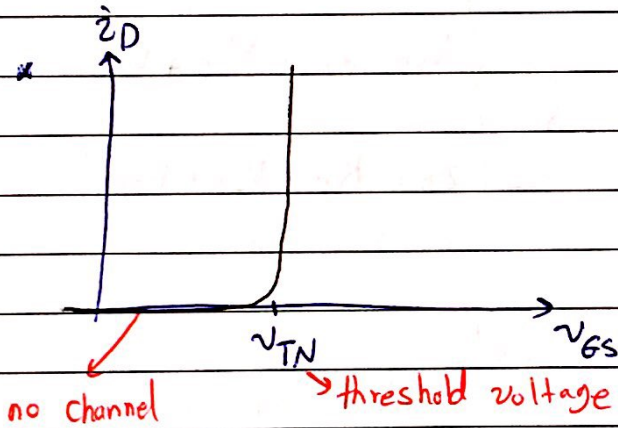

* DC analysis for MOSFET circuits:-

* n-channel MOSFET (NMOS):-

→ non-saturation mode:-

$$\left\{ \begin{array}{l} V_{DS} < V_{DS(sat)} \\ V_{DS(sat)} = V_{GS} - V_{TN} \\ i_D = K_n [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2] \end{array} \right.$$

→ saturation mode:-

$$\left\{ \begin{array}{l} V_{DS} > V_{DS(sat)} \\ V_{DS(sat)} = V_{GS} - V_{TN} \\ i_D = K_n (V_{GS} - V_{TN})^2 \end{array} \right.$$

Note:- $V_{TN} > 0$ (enhancement mode) }
 $V_{TN} < 0$ (depletion mode) } n-channel

* p-channel (PMOS)

⇒ non-saturation mode :-

$$\left\{ \begin{array}{l} V_{SD} < V_{SD(sat)} \\ V_{SD(sat)} = V_{SG} + V_{TP} \\ i_D = K_p [2(V_{SG} + V_{TP})V_{SD} - V_{SD}^2] \end{array} \right.$$

⇒ saturation mode :-

$$\left\{ \begin{array}{l} V_{SD} > V_{SD(sat)} \\ V_{SD(sat)} = V_{SG} + V_{TP} \\ i_D = K_p (V_{SG} + V_{TP})^2 \end{array} \right.$$

Note:- $V_{TP} < 0$ (enhancement mode) }
 $V_{TP} > 0$ (depletion mode) } p-channel

* K_n : conduction parameter (A/V^2)
 K_p

Steps of DC analysis:-

Step 1: Find from input loop V_{GS} .

Step 2: if $V_{GS} < V_{TN} \Rightarrow$ cutoff mode ($I_D = 0A$)

Step 3: if $V_{GS} > V_{TN}$

\Rightarrow assume saturation mode:-

A. Find $i_D = K_n (V_{GS} - V_{TN})^2$.

B. Find from output loop V_{DS} .

if $V_{DS} > V_{DS(sat)} \Rightarrow$ Saturation mode.

otherwise, non-saturation mode.



Ex:- Given

$$K_n = 0.1 \text{ mA/V}^2$$

$$V_{TN} = +1 \text{ V}$$


Find: ① the Q-point values

② the DC-load line

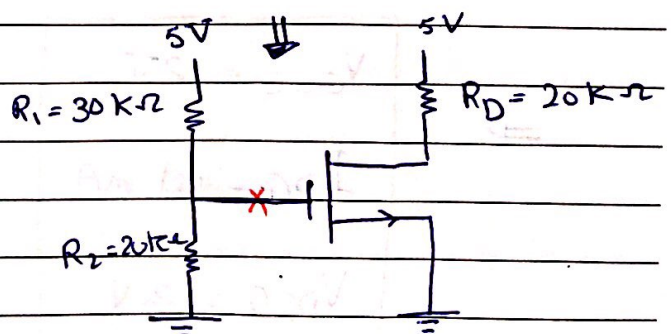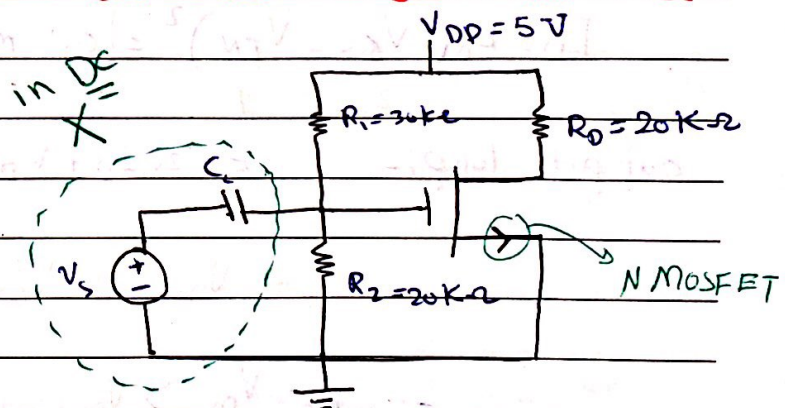

\Rightarrow followed Five Apple

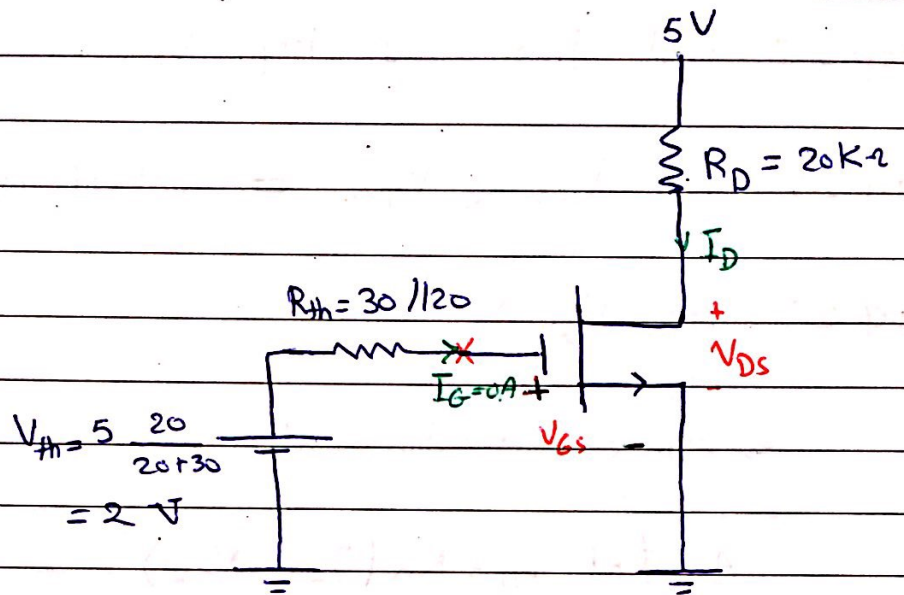⇒ we do first thevenin equivalent at point (x)



① $V_{GS} = 2V$

⇒ $V_{GS} > V_{TN} \Rightarrow$ yes, it is not in cutoff

⇒ Assume saturation mode :-

$$I_D = K_n \left(\frac{V_{GS}}{2} - \frac{V_{TN}}{1} \right)^2 = 0.1 \text{ mA}$$

output loop :- $5 + 20 I_D + V_{DS} = 0 \Rightarrow V_{DS} = 3V$

$$\Rightarrow V_{DS(sat)} = V_{GS} - V_{TN} = 1V$$

∴ $V_{DS} > V_{DS(sat)} \Rightarrow$ saturation mode



⇒

$V_{GSQ} = 2V$
$I_{DQ} = 0.1 \text{ mA}$
$V_{DSQ} = 3V$

To find the DC load line:-

output loop:- $-5 + 20I_D + V_{DS} = 0$
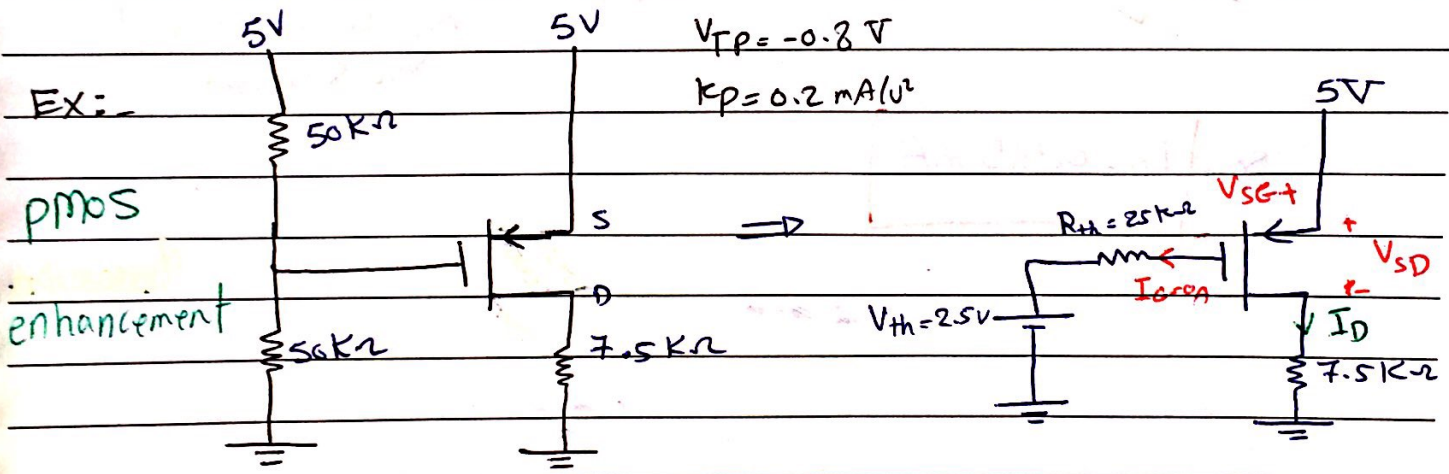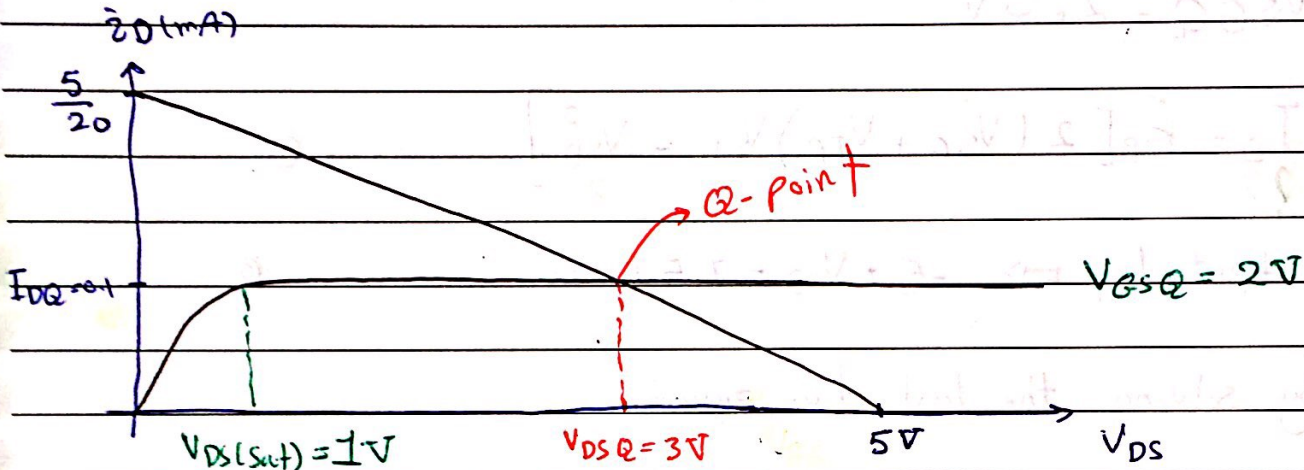
$$I_D = \frac{5}{20} - \frac{V_{DS}}{20} \text{ mA}$$



I/P $\Rightarrow -5 + V_{SG} + 2.5 = 0 \Rightarrow V_{SG} = 2.5V > 0 \Rightarrow$ not cut off

Assume saturation mode:- $I_D = K_p (V_{SG} - V_{TP})^2 = 0.578 \text{ mA}$

O/P loop:- $-5 + V_{SD} + 7.5 I_D = 0 \Rightarrow V_{SD} = 0.65V$

$$\Rightarrow V_{SD(sat)} = V_{SG} + V_{TP} = 2.5 - 0.8 = 1.7 \text{ V}$$

$\therefore V_{SD} < V_{SD(sat)} \Rightarrow$ non-saturation

② Find the Q-point values:-

$$\therefore V_{SGQ} = 2.5 \text{ V}$$

$$\Rightarrow I_D = K_p [2 (V_{SG} + V_{TP}) V_{SD} - V_{SD}^2] \quad \text{--- ①}$$

$$\Rightarrow \text{output loop} \Rightarrow -5 + V_{SD} + 7.5 I_D = 0 \quad \text{--- ②}$$


By solving the last two equations:-

$$V_{SD} = 1.14 \text{ V} \quad \text{or} \quad V_{SD} = 2.93 \text{ V} \rightarrow \text{since we assume non-saturation mode. } V_{SD} < V_{SD(sat)}$$

$$\text{So, } I_D = 0.515 \text{ mA}$$

Tuesday | Dr. Raed AL-Zoabi
3/5/2018

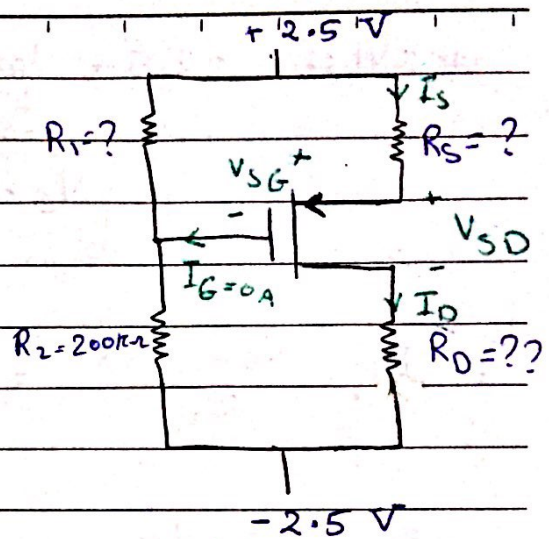Ex: Given $I_{DQ} = 100 \mu A$, $V_{SDQ} = 3V$
 $V_{RS} = 0.8V$, $K_p = 100 \mu A/V^2$
 $V_{TP} = -0.4V$



Find the mode of operation
 & R_1 , R_S , R_D & the power dissipated

⇒ PMOSFET - enhancement mode.

⇒ $R_S = \frac{V_{RS}}{I_{DQ}} = \frac{0.8V}{100 \mu A} = 8k\Omega$


⇒ Assume saturation mode:-

$I_D = K_p (V_{SG} + V_{TP})^2$

$V_{SG} = 1.4V$

$V_{SG} = \sqrt{\frac{I_{DQ}}{K_p}} - V_{TP} = 1.4V > V_{TP}$
 $= -0.6V < V_{TP} \times$

Since we assumed saturation mode.

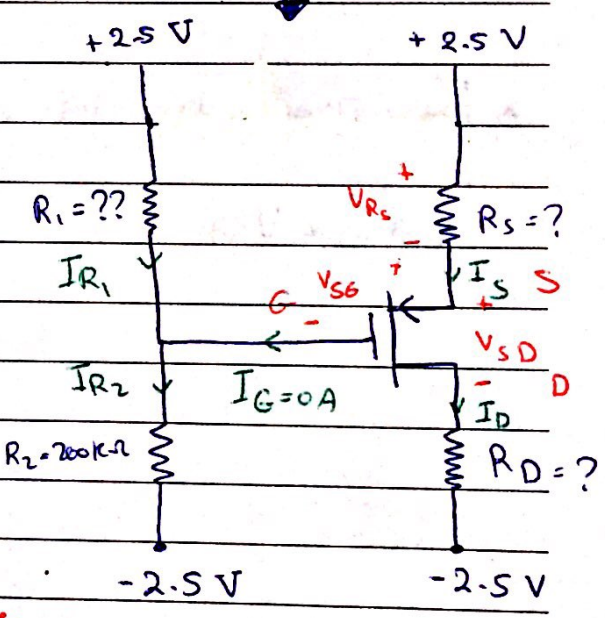

$V_{SD(sat)} = V_{SG} + V_{TP} = 1.4 - 0.4 = 1V$

Since $V_{SDQ} > V_{SD(sat)} \Rightarrow \therefore$ saturation mode.

* output loop :- $-2.5 + R_S I_{DQ} + V_{SDQ} + R_D I_{DQ} + (-2.5) = 0$

$R_D = 12k\Omega$

with respect to ground

$$\Rightarrow \text{KVL: } -2.5 + V_{RS} + V_{SG} + V_G = 0$$

$$\begin{matrix} \downarrow & & \downarrow \\ 0.8 & & 1.4 \end{matrix}$$

$$V_G = 0.3 \text{ V}$$

$$\Rightarrow I_{R_2} = \frac{V_G - (-2.5)}{R_2} = 0.014 \text{ mA} = I_{R_1}$$

$$\Rightarrow I_{R_1} = \frac{2.5 - V_G}{R_1} \rightarrow R_1 = 157 \text{ k}\Omega$$

The power dissipated on the transistor:-

$$P_T = I_D \times V_{SD}$$


EX: Find R_D & R_S

such that: $I_{DQ} = 0.5 \text{ mA}$

$$V_{TN} = 1.2 \text{ V}$$

$$V_{DSQ} = 4 \text{ V}$$

$$k_n = 0.25 \text{ mA/V}^2$$

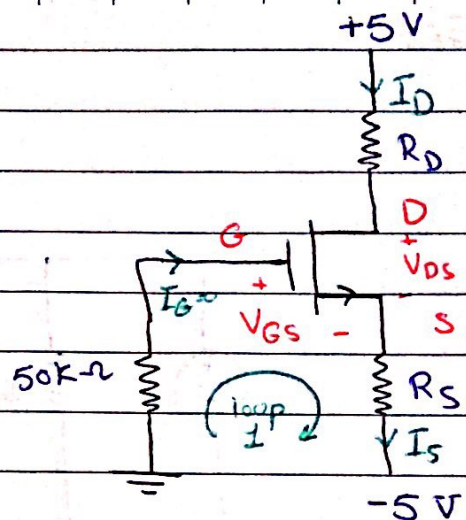

sol: MOSFET enhancement

Assume saturation mode:-

$$\Rightarrow I_D = k_n (V_{GS} - V_{TN})^2 \Rightarrow V_{GS} = \sqrt{\frac{I_D}{k_n}} + V_{TN} = 2.614 \text{ V}$$

$$\Rightarrow V_{DS(\text{sat})} = V_{GS} - V_{TN} = 2.614 - 1.2 = 1.414 \text{ V}$$

\therefore since $V_{DS} > V_{DS(\text{sat})}$ \Rightarrow saturation mode
 $4 \text{ V} \quad 1.414$

$$\Rightarrow \text{KVL @ loop 1: } V_{GS} + V_S = 0 \Rightarrow V_S = -2.614$$

the potential difference between point (s) and the ground.

since $I_G = 0 \text{ A}$

$$\Rightarrow I_S = I_D = \frac{V_S - (-5)}{R_S} \Rightarrow R_S = 4.77 \text{ k}\Omega$$


$$\Rightarrow V_D = V_{DS} + V_S \Rightarrow I_D = \frac{5 - V_D}{R_D}$$

with respect to ground

$$\Rightarrow R_D = 7.23 \text{ k}\Omega$$

Thursday | Dr. Raied AL-Zoabi
5/5/2016

Ex:

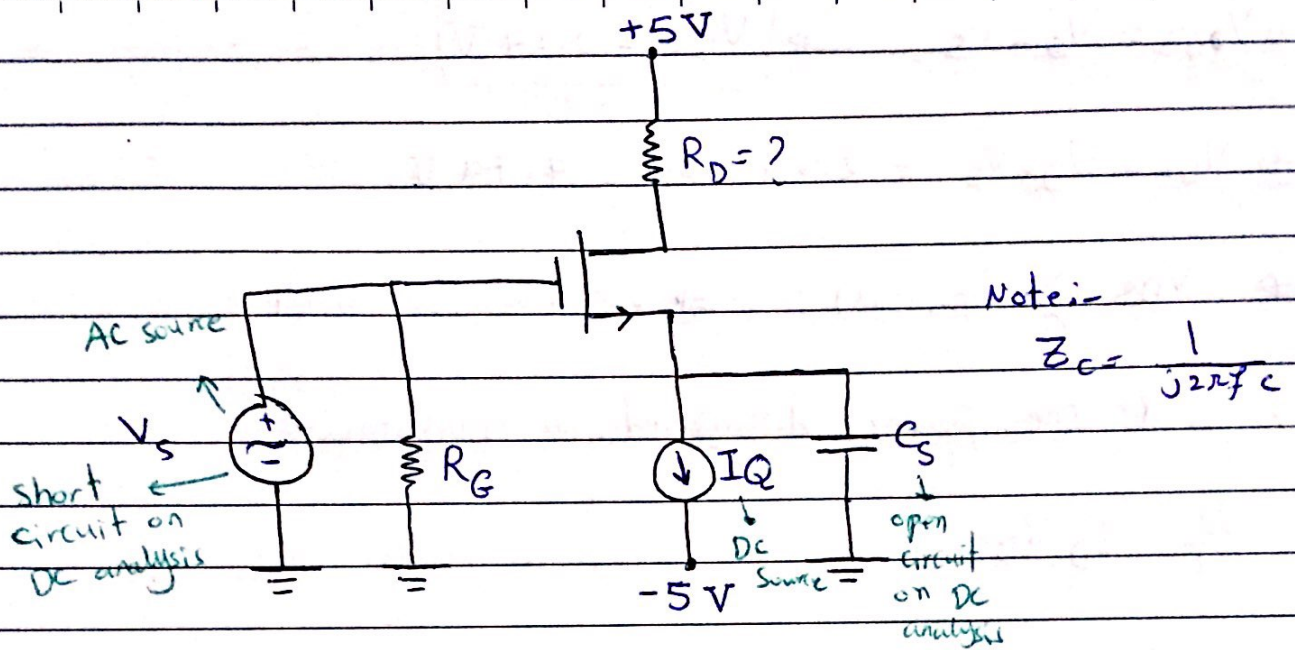

Given: $I_D = 250 \mu A$, $V_D = 2.5 V$, $V_{TN} = 0.8 V$, $K_n = 120 \mu A/V^2$
Find R_D & the mode of operation.

Sol: Note:- any capacitor is considered as open circuit in DC analysis.


$$\Rightarrow R_D = \frac{5 - 2.5}{I_D} = \frac{5 - 2.5}{250 \mu A} = 10 k\Omega$$

Assume saturation mode:-

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$V_{GS} = \pm \sqrt{\frac{I_D}{K_n}} + V_{TN} = 2.24 V$$
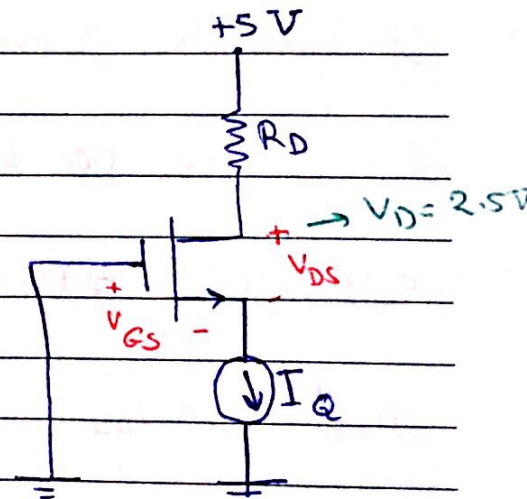
$$V_{DS(sat)} = V_{GS} - V_{TN} = 2.24 - 0.8 = 1.4 V$$



$$\Rightarrow V_{GS} = V_G - V_S \Rightarrow V_S = -2.24 \text{ V}$$

$$\Rightarrow V_{DS} = V_D - V_S = 2.5 + 2.24 = 4.74 \text{ V}$$

$$\Rightarrow V_{DS} > V_{DS(sat)} \Rightarrow \therefore \text{saturation mode.}$$

* find the power dissipated on transistor:-


$$P_T = I_D V_{DS}$$

EX: Given:- $V_{TN} = 0.8 \text{ V}$, $k_n = 0.05 \text{ nA/V}^2$

① find the mode of operation.

② find the Q-point values (V_{GSQ} , I_{DQ} , V_{DSQ})

③ find the DC load line.

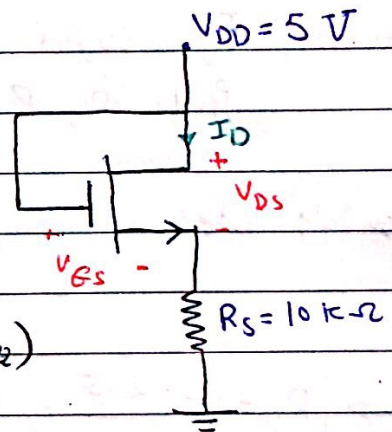

Sol: NMOSFET - Enhancement

$$\Rightarrow \textcircled{1} V_{GS} = V_{DS}$$

$$V_{DS(sat)} = V_{GS} - V_{TN} \Rightarrow V_{DS(sat)} = V_{DS} - V_{TN}$$

\Rightarrow check $V_{DS} > V_{DS(sat)}$ \therefore always \Rightarrow Saturation mode

$$\textcircled{2} \Rightarrow \text{output loop :- } -5 + V_{DS} + R_S I_D = 0 \quad \text{--- ①}$$

$$I_D = K_n \frac{(V_{GS} - V_{TN})^2}{V_{DS}} \quad \text{--- ②}$$


solve ① & ② $\rightarrow V_{DS} = -3.27 \text{ V} \times$
OR $= 2.87 \rightarrow > V_{TN}$

$$\therefore V_{GSQ} = V_{DSQ} = 2.87 \text{ V}$$

$$I_{DQ} = \frac{5 - 2.87}{10} = 0.213 \text{ mA}$$

③ Dc load line $I_D \propto V_{DS}$:-
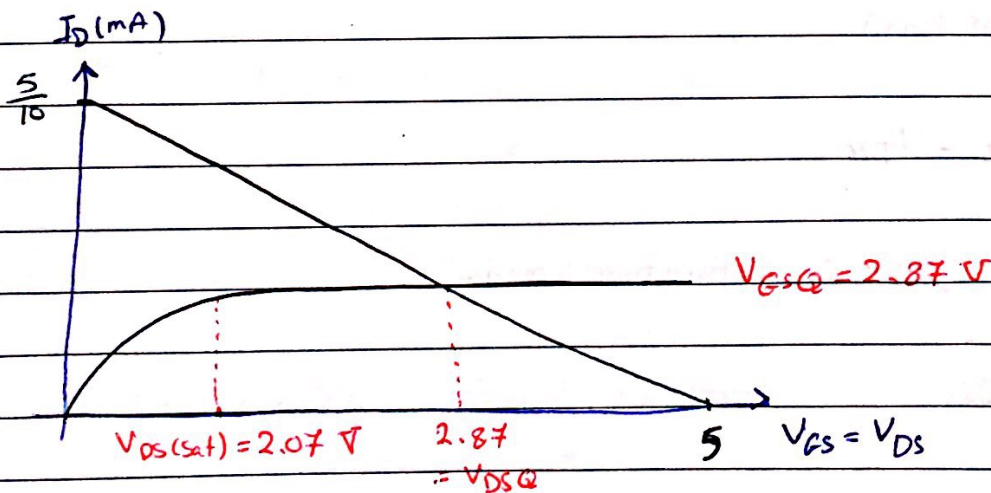
$$\text{d/p :- } -5 + V_{DS} + 10 I_D = 0 \rightarrow I_D = \frac{5}{10} - \frac{V_{DS}}{10} \text{ mA}$$




EX: - $V_{TN} = -2\text{ V}$

$k_n = 0.1\text{ mA/V}^2$

Find the mode of operation
& the Q-point values

sol: NMOSFET - depletion mode.

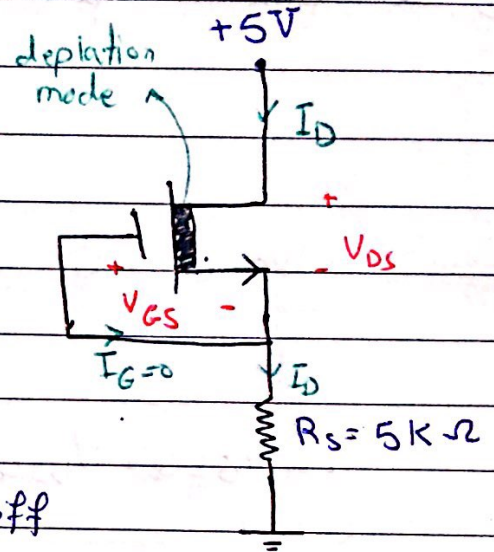

$V_{GS} = 0\text{ V} \Rightarrow V_{GS} > V_{TN} \Rightarrow$ not cut off

\Rightarrow Assume saturation mode.

$I_{DQ} = k_n (V_{GS} - V_{TN})^2 = 0.1(2)^2 = 0.4\text{ mA}$

$\Rightarrow -5 + V_{DS} + 5I_D = 0 \Rightarrow V_{DSQ} = 3\text{ V}$

$V_{DS} \stackrel{?}{>} V_{DS}(\text{sat})$

$3 > V_{GS} - V_{TN}$

$3 > 2$ yes \therefore Saturation mode.

* Applications of MOSFET :-


- ① Switch (non-saturation mode & cut off)
- ② Logic circuit
- ③ Amplifier (In Electronics II)

* Switch :-

→ if $V_I < V_{TN} \Rightarrow$ Cutoff

$I_D = 0A$

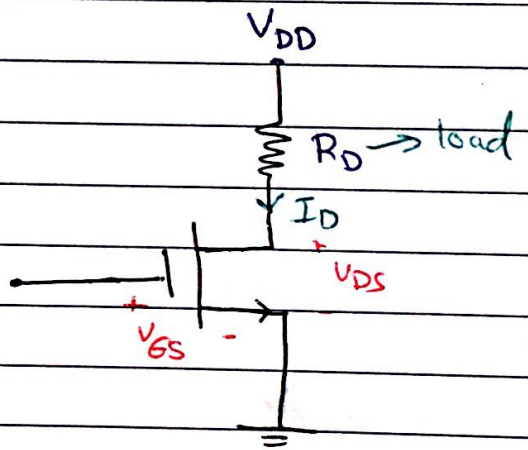→ if $V_I > V_{TN} \Rightarrow$ we have two cases:-



Ⓐ Saturation :- $V_{DS} > V_{DS(sat)}$

$$P_T = I_D V_{DS}$$

high value
high value

Ⓑ non-saturation $V_{DS} < V_{DS(sat)}$ (make $V_I = V_{DD}$)

$$P_T = I_D V_{DS}$$

small
small

😊 بالتوفيق