

Useful information : for silicon , $\mu_n = 1350 \text{ cm}^2/\text{V-s}$ and $\mu_p = 480 \text{ cm}^2/\text{V-s}$.

$n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$. $V_T = 0.026 \text{ V}$ at 300K.

Use the linearized diode model with $r_f = 0 \text{ ohm}$ unless otherwise mentioned.

- Q1 a) Consider n-type ~~GaAs~~ ^{Silicon} at ~~T = 300 K~~ doped to a concentration of $N_d = 5 \times 10^{15} \text{ cm}^{-3}$. Assume mobility values of $\mu_n = 6800 \text{ cm}^2/\text{V-s}$ and $\mu_p = 300 \text{ cm}^2/\text{V-s}$. Determine the conductivity of the material.

n


$$\rho_i = \frac{(n_i)^2}{5 \times 10^{15}} \Rightarrow 45000 \text{ cm}^{-3}$$

$$\sigma = (n \mu_n + p \mu_p) e$$

$$\sigma = (1.6 \times 10^{19}) \times ((5 \times 10^{15} \times 1350) + (45000 \times 480))$$

$$\sigma = 1.08 (\Omega \cdot \text{cm})^{-1}$$

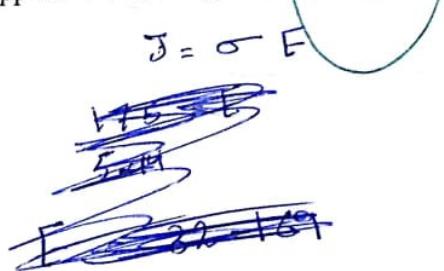Determine the applied electric field that induces a drift current density of 175 A/cm^2 .



$$E = \frac{J}{\sigma} = \frac{175}{1.08} = 162.03$$

4

- b) A silicon pn junction at $T = 300 \text{ K}$ is doped with $N_d = 10^{16} \text{ cm}^{-3}$ and $N_a = 10^{15} \text{ cm}^{-3}$. The junction capacitance is to be 0.8 pF when a reverse bias voltage of 13 V is applied. Find the zero-biased junction capacitance.

$$N_d = 10^{16}, N_a = 10^{15}, e_j = 0.8, V_R = 13$$

$$V_{bi} = 0.026 \ln \left(\frac{10^{15} \times 10^{16}}{(1.5 \times 10^{10})_2} \right)$$

$$V_{bi} = 0.637$$

$$C_j = \frac{C_{j0}}{\sqrt{1 + \frac{V_R}{V_{bi}}}}$$

$$C_{j0} = C_j \times \sqrt{1 + \frac{V_R}{V_{bi}}} \Rightarrow$$


$$C_{j0} = 0.8 \times \sqrt{1 + \frac{13}{0.637}}$$

$$C_{j0} = 3.7015 \text{ pF}$$


2

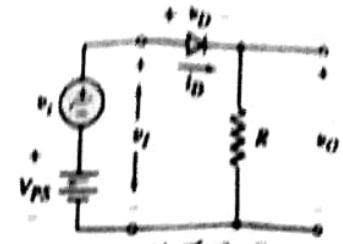Q3 a) The circuit and diode parameters for the circuit shown are $V_{PS} = 9.7$ V, $R = 9.9$ kohm, $V_T = 0.7$ V, $r_f = 100$ ohm and $v_t = 0.2 \sin \omega t$ V.

Calculate the time-varying diode current and voltage.




DC Analysis

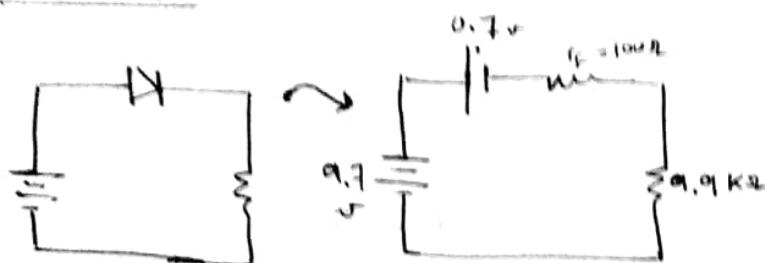

$$\begin{aligned} & \cancel{I_D = I_{DQ} + i_D} \\ & V_D = V_{DQ} + u_D \end{aligned}$$

$$I_{DQ} \Rightarrow -9.7 + 0.7 + 100 I_{DQ} + 9.9 \times 10^3 I_{DQ} = 0$$
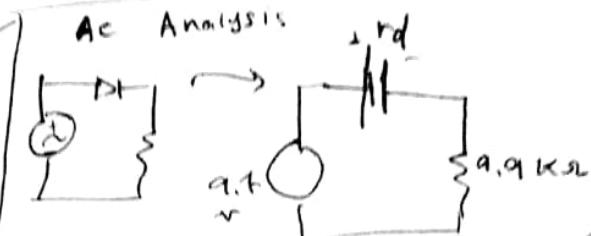
$$\begin{aligned} & q = 10000 I_{DQ} \\ & I_{DQ} = q \times 10^{-4} \text{ A} \\ & V_{DQ} = 0.026 \text{ V} \quad \cancel{I_D = \frac{q \times 10^{-4}}{I_S}} \\ & \text{AC Analysis} \end{aligned}$$




$$I_{dL} = \frac{I_{DQ}}{0.026} \text{ A}$$

$$V_d = \frac{0.026}{I_{DQ}} I_{dL}$$

$$r_{dL} = \frac{0.026}{I_{DQ}} = \frac{0.026}{9 \times 10^{-4}} = 28.88 \Omega$$

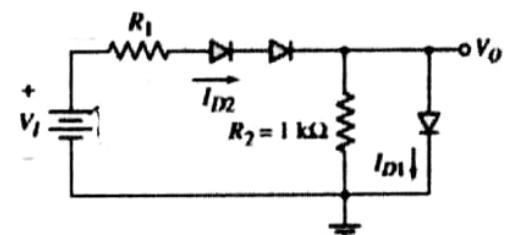b) Assume each diode in the circuit shown has a cut-in voltage of $V_T = 0.7$ V, $r_f = 50$ ohm and $V_I = 6.1$ V. Determine the value of R_1 required such that I_{D1} is one half the value of I_{D2} .



$$I_{D1} = 1.5 \cancel{I_{D2}}$$

$$① -6.1 = R_1 I_{D2} + \cancel{0.7} + 100 I_{D2} + \cancel{1 \times 10^3 (I_{D1} - I_{D2})}$$

$$1.5 I_{D2}$$

$$0 = 0.7 + 50 I_{D1} + 1 \times 10^3 (I_{D1} - I_{D2}) \quad ②$$

$$0.7 = I_{D2} (R_1 + 100 + 1 \times 10^3 - 1500) \quad \boxed{I_{D2}}$$


$$-0.7 = 75 I_{D2} + 1500 I_{D2} - 1 \times 10^3 I_{D2}$$

$$I_{D2} = -2.718 \downarrow = 2.718 \uparrow$$

$$R_1 = 401.729 \Omega$$

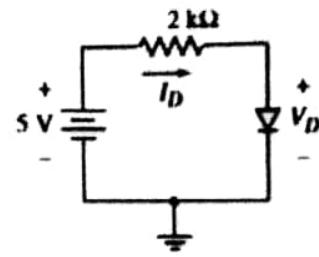Q2 a) Consider the following circuit, where $I_s = 10^{-12} \text{ A}$. Determine V_D , and I_D , using the diode equation and the trial and error method.

$$I_D = I_s (e^{\frac{V_D}{0.026}} - 1)$$



$$-5 + 2I_D + V_D = 0$$

$$5 = 2I_D + V_D$$

$$5 = 2 \left(I_s (e^{\frac{V_D}{0.026}} - 1) \right) + V_D$$

$$5 = 2 \times 10^{-12} \left(e^{\frac{V_D}{0.026}} - 1 \right) + V_D$$


~~$$V_D = 0.738 \text{ V}$$~~

~~$$I_D = 2.13 \text{ A}$$~~




3

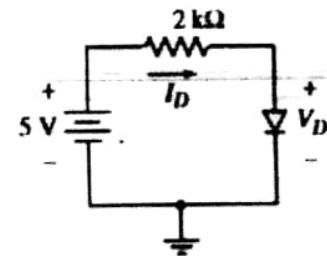b) Consider the circuit shown. Assume $V_T = 0.7 \text{ V}$, $r_f = 20 \text{ ohm}$, and $I_D = 1.2 \text{ mA}$. Use the piecewise linear model to calculate the voltage drop on the 2 K ohm resistor. $V_R = ?$



$$I_D = 1.2$$
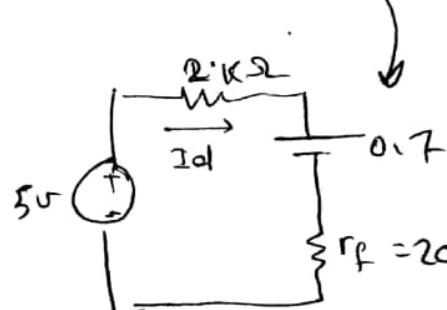
$$\begin{aligned} V &= I_D R \\ &= 1.2 \times 10 (2 \times 10^3) = 2400 \text{ V} \end{aligned}$$



1.5

What is the power dissipated in the diode?




Q4 Consider the circuit shown, where $V_T = 0.7 \text{ V}$, $r_f = 50 \text{ ohm}$ and $R_2 = 2 \text{ k}\Omega$.

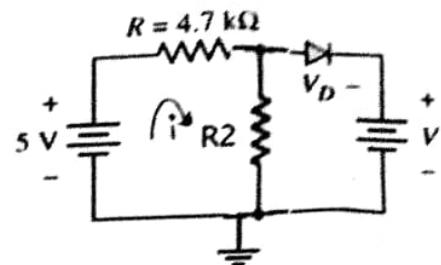i) Find the supply voltage V such that the diode current is 0.2 mA .

$$I_D = 0.2 \text{ mA}$$

$$5 = i \left(4.7 \times 10^3 + 2 \times 10^3 \right) + 2 \times 10^3 (i - I_D) \quad \xrightarrow{i = 0.2} \\ 5 = i (4.7 \times 10^3 + 2 \times 10^3) + 2 \times 10^3 (i - 0.2) \quad \longrightarrow i = 7.76$$



~~$$5 = i (4.7 \times 10^3 + 2 \times 10^3) + 2 \times 10^3 (i - I_D) + V = 0 \\ (0.7 + (50 \times I_D))$$~~

~~$$0.4 + 0.7 + 0.01 + V = 0 \\ -1.11 = V$$~~

ii) Calculate the current in the R_2 resistance when $V = 2 \text{ V}$.

~~$$(2 \times 10^3 \times I_D) + 0.7 + (50 \times I_D) + 2 = 0$$~~

~~$$I_D = -1.31707 \text{ A}$$~~