

Name: KEY

ID#

Section #


Serial #

Questions 1 (4 points)

The power absorbed by the load in the balanced three-phase Y-Δ system shown in the figure is 150

kVA at 0.85 PF lagging. If $V_{an} = 400 \angle 0$, find:

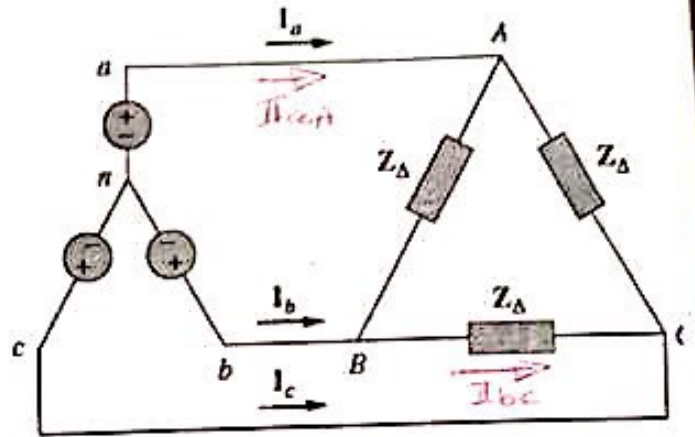- the phase current I_{bc} (magnitude and phase)
- the line current I_{aA} (magnitude and phase)
- the per-phase impedance.



$$V_{AB} = \sqrt{3} \times 400 \angle +30$$

$$= 692.82 \angle +30$$

$$S_{1\phi} = 50 \angle \cos^{-1}(0.85)$$

$$= 50 \angle 31.788 \text{ kVA}$$

(a)

$$S = V_{AB} I_{AB}^*$$

$$I_{AB}^* = \frac{S}{V_{AB}} = \frac{50 \times 10^3 \angle 31.79}{692.8 \angle 30}$$

$$= 72.2 \angle 1.79$$

$$I_{AB} = 72.2 \angle -1.79$$

$$I_{BC} = 72.2 \angle -121.79$$

(b)

$$I_{aA} = \sqrt{3} I_{AB} \angle -30$$

$$= 125 \angle -31.79$$

$$Z_{\Delta} = \frac{V_{AB}}{I_{AB}} = \frac{692.82 \angle +30}{72.2 \angle -1.79}$$

$$= 9.6 \angle 31.79$$

$$= 8.16 \angle 5.06$$

	1	2
I_{bc}	$125 \angle -31.79$	$9.6 \angle 31.79$
I_{ca}		
I_{ab}		

Questions (17 points)

In the figure below, two wattmeter's are properly connected to the unbalanced load supplied by a balanced source such that $V_{ac} = 100 \angle 30^\circ \text{ V}$.

- Determine the reading of each Wattmeter P_1 & P_2 .
- Determine the total real power of the load.
- Determine the total reactive power of the load.
- Calculate the total load power factor.

$$W_1 = V_{ac} \cdot I_a$$

$$W_2 = V_{bc} \cdot I_b$$

$$V_{ab} = 100 \angle 30^\circ = 173.2 \angle 30^\circ$$

$$V_{bc} = 173.2 \angle -90^\circ$$

$$V_{ca} = 173.2 \angle 150^\circ$$

$$V_{ac} = 173.2 \angle -30^\circ$$


$$I_{AB} = \frac{173.2 \angle 30^\circ}{20} = 8.66 \angle 30^\circ$$

$$I_{BC} = \frac{173.2 \angle -90^\circ}{10 - j10} = 13.0 \angle -45^\circ$$

$$I_{CA} = \frac{173.2 \angle 150^\circ}{12 + j5} = 13.82 \angle 127.5^\circ$$

$$I_{AA} = I_{AB} - I_{CA} = 16.8 \angle -21.4^\circ$$
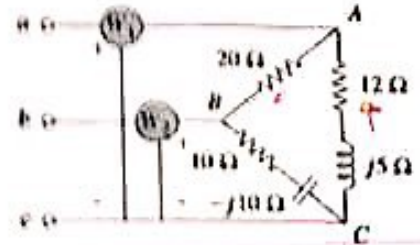
$$I_{BB} = I_{BC} - I_{AB} = 13.0 \angle -84.9^\circ$$



$$P_1 = V_{ac} \cdot I_a + \cos(\theta_v - \theta_i) = 173.2 \cdot 16.8 \cdot \cos(-30 + 21) = 2880.73 \text{ W}$$

$$P_2 = V_{bc} \cdot I_b + \cos(\theta_v - \theta_i) = 173.2 \cdot 13.0 \cdot \cos(-90 + 84) = 2242.7 \text{ W}$$

$$P_{total} = P_1 + P_2 = 5123.43$$

$$Q_{total} = \sqrt{3} (P_2 - P_1) = -11051$$

$$\theta = \tan^{-1} \left(\frac{Q_{total}}{P_{total}} \right)$$

$$= -12.17$$

$$PF = \cos \theta = 0.9775$$

P_1	P_2	P_{total}	Q_{total}	PF
2880.73	2242.7	5123.43	-11051	0.9775


2 2

1 1 1

P = 5123

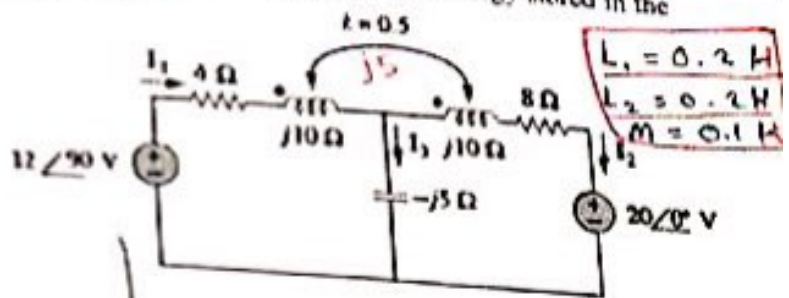Questions 3 (1 points)

The circuit shown below depicts a circuit with two mutually coupled coils. Find the value of the mutual inductance M , and write down the two loop equations that govern the circuit in their simplest form. If $i_1(t) = 5\sqrt{2} \cos(5t + 30^\circ) \text{ A}$ and $i_2(t) = 8\sqrt{2} \cos(5t + 50^\circ) \text{ A}$, then find the total energy stored in the two coils and their mutual inductance at $t = 0.1 \text{ sec}$ if $\omega = 50 \text{ rad/sec}$.



$$M = k \sqrt{L_1 L_2} = 0.1$$

$$j\omega M = j5$$

$$-12 \angle 90^\circ + 4I_1 + j10I_1 + (-j5)(I_1 - I_2) + j5I_2 = 0$$

$$20 \angle 0^\circ - j5(I_2 - I_1) + j10I_2 + 8I_2 + j5I_1 = 0$$

$$W(0.1) = \frac{1}{2} L_1 i_1^2(0.1) + \frac{1}{2} L_2 i_2^2(0.1) + M i_1(0.1) i_2(0.1)$$

$$= \frac{1}{2} \times 0.2 \times (5.13)^2 + \frac{1}{2} \times 0.2 \times (10.37)^2 + 0.1 \times 5.13 \times 10.37$$

$$= 18.7 \text{ J}$$

$$i_1(t) = \sqrt{2} \times 5 \cos(\omega t + 30^\circ)$$

$$i_1(0.1) = \sqrt{2} \times 5 \times \cos\left(5 \times \frac{180}{\pi} + 30^\circ\right) = 5.13$$

$$i_2(t) = \sqrt{2} \times 8 \cos(\omega t + 50^\circ)$$

$$i_2(0.1) = \sqrt{2} \times 8 \times \cos\left(5 \times \frac{180}{\pi} + 50^\circ\right) = 10.37$$

Equations	M	W _{total}
1) $(j5 + 4)I_1 + j10I_2 = 12 \angle 90^\circ$	1	1
2) $j10I_1 + (8 + j5)I_2 = 20 \angle 180^\circ$	j5 0.1	18.70 J



$$I_3 = I_1 - I_2$$

$$13.405$$

$$9.34$$

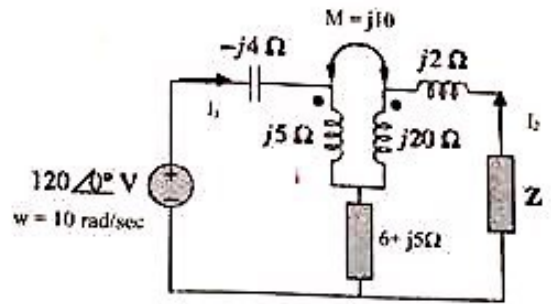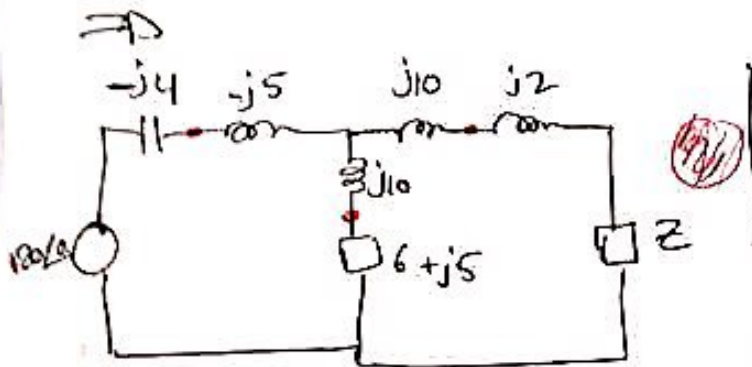Question 4 (5 points)

For the circuit shown in the figure, replace the transformer by its T-equivalent model and then find the value of the load Z that maximize the power transferred to the load. What is this maximum power.



$$Z_{Load} = Z_{Th}$$

$$Z_{Th} = -j9 // (6 + j15) + j12$$

$$= \frac{-j9 * (6 + j15)}{6 + j6} + j12$$

$$= 7.72 \angle -29 = 6.75 - j3.75$$

$$Z_{Load} = 7.72 \angle +29$$

$$= 6.75 + j3.75$$

$$P_{max} = \frac{V_{th}^2}{8R}$$

rms

$$V_{th} = \frac{6 + j15}{6 + j6} * 120 \angle 0$$

$$= 228.47 \angle 23.2$$

$$R = Z \cos \theta$$

$$= 6.75 \text{ } \Omega$$

$$P_{max} = 1933.28$$

$$\text{OR } 966.64$$

T-equivalent (draw and label)	Z_{Load}	P_{max}
	$7.72 \angle 29$	1933.28 OR 966.64

both

Questions 5 (5 points)

If the line voltage in the figure below is 2081.0 V (with abc sequence), determine the source currents, the current in the neutral line I_{nN} , and the load side neutral voltage V_N .

$$I_a + I_b + I_c = I_{nN}$$

⇒

$$\frac{V_a - V_N}{5 + j5} + \frac{V_b - V_N}{j5} + \frac{V_c - V_N}{5 - j5} = \frac{V_N}{5}$$

$$\Rightarrow \frac{120 \angle -30^\circ - V_N}{5 + j5} + \frac{120 \angle -150^\circ - V_N}{j5} +$$


$$+ \frac{120 \angle 90^\circ - V_N}{5 - j5} = \frac{V_N}{5}$$

⇒ Solving for V_N

$$V_N = 57.15 \angle 166.67^\circ$$

$$I_a = \frac{V_a - V_N}{5 + j5} = 24.8 \angle -69.6^\circ$$
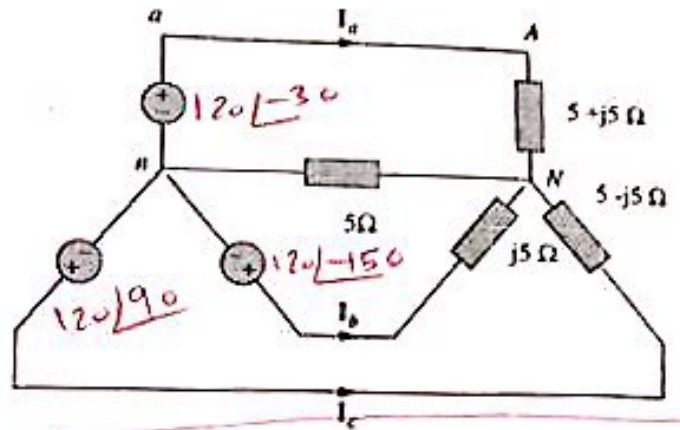
$$I_b = \frac{V_b - V_N}{j5} = 17.54 \angle 146.57^\circ$$



$$I_c = \frac{V_c - V_N}{5 - j5} = 17.03 \angle 107^\circ$$


$$I_{nN} = \frac{-V_N}{5} = 11.42 \angle -13.3^\circ$$

I_a	I_b	I_c	I_{nN}	V_N
24.8 / -69.6	17.5 / 146.5	17.03 / 107	11.42 / -13	57.15 / 166.67

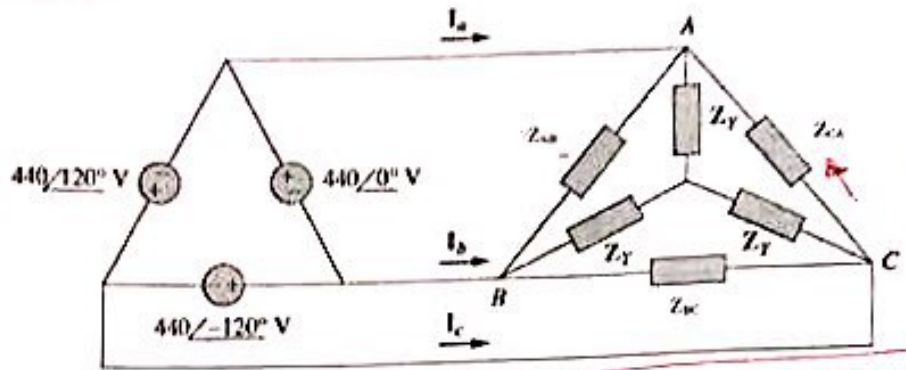Questions 6 (5 points)

The circuit drawn shows a balanced 3 phase A source of 440 V line to line voltage supplying a balanced Y connected load of $Z_Y = 6 + j8$ connected in parallel with unbalanced Delta load with $Z_{AB} = 6 + j8$, $Z_{BC} = 8 + j12$, and $Z_{CA} = 10 + j6$. Find:

- the phase current in phase A of the Y load.
- The phase current in phase AB in the Delta load.
- The total current in line A supplied by the source.



$$\textcircled{a} I_{A(Y)} = \frac{V_{an}}{6 + j8}$$

$$= \frac{440}{\sqrt{3}} \angle -30^\circ$$

$$= \frac{254 \angle -83.13^\circ}{6 + j8}$$

$$I_{CA} = \frac{440 \angle 120^\circ}{10 + j6} = 37.73 \angle 99^\circ$$

$$I_{AD} = I_{AB} - I_{CA} = 77.33 \angle -70.5^\circ$$

$$\textcircled{b} I_{AB} = \frac{V_{AB}}{Z_{DAB}} = \frac{440 \angle 0^\circ}{6 + j8}$$

$$= 44 \angle -53.13^\circ$$

$$I_{A \text{ total}} = I_{AD} + I_{AY}$$

$$= 77.33 \angle -70.56^\circ + 25.4 \angle -83.13^\circ$$

$$= 102.27 \angle -73.66^\circ$$

$$\textcircled{c} I_{BC} = \frac{V_{BC}}{Z_{BC}} = \frac{440 \angle -120^\circ}{8 + j12}$$

$$= 27.73 \angle -176.31^\circ$$

$I_{\text{A phase D}}$	$I_{\text{A phase Y}}$	$I_{\text{A total}}$
$25.4 \angle -83.13^\circ$	$44 \angle -53.13^\circ$	$102.27 \angle -73.66^\circ$

