



# Power 1 Notebook



**DR. DAIFALLAH DALBEEH**


**BY : SAUSAN ALMOHTASEB**

Monday  
28/9

## \* Basic Concept (per unit revision) :-

in the solution of the P.S. problems  
the per phase ckt is used.

$$Z_b = \frac{V_b^2}{S_b}$$

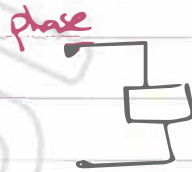

$$\Delta Z_b = \frac{(V_b/\sqrt{3})^2}{S_{3\phi}/3}$$



neutral

\* Usually in the specification of power systems lines voltages and 3 $\phi$

apparent power are given.


$$Z_b = \left( \frac{V_L^2}{S_{3\phi}} \right) = \frac{(V_L/\sqrt{3})^2}{S_{3\phi}/3}$$

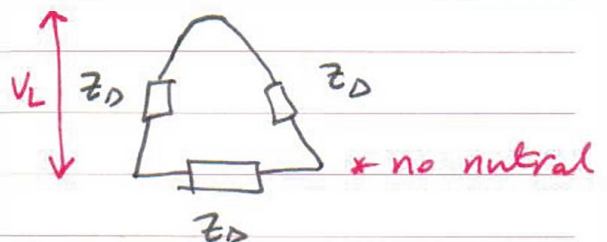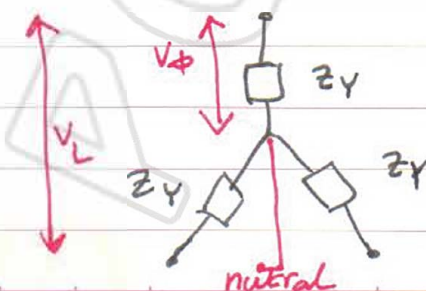→ This is the express of  $Z_b$  irrespective of the type of connection



\* The given per unit value of the impedance of the power system components (i.e.: generator, transformer, lines & loads) are usually based on the ratings of such components; however, to solve a given power system, then a common reference value should be used. Consequently all the given per unit values should be updated according to this common reference, as follows:-

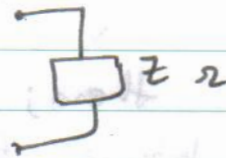\* if one select a reference value say  $Z_{b1} \Omega$



$$Z_1 (pu) = \frac{Z}{Z_{b1}}$$

\* if the base value is  $Z_{b2} \Omega$

$$\therefore Z_2 (pu) = \frac{Z}{Z_{b2}}$$

$$\rightarrow \frac{Z_2 \text{ (pu)}}{Z_1 \text{ (pu)}} = Z \times \frac{Z_{b1}}{Z} = \frac{Z_{b1}}{Z_{b2}}$$

$$= \frac{(V_{b1})^2}{S_{b1}} \cdot \frac{S_{b2}}{(V_{b2})^2}$$


$$= \left( \frac{V_{b1}}{V_{b2}} \right)^2 \times \frac{S_{b2}}{S_{b1}}$$

\* if 1 represent old value  
2 represent new value

then;

$$\rightarrow Z_{\text{new (pu)}} = Z_{\text{old (pu)}} \times \left( \frac{V_{b \text{ old}}}{V_{b \text{ new}}} \right)^2 \cdot \left( \frac{S_{b \text{ new}}}{S_{b \text{ old}}} \right)$$

### \* illustration:

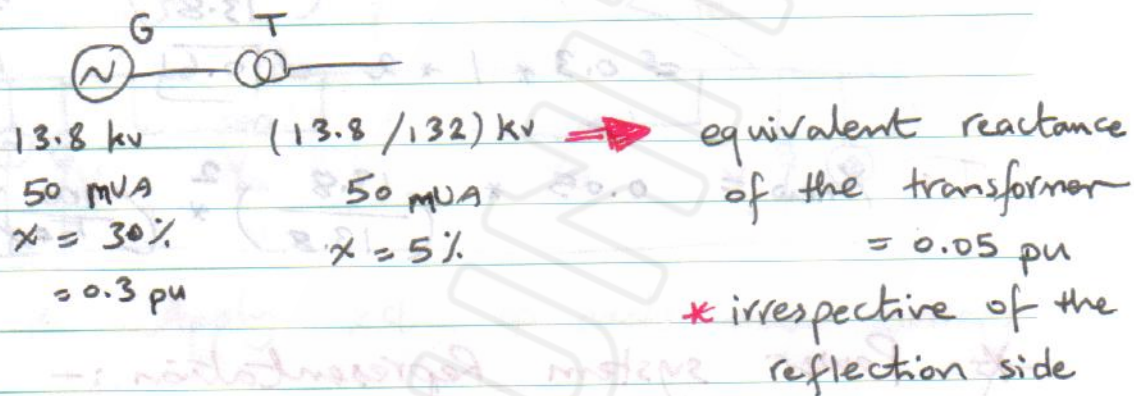

\* Usually in power station G is a 3-phase synch. generator. When generated voltage = 13.8 kV  
synch. reactance =  $X = 0.3$  pu

\* If this system is to be solved by using base value of (13.8 kV) and (100 MVA), then update the per unit values if necessary as follows:

$\rightarrow$

$$G: X_{\text{new}} = X_{\text{old}} \times \left( \frac{13.8}{13.8} \right)^2 \times \frac{100}{50}$$
$$= 0.3 \times 1 \times 2 = \boxed{0.6}$$

$$T: X_{\text{new}} = 0.05 \times \left( \frac{13.8}{13.8} \right)^2 \times \left( \frac{100}{50} \right) = \boxed{0.1}$$

### \* Power system Representation :-


There are two basic approaches:

- 1) mathematical rep.
- 2) graphical rep.

#### 1) mathematical:

this is based on the concept of the node equations, as follows:-

→

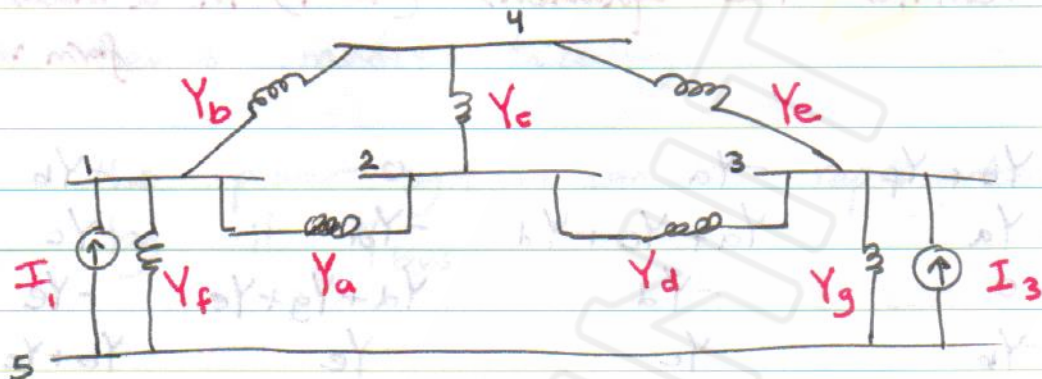

\* Apply KCL @ each node:

$$\begin{aligned} \text{(node 1): } & (V_1 - V_2) Y_a + (V_1 - V_4) Y_b + V_1 Y_f = I_1 \\ & V_1 (Y_a + Y_b + Y_f) - V_2 Y_a - Y_b V_4 = I_1 \dots \textcircled{1} \end{aligned}$$

\* by similar approach at other nodes it can be found:-

$$\begin{aligned} \text{(node 2): } & -V_1 Y_a + V_2 (Y_a + Y_c + Y_d) \\ & -V_3 Y_d - V_4 Y_c = 0 \dots \textcircled{2} \end{aligned}$$

$$\begin{aligned} \text{(node 3): } & -V_2 Y_d + (Y_d + Y_g + Y_e) V_3 \\ & -V_4 Y_e = I_3 \dots \textcircled{3} \end{aligned}$$

$$\begin{aligned} \text{(node 4): } & -V_1 Y_b - V_2 Y_c - V_3 Y_e + V_4 (Y_b + Y_c + Y_e) \\ & = 0 \\ & \textcircled{4} \end{aligned}$$

\* rewrite the equations (1-4) in a matrix form :-

$$\begin{bmatrix} Y_a + Y_b + Y_f & -Y_a & 0 & -Y_b \\ -Y_a & Y_a + Y_c + Y_d & -Y_d & -Y_c \\ 0 & -Y_d & Y_d + Y_g + Y_e & -Y_e \\ -Y_b & -Y_c & -Y_e & Y_b + Y_e + Y_c \end{bmatrix} \quad (*)$$

$$\begin{bmatrix} * \end{bmatrix} * \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} I_{00} \\ I_{00} \\ I_3 \\ 0 \end{bmatrix}$$

(5) can be written :

$$[Y][V] = [I]$$

this is called nodal bus admittance matrix written or bus voltages

the current source entering nodes or sometimes called the current injected to the nodes

$Y_{bus}$  where:

- i) its element  $Y_{ii} = \Sigma$  of admittances connected directly to the  $(i^{th})$  bus
- ii) its element  $Y_{ij} = -1 * \text{equivalent admittance between the } (i^{th}) \text{ and } (j^{th}) \text{ buses}$



\* hence mathematically:

the power system can be represented by its  $Y_{bus}$

note:  $[Y_{bus}]^{-1} \triangleq Z_{bus}$

where  $Z_{bus}$  is called Bus impedance matrix =  $\begin{bmatrix} Z_{11} & Z_{12} & \dots & Z_{1n} \\ \vdots & \vdots & \ddots & \vdots \\ Z_{n1} & Z_{n2} & \dots & Z_{nn} \end{bmatrix}$

Note: to find  $Z_{bus}$ :

i) find  $Y_{bus}$


ii) find its inverse:  $[Y_{bus}]^{-1}$

\* given the  $Y_{bus}$  matrix, find the corresponding equ. network:


\* [2] Graphical representation :-

this is represented by the so called one-line or single-line diagram, defined and deduced as follows:-

\* Consider the following sys. :-

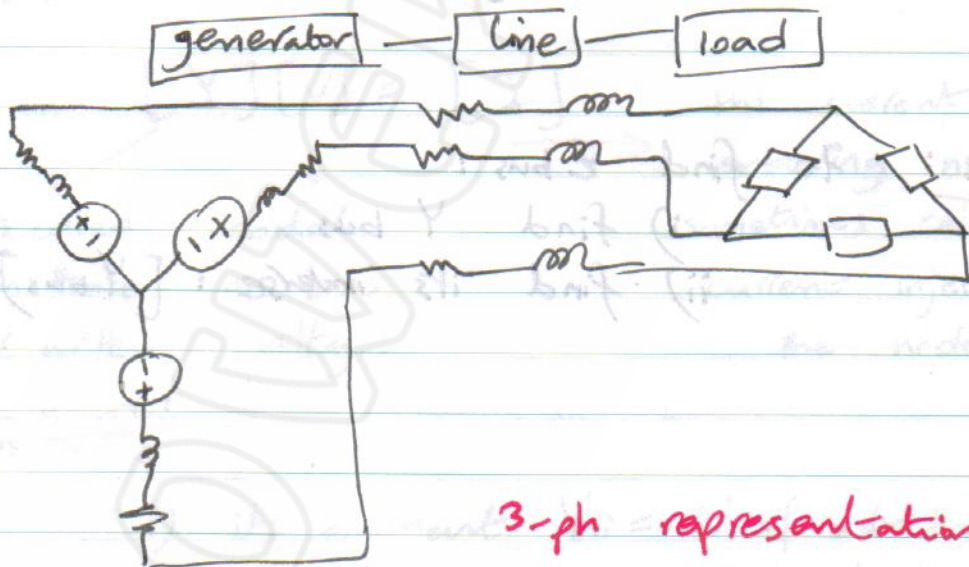

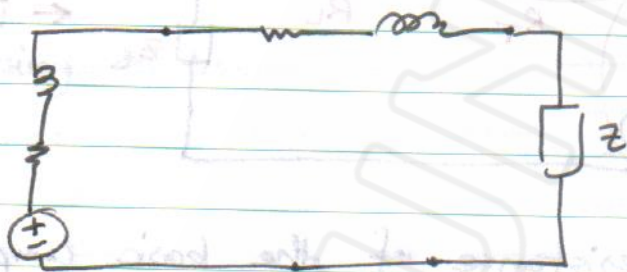
\* if the system is balanced, then the perphase representation can be used



→ this is also called impedance diagram.

\* if the resistance of the elements are neglected then it is called **reactance diagram**

Monday  
5/10

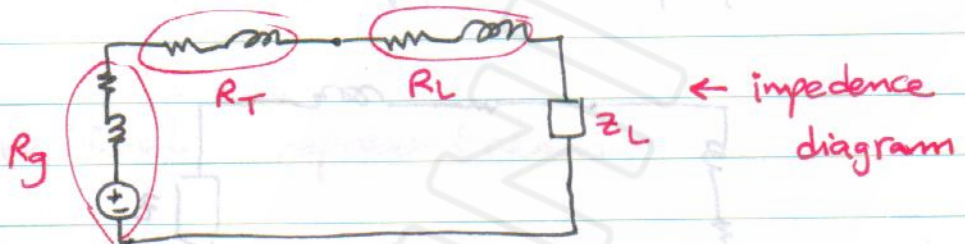

\* if the Resistance of the basic components are neglected, then the diagram is called "reactance diagram".

note: this circuit is usually used in power system analysis

now if one is only interested to see how the components of a given power sys. are interconnected, then these components are represented by the standard symbol instead of its equivalent ckt, the resultant diagram called single-line or one-line diagram

\* Component

Symbol

rotating machinery



~: generator  
M: motor

2 winding trans.



Transmission line



Busbar (node)



Load



ckt breaker





isolator



Current transformer




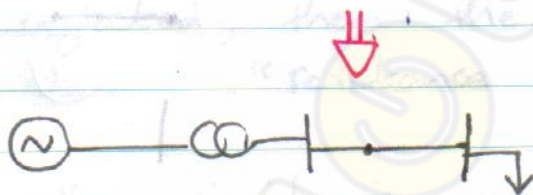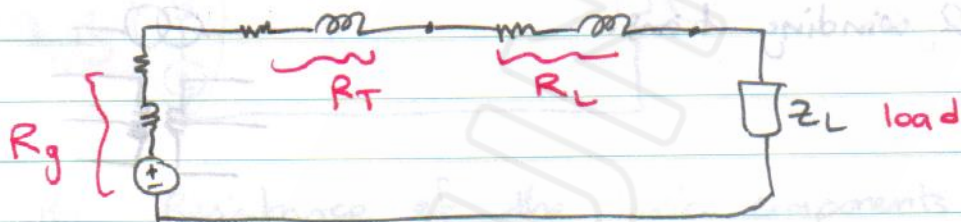hence, for our system, the single line diagram as follows:



\* given data on the single line diagram depend on the required analysis or Application

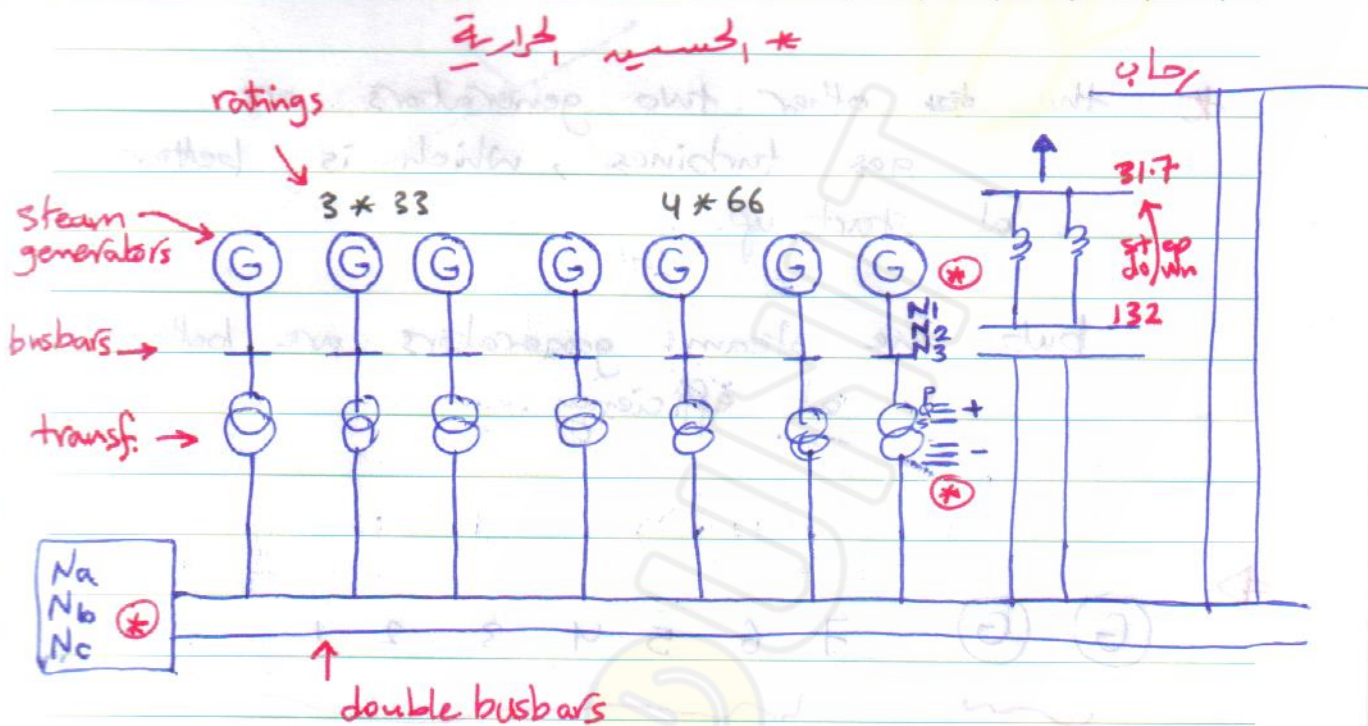\* As a practical example, consider the Jordanian electric single-line-diagram



\* the data on the diagram are the results of a given load flow analysis.

\* load flow is to calculate voltages at busbars and power flow in the system for a given load conditions.



* Na: voltage in kv	* N1: Power (MW)
Nb: voltage in per unit	N2: reactive $Q$ (MVAR)
Nc: voltage in angle	N3: apparent $S$ (MVA)

\* when we add + & - values it will give the losses

\* the ~~the~~ other two generators are gas turbines, which is better at start up.

but the steam generators are better at efficiency.

⇒

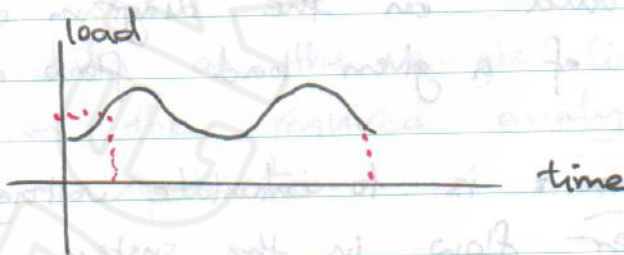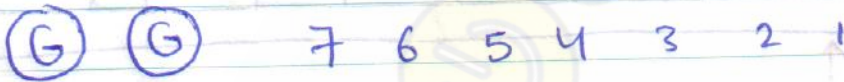


$$* \sum P_{in} = \sum P_{out}$$

Ex: Draw the single-line diagram of a given subsystem?



\* Consider a Y-Δ Transformation (Yd):

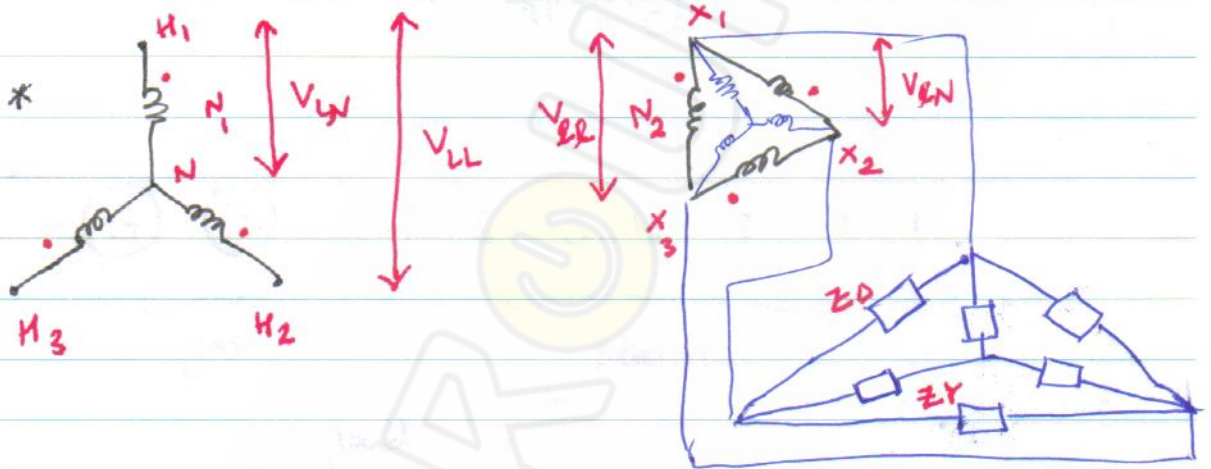$N_1$  and  $N_2$  are the number of turns at the HV and LV winding, which have voltage in phase.





\* from figure \* :

$$\frac{|V_{LN}|}{|V_{LL}|} = \frac{N_1}{N_2} \quad \text{--- (1)}$$

$$\frac{V_{LN}}{\sqrt{3} V_{LN}} = \frac{N_1}{N_2}, \quad \frac{|V_{LN}|}{|V_{LN}|} = \frac{N_1}{N_2/\sqrt{3}} \quad \text{--- (2)}$$

from 2: deduce the equ. per-phase ckt:

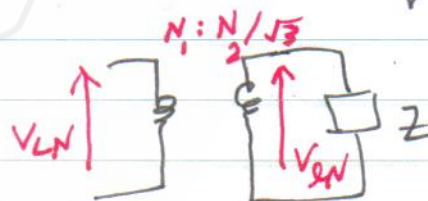


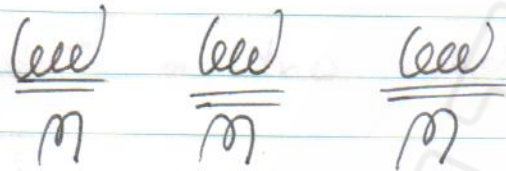

### \* Illustration:

consider a Y-Y connection among the  
 rep. is that the letters  $H_1, H_2, H_3$   
 used for high voltage side

and  $X_1, X_2, X_3$  for low voltage.

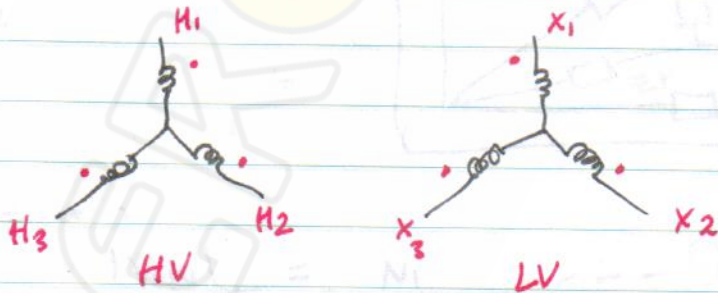


Sometimes the letters  $A, B, C$  used for HV  
 and  $a, b, c$  used for LV
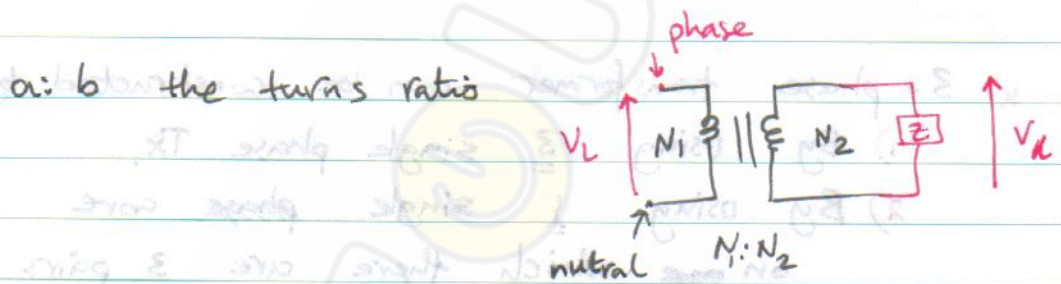
## \* Concept of parameters Reflection in 3 phase Tx

It was found that the Reflection in the single phase Tx is as follows:-

→  $N_1, N_2$  are the actual # of turns ratio.



$$a = \frac{N_1}{N_2} : 1$$

\* It was found that:-

- 1) to reflect  $Z$  to (a) side \* it by  $a^2$
- 2)  $V$  to (a) side \* it by  $a$
- 3)  $I$  to (a) side  $\div$  it by  $a$

## \* 3-phase transformer:-

The objective is to find its equivalent per phase ckt for any type or connection

## \* Revision and Basic concept:-

\* 3-phase transformer can be constructed by:

- 1) By using 3 single phase Tx.
- 2) By using 1 single ~~phase~~ core on ~~one~~ which there are 3 pairs of windings.

\* The winding can be connected as:

Y-Y, Y- $\Delta$ ,  $\Delta$ -Y,  $\Delta$ - $\Delta$

\* in the Y-Y or  $\Delta$ - $\Delta$  the phase voltages of the HV and LV side are in phase.

However in the Y- $\Delta$  or  $\Delta$ -Y there is a phase shift between the phase voltages


\* The winding or the core which are linked by the same flux linkage there induced voltages in phase.  
(useful in graphical rep.)

\* Consequently in graphical ~~core~~ schematic rep. such coils are drawn parallel to each other with a dot is located at one end of each coil or the coil at one phase are drawn parallel to each other.

Monday

12/10
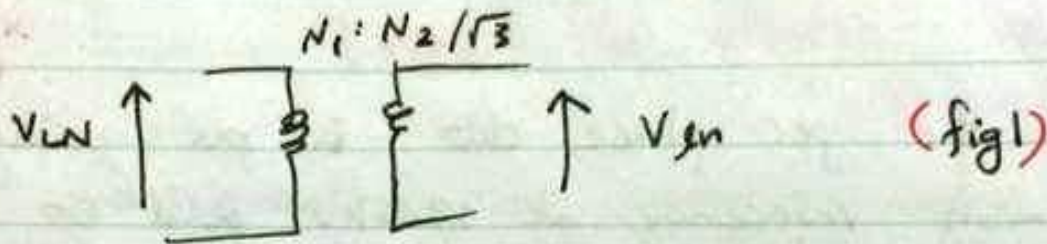
$$\begin{array}{l} \text{HV} \leftarrow \\ \text{LV} \leftarrow \end{array} \frac{V_{LN}}{V_{Ln}} = \frac{N_1}{N_2/\sqrt{3}} \rightarrow \text{effective turns ratio}$$




for all type of connections ; although the effective turns ratio is different , but it is also equal to line voltage ratio , hence (fig 1) can be used to reflect low voltage impedance ( $Z_L$ ) to the high voltage impedance ( $Z_H$ ) or the other ways round:

$$Z_H = \left( \frac{V_{LL}}{V_{LN}} \right)^2 Z_L$$

or

$$Z_L = \left( \frac{V_{LN}}{V_{LL}} \right)^2 Z_H$$

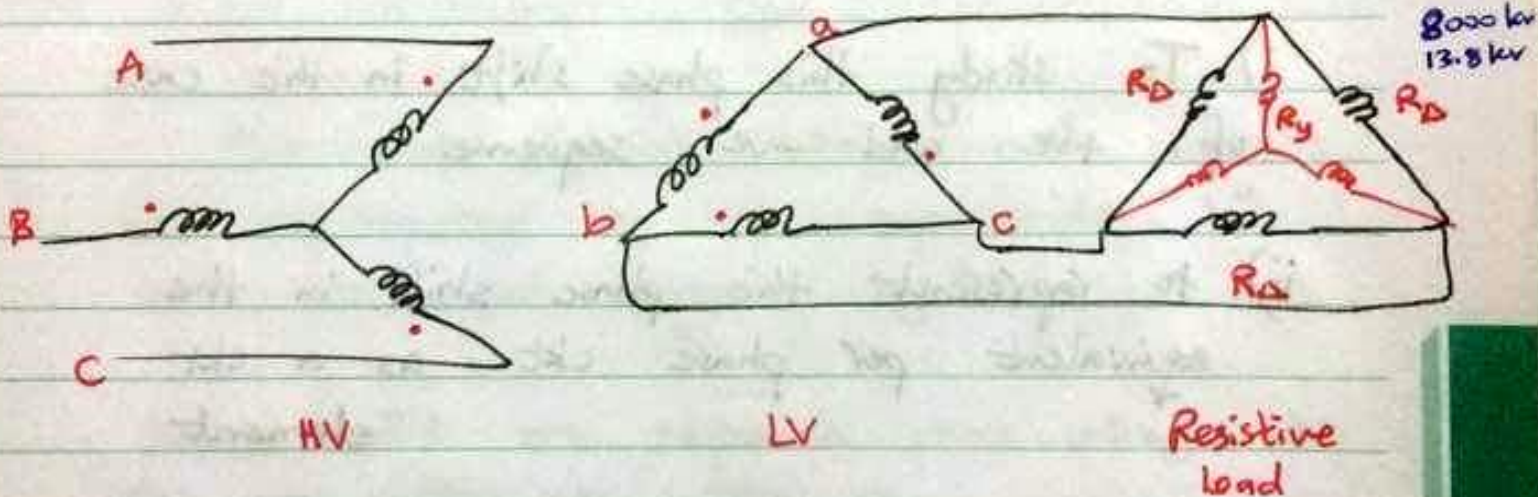\* e.g.: A balanced  $\Delta$ -connected resistive load of 8000 kW is supplied by a low voltage  $\Delta$  connected side of a Y- $\Delta$  transformer rated at  $10^4$  kVA, 138 / 13.8 kV. find the load resistance in ohms seen between the phase and neutral on the HV side assume rated voltage is supplied to primary.



$$\Rightarrow R_D = ? \quad , \quad P = \frac{V^2}{R}$$

$$\rightarrow R_D = \frac{V^2}{P} = \frac{(13.8 \times 10^3)^2}{\frac{8000 \times 10^3}{3}} = 71.415 \, \Omega$$

$$R_Y \triangleq \frac{R_D}{3} = \frac{71.415}{3} = 23.805 \, \Omega$$

\* Requirement:  $R_H = \left( \frac{V_{LL}}{V_{HL}} \right)^2 \times R_L \leftarrow R_Y$

$$R_H = \left( \frac{138}{13.8} \right)^2 \times 23.805 = 2380.5 \, \Omega$$

## \* Phase Shift in 3-phase transformer :-


As stated before Y- $\Delta$  or  $\Delta$ -Y introduce phase shift between the corresponding voltages on the HV and LV sides.

## \* Objectives:

- i) To study this phase shift in the case of +ve and -ve sequence
- ii) to represent this phase shift in the equivalent per phase ckt. as a ckt element
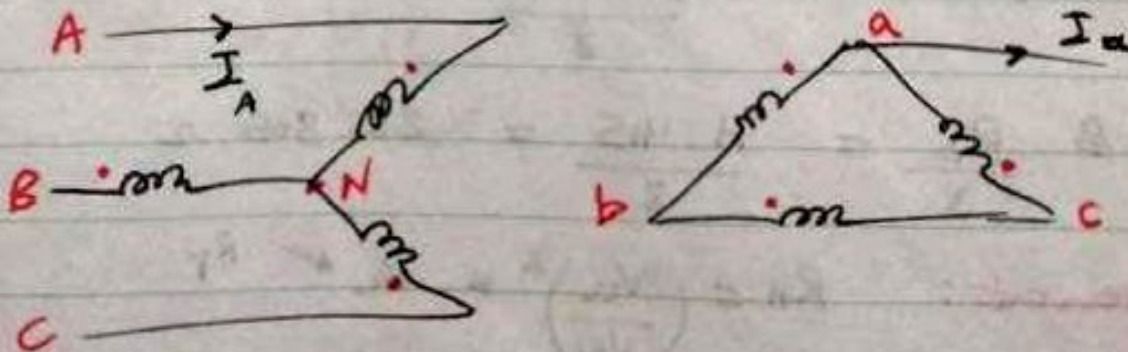
## \* Procedure:

consider a Y $\Delta$  3 phase transformer





Now:

$V_{AN}$  is in phase with  $V_{ab}$   
 $V_{BN}$  — — — — —  $V_{bc}$   
 $V_{CN}$  - - - - -  $V_{ca}$

let:  $N_1$  and  $N_2$  are the number of turns of the HV and LV winding of the corresponding in phase winding.

### \* Convention :-

The +ve sequence voltages and currents are represented by the superscript "1" and the -ve sequence by "2".

hence, the +ve sequence phase voltages on the HV side are written as:


$$V_{AN}^{(1)}, V_{BN}^{(1)}, V_{CN}^{(1)}$$

→ sometimes this is simplified to:

$$V_A^{(1)}, V_B^{(1)}, V_C^{(1)}$$

\* Let us solve the problem by using the concept of phasor diagram:


+ve sequence:

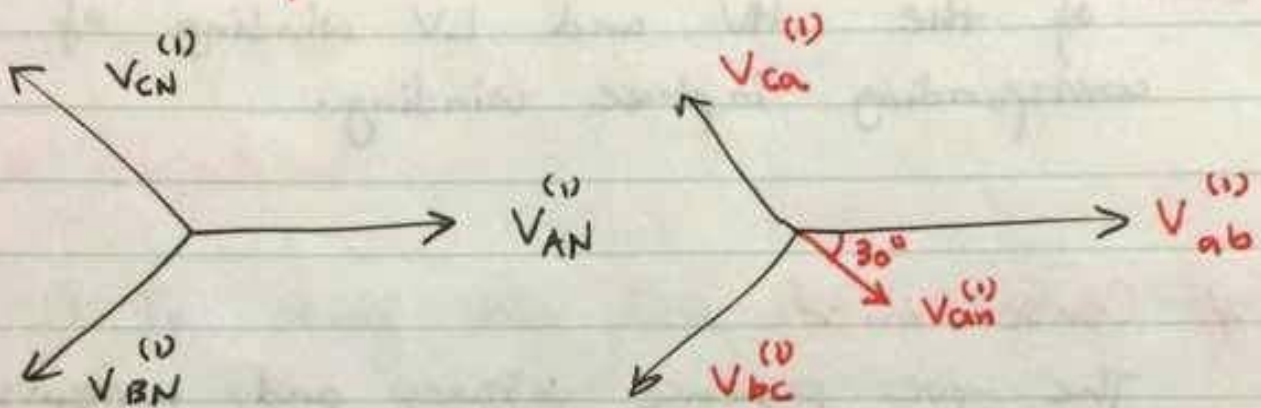

$$* \quad V_{AN}^{(1)} = \frac{N_1}{N_2 \sqrt{3}} V_{an}^{(1)} \angle 30^\circ$$

$$V_{AN}^{(1)} = \frac{N_1}{N_2 \sqrt{3}} V_{an}^{(1)} \angle 30^\circ \quad \text{----- (1)}$$

-ve sequence:-

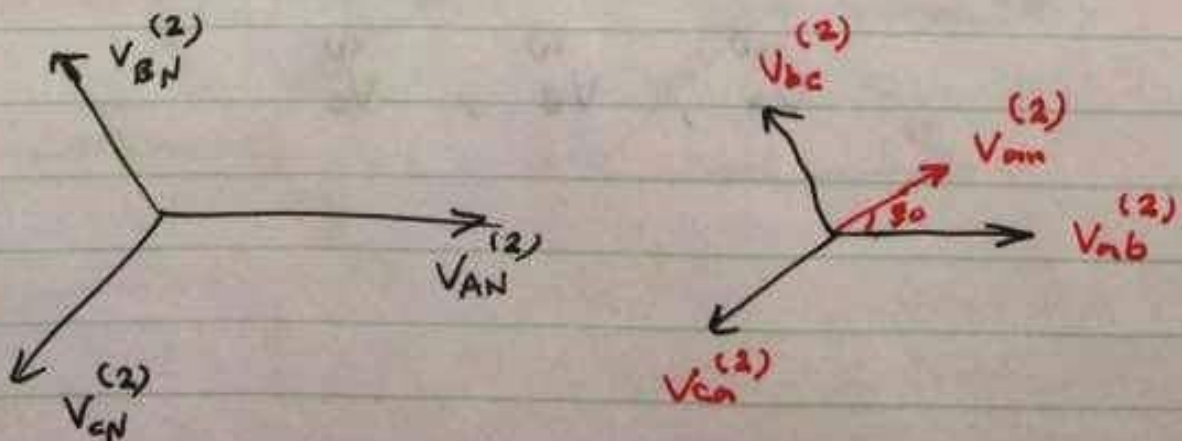

$$V_{AN}^{(2)} = \frac{N_1}{N_2/\sqrt{3}} V_{an}^{(2)} \angle -30^\circ$$

$$V_{AN}^{(2)} = \frac{N_1}{N_2/\sqrt{3}} V_{an}^{(2)} \angle -30^\circ \quad \text{----- (2)}$$

### \* Comments :-

i) in the +ve phase sequence HV quantities (i.e.: voltages and currents) lead the corresponding lw V quantities by  $30^\circ$ , where in the -ve phase sequence, the HV quantities lags LV by  $30^\circ$ .

ii) Since it was found that :

$$\frac{|V_{LL}|}{|V_{ll}|} = \frac{N_1}{N_2/\sqrt{3}}$$

$\therefore$  (1) and (2) can be written :-

$$\frac{V_{AN}^{(1)}}{|V_{LL}|} = \frac{V_{an}^{(1)}}{|V_{ll}|} \angle 30^\circ \quad \text{----- (3)}$$

$$\frac{V_{AN}^{(2)}}{|V_{LL}|} = \frac{V_{an}^{(2)}}{|V_{ll}|} \angle -30^\circ \quad \text{----- (4)}$$

\* if  $|V_{LL}|$  and  $|V_{LL}|$  are the rated voltages and used as base values, then:

$$3 \rightarrow V_{AN}^{(1)} \text{ (pu)} = V_{an}^{(1)} \text{ (pu)} \angle 30^\circ \text{ --- (5)}$$


$$4 \rightarrow V_{AN}^{(2)} \text{ (pu)} = V_{an}^{(2)} \text{ (pu)} \angle -30^\circ \text{ --- (6)}$$

hence, in (pu) the (HV) and (LV) quantities have the same magnitude

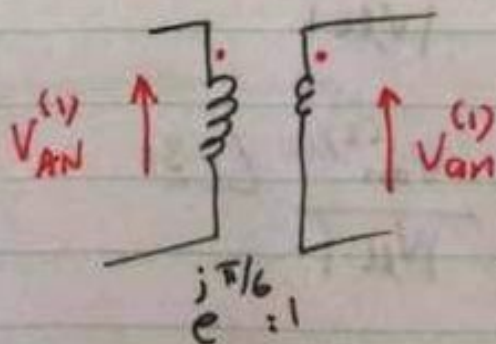
iii) in normal operation, one use +ve sequence:


$$\therefore 5 \rightarrow \frac{V_{AN}^{(1)} \text{ (pu)}}{V_{an}^{(1)} \text{ (pu)}} = 1 \angle 30^\circ = \frac{e^{j\pi/6}}{1} \text{ --- (7)}$$

graphically as a ckt diagram or element (7) can be represented as:



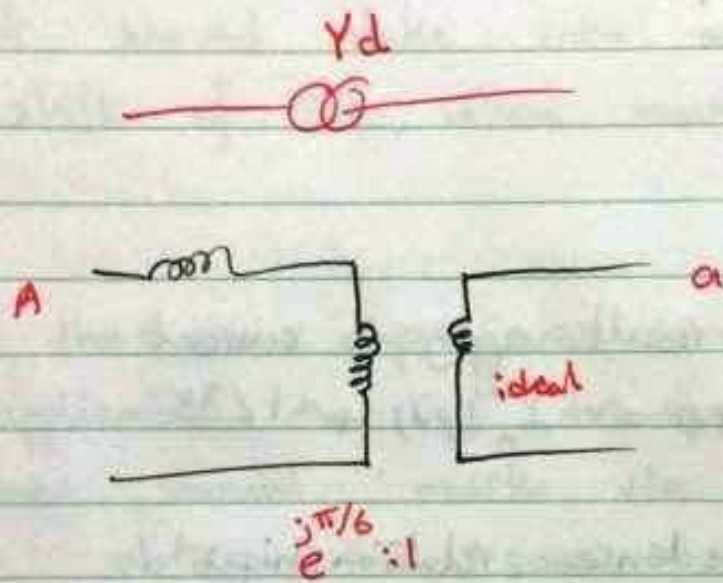$\therefore$  phase shift in  $Y-\Delta$  or  $\Delta-Y$  is represented by ideal transformer with a complex turns ratio



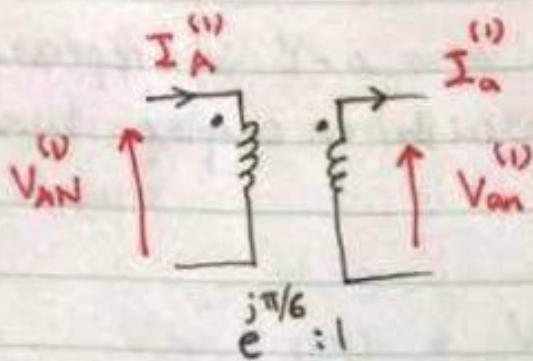

### \* Comments :-

i) The same result apply to current

$$I_A^{(1)} (\text{pu}) = I_a^{(1)} (\text{pu}) + 1 \angle 30$$

ii) hence, Impedence relationship:

$$\frac{V_{AN}^{(1)}}{I_A^{(1)}} = \frac{V_{an}^{(1)} * 1 \angle 30}{I_a^{(1)} * 1 \angle 30}$$

$$Z_{HV} (\text{pu}) = Z_{LV} (\text{pu})$$

iii) power relationship:

$$V_{AN}^{(1)} * (I_A^{(1)})^* = (V_{an}^{(1)} \angle 30) * (I_a^{(1)} \angle 30)$$


$$V_{AN}^{(1)} (I_A^{(1)})^* = V_{an}^{(1)} I_a^{(1)*}$$

→ If one is only interested in power calculations then there is no need to represent Y-D or D-Y by an Ideal transformer.

iv) in general as far as analysis concern, then one may not include the ideal transformer in the (pu) perphase ckt. But should take into account the phase shift of  $30^\circ$ , when moving from HV  $\rightleftharpoons$  LV

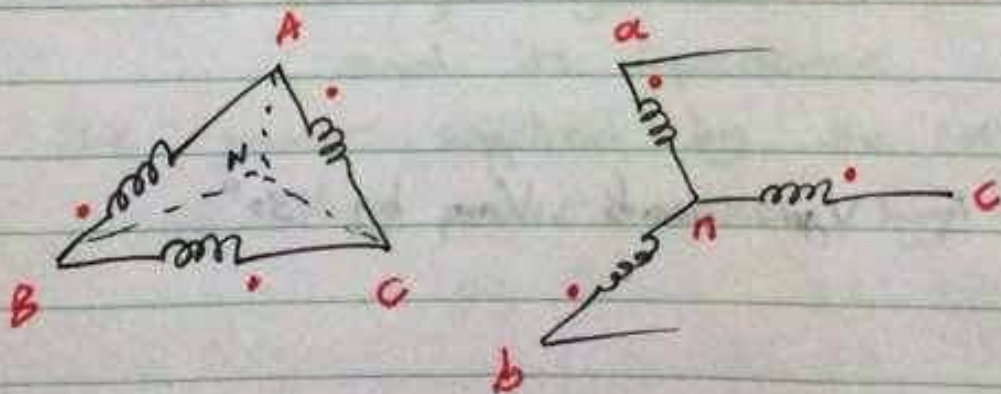v) the same previous results of Yd are applicable to Dy transformer, however one should mark the terminals to obtain the same results

\* As an illustration, consider the voltage relationship in the Dy:




\* from the schematic diagram :

$V_{AC}$  is in phase with  $V_{an}$

$V_{CB}$  --- --- ---  $V_{cn}$

$V_{BA}$  --- --- ---  $V_{bn}$

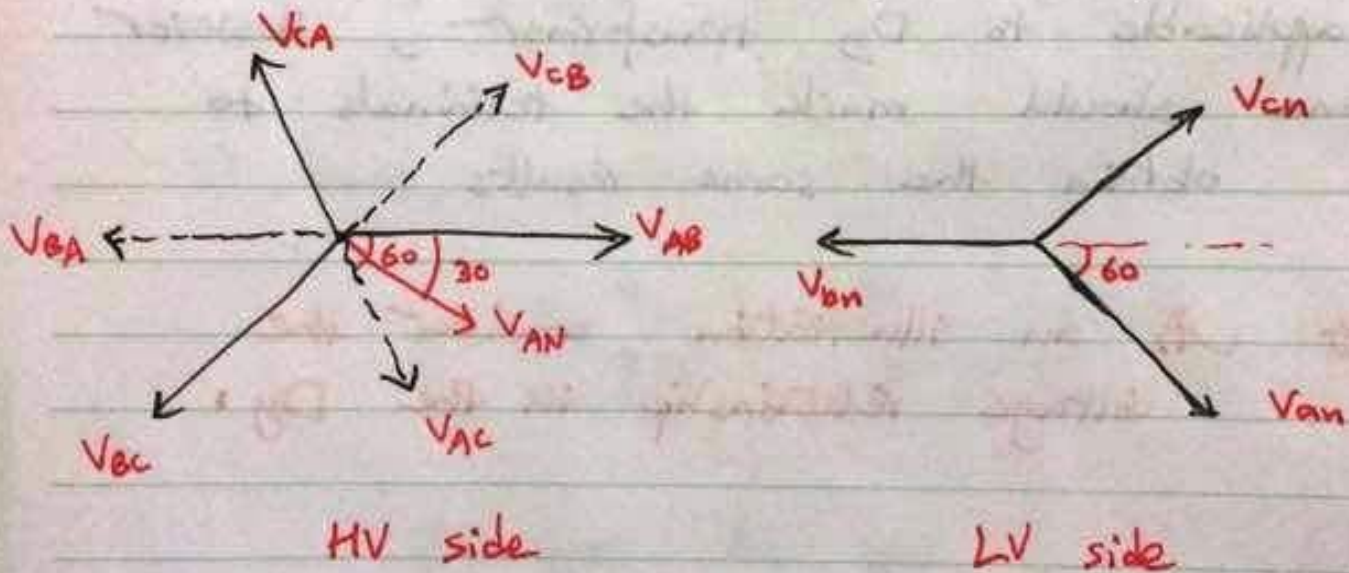\* by using the power diagram for +ve phase sequence



∴  $V_{AN}$  leads  $V_{an}$  by  $30^\circ$



\* Ex: Show for  $D_y$  in +ve phase sequence  $I_A$  leads  $I_a$  by  $30^\circ$  (prove).

\* e.g: A 3-phase generator supplying a load through a 3 phase transformer rated at 12 kV  $\Delta$  / 600 V Y, 600 kVA, the transformer has per phase reactance of 10%. The line voltage and current at the terminal of the generator are 11.9 kV and 20 A respectively. If the power factor seen by the G is 0.8 lagging, then by using +ve phase sequence, find:

- i) the current, voltage at the load and its impedance
- ii) the power supplied by the (HV) side and the power taken by the load

$\Rightarrow$


$$I_g P_{1.0} = P_{1.0} = (11.9 \text{ kV})$$

$$P_{1.0} = P_{1.0} = (11.9 \text{ kV})$$

Sol:



per phase ckt

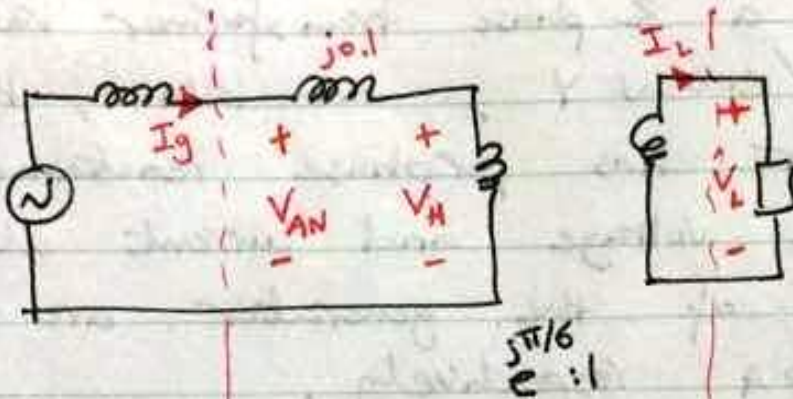

generator

transformer

load

\* let the base values be (12 kV) and (600 kVA)

$$\therefore 600 \times 10^3 = \sqrt{3} \times 12 \times 10^3 \times I_b$$

$$\rightarrow I_b = 28.87 \text{ A}$$

$$\rightarrow |I_g| = \frac{20}{28.87} = 0.69 \text{ pu}$$

$$\rightarrow |V_{AN}| = \frac{11.9}{12} = 0.99 \text{ pu}$$

$$\therefore V_{AN} = 0.99 \angle 0^\circ$$

$$I_g = 0.69 \angle \cos^{-1}(0.8) = 0.69 \angle -36.87^\circ$$

$$\rightarrow V_H = 0.99 \angle 0 - j0.1 * 0.69 \angle 36.87$$


$$V_H = 0.952 \angle -3.6^\circ$$

$$\therefore V_L = 0.952 \angle -3.6^\circ - 30^\circ$$

$$= 0.952 \angle -33.6^\circ$$

$$\rightarrow I_L = 0.69 \angle -36.87^\circ - 30^\circ$$

$$= 0.69 \angle -66.87^\circ$$

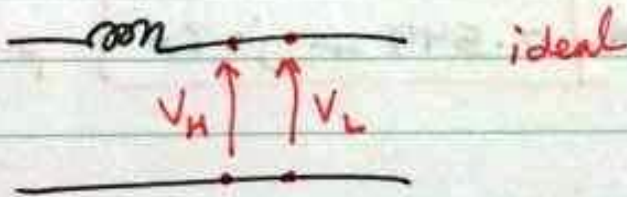

$$\rightarrow Z = \frac{V_L}{I_L} = \frac{0.952 \angle -33.6^\circ}{0.69 \angle -66.87^\circ} = 1.38 \angle 33.27^\circ \text{ pu}$$

$$\rightarrow Z_b = \frac{(V_b)^2}{S_b} = \frac{(600/\sqrt{3})^2}{\frac{600 \times 10^3}{3}}$$

$$\Rightarrow Z (\Omega) = Z (\text{pu}) * Z_b$$

$$\begin{aligned}
 \rightarrow S_{gen} &= V_{AN} * I_g^* \\
 &= 0.99 \angle 0 * 0.69 \angle 36.87 \\
 &= 0.6831 \angle 36.87
 \end{aligned}$$

$$\boxed{S = 0.546 + j0.41} \text{ pu} \quad \boxed{\text{in}}$$


$$\begin{aligned}
 S_{load} &= V_L * I_L^* \\
 &= 0.952 \angle 33.6 * 0.69 \angle 66.89
 \end{aligned}$$

$$= \cancel{0.657} \boxed{0.549 + j0.36} \text{ pu} \quad \boxed{\text{out}}$$

$*$  we have no resistors  $\rightarrow$  real part  $\approx$   
 but<sup>in</sup> the imaginary we have losses  
 because of  $\underline{m}$
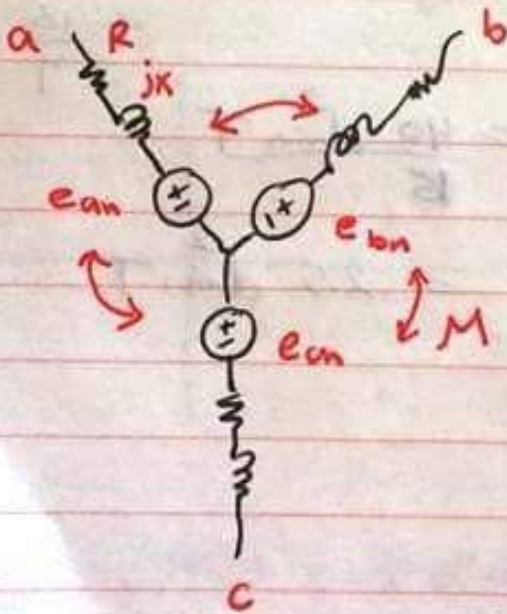
## \* 3-phase synch. generator :-

Revision: i) it contains of stator (which carry armature winding, in which the generator voltage is induced) + Rotor (field winding into which field current is applied)



\* equivalent ckt in the steady state :



$R$  = armature winding resistance

$$jX = j(\omega L_s + \omega M)$$

synch  
reactance

self  
inductance

mutual  
inductance

\* Equivalent circuits of 3-phase generator under short circuit conditions:

\* problem: if a solution <sup>(s.c)</sup> is applied at the terminals of the generator, find its equivalent ckt?


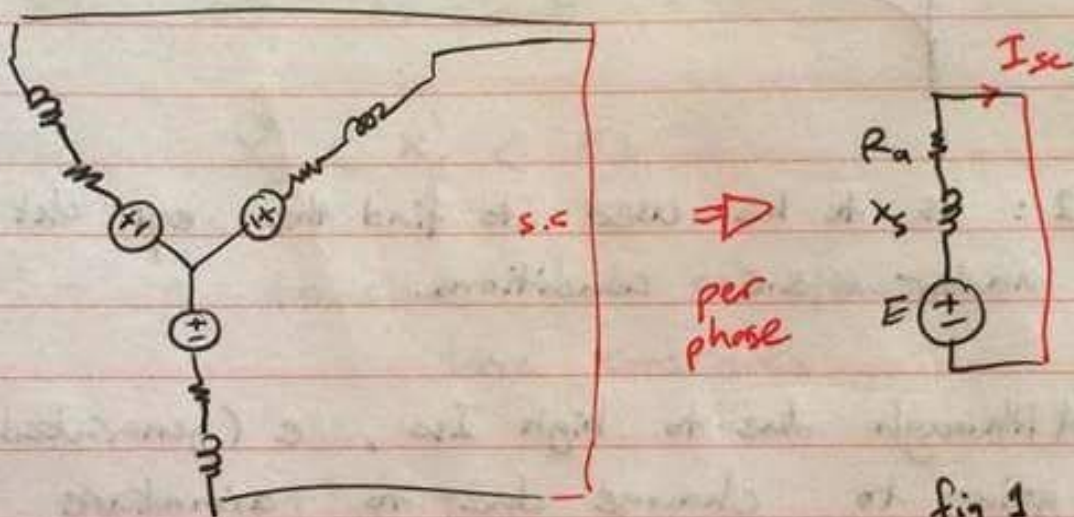



fig 1

\* (fig 1) looks like an RL circuit to which a sinusoidal forcing function (f.f) is suddenly applied to it.

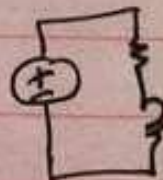\* As found before, the response consist of transient + forced  
↓  
dc response



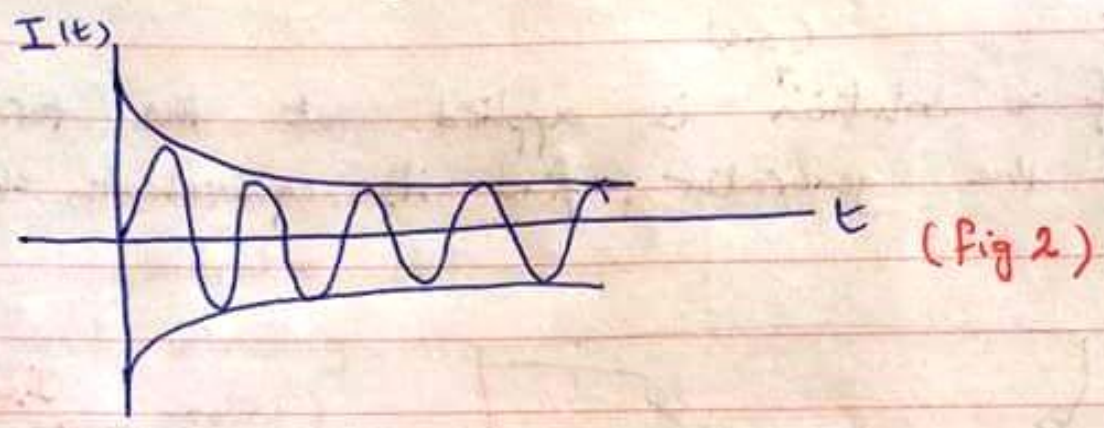\* If the DC of transient response is neglected then the s.c. current will have the following form:



\* Fig 2: is to be used to find the equ. ckt under s.c. conditions.

\* Although due to high  $I_{sc}$ ,  $e$  (generated  $v$ ) is going to change due to armature reaction; however, in the modeling it is assumed that  $e$  (i.e.: no load generated voltage) remains constant and it is assumed that the reactance of the generator changes

\* Consequently the magnitude of the current in fig 2 can be expressed as follows:-

$$I(t) = \frac{E}{X_d} + E \left( \frac{1}{X'_d} - \frac{1}{X_d} \right) e^{-t/T'} + E \left( \frac{1}{X''_d} - \frac{1}{X'_d} \right) e^{-t/T''}$$

\*  $E$  = RMS value of the generated voltage. (1)

$X_d$ : steady state reactance

$X'_d$ : transient reactance


$X''_d$ : sub-transient =

where:  $X''_d < X'_d < X_d$

\*  $T', T''$   $\equiv$  transient and sub-transient time constants

where  $T'' < T'$

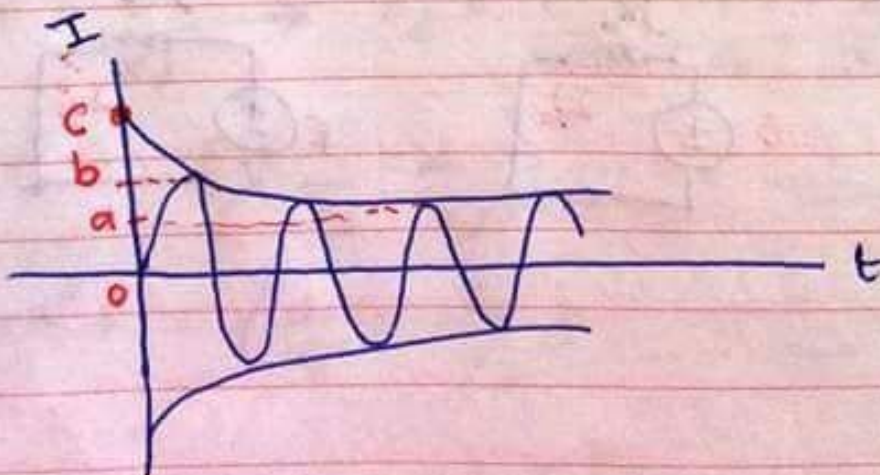\* if (fig 2) is given then one can determine  $X_d, X'_d, X''_d$  as follows:





\*  $oa \rightarrow \text{mag}$   
 (RMS)  $\frac{oa}{\sqrt{2}} = \frac{E}{X_d} \text{ ----- (2)}$

$X_d$  can be found from (2)

\*  $\frac{ob}{\sqrt{2}} = \frac{E}{X_d'} \text{ ----- (3)}$


\* neglect the 1<sup>st</sup> two cycles

$X_d'$  can be found from 3

\*  $\frac{oc}{\sqrt{2}} = \frac{E}{X_d''} \text{ ----- (4)}$

$X_d''$  can be found from 4

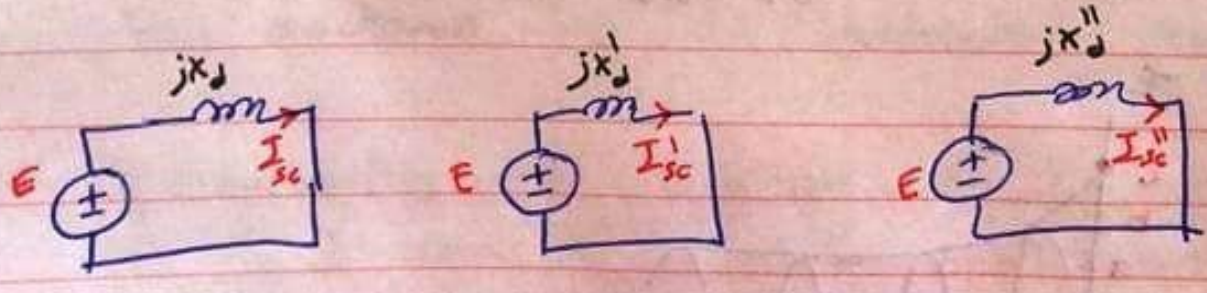\* If  $X_d, X_d', X_d''$  one can evaluate  $I_{sc}, I_{sc}', I_{sc}''$  by using the corresponding equ. ckt as follows:



\* Ex: a 300 MVA, 13.8 kV, 3 $\phi$ -Y connected 60 Hz generator is adjusted to rated voltage at open ckt. A balanced 3 $\phi$  force is applied to its terminals at  $t=0$ .

The obtained symmetrical current  $i(t)$  is:

$$i = 10^4 \left[ 1 + e^{-t/\tau_1} + 6e^{-t/\tau_2} \right] \text{ A}$$

$\downarrow$                        $\downarrow$                        $\downarrow$   
 SS                      trans.                      sub-trans.

When  $\tau_1 = 200 \text{ ms}$

$\tau_2 = 15 \text{ ms}$

$\rightarrow$  find  $X_d, X_d', X_d''$  ?

Sol:  $E = \frac{13.8 \text{ kv}}{\sqrt{3}}$

by comparing the coeff. of 1 and 5, then:-

$$1) \quad 10^4 = \frac{E}{X_d} \rightarrow X_d = \frac{E}{10^4} = \frac{13.8 \times 10^3}{\sqrt{3} \times 10^4} = \boxed{0.797} \Omega$$

$$2) \quad 10^4 = E \left( \frac{1}{X_d} - \frac{1}{X_d'} \right) \dots \dots \dots X_d' = \boxed{0.398} \Omega$$

$$3) \quad 6 \times 10^4 = E \left( \frac{1}{X_d'} - \frac{1}{X_d''} \right) \dots \dots \dots X_d'' = \boxed{0.0996} \Omega$$



\* to find the values in pu  $\rightarrow$  calculate  $Z_b \dots \dots$

## \* Transmission line :

objective: to find the relationships for voltage, current, power.

introduction to its equivalent ckt.
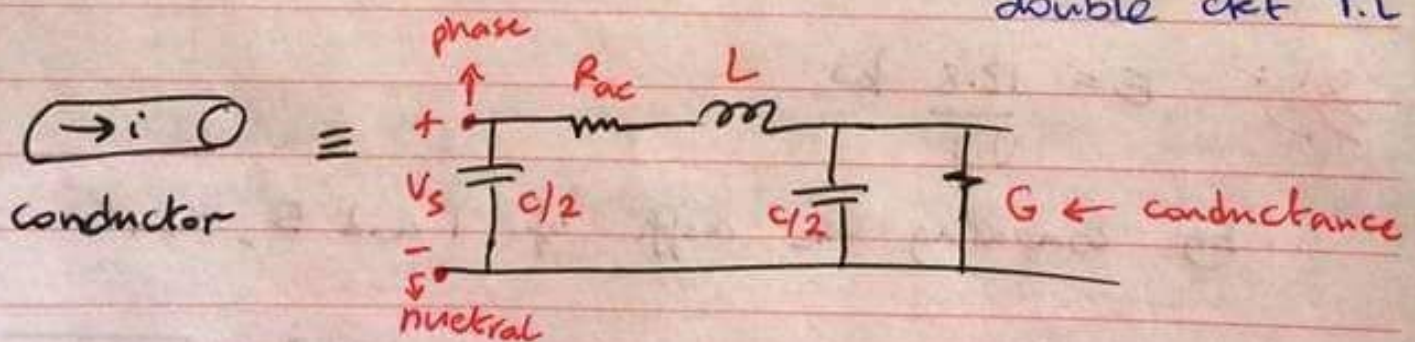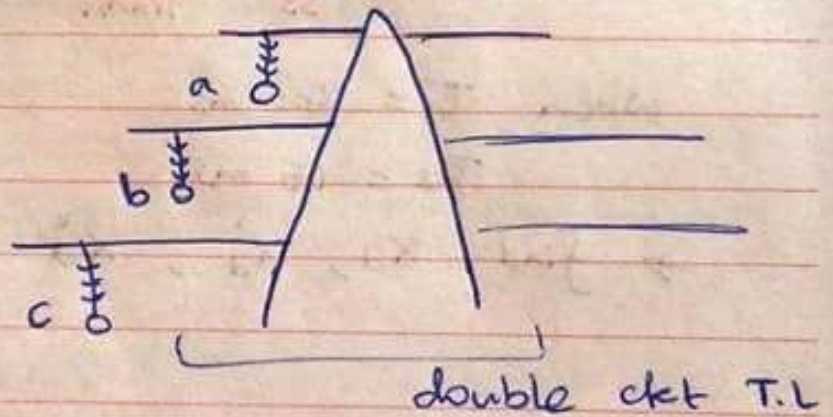
## \* $\pi$ equivalent ckt of transmission line (T.L)




$$* R_{dc} = \frac{\rho l}{A}$$

$$* R_{ac} > R_{dc}$$

\*  $G$  is usually neglected
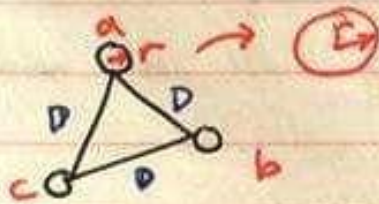
### \* Inductance:

This depends on the configuration of the transmission line (TL), for example if the phase conductors are equally spaced.



then it can be found that:

$$L = 2 \times 10^{-7} \ln \left( \frac{D}{D_s} \right) \text{ H/m}$$


$D_s$  it is called the geometrical mean radius and can be found from standards Tables

### \* Capacitance:

For the same equally spaced conductors, it can be found that capacitance to Neutral  $C_n$  is:

$$C_n = \frac{2\pi\epsilon}{\ln(D/r)}$$

$r$ : radius of conductor (F/m)

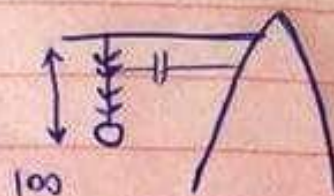


## \* Classifications of T.L :-

According to how one deal with the shunt capacitance, T.Ls are classified into:


i) Short T.L  $< 80$  km

→ here C is neglected.

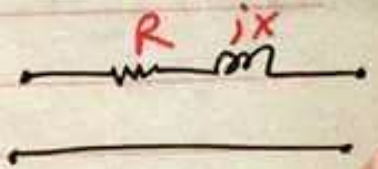

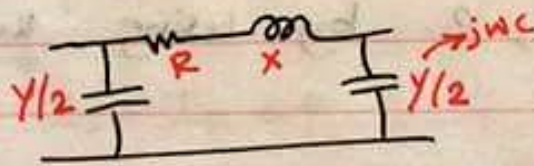
ii) medium line :  $80 < l < 240$  km

→ here C is taken into account and the line is represented by one  $\pi$ -ckt (i.e: lumped parameter)



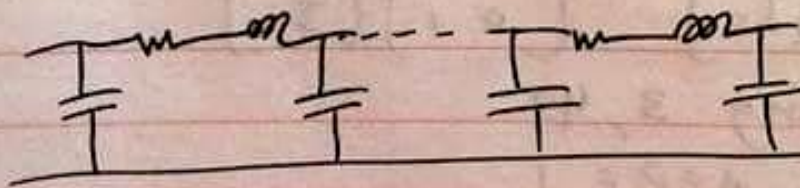
iii) long T.L :  $l > 240$  km

→ here C is taken into account, and the line is represented by a set of  $\pi$ -ckts connected in cascade.



\* distributed parameters

\* Short T.L.:

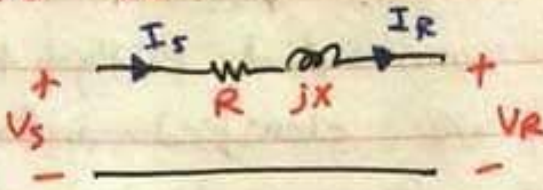

$$\begin{aligned}
 X &= \omega L \\
 &= 2\pi fL \\
 Z &= R + j\omega L
 \end{aligned}$$

fig 1

\* from the equivalent circuit, fig 1

$$\begin{aligned}
 V_s &= V_R + I_R Z \quad \text{--- (1)} \\
 Z &= R + j\omega L
 \end{aligned}$$

$$I_s = I_R \quad \text{--- (2)}$$

→ rewrite 1, 2 by using two ports network parameters:

→

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix} \quad \text{--- (3)}$$

1 and 2 →

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix} \quad \text{--- (4)}$$

→ by equating 3, 4:

$$A = D = 1$$

$$B = Z \quad (\text{total series impedance of the line})$$

$$C = 0$$

$\Rightarrow V_s, V_R$ : sending and receiving end voltages respectively

\* One of the tools used to measure the performance of T.L is called voltage regulation (VR)

$\rightarrow$  where: 
$$VR\% = \frac{|V_{RNL}| - |V_{RFL}|}{|V_{RFL}|} * 100\%$$

$\rightarrow$  NL: No load

FL: full load. (i.e: rated current)


$\therefore |V_{RNL}| = |V_s|$



$I_s = I_R = 0$



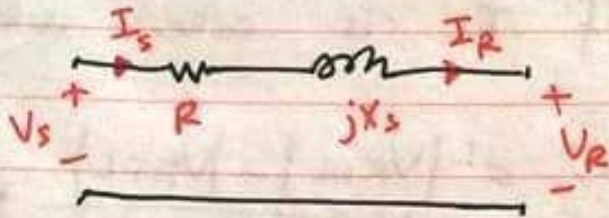
\* Performance of the line under various types of loads:



\* objective: to find relationship between required  $V_s$  for given  $V_R$  for inductive, resistive, capacitive loads.

\* procedure: here it is assumed that  $|V_R|$  and  $|I_R|$  are constants and the P.F. is changing. Hence, by using phasor diagram, it can be found that:

\* lagging p.f.:

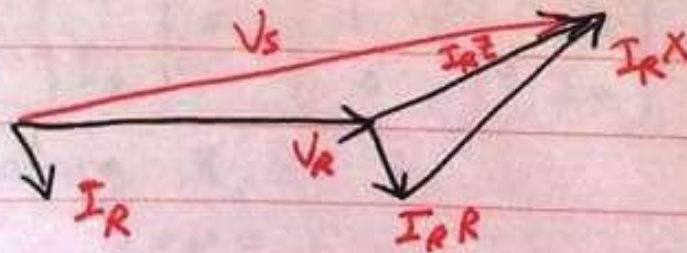


$$|V_{SL}| > |V_R|$$

↓  
lagging



\* Unity P.f.: (Resistive)

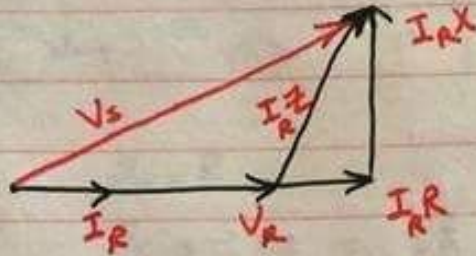


$$|V_{su}| > |V_R|$$

↓  
unity

note:  $|V_{su}| < |V_{sl}|$

\* leading P.f.: (capacitive)

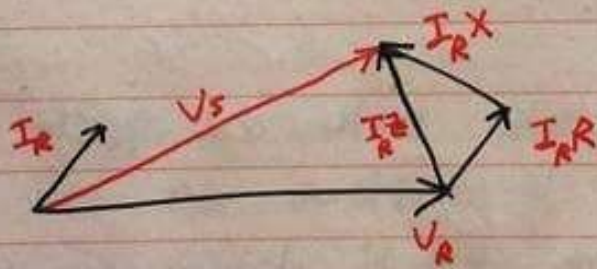

$$|V_{sc}| < |V_R|$$

↓  
capacitive


\* see: p 750, table A3

26/10

Monday

\* Ex: An 18 km, 60 Hz, single ckt, 3 phase transmission line is composed of partridge conductor equally spaced with 1.6 m between centers, the line delivers 2500 kW of 11 kV to a balanced load. Assume a wire temperature of 50°C find:-

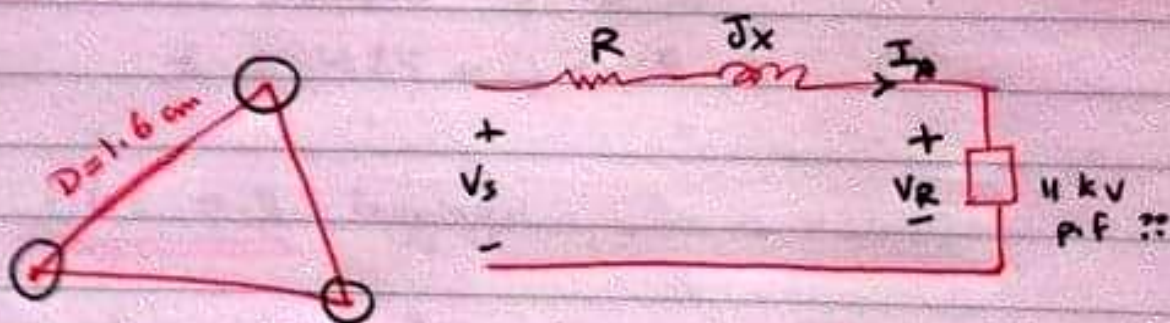- 1) the three phase series impedance of the line
- 2) the required sending-end voltages when the PF is 0.8 lag, unity, 0.9 leading



\*  $Z = R + jX$

\* from the standard table, is shown in the Appendix, it can be found that @ 50°C:

→  $R = 0.3792 \Omega/m$

$= 0.3792 \times \frac{18}{1.609} = 4.24 \Omega$

\* for equally spaced →  $L = 2 \times 10^{-7} \ln\left(\frac{D}{D_s}\right) \text{ H/m}$  \*



$$* X = 2\pi fL, \quad f = 60 \text{ Hz}$$

$$\rightarrow \text{from standard table: } D_s = 0.0217 \text{ ft}$$

foot

$$\rightarrow 1 \text{ foot} = 0.3048 \text{ m}$$

$$\rightarrow L = 2 \times 10^3 \ln\left(\frac{1.6}{0.0217 \times 0.3048}\right) = 10.98 \times 10^{-7} \text{ H/v}$$

$$L = 10.98 \times 10^{-7} \times 10^9 = 0.0197 \text{ H}$$

$$* X = 2\pi fL = 7.45 \Omega$$

$$Z = 4.24 + j7.45 \Omega$$

P.f = 0.8 lagging

$$V_R = \frac{11}{\sqrt{3}} \times 10^3 \angle 0^\circ \text{ V}$$

$$I_R = \frac{2500 \times 10^3}{\sqrt{3} \times 11 \times 10^3 \times 0.8} \angle -63.8^\circ = 164.02 \angle -36.87^\circ \text{ A}$$

$$V_S = V_R + I_R Z = 7660.66 \angle 4.19^\circ$$

→

PF = 1 unity =

$V_R =$  the same

$$I_R = \frac{2500 \times 10^3}{\sqrt{3} \times 11 \times 10^3 \times 1} \angle 0^\circ$$

$$V_S = V_R + I_R Z = 6975.9 \angle 84^\circ \text{ V}$$

PF = 0.9 leading:

$V_R =$  the same

$$I_R = \frac{2500 \times 10^3}{\sqrt{3} \times 11 \times 10^3 \times 0.9} \angle \cos^{-1}(0.9)$$

$$V_S = 6553.6 \angle 10.97^\circ \text{ V}$$

* P.F	$ V_S $	$V_R \%$
0.8 lag	7660.66	20.6
1	6975.9	9.84
0.9 lead	6553.6	3.19

\* high unacceptable V.R. can be solved by using the concept of compensation as will be explained later.

\* By KVL:

$$V_s = Z \left( I_R + V_R \frac{Y}{2} \right) + V_R$$

$$V_s = V_R \left( 1 + \frac{ZY}{2} \right) + Z I_R \quad \text{--- (1)}$$

A

\* By KCL:

$$I_s = V_s + \frac{Y}{2} + \left( I_R + V_R \frac{Y}{2} \right) \quad \text{--- (2)}$$

sub (1) into (2):

$$I_s = \frac{Y}{2} \left( V_R \left( 1 + \frac{ZY}{2} \right) + Z I_R \right) + I_R + V_R \frac{Y}{2}$$

$$= V_R \left( \frac{Y}{2} + Z \frac{Y^2}{4} + \frac{Y}{2} \right) + I_R \left( \frac{ZY}{2} + 1 \right)$$

$$I_s = V_R \left( X + \frac{ZY^2}{4} \right) + \left( 1 + \frac{ZY}{2} \right) I_R$$

C

D

$$2. \quad A = D = 1 + \frac{ZY}{2}$$

$$B = Z$$


$$C = Y + \frac{ZY^2}{4}$$

$$NL \rightarrow IR = \infty$$

$$VR = \frac{|VR_{NL}| - |VR_{FL}|}{|VR_{FL}|}$$

$$\textcircled{1} \Rightarrow VR_{NL} = V_S / A$$

$$VR = \frac{\left| \frac{V_S}{A} \right| - VR_{FL}}{VR_{FL}}$$

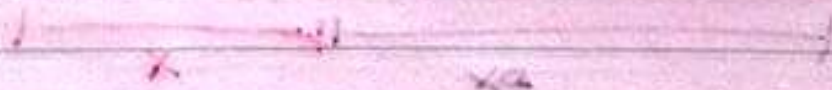


\* long transmission line:

let a line of length =  $l$   
 it's series impedance =  $Z \text{ } \Omega/\text{m}$

$\therefore$  shunt impedance =  $y \text{ S/m}$

$V_s, V_R \equiv$  it's sending and Receiving voltages

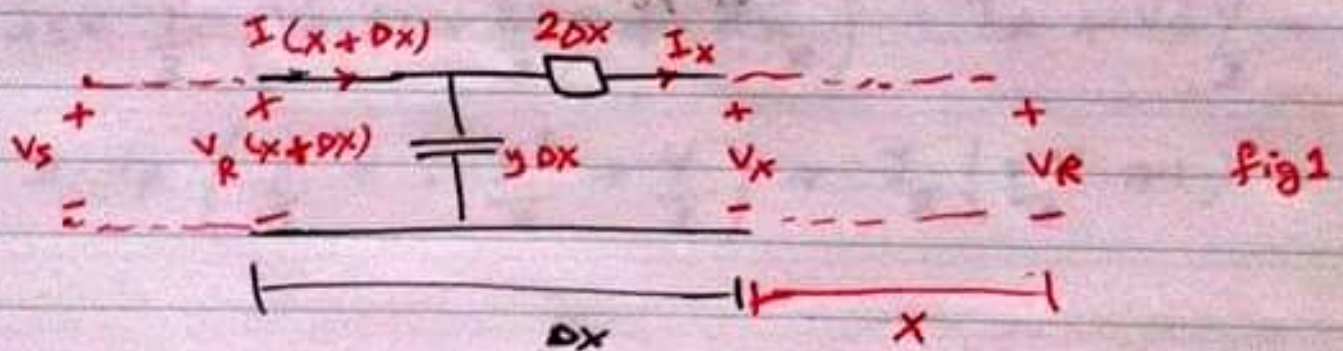\* Consider a segment  $\Delta x$  of this line  
 @ a distance  $x$  from the receiving end



\* objective: to use figure.1 in order to  
 formulate necessary equations in order  
 to evaluate  $v(x)$  and  $I(x)$

\* Analysis:-

→ By KVL:

$$V(x + \Delta x) = Z \Delta x I(x) + V(x)$$

$$\therefore \frac{V(x + \Delta x) - V(x)}{\Delta x} = Z I(x)$$

\* in the limit when  $\Delta x \rightarrow 0$

$$\therefore \frac{dV}{dx} = Z I(x) \quad \text{--- (1)}$$

→ By KCL:

$$I(x + \Delta x) = V(x + \Delta x) Y \Delta x + I(x)$$

$$\frac{I(x + \Delta x) - I(x)}{\Delta x} = V(x + \Delta x) Y$$

\* in the limit  $\Delta x \rightarrow 0$

$$\frac{dI}{dx} = V(x) Y \quad \text{--- (2)}$$

$$\text{diff (1) wr.t } x \Rightarrow \frac{d^2 V}{dx^2} = Z \frac{dI}{dx} \quad \text{--- (3)}$$

$$\text{sub (2) in (3)} \Rightarrow \frac{d^2 V}{dx^2} = Z \cdot Y \cdot V(x) = ZY V(x) \quad \text{--- (4)}$$

$$\text{Similarly it can be found } \frac{d^2 I}{dx^2} = ZY I(x) \quad \text{--- (5)}$$



$$* \frac{dv}{dx} = z I(x) \dots (1)$$

$$\frac{d^2 v}{dx^2} = zy v(x) \dots (3)$$

$$\frac{dI}{dx} = y v(x) \dots (2)$$

$$\frac{dI^2}{dx^2} = zy I(x) \dots (4)$$

\* To simplify let  $\gamma^2 = zy$   
 $\gamma = \sqrt{zy}$

$\gamma$  is called ~~propag~~ propagation constant  
 $\therefore$  Solve 1<sup>st</sup> equation (2):

$$\frac{d^2 v}{dx^2} = \gamma^2 v(x) \dots (5)$$

\* Solution of (5) is:

$$v(x) = A_1 e^{\gamma x} + A_2 e^{-\gamma x} \dots (6)$$

\*  $A_1$  and  $A_2$  can be found from initial conditions.

$$v(0) = V_R = A_1 + A_2 \dots (7)$$

$$\frac{dv}{dx} = A_1 \gamma e^{\gamma x} - A_2 \gamma e^{-\gamma x} \dots (8)$$

\* Substitute: (1) into (8):

$$Z I(x) = A_1 \delta e^{\delta x} - A_2 \delta e^{-\delta x} \quad (8)$$

$$\therefore Z I(0) = Z I_R = A_1 \delta - A_2 \delta \quad \text{--- (9)}$$

Solve 7, 9: to find  $A_1, A_2$ :

$$\therefore \delta * (7) + (9)$$

$$\delta V_R + Z I_R = 2 \delta A_1$$

$$\therefore A_1 = \frac{\delta V_R + Z I_R}{2 \delta}$$

$$= \frac{1}{2} \left( V_R + \frac{Z}{\delta} I_R \right) \quad \text{--- (10)}$$

$$= \frac{1}{2} V_R + \sqrt{\frac{Z}{y}} I_R$$

is called characteristic

impedance:  $Z_c$

$$= \frac{1}{2} (V_R + Z_c I_R)$$

$$* A_2 = V_R - A_1$$

$$= V_R - \frac{1}{2} (V_R + Z_c I_R)$$

$$\therefore A_2 = \frac{1}{2} (V_R - Z_c I_R) \quad \text{--- (11)}$$

\* substitute: (9) and (10) into (6):

$$V(x) = \frac{1}{2} (V_R + Z_c I_R) e^{\gamma x} + \frac{1}{2} (V_R - Z_c I_R) e^{-\gamma x}$$

$$\therefore V(x) = V_R \left[ \frac{1}{2} (e^{\gamma x} + e^{-\gamma x}) \right] + I_R Z_c \left[ \frac{1}{2} (e^{\gamma x} - e^{-\gamma x}) \right]$$

$\cosh(\gamma x)$                        $\sinh(\gamma x)$

$$V_R \cosh(\gamma x) + \frac{I_R Z_c}{R} \sinh(\gamma x)$$

\* By repeating the same procedure, it can be found that:

$$I(x) = \frac{1}{Z_c} \sinh(\gamma x) V_R + \cosh(\gamma x) I_R$$

\* when  $x = l$   $\therefore V(l) = V_s$  and  
 $I(l) = I_s$

$$\therefore V_s = V_R \underbrace{\cosh \gamma l}_A + I_R \underbrace{Z_c \sinh \gamma l}_B$$

$$I_s = V_R \underbrace{\frac{1}{Z_c} \sinh \gamma l}_C + I_R \underbrace{\cosh \gamma l}_D$$

$$\therefore A = D = \cosh \gamma l$$

$$B = Z_c \sinh \gamma l$$

$$C = \frac{1}{Z_c} \sinh \gamma l$$

$$* \text{VR} \% = \frac{\left| \frac{V_s}{A} \right| - |V_R|}{|V_R|} \times 100\%$$

\* e.g.: A 60 Hz, 3 $\phi$  T.L. is 175 miles long.  
 it has total series impedance =  $135 + j140 \Omega$   
 and total shunt admittance =  $930 \times 10^{-6} \angle 90^\circ \text{ S}$   
 it delivers 40 MW at 220 kV and 0.9 pf  
 lagging: a) find: voltage current and pf  
 at the sending end  
 b) find VR and efficiency of line.

$$\rightarrow V_s = AV_R + B I_R$$

$$I_s = CV_R + D I_R$$

$$Z_c = \sqrt{Z/Y}$$

$$= \sqrt{\frac{35 + j140}{930 \times 10^{-6} \angle 90^\circ}} = 393.9 \angle -7^\circ$$

$$* \gamma L = \sqrt{ZY}$$

$$= \sqrt{\underbrace{Z}_{35 + j140} \times \underbrace{Y}_{930 \times 10^{-6} \angle 90^\circ}}$$

$$= \sqrt{(35 + j140)(930 \times 10^{-6} \angle 90^\circ)}$$

$$= 0.3663 \angle 83^\circ$$

$$* F = 5 e^{j30}$$

$$\sqrt{F} = \sqrt{5} e^{j15}$$

$$= (5)^{1/2} e^{j30(\frac{1}{2})}$$

$$= (5)^{1/2} e^{j15}$$

$$\uparrow$$

$$1/15$$

$$* e^{\gamma L} = e^{0.3663} \angle 83^\circ$$

$$= e^{0.0446 + j0.3636} = e^{0.0446} * e^{j0.3636} \\ = 1.0456 \angle 20^\circ$$

$$\therefore e^{-\gamma L} = \frac{1}{1.0456 \angle 20^\circ}$$

$$= 0.9563 \angle -20^\circ$$

$$* A = D = \cosh \gamma L \\ \frac{1}{2} (e^{\gamma L} + e^{-\gamma L})$$

by substitution:-

$$A = D = 0.9407 \angle 1^\circ$$

$$B = Z_0 \sinh \gamma L = Z_0 \frac{1}{2} (e^{\gamma L} - e^{-\gamma L})$$

$$= 135.9 \angle 76^\circ$$

$$C = \frac{1}{Z_0} \sinh \gamma L = 875 * 10^6 \angle 90^\circ$$

$$\rightarrow V_R = \frac{220 * 10^3}{\sqrt{3}} \angle 0^\circ$$

$$\rightarrow I_R = \frac{40 * 10^6}{\sqrt{3} * 220 * 10^3 * 0.9} \angle -\cos^{-1} 0.9 = 116.6 \angle 25.8^\circ \text{ A}$$

$$\rightarrow V_s = A V_R + B I_R = 130.4 \angle 6.3^\circ \text{ Kv}$$

$$\rightarrow I_s = C V_R + D I_R = 119 \angle 33^\circ$$

$$\begin{aligned} \text{P.f.} &= \cos(6.3^\circ - 33^\circ) \\ &= 0.89 \text{ leading.} \end{aligned}$$

(b)  $V_R$ ?  $\eta$ ?

$$\rightarrow \text{VR}\% = \frac{|V_s| - |V_R|}{|V_R|} \times 100\%$$

$$= \frac{\frac{130.4}{0.9407} - \frac{200}{\sqrt{3}}}{\frac{200}{\sqrt{3}}} \times 100\% = 9.15\%$$


$$\rightarrow \eta = \frac{P_{out}}{P_{in}} = \frac{40 \times 10^6}{3 V_s * I_s * \text{P.f.}_s}$$

$$= \frac{40 \times 10^6}{3 * 130.4 * 10^3 * 119 * 0.89}$$
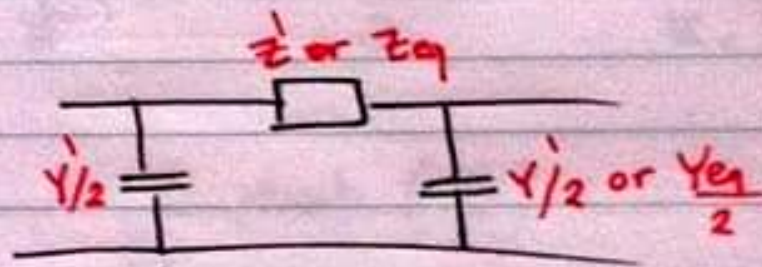
## \* Equivalent ckt of long T.L. $\rightarrow$

Since such lines are part of a given power system then it is required to represent it by an equ. ckt.

it is represented by a  $\pi$ -ckt as that of medium T.L as follows: -



\* for medium line

$$\rightarrow V_s = V_R \left( 1 + \frac{ZY}{2} \right) + Z I_R$$

However; for long line:

$$V_s = V_R \cosh \gamma L + Z_c \sinh \gamma L \cdot I_R$$

$\rightarrow$





# Power 1 Notebook



**DR. DAIFALLAH DALBEEH**

**BY : SAUSAN ALMOHTASEB**

\* To use the same  $\pi$ -equ. :-


force:  $Z_c \sinh \delta L = Z \quad \text{--- (1)}$

$\cosh \delta L = 1 + \frac{ZY}{2} \quad \text{--- (2)}$


\*  $Z' = Z_c \sinh \delta L$

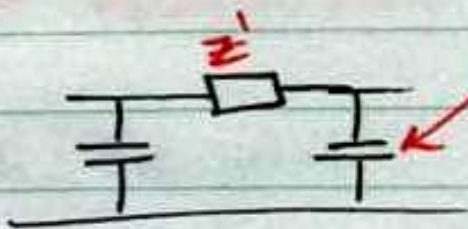(2)  $\rightarrow \frac{Y}{2} = \frac{\cosh \delta L - 1}{Z} = \frac{\cosh \delta L - 1}{Z_c \sinh \delta L}$

$= \frac{1}{Z_c} \tanh \left( \frac{\delta L}{2} \right)$



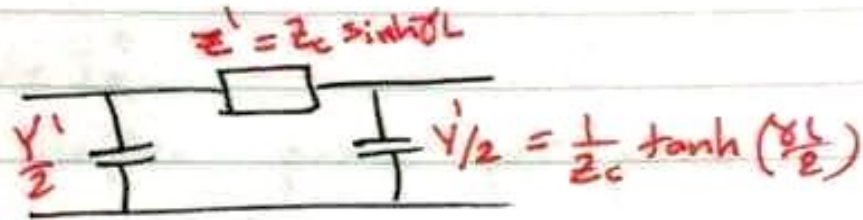c) find the equivalent ckt of the line in the previous fig:



\* by substitution it can be found that:


$$Z' = Z_c \sinh \delta L = 135.8995 \angle 76^\circ$$

$$\frac{Y'}{2} = \frac{1}{Z_c} \left( \frac{e^{\delta L/2} - e^{-\delta L/2}}{e^{\delta L/2} + e^{-\delta L/2}} \right) = 4.64 \times 10^{-4} \angle 90.98^\circ$$

\* Power relationship for T.L :-

→ Although the power at any point along the line can be calculated if one knows the  $V$ ,  $I$ , P.f

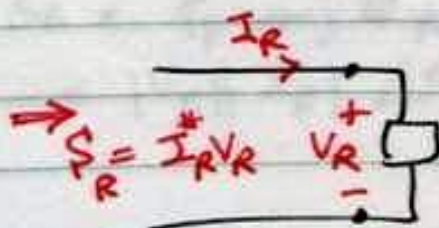→ the objective here is to find an expression for the power ~~system~~ in terms of  $\begin{bmatrix} A & B \\ C & D \end{bmatrix}$  parameters



## \* Procedure :

$$S_R = V_R I_R^* \quad \text{--- (1)}$$

$S_R$  : complex power per phase

$$V_S \triangleq AV_R + BI_R$$

$$\therefore I_R = \frac{V_S - AV_R}{B} \quad \text{--- (2)}$$

Let:

$$\left. \begin{aligned} V_S &= |V_S| \angle \delta \\ A &= |A| \angle \alpha \\ B &= |B| \angle \beta \\ V_R &= |V_R| \angle 0^\circ \end{aligned} \right\} \text{--- (3)}$$

\* Sub (3) into (1):

$$I_R = \frac{|V_S| \angle \delta - \frac{|A||V_R| \angle \alpha - \beta}{|B|}}{|B|} \quad \text{--- (4)}$$

\* Sub 4 into 1:

$$S_R = \frac{|V_R||V_S| \angle \beta - \delta - \frac{|A||V_R|^2 \angle \beta - \alpha}{|B|}}{|B|} \quad \text{--- (5)}$$

Since:  $S_R = P_R + jQ_R$

$$= |V_R||I_R| \angle \theta \quad \text{--- (6)}$$


\* hence, from 5 & 6 the following comments and conclusions can be made:

$$P_R = \frac{|V_R| |V_S|}{|B|} \cos(\beta - \delta) - \frac{|A| |V_R|^2}{|B|} \cos(\beta - \alpha) \quad \text{--- (7)}$$


$$Q_R = \frac{|V_R| |V_S|}{|B|} \sin(\beta - \delta) - \frac{|A| |V_R|^2}{|B|} \sin(\beta - \alpha) \quad \text{--- (8)}$$

⇒  $S_R$  can be expressed graphically by using the concept of phasor diagram, where in (5)  $S_R$  is the resultant of two phases as follows:

$$(5): S_R = \underbrace{\frac{|V_R| |V_S|}{|B|} \angle \beta - \delta}_{\text{1}} - \underbrace{\frac{|A| |V_R|^2}{|B|} \angle \beta - \alpha}_{\text{2}}$$

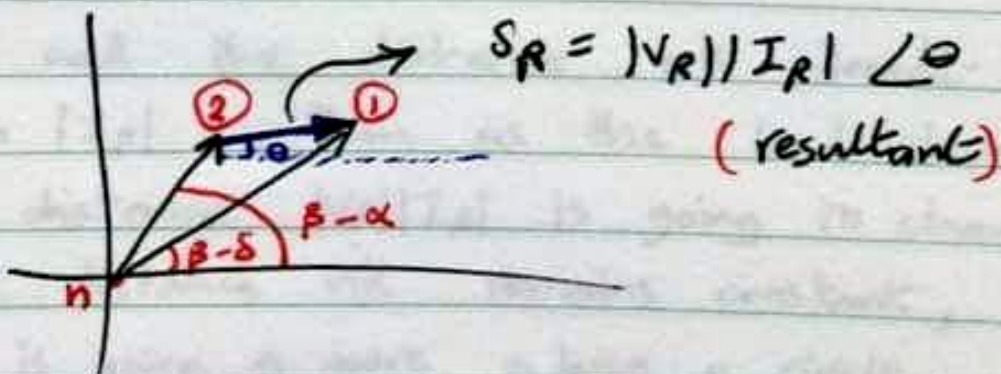

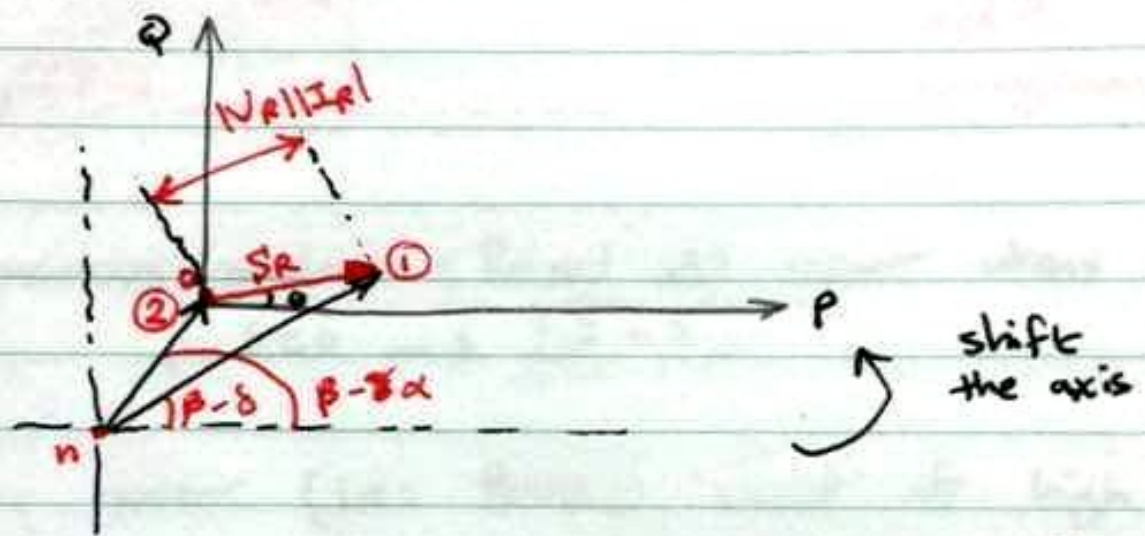\* if the axis are shifted from point (n) to point (o), then the resultant diagram is the power diagram




\* find the locus of the power when the load changes keeping  $|V_R|$  and  $|V_S|$  constants

$$|I_R| \ominus$$

\* Since  $n$  and the distance  $nk$  doesn't depend on  $|I_r|$ , then as the load changes, then the distance  $|V_n|/|I_r|$  is going to change with the distance  $nk$  remains constant, hence  $k$  is going to move along a circle

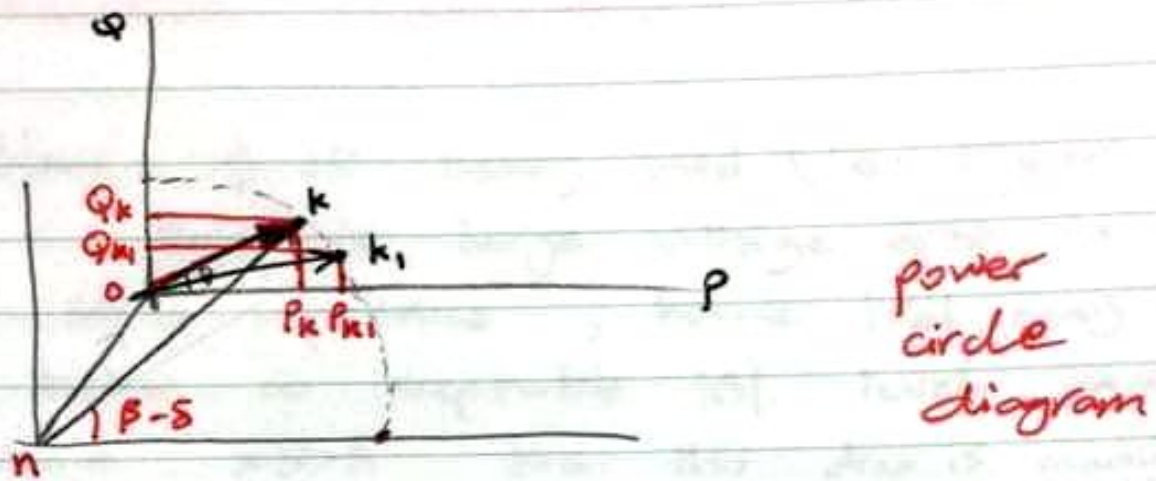Note: here  $(\delta)$  changes with load.





(a) maximum power ( $P_{max}$ ) will occur when  $\beta - \delta = 0 \rightarrow \boxed{\beta = \delta}$

(b) max. power (i.e.:  $P_{max}$ ) occur at high value of leading current

\* hence in practice  $\frac{|V_s|}{|V_R|}$  is limited to 0.95 or higher,  $\delta$  is limited to about  $35^\circ$

\* hence from (7):  $P_{max} = \frac{|V_R||V_s|}{|B|} - \frac{|A||V_R|^2 \cos(\beta - \alpha)}{|B|}$

from (9):

$$P_{max} \propto \frac{1}{|B|}$$

for medium & long lines  $\rightarrow |B| \propto |Z|$   
 $\therefore Z$  affect power capability of T.L

## \* Reactive Compensation :

problem : 1) at heavy load (i.e.: higher  $I_R$ ) there is large voltage drop in the series impedance, hence  $|V_R|$  may be below an acceptable  $|B|$  level, and since  $X \gg R$  then this drop is mainly due to inductive reactance.

Consequently, this problem can be solved by introducing series capacitor called : series reactive compensation




Wednesday

4/11

8

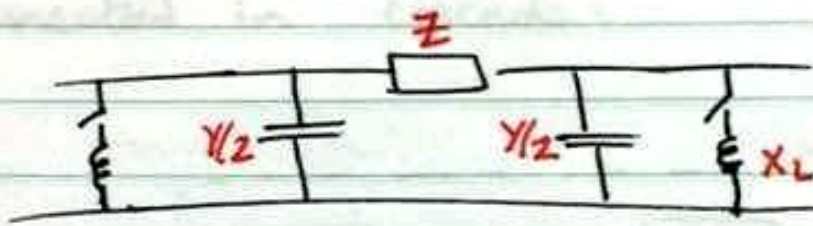\* At light load (no load), then inductive compensation is used to reduce the rise in receiving voltage.



\* The compensation factor in this case is

$$\frac{B_L}{B_C} ; \text{ where: } B_L = \frac{1}{X_L}$$

$$B_C = j\omega C$$

reactance of compensation (j $\omega L$ )

\* note = in ~~the~~ case of series or capacitive compensation the compensation factor =  $\frac{X_C}{X_L}$


inductive reactance of the T.L

reactance of the added capacitor

$$\begin{bmatrix} V_{in} \\ I_{in} \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_{out} \\ I_{out} \end{bmatrix}$$
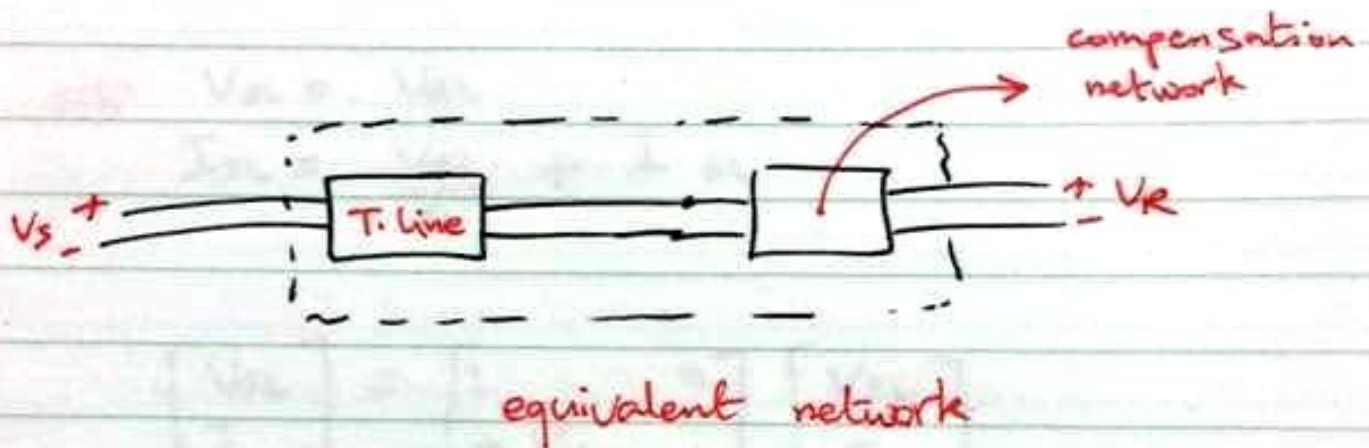
### \* Analysis :

Hence after introducing compensation, there will be two 2-port networks connected in cascade:



### \* Parameters of compensation network :

#### \* Series or capacitor compensation :




$$\therefore V_{sc} = V_{RC} + I_R X_c$$

$$I_{sc} = I_{RC}$$

$$\therefore \begin{bmatrix} V_{sc} \\ I_{sc} \end{bmatrix} = \begin{bmatrix} 1 & X_c \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_{RC} \\ I_{RC} \end{bmatrix}$$


\* Parallel or inductive compensation:

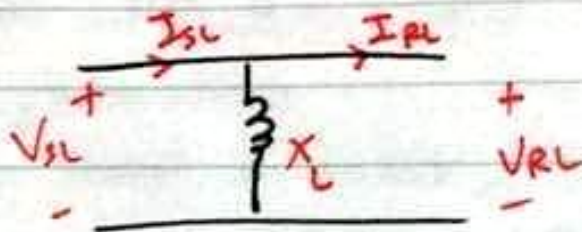

$$\Rightarrow V_{SL} = V_{RL}$$

$$I_{SL} = \frac{V_{RL}}{X_L} + I_{RL}$$
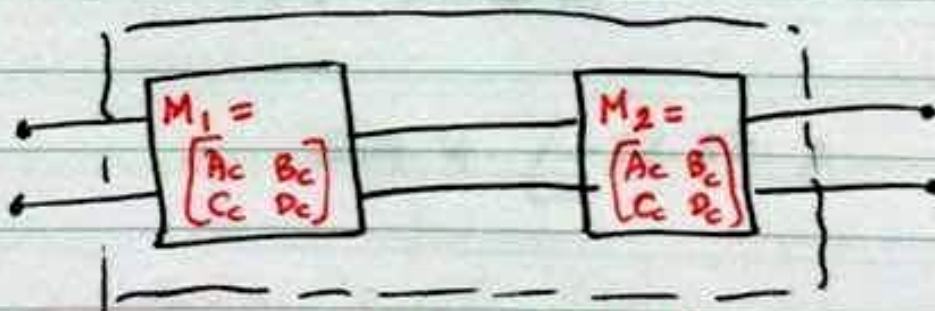
$$\begin{bmatrix} V_{SL} \\ I_{SL} \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ *Y_{X_L} & 1 \end{bmatrix} \begin{bmatrix} V_{RL} \\ I_{RL} \end{bmatrix}$$



M-equivalent

$$M_{eq} = M_1 * M_2$$

\* e.g.: 3-phase T.L. is 300 mile long and supply a load of 400 MVA with 0.8 pf lagging at 345 kv. The line has the following parameters:

$$A = D = 0.818 \angle 1.3^\circ$$

$$B = 172.2 \angle 84.2^\circ$$

$$C = 0.001933 \angle 90.4^\circ$$

a) find  $V_s$  and  $V_R\%$  ?

$$V_s = AV_R + BI_R$$

$$V_R = \frac{345 \angle 0^\circ \text{ kv}}{\sqrt{3}} = 199.2 \angle 0^\circ$$

$$I_R = \frac{400 \times 10^6}{\sqrt{3} \times 345 \times 10^3} \angle -\cos^{-1} 0.8$$

$$= 669.4 \angle -36.87^\circ \text{ A}$$

\* By substitution:

$$V_s = 256.8 \angle 20.1^\circ \text{ kv}$$

$$V_R\% = \frac{256.8}{0.818} - 199.2 \times 100\% = 57.6\%$$


---

199.2

b) If a series capacitor bank having reactance of  $146.6 \Omega$  is to be installed at the mid point of the line, and the  $\begin{bmatrix} A & B \\ C & D \end{bmatrix}$  constants for each 150 mile portion are

$$A = D = 0.9534 \angle 0.3^\circ$$

$$B = 90.33 \angle 84.1^\circ$$

$$C = 0.00104 \angle 90.1^\circ$$

b.1: find the equivalent  $\begin{bmatrix} A & B \\ C & D \end{bmatrix}$  constants for cascade connection:

$$\begin{bmatrix} \text{150} \\ \text{mile} \end{bmatrix} * \begin{bmatrix} \text{capacitor} \end{bmatrix} * \begin{bmatrix} \text{150} \\ \text{mile} \end{bmatrix}$$

given
}
given

$$\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \rightarrow \begin{bmatrix} 1 & -j146.6 \\ 0 & 1 \end{bmatrix}$$

\* it can be found:

$$= \begin{bmatrix} \overset{A_{eq}}{0.96 \angle 1.2^\circ} & \overset{B_{eq}}{42 \angle 64.8^\circ} \\ 0.002 \angle 9^\circ & 0.96 \angle 1.19^\circ \end{bmatrix}$$

b.2: find  $V_s$  and  $V_R$  %

$$V_s = A_{eq} V_R + B_{eq} I_R$$

by sub:  $V_s = 216.7 \angle 4.5^\circ$

$$\rightarrow V_R = \frac{216.7 - 199.2}{A_{eq}} \times 100\% = \boxed{13.3\%}$$

199.2

\* Comments on the equation of long line:  
it was found that:

$$V(x) = \frac{V_R + I_R Z_c e^{\gamma x}}{2} + \frac{V_R - I_R Z_c e^{-\gamma x}}{2}$$

incident-wave                      reflected wave

$$I(x) = \frac{\frac{V_R}{Z_c} + I_R e^{\gamma x}}{2} - \frac{\frac{V_R}{Z_c} - I_R e^{-\gamma x}}{2}$$

\* where:  $\gamma = \alpha + j\beta$

\* in this case no reflected wave

\* surge impedance =  $\sqrt{L/C}$  for lossless

$$* \boxed{e^{\gamma x} = e^{\alpha} \cdot e^{j\beta}}$$

9/11/2015  
Monday

### \* Surge Impedance Loading (SIL):

This is the power transmitted by the line to a pure resistive load whose value equal to surge impedance.



$$\begin{aligned} \rightarrow P &= \sqrt{3} V_L I_L \cos \theta \\ &= \sqrt{3} V_L I_L \\ &= \sqrt{3} V_L \left( \frac{V_L}{\sqrt{3} \sqrt{L/C}} \right) = \frac{V_L^2}{\sqrt{L/C}} \end{aligned}$$

\* The end of the voltage current for T.L.

## \* Fault Analysis:

\* objective:

what? definition: Any failure which causes the interruption of normal current or power flow is called Fault.

why? under fault, extreme high current flow, therefore power system should be protected against such high currents.

\* Protection systems consist of the following components:




for analysis is used to calculate fault current in order to make setting for Relay & circuit breaker.




How?

## \* Classifications of Faults:

here we are concerned with s/c fault

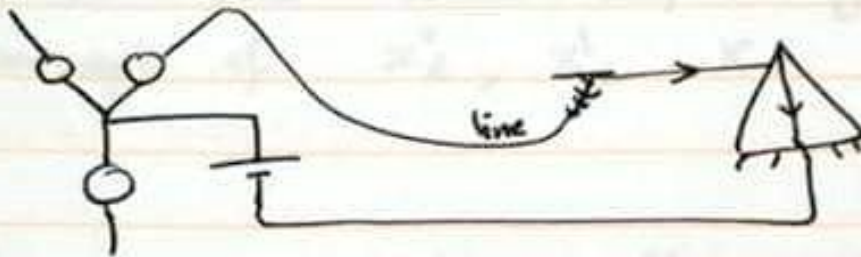

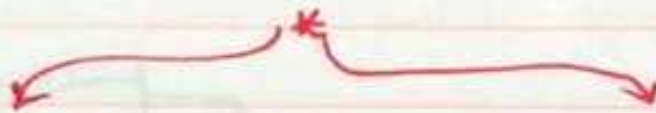So, need to stop the current by circuit breaker.



balanced  
or symmetrical fault



per phase ckt

unbalanced or  
unsymmetrical fault



- ① line to ground fault
- ② line to line fault
- ③ line to line to ground fault

## \* Balanced fault :-


\* There are two cases:

① Unloaded generator suffer short circuit at it's terminal.

→ This was solved before by using the concept of  $X_d''$ ,  $X_d'$ ,  $X_d$ .

② Loaded generator suffer s.c ~~and~~ at a certain point & analyzed as follows:

\* Consider the following sys:-

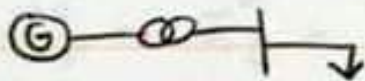

Let the problem that a short circuit occur at the terminal of the load and ~~the~~ let the load by 3-ph synch. motor

That perphase equ. ckt will be as follows:

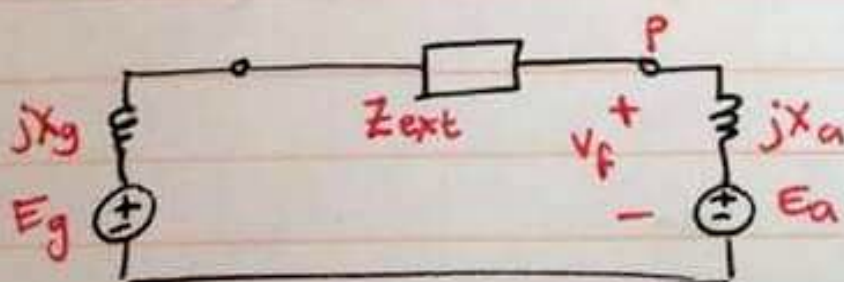



fig (v) : before fault.

$Z_{ext.}$  : equ. impedance between the generator terminals and load.

$P$  : is the location of the fault.

$V_f$  : pre fault voltage.

\* after fault:

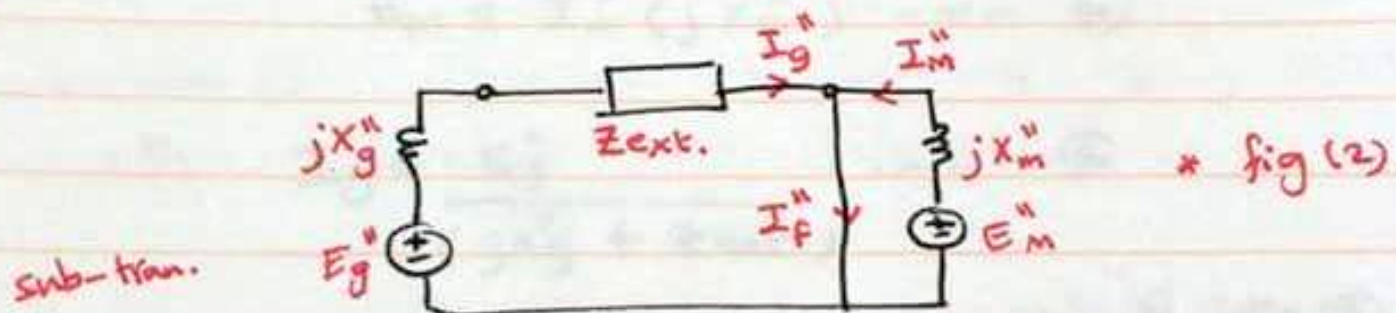

\*  $I_f''$  : fault current at subtransient fault  

$$I_f'' = I_g'' + I_m''$$

\* objective to evaluate:  $I_g''$ ,  $I_m''$ ,  $I_f''$

\* Analysis :

Here it is assumed that:  $E_g''$  &  $E_m''$  has the same value immediately before and immediately after the fault.



\* from fig (1):

$$E_g'' = I_L (jX_g'' + Z_{ext}) + V_f \quad \text{--- (1)}$$

$$E_m'' = V_f - I_L jX_m'' \quad \text{--- (2)}$$

\* from fig (2):

$$E_g'' = I_g'' (jX_g'' + Z_{ext}) \quad \text{--- (3)}$$

$$E_m'' = I_m'' (jX_m'') \quad \text{--- (4)}$$

3: 
$$I_g'' = \frac{E_g''}{(jX_g'' + Z_{ext})} \quad \text{--- (5)}$$

→ sub (1) into (5):

⇒ 
$$I_g'' = I_L + \left( \frac{V_f}{(jX_g'' + Z_{ext})} \right) \quad \text{--- (7)}$$

4: 
$$I_m'' = \frac{E_m''}{jX_m''} \quad \text{--- (6)}$$

→ sub (2) into (6):

⇒ 
$$I_m'' = \frac{V_f}{jX_m''} - I_L \quad \text{--- (8)}$$

∴ 
$$I_f'' = I_g'' + I_m'' \quad \text{--- (7) + (8)}$$

So: 
$$I_f'' = \frac{V_f}{jX_m''} - \cancel{I_L} + \cancel{I_L} + \frac{V_f}{jX_g'' + Z_{ext}} \quad \text{--- (9)}$$

\* This method up to how it is called the internal voltages method.

\* comment :


⑨ can be written as follows :

$$I_f'' = V_f \left( \frac{1}{jX_m''} + \frac{1}{jX_g'' + Z_{ext}} \right)$$

*parallel*

$$= \frac{V_f}{(jX_g'' + Z_{ext}) \parallel (jX_m'')} \quad \text{--- --- --- } \textcircled{10}$$

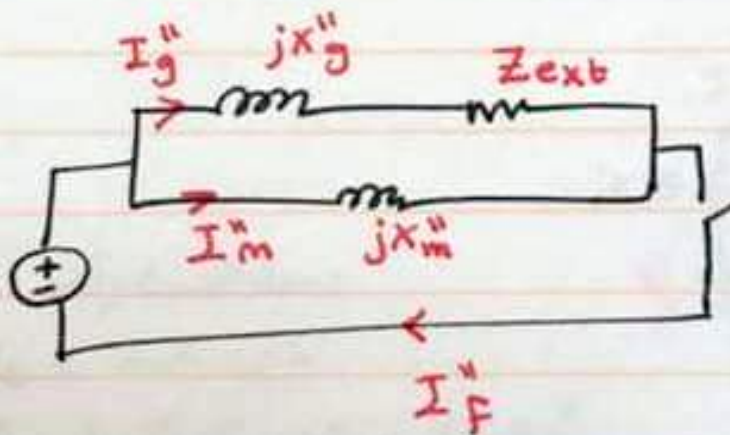\* So  $\textcircled{10}$  : can be represented by a thevenin equivalent as follows :



→ so, thevenin equ. is used to evaluate fault current ( $I_f''$ )

→ so,  $I_g''$  and  $I_m''$  can be found by using current division.

e.g.: A generator is connected through a transformer to a synch. motor for the same base pu reactances of the components  $X_g'' = 0.15$ ,  $X_T = 0.1$ ,  $X_m'' = 0.35$ .

A 3-ph fault occur at the terminal of the motor, when the terminal voltage of the ~~motor~~ generator = 0.9 pu at the gen-current = 1 pu at ~~0.8~~ 0.8 pf leading.


Find: the sub-transient current in pu in the fault gen. and motor:

⇒ sol:

\* given information:

$$V_t = 0.9 \angle 0$$
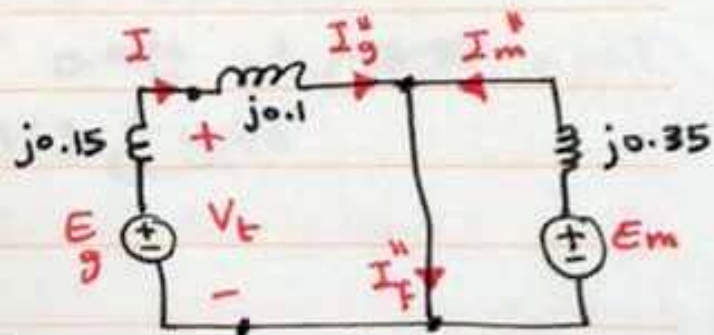
$$I = 1 \angle \cos^{-1} 0.8 = 36.87^\circ$$



\* using internal voltage method:

before:  $E_g'' = V_t + jX_g'' I = 0.82 \angle 8.42$


$$E_m'' = V_t - I(jX_T + jX_m'') = 1.22 \angle -17.1$$

(after): 
$$I_g'' = \frac{I_g''}{j0.15 + j0.1} = 8.28 \angle 81.58$$

$$I_m'' = \frac{E_m''}{j0.35} = 3.49 \angle 107.1$$

$$I_f = I_g'' + I_m'' = 6.6 \angle -94.78$$

\* Using Thevenin:

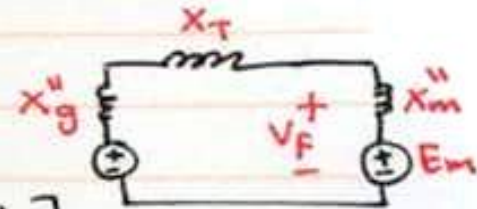

$$I_f = V_f / [(jX_g'' + jX_T) \parallel jX_m'']$$

$$V_f = V_t - I X_{ext} = 0.9 \angle -1 \angle 36.87 * j0.1 \\ = 0.963 \angle -4.76$$

\* by substitution:

$$I_f'' = 6.6 \angle -94.76$$

\* by current division:

$$I_g'' = I_f'' \left( \frac{jX_m''}{jX_m'' + jX_g'' + jX_T} \right) = 3.85 \angle -94.76$$

$$\rightarrow I_m'' = I_f'' - I_g'' = 2.75 \angle -94.76$$


\* The difference in the answer for  $I_g''$  and  $I_m''$  in the two methods is due to fact that Thev. ~~method~~ method neglect  $I_L$

$\therefore$  To take into account- add  $I_L$  to  $I_g''$  and subtract it from  $I_m''$

\* Z-bus method:

this method is used to evaluate the fault current due to a balanced 3-ph fault for a general power system.

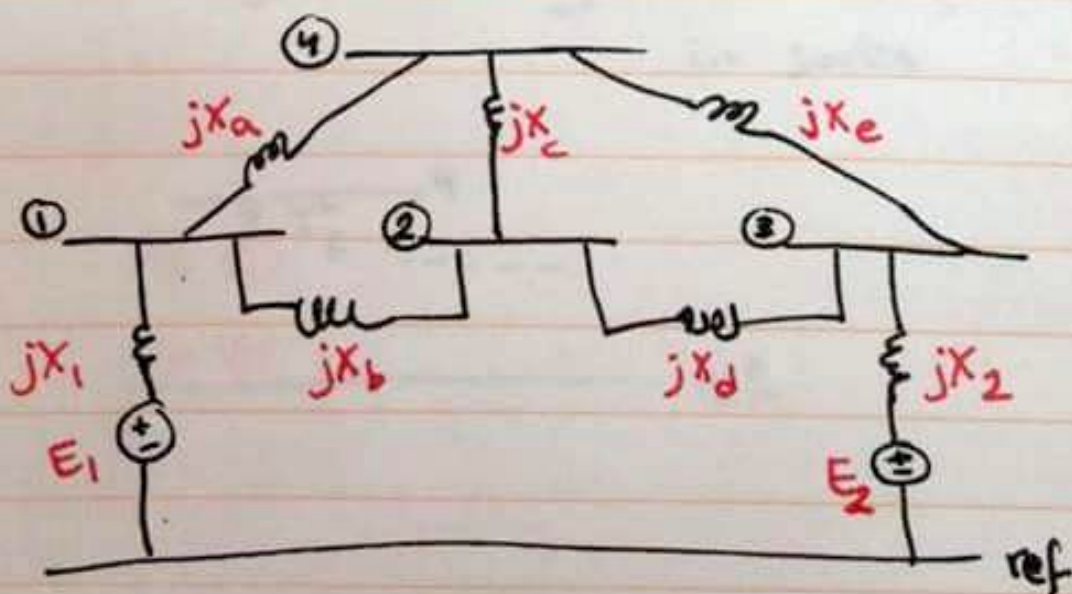\* procedure: Consider the following sys. :







\* problem :

for all given sub-transient parameters, evaluate the fault current ( $I_f''$ ) and the internal current when a fault occur at any busbar.

\* for e.g: let the fault at Bus (4).

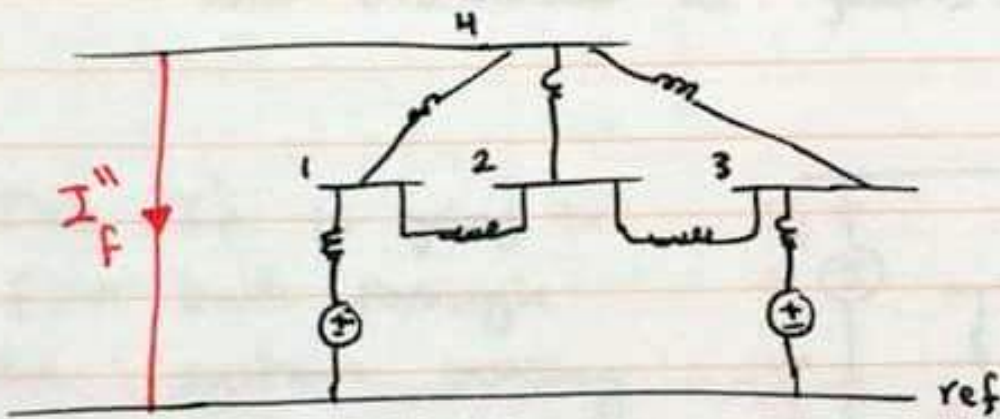

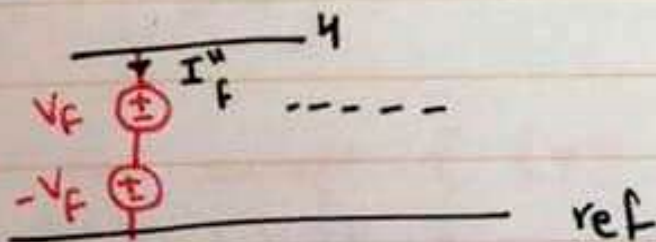now, the s.c of the fault can be represented by 2 voltage sources (i.e.:  $V_f$ ,  $-V_f$ ) in series.



\* Since there are 4 sources then super position can be used to evaluate ( $I_f''$ )

(a) if  $E_i''$ ,  $E_f''$ ,  $V_f$  are taken together, then  $I_f'' = 0$ , because these sources represent pre-fault condition.

(b) hence,  $I_f''$  is due only to the source ( $-V_f$ ) and evaluated as follows:

\* This  $I_f''$  is going to flow back through the system causing changes of voltages at the busbars =

$$\begin{bmatrix} \Delta V_1 \\ \Delta V_2 \\ \Delta V_3 \\ \Delta V_4 \end{bmatrix}$$

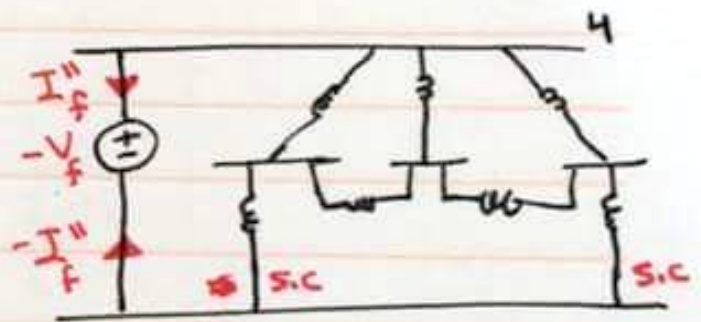


fig ①

\* By using the concept of  $[Y]$  and  $[Z]$ :

$$\therefore [I] = [Y][V]$$

$$\text{OR } [Y]^{-1}[I] = [V]$$

$$* Z \triangleq [Y]^{-1}$$

$$\text{OR } [V] = [Z][I] \text{ --- ①}$$

\* by applying ① to fig ①:

$$\begin{bmatrix} \Delta V_1 \\ \Delta V_2 \\ \Delta V_3 \\ \Delta V_4 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & Z_{13} & Z_{14} \\ Z_{21} & Z_{22} & Z_{23} & Z_{24} \\ Z_{31} & Z_{32} & Z_{33} & Z_{34} \\ Z_{41} & Z_{42} & Z_{43} & Z_{44} \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 0 \\ -I_f'' \end{bmatrix}$$

$$\begin{bmatrix} \Delta V_1 \\ \Delta V_2 \\ \Delta V_3 \\ -V_f \end{bmatrix} = -I_f'' \begin{bmatrix} Z_{14} \\ Z_{24} \\ Z_{34} \\ Z_{44} \end{bmatrix}$$

$$\therefore -V_f = -I_f'' Z_{44}$$

$$\therefore I_f'' = V_f / Z_{44}$$

\* in general:  $I_{f,k}'' = \frac{V_{f,k}}{Z_{kk}}$

$$\begin{bmatrix} \Delta V_1 \\ \Delta V_2 \\ \Delta V_3 \\ \Delta V_4 \end{bmatrix} = - \begin{bmatrix} Z_{14} V_f / Z_{44} \\ Z_{24} V_f / Z_{44} \\ Z_{34} V_f / Z_{44} \\ Z_{44} V_f / Z_{44} \end{bmatrix}$$



due to  
the source  $(-V_f)$

\* total voltages at the busbars:

now the voltages due to the sources  $E_1''$ ,  $E_2''$ ,  $V_f$  and neglecting load currents, will be:

$$\begin{bmatrix} V_f \\ V_f \\ V_f \\ V_f \end{bmatrix}$$

→ total voltage at busbars:

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} V_f \\ V_f \\ V_f \\ V_f \end{bmatrix} + \begin{bmatrix} \Delta V_1 \\ \Delta V_2 \\ \Delta V_3 \\ \Delta V_4 \end{bmatrix}$$

↓  
due to  
3 sources

↓  
due to  
( $-V_f$ )

\* e.g.:


$$\begin{aligned} V_4 &= V_f + \Delta V_4 \\ &= V_f - V_f \\ &= 0 \end{aligned}$$

$$* I_f'' = V_f / Z_{kk} \quad \text{--- (1)}$$

$$V_j = V_f - Z_{jk} I_f'' \quad \text{--- (2)}$$

$$V_j = V_f - \frac{Z_{jk} V_f}{Z_{kk}}$$

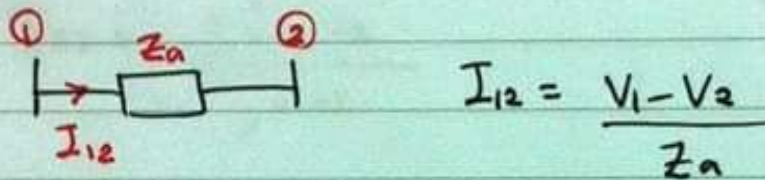\* Having evaluated the voltages at the busbars then one can calculate internal fault current.



\* eg: the bus-impedance matrix of a 4-bus system is:


$$Z = j \begin{bmatrix} 0.15 & 0.08 & 0.04 & 0.07 \\ 0.08 & 0.15 & 0.06 & 0.09 \\ 0.04 & 0.06 & 0.13 & 0.05 \\ 0.07 & 0.09 & 0.05 & 0.72 \end{bmatrix}$$

\* The system has generators connected to buses ① and ② if pre-fault current is neglected evaluate  $(I_f'')$ , for a 3 phase fault at bus ④

\* Assume  $V_f = 1 \angle 0$  pu, find also the current from generator ② whose  $X''_{G2} = j0.02$

$$\begin{aligned} * I_f'' &= V_f / Z_{44} \\ &= 1 \angle 0 / j0.12 \\ &= 8.33 \angle -90^\circ \end{aligned}$$

$$* I_{G2} = \frac{E_2'' - V_2}{j0.02}$$

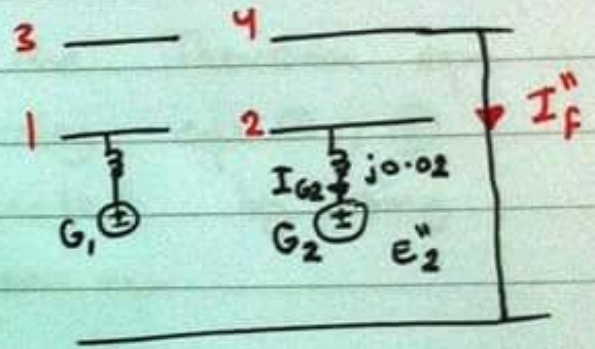

$$\begin{aligned} \rightarrow V_2 &= V_f - Z_{24} I_f'' \\ &= 1 \angle 0 - j0.09 * 8.33 \angle -90 \\ &= 0.251 \angle 0 \end{aligned}$$

$$\rightarrow E_2 = 1 \angle 0$$


$$\begin{aligned} * \text{by sub: } I_{G2}'' &= -3.75 \\ &= 3.75 \angle -90 \end{aligned}$$

### \* Equivalent ckt of Z-bus matrix:

it is impossible to find a single equ. ckt. for the Z-bus method.

However, one may find the Thevenin equ. for a pair of buses by using equ ①, ② so that  $(I_f'')$  can be evaluated by using Thev. equ.

### \* procedure:

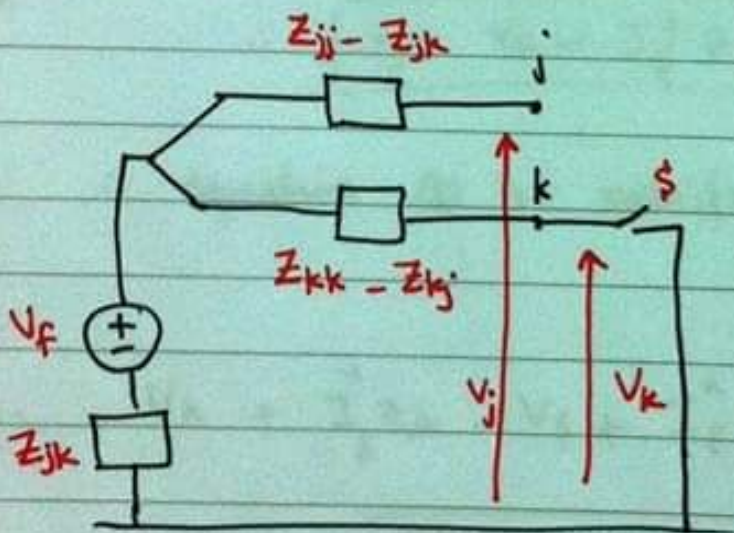

$k = \text{faulty bus}$   
 $j = \text{healthy bus}$



\* S open: (pre-fault)

by applying kVL:


$$V_k = V_j = V_f$$

\* S closed: (i.e.: sc fault between k and ref)

the  $I_f''$  is going to flow  
by kVL:

$$\underline{V_j}: \quad -V_j + 0 + V_f - I_f'' Z_{jk} = 0$$
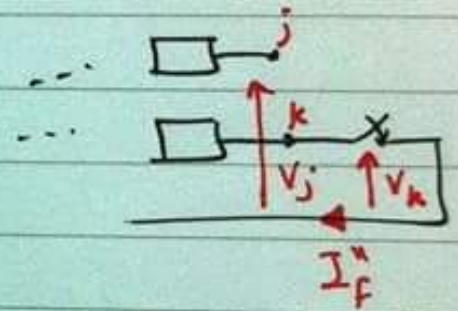
$$\therefore \boxed{V_j = V_f - I_f'' Z_{jk}}$$



$\therefore$  equation ② is satisfied


$$\underline{V_k}: \quad V_k + I_f'' Z_{jk} - V_f + I_f'' (Z_{kk} - Z_{kj}) = 0$$

$$\therefore \boxed{I_f'' = V_f / Z_{kk}}$$

$\therefore$  equation ① is satisfied




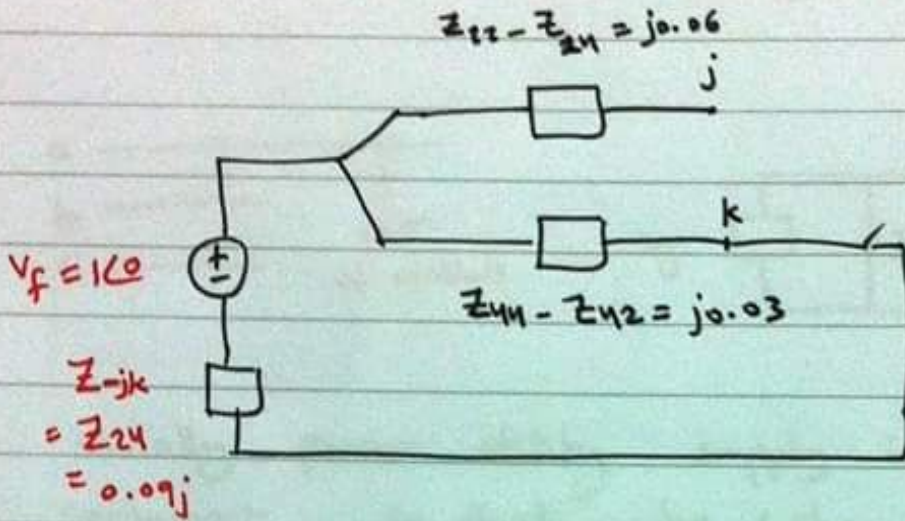\* Solve the previous example by using Thev. equ.:



\* by sub:  $I_f'' = 8.33 \angle -90^\circ$   
 $V_2 = 0.251 \angle 0^\circ$

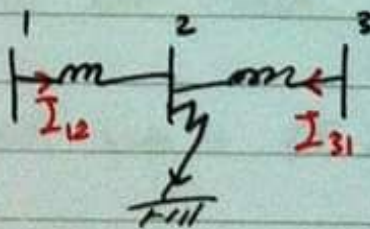
\* See and study the example in the text book.  
 e.g (10.4)  
 page 396



by using Thev. equ.

\* There are two steps for Thev. equ.

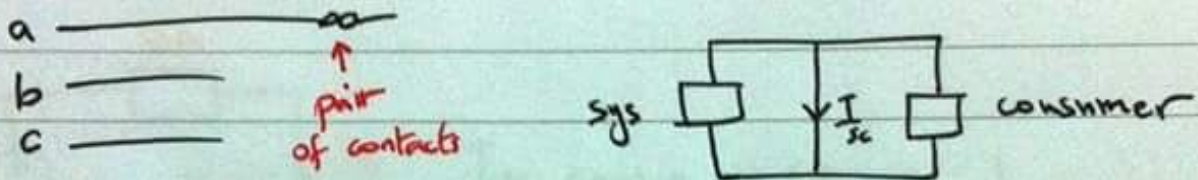\* Introduction for the selection of ckt breaker rating:



\* usually power utility supply information to consumer, so that he/she can evaluate s.c current

\* This information is called SC MVA and defined as follows:

$$\rightarrow \text{SC MVA} \triangleq \sqrt{3} * (\text{nominal line voltage}) * I_{sc} * 10^{-3}$$

(kV) (A) ①


\* if the MVA base is defined as:

$$\text{MVA base} = \sqrt{3} * (\text{base voltage})(\text{base current}) * 10^{-3}$$

②

$$\frac{\text{①}}{\text{②}} \Rightarrow \text{SC MVA (pu)} = I_{sc} \text{ (pu)}$$

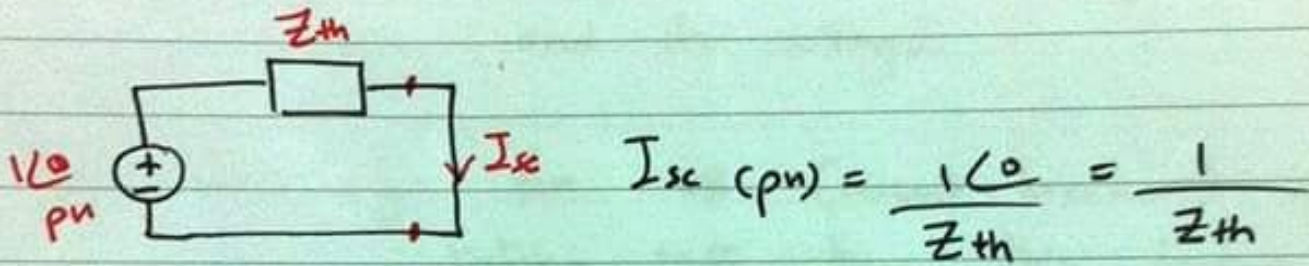\* If the utility sys. looking from the consumer terminals is represented by its Thew. equ. hence under SC :



\* hence utility is supplying:

- ① expected SC
- ②  $Z_{th}$  of the sys.


\* from current point of view, the most two important factors:

- i) the max ~~is~~ instantaneous current, which the breaker must withstand.
- ii) the interrupting current (i.e.: the current at which contact open)



i) in order to take into account the DC component then the sub-transient current ( $I''$ ) is multiplied by a factor  $\Xi (>1)$ . This factor ~~is~~ depend on the type of breaker and its voltage.

\* for e.g: for CB (circuit breaker) with rating  $>5$  kv, this factor = 1.6


\* hence this is called: **Momentary current**  $\Rightarrow$   
 $= \text{factor} * I''$  

\* this is current which the breaker should with stand for a short period  
 1, 2 cycles

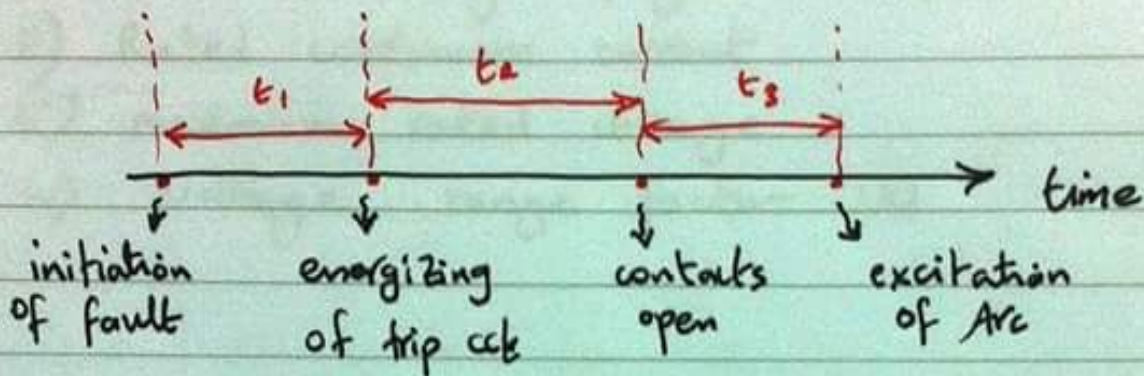ii) is defined by means of interrupting  $\text{kVA} = \sqrt{3} * \text{bus voltage at which breaker is connected (kv)} * \text{interrupting current (A)}$

\* this value depend on the speed of the breaker


\* Breakers with different speed are classified according to their interrupting time, which is defined as follows:



→  $t_1 \equiv$  delay time of relay to take into account starting normal current or guarding or coordination of protection.

→  $t_2 \equiv$  opening time

→  $t_3 \equiv$  Arc excitation time

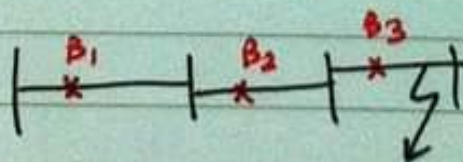

\*  $(t_2 + t_3)$  is called interrupting time.

## \* Conclusion:

Among the major Ratings of C.B are :

- i) nominal voltage (e.g: 132 kv)
- ii) Rated continuous current
- iii) maximum rated voltage
- iv) voltage range factor (k)

$$* k \triangleq \frac{\text{maximum rated voltage}}{\text{lower limit of voltage range}}$$

→ k is selected in such away that the product of (sc current \* operating voltage) is always constant

v) Rated sc current

\* e.g.: A circuit breaker having nominal voltage rating of 34.5 kv continuous current rating of 1500 A, has  $k=1.65$  rated maximum voltage is 38 kv and the rated SC current at this voltage is 22 kA

i) find the voltage below which rated SC current doesn't increase as operating voltage decreases and the value of that current.

$$\Rightarrow k = \frac{\text{max. voltage}}{\text{lower limit}} \Rightarrow V_{\text{lower}} = \frac{\text{max}}{k}$$

$$\frac{38}{1.65} = \boxed{23.03} \text{ kv}$$

\* SC current \* operating voltage = constant  
 $38 * 22 = 23.03 * I_{sc}$

$$\therefore I_{sc} = \frac{38 * 22}{23.03} = \boxed{36.3} \text{ kA}$$

## \* Unbalanced or Unsymmetrical faults :-

Here under unbalanced faults, current and voltages will be unbalanced.

Here the mathematical concept of symmetrical components will be used and defined as:

## \* Symmetrical components :-

Here any unbalanced voltage or current can be expressed as the sum of 3 components called:


+ve sequence  
-ve sequence  
Zero sequence

\* superscripts are used: (1)  $\rightarrow$  +ve  
(2)  $\rightarrow$  -ve  
(0)  $\rightarrow$  Zero

\* for e.g: consider system of unbalanced voltages  $V_{an}, V_{bn}, V_{cn}$


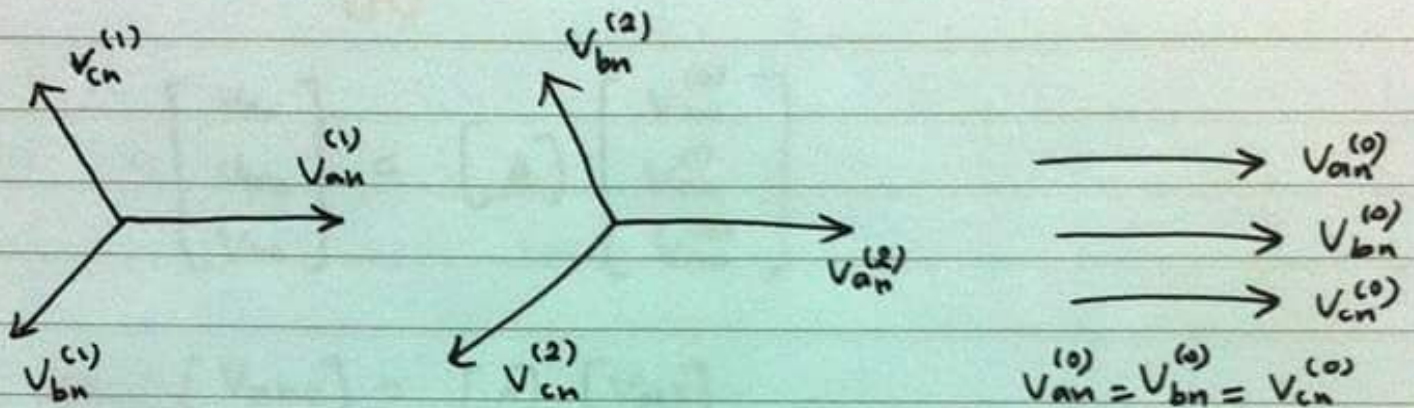
$$\therefore \begin{aligned} V_{an} &= V_{an}^{(0)} + V_{an}^{(1)} + V_{an}^{(2)} \\ V_{bn} &= V_{bn}^{(0)} + V_{bn}^{(1)} + V_{bn}^{(2)} \\ V_{cn} &= V_{cn}^{(0)} + V_{cn}^{(1)} + V_{cn}^{(2)} \end{aligned}$$



+ve

-ve

Zero

\* By introducing the mathematical complex operator  $a \triangleq 1 \angle 120^\circ$  hence, by using (a) all the voltages ~~can~~  $V_{an}, V_{bn}, V_{cn}$  can be expressed in terms of the symmetrical components of phase (a), as:

$$\begin{aligned} \rightarrow V_{an} &= V_{an}^{(0)} + V_{an}^{(1)} + V_{an}^{(2)} \\ V_{bn} &= V_{an}^{(0)} + a^2 V_{an}^{(1)} + a V_{an}^{(2)} \\ V_{cn} &= V_{an}^{(0)} + a V_{an}^{(1)} + a^2 V_{an}^{(2)} \end{aligned}$$



$$\Rightarrow \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_{an}^{(0)} \\ V_{an}^{(1)} \\ V_{an}^{(2)} \end{bmatrix}$$

[A]

$$\therefore \begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix} = [A] \begin{bmatrix} V_{an}^{(0)} \\ V_{an}^{(1)} \\ V_{an}^{(2)} \end{bmatrix}$$

$$\Rightarrow [V_{abc}] = [A] [V_{012}]$$

$$[V_{012}] = [A]^{-1} [V_{abc}]$$

$$* \text{ where: } [A]^{-1} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix}$$


\* note: the same expression can be applied to current:

$$[I_{abc}] = [A] [I_{012}]$$

$$[I_{012}] = [A]^{-1} [I_{abc}]$$


## \* Procedure :

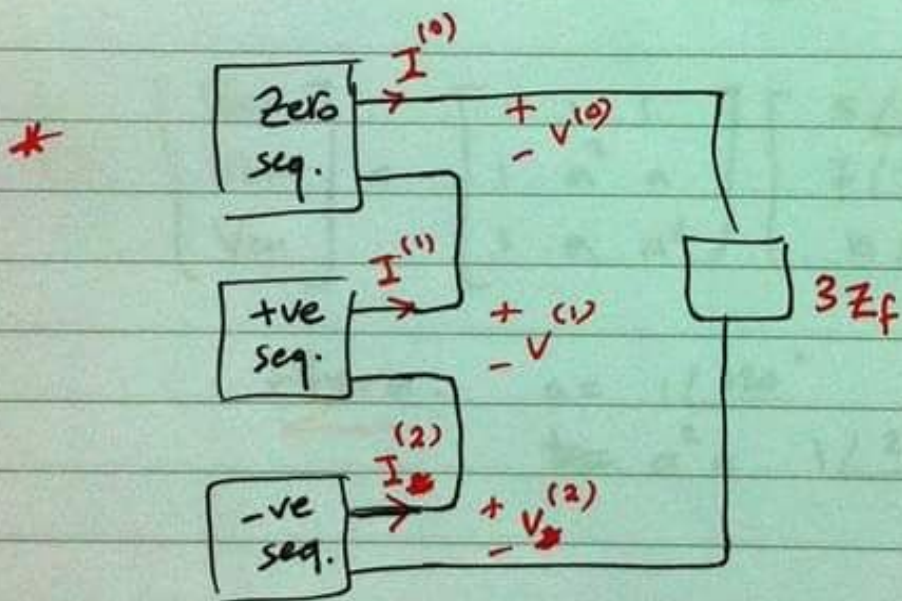- i) find the 0, +ve, -ve sequences ckt for each power system element  
(i.e.: generator, transf., line, load)
- ii) the inter connection of these sequence ckt ~~are~~ give sequence networks  
(i.e.: +ve, -ve, 0 sequence network)



- iii) the interconnection between networks depends on the type of the fault (i.e.: L-L  
L-G  
L-L-G)

\* eg: (L-G)

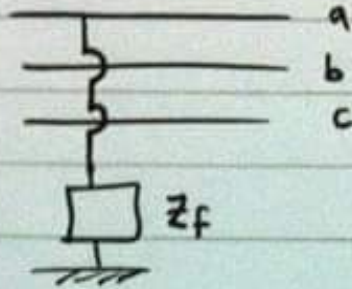

as will be shown later

\* eg:

Given:  $V_{an}^{(0)} = 5 \angle 30^\circ$  ; find  $[V_{abc}]$  ?  
 $V_{an}^{(1)} = 7 \angle -14^\circ$   
 $V_{an}^{(2)} = 10 \angle 41^\circ$

$$\Rightarrow \begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 5 \angle +30 \\ 7 \angle -14 \\ 10 \angle 41 \end{bmatrix}$$

where:  $a = 1 \angle 120^\circ$   
 $a^2 = 1 \angle 240^\circ$

\* e.g.: When a 3 phase generator has 1 terminal open ckt and the other two terminals are shorted to ground, the symm. component of the currents as follows:

$$I_a^{(1)} = 600 \angle -90^\circ$$

$$I_a^{(2)} = 250 \angle 90^\circ$$


and  $I_a^{(0)} = 350 \angle 90^\circ$

\* find the corresponding phase current and fault current?

$$\Rightarrow \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I^{(0)} \\ I^{(1)} \\ I^{(2)} \end{bmatrix} \quad \begin{cases} a = 1 \angle 120^\circ \\ a^2 = 1 \angle 240^\circ \end{cases}$$

\* By substitution and multiplication, it can be found:

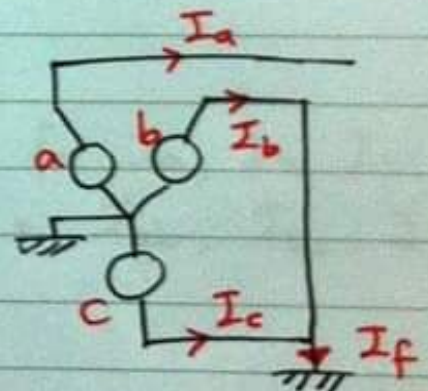
$$= \begin{bmatrix} 904.16 \angle 144.5^\circ \\ 904.16 \angle 33.5^\circ \end{bmatrix}$$



$$I_f = I_b + I_c = 1050.1 \angle 90^\circ$$

\* Relationship between symmetrical components for currents and voltages of Y and  $\Delta$  connections:

\* consider a  $\Delta$  connection:

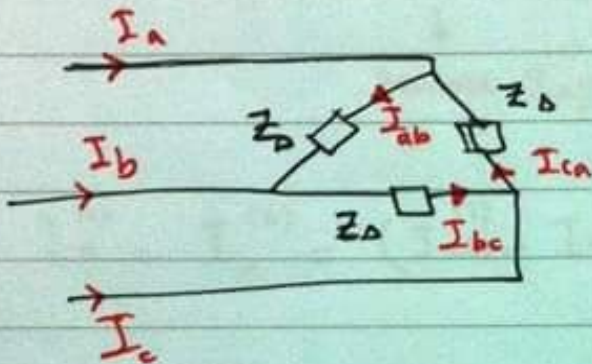

\* objective: to find relationship between:

$$I_a^{(1)}, I_{ab}^{(1)}$$

$$I_a^{(2)}, I_{ab}^{(2)}$$

note:  $(I_a)$  is taken as reference for  $I_a, I_b, I_c$   
and  $(I_{ab}) = = = = = I_{ab}, I_{bc}, I_{ca}$

\* Procedure:

by KCL:

$$I_a = I_{ab} - I_{ca} \quad \text{---} \quad \textcircled{1}$$

$$I_b = I_{bc} - I_{ab} \quad \text{---} \quad \textcircled{2}$$

$$I_c = I_{ca} - I_{bc} \quad \text{---} \quad \textcircled{3}$$

$$I_a^{(0)} \triangleq \frac{1}{3} (I_a + I_b + I_c) = 0 \quad * \text{ by sub. 1, 2, 3}$$

$\therefore$  linear currents don't have zero sequence components





\* rewrite ① in terms of its symmetrical components:

$$I_a^{(0)} + I_a^{(1)} + I_a^{(2)} = (I_{ab}^{(0)} + I_{ab}^{(1)} + I_{ab}^{(2)}) - (I_a^{(0)} + I_a^{(1)} + I_a^{(2)})$$

$$I_a^{(1)} + I_a^{(2)} = \cancel{(I_{ab}^{(0)} - I_{ca}^{(0)})} + (I_{ab}^{(1)} - I_{ca}^{(1)}) + (I_{ab}^{(2)} - I_{ca}^{(2)})$$

↓  
because  $I_a^{(0)} = I_b^{(0)} = I_c^{(0)}$
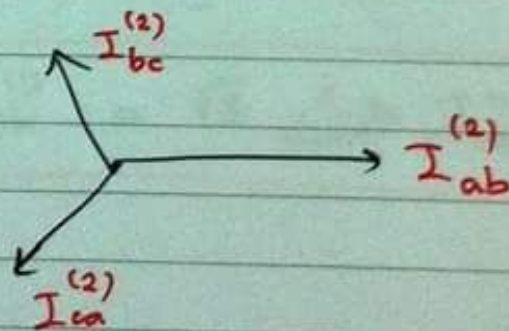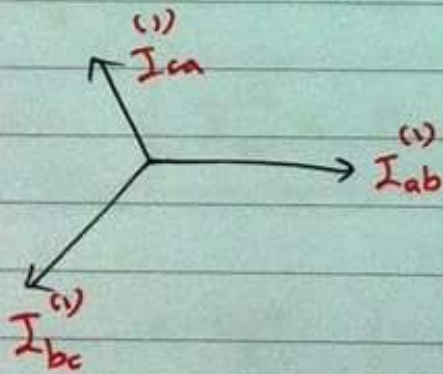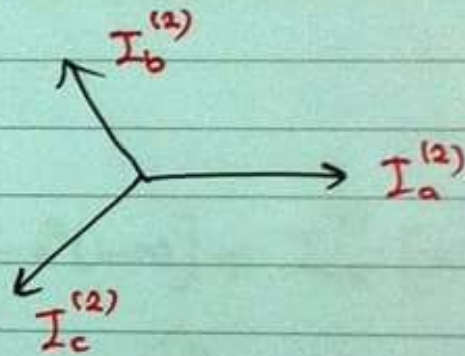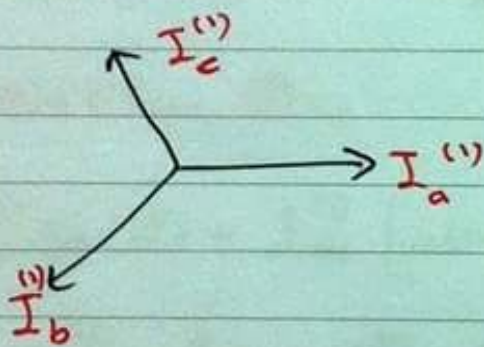
$$\therefore I_a^{(1)} + I_a^{(2)} = (I_{ab}^{(1)} - I_{ca}^{(1)}) + (I_{ab}^{(2)} - I_{ca}^{(2)})$$



\* If ① and ② are solved for  $I_a^{(2)}$ , it can be found that:

$$I_a^{(2)} = \sqrt{3} \angle 30^\circ I_{ab}^{(2)}$$

note: similar expression can be ~~found~~ obtained for  
 $I_b^{(1)}$  &  $I_b^{(2)}$  by replacing  $(I_{ab})$  by  $(I_{bc})$   
 $I_c^{(1)}$ ,  $I_c^{(2)}$  by replacing  $(I_{ab})$  by  $(I_{ca})$


\* Symm-components of voltage:

\* consider Y connection:

$$V_{ab} = V_{an} - V_{bn} \quad \text{--- ①}$$

$$V_{bc} = V_{bn} - V_{cn} \quad \text{--- ②}$$
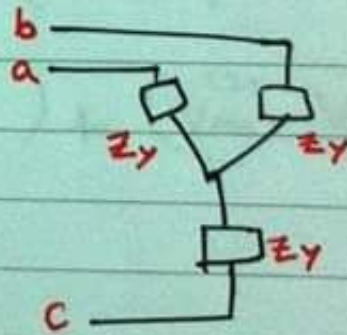
$$V_{ca} = V_{cn} - V_{an} \quad \text{--- ③}$$



\* let  $(V_{an})$  reference for  $V_{an}, V_{bn}, V_{cn}$   
 &  $(V_{ab}) =$  &  $V_{ab}, V_{bc}, V_{ca}$



\* now;

$$V_{ab} \triangleq \frac{1}{3} (V_{ab} + V_{bc} + V_{ca}) \text{ --- (4)}$$

\* sub 1, 2, 3 into (4) :  $V_{ab}^{(0)} = 0$ 

$$\text{Since } V_{ab}^{(0)} = V_{bc}^{(0)} = V_{ca}^{(0)} = 0$$

$\therefore$  line voltages doesn't have zero seq. comp.


\* rewrite (4) in terms of its symm-components:

$$\left( \cancel{V_{ab}^{(0)}} + V_{ab}^{(1)} + V_{ab}^{(2)} \right) = \left( V_{an}^{(0)} + V_{an}^{(1)} + V_{an}^{(2)} \right) - \left( V_{bn}^{(0)} + V_{bn}^{(1)} + V_{bn}^{(2)} \right)$$

$$\therefore V_{ab}^{(1)} + V_{ab}^{(2)} = \left( V_{an}^{(1)} - V_{bn}^{(1)} \right) + \left( V_{an}^{(2)} - V_{bn}^{(2)} \right) \text{ --- (5)}$$

$\rightarrow$  Since  $\left( V_{an}^{(0)} - V_{bn}^{(0)} \right) = 0$
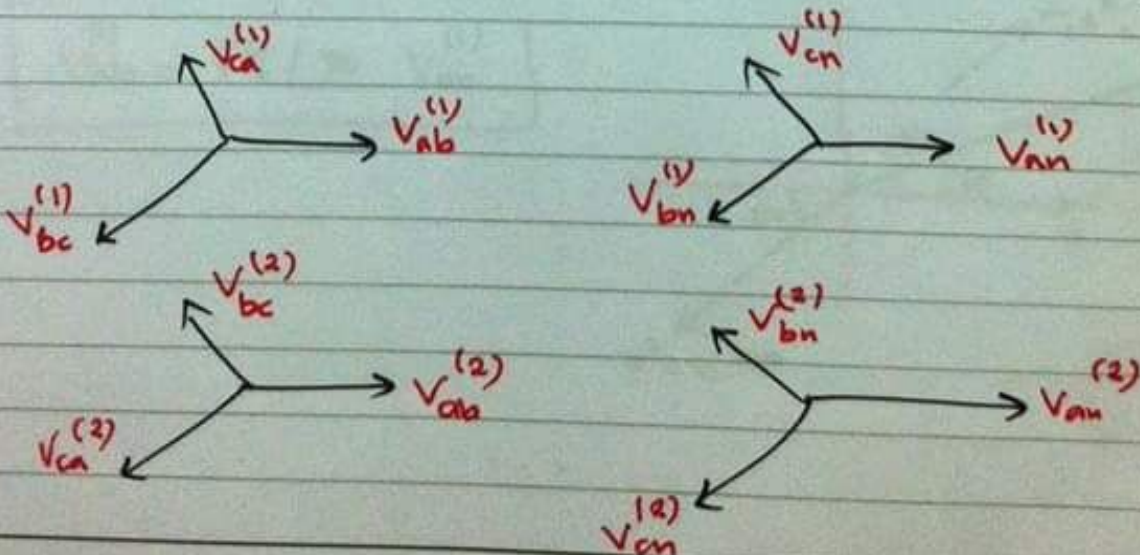
$$V_{ab}^{(1)} + V_{ab}^{(2)} = \left( V_{an}^{(1)} - a V_{an}^{(1)} \right) + \left( V_{an}^{(2)} - a V_{an}^{(2)} \right)$$



$$\Rightarrow \boxed{V_{ab}^{(1)} + V_{ab}^{(2)} = V_{an}^{(1)} (1-a^2) + V_{an}^{(2)} (1-a)} \quad \text{--- (6)}$$

by using (2) similar equation can be written for  $V_{bc}$ :

$$V_{bc}^{(1)} + V_{bc}^{(2)} = V_{bn}^{(1)} (1-a^2) + V_{bn}^{(2)} (1-a)$$

$$a^2 V_{ab}^{(1)} + a V_{ab}^{(2)} = a^2 V_{an}^{(1)} (1-a^2) + a V_{an}^{(2)} (1-a) \quad \text{--- (7)}$$

$\Rightarrow a \times \text{(6)} - \text{(7)}$ :


$$V_{ab}^{(1)} (a - a^2) = V_{an}^{(1)} (a(1-a^2) - a^2(1-a^2))$$

$$+ V_{an}^{(2)} (a(1-a) - a(1-a))$$

$$V_{ab}^{(1)} (a - a^2) = V_{an}^{(1)} (1-a^2) (a - a^2)$$

$$\star \boxed{V_{ab}^{(1)} = V_{an}^{(1)} (1-a^2)}$$
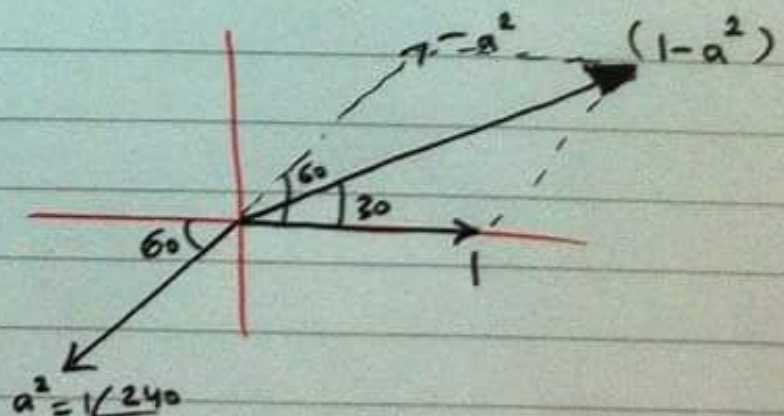
$$\therefore \boxed{V_{ab}^{(1)} = \sqrt{3} / 30 V_{an}^{(1)}}$$



\* if the same 2 equations are solved for  $V_{ab}^{(2)}$ , it can be found:

$$V_{ab}^{(2)} = \sqrt{3} \angle -30^\circ V_{an}^{(2)}$$

\* note: similar equations can be obtained for  $V_{bc}$  and  $V_{ca}$  by:

replacing  $(V_{ab})$  by  $(V_{abc})$  and  $(V_{an})$  by  $(V_{bn})$   
 and  $(V_{ab})$  by  $(V_{ca})$  and  $(V_{an})$  by  $(V_{cn})$

\* Power in terms of symm-components :

\* conclusions and comments :

⇒ symm-components

$$I_a^{(1)} = \sqrt{3} I_{ab}^{(1)} \angle -30^\circ \quad \text{--- (1)}$$


$$I_a^{(2)} = \sqrt{3} I_{ab}^{(2)} \angle 30^\circ \quad \text{--- (2)}$$

$$V_{ab}^{(1)} = \sqrt{3} V_{an}^{(1)} \angle 30^\circ \quad \text{--- (3)}$$

$$V_{ab}^{(2)} = \sqrt{3} V_{an}^{(2)} \angle -30^\circ \quad \text{--- (4)}$$

$$Z_D = \frac{V_{ab}^{(1)}}{I_{ab}^{(1)}} = \frac{\sqrt{3} V_{an}^{(1)} \angle 30^\circ}{I_a^{(1)} / \sqrt{3} \angle 30^\circ} \quad \text{by using 3, 1}$$
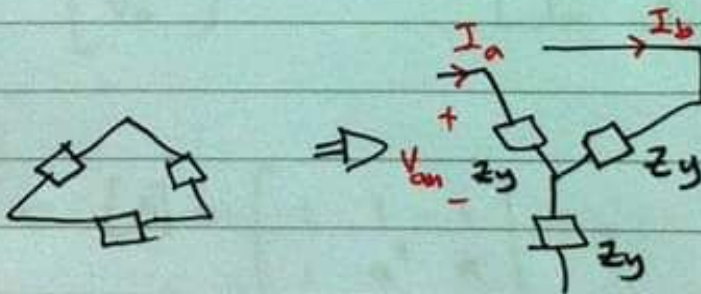
$$Z_D = \frac{\sqrt{3} \sqrt{3} V_{an}^{(1)} \angle 30^\circ}{\sqrt{3} I_a^{(1)} \angle 30^\circ} = \frac{3 V_{an}^{(1)}}{I_a^{(1)}} = 3 Z_y$$



\* power in terms of symm. components:

$$S \triangleq V_{an} I_a^* + V_{bn} I_b^* + V_{cn} I_c^*$$

$$= \begin{bmatrix} V_{an} & V_{bn} & V_{cn} \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}^*$$

$$\therefore S = \begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix}^T \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}^* = \begin{bmatrix} [A] \\ \begin{bmatrix} V_a^{(0)} \\ V_a^{(1)} \\ V_a^{(2)} \end{bmatrix} \end{bmatrix}^T * \begin{bmatrix} [A] \\ \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix} \end{bmatrix}^*$$

$$\rightarrow S = \begin{bmatrix} V_a^{(0)} \\ V_a^{(1)} \\ V_a^{(2)} \end{bmatrix}^T [A]^T [A]^* \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix}^* \quad \text{--- (1)}$$

$$* [A]^T = [A] = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}, \quad [A]^* = \begin{bmatrix} 1^* & 1^* & 1^* \\ 1^* & a^{2*} & a^* \\ 1^* & a^* & a^{2*} \end{bmatrix}$$

where:

$$\left\{ \begin{aligned} 1^* &= 1 \\ a^* &= 1 \angle -120^\circ = 1 \angle 240^\circ = a^2 \\ a^{2*} &= 1 \angle 240^\circ = 1 \angle 120^\circ = a \end{aligned} \right.$$

$$[A]^* = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix}$$

⇒ Also it can be shown:

$$1 + a + a^2 = 0$$

$$[A]^T [A]^* = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} = \begin{bmatrix} 3 & 0 & 0 \\ 0 & 3 & 0 \\ 0 & 0 & 3 \end{bmatrix} \text{--- (2)}$$

substitute (2) in (1):

$$S = \begin{bmatrix} V_a^{(0)} & V_a^{(1)} & V_a^{(2)} \end{bmatrix} \begin{bmatrix} 3 & 0 & 0 \\ 0 & 3 & 0 \\ 0 & 0 & 3 \end{bmatrix} \begin{bmatrix} I_a^{(0)*} \\ I_a^{(1)*} \\ I_a^{(2)*} \end{bmatrix}$$

$1 \times 3$                        $3 \times 3$                        $3 \times 1$

$$\Rightarrow S = 3V_a^{(0)} I_a^{(0)*} + 3V_a^{(1)} I_a^{(1)*} + 3V_a^{(2)} I_a^{(2)*}$$

\* Ex: A balanced Y connected resistive load of  $10\Omega$  have the following voltages at its terminals:  
 $V_{ab} = 100 \angle 0^\circ$ ,  $V_{bc} = 80.8 \angle -121.44^\circ$ ,  $V_{ca} = 90 \angle 130^\circ$  V  
 by assuming that there is no connection to the neutral of the load. find:

- 1) line currents from the symm-comp. of the given lines voltages.
- 2) the supplied power by using symm-comp. of voltage and current.




## \* sequence ckt of power system analysis :-

\* objective: to find the equivalent Zero, +ve, -ve sequence ccts of Generator, transformer, line, load.

\* consider a 3ph Y connected load:

$V_{an}$  = phase voltage

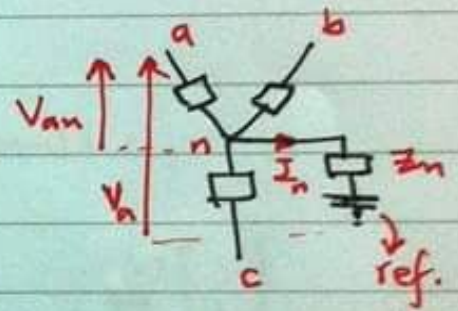$V_a$  = voltage between line terminal and ref.



\* By KVL:

$$V_a = V_{an} + I_n Z_n \quad \text{--- (1)}$$

$$V_b = V_{bn} + I_n Z_n \quad \text{--- (2)}$$

$$V_c = V_{cn} + I_n Z_n \quad \text{--- (3)}$$

$$I_n = I_a + I_b + I_c$$

$$\Rightarrow (I_a^{(0)} + I_a^{(1)} + I_a^{(2)}) + (I_b^{(0)} + I_b^{(1)} + I_b^{(2)}) + (I_c^{(0)} + I_c^{(1)} + I_c^{(2)})$$

$$= (I_a^{(0)} + I_b^{(0)} + I_c^{(0)}) + (I_a^{(1)} + I_b^{(1)} + I_c^{(1)}) + (I_a^{(2)} + I_b^{(2)} + I_c^{(2)})$$

$$I_a^{(0)} = I_b^{(0)} = I_c^{(0)}$$

(balanced)

$$\Rightarrow \boxed{I_n = 3I_a^{(0)}} \quad \text{--- (4)}$$

\* Rewrite 1, 2, 3:

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix} + 3Z_n I_a^{(0)}$$

$$= \begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix} + 3Z_n I_a^{(0)} \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} \text{ --- (5)}$$

\* rewrite in terms of symm ~~com~~ components:

$$[A] \begin{bmatrix} V_a^{(0)} \\ V_a^{(1)} \\ V_a^{(2)} \end{bmatrix} = [A] \begin{bmatrix} V_{an}^{(0)} \\ V_{an}^{(1)} \\ V_{an}^{(2)} \end{bmatrix} + 3Z_n I_a^{(0)} \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} \text{ --- (6)}$$

$\Rightarrow$  ~~Eq~~ (6) \*  $[A]^{-1}$ :

$$\begin{bmatrix} V_a^{(0)} \\ V_a^{(1)} \\ V_a^{(2)} \end{bmatrix} = \begin{bmatrix} V_{an}^{(0)} \\ V_{an}^{(1)} \\ V_{an}^{(2)} \end{bmatrix} + 3Z_n I_a^{(0)} [A]^{-1} \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} \text{ --- (7)}$$

note:

$$V_{an} = Z_y I_a$$

$$V_{bn} = Z_y I_b$$

$$V_{cn} = Z_y I_c$$



$$\Rightarrow [A] \begin{bmatrix} V_{an}^{(0)} \\ V_{an}^{(1)} \\ V_{an}^{(2)} \end{bmatrix} = Z_y [A] \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix}$$

$$\therefore \begin{bmatrix} V_{an}^{(0)} \\ V_{an}^{(1)} \\ V_{an}^{(2)} \end{bmatrix} = Z_y \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix} \text{ --- (8)}$$

sub 8 into 7:

$$\begin{bmatrix} V_a^{(0)} \\ V_a^{(1)} \\ V_a^{(2)} \end{bmatrix} = Z_y \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix} + 3Z_n I_a^{(0)} \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix} \text{ --- (9)}$$




$$* \begin{bmatrix} V_a^{(0)} \\ V_a^{(1)} \\ V_a^{(2)} \end{bmatrix} = Z_y \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix} + 3I_a^{(0)} Z_n \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix}$$

$$V_a^{(0)} = Z_y I_a^{(0)} + 3I_a^{(0)} Z_n \text{ --- (1)}$$

$$V_a^{(1)} = Z_y I_a^{(1)} + 0 \text{ --- (2)}$$

$$V_a^{(2)} = Z_y I_a^{(2)} \text{ --- (3)}$$

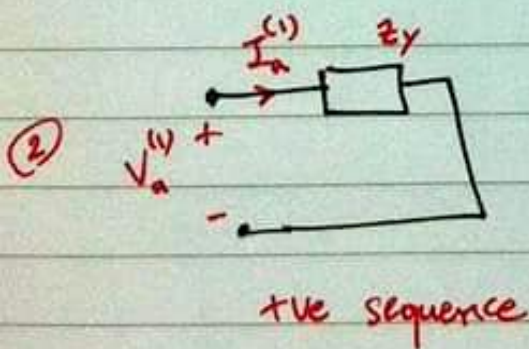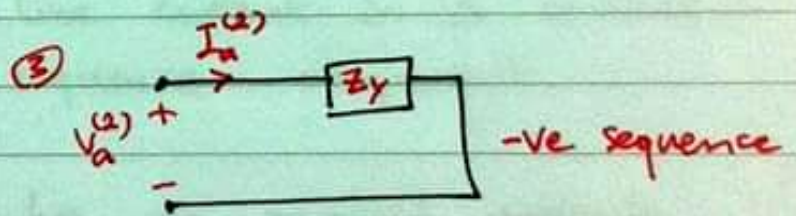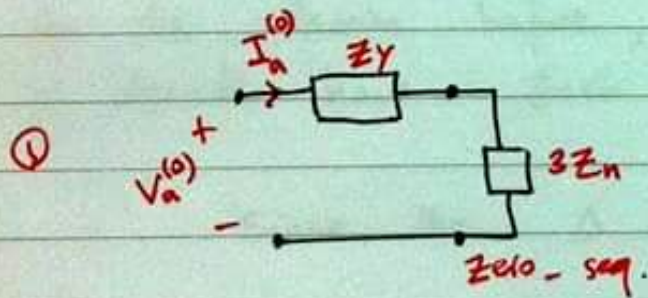\* 1, 2, 3 represent 3 decoupled equations.  
Hence, these equations can be used to deduce the equivalent sequence ckt




$$\therefore \begin{aligned} Z_0 &= Z_y + 3Z_n \\ Z_1 &= Z_y \\ Z_2 &= Z_y \end{aligned}$$

\* Consider the  $\Delta$ -connected load:

$$V_{ab} = I_{ab} Z_{\Delta}$$

$$V_{bc} = I_{bc} Z_{\Delta}$$

$$V_{ca} = I_{ca} Z_{\Delta}$$

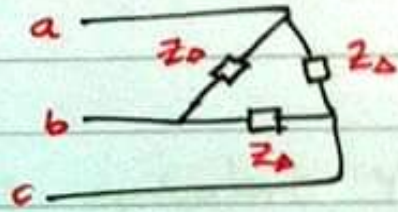

$$\therefore (V_{ab} + V_{bc} + V_{ca}) = (Z_{\Delta} I_{ab} + I_{bc} + I_{ca})$$

0 ↙


$$3 V_{ab}^{(0)} = Z_{\Delta} (3 I_{ab}^{(0)})$$

$$\therefore 0 = 3 V_{ab}^{(0)} = Z_{\Delta} (3 I_{ab}^{(0)})$$

$$\therefore V_{ab}^{(0)} = I_{ab}^{(0)} = \boxed{0}$$

→ As shown before, line current in  $\Delta$  connection doesn't have zero sequence component.

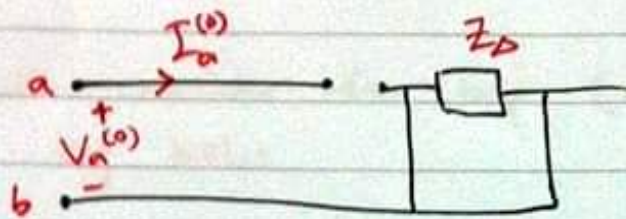
Since the  $\Delta$  has no neutral ~~exists~~ return earth path



Hence, in converting  $\Delta$  to its equivalent  $Y$ , then there is no connection between neutral and ref.

\* Sequence cts of T.L :

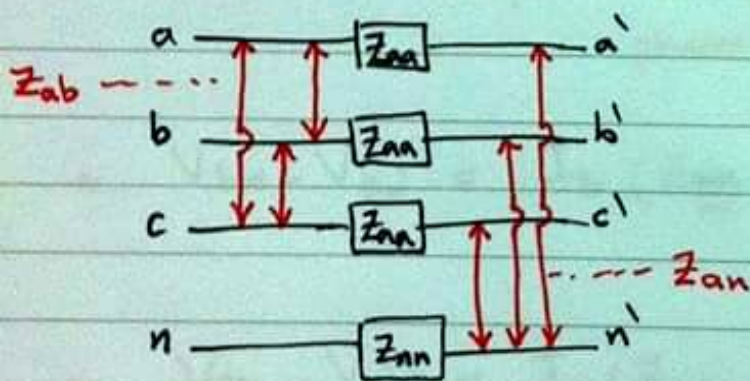\* Consider the following section of a symmetrical T.L :



\*  $Z_{aa}$  = self impedance of each phase conductor

\*  $Z_{nn}$  = self impedance of ~~each~~ neutral

\*  $Z_{ab}$  = mutual impedance ~~between~~ between phases

\*  $Z_{an}$  = mutual impedance between the ~~each~~ neutral and each phase

\* consider the loop (a a' n a)  
by KVL:

$$V_{an} = I_a Z_{an} + I_b Z_{ab} + I_c Z_{ab} + I_n Z_{an} + V_{a'n'} - (I_n Z_{nn} + I_a Z_{an} + I_b Z_{nn} + I_c Z_{an})$$

$$\therefore V_{an} - V_{a'n'} = I_a (Z_{aa} - Z_{an}) + I_b (Z_{ab} - Z_{an}) + I_c (Z_{ab} - Z_{an}) + I_n (Z_{an} - Z_{nn})$$

$$\therefore V_{an} - V_{a'n'} = I_a (Z_{aa} - Z_{an}) + (I_b + I_c) (Z_{ab} - Z_{an}) + I_n (Z_{an} - Z_{nn}) \quad \text{--- (1)}$$


\* Similar equations can be written for phases b, c as follows:

$$* V_{bn} - V_{b'n'} = I_b (Z_{bb} - Z_{bn}) + (I_a + I_c) (Z_{ab} - Z_{bn}) + I_n (Z_{bn} - Z_{nn}) \quad \text{--- (2)}$$

$$* V_{cn} - V_{c'n'} = I_c (Z_{cc} - Z_{cn}) + (I_a + I_b) (Z_{ab} - Z_{cn}) + I_n (Z_{cn} - Z_{nn}) \quad \text{--- (3)}$$

but: by KCL:
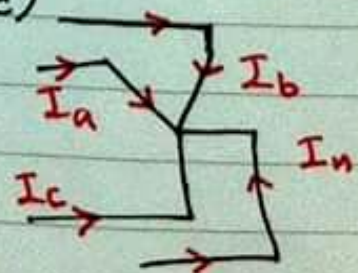
$$I_n = -(I_a + I_b + I_c) \quad \text{--- (4)}$$



\* Sub 4 into 1, 2, 3: and rearrange:

$$\begin{aligned}
 V_{an} - V_{a'n'} &= I_a (Z_{aa} - 2Z_{an} + Z_{nn}) \xrightarrow{Z_s} \\
 &+ I_b (Z_{ab} - 2Z_{an} + Z_{nn}) \xrightarrow{Z_m} \\
 &+ I_c (Z_{ab} - 2Z_{an} + Z_{nn}) \dots \textcircled{5}
 \end{aligned}$$

$$\begin{aligned}
 V_{bn} - V_{b'n'} &= I_a (Z_{ab} - 2Z_{an} + Z_{nn}) \\
 &+ I_b (Z_{an} - 2Z_{an} + Z_{nn}) \\
 &+ I_c (Z_{ab} - 2Z_{an} + Z_{nn}) \dots \textcircled{6}
 \end{aligned}$$

$$\begin{aligned}
 V_{cn} - V_{c'n'} &= I_a (Z_{ab} - 2Z_{an} + Z_{nn}) + \\
 &+ I_b (Z_{ab} - 2Z_{an} + Z_{nn}) \\
 &+ I_c (Z_{aa} - 2Z_{an} + Z_{nn}) \dots \textcircled{7}
 \end{aligned}$$

let:  $Z_s = Z_{aa} - 2Z_{an} + Z_{nn}$   
 $Z_m = Z_{ab} - 2Z_{an} + Z_{nn}$

let:  $V_{a'a} = V_{an} - V_{a'n'}$   
 $V_{b'b} = V_{bn} - V_{b'n'}$   
 $V_{c'c} = V_{cn} - V_{c'n'}$

\* 5, 6, 7 can be written as:

$$\begin{bmatrix} V_{aa'} \\ V_{bb'} \\ V_{cc'} \end{bmatrix} = \begin{bmatrix} Z_s & Z_m & Z_m \\ Z_m & Z_s & Z_m \\ Z_m & Z_m & Z_s \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} \text{----- (8)}$$

\* Express (8) in terms of symm. components:

$$[A] \begin{bmatrix} V_{aa'}^{(0)} \\ V_{aa'}^{(1)} \\ V_{aa'}^{(2)} \end{bmatrix} = \begin{bmatrix} Z_s & Z_m & Z_m \\ Z_m & Z_s & Z_m \\ Z_m & Z_m & Z_s \end{bmatrix} [A] \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix} \text{----- (9)}$$

\* multiply (9) by  $[A]^{-1}$ :

$$\begin{bmatrix} V_{aa'}^{(0)} \\ V_{aa'}^{(1)} \\ V_{aa'}^{(2)} \end{bmatrix} = [A]^{-1} \begin{bmatrix} Z_s & Z_m & Z_m \\ Z_m & Z_s & Z_m \\ Z_m & Z_m & Z_s \end{bmatrix} [A] \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix}$$

↓

$$\begin{bmatrix} Z_s + 2Z_m & 0 & 0 \\ 0 & Z_s - Z_m & 0 \\ 0 & 0 & Z_s - Z_m \end{bmatrix}$$

$$\rightarrow V_{aa'}^{(0)} = I_a^{(0)} (Z_s + 2Z_m) = I_a^{(0)} (Z_{aa} + 2Z_{ab} - 6Z_{an} + 3Z_{nn})$$

$$V_{aa'}^{(1)} = I_a^{(1)} (Z_{aa} - Z_{ab}) \rightarrow Z_1$$


$$V_{aa'}^{(2)} = I_a^{(2)} (Z_{aa} - Z_{ab}) \rightarrow Z_2$$

$Z_0$




$$\Rightarrow \begin{aligned} V_{aa'}^{(0)} &= I_a^{(0)} Z_0 \\ V_{aa'}^{(1)} &= I_a^{(1)} Z_1 \\ V_{aa'}^{(2)} &= I_a^{(2)} Z_2 \end{aligned}$$

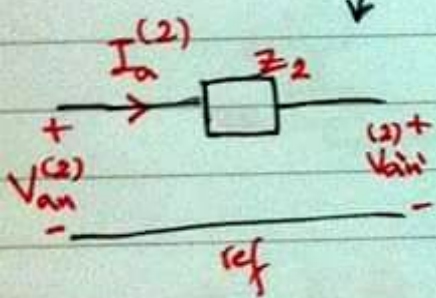
\* where:  $Z_1 = Z_2$   
 $Z_{aa} = R + j\omega L$



+ve sequence

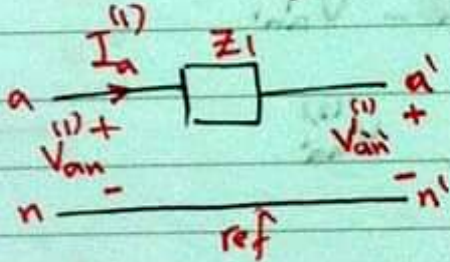

-ve sequence

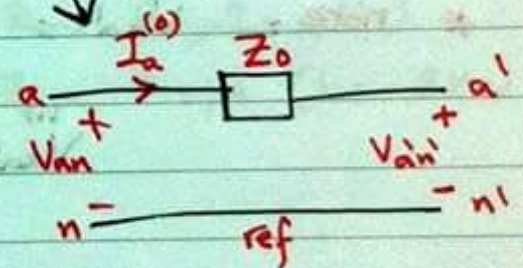


Zero - seq ckt



\* **Comment:**

usually T.L have overhead conductor (2 or more) which are ~~neglected~~ grounded at regular points

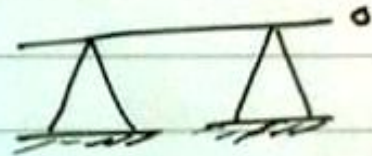these conductors with the earth provide the so called:







(effective neutral return part)

\* **note:**  $V_{aa'}^{(0)} = V_{an}^{(0)} - V_{a'n'}^{(0)}$

$V_{aa'}^{(1)}, V_{aa'}^{(2)}$

\* **note:** by applying some analysis and procedure one can find sequence ccts of gen. + transf.

\* Sequence ccts of 3 phase generator:

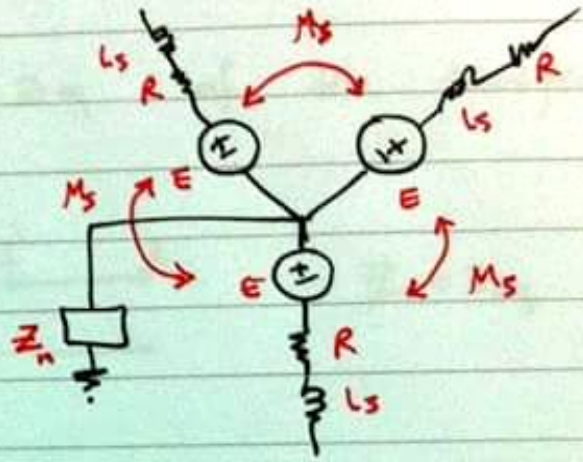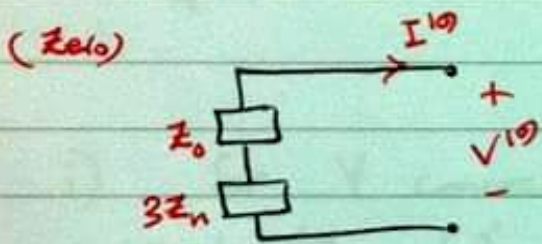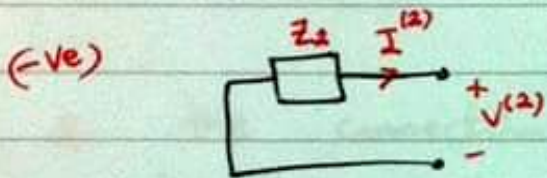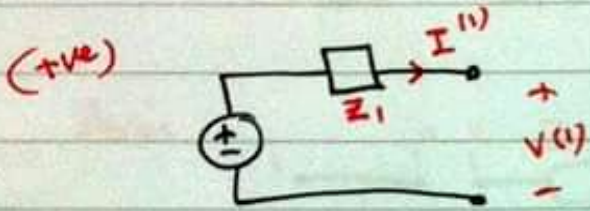




where:



$$Z_1 = Z_2 = R + j\omega(L_s + M_s)$$

$$Z_0 = R + j\omega(L_s - 2M_s)$$

\* 3-ph transformer:

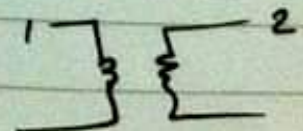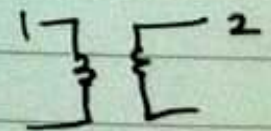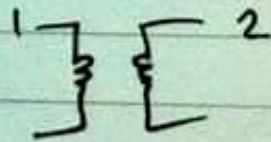
each side (1 and 2) can be connected as  $\Delta$  or Y hence as shown before there are 4 types of connections YY,  $\Delta\Delta$ ,  $\Delta Y$ ,  $Y\Delta$



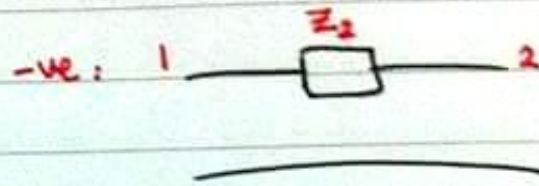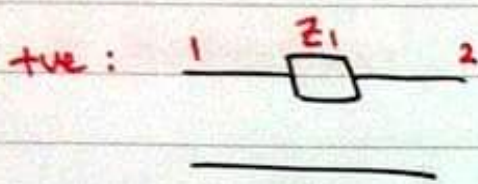

where:  $Z_1 = Z_2 = Z_{eq}$  of the transformer

Zero:

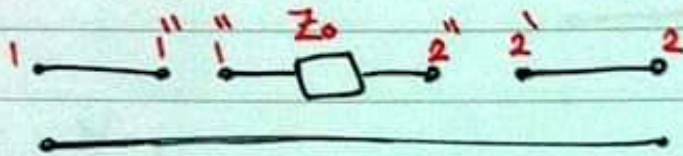


$$Z_0 = Z_{eq}$$

\* the connection between ( $1'$  and  $1''$ ) and ( $2'$  and  $2''$ ) depends on the type of connection for the given side:









i) for Y connection, then connect ( $1'$ ,  $1''$ ) and/or ( $2'$ ,  $2''$ ) by an impedance =  $3Z_n$  where  $Z_n$  = earthing impedance of the neutral.

ii) for  $\Delta$  connection, then short ckt  $1''$  or  $2''$  to the ref.

illustration:

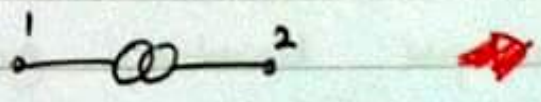


ex:

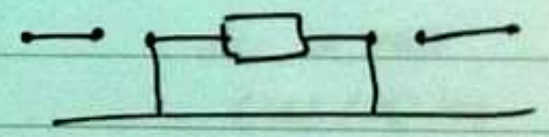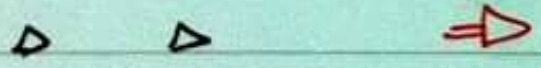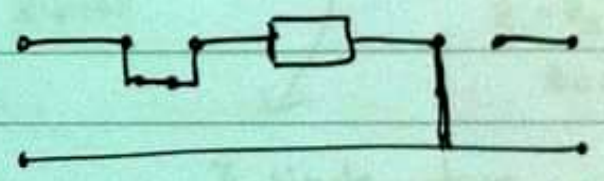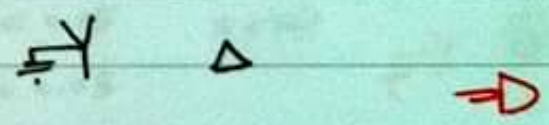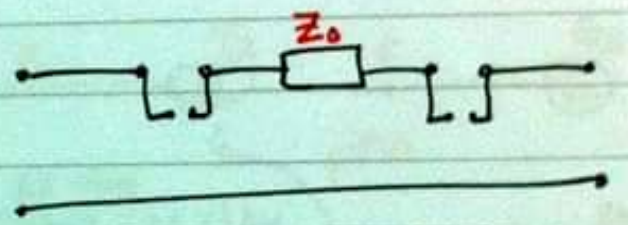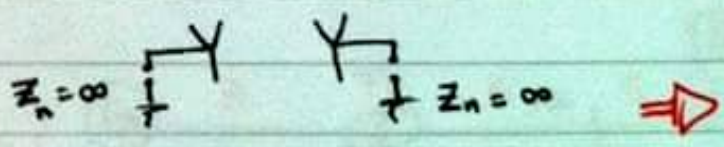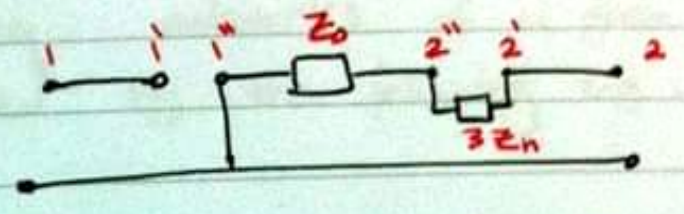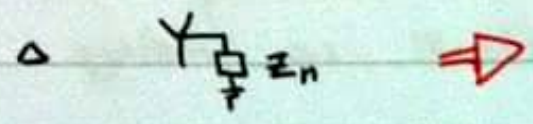

\* Sequence networks:

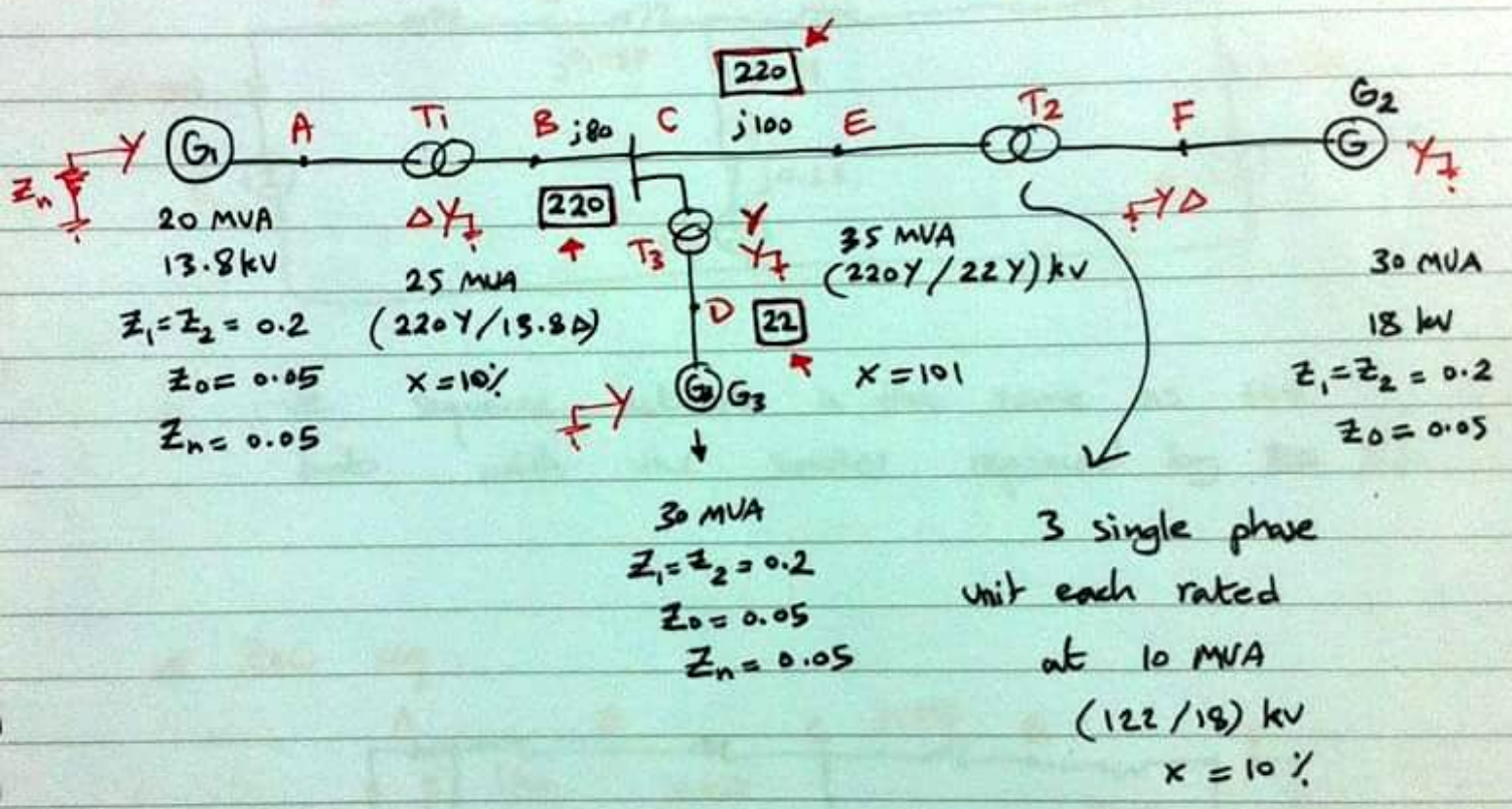Having produced seq. ccts. of individual components, one can produce the seq. networks of a given power system as illustrated - by the following e.g.:




\* for the given power system draw the per unit +ve, -ve, 0 seq networks by using phase values of (50 MVA) and (13.8 kV), also the zero seq impedance of T.L area for BC,  $Z_0 = 210 \Omega$  CE,  $Z_0 = 250 \Omega$

\* pnt base voltages

\* Note:


The pu values of each component are based on the rating of each component.

\* +ve seq:

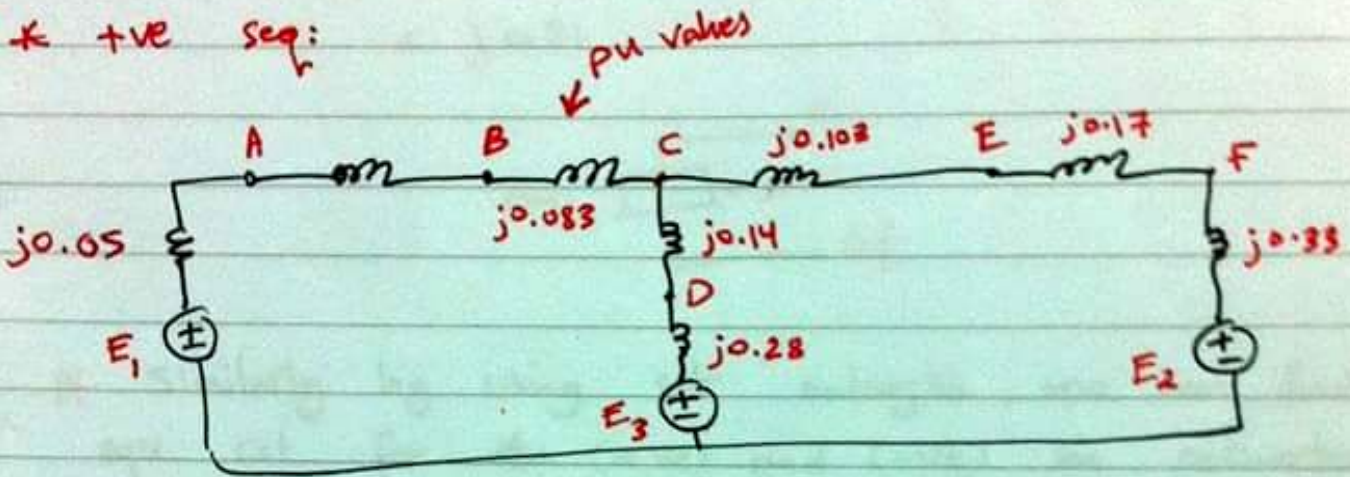


\* -ve sequence network is the same as +ve but with the sources replaced by ~~BE~~ S.C

\* Zero seq:

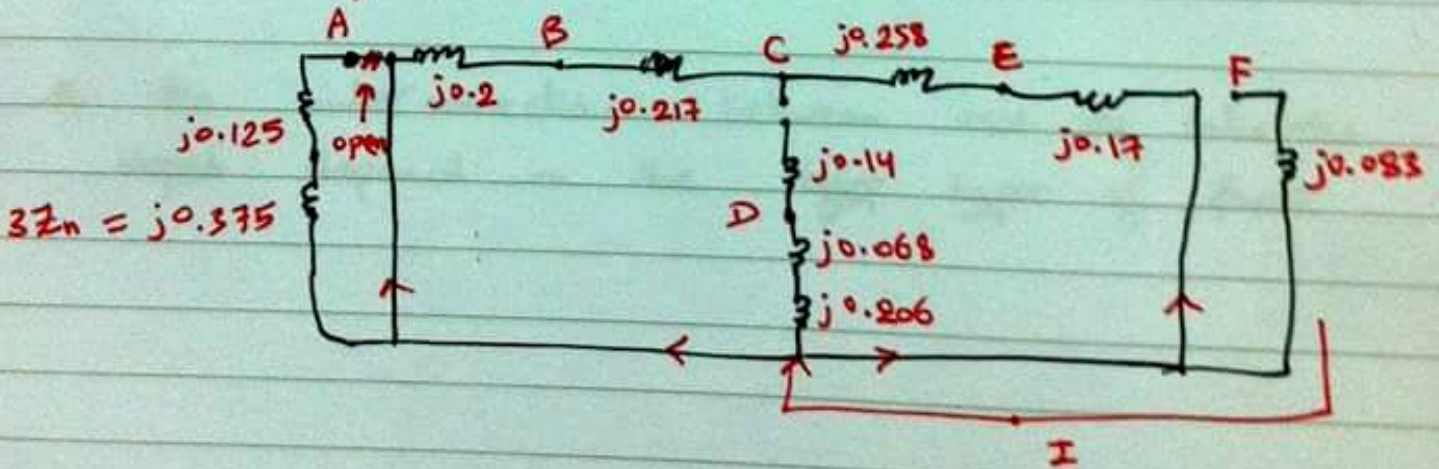


\* Comments:

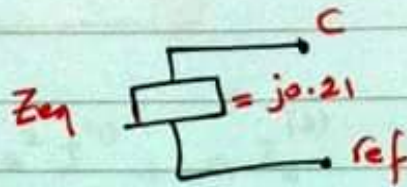i) for example: find  $Z_{eq}$  between C and the ref  
 $Z_{eq} = (j0.217 + j0.2) \parallel (j0.258 + j0.17)$   
 $= j0.21$



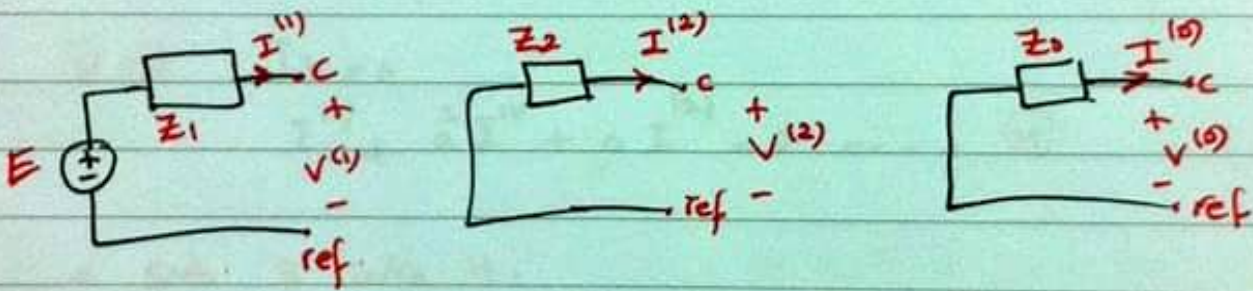\* Similarly by using ckt analysis, one can find equ. ckt. for ~~the~~ (+ve) and (-ve) seq networks




\* the interconnection between the seq. networks ~~depend~~ depend on the ~~type~~ type of fault

## \* Single line - to - ground fault

\* from fig (1):

$$I_b = I_c = 0 \quad \text{--- (1)}$$

$$V_a = I_a Z \quad \text{--- (2)}$$

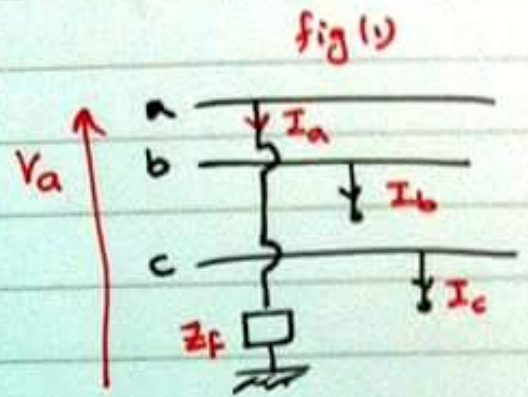

$$\textcircled{1} \Rightarrow I_a^{(0)} + a^2 I_a^{(1)} + a I_a^{(2)} = I_a^{(0)} + a I_a^{(1)} + a^2 I_a^{(2)}$$

 $Z_f = \text{fault imped.}$ 

$$\therefore I_a^{(1)} (a^2 - a) = I_a^{(2)} (-a + a^2)$$

$$\therefore I_a^{(1)} = I_a^{(2)} \quad \text{--- (3)}$$

$$\textcircled{1} \Rightarrow I_b = 0$$

$$I_a^{(0)} + a^2 I_a^{(1)} + a I_a^{(2)} = 0 \quad \text{--- (4)}$$

\* Sub 3 into 4:

$$I_a^{(0)} + I_a^{(1)} (a^2 + a) = 0$$

 $\downarrow -1, \text{ since } (1+a=0)$ 

$$\therefore I_a^{(0)} - I_a^{(1)} = 0$$


$$\boxed{I_a^{(0)} = I_a^{(1)} = I_a^{(2)}} \quad \text{--- (5)}$$

$$\textcircled{2} \Rightarrow V_a^{(0)} + V_a^{(1)} + V_a^{(2)} = Z_f (I_a^{(0)} + I_a^{(1)} + I_a^{(2)})$$

$$\boxed{V_a^{(0)} + V_a^{(1)} + V_a^{(2)} = 3 Z_f I_a^{(0)}} \quad \text{--- (6)}$$



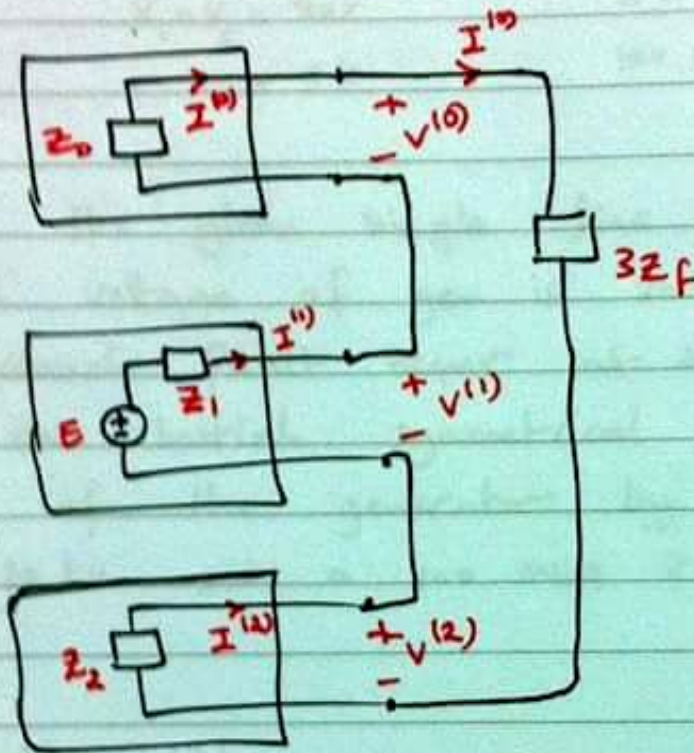\* Sequence networks should be connected in such way that (5) and (6) are satisfied:



$$\therefore I^{(0)} = I^{(1)} = I^{(2)} = \frac{E}{Z_0 + Z_1 + Z_2 + Z_f}$$

$$V^{(0)} = -I^{(0)} Z_0$$


$$V^{(1)} = E - I^{(1)} Z_1$$

$$V^{(2)} = -I^{(2)} Z_2$$

\* Having found  $[I_{abc}]$  and  $[V_{abc}]$  one can find

$$[I_{abc}] \text{ and } [V_{abc}]$$

\* e.g.:

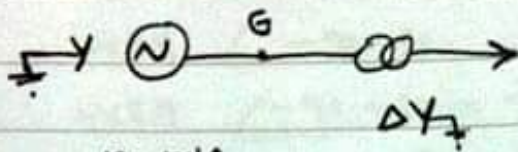

100 MVA  
20 kV  
 $X_1 = X_2 = 20\%$   
 $X_0 = 5\%$

$\Delta Y$   
(20  $\Delta$  / 230 Y) kV  
 $X = 10\%$   
100 MVA

\* for the given single line diagram, when the terminal voltage of gen is 20 kV, a single line to ground fault occur at the high voltage side,  
→ Find the initial symmetrical current and the phases of the generator by using phase values of 20 kV and a 100 MVA ?

\*  $I^{(0)} = I^{(1)} = I^{(2)} = I$


$$= \frac{1 \angle 0}{j0.2 + j0.1 + j0.2 + j0.1 + j0.1}$$

\* for the transformer:

$$I_{abc} = [A] [I_{012}]$$

$$= \begin{bmatrix} -4.287j \\ 0 \\ 0 \end{bmatrix}$$

↳

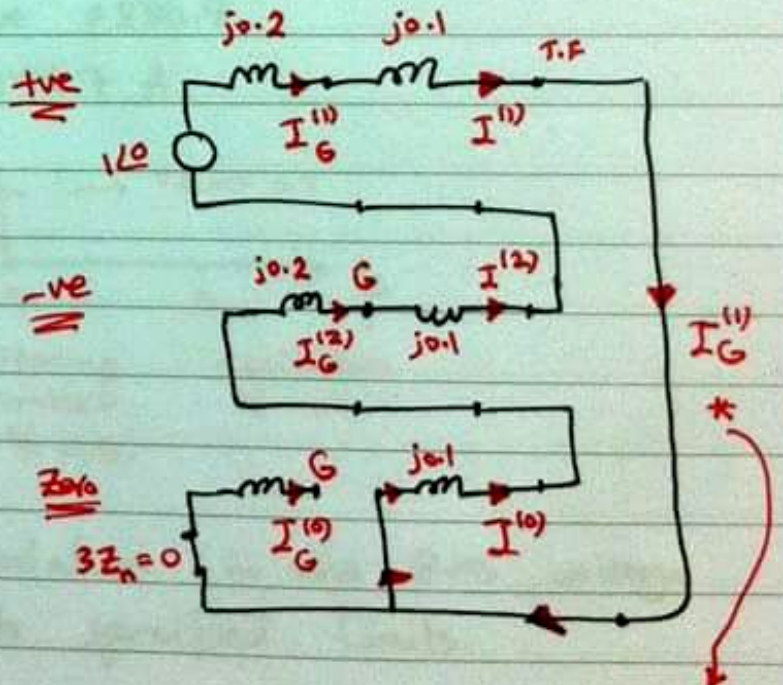

note here  
 $Z_f = 0$   
i.e. s/c  
direct to ground

$$I_G^{(1)} = 1.429 \angle -90 - 30$$

$$* I_G^{(2)} = 1.429 \angle -90 + 30 = -60$$


$$I_G^{(0)} = 0 \quad \text{because of the open circuit}$$

$$\rightarrow [I_{abc}]_G = [A] [I_{012}]_G = \begin{bmatrix} 2.475 \angle -90 \\ 2.475 \angle 90 \\ 0 \end{bmatrix}$$

\* Comments:


$$I_{base} = I_{rated} = \frac{100 \times 10^6}{\sqrt{3} \times 20 \times 10^3} = \boxed{2886.8} \text{ A}$$
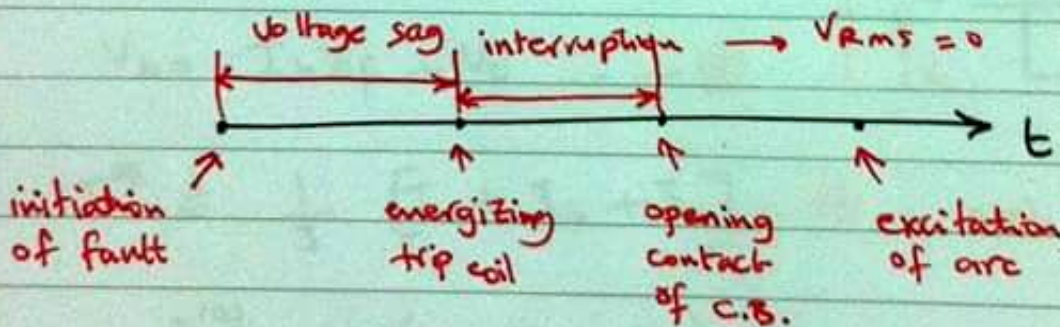
$$\therefore I_{fault} = 2.475 * 2886.8 \\ = 7144.7 \text{ A}$$



voltage sag: large variation in the RMS voltage outside its specified limits.

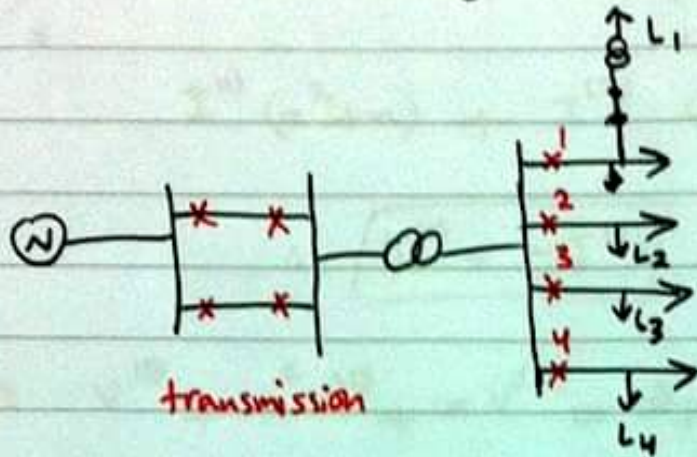\* in power system quality there are the problems of voltage sag and interruption which occur during SC faults.



features of radial system


distribution

\* line-to-line fault :

$$I_a = 0 \quad \text{--- (1)}$$

$$I_b = -I_c \quad \text{--- (2)}$$
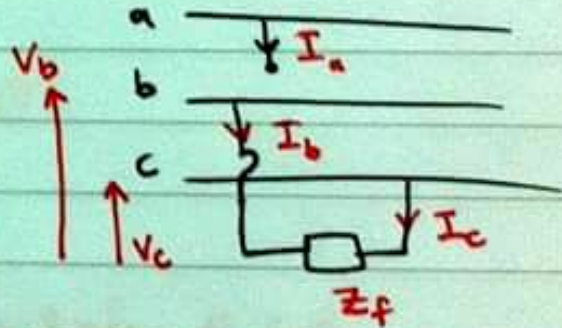
$$V_b = I_b Z_f + V_c \quad \text{--- (3)}$$



$$I^{(0)} \triangleq \frac{1}{3} [I_a + I_b + I_c] \quad \text{--- (4)}$$

sub 1, 2 into (4)

$$\rightarrow I^{(0)} = \frac{1}{3} (0 + I_b - I_b)$$

$$I^{(0)} = 0 \quad \text{--- (5)}$$

since,  $V^{(0)} \triangleq -I^{(0)} Z_0$

$$\therefore \boxed{V^{(0)} = 0}$$

\* Zero seq. network is isolated:

$$\textcircled{2} \Rightarrow \cancel{I^{(0)}} + a^2 I^{(1)} + a I^{(2)} = -(\cancel{I^{(0)}} + a I^{(1)} + a^2 I^{(2)})$$

$$I^{(1)}(a^2 + a) + I^{(2)}(a + a^2) = 0$$

$$\therefore \boxed{I^{(1)} = -I^{(2)}} \quad \text{--- (6)}$$

$$\textcircled{3} \Rightarrow V^{(0)} + a^2 V^{(1)} + a V^{(2)} = Z_f \left( I^{(0)} + a^2 I^{(1)} + a I^{(2)} \right) + (V^{(0)} + a V^{(1)} + a^2 V^{(2)})$$

$$V^{(1)}(a^2 - a) - V^{(2)}(a^2 - a) = Z_f (a^2 I^{(1)} - a I^{(1)}) \\ = Z_f I^{(1)} (a^2 - a)$$

$$\boxed{V^{(1)} - V^{(2)} = Z_f I^{(1)}} \quad \text{--- (7)}$$

\* connect seq. networks to satisfy 5, 6, 7

# second.




# Power 1 Notebook



**DR. DAIFALLAH DALBEEH**

**BY : SAUSAN ALMOHTASEB**

↳ L-L fault:

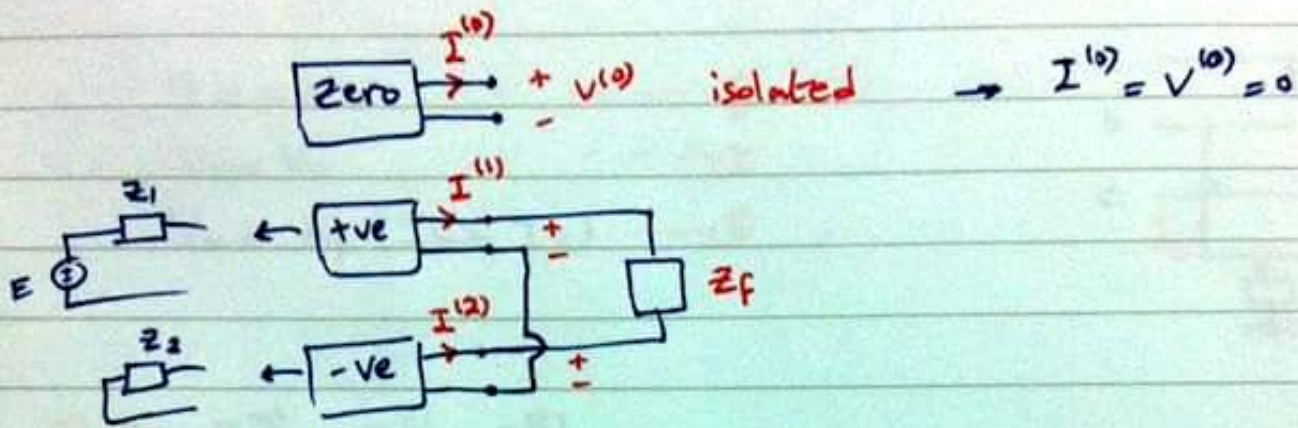

Ex: solve the previous example by assuming L-L fault:

$$I^{(1)} = -I^{(2)} = \frac{E}{Z_1 + Z_2 + Z_f}$$

$$V_1 = E - I^{(1)} Z_1$$


$$V_2 = -I^{(2)} Z_2$$

\* line - line - ground fault:

$$\therefore I_a = 0 \quad \text{--- (1)}$$

$$V_b = V_c \quad \text{--- (2)}$$
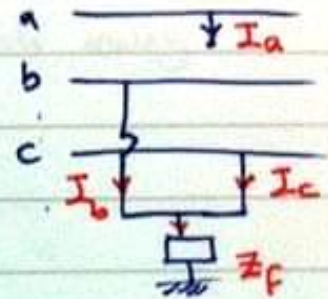
$$V_b = Z_f (I_b + I_c) \quad \text{--- (3)}$$



$$\textcircled{1} \Rightarrow I^{(0)} + I^{(1)} + I^{(2)} = 0$$

$$I^{(0)} = -(I^{(1)} + I^{(2)}) \quad \text{--- (4)}$$

$$\textcircled{2} \Rightarrow V^{(0)} + a^2 V^{(1)} + a V^{(2)} = V^{(0)} + a V^{(1)} + a^2 V^{(2)}$$

$$V^{(1)} (a^2 - a) = V^{(2)} (a^2 - a)$$

$$\therefore V^{(1)} = V^{(2)} \quad \text{--- (5)}$$

$$\textcircled{3} \Rightarrow V^{(0)} + a^2 V^{(1)} + a V^{(2)} = Z_f (I^{(0)} + a^2 I^{(1)} + a I^{(2)} + I^{(0)} + a I^{(1)} + a^2 I^{(2)})$$

~~$$V^{(0)} + a^2 V^{(1)} + a V^{(2)} = Z_f (2I^{(0)} + a^2 I^{(1)} + a I^{(2)} + I^{(0)} + a I^{(1)} + a^2 I^{(2)})$$~~

$$\rightarrow V^{(0)} + V^{(1)} (a^2 + a) = Z_f (2I^{(0)} + I^{(1)} (a^2 + a) + I^{(2)} (a^2 + a))$$

$$\therefore (V^{(0)} - V^{(1)}) = Z_f (2I^{(0)} - I^{(1)} - I^{(2)})$$

$$\therefore = Z_f (2I^{(0)} - (I^{(1)} + I^{(2)}))$$


since  $(a^2 + a = -1)$

$$= 3 Z_f I^{(0)}$$



$$\therefore \boxed{V^{(0)} - V^{(1)} = 3Z_f I^{(0)}} \quad \text{--- (6)}$$

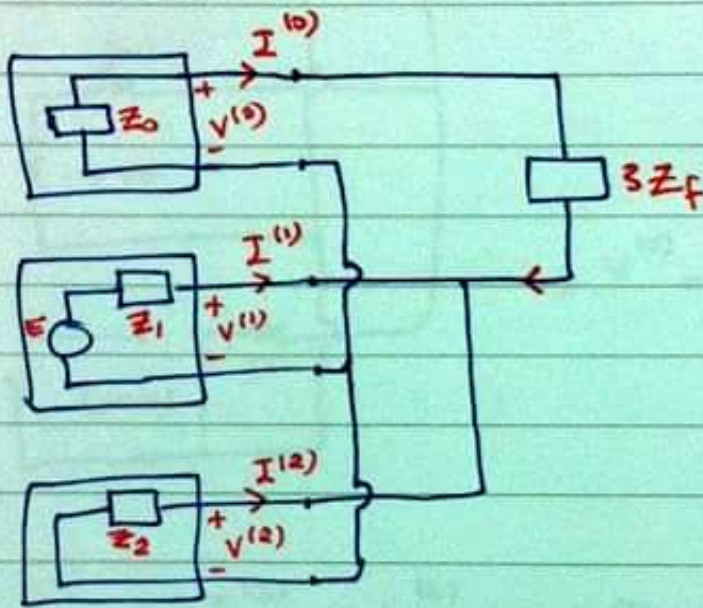\* connect the sequence ckt's in such away to satisfy 3, 5, 6 :



$$\rightarrow I^{(1)} = \frac{E}{Z_1 + ((Z_0 + 3Z_f) \parallel Z_2)}$$

$$\rightarrow I^{(0)} = -I^{(1)} \frac{Z_0}{Z_2 + (Z_0 + 3Z_f)}$$


$$\rightarrow I^{(0)} = -(I_1 + I_2)$$

$$\rightarrow V^{(0)} = -I^{(0)} Z_0$$

$$\rightarrow V^{(1)} = E - I^{(1)} Z_1$$

$$\rightarrow V^{(2)} = -I^{(2)} Z_2$$

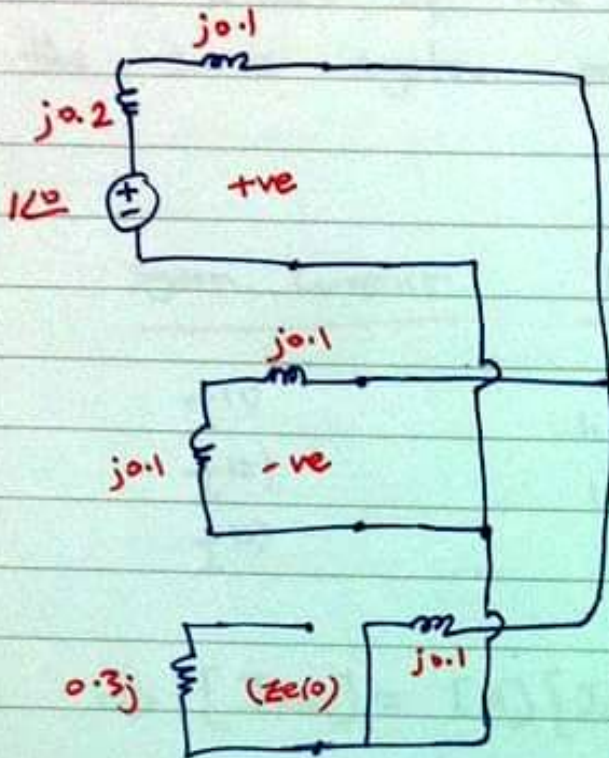\* e.g.: Solve the previous e.g for L-L-G fault:



\* by sub:

$$\rightarrow I^{(1)} = \frac{1\angle 0}{j0.3 + (j0.3 \parallel j0.1)}$$

$$= 2.67 \angle -90^\circ$$

$$\rightarrow V^{(0)} = V^{(2)} = V^{(1)} = E - I_1 Z_1$$

$$= 1\angle 0 - (2.67 \angle -90^\circ)(j0.03)$$

$$= 0.2$$

$$\rightarrow \therefore I^{(2)} = \frac{-V^{(2)}}{Z_2} = 0.67 \angle 90^\circ$$

$$\rightarrow I^{(0)} = \frac{-V^{(0)}}{Z^{(0)}} = j2 = 2 \angle 90^\circ$$

\* for the Generator:

$$I_g^{(1)} = 2.67 \angle -90 - 30 = -120$$

$$I_g^{(2)} = 0.67 \angle 90 + 30 = 120$$

$$I_g^{(0)} = 0$$

$$\Rightarrow [I_{abc}] = [A][I_{one}] \dots$$

## \* Summary:

The results of the three types of faults for the same system are as follows:

* <u>Symm. current</u>	<u>L-G</u>	<u>L-L</u>	<u>L-L-G</u>
$I^{(1)}$	$1.429 \angle -120$	$1.67 \angle -120$	$2.67 \angle -120$
$I^{(2)}$	$1.429 \angle -60$	$1.67 \angle -60$	$0.67 \angle 120$
$I^{(0)}$	0	0	0

$$\Rightarrow [I_{abc}] = [A] [I_{012}] \quad \text{for each.}$$

\* Having performed fault analysis, which value of fault current is used to set the setting of protection system component. (search)

## \* Load flow or power flow:

what? : definition: load flow is the calculation of the voltages of the busbars at a given power system for a given load condition.


\* having found voltages, one can find other quantities:

- 1) current in the lines
- 2) power flow in the power sys. components
- 3) losses in the system.

why? objective: load flow analysis is used in the planning, design, and operation of power sys.

How? Mathematical formulation of the load flow problem:

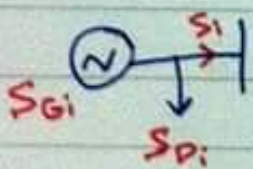\* consider a given busbar say the  $i^{\text{th}}$  busbar



$S_{Gi}$  = complex generated power at the  $i^{\text{th}}$  busbar

$S_{Di}$  = demand power at the  $i^{\text{th}}$  busbar (i.e.: load)

$S_i$  = complex power entering the  $i^{\text{th}}$  busbar

\* let:  $V_i =$  voltage at the  $i^{\text{th}}$  busbar  
 $\therefore V_i = |V_i| \angle \delta_i$  --- (1)

\* by using the concept of bus admittance matrix

$$[I] = [Y][V]$$

$$I_i = \sum_{j=1}^N Y_{ij} V_j \text{ --- (2)}$$

$\left\{ \begin{array}{l} I_i = \text{current entering the busbar} \\ N = \text{No. of busbars} \end{array} \right.$

\* let:  $Y_{ij} = |Y_{ij}| \angle \theta_{ij}$  --- (3)

$$\text{Now; } S_i \triangleq V_i I_i^* \text{ --- (4)}$$

\* sub 1, 2, 3 into 4:

$$S_i = |V_i| \angle \delta_i \left( \sum_{j=1}^N Y_{ij} \angle \theta_{ij} * |V_j| \angle \delta_j \right)^*$$

$$= |V_i| \angle \delta_i \sum_{j=1}^N |Y_{ij}| |V_j| \angle (-\delta_j - \theta_{ij})$$

$$= \sum_{j=1}^N N_i |V_j| |Y_{ij}| \angle (\delta_i - \delta_j - \theta_{ij})$$

since:  $S_i = P_i + Q_i$


$$\therefore \underline{P_i} = \sum_{j=1}^N N_i |V_j| |Y_{ij}| \cos (\delta_i - \delta_j - \theta_{ij}) \text{ --- (5)}$$

$$\underline{Q_i} = \sum_{j=1}^N |V_j| |Y_{ij}| \sin (\delta_i - \delta_j - \theta_{ij}) \text{ --- (6)}$$

## \* Comments:

- 1) equations 5, 6 are called (power flow equations)
- 2) if the voltages are known then  $(P_i)$  and  $(Q_i)$  can be calculated, i.e.:  $P_{i, cal}$   
 $Q_{i, cal}$

Ch9:

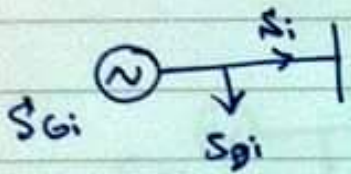

if  $P_{Gi} = \text{scheduled gen. power}$   
 $P_{Di} = \text{load}$

$$\left. \begin{aligned} P_{sch} &= P_{Gi} - P_{Di} \\ Q_{sch} &= Q_{Gi} - Q_{Di} \end{aligned} \right\}$$

\* Hence in the process of load flow solution  
 $P_{cal} \neq P_{sch}$  and  $Q_{cal} \neq Q_{sch}$

\* one may say that there is a power mismatch:  
 $\Delta P_i = P_{sch, i} - P_{cal, i}$   
 $\Delta Q_i = Q_{sch, i} - Q_{cal, i}$


⇒ Therefore a solution is obtained when  $\Delta P_i$   
and  $\Delta Q_i = 0$ , Hence one may say that  
a power balance is obtained. Consequently there are  
2 functions to be satisfied.

$$g_i = P_{sch} - P_{cal} = (P_{Gi} - P_{Di}) - P_{cal} = 0$$

$$g_i'' = Q_{sch} - Q_{cal} = (Q_{Gi} - Q_{Di}) - Q_{cal} = 0$$

→ In the 2 equations of the power flow, there are 4 unknowns:  $P_i$ ,  $Q_i$ ,  $|V_i|$ ,  $\delta_i$

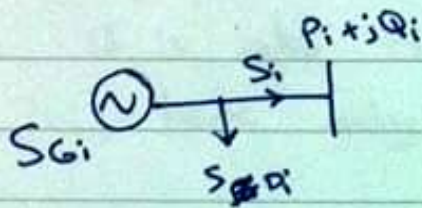\* Hence to overcome this problem, one has to specify values for 2 unknowns and calculate values for other 2.



→ therefore, in practice 3 types of busbars are specified as follows:

i) **load bus**: this is a **non-generator bus**, Hence  $P_{Gi} = Q_{Gi} = 0$   $\therefore$  (unknowns  $\rightarrow |V_i|, \delta_i$ )

since load on the bus can be estimated by load forecast or historical data or measurement. This is usually for  $P_D$ , hence by assuming certain power factor for eg: 0.85, then  $Q_D$  can be found:

$$Q_D = P_D \tan \theta$$

$\theta = \text{P.F. (angle)}$

$$\therefore Q_{i, \text{sch}} = 0 - Q_{Di} \quad \therefore P_{i, \text{sch}} = 0 - P_{Di}$$

hence this bus is also called **PQ-bus**

$\therefore$  at this bus  $\Delta P_i$  and  $\Delta Q_i$  are to be satisfied.

ii) **voltage controlled bus**: this is usually has a generator by means of its prime mover, one can control ( $P_i$ ), and by means of its excitation  $\rightarrow$  one can control  $|V_i|$

$\therefore$  at this busbar ( $P_i$ ) and  $|V_i|$  are specified here ( $Q_i$ ) will be calculated when the load flow is complete  $\therefore$  the unknowns here is  $\delta_i$   
it is also called **PV-bus**  
 $\rightarrow$  here only  $\Delta P_i = 0$  to be satisfied

iii) **reference or slack busbar**: as a convention busbar #1 is taken as a slack, here  $\delta_1$  is ~~satisfied~~ specified, and taken as the convention  $= 0^\circ$ .

Here ( $P_i$ ) and ( $Q_i$ ) can't be satisfied in advance, as will be explained later.

$\rightarrow$  Therefore, no need to satisfy ( $\Delta P = 0$ ) and ( $\Delta Q = 0$ ), at each busbar:  $P_i \triangleq P_{G_i} - P_{D_i}$   
for the total number of busbars  $= N$   
there are  $N$  equations like (1)

$\therefore$  Summating these equations:

$$\sum_{i=1}^N P_i = \sum_{i=1}^N P_{G_i} - \sum_{i=1}^N P_{D_i} = P_{\text{losses}}$$

$\leftarrow$  total generation
 $\leftarrow$  total demand or load

$\rightarrow$



$$\Rightarrow \sum_{i=1}^N P_i = \sum_{i=1}^N P_{Gi} - \sum_{i=1}^N P_{Di} = P_{\text{losses}}$$

$$\Rightarrow P_{\text{losses}} = \sum 3 |I|^2 R$$

this should be supplied the slack bus

$$* \text{ Similarly: } \sum Q_i = \sum Q_{Gi} - \sum Q_{Di} = Q_{\text{losses}} \quad (\text{reactive power loss})$$

$$* \text{ for the slack bus: } S_1 = P_{\text{loss}} + jQ_{\text{loss}}$$

### \* Conclusion :

The unknown in the load flow problem are called state or dependent variables.

Hence the number of state variables determine the number of equations to be solve as illustrated by table (9.1)

study.

$$\rightarrow i=1$$

$$\rightarrow i=2 \dots, N_g+1$$

$$\rightarrow i=N_g+2 \dots, N$$

$$\text{equations} = 2N - N_g - 2$$

$$N=10 \rightarrow 20 - 3 - 2 = 15 \text{ equations}$$

$$N_g=3$$

## \* Gauss - seidel method :

This method is based on the power flow equations as follows :

$$S_i = V_i I_i^*$$

$$S_i^* = V_i^* I_i$$

to simplify, let the system has 4 busbars with bus 1 is taken as a slack.

$$\begin{aligned} * \text{ bus 2 } \rightarrow S_2^* &= V_2^* I_2 \\ P_2 - jQ_2 &= V_2^* \left( \sum_{j=1}^4 Y_{ij} V_j \right) \\ &= V_2^* (Y_{21} V_1 + Y_{22} V_2 + Y_{23} V_3 + Y_{24} V_4) \end{aligned}$$

$$\therefore V_2 = \frac{1}{Y_{22}} \left( \frac{P_2 - jQ_2}{V_2^*} - (Y_{21} V_1 + Y_{23} V_3 + Y_{24} V_4) \right) \dots \textcircled{1}$$

\* Similarly one can write equations for  $V_3$  and  $V_4$  as:

$$V_3 = \frac{1}{Y_{33}} \left( \frac{P_3 - jQ_3}{V_3^*} - (Y_{31} V_1 + Y_{32} V_2 + Y_{34} V_4) \right) \dots \textcircled{2}$$

$$V_4 = \frac{1}{Y_{44}} \left( \frac{P_4 - jQ_4}{V_4^*} - (Y_{41} V_1 + Y_{42} V_2 + Y_{43} V_3) \right) \dots \textcircled{3}$$

→ here it is assumed that 2, 3, 4 are PQ buses

## \* Procedure :

- i) on the RHS of 2, 3, 4 one substitute the assumed solution and specified values
- ii) initially one assume solutions for the unknowns  $V_2^{(0)}$ ,  $V_3^{(0)}$ ,  $V_4^{(0)}$  usually  $V_2^{(0)} = V_3^{(0)} = V_4^{(0)} = 1 \angle 0^\circ$  this is called: flat start.
- iii) always use most recent values

$\Rightarrow$   $V_2^{(1)} = \frac{1}{Y_{22}} \left( \frac{P_2 - jQ_2}{V_2^{(0)*}} - (Y_{21} V_1 + Y_{23} V_3^{(0)} + Y_{24} V_4^{(0)}) \right)$

↑  
specified  $V_1 = 1 \angle 0^\circ$

$$V_3^{(1)} = \frac{1}{Y_{33}} \left( \frac{P_3 - jQ_3}{V_3^{(0)*}} - (Y_{31} V_1 + Y_{32} V_2^{(1)} + Y_{34} V_4^{(0)}) \right)$$

$$V_4^{(1)} = \frac{1}{Y_{44}} \left( \frac{P_4 - jQ_4}{V_4^{(0)*}} - (Y_{41} V_1 + Y_{42} V_2^{(1)} + Y_{43} V_3^{(1)}) \right)$$

$\therefore$  1<sup>st</sup> iteration is completed ✓

\* Check that for all buses  $|V_i^{(k)} - V_i^{(k-1)}| \leq \epsilon$   
 where  $\epsilon$  is certain specified tolerance, e.g.: ( $\epsilon = 10^{-6}$ )


→ if Yes → solution is obtained  
 No → go to next iteration

\* The general defining equation is:

$$V_i^{(k)} = \frac{1}{Y_{ii}} \left( \frac{P_i - jQ_i}{V_i^{(k-1)*}} - \sum_{j=1}^{i-1} Y_{ij} V_j^{(k)} - \sum_{j=i+1}^N Y_{ij} V_j^{(k-1)} \right)$$

(k: # of iteration)

\* e.g 9.2: (p 337):

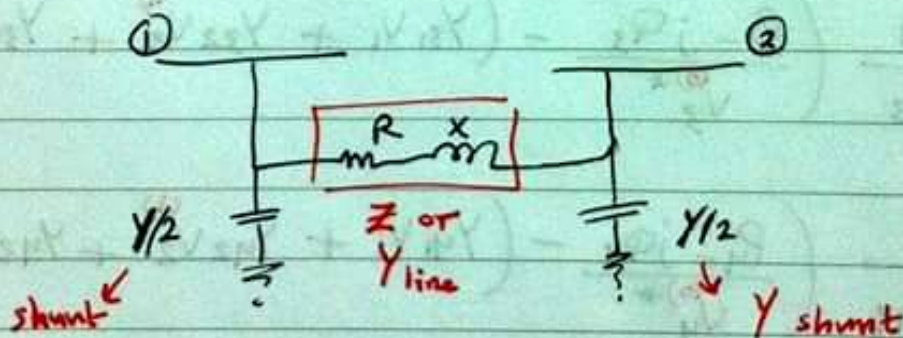

→

$$\rightarrow L_{12} \rightarrow Z = 0.01008 + j 0.05040 = 0.05 \angle 78.69$$

$$\rightarrow Y_{\text{line}} = G + j\beta = \frac{1}{Z} = \frac{1}{0.05 \angle 78.69}$$

$$= 3.815629 - j 19.078144$$

\* total charging MVAR is related to shunt capacitors of the line :

$$\rightarrow V_{\text{AR total}} = 3 V_p I_p = 3 V_p (V_p W_c) = 3 V_p^2 W_c = 3 V_p^2 Y_{\text{shunt}}$$

↑  
phase quantity

$$\therefore Y_{\text{sh}} = \frac{\text{VAR (total)}}{3 V_p^2} = \frac{10.25 \times 10^6}{3 \left( \frac{230 \times 10^3}{\sqrt{3}} \right)^2} = \frac{10.25}{(230)^2} \text{ (S)}$$

$$\rightarrow Y_{\text{sh (b)}} = \frac{1}{Z_b} = \frac{S_b}{V_b^2} = \frac{100}{(230)^2}$$

$$\rightarrow Y_{\text{sh (pu)}} = \frac{10.25}{(230)^2} \div \frac{100}{(230)^2} = \frac{10.25}{100} = 0.1025$$


$$\Rightarrow \frac{Y_{\text{sh}}}{2} = \frac{0.1025}{2} = \boxed{0.05125}$$

\* Here it is assumed that each load has a power factor:  $pf = 0.85$  lagging

→ Bus 1  
 $P_L = 50$

$$Q_L = P_L \tan \theta = 50 \tan(\cos^{-1}(0.85)) = 30.99$$

\* flow chart:

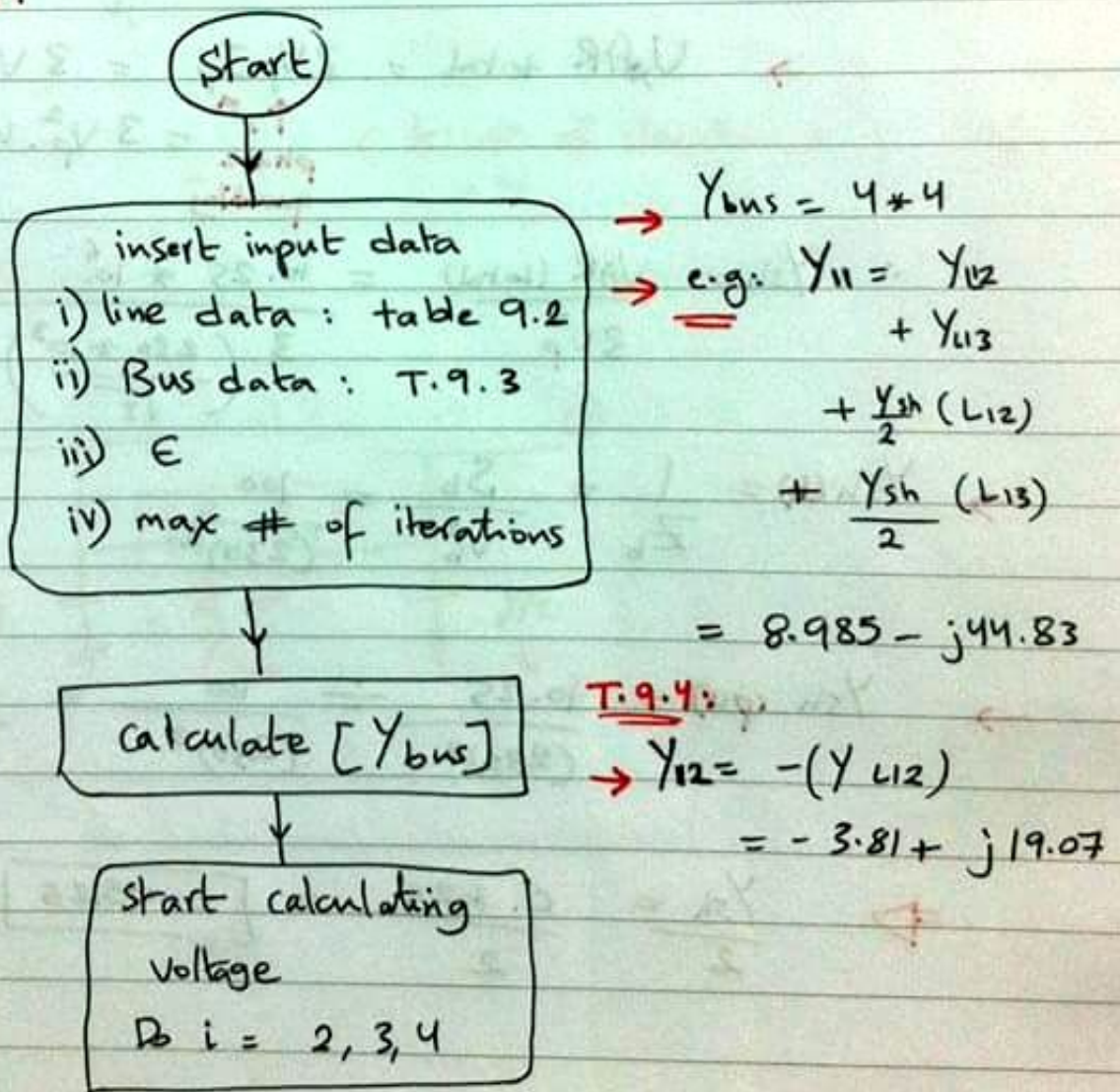

$$\# V_2^{(1)} = \frac{1}{Y_{22}} \left( \frac{P_{2, sch} - Q_{2, sch}}{V_2^{(0)}} - (Y_{21}V_1 + \overset{\substack{\uparrow \\ =0 \\ \text{(no line)}}}{Y_{23}V_3^{(0)} + Y_{24}V_4^{(0)}}} \right)$$

(page 339)

- $P_{2, sch} = P_{2, gen} - P_{2, load} = -P_{2, load} = -1.7$
  - $Q_{2, sch} = Q_{2, gen} - Q_{2, load} = -Q_{2, load} = 1.0535$
  - $V_2^{(0)} = 1 \angle 0$
  - $V_1$  (slack bus) =  $1 \angle 0$
  - $V_3^{(0)}$  (flat start) =  $1 \angle 0$
  - $V_4 = |V_4| \angle 0^\circ = 1.02 \angle 0$
- $\uparrow$  specified       $\uparrow$  flat start

# by substitution:

$$V_2^{(1)} = 0.983564 - j0.032316$$

in order to accelerate the process of convergence, then the calculated value of  $V_2^{(1)}$  has to be modified as follows:

$$\# \text{ of iteration} \rightarrow (k) \quad \Rightarrow V_{i, acc}^{(k)} = V_{i, acc}^{(k-1)} + \alpha (V_i - V_{i, acc}^{(k-1)}) \quad \text{--- (9.21) book}$$

$$1 < \alpha < 2$$

$$\text{usually: } \alpha = 1.6$$

$$\Rightarrow V_{2,acc}^{(1)} = V_{2,acc}^{(0)} + 1.6 \left( V_2^{(1)} - V_{2,acc}^{(0)} \right)$$

$\uparrow$  (0)  $\uparrow$  calculated

(page: 340):

$$= 1\angle 0 + 1.6 \left( V_2^{(1)} - V_{2,acc}^{(0)} \right)$$

$\uparrow$  calculated

$$= 1\angle 0 + 1.6 \left[ (0.98 - j0.03) - 1\angle 0 \right]$$

$$V_{2,acc}^{(1)} = 0.97 - j0.05$$

\* Next, apply the same procedure for bus 3 to find  $V_3^{(1)}$  (use  $V_{2,acc}^{(1)}$ ), then find  $V_{3,acc}^{(1)}$


\* Next evaluate  $V_4^{(1)}$

$\Rightarrow$  the 1<sup>st</sup> thing evaluate  $Q_4^{(1)}$  why??

\* for any 3-phase synch. generator, it has the following characteristics:

constraints  $\Rightarrow P_{min} \leq P \leq P_{max}$

$$Q_{min} \leq Q \leq Q_{max}$$

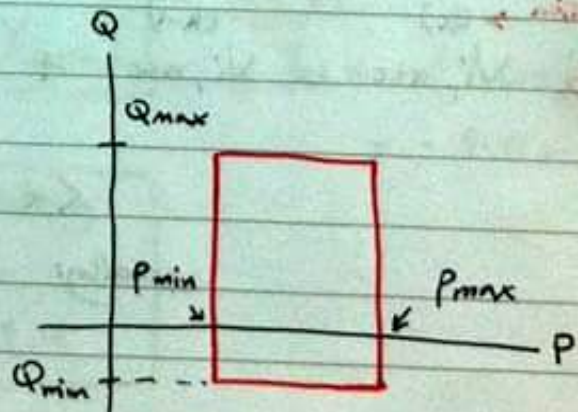



→ But for PV-bus:  $|P|$  is specified, and one can specify a value within its limit

→ How?

$$S_i = V_i I_i^*$$

$$S_i^* = V_i^* I_i$$

$$\therefore P_i - jQ_i = V_i^* I_i$$

$$\therefore Q_i = - * \operatorname{Im} [V_i^* I_i]$$

↳ imaginary

$$\therefore Q_i = - * \operatorname{Im} \left[ V_i^* \sum_{j=1}^N Y_{ij} V_j \right]$$

\* in our example:  $i=4$ ,  $N=4$ ,  $k=1$   
busbars

$$\rightarrow Q_4^{(1)} = - * \operatorname{Im} \left\{ V_4^{(0)*} \left[ Y_{41} V_1 + Y_{42} V_{2,acc}^{(1)} + Y_{43} V_{3,acc}^{(1)} + Y_{44} V_4^{(0)} \right] \right\}$$

$$= 1.654151$$

\* check that:  $Q_{4,min} < Q_4^{(1)} < Q_{4,max}$

→ if Yes: go and calculate  $V_4^{(1)}$  by using the same equation for PQ-buses, using  $Q_4^{(1),sch}$

$$\Rightarrow V_4^{(1)} = |V_4^{(1)}| \angle V_4^{(1)}$$

\* Next multiply  $V_4^{(1)}$  by the factor:  $\frac{|V_4|_{\text{specified}}}{|V_4^{(1)}|}$

$$\rightarrow V_4^{(1)} (\text{modified}) = |V_4^{(1)}| \angle V_4^{(1)} * \frac{|V_4|_{\text{specified}}}{|V_4^{(1)}|}$$

$$\rightarrow \boxed{V_4^{(1)} (\text{modified}) = |V_4|_{\text{specified}} \angle V_4^{(1)}}$$

$\rightarrow$  if No: then set  $Q_4$  at the violated limit,  
 i.e.:  $Q_4 = Q_{4 \text{ max}}$ , if  $Q_4^{(1)} > Q_{4 \text{ max}}$   
 $= Q_{4 \text{ min}}$  if  $Q_4^{(1)} < Q_{4 \text{ min}}$

$\rightarrow$  and since now  $P_4$  and  $Q_4$  are specified then convert busbar 4 from PV-bus to PQ-bus and calculate  $V_4^{(1)}$ , using the same equation of PQ-buses

$\rightarrow$  next, check that  $(|V_i^{(k)} - V_i^{(k-1)}| \leq \epsilon)$  for All buses  
 certain specified tolerance

if Yes: solution is obtained

if No: go to next iteration

\* to find  $V_2^{(2)}, V_3^{(2)}, V_4^{(2)} \rightarrow$  1<sup>st</sup> check  $Q_4$  if within limits  $\rightarrow$  Reinstate bus 4 in PV bus keep  $|V_4| = |V_4|_{\text{specif.}}$

## \* Newton Raphson method, for power-flow solution.

This method is based on the Taylor's series expansion of the function with 2 or more variables

### \* procedure :

- i) mathematical concept
- ii) its application to load flow

### \* Mathematical concept :

let the function:  $h_1(x_1, x_2, u) = b_1$  ----- (1)

and let the function:  $h_2(x_1, x_2, u) = b_2$  ----- (2)

$x_1, x_2 =$  variables or unknowns to be found

$u =$  is called independent control variable

$b_1 =$  constant represent specified value of  $\underline{h_1}$

$b_2 =$  = = = = =  $\underline{h_2}$

→ Since  $x_1$  and  $x_2$  will be evaluated by iterative techniques, then the following function:

$(g_1)$  and  $(g_2)$  are introduced as follows:

$$g_1(x_1, x_2, u) = h_1(x_1, x_2, u) - b_1 = 0 \text{ ----- (3)}$$

$$g_2(x_1, x_2, u) = h_2(x_1, x_2, u) - b_2 = 0 \text{ ----- (4)}$$

→  $g_1, g_2$  represent mismatch or difference between calculated and specified values.

2  
 → let  $x_1^{(0)}$  and  $x_2^{(0)}$  be the initial estimates of  $x_1$  and  $x_2$ .

→ if the actual solution is  $x_1^*$  and  $x_2^*$ , then a correction has to be ~~found~~ made to  $x_1^{(0)}$  and  $x_2^{(0)}$  to get the required answer; hence:

$$g_1(x_1^*, x_2^*, u) = g_1(x_1^{(0)} + \Delta x_1^{(0)}, x_2^{(0)} + \Delta x_2^{(0)}, u) \quad \text{--- (5)}$$

$$g_2(x_1^*, x_2^*, u) = g_2(x_1^{(0)} + \Delta x_1^{(0)}, x_2^{(0)} + \Delta x_2^{(0)}, u) \quad \text{--- (6)}$$

→ the objective now is to evaluate  $\Delta x_1^{(0)}$  and  $\Delta x_2^{(0)}$

→ this can be achieved by the Taylor's expansion about the assumed solution as follows:

$$\therefore g_1(x_1^*, x_2^*, u) = g_1(x_1^{(0)}, x_2^{(0)}, u) + \Delta x_1^{(0)} \left. \frac{dg_1}{dx_1} \right|^{(0)} + \Delta x_2^{(0)} \left. \frac{dg_1}{dx_2} \right|^{(0)} + \dots = 0$$

$$g_2(x_1^*, x_2^*, u) = g_2(x_1^{(0)}, x_2^{(0)}, u) + \Delta x_1^{(0)} \left. \frac{dg_2}{dx_1} \right|^{(0)} + \Delta x_2^{(0)} \left. \frac{dg_2}{dx_2} \right|^{(0)} + \dots = 0 \quad \text{--- (7)}$$

→ the partial derivative of  $g_2$  is evaluated at  $x_1^{(0)}$  and  $x_2^{(0)}$

the same thing for other partial derivative

the

→ Here in (7) and (8) the higher partial derivatives are neglected.

→ rewrite 7, 8 in a matrix form as:

$$\begin{bmatrix} \frac{dg_1}{dx_1} & \frac{dg_1}{dx_2} \\ \frac{dg_2}{dx_1} & \frac{dg_2}{dx_2} \end{bmatrix}^{(0)} \begin{bmatrix} \Delta X_1^{(0)} \\ \Delta X_2^{(0)} \end{bmatrix} = \begin{bmatrix} -g_1(x_1^{(0)}, x_2^{(0)}, u) \\ -g_2(x_1^{(0)}, x_2^{(0)}, u) \end{bmatrix} \quad \text{--- (9)}$$

→ called: Jacobian matrix:  $J^{(0)}$

$$\therefore J^{(0)} \begin{bmatrix} \Delta X_1^{(0)} \\ \Delta X_2^{(0)} \end{bmatrix} = \begin{bmatrix} -g_1(x_1^{(0)}, x_2^{(0)}, u) = b_1 - h_1(x_1^{(0)}, x_2^{(0)}, u) = \Delta g_1^{(0)} \\ -g_2(x_1^{(0)}, x_2^{(0)}, u) = b_2 - h_2(x_1^{(0)}, x_2^{(0)}, u) = \Delta g_2^{(0)} \end{bmatrix}$$

$$\therefore \begin{bmatrix} \Delta X_1^{(0)} \\ \Delta X_2^{(0)} \end{bmatrix} = [J^{(0)}]^{-1} \begin{bmatrix} \Delta g_1^{(0)} \\ \Delta g_2^{(0)} \end{bmatrix} \quad \text{--- (10)}$$

i) since the RHS of (10) is known, then  $\Delta X_1^{(0)}$  and  $\Delta X_2^{(0)}$  can be calculated

ii) find new values:  $X_1^{(1)} = X_1^{(0)} + \Delta X_1^{(0)}$

$X_2^{(1)} = X_2^{(0)} + \Delta X_2^{(0)}$

iii) repeat the same procedure to find new correction


$\Delta X_1^{(1)}$  and  $\Delta X_2^{(1)}$

iv) the process terminates when  $|\Delta X_1^{(k)}|$  and  $|\Delta X_2^{(k)}| \leq \epsilon$

where:  $\epsilon$  is certain specified tolerance

see:

\* Ex (9.4), page (344):

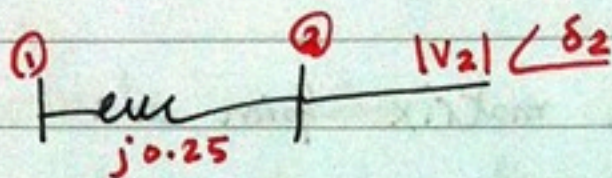

$$P_i = \sum_{j=1}^N |V_i| |V_j| |Y_{ij}| \cos(\delta_i - \delta_j - \theta_{ij})$$

$$Q_i = \dots \dots \dots \sin(\dots)$$

here:  $N=2$ ,  $i=2$ 

\* Application of mathematical concept to load flow problem:

The starting point is the complex power ( $S_i = P_i + jQ_i$ ) which is entering the  $i^{\text{th}}$  bus

$$\rightarrow P_i = \sum_{j=1}^N (|V_i| |V_j| |Y_{ij}| \cos(\delta_i - \delta_j - \theta_{ij}))$$

$$|V_i|^2 \underbrace{(|Y_{ii}| \cos \theta_{ii})}_{G_{ii}} + \sum_{\substack{j=1 \\ j \neq i}}^N (\dots)$$

note:  $Y_{ij} = |Y_{ij}| \angle \theta_{ij}$

$$= |Y_{ij}| \underbrace{\cos \theta_{ij}}_{G_{ij}} + j |Y_{ij}| \underbrace{\sin \theta_{ij}}_{B_{ij}}$$

$$\rightarrow Q_i = \sum_{j=1}^N \dots \dots \dots \sin(\delta_i - \delta_j - \theta_{ij}) = |V_i|^2 B_{ij} + \sum_{\substack{j=1 \\ j \neq i}}^N \dots$$

$\therefore$  ① and ② can be used to find the partial derivatives of  $P_i$  and  $Q_i$  with respect to  $|V_i|$  and  $\delta_i$

$$\Delta P_i = P_{i,sch} - P_{i,cal} \text{ --- (3)}$$

$$\Delta Q_i = Q_{i,sch} - Q_{i,cal} \text{ --- (4)}$$

\* assume the system has 4 buses, whose bus #1 is slack, and assume that the remaining 3 are PQ or load buses.

\* the state variables are:  $|V_2|, |V_3|, |V_4|, \delta_2, \delta_3, \delta_4$

\* the mismatch equations will be:

$$\begin{aligned} \Delta P_i = & \frac{\partial P_i}{\partial \delta_2} \cdot \Delta \delta_2 + \frac{\partial P_i}{\partial \delta_3} \cdot \Delta \delta_3 + \frac{\partial P_i}{\partial \delta_4} \cdot \Delta \delta_4 + |V_2| \frac{\partial P_i}{\partial |V_2|} \cdot \frac{\Delta V_2}{|V_2|} \\ & + |V_3| \frac{\partial P_i}{\partial |V_3|} \cdot \frac{\Delta V_3}{|V_3|} + |V_4| \frac{\partial P_i}{\partial |V_4|} \cdot \frac{\Delta V_4}{|V_4|} \end{aligned} \text{ --- (5)}$$

\* Note:  $\frac{\Delta |V_i|}{|V_i|}$  is introduced for mathematical simplification as will be shown later.

$\Delta Q_i$  is the same as (5) but with  $P_i$  replaced by  $Q_i$ .

$$\Delta Q_i = \frac{\partial Q_i}{\partial \delta_2} \Delta \delta_2 + \text{---} + |V_4| \frac{\partial Q_i}{\partial |V_4|} \cdot \frac{\Delta V_4}{|V_4|} \text{ --- (6)}$$

\* rewrite 5, 6 in a matrix form as follows:  
eqn (9.45) in the book

$$\begin{array}{c}
 \left[ \begin{array}{cc|cc}
 \frac{\partial P_2}{\partial \delta_2} & \dots & \frac{\partial P_2}{\partial \delta_4} & \\
 \vdots & \mathbf{J_{11}} & \vdots & \\
 \frac{\partial P_4}{\partial \delta_2} & \dots & \frac{\partial P_4}{\partial \delta_4} & \\
 \hline
 \frac{\partial Q_2}{\partial \delta_2} & \dots & \frac{\partial Q_2}{\partial \delta_4} & \\
 \vdots & \mathbf{J_{21}} & \vdots & \\
 \frac{\partial Q_4}{\partial \delta_2} & \dots & \frac{\partial Q_4}{\partial \delta_4} & 
 \end{array} \right]
 \left[ \begin{array}{cc|cc}
 |V_2| \frac{\partial P_2}{\partial |V_2|} & \dots & |V_4| \frac{\partial P_2}{\partial |V_4|} & \\
 \vdots & \mathbf{J_{12}} & \vdots & \\
 |V_2| \frac{\partial P_4}{\partial |V_2|} & \dots & |V_4| \frac{\partial P_4}{\partial |V_4|} & \\
 \hline
 |V_2| \frac{\partial Q_2}{\partial |V_2|} & \dots & |V_4| \frac{\partial Q_2}{\partial |V_4|} & \\
 \vdots & \mathbf{J_{22}} & \vdots & \\
 |V_2| \frac{\partial Q_4}{\partial |V_2|} & \dots & |V_4| \frac{\partial Q_4}{\partial |V_4|} & 
 \end{array} \right]
 \begin{bmatrix}
 \Delta \delta_2 \\
 \Delta \delta_3 \\
 \Delta \delta_4 \\
 \hline
 \frac{\Delta |V_2|}{|V_2|} \\
 \frac{\Delta |V_3|}{|V_3|} \\
 \frac{\Delta |V_4|}{|V_4|}
 \end{bmatrix}
 =
 \begin{bmatrix}
 \Delta P_2 \\
 \Delta P_3 \\
 \Delta P_4 \\
 \hline
 \Delta Q_2 \\
 \Delta Q_3 \\
 \Delta Q_4
 \end{bmatrix}
 \end{array}$$

⋮ (7)

\* (7) is used for load flow solution by using Newton Raphson method

1) The partial derivatives of the Jacobian, can be derived from the equations (1) and (2) (i.e.:  $P_{cal}$ ,  $Q_{cal}$ )  
see equations: 9.52, 9.53, 9.55, 9.56, 9.58, 9.60

2) By assuming initial values for state variables, using flat start:  $V_2^{(0)} = V_3^{(0)} = V_4^{(0)} = 1 \angle 0^\circ$ , then:

(a) the elements of the Jacobian matrix can be evaluated

(b) evaluate  $P_{cal}$ ,  $Q_{cal}$ , then find:  $\Delta P_i = P_{i,sch} - P_{i,cal}$

$$\Delta Q_i = Q_{i,sch} - Q_{i,cal}$$

where:  $P_{sch} = P_G - P_D$

$$Q_{sch} = Q_G - Q_D$$

for  $i = 2, 3, 4$



3) evaluate the state variables:

$$\begin{bmatrix} \Delta \delta_2 \\ \vdots \\ \frac{\Delta |V_4|}{|V_4|} \end{bmatrix} = [J]^{-1} \begin{bmatrix} \Delta P_2 \\ \vdots \\ \Delta Q_2 \end{bmatrix}$$

4) calculate new values:

$$\delta_i^{(1)} = \delta_i^{(0)} + \Delta \delta_i^{(0)}$$

$$|V_i|^{(1)} = |V_i|^{(0)} + \Delta |V_i|^{(0)} = |V_i|^{(0)} \left( 1 + \frac{\Delta |V_i|^{(0)}}{|V_i|^{(0)}} \right)$$

5) Repeat the process to calculate new values for the state variables

6) the process terminates when  $|V_i^{(k)} - V_i^{(k-1)}| \leq \epsilon$  for all  $i$   
 or  $|\Delta P_i|$  and  $|\Delta Q_i| \leq \epsilon$  for all  $i$   $i = 2, 3, 4$

## \* Comments :

i) in this example (i.e. all buses except the slack) the order of the Jacobian is  $(6 \times 6)$

ii) if bus # 4 is PV (i.e.  $|V_4|$  is specified)  $\therefore$   ~~$\Delta V_4 = 0$~~

$$|\Delta V_4| = 0$$

$\therefore$  (a) the 6<sup>th</sup> column of the  $[J]$  will be eliminated.

(b)  $Q_4$  can not be calculated until load flow is complete.

$\therefore$  6<sup>th</sup> row will be eliminated

$\therefore$  the order of the Jacobian will be :  $(5 \times 5)$

\* in general the order of Jacobian =  $(2N - N_g - 2)$

in this example :  $N = 4$   
 $N_g = 1$

# of busbars

# of PV buses

$$\therefore \text{order} = (2(4) - 1 - 2) = 5$$

\* see: e.g. : (9.5) page 353