



Electrical Circuits (1) (EE211)

First Exam

3<sup>rd</sup> Term, 2016-2017

June 19<sup>th</sup>, 2017. 13:00 – 14:00

20




الاسم ..... رقم ..... (7)  
Reg. No.: 0140754

Problem 1: (6 points)

- a) Find the equivalent resistor ( $R_{ab}$ ) if all the resistors have a value of  $30 \Omega$ .

6

$$(b+c)/d \Rightarrow 20\Omega$$

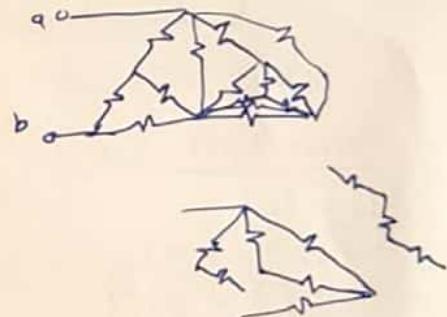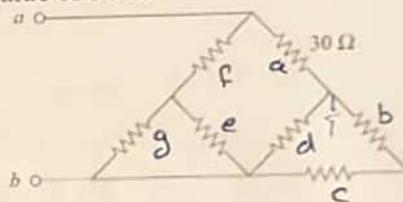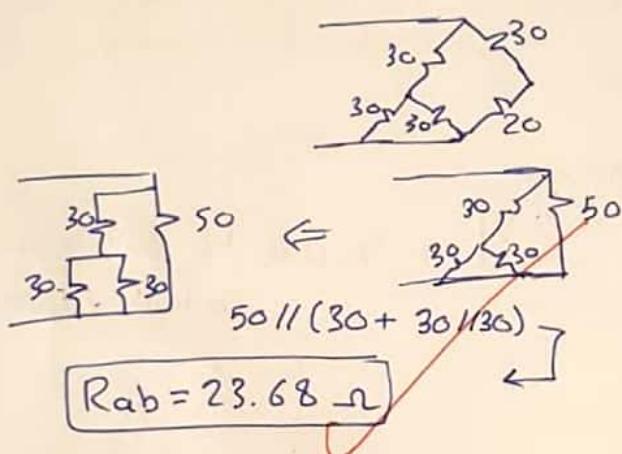

$$R_{ab} = 34 \Omega$$

- b) Find the value of  $\alpha$  such that  $|V_o/V_s| = 10$

$$I_o = \frac{V_s}{2R}$$

$$\alpha I_o + V_o \left( \frac{2}{R} \right) = 0$$

$$\alpha I_o = -2 \frac{V_o}{R}$$


$$I_o = -2 \frac{V_o}{\alpha R}$$

$$V_o = \frac{R \times I_o}{-2}$$

$$V_o = \frac{\alpha V_s}{-4 R}$$

~~$$V_o = -40$$~~

marked

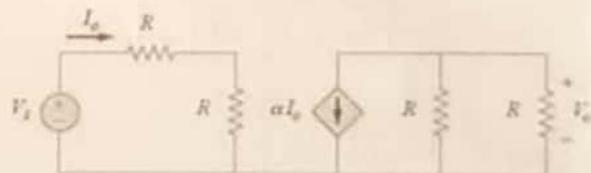

$$\frac{V_s}{2R} = -2 \frac{V_o}{\alpha R}$$

$$\alpha = -4 \frac{V_o}{V_s}$$


$$\left| \frac{V_o}{V_s} \right| = 10$$

~~$$\alpha = -40$$~~

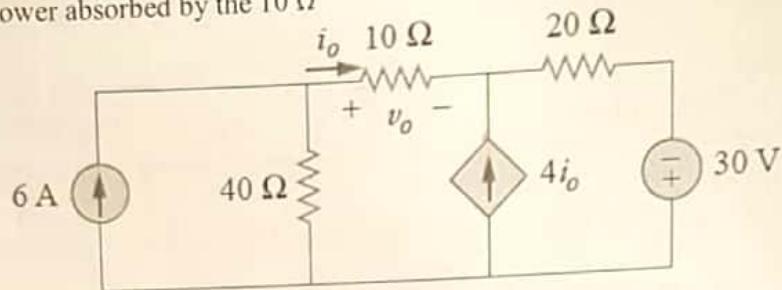
**Problem 2: (3 points)**

In the circuit shown, if  $i_o$  due to 6 A source only is 1.6 A

- Find  $v_o$  due to 30 V source active alone
- Find the power absorbed by the  $10 \Omega$



a)  $\frac{30V}{10\Omega}$  active alone

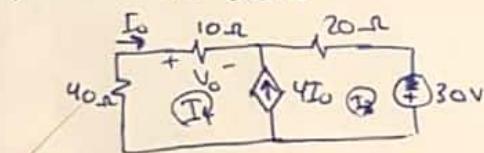

$$v_o = 10i_o$$

Super mesh 1-2

$$I_1 = I_o$$

$$I_2 - I_1 = 4i_o$$

$$I_2 = 5I_1$$

$$50I_1 + 20I_2 - 30 = 0$$

$$5I_1 + 2I_2 = 3$$

$$15I_1 = 3$$

$$I_1 = 0.2A$$

Answer

$$v_o = 2V$$

$v_o$  due to 30V Source  
active alone.

b)  $P_{10\Omega} = 10 I_o^2$

$$I_o = I_o' + I_o''$$

$$I_o' = 0.2A \rightsquigarrow \text{by } 30V$$

$$I_o'' = 1.6A \rightsquigarrow \text{by } 6A$$




$$I_o = 1.8A$$

$$P_{10\Omega} = 10(1.8)^2$$




$$P_{10\Omega} = 32.4 \text{ watt (absorbed)}$$

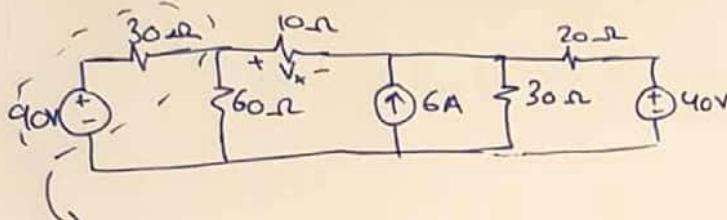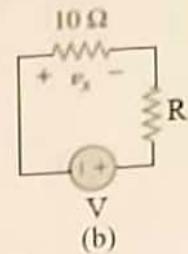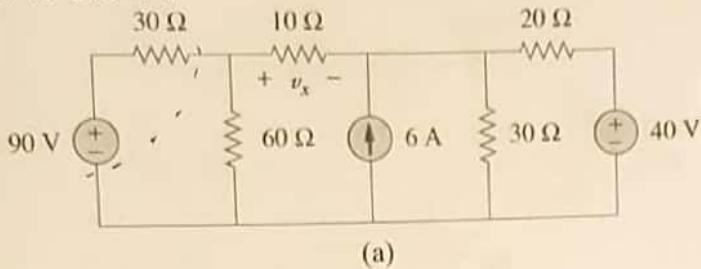**Problem 3: (5 points)**

Simplify the circuit in Fig. (a) to look like the circuit in Fig. (b) using source transformation then find the value of 'R' and 'V'.




$$3A \uparrow \quad | \quad 10\Omega \quad | \quad +V_x - \\ | \quad 30\Omega \quad | \quad 60\Omega \\ 30//60 = 20$$

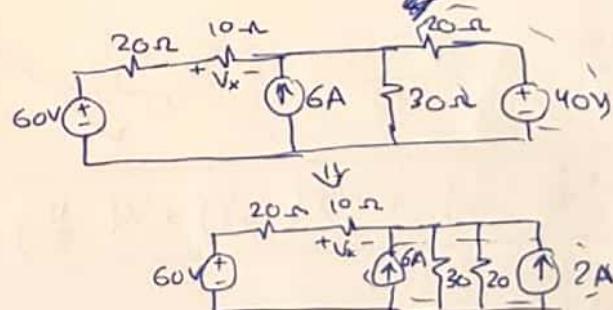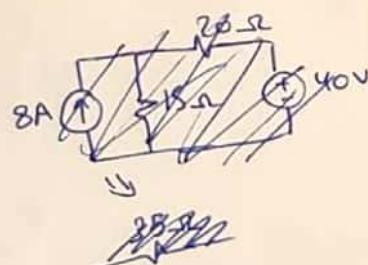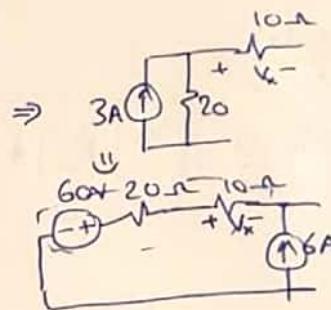

$$60V \quad | \quad 20\Omega \quad | \quad 10\Omega \quad | \quad 12\Omega \\ +V_x - \quad | \quad 96V$$

$$36V \quad | \quad 10\Omega \quad | \quad 32\Omega \\ +V_x -$$


$$R = 32\Omega \\ V = 36V$$

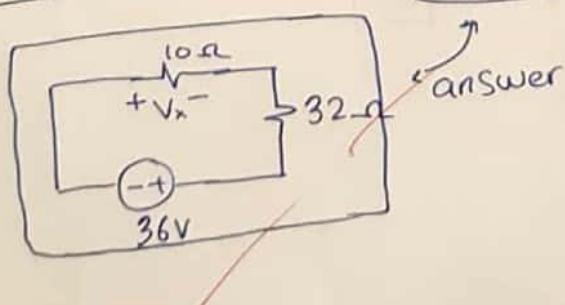

$$12 \quad | \quad 8 \Rightarrow 96V$$

⑥ Problem 4: (6 points)

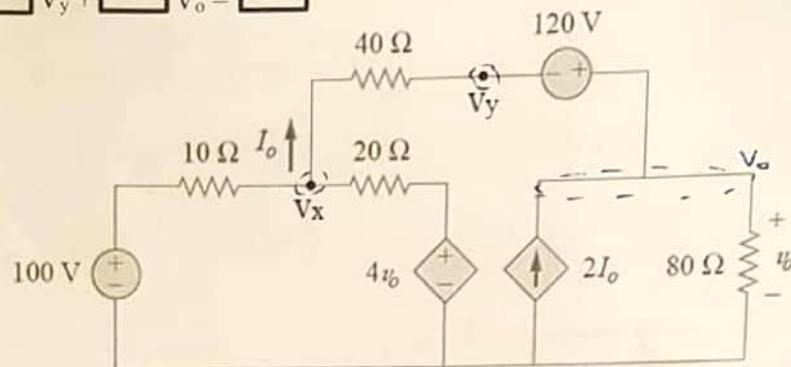Write all the nodal equations in terms of  $v_x$ ,  $v_y$  and  $v_o$  only as the following form:



$$I_o = \frac{V_x - V_y}{40}$$

KCL @  $V_o, V_y$  (Super Node)

$$\frac{V_o}{80} - 2I_o + \frac{V_y - V_x}{40} = 0 \Rightarrow \boxed{V_o \left( \frac{1}{80} \right) + V_y \left( \frac{3}{40} \right) + V_x \left( -\frac{3}{40} \right) = 0}$$

$$\boxed{V_o - V_y = 120V}$$

KCL @  $V_x$

$$\frac{V_x - 4V_o}{20} + \frac{V_x - 100}{10} + \frac{V_x - V_y}{40} = 0 \quad \textcircled{2}$$

$$\boxed{V_x \left( \frac{1}{20} + \frac{1}{10} + \frac{1}{40} \right) + V_y \left( -\frac{1}{40} \right) + V_o \left( -\frac{4}{20} \right) = 10}$$

$$\frac{V_o}{80} + 3 \left( \frac{-V_x + V_y}{40} \right) \\ I_o = \frac{V_x - V_y}{4}$$

3 equations

$$\boxed{\frac{-3}{40}} V_x + \boxed{\frac{3}{40}} V_y + \boxed{\frac{1}{80}} V_o = \boxed{0}$$

$$\boxed{0} V_x + \boxed{-1} V_y + \boxed{1} V_o = \boxed{120}$$

$$\boxed{\frac{7}{40}} V_x + \boxed{\frac{-1}{40}} V_y + \boxed{\frac{-1}{5}} V_o = \boxed{10}$$