

By: Helda Khader

# Circuits 1

*Dr. Ahmad Atieh*

POWER UNIT

Fall 2016

No. Chapter 1

→ Electric circuit is a mathematical model to approximate the behavior of an actual power system.


→ Lumped parameter system is the system where the effects are studied instantaneously and the signal propagates in it is larger than 10 times the dimension of the system

V 220 V

f 60 Hz

$$\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/s}}{60 \text{ Hz}} = 5 \times 10^6 \text{ m}$$

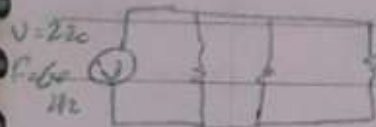The dimension of the system  $\leq 5 \times 10^5 \text{ m}$



International system of units SI

length	m	frequency (f)	Hz	$s^{-1}$
mass	kg	force	F N	$\frac{m}{s^2}$
time	s	energy/work	w J	N.m
current	A	electric charge	C c	A.s
thermo dynamic temp	k	power	p W	J
luminous intensity	cd	electric potential	V v	J
		electric resistance	R $\Omega$	V/A
		electric conductance	G S	$\frac{1}{\Omega}$
		electric capacitance	C F	$\frac{s}{\Omega}$
		magnetic flux	wb	$\frac{V}{A}$
		Inductance	L H	$\frac{wb}{A}$



⇒ Many of SI units has small or large values, then we use prefix to quantify them:-

atto	a	$10^{-18}$	→ as
femto	f	$10^{-15}$	→ fs
pico	p	$10^{-12}$	→ pF, pS, pm
nano	n	$10^{-9}$	→ ns, nm, nF
micro	μ	$10^{-6}$	→ μs, μm, μF, MHz
milli	m	$10^{-3}$	→
Centi	c	$10^{-2}$	→ cm
deci	d	$10^{-1}$	
deka	da	$10^{-2}$	
hecto	h	$10^{-2}$	
kilo	k	$10^3$	→ kg, kΩ
mega	M	$10^6$	
giga	G	$10^9$	
tera	T	$10^{12}$	

- engineers

- engineers uses prefixes

that has power

divisible by 3

exactly

$10^5$  NS ✓

10 000 000 pS ✗

0.01 ms ✗

900 NS ✓


1001 μS ✗

1.001 ms ✓

⇒ Voltage and current

$$q = 1.602 \times 10^{-19} \text{ C}$$

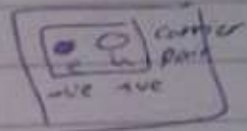↓  
 electrical effects are attributed to the separation of charges and motion of charges



h Mole  
 e electron

⇒ voltage is the rate of change of energy per unit charge created by separation

$$V = \frac{dw}{dq} \cdot \frac{J}{C}$$

⇒ current is the rate of flow of charge per second

$$I = \frac{dq}{dt} \frac{C}{s}$$

I is in A

$$v = \frac{dw}{dq}$$

$$i = \frac{dq}{dt}$$

Current elements


	symbol		circuit symbol
① Resistor	R	dissipate energy →	
Capacitor	C	charges →	
Inductor	L	magnetic field →	

Storage elements



No.	Symbol	Circuit symbol
④ Source voltage $V$	$V$	
⑤ Source current $I$	$I$	

$V$  DC supplied  
 $V$  AC supplies

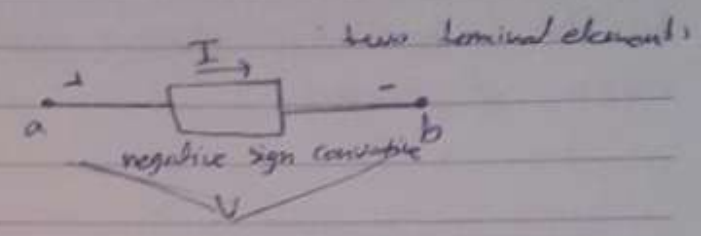


two terminal element  
 current flowing in the element is  $I$  voltage drop is voltage from terminal a to terminal b
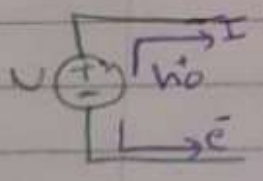
### → Ideal Basic circuit Element

Ideal element is a non-realizable element (not practical) values don't change with time

Basic element can't be broken to other element




power :-

$$p = \frac{dw}{dt} = \frac{dw}{dq} \frac{dq}{dt}$$

$$p = V \cdot I$$

$$W = V \cdot A$$

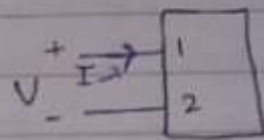


$$p = VI$$




$$p = -VI$$

$p > 0$  power is delivered to the circuit element

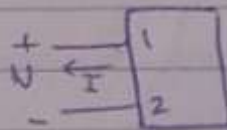$p < 0$  power is extracted from the element





$$p = -VI$$



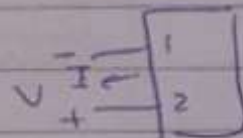


$$p = VI$$

not VC sign convention

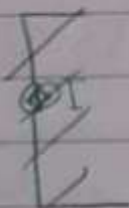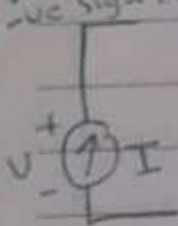

↔

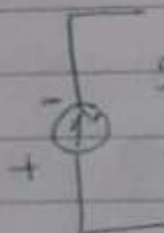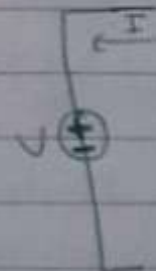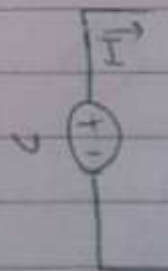


generating power to the circuit  
"extracting"

$V, I > 0$   
generating power to the circuit

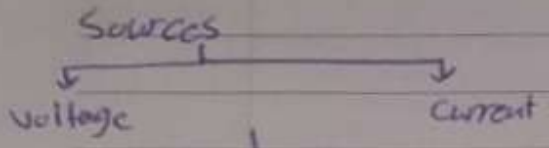
$V, I > 0$   
extracting power from the circuit





**independent**  
 The voltage or current value does not depend on other current or voltage anywhere in the circuit

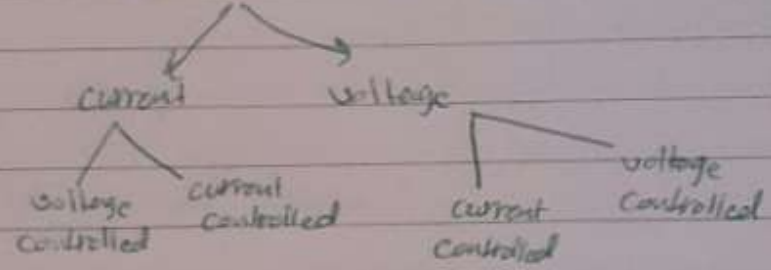**dependent**  
 The current or voltage value depends on the current or voltage in the circuit



$V_s = \mu V_x$   
 dependent voltage controlled voltage source




unit of  $\mu$  is dimensionless



$I_s = \alpha I_x$   
 dependent voltage controlled current source  
 $\alpha : \Omega$

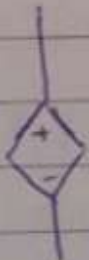$V_s = \rho I_x$   
 dependent current controlled voltage source




$I_s = \beta I_x$   
 dependent current-controlled current source  
 $y = f(x)$   
 $\beta = \text{dimensionless}$

$$\rho = \frac{V}{A} = \Omega$$


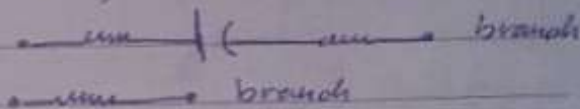
## Circuit Analysis :-

- elements


- branch :- two terminal device that may contain more than one element



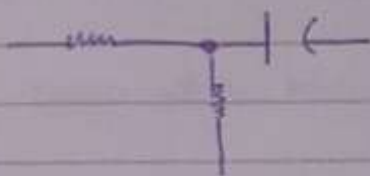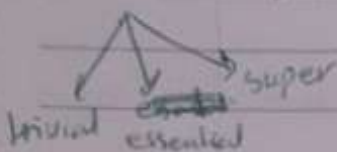- Node or is a junction between two or more branches




trivial between two branches

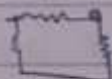

essential -> three or more branches



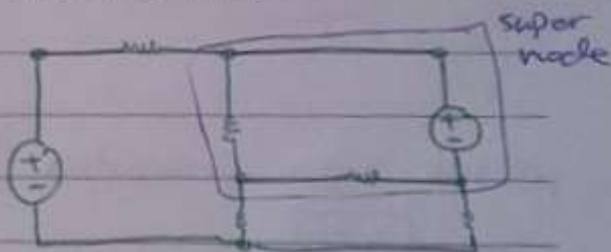
super -> Region that contains more than one node



~~trivial~~  
~~essential~~





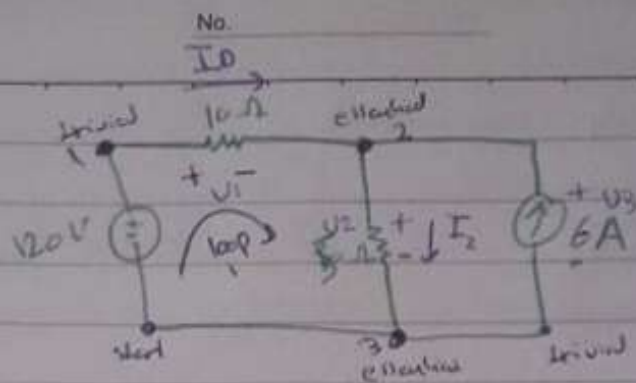

KVL

- works in loops
- $\sum_{j=1}^k V_j = 0$   
is the voltage across an element
- $k$  # of elements in the loop

- Find  $I_0$
- check power generated and dissipated for each element?

KCL

- works at nodes
- $\sum_{j=1}^k I_j = 0$


KVL for loop #1

$-120 + V_1 + V_2 = 0$  CW  
clockwise

$-V_2 - V_1 + 120 = 0$  CCW  
counter clockwise

$-120 + 10I_0 + 50I_2 = 0 \dots \text{--- (1)}$

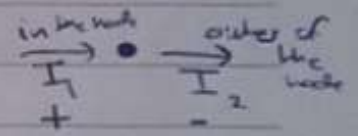$k$  = number of branches connected to the node



KCL (using node 2)

$+I_0 - I_2 + 6 = 0 \dots \text{--- (2)}$

$I_0 = -3A$  (current is in opposite direction set on the diagram)

$I_2 = 3A$

dissipated power

$P = VI = IR \cdot I = I^2 R$






$P_{R1} = I_0^2 R_1$   
 $= (-3)^2 (10)$

$P_{S1} = +VI$   
 $= 120 \times (-3)$   
 $= -360 \text{ W}$

$P_{R2} = I_2^2 R_2$   
 $= (3)^2 (50)$   
 $= 450 \text{ W}$

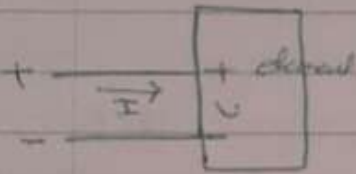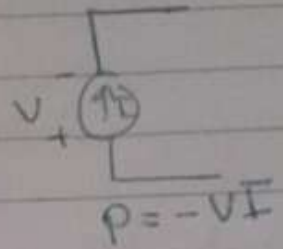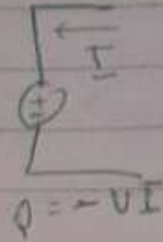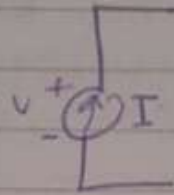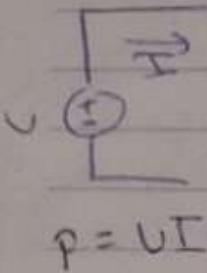source  $V_{S1}$  is extracting power from the circuit






Passive sign convention

$$P = +IV$$

$$P < 0$$

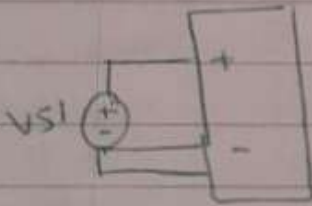

$$P = +VI$$

$$= 120 \times -3 = -360 \text{ W}$$

$$P_{S_2} = +VI$$

$$= 130 \times 6$$

$$= 900 \text{ W}$$

$$125 I_0 = 500$$

$$I_0 = 4$$


No.

$$500 = I \cdot I_0 / 100$$

## Analysis of a circuit containing Dependent sources

using KCL of node a:-

$$\sum_{j=1}^3 I_j = 0$$

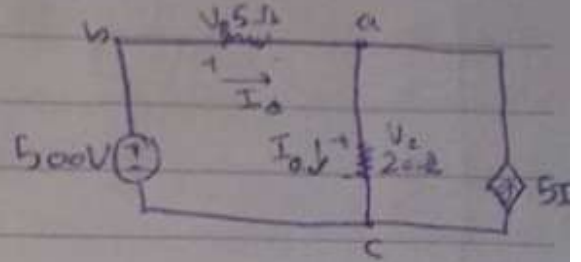

$$-I_0 + 5I_0 + I_0 = 0$$

$$6I_0 = I_0 \quad \text{--- (1)}$$

→ Using KVL for loop 1:-

$$\sum_{j=1}^3 V_j = 0 \Rightarrow -500 + 5I_0 + 20I_0 = 0$$

$$20I_0 = 500 - 5I_0 \quad \text{--- (2)}$$

$$I_0 = 24 \text{ A}$$

$$V_0 = 20I_0$$



$$= 20 \times 24 = 480 \text{ V}$$

<del>physiological relation</del>	current	physiological relation
<del>Barely feel it</del>	3-5 mA	Barely feel it
<del>Extrem pain</del>	35-50 mA	Extrem pain
<del>muscles paralysis</del>	50-70 mA	muscles paralysis
<del>heart stop</del>	50 V/mA	heart stop



No

black box

$V_1$	$I_1$
30	0
15	3
0	6

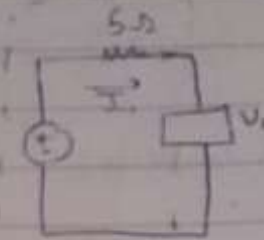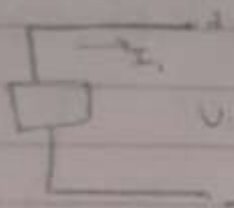

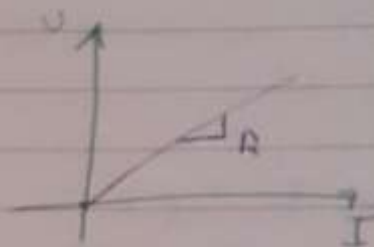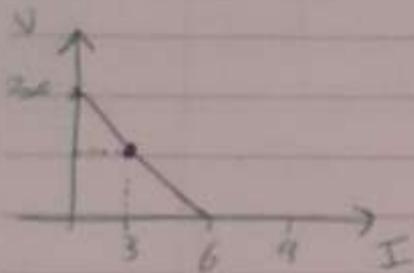Construct  
Circuit model for the device shown.



$$V = IR + C$$


$$V = R'I$$

$$k = \frac{-\Delta I}{\Delta V} = \frac{-V}{A} \Rightarrow 30 = -\frac{0}{5}I + C$$

$$C = 30$$

$$V_1 = -5I_1 + 30$$

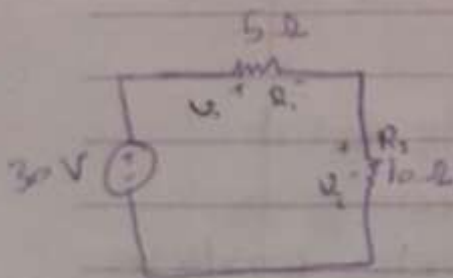→ Using the ~~black box~~ circuit model predict the power that the device will deliver to a  $10 \Omega$  resistor?



KVL :-

$$-30 + 5I_1 + 10I_1 = 0$$

$$-30 + 15I_1 = 0$$

$$I_1 = 2A$$



$$P_{R_2} = I^2 R = 4 \times 10 = 40 W$$

40 W



\* Simple Resistor circuits -

→ Resistors in series

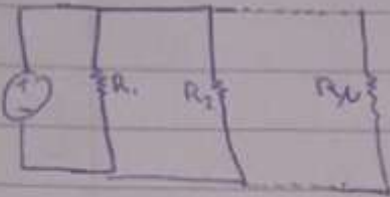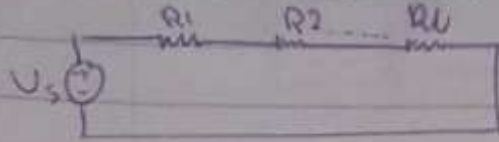

R  
Resistor



G  
Conductor

Ω  
R

S  
G

$$R = \frac{1}{G}$$

unit  $\Omega$  — S

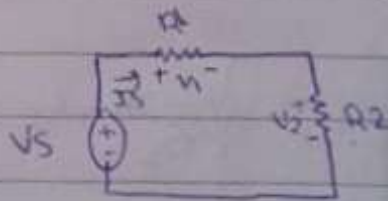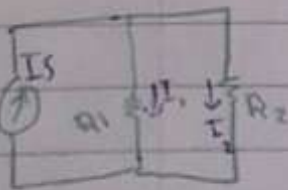

$$I_2 = \frac{R_1}{R_1 + R_2} I_s$$

$$V_2 = I_s R_2$$


$$I_s = \frac{V_s}{R_{eq}}$$

$$I_s = I_1 = I_2 = \frac{V_s}{R_1} = \frac{V_2}{R_2}$$

$$V_2 = V_s \frac{R_2}{R_{eq}}$$

$$V_2 = V_s \frac{R_2}{R_1 + R_2}$$

Ex 3.1  
Nelson

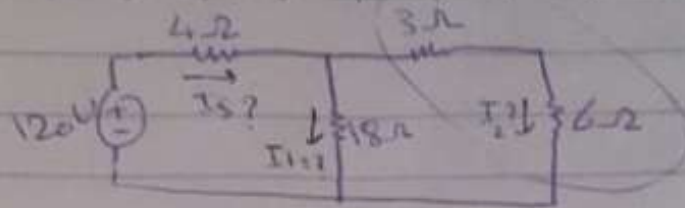

$$R_{eq} \rightarrow I_s = \frac{V_s}{R_{eq}}$$

$$3 + 6 = 9 \Omega$$

$$9 \parallel 18 \rightarrow \frac{9 \times 18}{9 + 18} = 6 \Omega$$


$$4 + 6 = 10 \Omega \rightarrow R_{eq}$$

$$I_s = \frac{V_s}{R_{eq}} = \frac{120}{10} = 12 A$$

$$I_1 = \frac{9}{9 + 18} \times 12 = 4 A$$

$$I_2 = \frac{18}{18 + 9} \times 12 = 8 A$$

Leading Effect

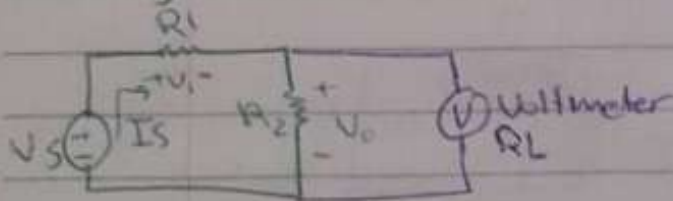



$$\text{Theoretically: } V_0 = \frac{R_2}{R_1 + R_2} V_s$$

$$I_2 = I_s$$

practically :-

$$I_2 \neq I_s$$

$$I_2 = I_s - I_L$$

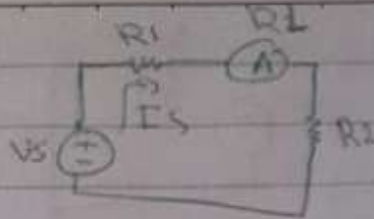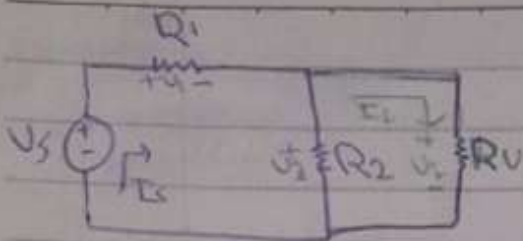

Theoretically

$$I_s = \frac{V_s}{R_1 + R_2}$$

practically

$$I_s = \frac{V_s}{R_1 + R_2 + R_3}$$



$R_L$  as high as possible  $\rightarrow \infty$

$R_L$  as small as possible  $\rightarrow 0$

$$V_o = I_2 R_2$$

$$V_o = I_L R_L$$

$$V_o = I_s R_{eq}$$

$$R_{eq} = \frac{R_2 R_L}{R_2 + R_L}$$

$$I_s = \frac{V_s}{R_1 + R_{eq}} = \frac{V_s}{R_1 + \frac{R_2 R_L}{R_2 + R_L}} = \frac{V_s}{\frac{R_1 R_2 + R_1 R_L + R_2 R_L}{R_2 + R_L}}$$

$$V_o = \frac{R_2 R_L}{R_2 + R_L} \cdot \frac{V_s}{\frac{R_1 R_2 + R_1 R_L + R_2 R_L}{R_2 + R_L}} = \frac{R_2 V_s}{\frac{1}{R_L} [R_1 R_2 + R_1 R_L + R_2 R_L]}$$

$$V_o = \frac{R_2 V_s}{R_1 \left[ 1 + \frac{R_2}{R_L} \right] + R_2}$$

$$V_o = \frac{R_2}{R_1 + R_2} V_s$$

$$\frac{R_2}{R_L} \rightarrow 0$$

$R_L \rightarrow \infty$  it's an open circuit



100 Ω  
125 Ω

No.

Ex 3.2



$R_1$

$V_o$  min

$V_o$  max

when

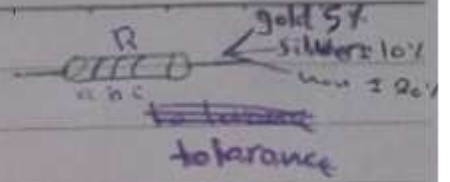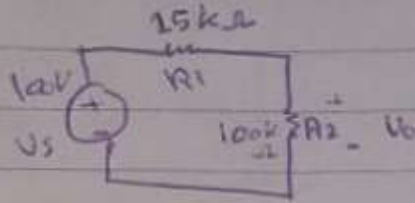$R_1$  and  $R_2$  has tolerance values of  $\pm 10\%$ ?



black 0  $10^0$

brown 1  $10^1$

Red 2  $10^2$

orange 3  $10^3$

yellow 4  $10^4$

Green 5  $10^5$

blue 6  $10^6$

Violet 7  $10^7$

Gray 8  $10^8$

white 9  $10^9$

$$V_o = \frac{R_2}{R_1 + R_2} V_S$$

$$\pm \frac{10}{100} \times 25000 = \pm 2500 \Omega$$

$$\frac{25000 - 2500}{2500} \leq R_1 \leq \frac{25000 + 2500}{2500}$$

$$\pm \frac{10}{100} \times 100000 = 10000 \Omega$$

$$100000 - 10000 \leq R_2 \leq 100000 + 10000$$


$\frac{R_1}{R_{1 \min}}$	$\frac{R_2}{R_{2 \min}}$	$V_o$
		80V

$R_{1 \min}$	$R_{2 \max}$	83.02V	$V_o$ max
--------------	--------------	--------	-----------

$R_{1 \max}$	$R_{2 \min}$	76.60V	$V_o$ min
--------------	--------------	--------	-----------

$R_{1 \max}$	$R_{2 \max}$	90V
--------------	--------------	-----

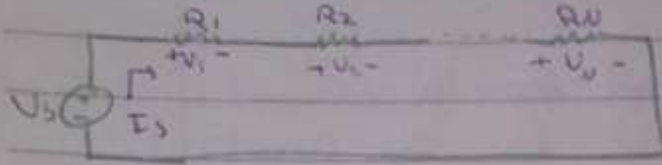
## Generalization of current divider and voltage divider



$$U_j = I_s \cdot R_j \quad j=1, 2, \dots, N$$

$$I_s = \frac{U_s}{R_{eq}}$$

$$U_j = \frac{U_s R_j}{R_{eq}}$$

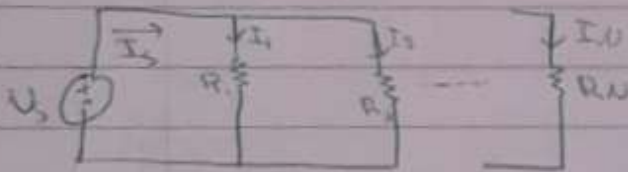

$$I_j = \frac{U_s}{R_j}$$

$$U_s = I_s \cdot R_{eq}$$


$$I_j = I_s \cdot \frac{R_{eq}}{R_j}$$

## passive sign ~~convention~~ Convention


$p < 0$  power is extracted from the element  
power is supplied to the circuit

$p > 0$  power is delivered to the element

## practical

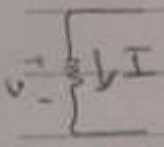


$$p = IV$$

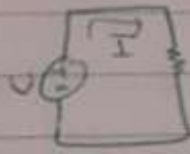

$$p = VI$$

$$p > 0$$

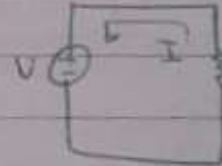- power is delivered to the circuit
- supplied to the surface





$$p = -VI$$



$$p < 0$$

- power is delivered to the source

independent source

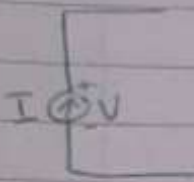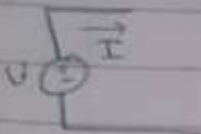

dependent source

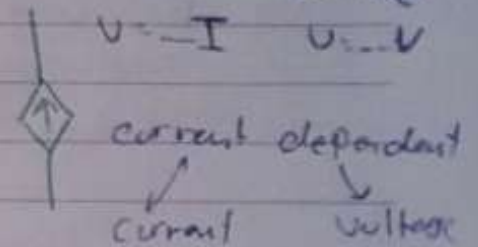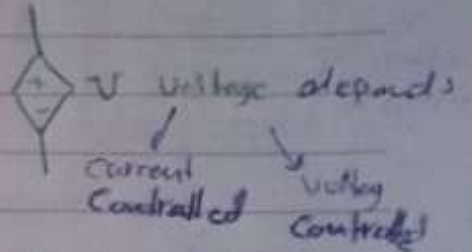

$V = \dots I$        $V = \dots V$   
 $I = \dots V$        $I = \dots V$

$I_j = I_s \frac{R_o}{R_j}$



$V_j = V_s \frac{R_i}{R_o}$

Voltmeter

- measure voltage
- parallel to the element
- very high resistor

Ammeter

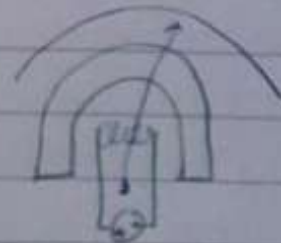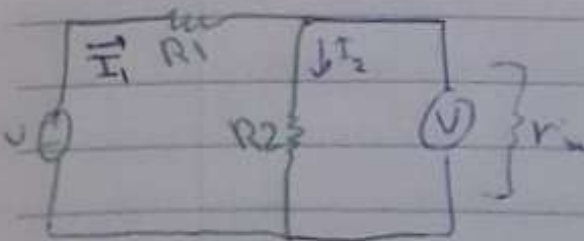- measure current
- Connected in series
- very low resistor




$V = I_2 R_2$

$I_2 = ??$


$r_{in}$  is the internal resistor of the meter

$I_2 = I_s \frac{r_{in}}{r_{in} + R_2}$

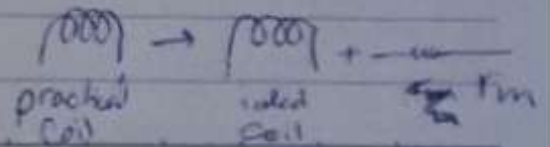





No. \_\_\_\_\_

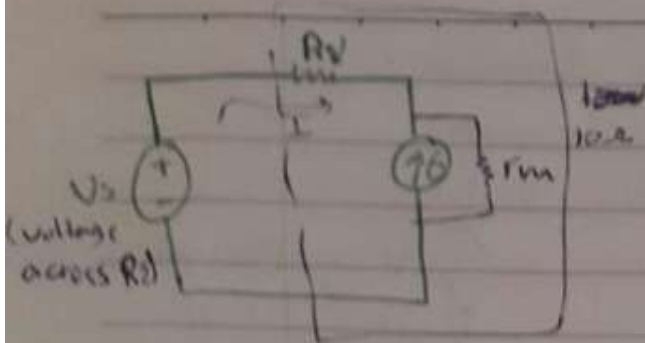

$$I = \frac{V_s}{r_m + R_v}$$

voltmeter

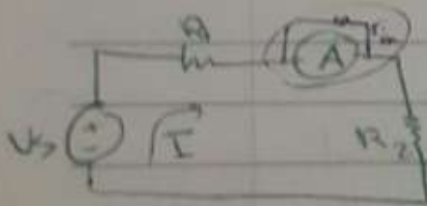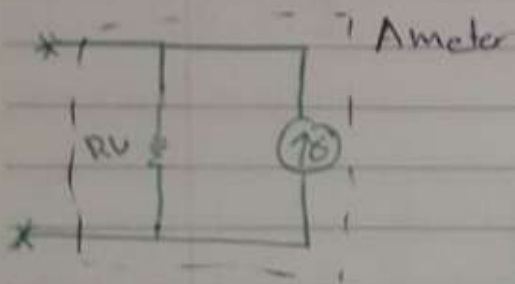$R_v$  very high  
and connected in  
series



$$I = \frac{V_s}{R_1 + r_m + R_2}$$


## \* Measuring Resistances using wheat stone Bridge

→ Adjust  $R_3$  until  $G$  reads 0 A.

$$V_{ab} = 0 \text{ V}$$

$$I_1 = I_2, \quad I_3 = I_x$$

$$V_a = V_b$$

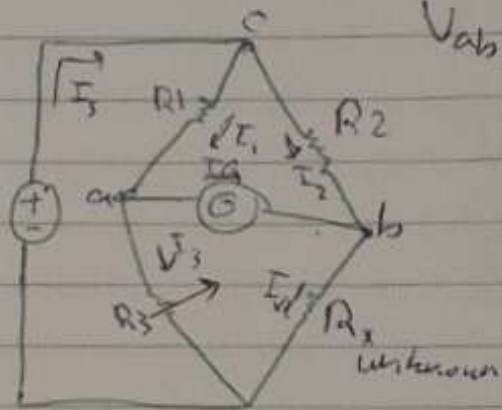

$$V_{ab} = V_a - V_b$$

$$\text{Then } V_{ad} = V_{bd} \Rightarrow I_3 R_3 = I_1 R_1$$

G: Galvanometer

$$V_{ca} = V_{cb} \Rightarrow \cancel{I_3 R_3} = \cancel{I_2 R_2} \quad I_1 R_1 = I_2 R_2 \rightarrow I_2 = I_1 \frac{R_1}{R_2}$$

$$I_3 R_3 = I_2 R_2$$

$$\cancel{I_3} R_3 = \cancel{I_2} \frac{R_1}{R_2} R_2 \Rightarrow R_x = \frac{R_2}{R_1} R_3$$

$\frac{R_2}{R_1} = 1 \Rightarrow$  This is not right (practical)

$R_3$  range 0 - 10  $\Omega$  - 10  $\text{k}\Omega$

measure  $R_x = 1000 \Omega$  (No We can't)





typical value  $\frac{R_2}{R_1} \approx 0.01$  to 1000

$R_3$  11  $\text{k}\Omega$



range of  $R_x$  that can be measured up to 111  $\text{k}\Omega$

No. ....

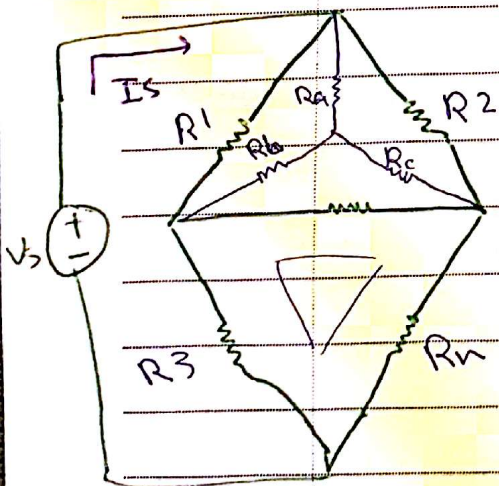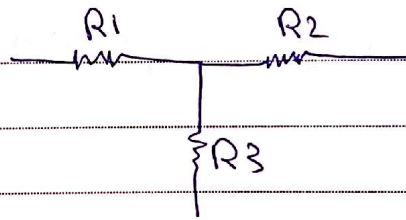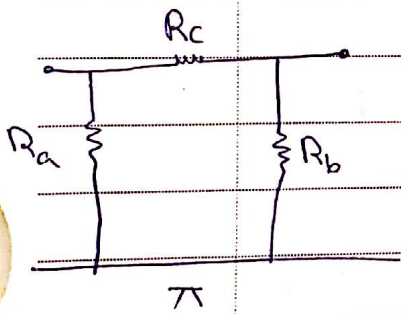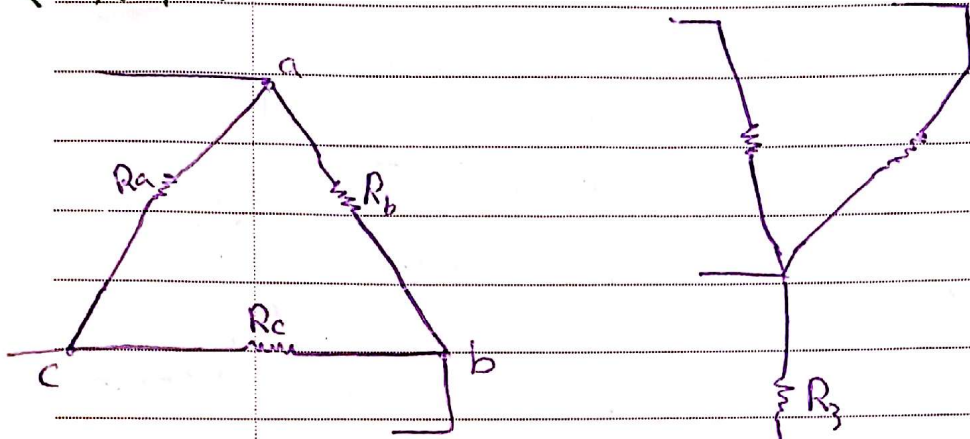(Delta - wye) equivalent circuits  
•  $\pi + T$



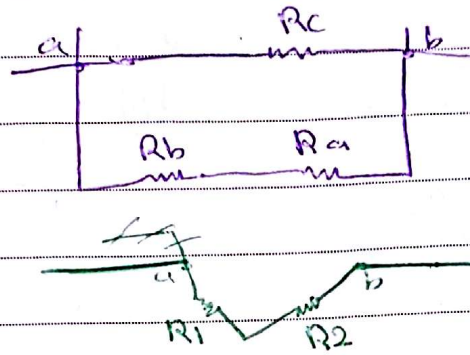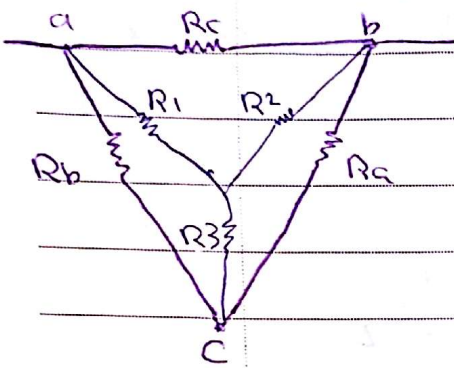

in  $\Delta$ -Conf.in  $Y$ -Conf

Terminals a and b equivalent Resistance in  $\Delta$  Configuration should be equal to equivalent Resistance in  $Y$ -Configuration

$$\frac{R_c (R_b + R_a)}{R_c + R_b + R_a} = R_1 + R_2$$

$$\left\{ \begin{aligned} R_c // R_b + R_a &= R_1 + R_2 \\ R_b // R_c + R_a &= R_1 + R_3 \\ R_a // R_b + R_c &= R_3 + R_2 \end{aligned} \right.$$

$$\frac{R_b (R_c + R_a)}{R_b + R_c + R_a} = R_1 + R_3$$

$$R_a // R_b + R_c = R_3 + R_2$$

 $\Delta \rightarrow Y$  $Y \rightarrow \Delta$ 

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$



$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

$$R_3 = \frac{R_b R_a}{R_a + R_b + R_c}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

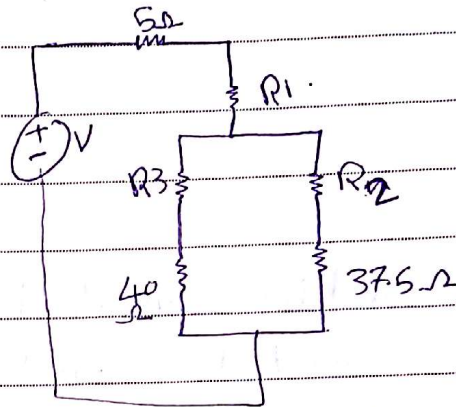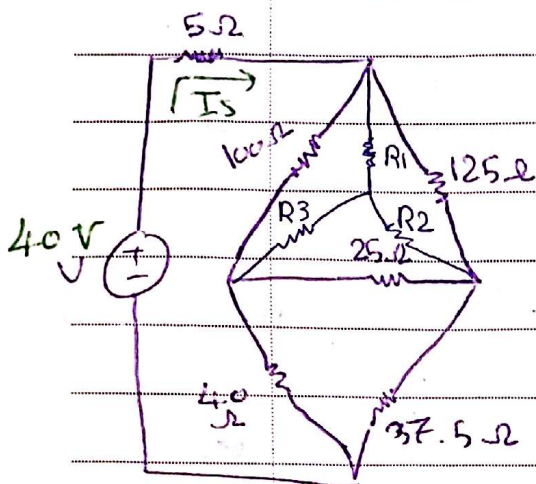
Find current and power supplied by the source.



$$R_1 = \frac{125 \times 100}{100 + 25 + 125} = 50 \Omega$$

$$R_2 = \frac{125 \times 25}{100 + 25 + 125} = 12.5 \Omega$$
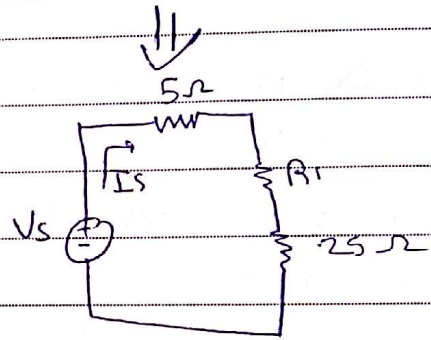
$$R_3 = \frac{100 \times 25}{100 + 25 + 125} = 10 \Omega$$



$$50 \Omega \parallel 50 \Omega = 25 \Omega$$

$$R_{\text{total}} = 5 + 50 + 25 = 80 \Omega$$

$$I_s = \frac{V_s}{R_{\text{total}}} = \frac{40}{80} = 0.5 \text{ A}$$

-ve sign convention

$$P = -VI$$


$$= -40 \times 0.5$$

$$= -20 \text{ W} \quad \text{power is extracted from the element}$$


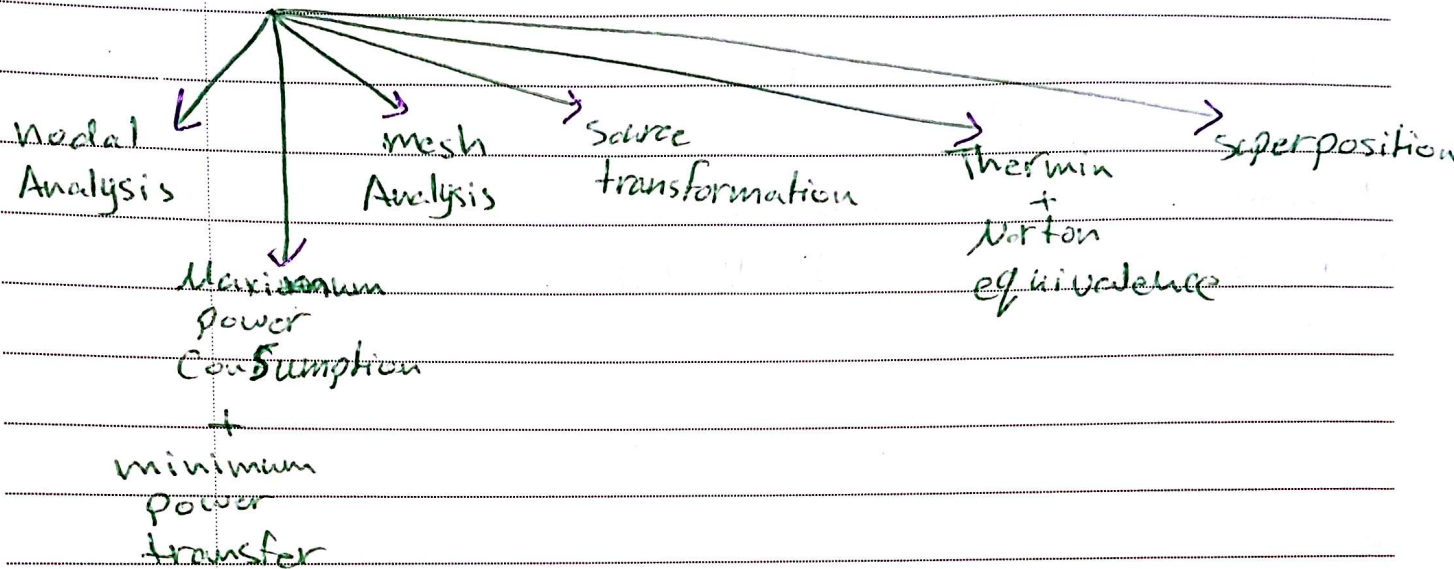
# Circuit Analysis

finding nodes' voltage and branches' current.





## Nodal Analysis :-

- ① Define the nodal voltages as independent variables.
- ② Determine the number of equations to write.
  - \*  $n$  of nodes
  - \*  $m$  of independent or dependent voltage sources
  - \* Define the reference node as the node with maximum number of elements connected to it.
  - \* of nodal equations =  $n - m - 1$

③ Use KCL at each node  $\sum_{j=1}^n I_j = 0$

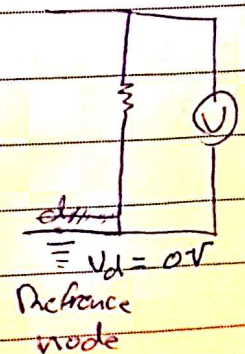- ④ current in each branch is specified using node's voltage



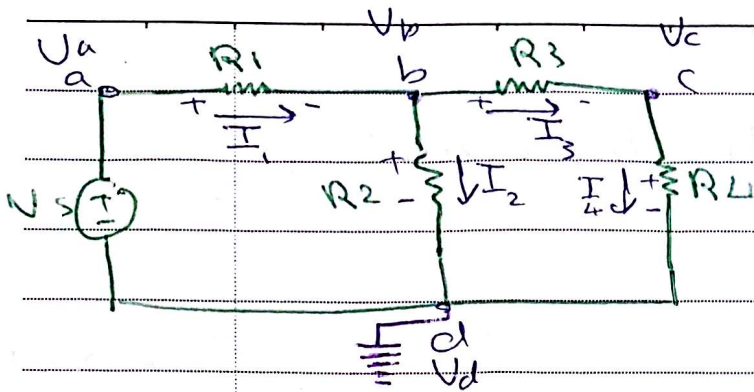knowns

$$R_1, R_2, R_3, R_4$$

$$V_s$$

unknowns

$$V_a, V_b, V_c, V_d \text{ or}$$

$$V_s$$

$$n = 4$$

$$m = 1$$

$$\# \text{ eq} \Rightarrow 4 - 1 - 1 = 2$$

node b or

$$I_1 - I_2 - I_3 = 0$$

$$\frac{V_s - V_b}{R_1} - \frac{V_b - V_d}{R_2} - \frac{V_b - V_c}{R_3} = 0$$


$$I_3 - I_4 = 0$$

$$\frac{V_b - V_c}{R_3} - \frac{V_c - V_d}{R_4} = 0$$



$N_e$  : # of essential nodes

# of equation =  $N_e - 1$

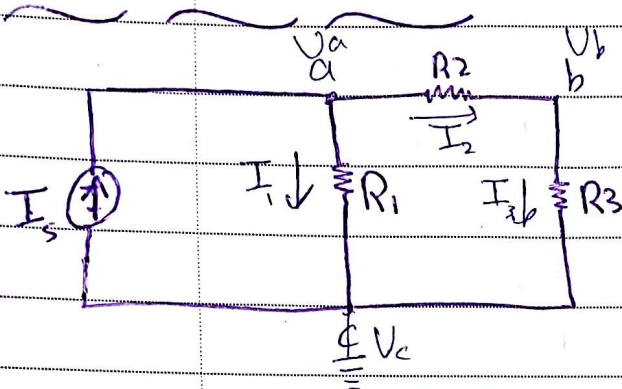

Sol:-

knowns

unknowns

$$V_c = 0 \text{ V}$$

$$R_1, R_2, R_3$$

$$V_a, V_b, V_c$$

$$V_a = ?$$

$$V_b = ?$$

node a :-

$$+I_s - I_1 - I_2 = 0$$

$$I_s - \frac{V_a - V_c}{R_1} - \frac{V_a - V_b}{R_2} = 0$$

$$I_s = \frac{V_a - V_c}{R_1} + \frac{V_a - V_b}{R_2}$$


$$I_s = V_a \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] - V_b \left[ \frac{1}{R_2} \right] \quad \text{--- (1)}$$

node b :-

$$I_2 - I_3 = 0$$

$$\frac{V_a - V_b}{R_2} - \frac{V_b - V_c}{R_3} = 0$$
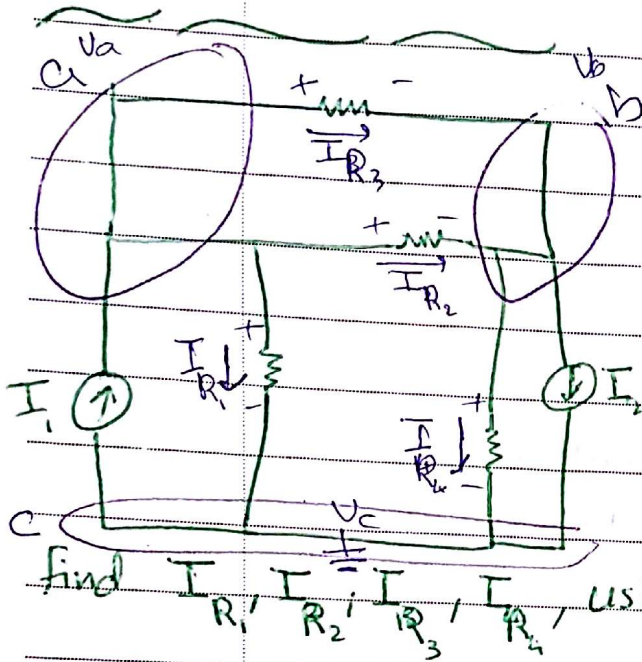
$$V_a \left[ \frac{1}{R_2} \right] - V_b \left[ \frac{1}{R_2} + \frac{1}{R_3} \right] = 0 \dots \textcircled{2}$$



- $I_1 = 10 \text{ mA}$
- $I_2 = 50 \text{ mA}$
- $R_1 = 1 \text{ k}\Omega$
- $R_2 = 2 \text{ k}\Omega$
- $R_3 = 10 \text{ k}\Omega$
- $R_4 = 2 \text{ k}\Omega$

find  $I_{R_1}, I_{R_2}, I_{R_3}, I_{R_4}$  using nodal voltage method?

$n = 3$	$n_e = 3$	unknowns	<del>knowns</del>
$m = 0$	$3 - 1 = 2$	$V_a, V_b, V_c$	
$3 - 0 - 1 = 2$			

node a :-

$$\frac{I_1}{1} - \frac{I_{R_1}}{R_1} - \frac{I_{R_2}}{R_2} - \frac{I_{R_3}}{R_3} = 0$$

$$\frac{I_1}{1} - \frac{V_a - V_c}{R_1} - \frac{V_a - V_b}{R_2} - \frac{V_a - V_b}{R_3} = 0$$

$$I_1 = V_a \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] - V_b \left[ \frac{1}{R_2} + \frac{1}{R_3} \right] \dots \textcircled{1}$$

node b :-

$$\frac{I_{R_3}}{R_3} + \frac{I_{R_2}}{R_2} - \frac{I_2}{1} + \frac{I_{R_4}}{R_4} = 0$$

$$\frac{V_a - V_b}{R_3} + \frac{V_a - V_b}{R_2} - \frac{I_2}{1} + \frac{V_b - V_c}{R_4} = 0$$



$$I_2 = V_a \left[ \frac{1}{R_3} + \frac{1}{R_2} \right] - V_b \left[ \frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_4} \right] \dots (2)$$

$$I_{R_1} = -13.57 \text{ mA} \quad \text{Current } +I_{R_1} \text{ has to be reversed as assumed.}$$

as assumed

$$I_{R_2} = 19.65 \text{ mA}$$


$$I_{R_4} = -26.43 \text{ mA}$$

Cramer's Rule:-

$$\begin{aligned} a_1 x_1 + b_1 x_2 &= u \\ a_2 x_1 + b_2 x_2 &= v \end{aligned} \Rightarrow \begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix} = a_1 b_2 - b_1 a_2$$

$$\begin{bmatrix} a_1 & b_1 \\ a_2 & b_2 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} u \\ v \end{bmatrix}$$
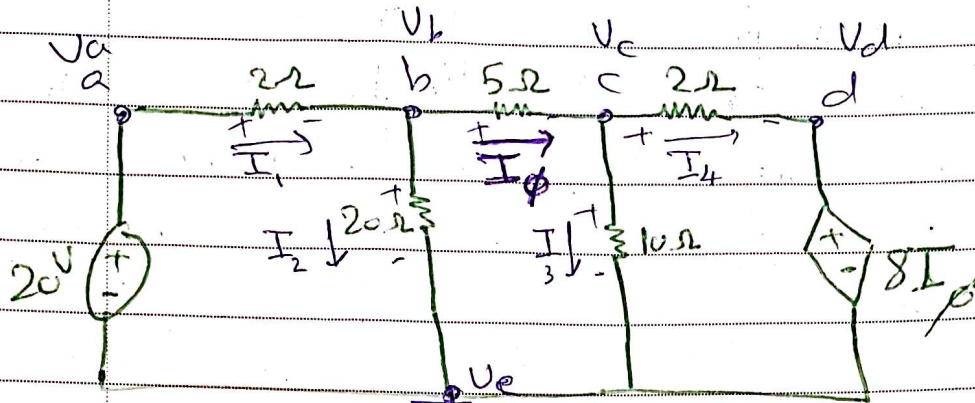
$$x_2 = \frac{\begin{vmatrix} a_1 & u \\ a_2 & v \end{vmatrix}}{\begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix}}$$



Find power dissipated in ~~5Ω~~ resistor using nodal voltage method

resistor

$$n = 5$$

$$n_e = 3$$

unknowns:

$$m = 2$$

$$n_e - 1 = 2$$

$$V_a, V_b, V_c, V_d, V_e$$

$$= 20V$$

$$= 8I_\phi$$

$$= 0V$$

$$5 - 2 - 1 = 2$$

$$I_\phi = \frac{V_b - V_e}{5}$$

node b:

$$I_1 - I_2 - I_\phi = 0$$

$$\frac{20 - V_b}{2} - \frac{V_b - V_e}{20} - \frac{V_b - V_c}{5} = 0$$

$$10 = V_b \left[ \frac{1}{2} + \frac{1}{5} + \frac{1}{20} \right] - V_c \left[ \frac{1}{5} \right] \dots \textcircled{1}$$

node c:

$$I_\phi - I_3 - I_4 = 0$$

$$\frac{V_b - V_c}{5} - \frac{V_c - V_e}{10} - \frac{V_c - V_d}{2} = 0$$

$$V_b = 16V$$

$$V_c = 10V$$

$$P = 7.2W$$


$$V_d = 8I_\phi = 8 \left[ \frac{V_b - V_c}{5} \right] = \frac{8}{5} V_b - \frac{8}{5} V_c$$



\* Special cases for nodal voltage method

\* When there is a voltage source between two essential nodes

\* In nodal analysis we use Kcl

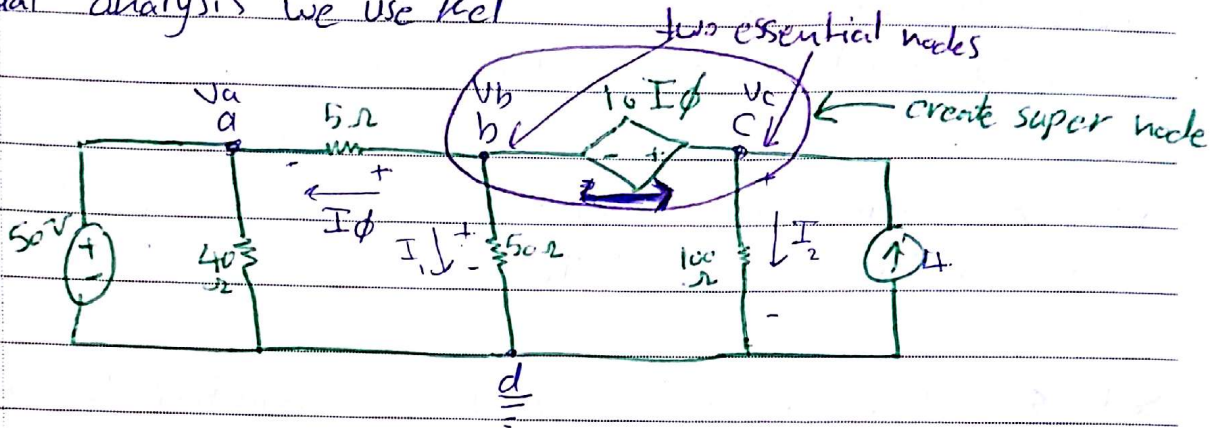

$n = 4$

$n_e = 4$

$m = 2$

$n_e - 1 = 3$  ?

$4 - 2 - 1 = 1$  ?

Kcl node b :-

$-I_\phi - I_1 - I = 0$

$-\frac{V_b - V_a}{5} - \frac{V_b - V_d}{50} - I = 0$

$V_c - V_b = 10 I_\phi$

$I_\phi = \frac{V_b - V_a}{50}$

Kcl node c :-

$+I - I_2 + 4 = 0$

$I = I_2 - 4$

$I = \frac{V_c - V_d}{100} - 4$

⇒ using super node

Kcl

$-I_\phi - I_1 - I_2 + 4 = 0$

$V_c - V_b = 10 I_\phi$

$V_c - V_b = 10 \frac{V_b - V_a}{50}$  (2)

$-\frac{V_b - V_a}{5} - \frac{V_b - V_d}{50} - \frac{V_c - V_d}{100} + 4 = 0$  (1)

$V_b = 60 \text{ V}$
$V_c = 80 \text{ V}$
$I_\phi = 2 \text{ A}$
$I = -3.2 \text{ A}$

## 1.7.2 Electricity Bill

V

- Power Consumption  $W$

- Electricity Utility charge based on energy  
=  $p \cdot \text{time}$

→ power consumed in certain time amount (energy)

200 W → 3 hrs <sup>consumption</sup> → 600 Wh

→ Base charge is a fee for being connected to the grid.

→ The peak hour (usually more money, they charge you).

→ The amount of consumed energy: they have ranges and your price goes up.

They charge you based on

Ex: 200 W VA price 19



Ex 1.9  
Q 19


Consumes 700kwh / in a month

Base rate ~~12~~ \$ 12.00

1st 100 kwh 16 ¢ / kwh

next 200 kwh 10 ¢ / kwh

over 300 kwh 6 ¢ / kwh

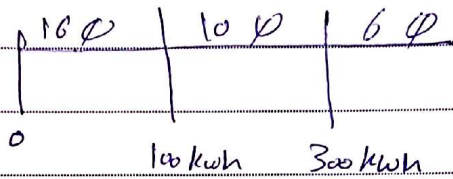


$100 \times 0.16 = \$ 16$

$200 \times 0.1 = \$ 20$

$400 \times 0.06 = \$ 24$

Base  $\frac{\$ 12}{\$ 72}$


2.2 Ohm's law

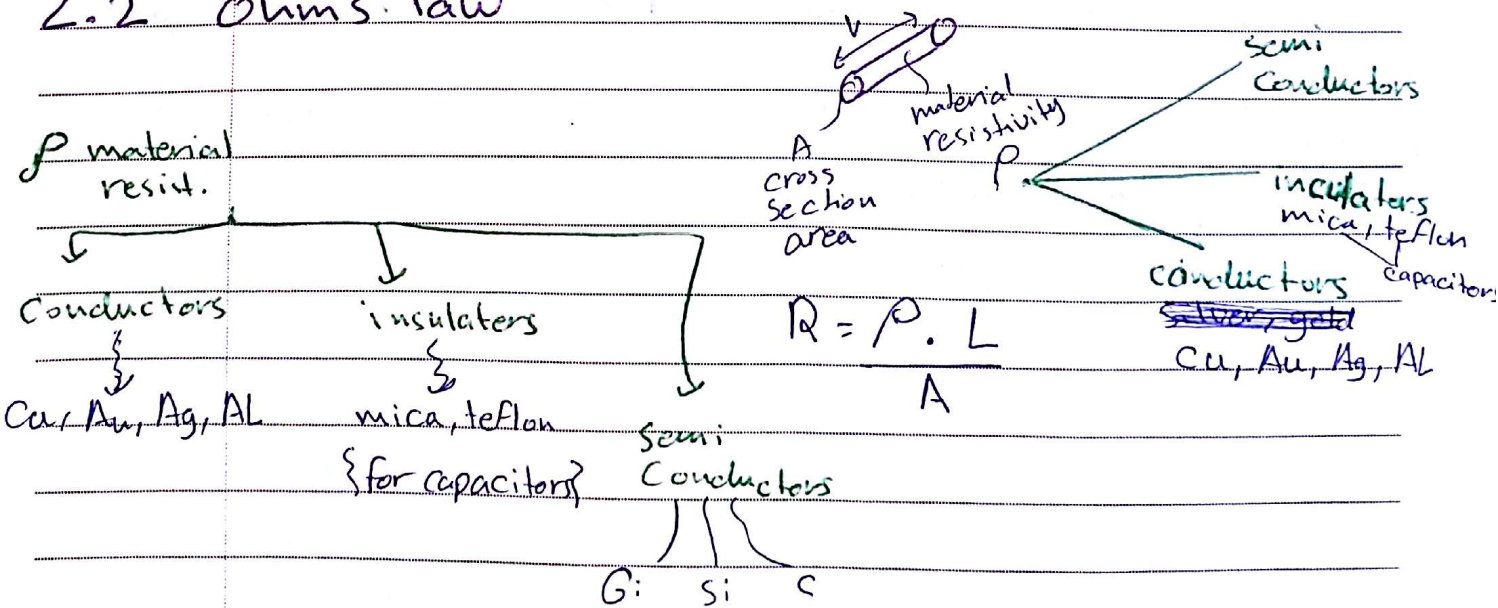

by applying electric field it becomes a conductor.

## 2.7 Wye - Delta Transformation



Network balanced

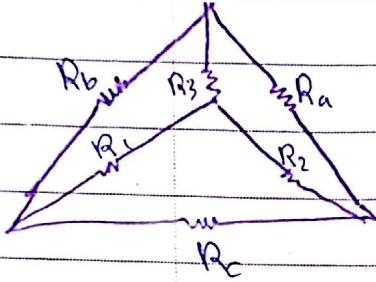


$$R_1 = R_2 = R_3 = R_Y$$

$$R_a = R_b = R_c = R_\Delta$$
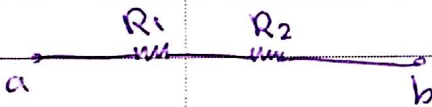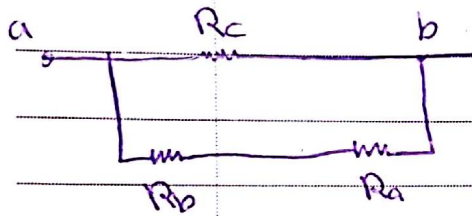
$$R_Y = \frac{R_\Delta}{3} \Rightarrow R_\Delta = 3R_Y$$



## 2.8.1 Lighting System

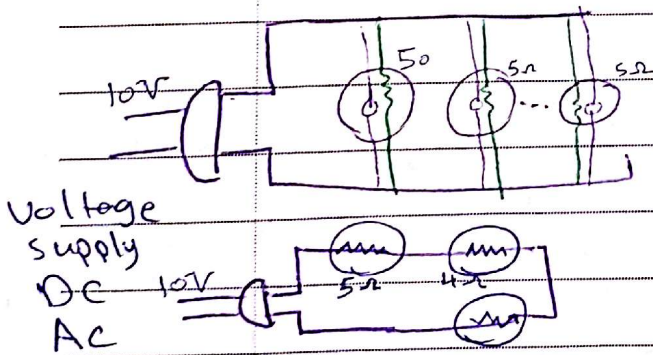


lamp could be defective

open / short



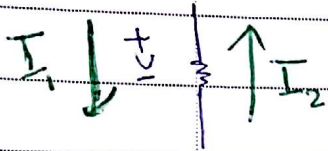
# Mesh Analysis

- ① The independent variables are the Mesh currents
- ② Use KVL  $\sum_{j=1}^n V_j = 0$
- ③ Assign voltage for each branch then state the current flowing through it.



$$R(I_1 - I_2) = V$$

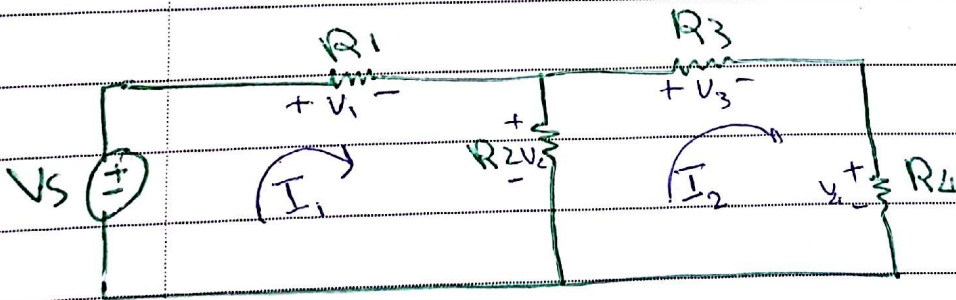- ④ \* of equations = \* of meshes (no current sources in the mesh)  
 $= n - m$  (for circuit with current sources)



KVL mesh #1


$$-V_s + V_1 + V_2 = 0$$

$$-V_s + I_1 R_1 + R_2(I_1 - I_2) = 0$$

KVL mesh #2

$$-V_2 + V_3 + V_4 = 0$$
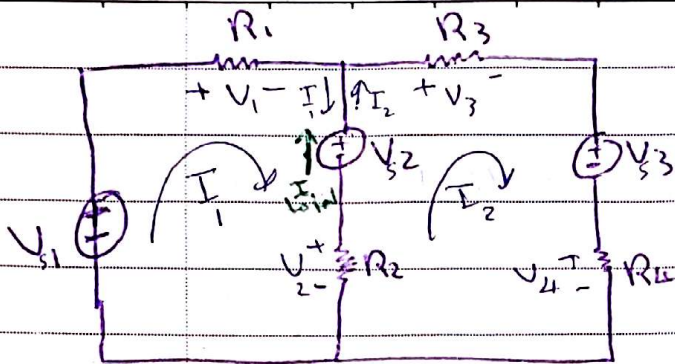
$$-R_2(I_1 - I_2) + I_2 R_3 + I_2 R_4 = 0$$



$$V_1 = 10V$$

$$V_2 = 9V$$

$$V_3 = 1V$$

$$R_1 = 5\Omega$$

$$R_2 = 10\Omega$$

$$R_3 = 5\Omega$$

$$R_4 = 5\Omega$$

$$V_2 = R_2(I_1 - I_2)$$

kVL mesh #1:

$$-V_{s1} + V_1 + V_{s2} + V_2 = 0$$

$$-V_{s1} + R_1 I_1 + V_{s2} + R_2(I_1 - I_2) = 0 \quad \text{--- ①}$$

kVL mesh #2:


$$-V_2 + V_3 + V_4 = 0$$

$$-R_2(I_1 - I_2) + I_2 R_3 + I_2 R_4 = 0$$

$$I_1 = \frac{1}{2} A$$

$$I_2 = 0.65 A$$



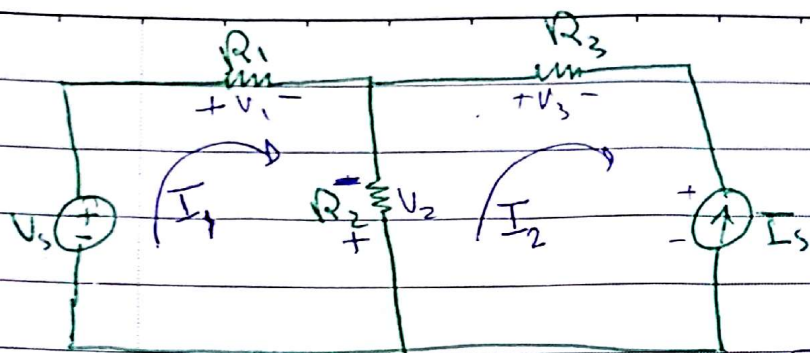

$n = 2$

$m = 1$

$\# \text{ eq} = 2 - 1 = 1$

$$I_2 = -I_s$$

$$V_2 = R_2 (I_2 - I_s)$$


meth  $\times 1$

kvl

$$-V_s + V_1 - V_2 = 0$$

$$-V_s + I_1 R_1 - R_2 (I_2 - I_s) = 0$$

$\downarrow$   
 $-I_s$

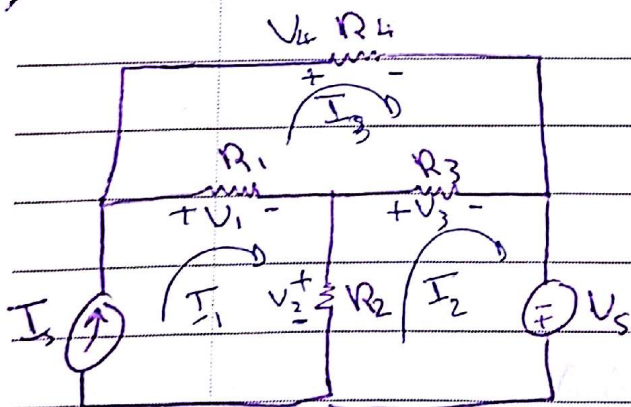

$R_1 = 3 \Omega$

$R_2 = 8 \Omega$

$R_3 = 6 \Omega$

$R_4 = 4 \Omega$

$V_s = 6 \text{ V}$

$I_s = 0.5 \text{ A}$

$$I_3 = I_1$$

$I_2 = ?$

$I_3 = ?$

$$n = 3$$

$$m = 1$$

$$3 - 1 = 2$$

$$V_1 = R_1(I_1 - I_3)$$

$$V_2 = R_2(I_1 - I_2)$$

$$V_3 = R_3(I_2 - I_3)$$

**KVL mesh #2**

$$-V_2 + V_3 - V_5 = 0$$

$$-R_2(I_1 - I_2) + R_3(I_2 - I_3) - V_5 = 0 \quad \text{--- (1)}$$

**KVL mesh #3**

$$+V_4 - V_3 - V_1 = 0$$

$$R_4 I_3 - R_3(I_2 - I_3) - R_1(I_1 - I_3)$$



$$I_2 = 0.95 \text{ A}$$

$$I_3 = 0.55 \text{ A}$$

$V_5$  is supplying power



The Concept of super node Mesh.

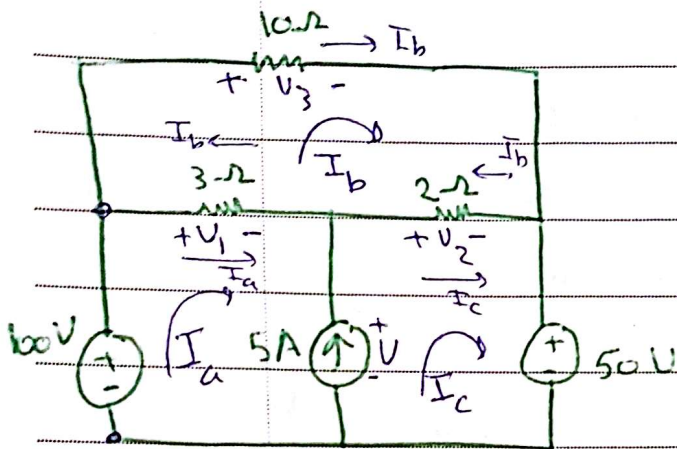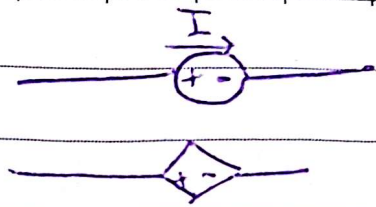

Super mesh:-

$$-100 + V_1 + V_2 + 50 = 0$$

$$V_1 = 3(I_a - I_b)$$

$$-100 + 3(I_a - I_b) + 2(I_c - I_b) + 50 = 0$$

$$V_2 = 2(I_c - I_b)$$

$$V_3 = 10 I_b$$

$$5 = I_c - I_a$$

mesh \*3 :-

$$+V_3 - V_2 - V_1 = 0$$

$$10 I_b - 2(I_c - I_b) - 3(I_a - I_b) = 0$$


$$I_a = 1.75 A$$

$$I_b = 1.25 A$$

$$I_c = 6.75 A$$

No. Applications

Transistor

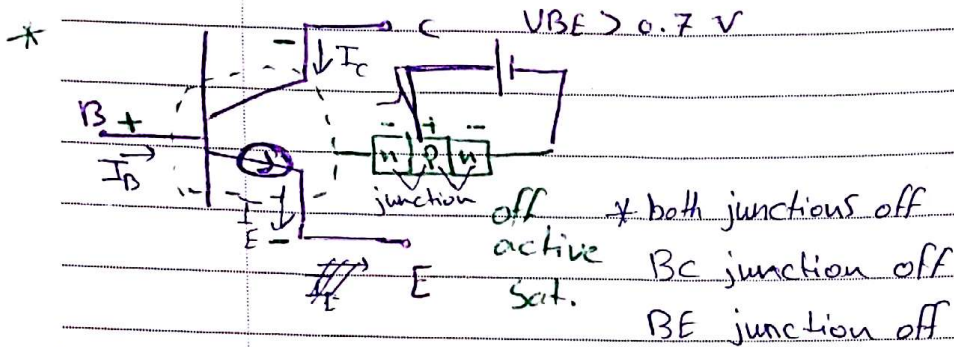

- KCL  $I_B + I_C - I_E = 0$

$I_E = I_B + I_C$




$V_{ab} > 0$

$I_C = \beta I_B$


$\beta = 100, 50$

\* BE junction on } Saturation  
BC junction on }

Example

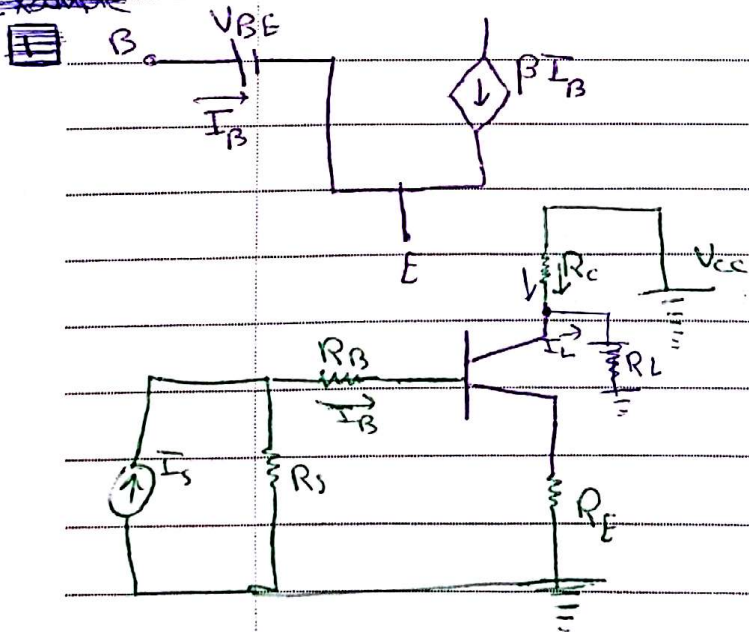



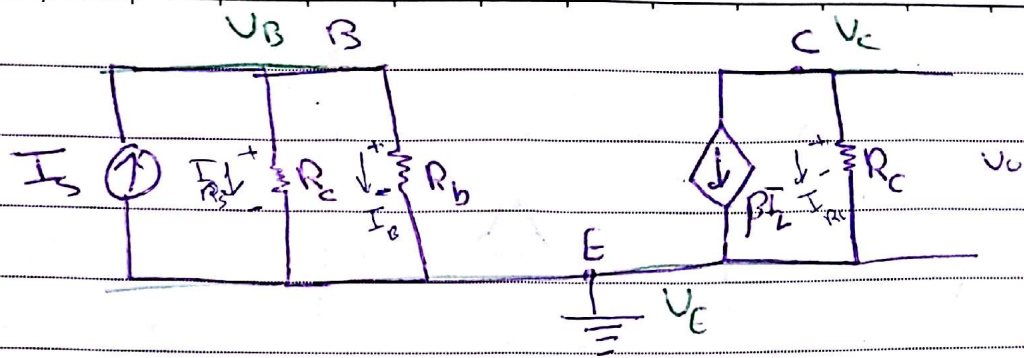

Voltage gain

unknowns $V_B, V_E, V_C$ 

$$\rightarrow n=3 \quad n_e=2$$

$$m=0 \quad 2-1=1$$

$$3-0-1=2$$

→ kcl node B :-

$$+I_s - I_{R_s} - I_B = 0$$

$$I_s - \frac{V_B - V_E}{R_s} - \frac{V_B - V_E}{R_b} = 0$$


→ kcl node c

$$-\beta I_L - I_{R_c} = 0$$

$$-\beta \frac{V_b}{R_b} - \frac{V_c}{R_c} = 0$$



No.

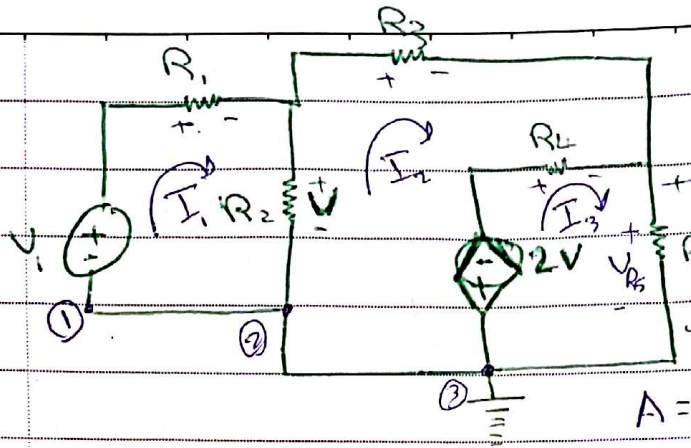

إذا كان التيار عكس  $V_2$

نضع الإشارة سالبة في  $A = -\frac{V_2}{V_1}$

$$R_1 = 1 \Omega \quad R_2 = 0.5 \Omega \quad R_3 = 0.25 \Omega \quad R_4 = 0.25 \Omega \quad R_5 = 0.25 \Omega$$

$A = \frac{V_2}{V_1}$  using mesh Analysis

$$\text{①} \rightarrow -V_1 + V_{R_1} + V = 0 \quad \rightarrow V = R_2(I_1 - I_2)$$

$$-V_1 + R_1 I_1 + R_2(I_1 - I_2) = 0$$

$$\text{②} \rightarrow -V + V_3 - V_4 - 2V = 0$$

$$-R_2(I_1 - I_2) + R_3 I_2 - R_4(I_3 - I_2) - 2R_2(I_1 - I_2) = 0$$

$$\text{③} \rightarrow +2V + V_4 + V_5 = 0$$

$$2R_2(I_1 - I_2) + R_4(I_3 - I_2) + R_5 I_3 = 0$$

$$\begin{bmatrix} R_1 + R_2 & -R_2 & 0 & 0 \\ -3R_2 & 3R_2 + R_3 + R_4 & -R_4 & 0 \\ 2R_2 & -2R_2 - R_4 & R_4 + R_5 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ 0 \\ 0 \end{bmatrix}$$


$$I_1 = 0.88 V_1 \quad I_2 = 0.64 V_1 \quad I_3 = -0.16 V_1 \rightarrow \text{current is reversed as assume}$$

$$A = \frac{V_2}{V_1} = \frac{R_5 I_3}{V_1} = -R_5 (0.16 V_1) / V_1 = -0.04$$

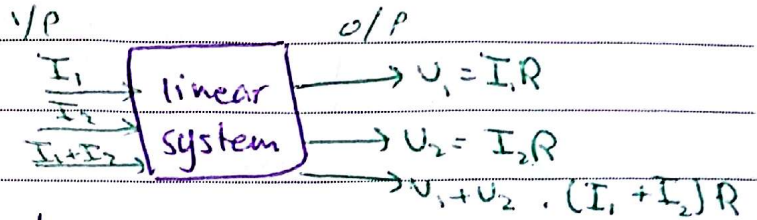
# The principle of super position.

→ depends on the concept of circuit linearity.

Voltage sources  
Current sources } inputs



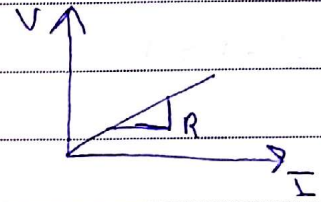
Voltage drop across any branch } output  
Current in any branch }



→ zeroing of

voltage source → short circuit it.

current source → open circuit it.

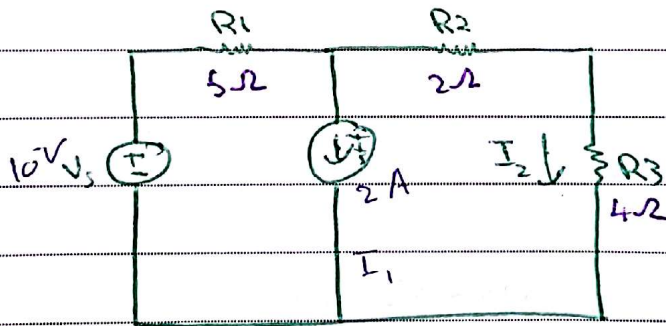



$$I_2 = \frac{V_s}{R_1 + R_2 + R_3} = 0.909 \text{ A}$$

if we removed  $V_s$

$$I_2 = \frac{R_1}{R_1 + R_2 + R_3} I_1 = \frac{5}{5+2+4} \cdot 2 = -0.909 \text{ A}$$

$$I_2 = 0 \text{ A}$$



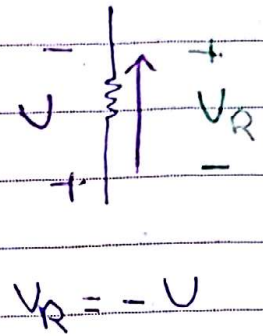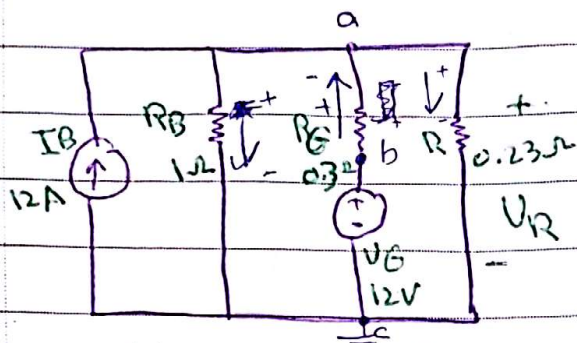

$V_R$ ? superposition method.

$$3 - 1 - 1 = 1$$

$$n_c = 2$$

$$2 - 1 = 1$$

$$V_b = 12 \text{ V}$$

$$V_c = 0 \text{ V}$$

$$V_a = ??$$

KCL ✗

node a:-

$$-I_{R_B} + I_{R_G} - I_R = 0$$

$$-\frac{V_a - V_c}{R_B} + \frac{V_b - V_a}{R_G} - \frac{V_a - V_c}{R} = 0$$

$$V_R = 4.61 \text{ V}$$

if we removed  $V_G$

$$I_R = I_B \cdot \frac{R_{eq}}{R}$$

$$R_{eq} = \frac{1}{\frac{1}{1} + \frac{1}{0.3} + \frac{1}{0.23}}$$

$$= 12 \times \frac{R_{eq}}{0.23}$$



$$V_{R_{I_B}} = 1.38 \text{ V}$$


$$V_{R_{I_B}} + V_{R_{V_G}} = 4.61 + 1.38 = 5.99 \text{ V}$$


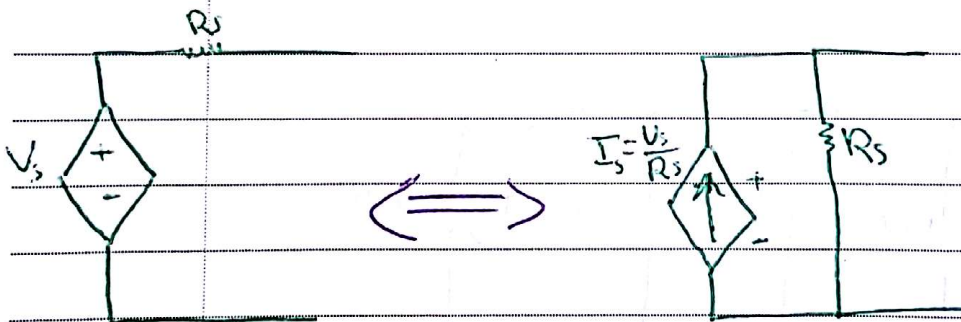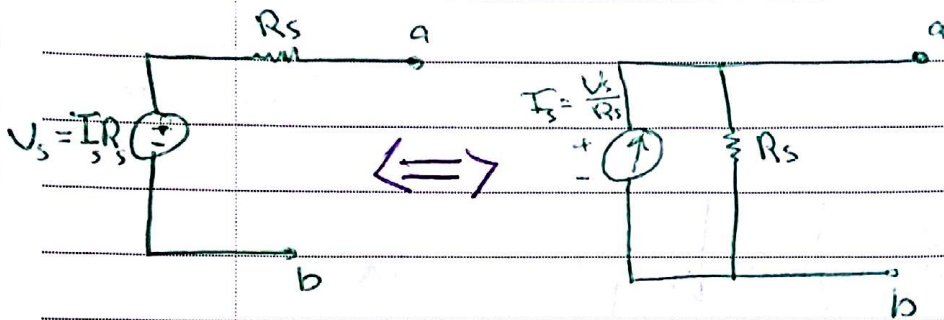
# Source Transformation.

Voltage + Series resistor  $\Rightarrow$  Current + parallel resistance  
dep.  $\swarrow$   $\searrow$  indep.



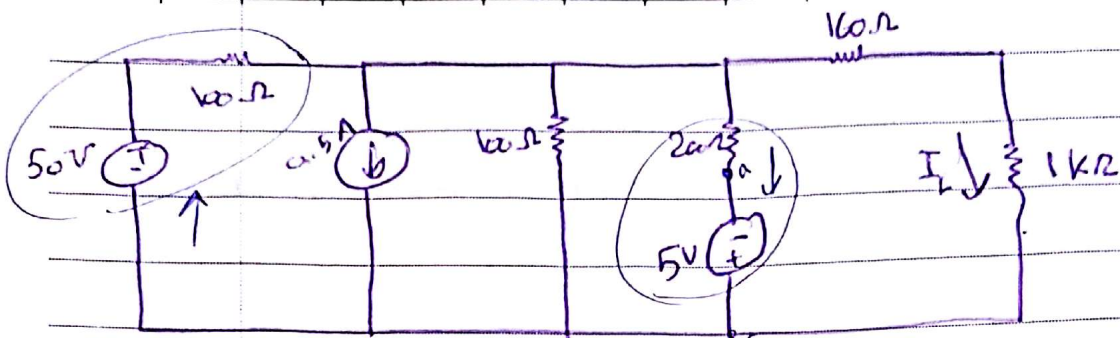




find  $I_L$  using source transform

$$V_{ca} = -5V$$

$$V_c - V_a = 5$$

$$V_a = -5V$$





Sol :-

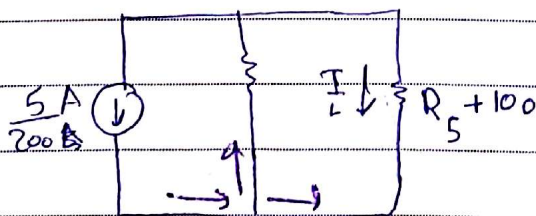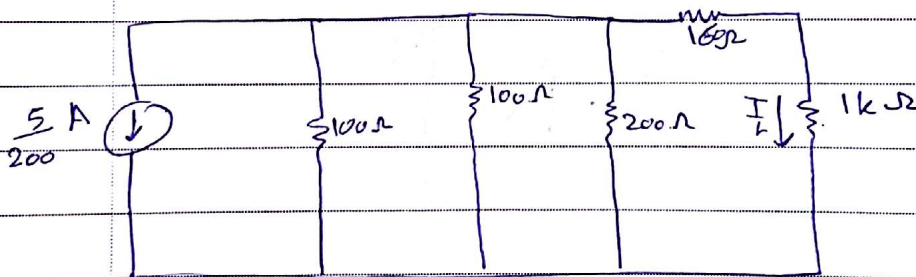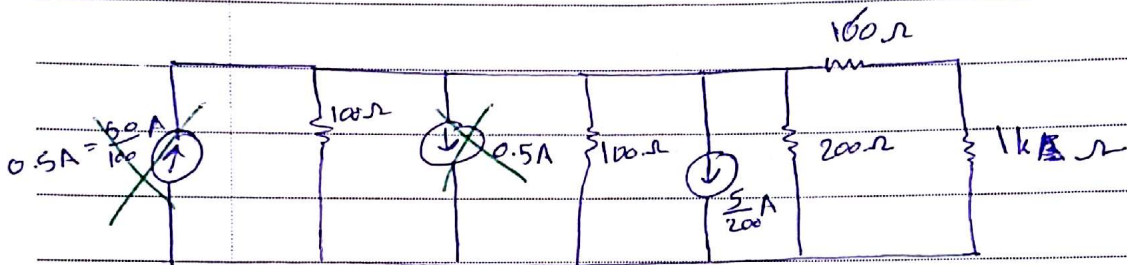

$$I_L = \frac{-40}{1000 + 160 + 40} \cdot \frac{5}{200} = -0.83 \text{ mA}$$


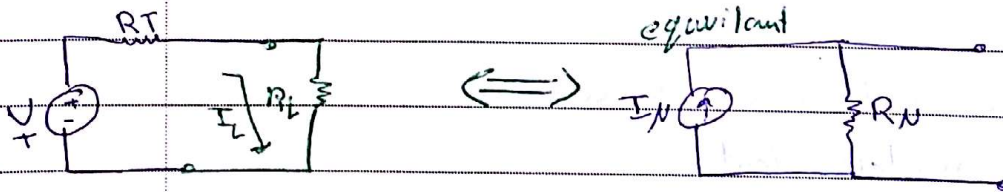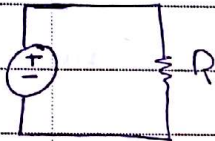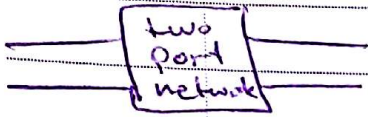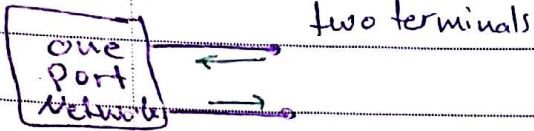
# One port Network $\rightarrow$ Thevenin and Norton equivalence



$$R_N = R_T$$

$$I_N = \frac{V_T}{R_T} = I_{sc}$$

## Purpose

$\rightarrow$  simply analysis for load

$$I_L = \frac{V_T}{R_T + R_L}$$


$\rightarrow$  maximum power transfer

$$R_T = R_L$$





## Norton and Thevenin equivalent.

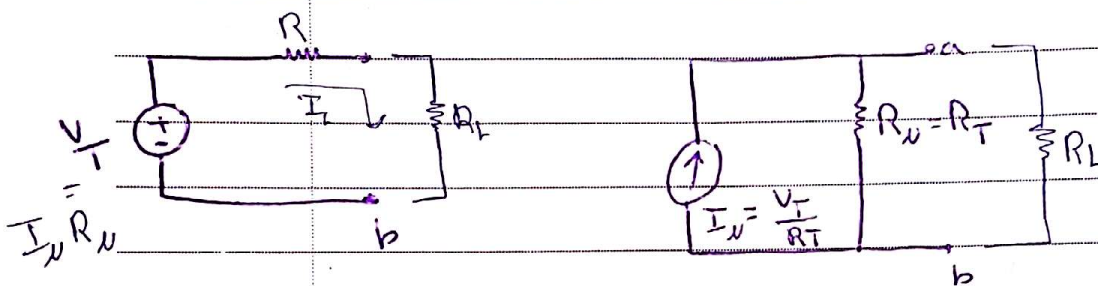

purpose of Thevenin + Norton :-

- ① Simplify the circuit analysis when load is connected
- ② Maximize the power transformed to the load

we use Thevenin + Norton when :-

- ① all sources independent
- ② Mixture of dependent and independent sources
- ③ dependent sources only.

① only independent sources

Thevenin equivalent

Norton eq.

① remove load

① replace the load with short circuit.

② zero all sources

② zero all sources find  $R_{Th}$  when load is away of circuit.



→ open circuit for current source  
→ short " " voltage "

③ find  $R_{Th}$

④ find  $V_{oc}$  (open circuit (oc)) voltage across the terminal where the load exist

③ find short circuit current

$$I_{sh} = I_N$$

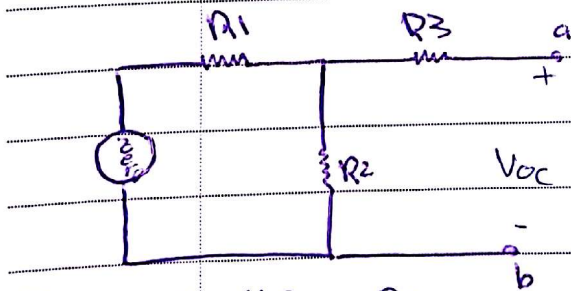
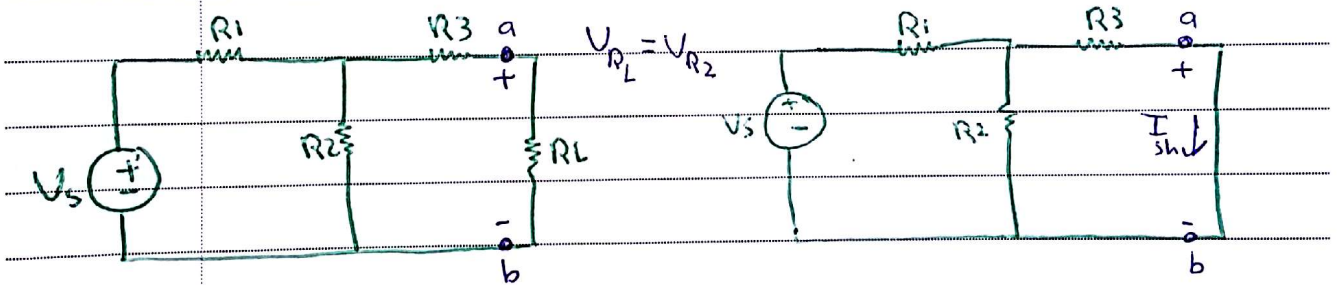


$$3 - 1 - 1 = 2$$

- ① Nodal method
- ② mesh method
- ③ Trans.

$$R_{Th} = R_1 // R_2 + R_3$$
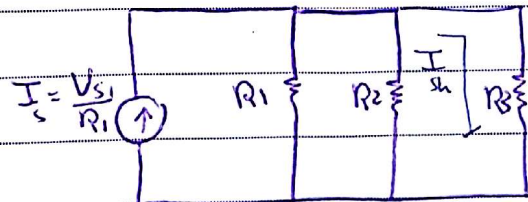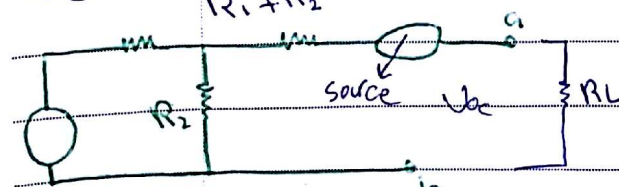
$$V_{oc} = \frac{R_2}{R_1 + R_2} V_{s1}$$



$$\text{Current division} = \frac{R_2}{R_3} I_s$$


Mesh  $V_{R1} \neq V_{R2}$  ل source ال loop و نكاد العمل

④ توالي و توازي

$$-V_{oc} + V_{R3} + V_{R2} = 0$$



Ex 0

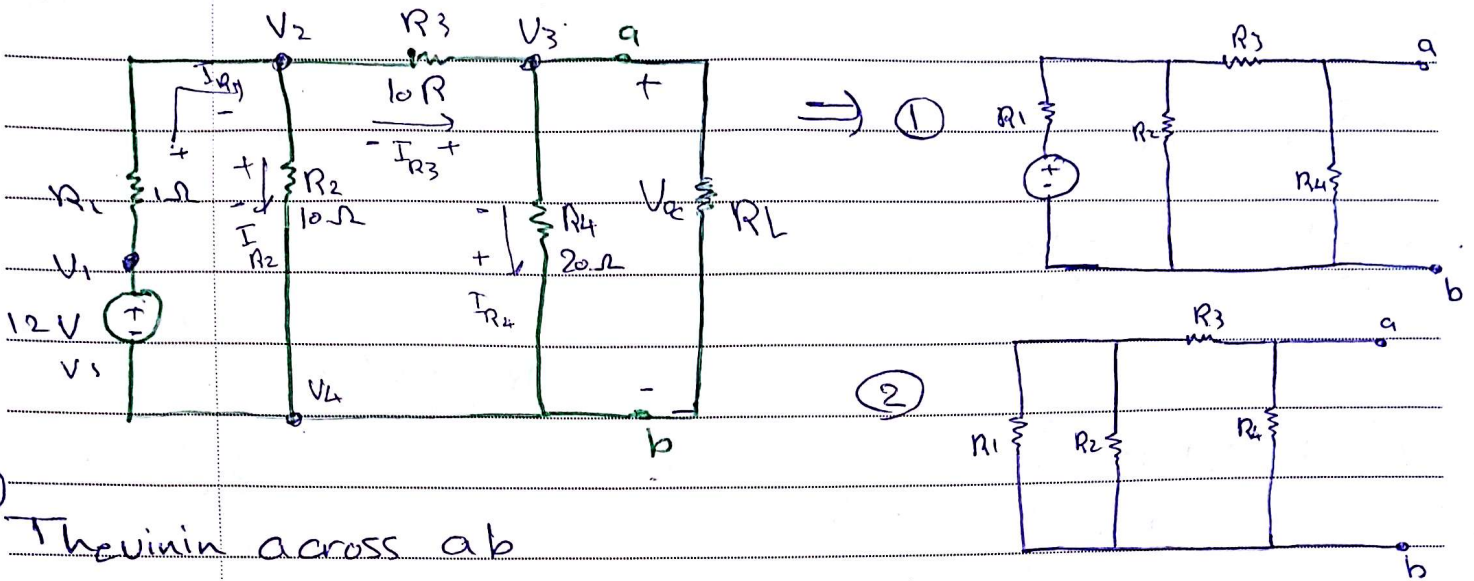


③ Thevenin across ab

$$R_{Th} = (R_1 // R_2 + R_3) // R_4$$

at last it will become like this.

Voc ?!

$$V_{oc} = V_{R4}$$

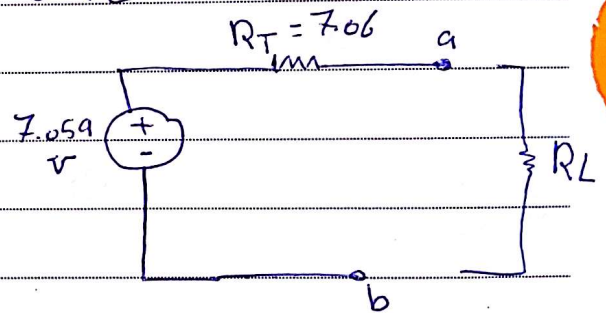

(using nodal voltage method) :-

$$n = 4$$

$$m = 1$$

$$4 - 1 - 1 = 2$$

$$V_1 = 12V$$

node 2 :-

$$+I_{R1} - I_{R2} - I_{R3} = 0$$

$$\frac{V_1 - V_2}{R_1} - \frac{V_2 - V_4}{R_2} - \frac{V_2 - V_3}{R_3} = 0 \quad \text{--- (1)}$$



node 3 is



lecl

$$+I_{R3} - I_{R4} = 0$$

$$\frac{V_2 - V_3}{R_3} - \frac{V_3 - V_4^0}{R_4} = 0$$


$$\begin{aligned} V_2 &= 10.59 \text{ V} \\ V_3 &= 7.059 \text{ V} \end{aligned}$$

⇒

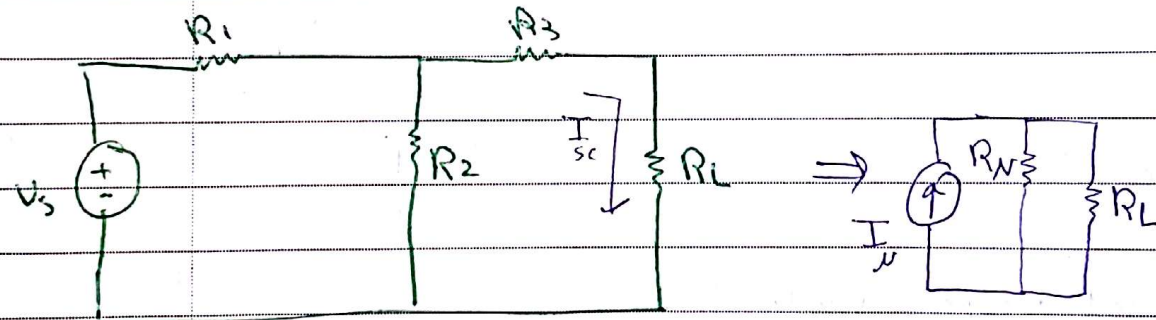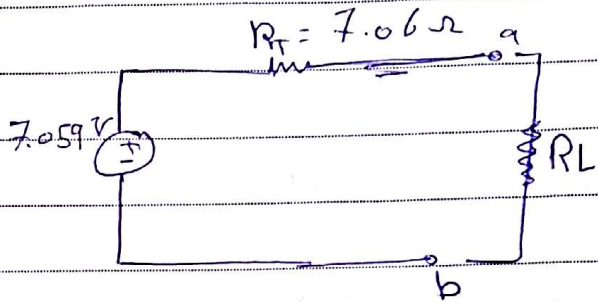


$I_N, R_N$  ?!

$$R_N = (R_1 // R_2) + R_3$$

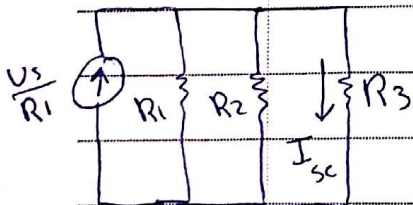

$$I_N = I_{sc} = \frac{R_2}{R_2 + R_3} \cdot \frac{V_s}{R_1}$$

making an open circuit in the first step

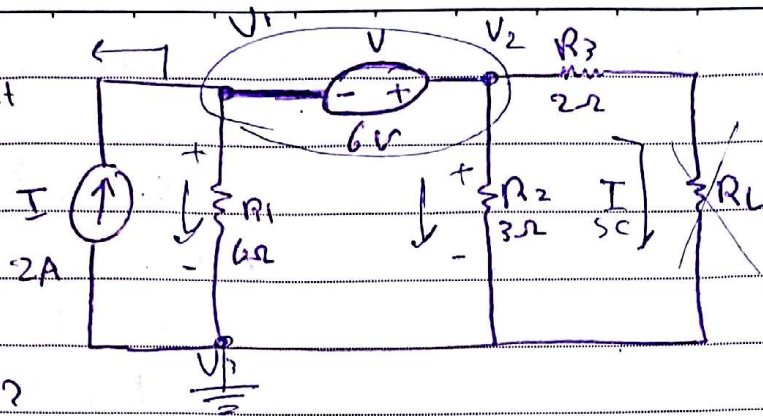

removing the load in the first step

Find  $I_N$ ?  
 $R_N$ ?

$$R_N = (R_1 \parallel R_2) + R_3$$

kcl supernode:-

$$+I - I_{R_1} - I_{R_2} - I_{sc} = 0$$


$$2 - \frac{V_1}{R_1} - \frac{V_2}{R_2} - \frac{V_2}{R_3} = 0$$

$$V_2 - V_1 = 6$$

$$V_2 = 3V$$

$$V_1 = -3V$$
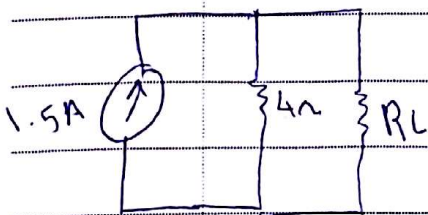
$$I_{R_1} = 2.5A, \quad I_{sc} = 1.5A, \quad R_N = 4\Omega$$





## ② Combined dependent and Independent sources

Regular way to find

$$V_{oc}, I_{sc}$$

find  $R_{Th}$  using

$$R_{Th} = \frac{V_{oc}}{I_{sc}}$$

alternative way

① Include a voltage test



source  $V_T$  which supplies the test current

$$I_T$$

② Zeroing all independent sources.

$$③ R_{Th} = \frac{V_T}{I_T}$$

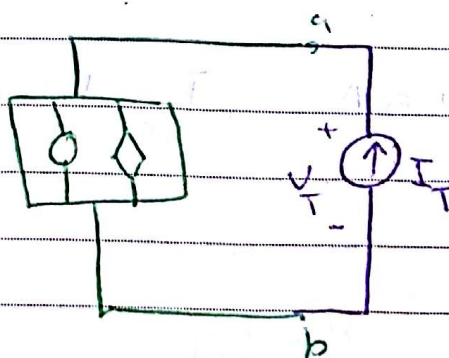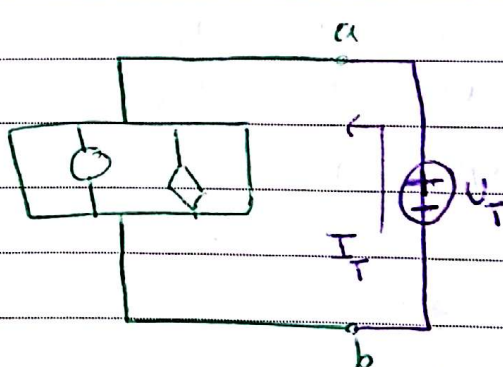④ find  $V_{oc}$  or  $I_{sc}$  using Regular way.






III) only dependent sources.

→ we can find only  $R_{Th}$  using alternative scheme.

Example 9

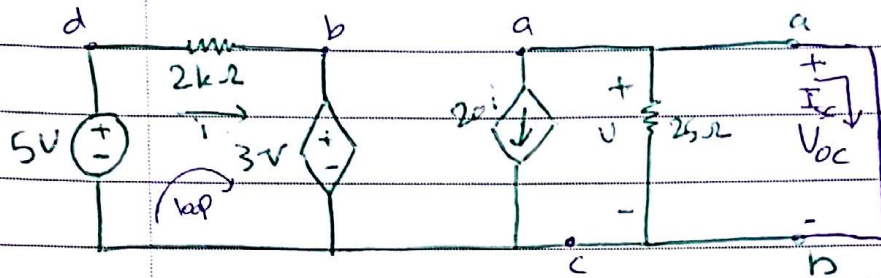

i)

$$-V_{oc} + V = 0$$

$$V_{oc} = V$$

ii)  $I_{sc} = -20i \Rightarrow$  node c

$$-5 + 2000i = 0$$

kcl node c:-

$$+20i + \frac{V}{25} = 0$$

$$I_{sc} = -50 \text{ mA}$$

$$20i = -\frac{V}{25}$$


$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{-5}{-50 \text{ m}} = 100 \Omega$$


$$i = -\frac{V}{500}$$

kul in the loop:-

$$-5 + 2000i + 3V = 0$$

$$V = -5 \text{ V}$$

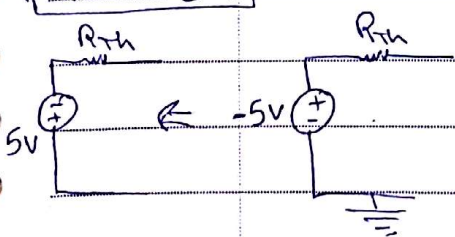

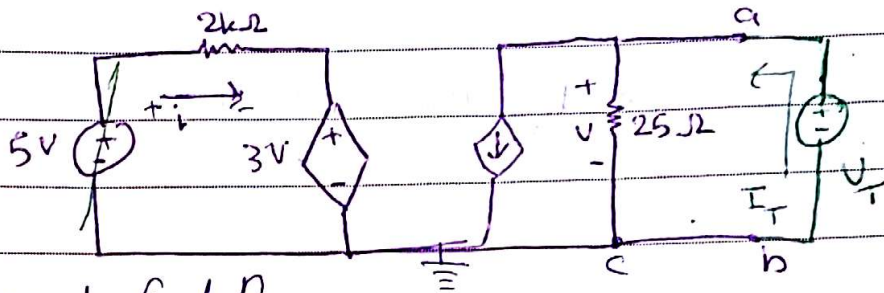

alternative way to find  $R_{Th}$

$$U_T = V_T$$

kcl at c :

$$+20i + \frac{V}{25} - I_T = 0$$

$$I_T = 20 + \frac{V}{25} \quad \text{--- (I)}$$

$$2000i + 3V_T = 0$$

$$2000i + 3V_T = 0$$

$$i = -\frac{3}{2000} \frac{V_T}{T}$$

going back to (I)




$$I_T = 20i + \frac{V_T}{25}$$

$$I_T = 20 \left( -\frac{3}{2000} \frac{V_T}{T} \right) + \frac{V_T}{25}$$



$$\frac{V_T}{I_T} = 100 \Omega$$



No. \_\_\_\_\_

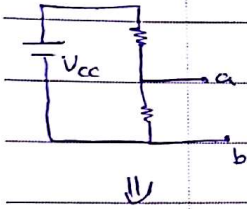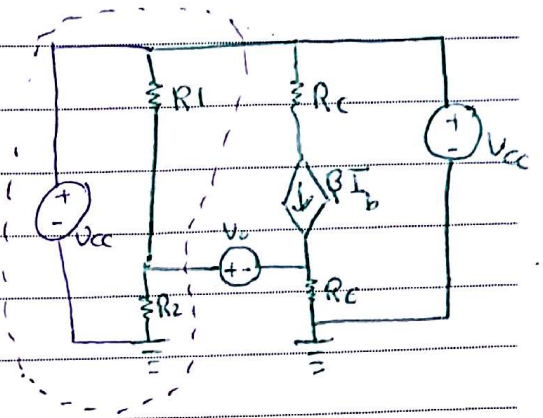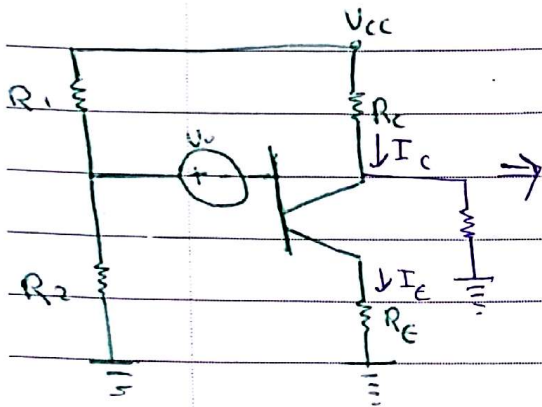

find  $I_B$  ?

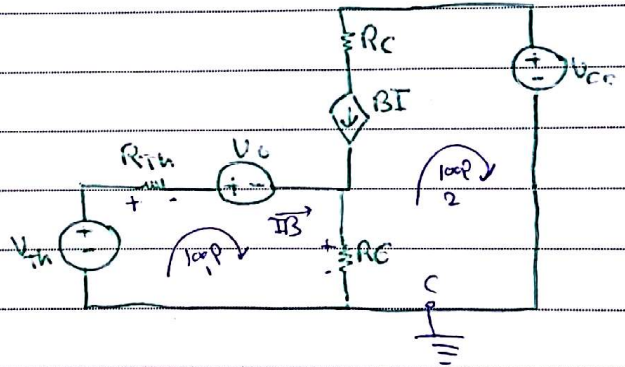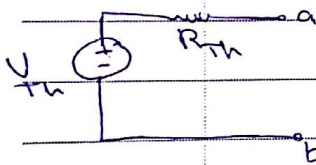

$$V_{Th} = \frac{R_2}{R_1 + R_2} V_{cc}$$

$$R_{Th} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

loop ① :-

$$-V_{Th} + R_{Th} I_B + V_0 + I_E R_E = 0$$

kcl at node c :-


$$+I_B + \beta I_B - I_E = 0$$

$$(1 + \beta) I_B = I_E$$


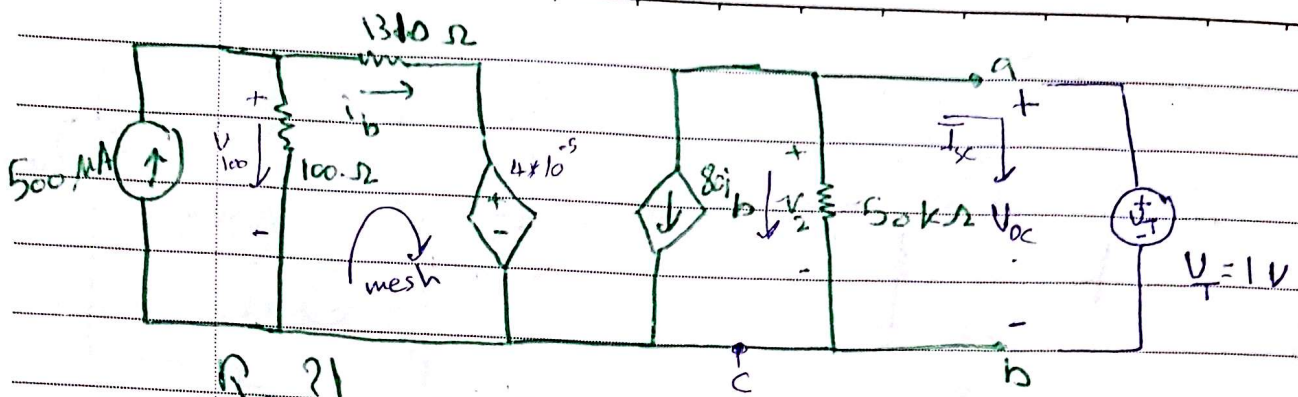
$$I_B = \frac{V_{cc} R_2 - V_0}{R_1 R_2 + R_E (1 + \beta)}$$



without  $V_T$ with  $V_T$ 

KCL at node c :-

$$80 i_b + \frac{V_2}{50000} = 0$$

$$0.5 \times 10^{-3} - \frac{V}{100} - i_b = 0$$

$$-V + 1310 i_b + 4 \times 10^{-5} V_2 = 0$$

$$V_2 = -50000 \times 80 i_b$$

$$V_2 = -160 V$$


$$V_{oc} = -160 V$$

$$\frac{I}{I_{sc}} = -80 i_b$$

$$i_b = \frac{100}{100 + 1310} \times 0.5 \times 10^{-3} = 35.461 \mu A$$

$$R_{Th} = 56.4 k\Omega$$

# Maximum Power Transfer

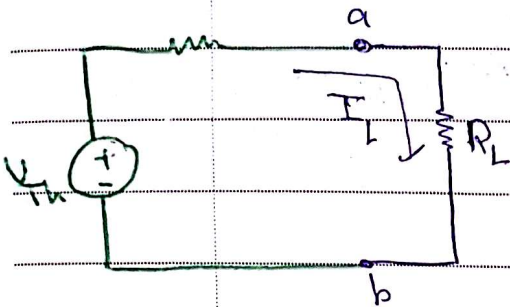

$$I_L = \frac{V_{Th}}{R_L + R_{Th}}$$

→ power dissipated in  $R_L$

$$P = I_L^2 R_L$$

$$= \left( \frac{V_{Th}}{R_L + R_{Th}} \right)^2 R_L$$

to maximize  $P$

$$\frac{dP}{dR_L} = \frac{d}{dR_L} \left[ R_L V_T^2 (R_L + R_{Th})^{-2} \right]$$

$$= V_T^2 \cdot \left[ R_L (-2)(R_L + R_{Th})^{-3} + (R_L + R_{Th})^{-2} \cdot 1 \right]$$

$$= V_T^2 \left[ \frac{-2R_L}{(R_L + R_{Th})^3} + \frac{1}{(R_L + R_{Th})^2} \right] = 0$$



$$\frac{dP_L}{dR_L} = \frac{V_T^2}{(R_L + R_{Th})^3} [-2R_L + (R_L + R_{Th})] = 0$$

$$V_T \neq 0$$

$$(R_L + R_{Th}) \neq 0$$

$$-2R_L + (R_L + R_{Th}) = 0$$

$$2R_L = R_L + R_{Th}$$

$$R_L = R_{Th}$$



Determine the increase in power delivered to a loud speaker when matching it's resistance to an amplifier equivalent resistor?

Assuming amp. is linear (amp. has resistor load)

$$R_{Th} = 8 \Omega$$

$$R_{LU} = 16 \Omega \text{ (load unmatched)}$$
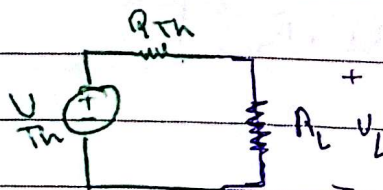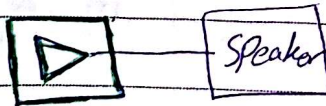
$$R_{Lm} = 8 \Omega \text{ (match resistance of the load)}$$





No. \_\_\_\_\_

$$V_L = \frac{R_L}{R_L + R_{Th}} \cdot V_{Th}$$

$$P_L = \frac{V_L^2}{R_L}$$


$$P_L = \frac{\left(\frac{R_L}{R_{Th} + R_L}\right)^2 V_{Th}^2}{R_L}$$

$$P_{L1} = \frac{\left(\frac{16}{8+16}\right)^2 V_{Th}^2}{16} = 0.0278 V_{Th}^2$$

$$P_{L2} = \frac{\left(\frac{8}{8+8}\right)^2 V_{Th}^2}{8}$$

$$= 0.03125 V_{Th}^2$$

percentage of the increase  $\frac{0.03125 V_{Th}^2 - 0.0278 V_{Th}^2}{0.0278 V_{Th}^2} = 12.5\%$

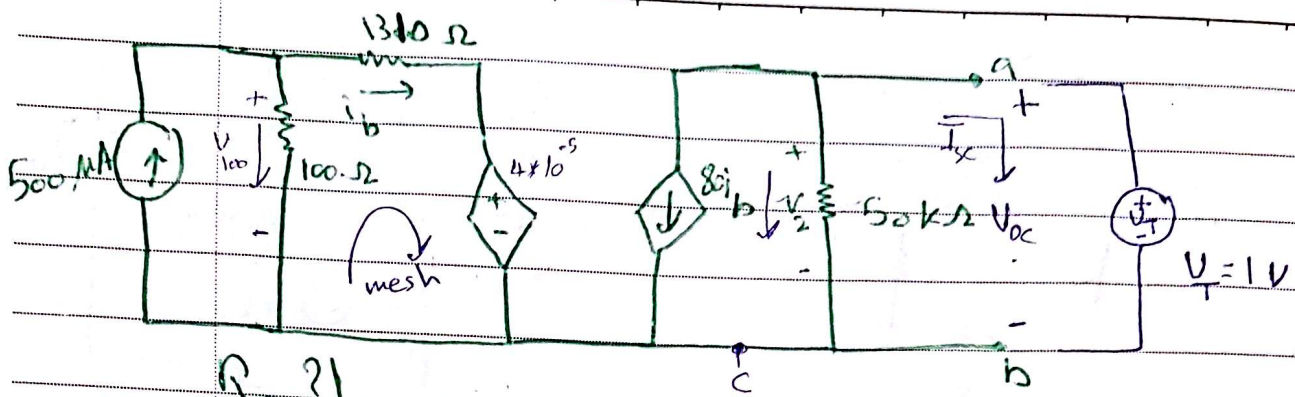without  $V_T$ with  $V_T$ 

KCL at node c :-

$$80 i_b + \frac{V_2}{50000} = 0$$

$$0.5 \times 10^{-3} - \frac{V}{100} - i_b = 0$$

$$-V + 1310 i_b + 4 \times 10^{-5} V_2 = 0$$

$$V_2 = -50000 \times 80 i_b$$

$$V_2 = -160 V$$


$$V_{oc} = -160 V$$

$$\frac{I}{I_{sc}} = -80 i_b$$

$$i_b = \frac{100}{100 + 1310} \times 0.5 \times 10^{-3} = 35.461 \mu A$$

$$R_{Th} = 56.4 k\Omega$$

# Maximum Power Transfer

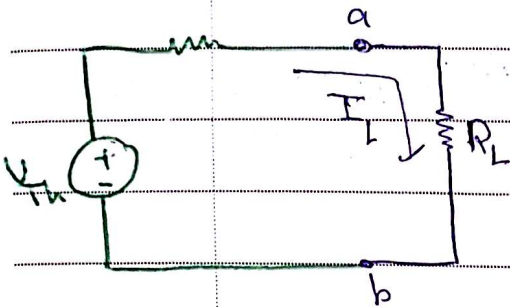

$$I_L = \frac{V_{Th}}{R_L + R_{Th}}$$

→ power dissipated in  $R_L$

$$P = I_L^2 R_L$$

$$= \left( \frac{V_{Th}}{R_L + R_{Th}} \right)^2 R_L$$

to maximize  $P$

$$\frac{dP}{dR_L} = \frac{d}{dR_L} \left[ R_L V_T^2 (R_L + R_{Th})^{-2} \right]$$

$$= V_T^2 \cdot \left[ R_L (-2)(R_L + R_{Th})^{-3} + (R_L + R_{Th})^{-2} \cdot 1 \right]$$

$$= V_T^2 \left[ \frac{-2R_L}{(R_L + R_{Th})^3} + \frac{1}{(R_L + R_{Th})^2} \right] = 0$$



$$\frac{dP_L}{dR_L} = \frac{V_T^2}{(R_L + R_{Th})^3} [-2R_L + (R_L + R_{Th})] = 0$$

$$V_T \neq 0$$

$$(R_L + R_{Th}) \neq 0$$

$$-2R_L + (R_L + R_{Th}) = 0$$

$$2R_L = R_L + R_{Th}$$

$$R_L = R_{Th}$$



Determine the increase in power delivered to a loud speaker when matching it's resistance to an amplifier equivalent resistor?

Assuming amp. is linear (amp. has resistor load)

$$R_{Th} = 8 \Omega$$

$$R_{LU} = 16 \Omega \text{ (load unmatched)}$$
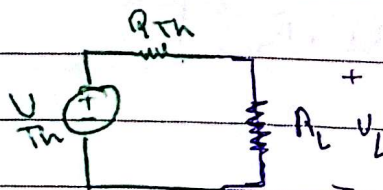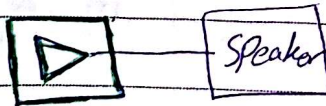
$$R_{Lm} = 8 \Omega \text{ (match resistance of the load)}$$



No. \_\_\_\_\_

$$V_L = \frac{R_L}{R_L + R_{Th}} \cdot V_{Th}$$

$$P_L = \frac{V_L^2}{R_L}$$

$$P_L = \left( \frac{R_L}{R_{Th} + R_L} \right)^2 \frac{V_{Th}^2}{R_L}$$

$$P_{L1} = \frac{\left( \frac{16}{8+16} \right)^2 V_{Th}^2}{16} = 0.0278 V_{Th}^2$$

$$P_{L2} = \frac{\left( \frac{8}{8+8} \right)^2 V_{Th}^2}{8}$$

$$= 0.03125 V_{Th}^2$$

percentage of the increase  $\frac{0.03125 V_{Th}^2 - 0.0278 V_{Th}^2}{0.0278 V_{Th}^2} = 12.5\%$



# Ac Network Analysis



in Dc regime

- ① resistors
- ② sources

Ac } regimes  
Dc }

when we have  
R, c, L

→ passive elements  
R, c, L

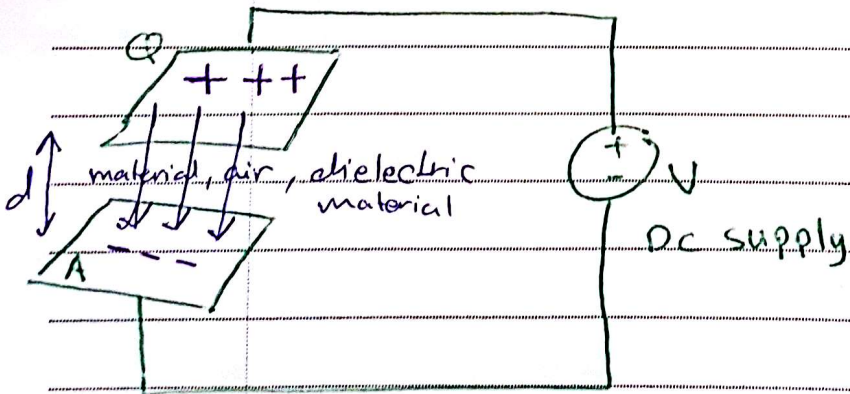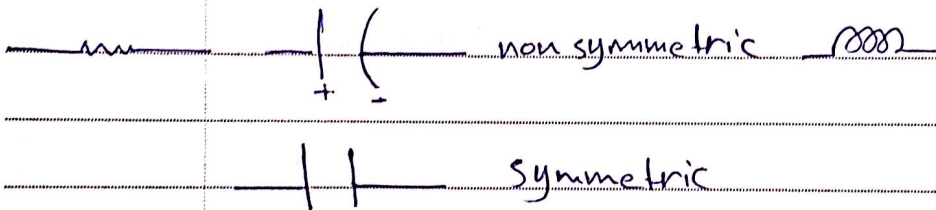

$$Q = CV$$


$$C = \frac{\epsilon A}{d} \quad [F] \text{ Farad}$$

permittivity of material

$$i = \frac{dq}{dt} = 0 \text{ A}$$



when source is Dc, charge is constant



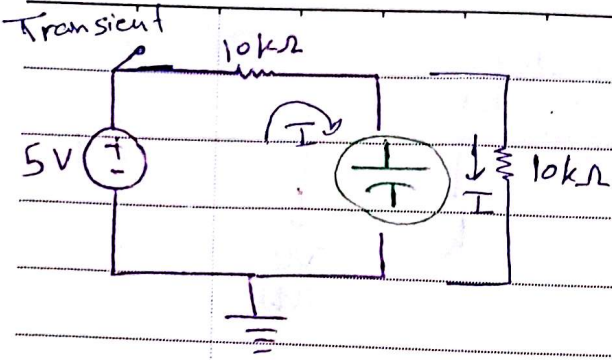

$$I = \frac{5}{10k + 10k}$$

$$= 0.2 \text{ mA}$$

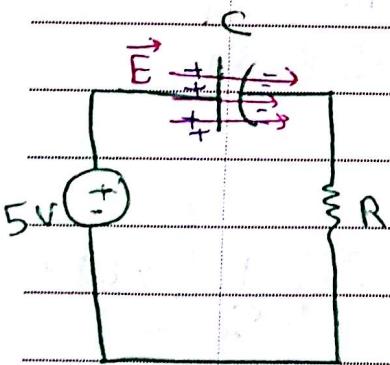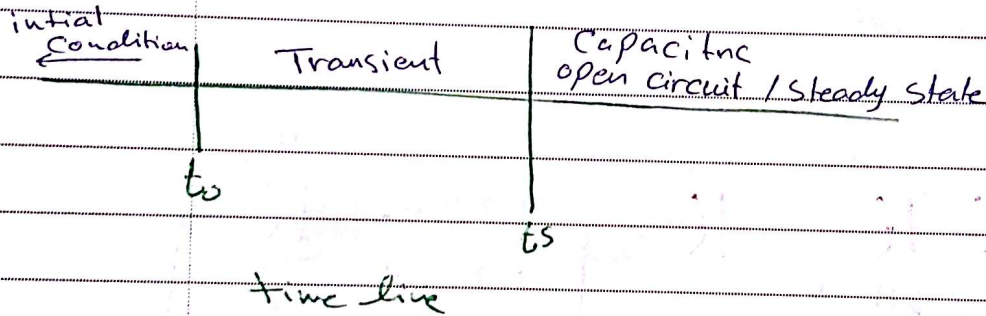


$$Q = CV \quad \uparrow \quad \bar{C}$$

$$i = \frac{dq}{dt}$$


i.

$$i(t) = \frac{d(V(t))}{dt}$$

$$i(t) = C \frac{dV(t)}{dt}$$

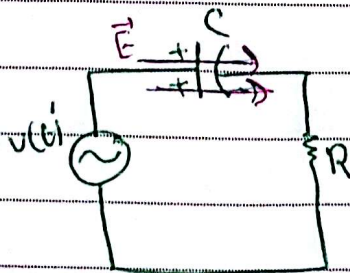
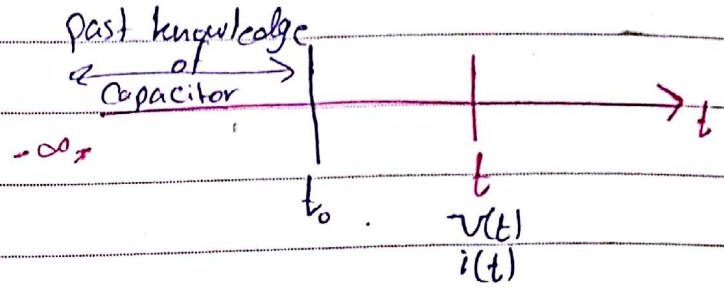
$$V(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt$$




$$v(t) = \frac{1}{C} \int_{-\infty}^t i(t') dt'$$

$$= \boxed{\frac{1}{C} \int_{-\infty}^{t_0} i(t') dt'} + \frac{1}{C} \int_{t_0}^t i(t') dt'$$

initial condition
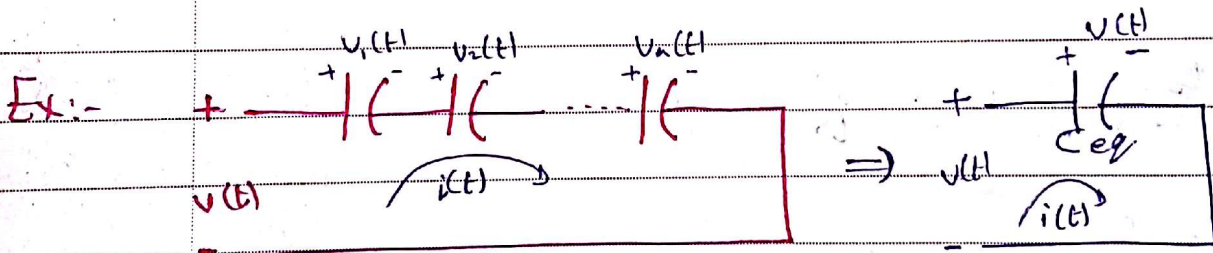
$$v(t) = V_0 + \frac{1}{C} \int_{t_0}^t i(t') dt'$$





$$v(t) = v_1(t) + v_2(t) + \dots + v_n(t)$$

$$\frac{1}{C_{eq}} \int_{-\infty}^t i(t') dt' = \frac{1}{C_1} \int_{-\infty}^t i_1(t') dt' + \frac{1}{C_2} \int_{-\infty}^t i_2(t') dt' + \dots + \frac{1}{C_n} \int_{-\infty}^t i_n(t') dt'$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \quad \dots \text{Same to resistors in parallel.}$$



Ex:-

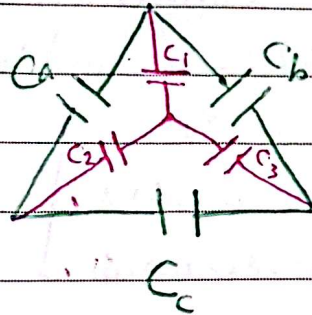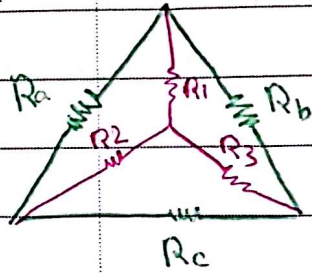 $\Delta \rightarrow Y$ 

$$R_1 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$C_1 = \frac{C_a C_b + C_a C_c + C_b C_c}{C_c}$$

 $Y \rightarrow \Delta$ 

$$R_c = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

\* Calculate the charge stored in an ultraCapacitor, how long it will take to discharge the capacitor at minimum current rate.

- capacitor 100F (±10% - 30%)

- series resistance (DC) 15 mΩ ±25%

(AC) at 1k Hz 7 mΩ ±25%

Voltage continuous 2.5 V, peak 2.7 V

current rated 25A

$$Q = CV$$

$$= 100 \times 2.5$$

$$= 250 \text{ C}$$

$$\Delta t = \frac{250}{25} = 10 \text{ Sec.}$$





Calculate current flow through a capacitor

$$V(t) = 5(1 - e^{-t/10^{-6}}) \text{ V} \quad t \geq 0 \text{ Sec.}$$

$$C = 0.1 \mu\text{F}$$

اذا كان ثابت فلا يوجد تيار مستمر غيره  
اذا كان متغير فلا يوجد تيار مستمر غيره.

Sol:-

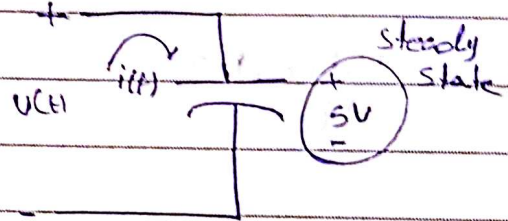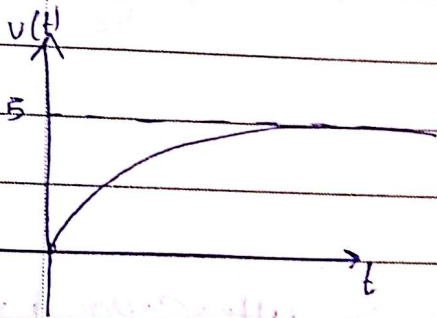


$$i(t) = C \frac{dV(t)}{dt}$$

$$= 0.1 \times 10^{-6} \frac{d}{dt} [5 - 5e^{-t/10^{-6}}]$$

$$= 0.1 \times 10^{-6} \left[ -5 \left( \frac{-1}{10^{-6}} \right) e^{-t/10^{-6}} \right]$$

$$= 0.5 e^{-t/10^{-6}} \quad t \geq 0$$

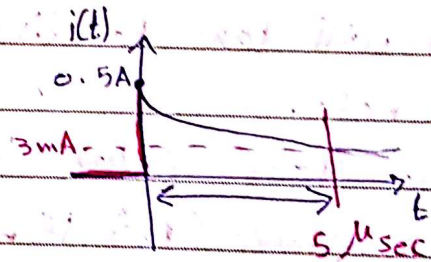



$$i(15) = 0.003 \text{ A}$$

$$= 3 \text{ mA}$$

Max charge stored in capacitor


$$Q_{\text{max}} = C V_{\text{max}} = 0.1 \times 10^{-6} \times 5 = 0.5 \mu\text{C}$$

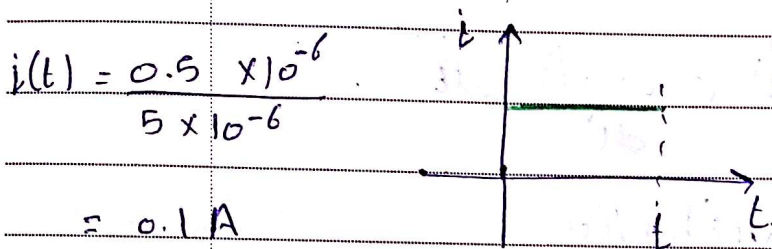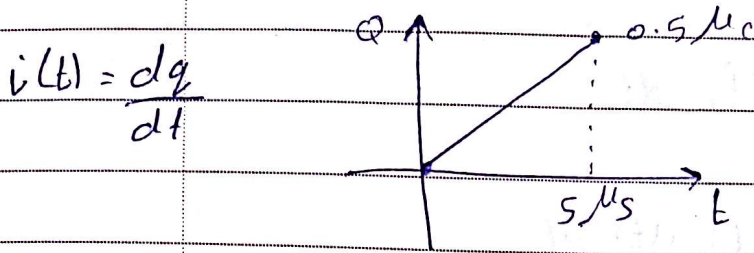- within  $5 \mu s$  assuming charge increased to max value, find current flowing in the capacitor



find voltage across the capacitor from the current flowing through it given that  $V_c(t) = 2 V$  at  $t=0$

$C = 1000 \mu f$

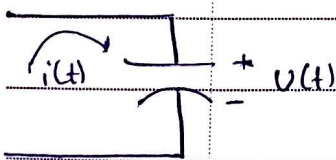



$$i_c(t) = \begin{cases} 0 & t < 0 \text{ sec} \\ 10 \text{ mA} & 0 \leq t \leq 1 \\ 0 & t > 1 \end{cases}$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(t) dt + \frac{v_0}{1}$$

$$= \frac{1}{10^{-3}} \int_0^t 10^{-2} dt + 2$$

$$= 10^3 \cdot 10^{-2} t + 2$$

$$= 10t + 2$$

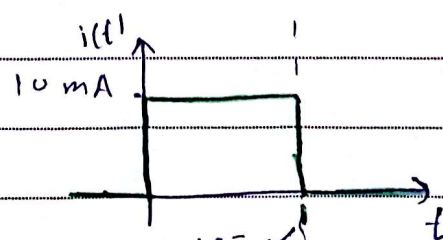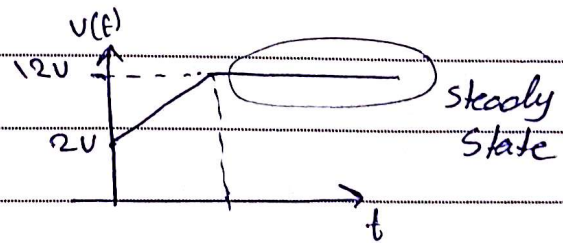

تحويل إلى SI  
Constant ← V  
Current ← A



$$p = \frac{dw}{dt}$$

$$p = v(t) \cdot i(t)$$

$$W(t) = \int_{-\infty}^t p(t) dt$$

$$= \int v(t) i(t) dt$$

$$= \int v(t) c \frac{dv(t)}{dt} dt$$

$$= c \int v(t) dv(t)$$



$$= \frac{1}{2} c v(t)^2 + \text{const}$$

$$W_{\max} = \text{Steady State } W = \frac{1}{2} c v^2$$

C




## Inductors

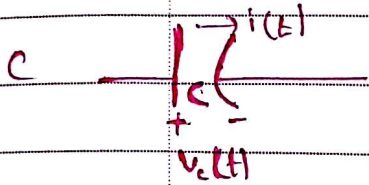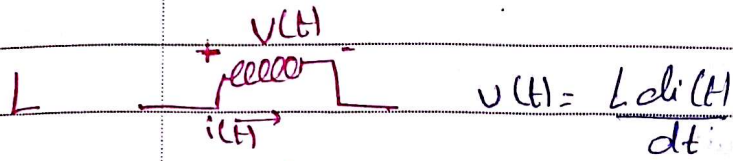

$$i(t) = C \frac{dv(t)}{dt}$$

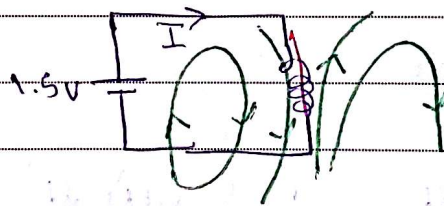- The ideal inductor  $v(t) = L \frac{di}{dt}$
- No resistance for the coil
- practical coil  $\Rightarrow$   $r_m$



## Faraday's Law:-

$$v_L = \frac{d\lambda}{dt}$$

$$v = \frac{d}{dt} N \rho i$$

$\lambda =$  magnetic flux



$$= \frac{N^2 \rho}{L} \frac{di}{dt}$$

$\lambda = N \phi$   $N$  # of turns

$$\lambda = \mu \rho N^2 i$$

$\uparrow$   
permeance

# DC analysis

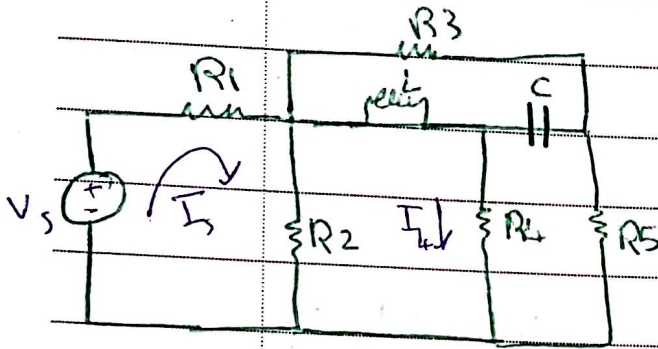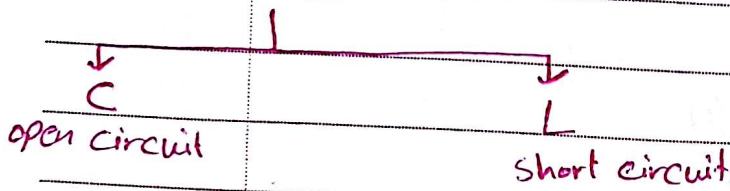

$L \equiv$  inductance is measured in Henry (H).


$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v(t') dt'$$

$$= \frac{1}{L} \int_{-\infty}^{t_0} v(t') dt' + \frac{1}{L} \int_{t_0}^t v(t') dt'$$

initial condition

$$i_L(t) = I_0 + \frac{1}{L} \int_{t_0}^t v_L(t') dt'$$



## duality concept

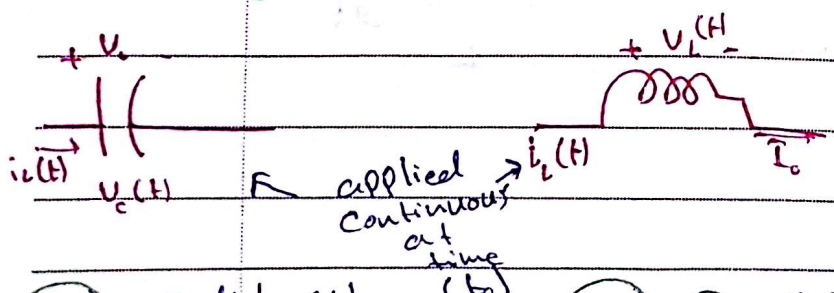

$$i_c(t) = C \frac{dV_c(t)}{dt}$$

$$V_L(t) = L \frac{di_L(t)}{dt}$$




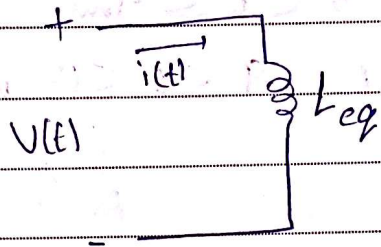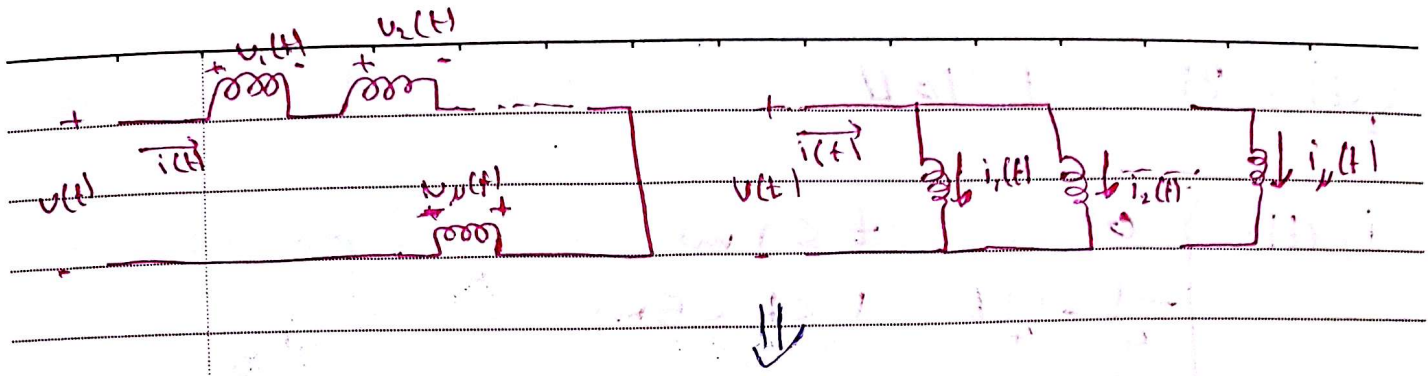

$$V(t) = L_{eq} \frac{di(t)}{dt} = V_1(t) + V_2(t) + \dots + V_n(t)$$

$$L_1 \frac{di(t)}{dt} + L_2 \frac{di(t)}{dt} + \dots + L_n \frac{di(t)}{dt}$$

$$L_{eq} = L_1 + L_2 + \dots + L_n$$


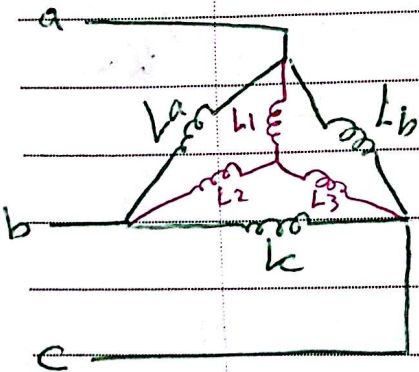


$$V_L(t) = ? \quad L = 10 \text{ H}$$

$$i_L(t) = \begin{cases} 0 & t < 1 \text{ ms} \\ -\frac{0.1}{4} + \frac{0.1}{4}t & 1 \leq t \leq 5 \text{ ms} \\ 0.1 & 5 < t \leq 9 \text{ ms} \\ 13 \times \frac{0.1}{4} - \frac{0.1}{4}t & 9 < t \leq 13 \text{ ms} \\ 0 & t > 13 \text{ ms} \end{cases}$$

$$V_L(t) = L \frac{di_L(t)}{dt}$$
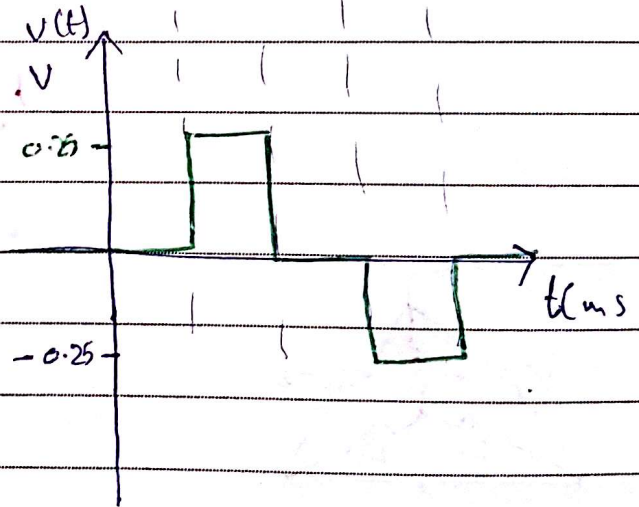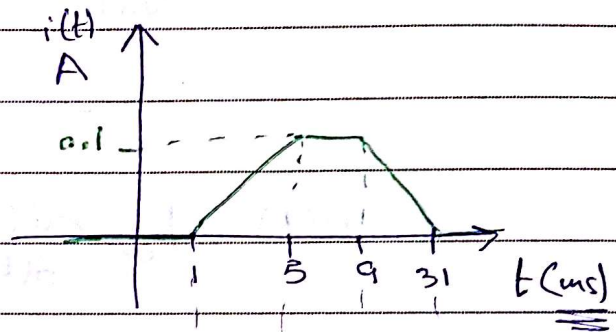
$$V_L(t) = \begin{cases} 0 \text{ V} & t < 1 \text{ ms} \\ 0.25 & 1 \leq t \leq 5 \text{ ms} \\ 0 & 5 \leq t \leq 9 \text{ ms} \\ -0.25 & 9 < t < 13 \text{ ms} \\ 0 & t > 13 \text{ ms} \end{cases}$$





$i_L(t)$  ?

$L = 10 \text{ mH}$

$i_L(t)$

DC


$$v_L(t) = \begin{cases} 0 & t < 0 \text{ sec} \\ -10 \text{ mV} & 0 \leq t < 1 \\ 0 & t > 1 \text{ s} \end{cases} \quad I_0 = 0 \text{ A}$$

$v_L(t) = 0$

so we have


a constant current.

Sol:-

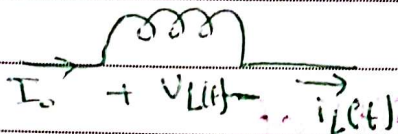

$$i_L(t) = I_0 + \frac{1}{L} \int_{t_0}^t v_L(t) dt$$


$v_L(t)$   
mV

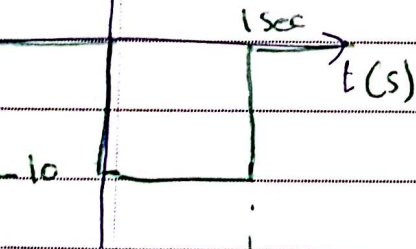

$i_L(t)$

$$-10 \text{ m} \times \frac{1}{10 \text{ m}} = -1$$

-1A

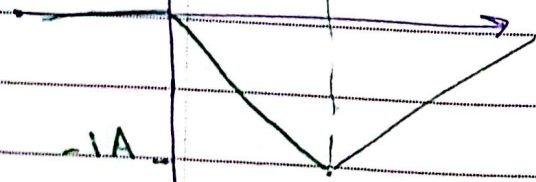

initial  
Condition

$$W_C = \frac{1}{2} C V^2$$

or  
Steady  
State

$$W_L = \frac{1}{2} L I^2$$

$$W = \int p(t) dt$$

$$W_L(t) = \int_{-\infty}^t i_L(t) di_L(t)$$


$$= \int v(t) i(t) dt$$

$$= \int L \frac{di(t)}{dt} i(t) dt$$

$$= \frac{1}{2} L I^2 + \text{Const.}$$



Sinusoidal Sources

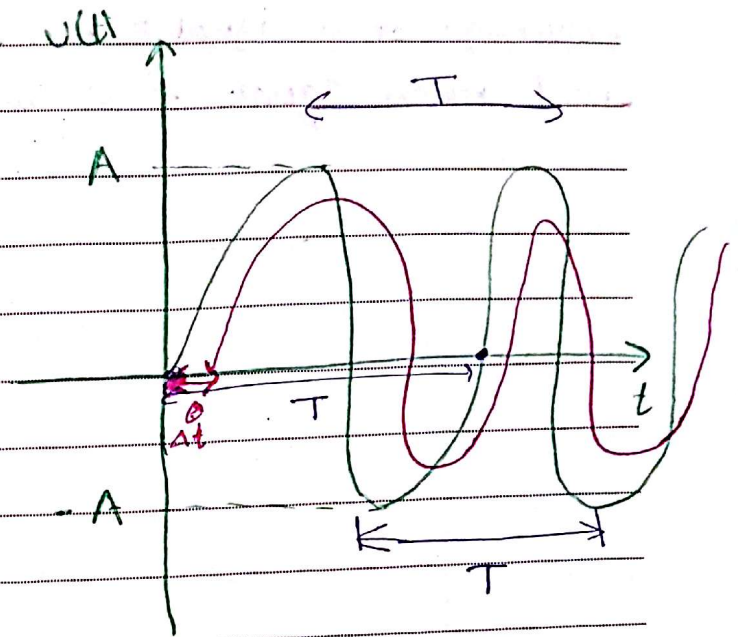

\*  $v(t) = A \sin(\omega t + \theta)$

$\omega = 2\pi f \rightarrow \frac{1}{T}$

\*  $V_{\text{peak}} = A$

\*  $V_{\text{pp}} = 2A$   
Peak to Peak


\*  $\theta$  measured in degrees, in rad

rad	degree
$2\pi$	360
$\theta$	$\theta$

$\Delta t = \frac{T \theta}{360}$

$\Delta t = \frac{T \theta}{2\pi}$

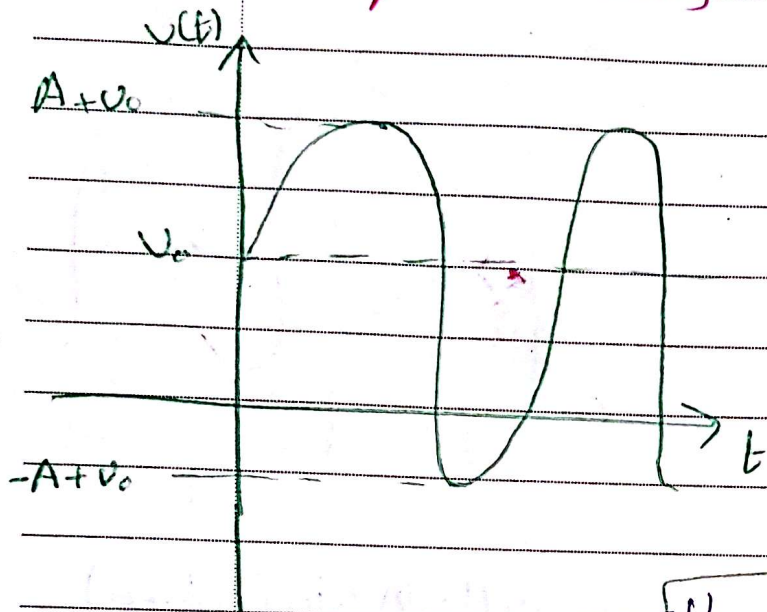- Average of a signal  $\equiv$  DC Component of the signal.
- root mean square of a signal



periodic signal  
 $v(t) = v(t - nT)$


$$v(t) = A \sin(\omega t + \theta) + V_0$$

$$V_{rms} = 0.707 A$$

$$\overline{v(t)} = V_0$$

DC of the signal  $= \overline{v(t)} = V_0 = \frac{1}{T} \int_T v(t) dt$
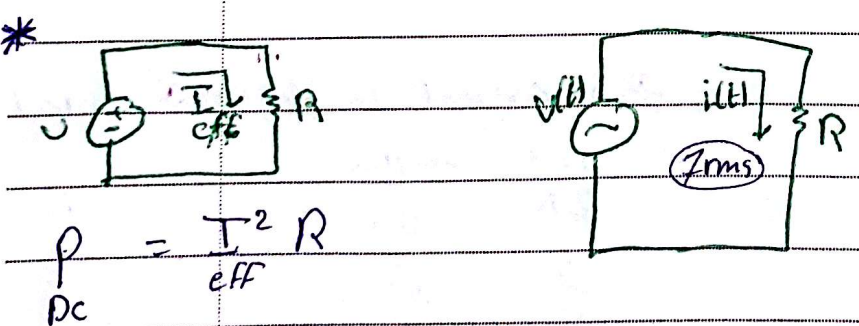
$$V_{rms} = \sqrt{\frac{1}{T} \int_T v^2(t) dt}$$



$$P_{DC} = I_{eff}^2 R$$

power dissipated in the resistor for ac or <sup>dc</sup> supplies should be the same.



$$W_{dc} = T \langle P_{ac} \rangle$$

$$= T \frac{1}{T} \int_T i^2(t) R dt$$

$$= \int_T i^2(t) R dt$$

$$I_{eff}^2 T = \int i^2(t) dt$$

$$= R I_{eff}^2 T \rightarrow \text{Pole power}$$

$$I_{eff}^2 = \frac{1}{T} \int i^2(t) dt$$


$$I_{eff} = \sqrt{\frac{1}{T} \int i^2(t) dt}$$

ch. 10


→ phasor Representation.

Euler identity

$$v(t) = A \cos(\omega t + \theta)$$

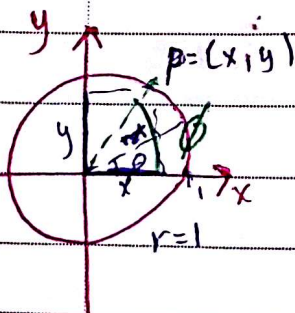

Cartesian Coordinates →

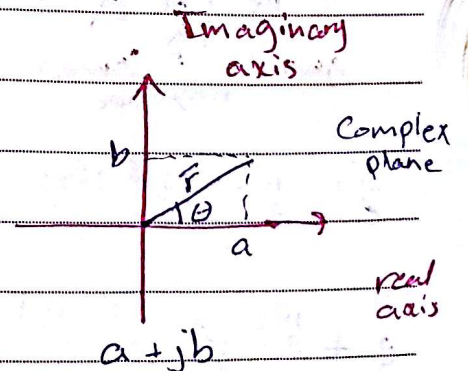

$$x = 2 \cos \theta$$

$$y = 1 \sin \theta$$

$$(1 \cos \theta, 2 \sin \theta)$$

$$(x, y)$$

$$p = (1, \theta)$$

polar

Coordinates

(cylindrical) Coordinates

$$a + jb$$

$$j = \sqrt{-1}$$

$$|r| < \theta$$

$$\sqrt{a^2 + b^2}$$

$$\theta = \tan^{-1} \frac{b}{a}$$

Euler representation:

$$\vec{r} = |\vec{r}| e^{j\theta}$$

$$= |\vec{r}| \{ \cos\theta + j \sin\theta \}$$

$$v(t) = A \cos(\omega t + \theta)$$

$$v(t) = \underset{\text{real}}{\text{Re}} \left\{ \underbrace{A e^{j(\omega t + \theta)}}_{\text{Euler representation}} \right\}$$

$$= \text{Re} \left\{ A [\cos(\omega t + \theta) + j \sin(\omega t + \theta)] \right\}$$

$$= \text{Re} \left\{ A \cos(\omega t + \theta) + j A \sin(\omega t + \theta) \right\}$$


$$= A \cos(\omega t + \theta)$$

$$v(t) = A \cos(\omega t + \theta)$$

$$= \text{Re} \left\{ A e^{j(\omega t + \theta)} \right\}$$

$$\Rightarrow v(t) = A e^{j\theta}$$

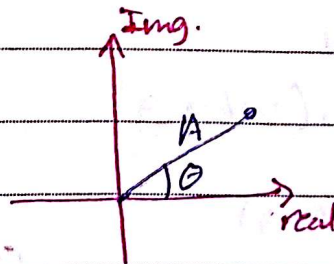
$$= \text{Re} \left\{ \underbrace{A}_{\substack{\uparrow \\ \text{magnitude}}} \underbrace{e^{j\omega t}}_{\text{ignored}} \underbrace{e^{j\theta}}_{\text{ignored}} \right\}$$




$$e^{j\theta_1} \cdot e^{j\theta_2} = e^{j(\theta_1 + \theta_2)}$$
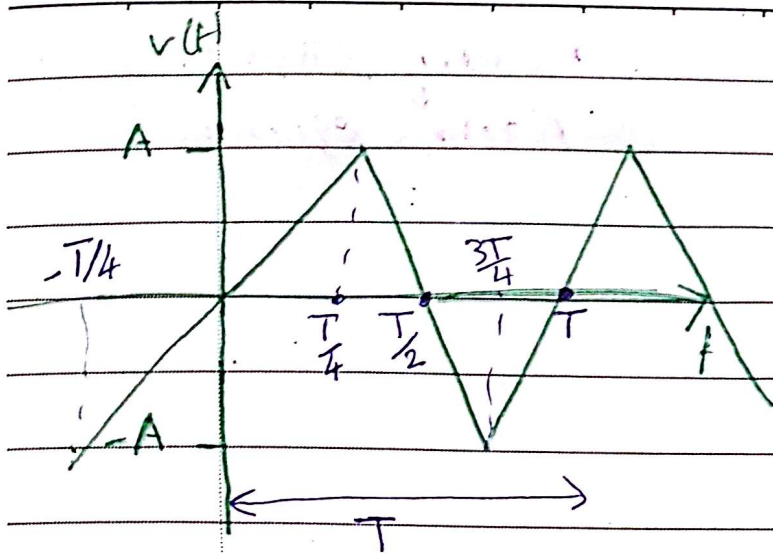
$$e^{j\theta_1} + e^{j\theta_2} \neq e^{j(\theta_1 + \theta_2)}$$







Triangle wave

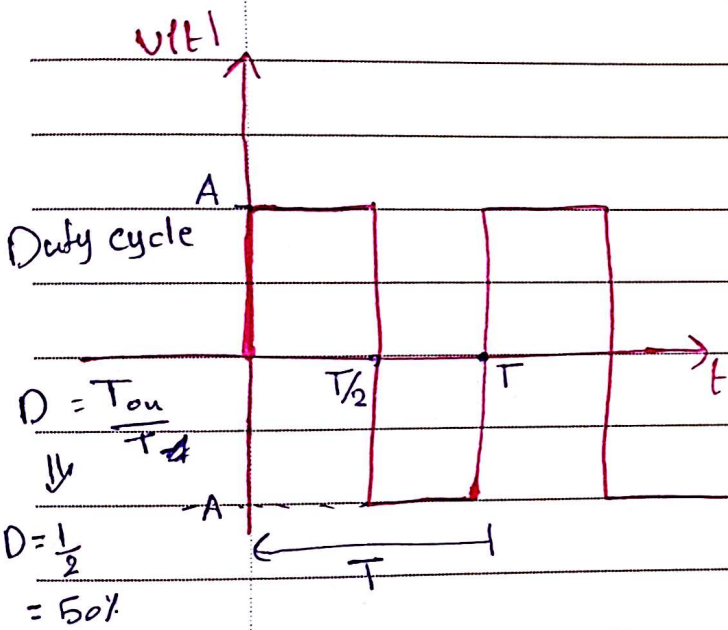

Square wave

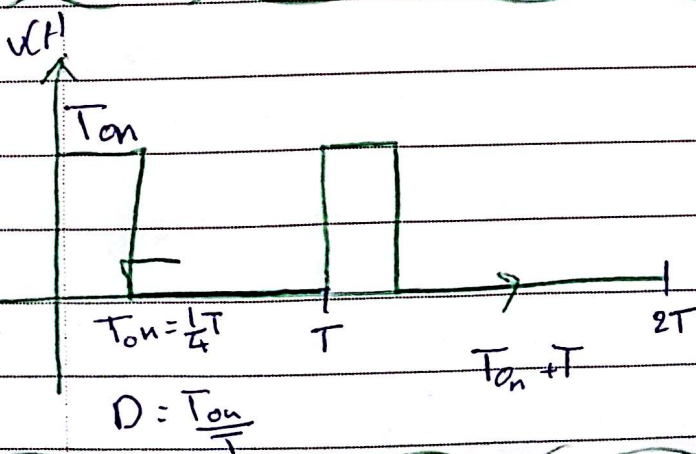

pulsed signal

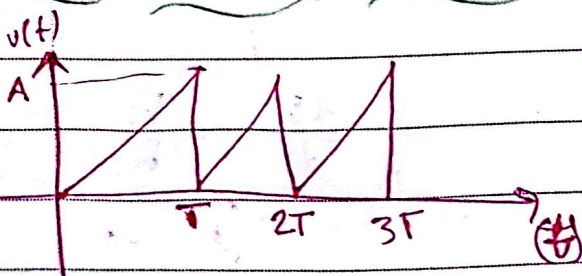

Sawtooth

differential equations

RL, RC

first order

Resistive circuit

↓  
Algebraic equations

DC/switching

AC

ch. 7


ch. 8

ch. 9  
ch. 10

RLC (2nd order)

parallel

series

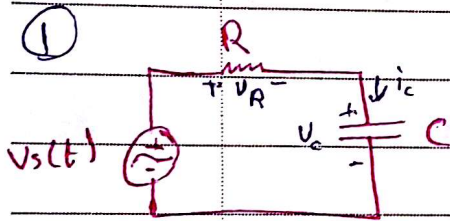

$V_s(t) = A \cos \omega t$

- two ways or
- ① kcl
  - ② kvl

kcl

$i_R - i_C = 0$

$\frac{V_s - V_L}{R} - C \frac{dV_C}{dt} = 0$


$\frac{V_s}{R} - \frac{V_L}{R} - C \frac{dV_C}{dt} = 0$

$C \frac{dV_C}{dt} + \frac{V_C}{R} = \frac{V_s}{R}$

$\frac{dV_C}{dt} + \frac{V_C}{Rc} = 0$  natural response

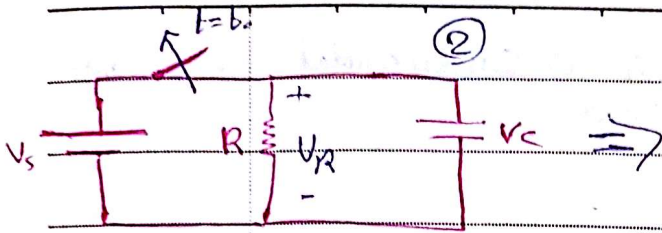$\frac{dV_C}{dt} + \frac{V_C}{Rc} = \frac{V_s}{Rc}$  step Response





initial condition

 $V_0$ 
 $t_0^- \quad t_0^+$   
 $t_0$ 

Switching action

time li

→ switch stays in it's position for long time.

→ voltage continuous at switching action

→ current is discont. || || ||.

back to ①:-

$$-V_s + V_R + V_C = 0$$

$$\frac{d}{dt} [-V_s(t) + Ri(t) + \frac{1}{C} \int_{-\infty}^t i(t') dt'] = 0$$

$$V_0 + \frac{1}{C} \int_{t_0}^t i(t') dt'$$

$$-\frac{d}{dt} V_s(t) + R \frac{di}{dt} + \frac{1}{C} i(t) = 0$$

$$R \frac{di}{dt} + \frac{1}{C} i(t) = \frac{d}{dt} V_s(t)$$

$$\frac{di(t)}{dt} + \frac{1}{RC} i(t) = \frac{1}{R} \frac{d}{dt} V_s(t)$$

Time Constant

$$\tau = RC$$

$V_s(t) = V \cos \omega t$  \*when we have a sinusoidal source we use phasor.

$$V_c(t) = A \sin \omega t - B \cos \omega t$$

$$\frac{dV_c(t)}{dt} + \frac{1}{R_c} V_c(t) = \frac{1}{R_c} V_s(t)$$

$$A \omega \cos \omega t - B \omega \sin \omega t + \frac{A}{R_c} \sin \omega t + \frac{B}{R_c} \cos \omega t = \frac{1}{R_c} V \cos \omega t$$

$$\left( \frac{A}{R_c} - B \omega \right) \sin \omega t + \left( A \omega + \frac{B}{R_c} - \frac{V}{R_c} \right) \cos \omega t = 0$$


$$\frac{A}{R_c} - B \omega = 0$$

$$A \omega + \frac{B}{R_c} - \frac{V}{R_c} = 0$$

$$A = \frac{V \omega R_c}{1 + \omega^2 (R_c)^2}$$


$$B = \frac{V}{1 + \omega^2 (R_c)^2}$$



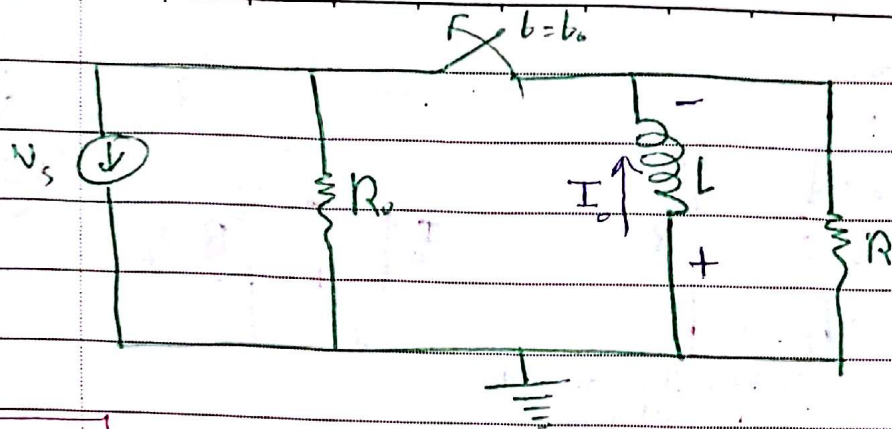


\* at  $t = t_0^-$

$$I_L = I_0 = I_s$$

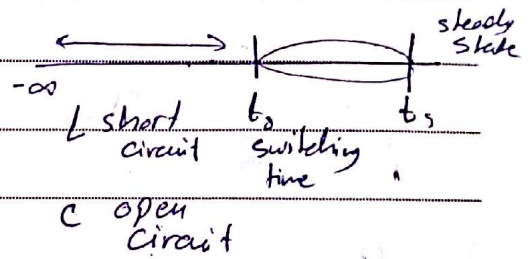

\* at  $t = t_0$

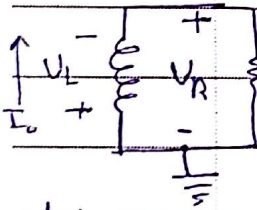

KVL:-

$$+V_L + V_R = 0$$

$$L \frac{di(t)}{dt} + Ri = 0$$

$$L \frac{di(t)}{dt} = -Ri$$

$$\frac{di(t)}{dt} = -\frac{R}{L} i(t)$$

$$\ln i(t) - \ln i(t_0) = -\frac{R}{L} t$$

$$\ln \frac{i(t)}{i(t_0)} = -\frac{R}{L} t$$



$$\int_{i(t_0)}^{i(t)} \frac{di(t)}{i(t)} = \int_{t_0}^t -\frac{R}{L} dt$$

$$\Rightarrow \frac{i(t)}{i(t_0)} = e^{-\frac{R}{L} t}$$

$$i(t) = I_0 e^{-\frac{R}{L} t} \quad t \geq 0$$

$$\ln i(t) \Big|_{i(t_0)} = -\frac{R}{L} (t - t_0)$$

# RL natural Response

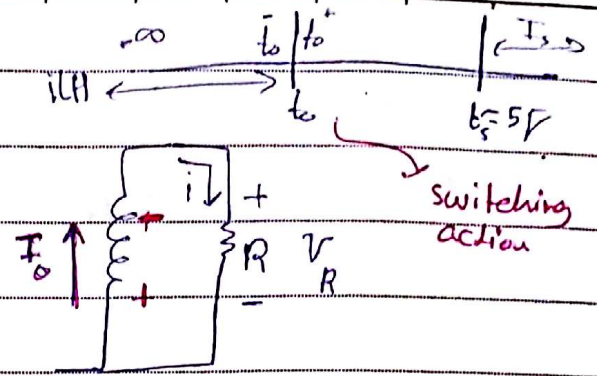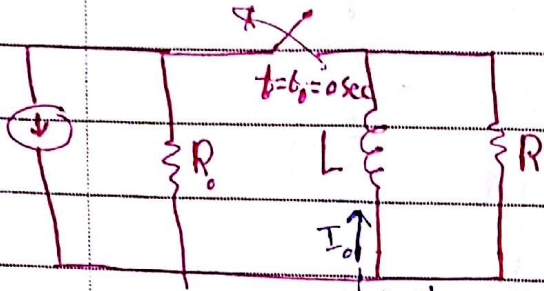



when the switch is closed

$$i(t) = I_s e^{-t/T} \quad t \geq 0$$

$$T = \frac{L}{R}$$

Time constant (delay factor)
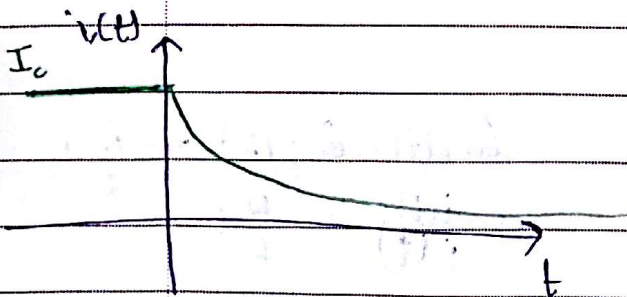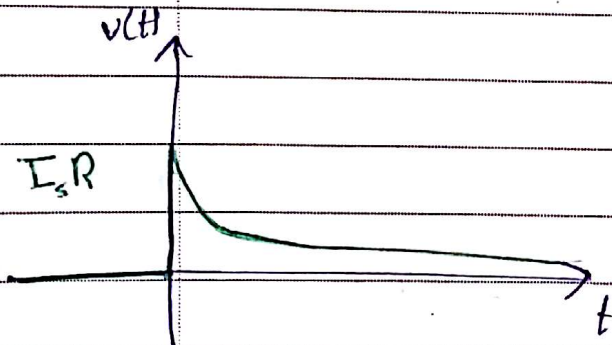
$$V_R = iR = I_s R e^{-t/T} \quad t > 0$$



t	$e^{-t/T}$
0	1
T	0.37
2T	0.14
3T	0.05
4T	0.02
5T	0.007 ≈ 0.01
10T	$4.7 \times 10^{-5}$

Steady State time  $t_s = 5T$




→ How to find  $\tau$  graphically.

$$i(t) = I_0 e^{-t/\tau}$$

$$\left. \frac{di(t)}{dt} \right|_{t=t_0} = I_0 \left( -\frac{1}{\tau} \right) e^{-t_0/\tau} \Big|_{t=t_0}$$

$$= -\frac{I_0}{\tau}$$

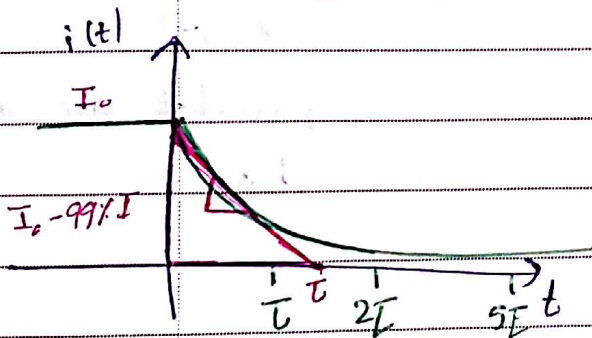we can find  $\tau$  using the slope of the line



$$p = v(t) i(t)$$


$$= R i^2(t)$$

$$= R I_s^2 e^{-2t/\tau}$$

$$t < 0$$

$$t > 0$$

max energy stored in the inductor

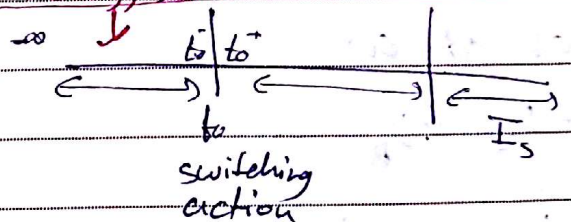

$$W = \int p dt$$

energy dissipated in the resistor

$$= \int_{t_0}^{\infty} R I_s^2 e^{-2t'/\tau} dt'$$


$$= \frac{-\tau}{2} R I_s^2 e^{-2t'/\tau} \Big|_{t_0}^{\infty}$$

$$= \frac{\tau}{2} R I_s^2 (1 - e^{-2t_0/\tau}) = \frac{1}{2} L I_s^2 (1 - e^{-2t_0/\tau})$$

$$t \geq 0 \checkmark$$

$$t > 0 \times$$


# Natural response for RC

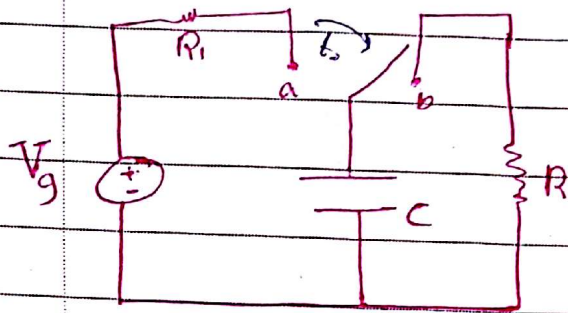

Single pole Single throw  
 → Single pole double throw

initial condition  
 $V_0$  at  $t_0 = 0s$

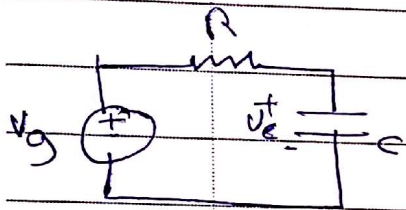step 1 :- Switch stays at a for long time




$$t = t_0^- = 0^-$$

$$V_c(t) = V_g$$

$$t = 0^+$$

→ Switch goes to b

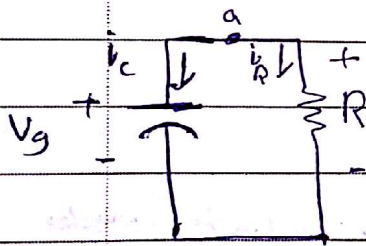

KCL at a :-

$$-i_c - i_R = 0$$

$$i_c = -i_R$$


$$C \frac{dV_c}{dt} = -\frac{V_c(t)}{R}$$

$$V_c(t) = V_0 e^{-t/RC}$$

$$\frac{dV_c}{dt} = -\frac{V_c(t)}{RC}$$

⇒  $\tau = RC$  Time Constant
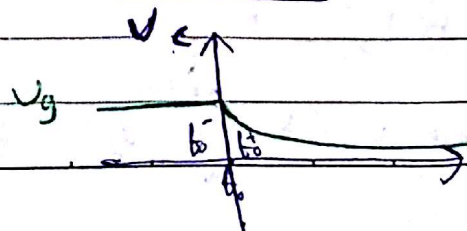
$$\int_{V_c(t_0)}^{V_c} \frac{dV_c}{V_c} = \int_{t_0}^t -\frac{1}{RC} dt$$






$$V_R = V_g e^{-t/\tau} \quad t > 0$$

$$V_R(t=t_0^+) = V_g$$
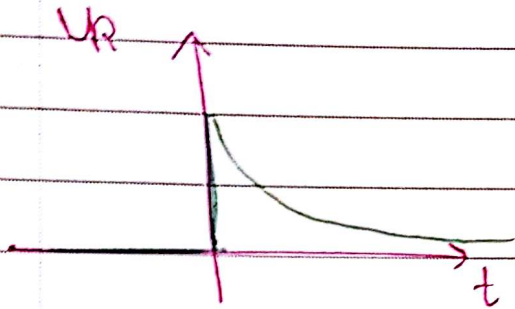
$$V_C(t_0^+) = V_C(t_0^-) = V_C(t_0) = V_g$$



$$P = i^2 R = \frac{V_g^2}{R} e^{-2t/\tau} \quad t > 0$$

$$= \frac{V^2}{R}$$

$$W_R = \int_{t_0}^t \frac{V_g^2}{R} e^{-2t'/\tau} dt' = \frac{\tau}{2} \frac{V_g^2}{R} [1 - e^{-2t/\tau}]$$

$$= \frac{RC}{2} \frac{V_g^2}{R} [1 - e^{-2t/\tau}]$$

$$W_R = \frac{1}{2} C V_g^2 [1 - e^{-2t/\tau}] \quad t > 0$$

6/11/2016



forced response for RL

Simulation  
CH.9


Step response

Step function

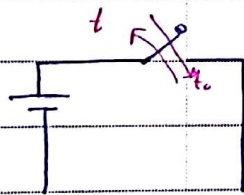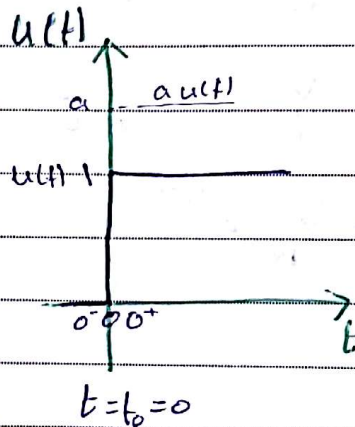
$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$



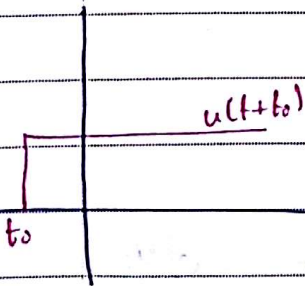→ we call it step response because we apply DC source.


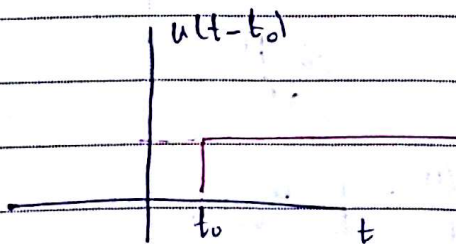
$$u(t + t_0) = \begin{cases} 0 & t < -t_0 \\ 1 & t > -t_0 \end{cases}$$





$$u(t - t_0) = \begin{cases} 0 & t < t_0 \\ 1 & t > t_0 \end{cases}$$
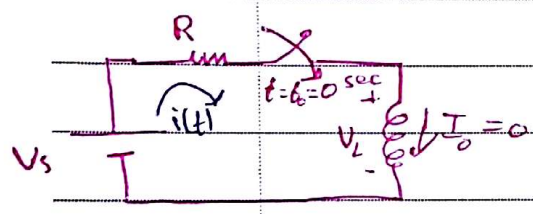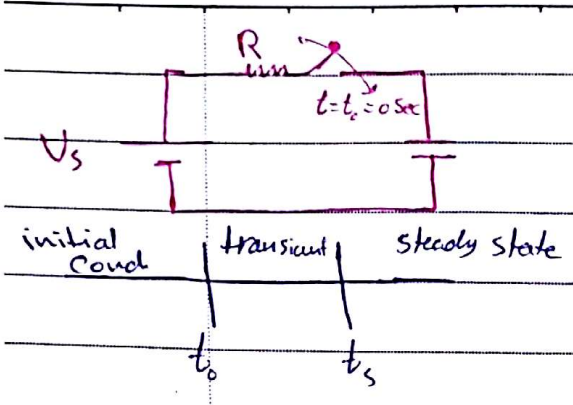
$$\frac{du(t)}{dt} = \delta(t) \text{ delta function}$$







KVL

$$-V_s + Ri + V_L = 0$$

$$-V_s + Ri + L \frac{di}{dt} = 0$$

$$L \frac{di}{dt} = V_s - Ri$$

$$\int_{I_0}^{i(t)} dx = \int_{t_0}^t \frac{-R}{L} dy$$

$I_0$  initial

$$L \frac{di}{dt} = -R \left( i - \frac{V_s}{R} \right) \Rightarrow$$

$$\ln \left( i(t) - \frac{V_s}{R} \right) = \frac{-R}{L} (t - t_0)$$

$$\frac{di}{dt} = \frac{-R}{L} \left( i - \frac{V_s}{R} \right)$$


$$\int_{i(t_0)}^{i(t)} di' = \int_{t_0}^t \frac{-R}{L} dt'$$

$I_f$

$$i(t) - \frac{V_s}{R} = \left( I_0 - \frac{V_s}{R} \right) e^{-\frac{R}{L}(t-t_0)}$$

$$i(t) = \frac{V_s}{R} + \left( I_0 - \frac{V_s}{R} \right) e^{-\frac{R}{L}(t-t_0)}$$

$I_f + (I_{initial} - I_f) e^{-t/\tau}$

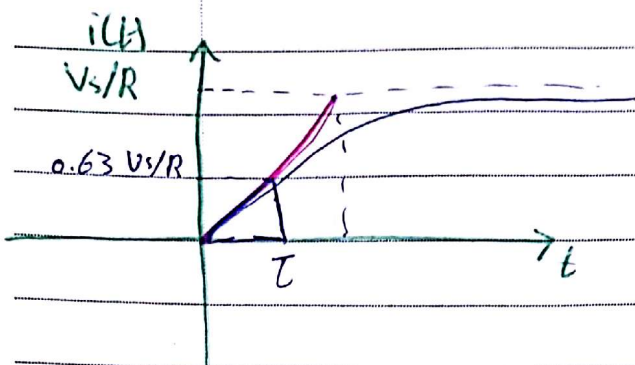

$$\left. \frac{di(t)}{dt} \right|_{t=0} = \frac{-V_s}{R} \cdot \left( \frac{-R}{L} \right)$$

$$= \frac{V_s}{L} \quad t = \tau$$


$$i(t) = \frac{V_s}{R} - \frac{V_s}{R} e^{-t/\tau}$$

### Transient

$$v_L(t) = L \frac{di(t)}{dt}$$

$$= L \left( \frac{-V_s}{R} \right) \left( \frac{-R}{L} \right) e^{-t/\tau}$$

$$v_L(t) = V_s e^{-t/\tau}$$

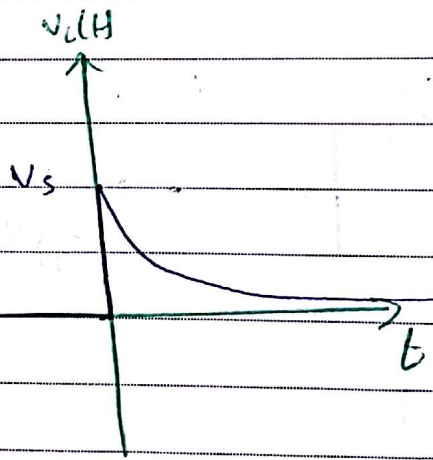

$$\rightarrow \frac{di(t)}{dt} + \frac{R}{L} i(t) = \frac{V_s}{L}$$

$$\frac{di(t)}{dt} = -\frac{1}{R} \frac{dv_L}{dt} \quad (1)$$

$$-V_s + R i(t) + v_L = 0 \quad \Rightarrow$$

$$i(t) = \frac{1}{R} V_s - \frac{1}{R} v_L$$

$$v_L = L \left( \frac{di(t)}{dt} \right)$$


$$\frac{di(t)}{dt} = \frac{1}{L} v_L$$



No. \_\_\_\_\_

$$\frac{1}{L} V_L - - \frac{1}{R} \frac{dV_L}{dt}$$

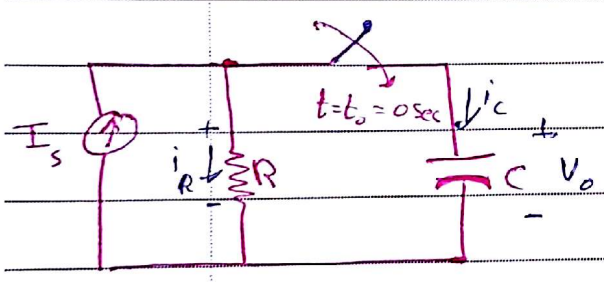
$$\int_{V_L(t_0)}^{V_L(t)} \frac{dV_L}{V_L} = \int_{t_0}^t -\frac{R}{L} dt'$$



$$t = t_0^-$$

$$V_C(t) = V_0 = 0V$$

$$t = t_0^+$$

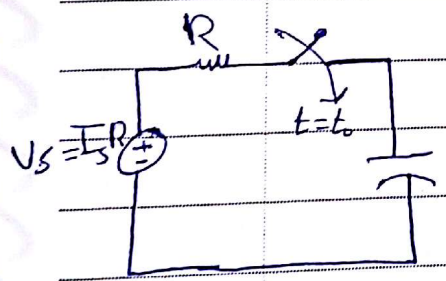

$$I_s - i_R - i_C = 0$$

$$I_s - \frac{V_C(t)}{R} - C \frac{dV_C(t)}{dt} = 0$$

$$C \frac{dV_C(t)}{dt} = I_s - \frac{V_C}{R}$$

$$\frac{dV_C(t)}{dt} = -\left(\frac{V_C}{R_C} - \frac{I_s}{C}\right)$$

$$\frac{dV_C(t)}{dt} = -\frac{1}{R_C} (V_C - RI_s)$$

$$\int_{V_C(t_0)}^{V_C(t)} \frac{dV_C(t)}{V_C - (RI_s)} = \int_{t_0}^t -\frac{1}{R_C} dt'$$

Initial  $V_0 = 0$


$$V_C(t) = V_f + (V_{in} - V_0) e^{-t/\tau}$$

No. \_\_\_\_\_

$$V_c(t) = V_f + (V_{in} - V_f) e^{-t/\tau}$$

$$= I_s R - I_s R e^{-t/\tau}$$

$t > 0$  <sup>pro</sup> <sub>beles</sub>

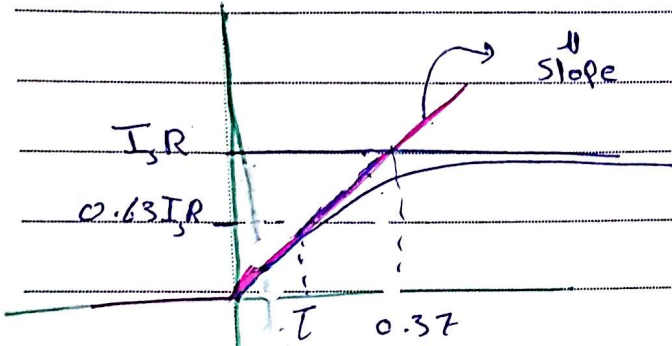

$$I_s R - I_s R e^{-t/\tau}$$

$$\left. \frac{dV_c(t)}{dt} \right|_{t=0} = -I_s R \left( \frac{-1}{\tau} \right) = +\frac{I_s}{C}$$




8/11/2016

→ The step response for RC

kel at point a

$$I_s - i_R - i_c = 0$$

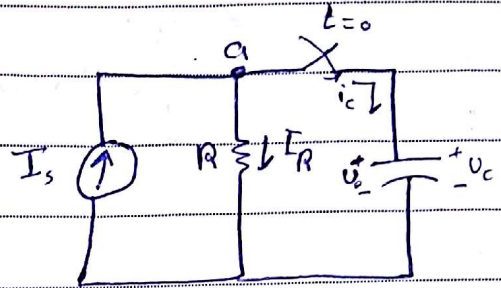

$$I_s - \frac{V_c}{R} - C \frac{dV_c}{dt} = 0$$

$$i_c = C \frac{dV_c}{dt}$$

$$C \frac{dV_c}{dt} = I_s - \frac{V_c}{R}$$

$$\frac{dV_c}{dt} = \frac{I_s}{C} - \frac{V_c}{RC}$$

$$\frac{dV_c}{dt} = -\frac{1}{RC} [V_c - RI_s]$$

$$V_0 > t \geq 0^-$$

$$V_0 = 0 \text{ V}$$

$$V_f = I_s R$$

$$\int_{V_0}^{V_c(t)} \frac{dV_c}{V_c - RI_s} = \int_{t_0=0}^t -\frac{1}{RC} dt$$

$$V_c(t_0) = V_0$$

⇒ The voltage across the capacitor is continuous then  $t \geq 0$



$$\hookrightarrow V_c(t) = V_f + (V_0 - V_f) e^{-t/\tau} \quad \tau = RC$$

$$V_c(t) = V_f + (V_0 - V_f) e^{-(t-t_0)/\tau} \quad t_0 \neq 0$$


$$i_c(t) = C \frac{d}{dt} [I_s R + (0 - I_s R) e^{-t/\tau}]$$

$$i_c(t) = C \left[ -(-I_s R) \left(-\frac{1}{\tau}\right) e^{-t/\tau} \right]$$
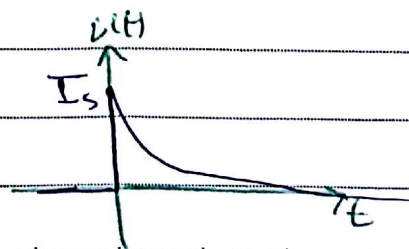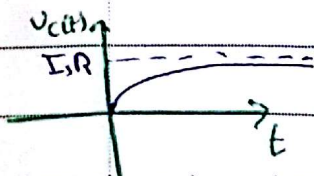
$$i_c(t) = I_s e^{-t/\tau} \rightarrow t > 0$$



No. \_\_\_\_\_

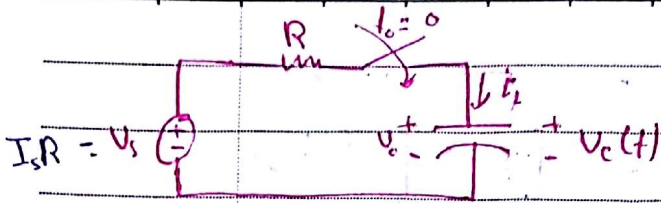

KVL &

$$\frac{d}{dt} [-V_s + R i_c + V_c + V_c(t) = 0]$$

$$-0 + R \frac{d i_c}{dt} + 0 + \frac{d V_c(t)}{dt} = 0$$

$$i_c = C \frac{d V_c}{dt}$$


$$\frac{d V_c}{dt} = \frac{1}{C} i_c \quad i_c(t) = I_0 e^{-t/\tau} \quad t > 0$$

$$R \frac{d i_c}{dt} + \frac{1}{C} i_c = 0$$

$$\frac{d i_c}{dt} = -\frac{1}{R C} i_c$$
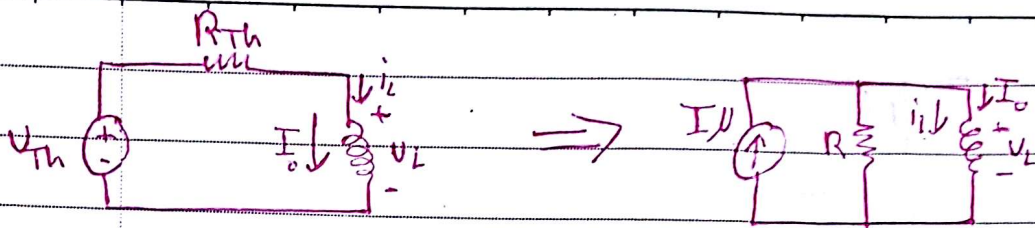
$$\int_{i_c(t=0)}^t \frac{d i_c}{i_c} = \int_{t_0=0}^t -\frac{1}{R C} dt$$






$$i_L(t) = I_f + (I_0 - I_f) e^{-(t-t_0)/\tau} \quad t \geq t_0$$



$$v_L(t) = V_0 e^{-(t-t_0)/\tau} \quad t > t_0$$

step response

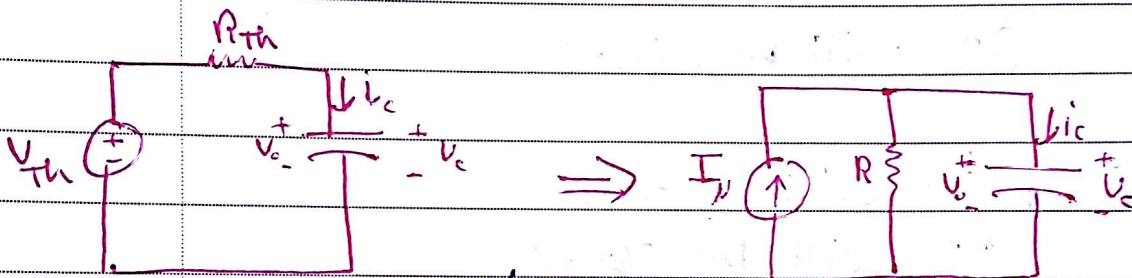

$$v_C(t) = V_f + (V_0 - V_f) e^{-(t-t_0)/\tau} \quad t \geq t_0$$
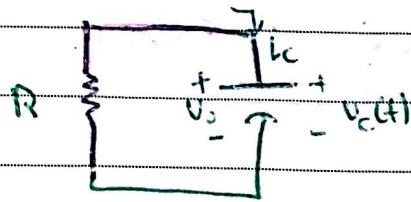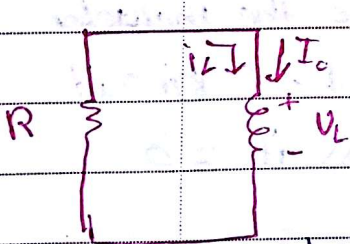
$$i_C(t) = I_0 e^{-(t-t_0)/\tau} \quad t > t_0$$




$$i_L(t) = I_0 e^{-(t-t_0)/\tau} \quad t \geq t_0$$

$$v_L(t) = I_0 R e^{-(t-t_0)/\tau} \quad t > t_0$$


$$v_C(t) = V_0 e^{-(t-t_0)/\tau} \quad t > t_0$$
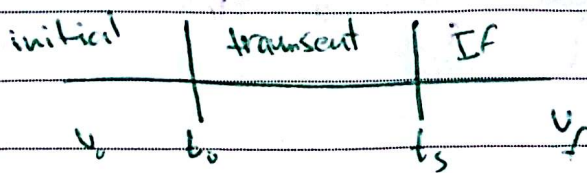
$$i_C(t) = \frac{V_0}{R} e^{-(t-t_0)/\tau} \quad t > t_0$$



No. \_\_\_\_\_

# Sequential switching

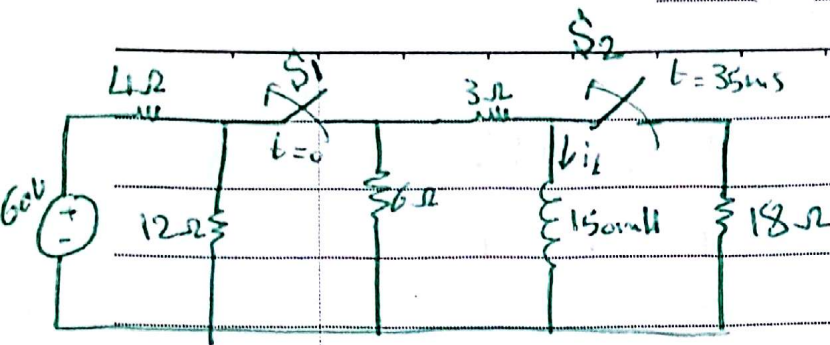

at  $t = 0^- \Rightarrow$  the switches will be closed


at  $t = 0^+ \Rightarrow$  S1 will open

S2 will be closed

at  $t = 35ms^- \Rightarrow$  S1 will be open


S2 will be closed

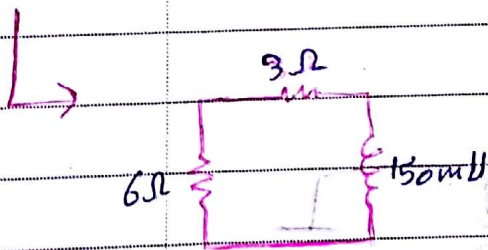at  $t = 35ms^+ \Rightarrow$  S1 will be open, S2 will open




$\Rightarrow$  in steady state the inductor will be like a short circuit  
So  $V$  across it  $= 0$ .

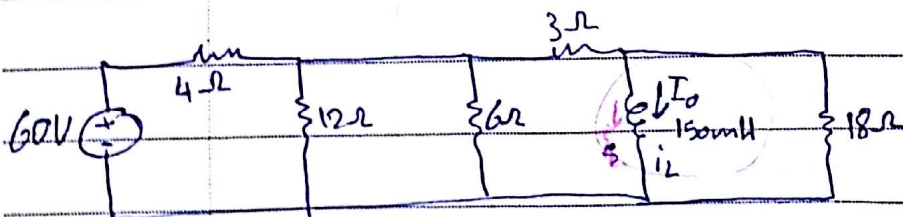$\Rightarrow$  at  $t = 0^-$   $i_L(t) = I_0 e^{-(t-t_0)/\tau}$   $t \geq t_0$







No. 10/11/2016

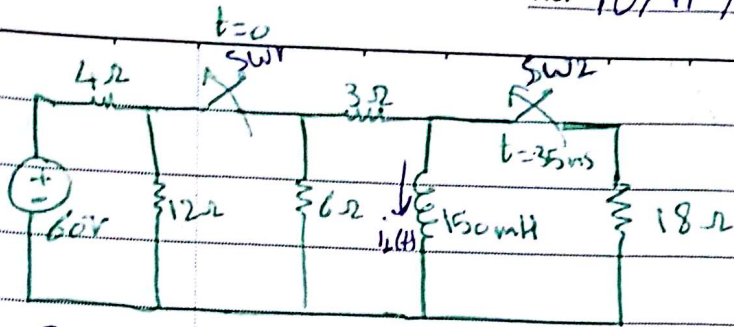

Find the  $i_L(t)$   $0 < t < 35 \text{ms}$


$$i_L(t=0^-) = I_0$$

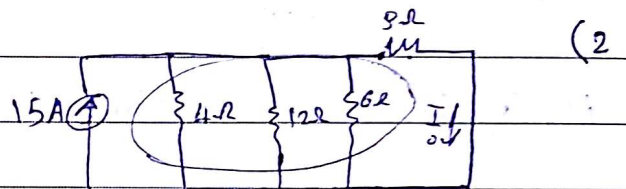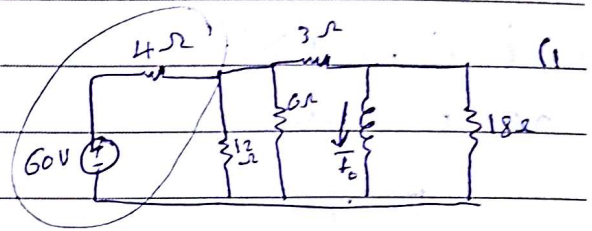

$$4 \parallel 12 \parallel 6 = 2 \Omega$$

$$I_0 = \frac{2}{2+3} (15) = 6 \text{A}$$

at  $t=0^+$

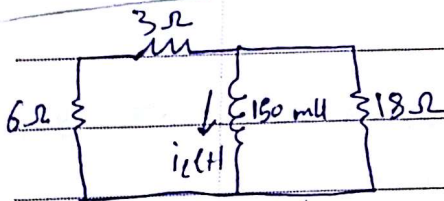


$$i_L(t) = I_0 e^{-t/\tau} \quad t \geq 0$$

$$\tau = \frac{L}{R} = \frac{150 \times 10^{-3}}{6} = 25 \text{ms}$$

$$R = (3+6) \parallel 18 = 6 \Omega$$


$$i_L(t) = 6 e^{-t/25 \times 10^{-3}} = 6 e^{-40t} \quad t \geq 0$$
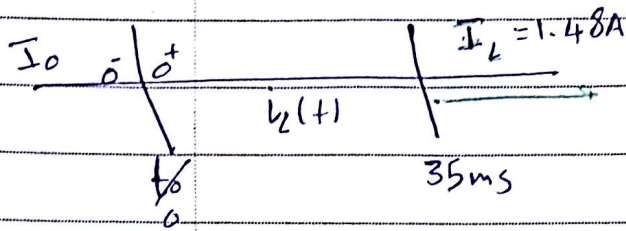
$$i_L(35\text{ms}) = 6 e^{-40(35 \times 10^{-3})} = 1.48\text{A}$$



b)  $i_L(t)$  for  $t > 35\text{ms}$

at  $t = 35\text{ms}^+$

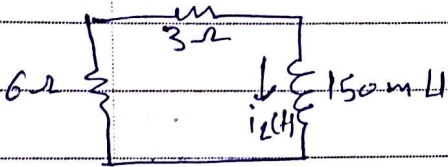

$$i_L(t) = I_0 e^{-t/\tau} \quad t > 35\text{ms}$$

$$= 1.48 e^{-t/\tau}$$

$$\tau = \frac{L}{R} = \frac{150 \times 10^{-3}}{9} = 16.67\text{ms}$$

$$i_L(t) = 1.48 e^{-\frac{t - 35\text{ms}}{16.67 \times 10^{-3}}} = 1.48 e^{-60(t - 35 \times 10^{-3})} \quad t > 35\text{ms}$$

c) What is percentage of initial energy in the  $150\text{mH}$  inductor is dissipated in the  $18\Omega$  resistor?

$$W = \int p dt$$

$$p = iV$$

$$= i^2 R$$

$$= \frac{V^2}{R}$$

$$V_L = L \frac{di}{dt} \quad t < 35, t > 0$$

$$= 150 \times 10^{-3} \frac{d}{dt} [6 e^{-40t}]$$

$$= -36 e^{-40t} \text{ V}$$

$$0 < t < 35\text{ms}$$



$$V = VL$$

$$R = 18 \Omega = -36 e^{-40t}$$

$$t = 35 \text{ ms}$$

$$W = \int_0^{35 \text{ ms}} \frac{(-36 e^{-40t})^2}{18} dt$$

$$= 0.85 \text{ J}$$

initial energy in inductor

$$W_L = \frac{1}{2} L I_0^2$$

$$= \frac{1}{2} \times 150 \times 10^{-3} \times 6^2$$

$$= 2.7 \text{ J}$$

$$\% W = \frac{0.85}{2.7} \times 100\%$$

$$= 31.48\%$$

d) percentage energy in  $3 \Omega$

for two cases to calculate energy dissipation?

①  $0 < t < 35 \text{ ms}$

②  $t > 35 \text{ ms}$

$$V_{R3\Omega} = \frac{3}{3+6} \cdot V_L(t) = 12 e^{-40t} \quad 0 < t < 35 \text{ ms}$$

$$W_{3\Omega} = \int_0^{35 \text{ ms}} \frac{(12 e^{-40t})^2}{3} dt = 0.5634 \text{ J}$$

$$V_{3\Omega} = 3 i_L$$

$$= 3 (1.48 e^{-60(t-0.035)})$$

$$W = \int_{0.035}^{\infty} 6.57 e^{-120(t-0.035)} dt$$

$$W_{3\Omega} = 0.055 \text{ J}$$

$$W_{3\Omega} = 0.055 + 0.5634$$

$$= 0.6182 \text{ J}$$

$$W\% = \frac{0.6182}{2.27} = 22.89\%$$

e) in  $6\Omega$

$$W_{6\Omega} = 1236.48 \text{ mJ}$$


$$= 1.236 \text{ J}$$

$$W_{6\Omega} \% = \frac{1.236}{2.7} \times 100\% = 45.8\%$$

$$1236.48 + 618.24 + 8 + 5.27 = \frac{2699.99 \text{ mJ}}{2.7 \text{ J}}$$



Natural response of RLc parallel

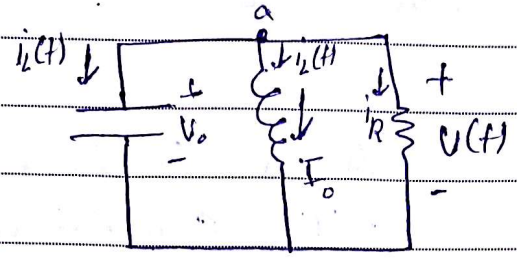

KCL at node a:-

$$i_R + i_C + i_L = 0$$

$$V_L = L \frac{di}{dt}$$

$$\left( \frac{V}{R} + C \frac{dV}{dt} + \frac{1}{L} \int V_L dt + I_0 = 0 \right) \frac{d}{dt}$$

$$\frac{1}{R} \frac{dV}{dt} + C \frac{d^2 V}{dt^2} + \frac{1}{L} V = 0$$

$$\frac{d^2 V}{dt^2} + \frac{1}{Rc} \frac{dV}{dt} + \frac{1}{Lc} V = 0$$

$$As^2 e^{st} + \frac{1}{Rc} As e^{st} + \frac{1}{Lc} A e^{st} = 0$$

$$A e^{st} \left[ s^2 + \frac{s}{Rc} + \frac{1}{Lc} \right] = 0$$

$\neq 0$

$$s^2 + \frac{s}{Rc} + \frac{1}{Lc} = 0$$

characteristic equation

for transient with DC supply

$$V(t) = V_0 e^{-t/\tau}$$

$$i(t) = I_0 e^{-t/\tau}$$

$$V(t) = A e^{st}$$

$$\frac{dV}{dt} = A s e^{st}$$


$$\frac{d^2 V}{dt^2} = A s^2 e^{st}$$

$$s_1, s_2 = \frac{-1}{2Rc} \mp \sqrt{\left(\frac{1}{2Rc}\right)^2 - \frac{1}{Lc}}$$

$$V_1(t) = A_1 e^{s_1 t}$$

$A_1, A_2$  can be found using initial condition  $I_0, U_0$

$$V_2(t) = A_2 e^{s_2 t}$$

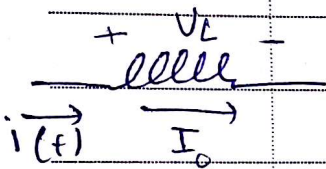

$$i_L(t) = c \frac{dV(t)}{dt} \quad i_L(t_0^-) = i_L(t_0) = i_L(t_0^+) = I_0$$


$$= c \frac{d}{dt} (A_1 e^{s_1 t} + A_2 e^{s_2 t})$$

$$= c A_1 s_1 e^{s_1 t} + c A_2 s_2 e^{s_2 t}$$

$$= c A_1 s_1 + c A_2 s_2$$



20/11/2016

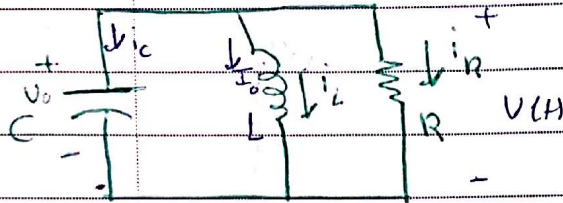

$$\frac{d^2 v}{dt^2} + \frac{1}{Rc} \frac{dv}{dt} + \frac{1}{Lc} v = 0$$

kcl :-

$$\text{for } \Rightarrow i_c + i_L + i_R = 0$$

initial condition

$$S^2 + \frac{1}{Rc} S + \frac{1}{Lc} = 0 \quad \text{characteristic equation}$$

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_1, s_2 = \frac{-1}{2Rc} \pm \sqrt{\frac{1}{(2Rc)^2} - \frac{1}{Lc}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -\alpha \pm \omega_d$$

$$\alpha \equiv \text{Neper frequency} \equiv \text{rad/s} \quad \alpha = \frac{1}{2Rc}$$

damping factor

$$\omega_0 = \text{resonance frequency} \equiv \text{rad/s}$$

$$\omega_0 = \sqrt{\frac{1}{Lc}}$$

$$\omega_d = \text{damping radian frequency} \equiv \text{rad/s}$$

$$\omega_d = \sqrt{\alpha^2 - \omega_0^2}$$

units of  $A_1, A_2$  (V) $s_1, s_2$  (sec<sup>-1</sup>)

1) if  $\alpha^2 > \omega_0^2$  (over damping)



We have two real, distinct solution for the characteristic eq.

2) if  $\alpha^2 < \omega_0^2$

$$\begin{aligned}\sqrt{\alpha^2 - \omega_0^2} &= \sqrt{-\alpha^2 - \omega_0^2} \\ &= \sqrt{-1} \sqrt{\alpha^2 + \omega_0^2} \\ &= j \sqrt{\alpha^2 + \omega_0^2}\end{aligned}$$

$$\begin{aligned}\sqrt{\alpha^2 - \omega_0^2} &= \sqrt{-\omega_0^2 - \alpha^2} \\ &= \sqrt{-1} \sqrt{\omega_0^2 - \alpha^2} \\ &= j \omega_d\end{aligned}$$
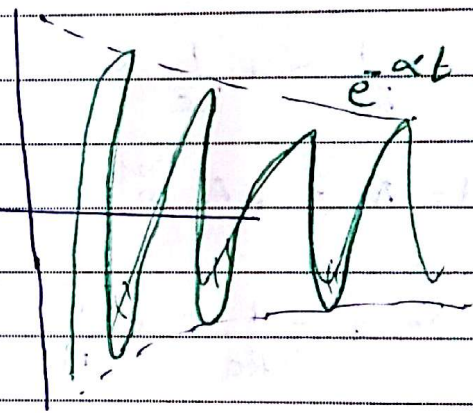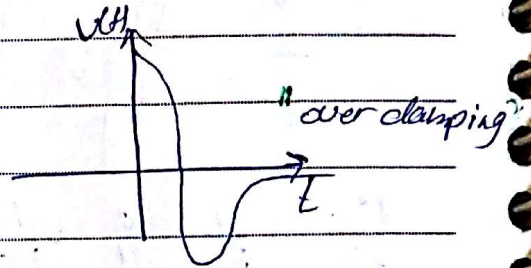
$$\begin{aligned}u(t) &= A_1 e^{s_1 t} + A_2 e^{s_2 t} \\ &= A_1 e^{(-\alpha + j\omega_d)t} + A_2 e^{(-\alpha - j\omega_d)t}\end{aligned}$$



$s_{1,2}$  are complex conjugate solution

$$u(t) = A_1 e^{(-\alpha + j\omega_d)t} + A_2 e^{(-\alpha - j\omega_d)t}$$

3)  $\alpha^2 = \omega_0^2$

→ critical damping


$$s_{1,2} = -\alpha$$

are real solution

↓  
difficult to  
obtain in practice

$$\begin{aligned}u(t) &= A_1 e^{-\alpha t} + A_2 e^{-\alpha t} \\ &= (A_1 + A_2) e^{-\alpha t} \\ &= A_0 e^{-\alpha t} \quad \times\end{aligned}$$

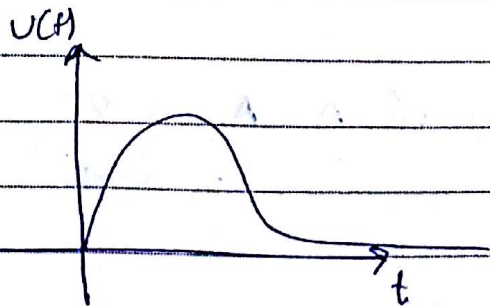
$$u(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$





$$v(t) = A e^{j\omega t} \\ = A \cos \omega t + A j \sin \omega t$$

Euler

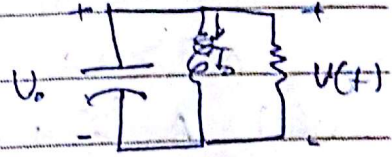

→  $\alpha^2 < \omega_0^2$  under damping

$$v(t) = A_1 e^{-\alpha t} e^{j\omega t} + A_2 e^{-\alpha t} e^{-j\omega t} \quad \text{practic}$$

$$= A_1 e^{-\alpha t} (\cos \omega t + j \sin \omega t) + A_2 e^{-\alpha t} (\cos \omega t - j \sin \omega t)$$

$$= e^{-\alpha t} \underbrace{(A_1 + A_2)}_{B_1} \cos \omega t + \underbrace{j e^{-\alpha t} (A_1 - A_2)}_{B_2} \sin \omega t$$

$$= B_1 e^{-\alpha t} \cos \omega t + B_2 e^{-\alpha t} \sin \omega t$$

$$v(0) = (V_0 = B_1) \quad \text{①}$$

$$i_L + i_L + i_R = 0$$

$$C \frac{dv_C}{dt} + I_0 + \frac{V_0}{R}$$

$$C [-B_1 e^{-\alpha t} \omega \sin \omega t - B_1 \cos \omega t \alpha e^{-\alpha t} + B_2 e^{-\alpha t} \omega \cos \omega t - B_2 \sin \omega t \alpha e^{-\alpha t}]$$

$$C [B_2 \omega d - B_1 \alpha] + I_0 + \frac{V_0}{R} = 0 \quad \text{②}$$

$$\rightarrow \alpha^2 = \omega_0^2$$

$$v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

$$v(0) = v_0 = D_2 \quad \text{--- (1)}$$

$$\text{Kcl} \quad i_c + i_L + i_R = 0$$

$$C \frac{dv_c(t)}{dt} + I_0 + \frac{V_0}{R} = 0$$

$$C \left[ -D_1 t e^{-\alpha t} + D_2 e^{-\alpha t} + D_2 (-\alpha) e^{-\alpha t} \right]$$

$$C D_1 - (C \alpha D_2 + I_0 + \frac{V_0}{R}) = 0 \quad \text{--- (2)}$$

(Characteristic of under damping)



$$\rho = \frac{V^2}{R}$$

as dissipative losses ~~decreasing~~ decreases

$\rho \downarrow$        $R \uparrow$

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$
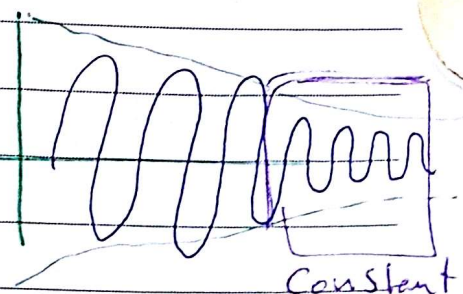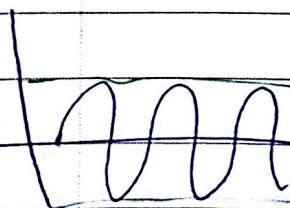
$$\rho \rightarrow 0 \quad R \rightarrow \infty \quad \alpha \rightarrow 0$$






No. 22/11/2016

→ natural response for RLC series circuits

KVL:

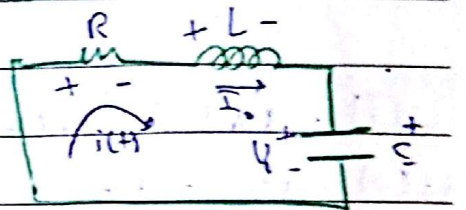

$$V_R + V_L + V_C = 0$$

$$i(t)R + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt + V_0 = 0$$

$$\frac{d}{dt} \left[ iR + L \frac{di}{dt} + \frac{1}{C} \int i dt + V_0 \right] = 0$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{1}{C} i(t) + V_0 = 0$$

→ in parallel RLC circuit

$$\alpha = \frac{1}{2RC}, \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i(t) = 0 \quad \text{--- ①}$$

→ in series RLC circuit

$$\alpha = \frac{R}{2L}, \omega_0 = \frac{1}{\sqrt{LC}}$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad \text{characteristic eqn.}$$

$$s_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Review:

→  $\alpha^2 > \omega_0^2$  over-damped case

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

→  $\alpha^2 < \omega_0^2$  under damped

$$i(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

→  $\alpha^2 = \omega_0^2$  critical

$$i(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

$$V_c(t) = L \left. \frac{di(t)}{dt} \right|_{t=0} = L \left[ \text{derive the proper equation for } i(t) \text{ depending on case of } \alpha^2 \text{ and } \omega_0^2 \text{ relationship} \right]$$

$$\alpha^2 > \omega_0^2$$

$$L \frac{di(t)}{dt} = L A_1 S_1 e^{s_1 t} + L A_2 S_2 e^{s_2 t}$$

$$V_L(t) \Big|_{t=0} = L A_1 S_1 + L A_2 S_2$$

$$I_0 R + L A_1 S_1 + L A_2 S_2 + V_0 = 0 \dots \textcircled{1}$$

$$I_0 = A_1 + A_2 \dots \textcircled{2}$$

→ To find constants  $B_1, B_2$

$\alpha^2 < \omega_0^2$  underdamped case

$$I_0 = B_1 \dots \textcircled{1}$$

$$V_R + V_L + V_C = 0$$

$$R I_0 + \overset{L\omega_0 B_2 - \alpha L B_1}{\text{---}} + V_0$$

$$V_L = L \frac{di}{dt} \Big|_{t=0}$$

$$\left. \frac{L di}{dt} \right|_{t=t_0=0} = -L B_1 e^{-\alpha t} \omega_d \sin \omega_d t + B_1 L (-\alpha) e^{-\alpha t} \cos \omega_d t$$


$$+ L B_2 e^{-\alpha t} \omega_d \cos \omega_d t + L B_2 (-\alpha) e^{-\alpha t} \sin \omega_d t$$



The step response ~~is~~ "forced response"  
for RLC parallel  
circuits

$$t > 0$$

$$I_s = i_L + i_C + i_R$$

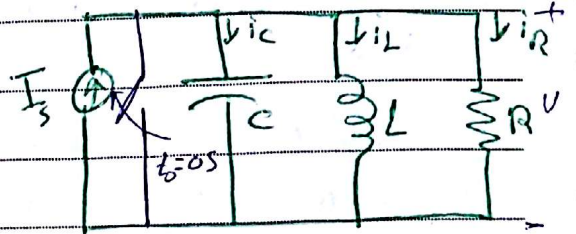

$$\frac{d}{dt} \left[ I_s = \frac{1}{L} \int_{-\infty}^t v_L(t) dt + C \frac{dv_c}{dt} + \frac{v_c}{R} \right]$$

$$\frac{1}{L} \int_0^t v_c(t) dt + I_0$$

$$0 = \frac{v}{L} + C \frac{dv}{dt^2} + \frac{1}{R} \frac{dv}{dt}$$

$$\alpha^2 > \omega_0^2 \quad \alpha^2 < \omega_0^2 \quad \alpha^2 = \omega_0^2$$

RCI :-

$$I_s = i_L + C \frac{dv}{dt} + \frac{v}{R} \quad (*)$$

$$v_L = v_C = v_R = v$$

$$v_L = L \frac{di}{dt}$$

$$\frac{dv}{dt} = L \frac{d^2 i}{dt^2}$$

back to (\*)

$$I_s = i_L + C L \frac{d^2 i}{dt^2} + \frac{L}{R} \frac{di}{dt}$$

To solve this equation 
 $\left\{ \begin{array}{l} \text{direct} \\ \text{indirect} \end{array} \right.$

$t < 0$

$V_0 = 0$  (The switch is closed)

back to  $t > 0$

$$\rightarrow \alpha^2 > \omega_0^2 \quad v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\alpha^2 < \omega_0^2 \quad v(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

$$\alpha^2 = \omega_0^2 \quad v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

$$i_L(t) = I_p + A_1' e^{s_1 t} + A_2' e^{s_2 t} \quad \alpha^2 > \omega_0^2$$

$$i(t) = I_p + B_1' e^{-\alpha t} \cos \omega_d t + B_2' e^{-\alpha t} \sin \omega_d t \quad \alpha^2 < \omega_0^2$$

$$i(t) = I_p + D_1' t e^{-\alpha t} + D_2' e^{-\alpha t} \quad \alpha^2 = \omega_0^2$$

The step response for RLC series circuit is

ku

$$-V_s + V_L + V_R + V_C = 0 \quad \text{--- (1)}$$

$$-V_s + L \frac{di}{dt} + iR + \frac{1}{C} \int_{-\infty}^t i(t') dt' = 0$$

$$0 + L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i(t) = 0$$


$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

or

$$i(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

or
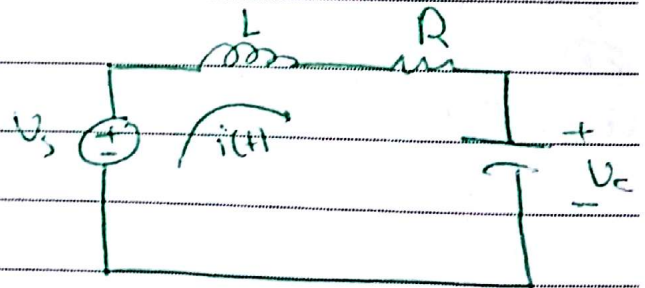
$$i(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$





~~V<sub>L</sub>~~

$$V_L = L \frac{di}{dt} \quad \text{and} \quad i_c = C \frac{dv_c}{dt}$$

Back to (\*)  $\frac{v_c}{i_c}$

$$-U_s + V_L + \underline{V_R} + V_C = 0$$

$$-U_s + L \frac{di}{dt} + iR + V_C = 0$$

$$-U_s + L \left( C \frac{dv_c}{dt} \right) + C \frac{dv_c}{dt} R + V_C = 0$$

$$-U_s + LC \frac{d^2 v_c}{dt^2} + RC \frac{dv_c}{dt} + V_C = 0$$

$$V_C(t) = V_f + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

(or)

$$V_f + B_1 e^{-\alpha t} \cos \omega_d t + e^{-\alpha t} \sin \omega_d t$$

(or)

$$V_f + D_1 e^{-\alpha t} + D_2 e^{-\alpha t}$$

## 8.7 General 2nd order RLC circuit analysis

① Determine the initial conditions

$$\begin{array}{c}
 x(t) \leftarrow \begin{array}{l} i(t) \\ v(t) \end{array} \\
 \swarrow \quad \searrow \\
 x(0) \quad , \quad \frac{dx(0)}{dt} \\
 \swarrow \quad \searrow \\
 i(0) \quad v(0) \quad \frac{di(0)}{dt} \quad , \quad \frac{dv(0)}{dt}
 \end{array}$$

② Determine the final value  $x_{ss}(t)$

$$x_{ss}(t) \xrightarrow{t \rightarrow \infty} x(\infty)$$

③ turn off all independent sources and find the transient response  $x_t(t)$  by applying kcl or kvl

④ solve the characteristic equation of 2nd order DE

$$a \frac{d^2 v}{dt^2} + b \frac{dv}{dt} + cv = 0$$

$$as^2 + bs + c = 0 \quad s_{1,2} \leftarrow$$

⑤ find the proper form of the transient response.

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \text{overdamped solution}$$

$$x(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

$$x(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$


⑥ express the total response for  $x(t)$

$$x(t) = x_t(t) + x_{ss}(t)$$





Find the values of the constants in the total solution using  $x(0)$  at  $\frac{dx(0)}{dt}$



Ex 88  
p. 335

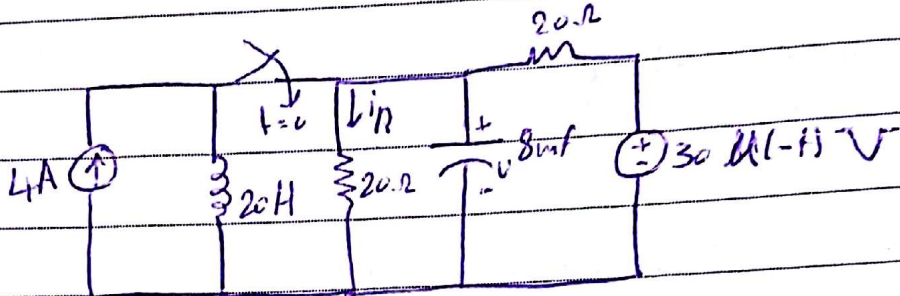


Find  $i(t)$ ,  $i_p(t)$   $t > 0$

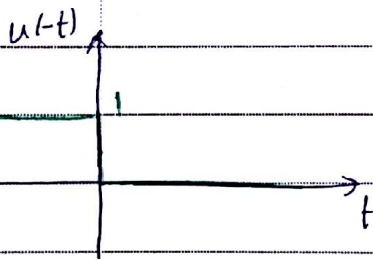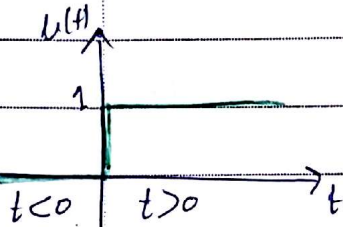



$t < 0$

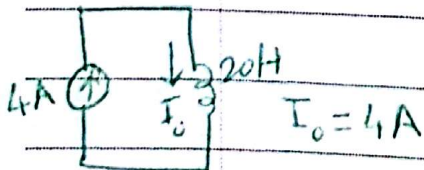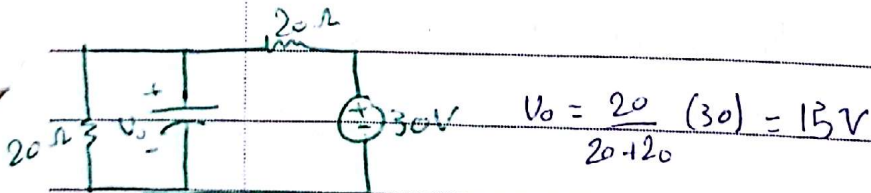

No. \_\_\_\_\_

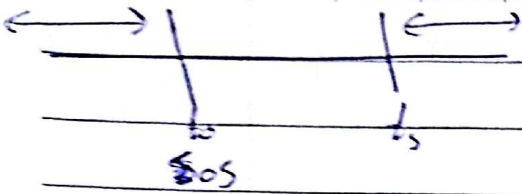



$t \rightarrow \infty$

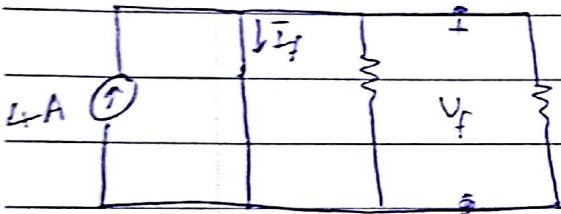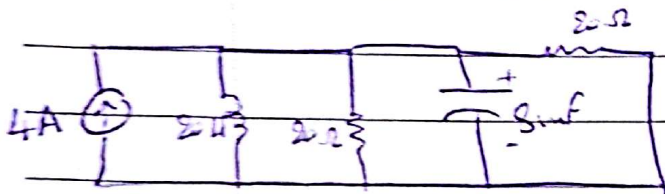

$$I_f = 4A$$

$$V_f = 0V$$

$t > 0$

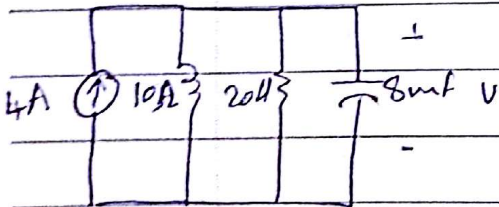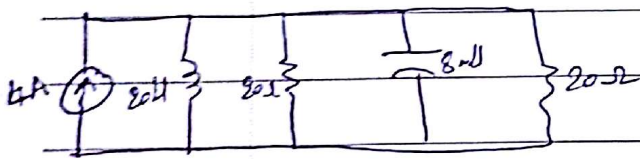

$$\alpha = \frac{1}{2Rc} = \frac{1}{2 \times 10 \times 8 \times 10^{-3}} = 6.25 \text{ rad/s}$$

$$\sqrt{\alpha^2 - \omega_0^2}$$

bigger  
So it's over damping

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 8 \times 10^{-3}}} = 2.5 \text{ rad/s}$$

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$s_{1,2} = -11.978 \text{ s}^{-1}, -0.5218 \text{ s}^{-1}$$

$$v(t) = A_1 e^{-11.978t} + A_2 e^{-0.5218t} \text{ V}$$



$$i_L(t) = \frac{V}{L} + A_1' e^{-11.978t} + A_2' e^{-0.5218t} \quad A \quad \text{--- } (*)$$

$$4 = 4 + A_1' + A_2'$$

$$A_1' + A_2' = 0 \quad \text{--- } (1)$$

$$V_L = L \frac{di_L(t)}{dt}$$

$$V_L(t) = 20 \frac{d(*)}{dt}$$


$$A_1' = -0.0655$$

$$A_2' = 0.0655$$


$$i_L(t) = 4 + 0.0655 \left[ e^{-0.521t} - e^{-11.976t} \right] A$$


Ex 8.10

P. 339


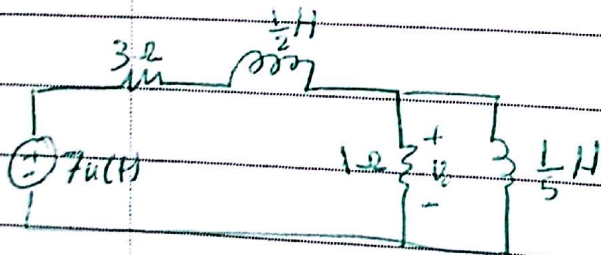


$$V_o(t) \quad t > 0$$

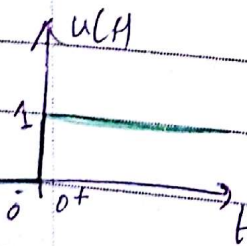

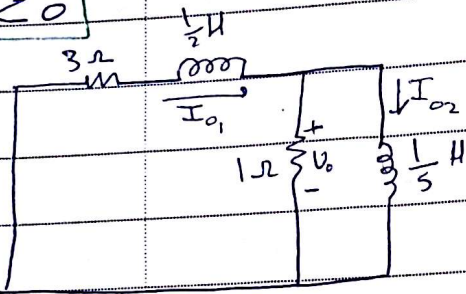
$t < 0$ 

$$I_{01} = I_{02} = 0A$$

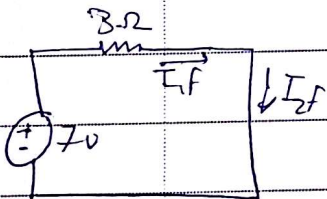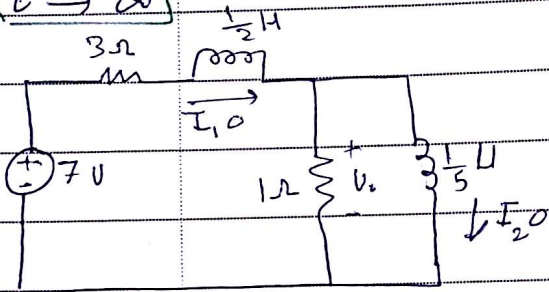 $t \rightarrow \infty$ 

$$I_{1f} = I_{1f} = \frac{7}{3}A$$



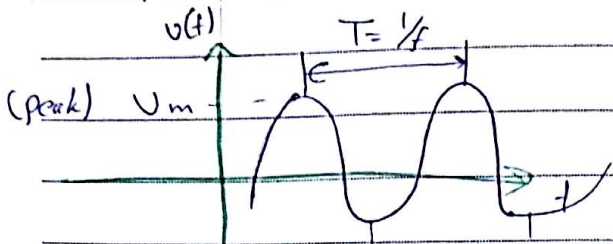


$$v(t) = V_m \cos(\omega t + \theta)$$

advance  
delay


$$i(t) = I_m$$

$$V_m \cos \omega t$$


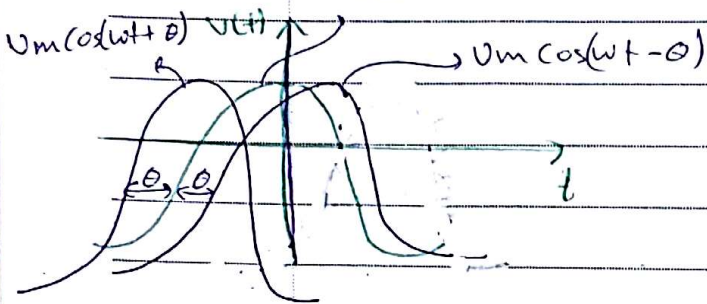


$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = 0.707 V_m$$


$V_m \cos(\omega t + \theta)$

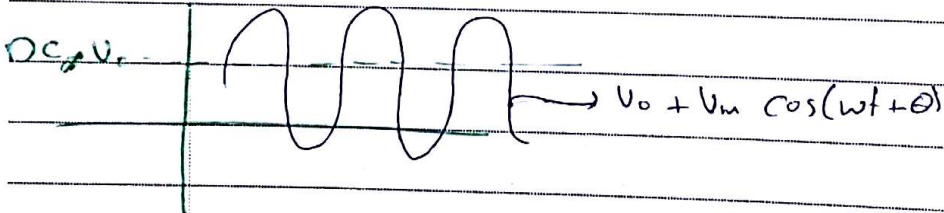
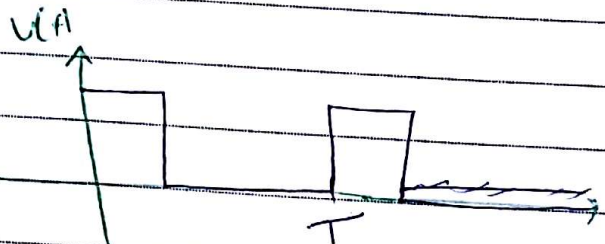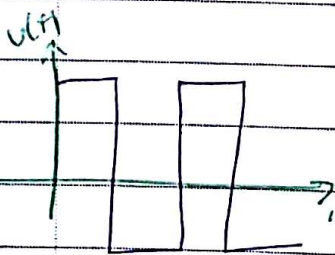
$$V_{mean} = \text{DC component of a signal} = \frac{1}{T} \int_0^T v(t) dt$$


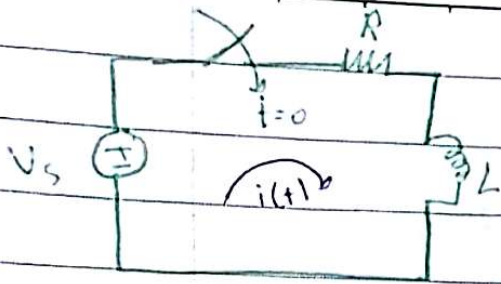
$$\frac{V(t)}{V_{rms}} \equiv \text{average?}$$




$$i(t) = I_f + (I_0 - I_f) e^{-t/\tau}$$

$$\tau = \frac{L}{R}$$

$$I_f = \frac{V_s}{R}$$

$$I_0 = 0 \text{ A}$$

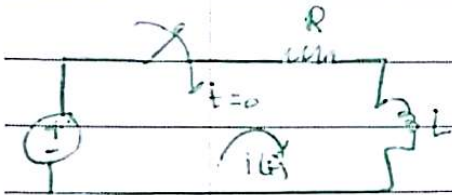

$$v_s(t) = V_m \cos(\omega t + \theta)$$

$$-v_s(t) + iR + L \frac{di}{dt} = 0$$

$$-V_m \cos(\omega t + \theta) + iR + L \frac{di}{dt} = 0$$

$$i(t) = \underbrace{-\frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\theta - \beta) e^{-\frac{R}{L}t}}_{\text{transient solution}} + \underbrace{\frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \beta)}_{\text{steady state solution}}$$

transient  
solution

$$\beta = \frac{\omega L}{R}$$

steady state  
solution


→ phasor is a complex number that carries the amplitude and phase information of a sinusoidal signal

$$v(t) = A \cos(\omega t + B)$$


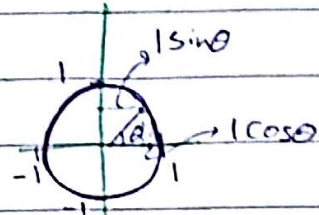
### Euler Representation

$$v(t) = \text{Re} \{ A e^{j(\omega t + \theta)} \}$$



$$= \text{Re} \{ A \cos(\omega t + \theta) + j A \sin(\omega t + \theta) \} = \text{Re} \{ A e^{j(\omega t + \theta)} \}$$

$$1 e = 1 \cos \theta + j 1 \sin \theta$$

$$= A \cos(\omega t + \theta)$$

$$\vec{V}_s(t) \rightarrow \vec{V}_s = A e^{j\theta} = A \cos \theta + j A \sin \theta$$

$$a + j b$$


phasor representation of the source voltage

$$v(t) = 5 \sin 2000t \text{ V}$$

$$= 5 \cos(2000t - \frac{\pi}{2})$$

$$j\theta_1 \cdot j\theta_2 = j(\theta_1 + \theta_2)$$

$$e \cdot e = e$$

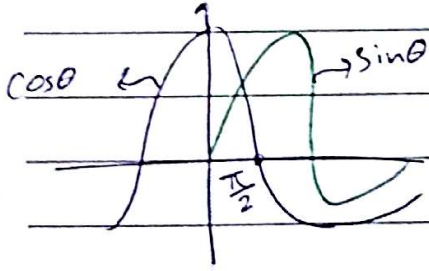

$$j\theta_1 \cdot j\theta_2 \neq j(\theta_1 + \theta_2)$$

$$e + e \neq e$$

$$\frac{j\theta_1}{e} = \frac{j(\theta_1 - \theta_2)}{e}$$


$$\frac{j\theta_2}{e}$$

$$\vec{V}_s = 5 \angle -\frac{\pi}{2} \text{ V}$$

$$= 5 \angle -90^\circ \text{ V}$$

$$-V_s + Ri + L \frac{di}{dt} = 0$$


$$Ri + L \frac{di}{dt} = V_s$$

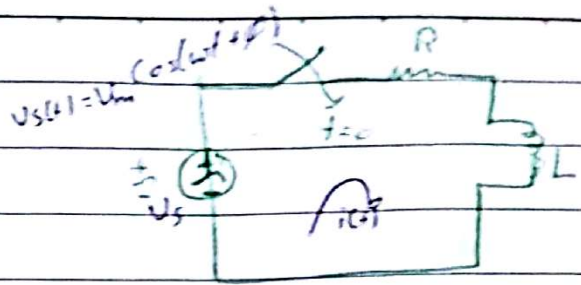

$$i(t) = I_m \cos(\omega t + \phi)$$

$$\text{Re} \{ I_m e^{j(\omega t + \phi)} \} + \text{Re} \{ j\omega L I_m e^{j(\omega t + \phi)} \} = \text{Re} \{ V_m e^{j(\omega t + \phi)} \}$$
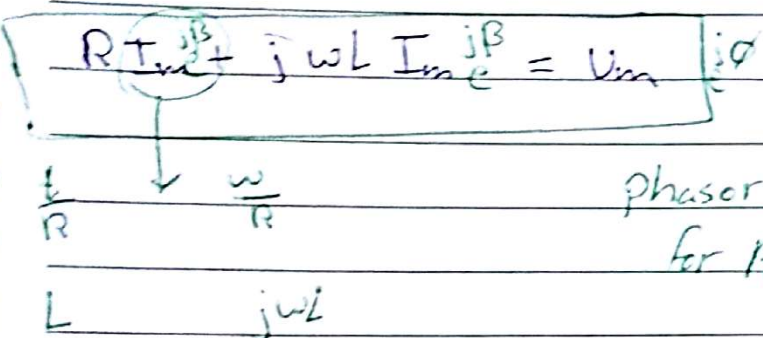
$$\frac{d}{dt} \left[ \text{Re} \left[ I_m e^{j(\omega t + \phi)} \right] \right] = \text{Re} \left[ j I_m \omega L e^{j(\omega t + \phi)} \right]$$



phasor equation for RL circuit

$$I_m e^{j\phi} [R + j\omega L] = V_m e^{j\phi}$$

$V_1(t) + V_2(t)$  time domain  $\iff$   $\vec{V}_1 + \vec{V}_2$  frequency

$$I_m = \frac{V_m}{R + j\omega L} e^{j(\phi - \beta)}$$



No. 30/11/2016

Ex 2:  $y_1 = 20 \cos(\omega t - 30^\circ)$


$y_2 = 40 \cos(\omega t + 60^\circ)$

$y_1 + y_2 \Leftrightarrow Y_1 + Y_2$

Sol:-  $y_1 = 20 \cos \omega t (\cos 30^\circ) + \sin \omega t (\sin 30^\circ)$

$y_2 = 40 \cos \omega t (\cos 60^\circ) - 40 \sin \omega t (\sin 60^\circ)$

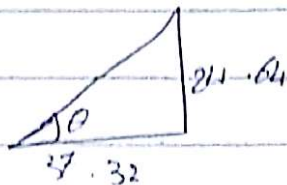$y_1 + y_2 = 37.32 \cos \omega t - 21.64 \sin \omega t$



→ phasors are complex quantities and characterized by frequency component ( ).

frequency  $\vec{I} = 10 \angle 30^\circ \text{ mA} = 10 e^{j30^\circ} = 10 [\cos 30^\circ + j \sin 30^\circ]$

$\omega = 1000 \text{ rad/sec} = 10 \frac{\cos 30^\circ}{a} + j 10 \frac{\sin 30^\circ}{b}$

$f = \frac{1}{T}$   $\omega = 2\pi f$   $i(t) = 10 \cos(1000t + 30^\circ) \text{ mA}$

$$y_1(t) + y_2(t) \leftrightarrow \vec{Y}_1 + \vec{Y}_2$$

must have same  
frequency

$$y_1 = 20 \cos(\omega t - 30^\circ) \rightarrow \vec{Y}_1 = 20 \angle -30^\circ = a + jb = 20 \cos(-30^\circ) + j20 \sin(-30^\circ)$$

$$y_2 = 40 \cos(\omega t + 60^\circ) \rightarrow \vec{Y}_2 = 40 \angle 60^\circ = c + jd = 40 \cos(60^\circ) + j40 \sin(60^\circ)$$

$$\vec{Y}_1 + \vec{Y}_2 = 37.32 + j24.64$$

$$\vec{Y}_1 + \vec{Y}_2 = 37.32 + j24.64 = \sqrt{37.32^2 + (-24.64)^2} = \frac{44.72}{37.32} + \frac{24.64}{37.32}j$$

$$= 44.72 \angle 33.43^\circ$$

$$y_1 + y_2 = 44.72 \cos(\omega t + 33.43^\circ)$$


$$\rightarrow y_1 = 20 [\cos \omega t \cos(30^\circ) + \sin \omega t \sin 30^\circ]$$

$$\rightarrow y_2 = 40 [\cos \omega t \cos(60^\circ) - \sin \omega t \sin 60^\circ]$$


$$y_1 + y_2 = \frac{44.72 \cdot 37.32}{44.72} \cos \omega t - \frac{44.72 \cdot 24.64}{44.72} \sin \omega t$$

$$= 44.72 \cos 33.43^\circ \cos \omega t - \sin 33.43^\circ \sin \omega t$$

$$= 44.72 \cos(\omega t + 33.43^\circ)$$

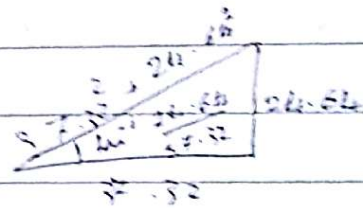



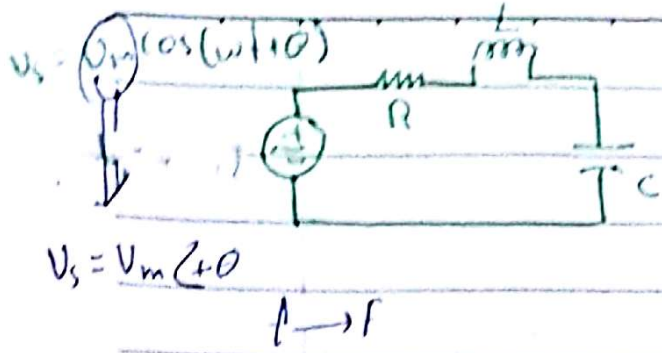

$$i = \frac{v}{R}$$

$$i = I_m \cos(\omega t + \theta_i) \text{ A}$$

$$I = I_m \angle \theta_i \text{ A}$$

$$\begin{aligned} \rightarrow V &= iR \\ &= R I_m \cos(\omega t + \theta_i) \\ &= R I_m \operatorname{Re} \left\{ \begin{matrix} e^{j(\omega t + \theta_i)} \\ e^{j\omega t} \\ e^{j\theta_i} \end{matrix} \right\} \end{aligned}$$

$$= I_m e^{j\theta_i}$$


$$\vec{V} = R \underbrace{I_m e^{j\theta_i}}_{\vec{I}_m}$$


$$\vec{V} = R \vec{I}_m \quad \text{Ohm's law}$$

↑  
impedance

$$Z = a + jb^0$$

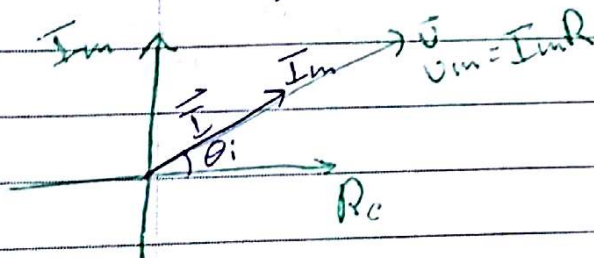→ Impedance ( $\vec{Z}$ ) is a complex number but not a phasor because no freq. component is attached to it.



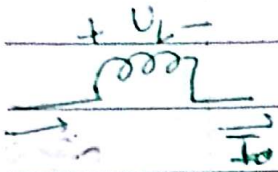

$$i = I_m \cos(\omega t + \theta_i) \text{ A}$$

$$\vec{I} = I_m e^{j\theta_i} \text{ A}$$

$$V_L = L \frac{di}{dt}$$


$$= L \frac{d}{dt} [I_m \cos(\omega t + \theta_i)]$$

$$= L I_m \omega \sin(\omega t + \theta_i)$$

$$= -L I_m \omega \cos(\omega t + \theta_i - \frac{\pi}{2})$$

$$= -L I_m \omega \text{ Re} \left\{ e^{j(\omega t + \theta_i - \frac{\pi}{2})} \right\}$$
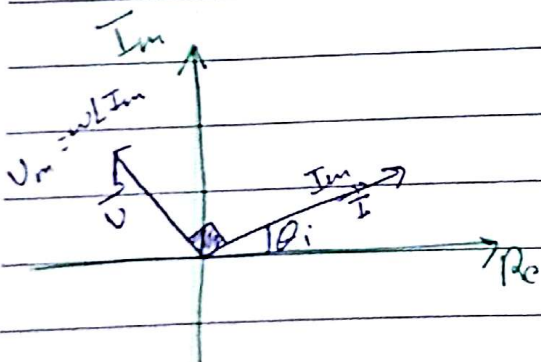
$$\vec{V} = j\omega L \underbrace{I_m e^{j\theta_i}}_I$$



$$V_L(t) = \omega L I_m \cos(\omega t + \theta_i + \frac{\pi}{2})$$

$$e^{j\frac{\pi}{2}} = \cos \frac{\pi}{2} + j \sin \frac{\pi}{2} = j$$


$$e^{-j\frac{\pi}{2}} = \cos \frac{\pi}{2} - j \sin \frac{\pi}{2} = -j$$

$$e^{j\pi} = \cos \pi + j \sin \pi = -1$$

$$\vec{V} = j\omega L \vec{I}$$

$$\vec{Z}_L$$



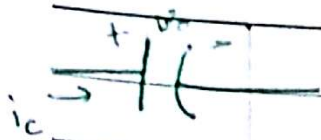

$$v_c = U_m \cos(\omega t + \theta_v)$$

$$i_c = C \frac{dv_c}{dt}$$



$$i_c = C \frac{d}{dt} [U_m \cos(\omega t + \theta_v)]$$

$$= -C U_m \omega \sin(\omega t + \theta_v)$$

$$= -C U_m \omega \cos(\omega t + \theta_v - \frac{\pi}{2})$$

$$= -C U_m \omega \operatorname{Re} \left\{ e^{j(\omega t + \theta_v - \frac{\pi}{2})} \right\}$$

$$\vec{I}_c = j\omega C U_m \vec{V}$$

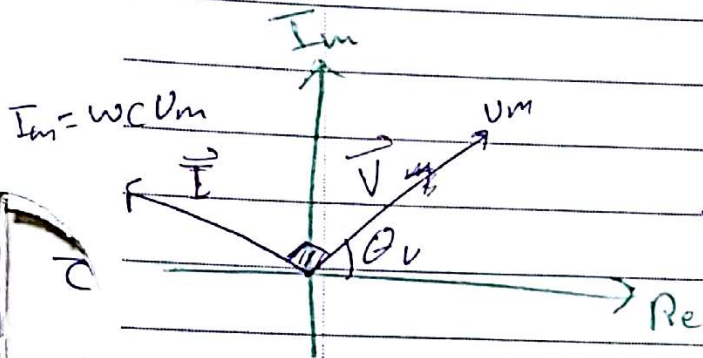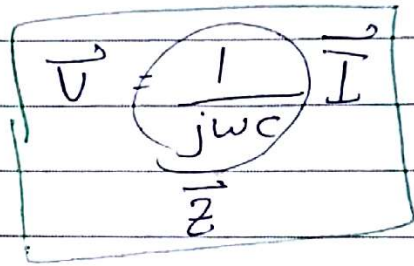




→ voltage is lagging the current

$$i(t) = I_m \cos(\omega t + \theta)$$

$$v = iR$$

$$\vec{V} = R \vec{I}$$

$R > 1$

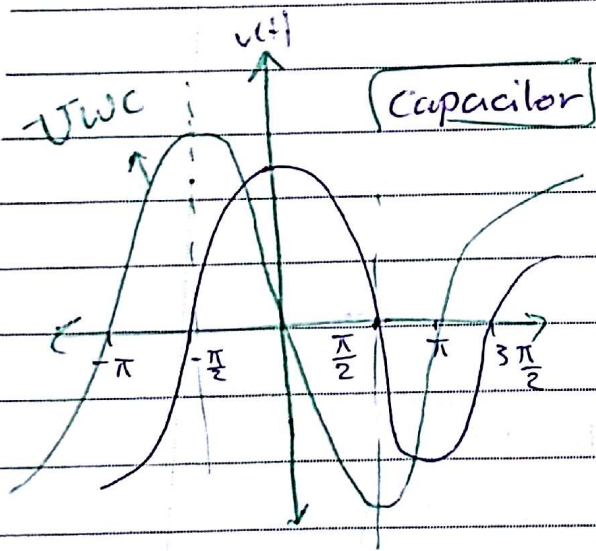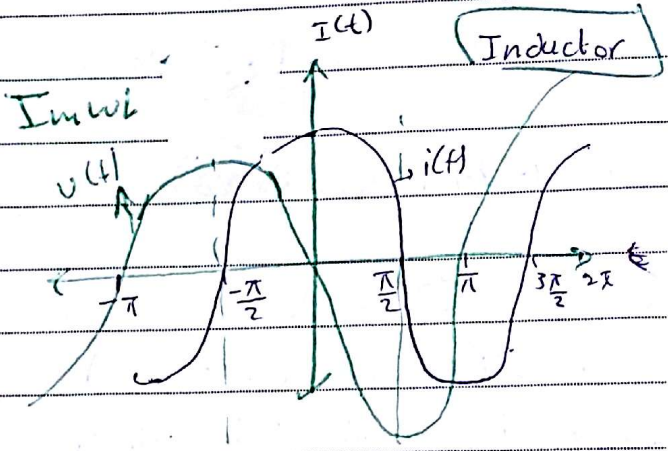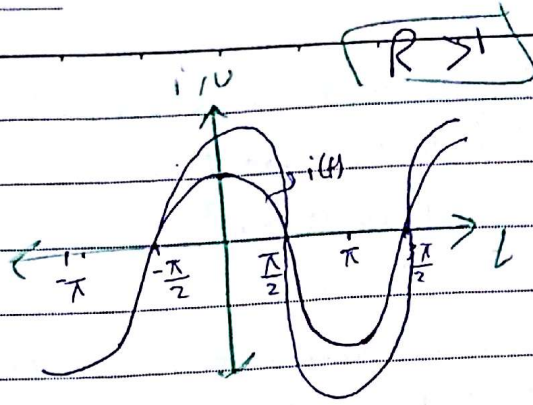



No. 1/12/2016


The current in a 20 mH inductor is  $10 \cos(10000t + 30^\circ)$  mA

$\omega = 10000$  rad/s

→ inductive reactance

$$X_L = 10000 \times 20 \times 10^{-3}$$

$$= 200 \Omega$$

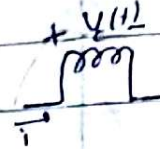

→ impedance of the inductor

$$Z = jX_L = j200 \Omega$$

$$Z = j\omega L$$

$$X_L = \omega L$$

$$\vec{V} = Z \vec{I} = j200 \cdot 10 \angle 30^\circ$$

$$= 200 \angle 120^\circ \cdot 10 \angle 30^\circ = 2000 \angle 120^\circ \text{ mV}$$

$$= 2 \angle 120^\circ \text{ V}$$

$$i(t) = 10 \cos(10000t + 30^\circ)$$

$$\vec{I} = 10 \angle 30^\circ \text{ mA}$$

$$= 10 (\cos 30^\circ + j \sin 30^\circ)$$

→ find steady state voltage

$$v(t) = 2 \cos(10000t + 120^\circ) \text{ V}$$

kirchoff's voltage and current laws in frequency domains

$$\sum_{i=1}^N v_i(t) = 0 \quad \Rightarrow \quad \sum_{i=1}^N \vec{V}_i = 0$$

$$v_1(t) = V_{m1} \cos(\omega t + \theta_1) \rightarrow V_{m1} \operatorname{Re} \left\{ e^{j(\omega t + \theta_1)} \right\}$$

$$v_2(t) = V_{m2} \cos(\omega t + \theta_2) \rightarrow V_{m2} \operatorname{Re} \left\{ e^{j(\omega t + \theta_2)} \right\}$$

⋮

$$v_N(t) = V_{mN} \cos(\omega t + \theta_N) \rightarrow V_{mN} \operatorname{Re} \left\{ e^{j(\omega t + \theta_N)} \right\}$$

$$\sum_{i=1}^N v_i(t) = v_1 + v_2 + v_3 + \dots + v_N = 0$$

$$V_{m1} \operatorname{Re} \left\{ e^{j\omega t} e^{j\phi_1} \right\} + V_{m2} \operatorname{Re} \left\{ e^{j\omega t} e^{j\phi_2} \right\} + \dots + V_{mN} \operatorname{Re} \left\{ e^{j\omega t} e^{j\phi_N} \right\} = 0$$


$$V_{m1} e^{j\phi_1} + V_{m2} e^{j\phi_2} + \dots + V_{mN} e^{j\phi_N} = 0$$

$$\vec{V}_1 + \vec{V}_2 + \dots + \vec{V}_N = 0$$

Kcl :-

$$\sum_{j=1}^N i_j(t) = 0 \Rightarrow \sum_{j=1}^N \vec{I}_j = 0$$


Series and parallel Impedance

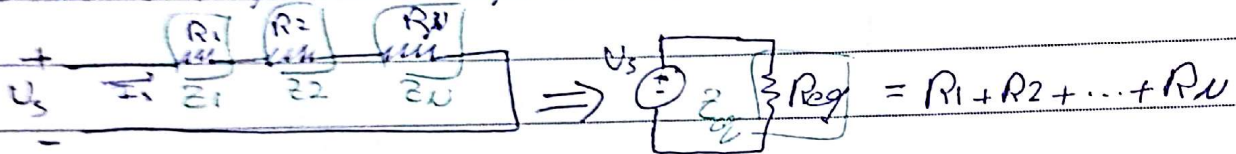

$$Z_{eq} = Z_1 + Z_2 + \dots + Z_N$$

$$V_s = I_s R_1 + I_s R_2 + \dots + I_s R_N$$

$I_s R_{eq}$

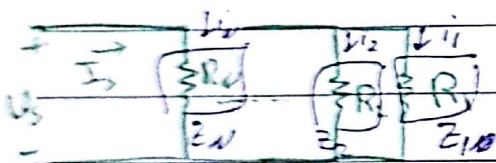

$$Z_1 = j\omega L \quad R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$


$$Z_2 = \frac{1}{j\omega C}$$

$$Z_3 = \frac{-j}{\omega C} \quad Z_{eq} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}}$$



$Z = a + jb$   
 $a \rightarrow R$   
 $b \rightarrow c$   
 $\quad \quad \quad L$   
 reactance  
 $X_L$  or  $X_C$

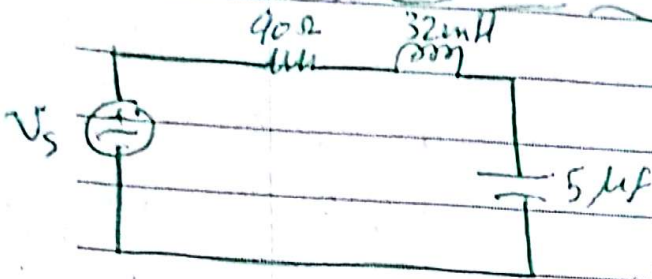
$Z = a + jb$   
 $b \equiv L \quad b > 0$   
 $b \equiv C \quad b < 0$



$V_s(t) = 750 \cos(5000t + 30^\circ) \text{ V}$


↓

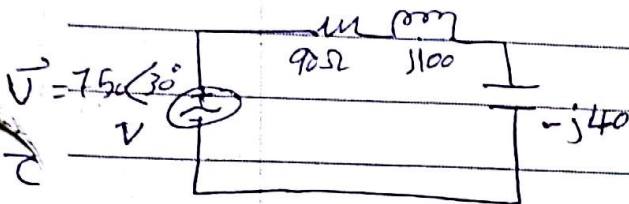find equivalent circuit in frequency domain



$Z_L = j\omega L = j 5000 \times 32 \times 10^{-3} = j160 \Omega$

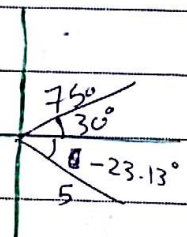$Z_C = \frac{1}{j\omega C} = -j \frac{1}{5000 \times 5 \times 10^{-6}} = -j40 \Omega$



→ calculate the steady state current?

$\vec{I} = \frac{\vec{V}}{Z_{eq}} = \frac{750 \angle 30^\circ}{150 \angle 53.13^\circ} = 5 \angle -23.13^\circ \text{ A}$

$Z_{eq} = Z_R + Z_L + Z_C = 90 + j160 - j40$   
 $= 90 + j120 = 150 \angle 53.13^\circ \Omega$

Admittance  $Y$  unit is Siemens (S)

$$Y = \frac{1}{Z}$$

resistance

$$\frac{1}{R+jX} \cdot \frac{R-jX}{R-jX}$$

$$Z = R + jX \leftarrow \text{reactance}$$

$$\frac{R-jX}{R^2+X^2}$$

$$Y = G + jB$$

conductance


susceptance

$$\frac{R}{R^2+X^2} - j \frac{X}{R^2+X^2}$$

$$G + jB$$

$$G = \frac{1}{R}$$

$$B = \frac{1}{X}$$

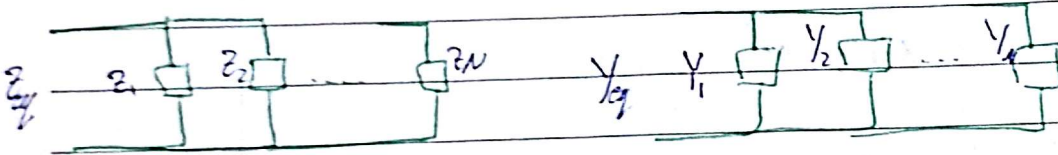


$$Z_{eq} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}}$$

$$Y_{eq} = Y_1 + Y_2 + \dots + Y_N$$


	symbol	impedance	reactance	Admittance	Susceptance
Resistor	R	$Z_R = R$	0	$Y = \frac{1}{R}$	0
inductor	L	$Z = j\omega L$	$\omega L$	$Y = \frac{1}{j\omega L}$	$-\frac{1}{\omega L}$
Capacitor	C	$Z = \frac{1}{j\omega C}$ $\Downarrow$ $-\frac{j}{\omega C}$	$-\frac{1}{\omega C}$	$Y = j\omega C$	$\omega C$



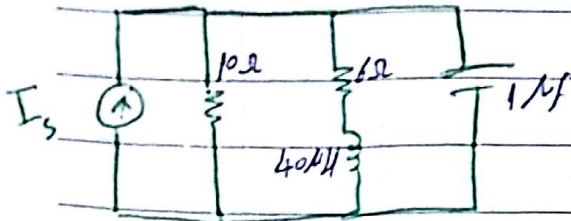

$$i_s(t) = 8 \cos(200000t)$$

$$\omega = 200000 \text{ rad/sec}$$

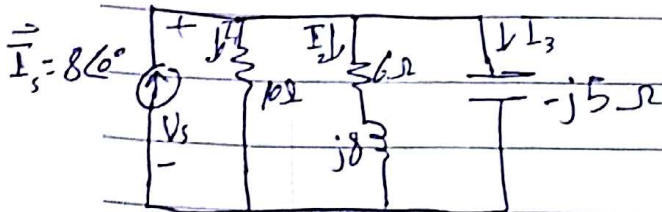

$$Z_L = j\omega L = j 200000 \times 40 \times 10^{-6} = j8 \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j 200000 \times 1 \times 10^{-6}} = -j5 \Omega$$

$$Y_1 = \frac{1}{10} \text{ S}, \quad Y_2 = \frac{1}{6+j8} = \frac{1}{\sqrt{6^2+8^2}} \angle \tan^{-1} \frac{8}{6}$$

$$Y_3 = \frac{1}{-j5} = 0.2j \text{ S}$$

$$Y_{eq} = Y_1 + Y_2 + Y_3 = 0.06 - j0.08 \text{ S}$$


$$= 0.16 + j0.12$$

$$0.2 \angle 36.87^\circ \text{ S}$$

$$\vec{V} = Z \vec{I}$$

$$Z = \frac{1}{Y} = \frac{1}{0.2 \angle 36.87^\circ} = 5 \angle -36.87^\circ \Omega$$
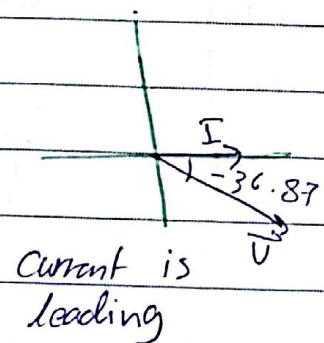
$$V = 5 \angle -36.87^\circ \cdot 8 \angle 0^\circ = 40 \angle -36.87^\circ$$




Current is leading

No. 6/12/2016

$$v(t) = 40 \cos(200000t - 36.87^\circ)$$

$$\vec{I} = \frac{40}{10} \angle -36.87^\circ = 4 \angle -36.87^\circ \text{ A}$$

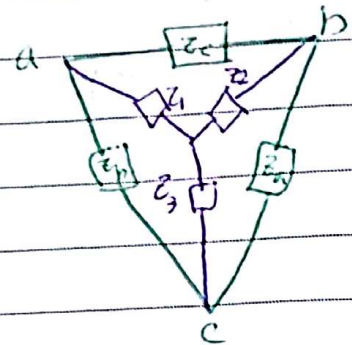Delta - to - wye conversion and vice versa



$\Delta - Y$

$$Z_1 = \frac{Z_c Z_b}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_b Z_a}{Z_a + Z_b + Z_c}$$

$Y - \Delta$

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_3}$$

Time domain

$$\frac{dv(t)}{dt}$$



frequency domain

$$j\omega \vec{v}$$

$$\int v(t) dt$$



$$\frac{v}{j\omega}$$



$$v(t) = V_m \cos(\omega t + \phi) \Rightarrow \vec{V} = V_m \angle \phi$$

$$\frac{dv(t)}{dt} = V_m \omega \sin(\omega t + \phi) = \text{Re} \left\{ V_m e^{j(\omega t + \phi)} \right\}$$


$$= \text{Re} \left\{ V_m e^{j\omega t} e^{j\phi} \right\}$$

$$= -V_m \omega \cos(\omega t + \phi - \pi)$$

$$= -V_m \omega \phi e^{j\omega t} e^{j\phi} e^{-j\frac{\pi}{2}}$$

$$= j\omega (V_m e^{j\omega t} e^{j\phi})$$

### Example :-

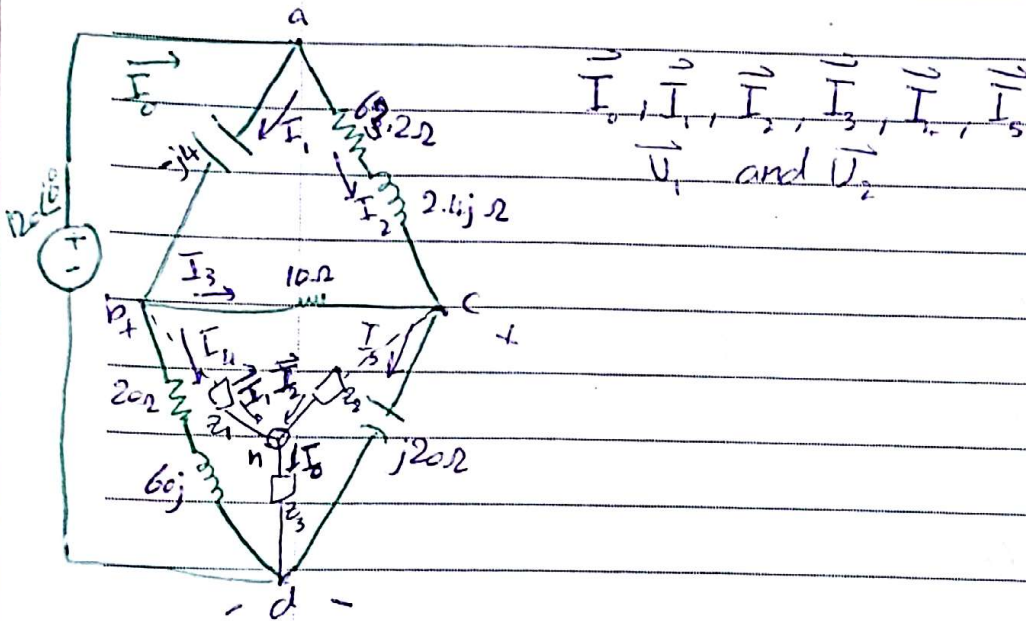

$$Z_1 = \frac{(10)(20 + j60)}{10 + 20 + j60 - j20}$$

$$= \frac{200 + j600}{30 + j40} \cdot \frac{30 - j40}{30 - j40} \quad \text{method (1)}$$

$$\frac{|\vec{z}_1| \angle \theta_1}{|\vec{z}_2| \angle \theta_2} = \frac{\vec{z}_1 \angle \theta_1}{\vec{z}_2 \angle \theta_2} \quad \text{method (2)}$$

$$= 12 + j4 \Omega$$

No. \_\_\_\_\_

$$Z_2 = \frac{(10)(-j20)}{30 + j40} = -3.2 - j2.4 \Omega$$


$$Z_3 = \frac{(-j20)(20 + j60)}{30 + j40} = 8 - j24 \Omega$$

$$Z_{abn} = -j4 + 12 + j4 = 12 \Omega$$

$$Z_{acn} = 63.2 + j2.4 - 3.2 - j2.4 = 60 \Omega$$


$$Z_{abn} \parallel Z_{acn} = \frac{12 \times 60}{12 + 60} = 10 \Omega$$
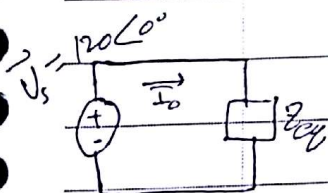
$$Z_{eq} = 10 + 8 - j24 = 18 - j24 \Omega$$



$$\vec{I}_0 = \frac{\vec{V}}{Z_{eq}} = \frac{120 \angle 0^\circ}{18 - j24} = \frac{120 \angle 0^\circ}{30 \angle -53.13^\circ} = 4 \angle 53.13^\circ \text{ A}$$

$$= 2.4 + j3.2 \text{ A}$$

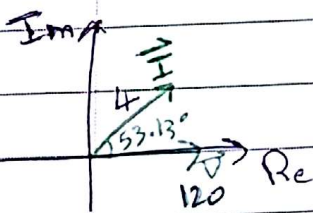

$$\begin{aligned} \vec{V}_{nd} &= \vec{I}_0 \cdot Z_3 \\ &= 4 \angle 53.13^\circ (8 - j24) \\ &= 4 \angle 53.13^\circ \cdot 11 \angle 0^\circ \\ &= 96 - j32 \text{ V} \end{aligned}$$

kvl

$$-\vec{V}_s + \vec{V}_{an} + \vec{V}_{nd} = 0$$

$$\vec{V}_{an} = \vec{V}_s - \vec{V}_{nd}$$

$$= 120 \angle 0^\circ - 96 - j32 = 24 + j32 \text{ V}$$



No. \_\_\_\_\_

$$\vec{I}_1 = \frac{\vec{V}_{an}}{Z_1 + (-j4)} = \frac{24 + j32}{12} = 2 + j2.67 \text{ A}$$

$$\vec{I}_2 = \frac{\vec{V}_{an}}{63.2 + j2.4 + 22} = \frac{24 + j32}{60} = 0.4 + j0.53 \text{ A}$$

KVL  $\quad \quad \quad V_1$

$$-\vec{V}_s + \vec{V}_{ab} + \frac{\vec{V}}{bd} = 0$$

$$\begin{aligned} \vec{V}_1 &= \vec{V}_s - \vec{V}_{ab} \\ &= 120 \angle 0^\circ - (\vec{I}_1 \cdot (j4)) = 109.32 + j8 \text{ V} \end{aligned}$$

KVL  $\quad \quad \quad V_2$

$$-\vec{V}_3 + \vec{V}_{ac} + \frac{\vec{V}}{cd} = 0$$

$$\begin{aligned} \vec{V}_2 &= \vec{V}_3 - \vec{V}_{ac} = 120 \angle 0^\circ - (\vec{I}_2 \cdot (63.2 + j24)) \\ &= 96 - j34.46 \text{ V} \end{aligned}$$


KCL:

$$\begin{aligned} \vec{I}_1 &= \vec{I}_3 + \vec{I}_4 \\ \vec{I}_3 &= \vec{I}_1 - \vec{I}_4 \\ &= 1.33 + j4.27 \text{ A} \end{aligned}$$

$$\vec{I}_4 = \frac{V_1}{20 + j60}$$

$$= 0.667 - j1.6 \text{ A}$$
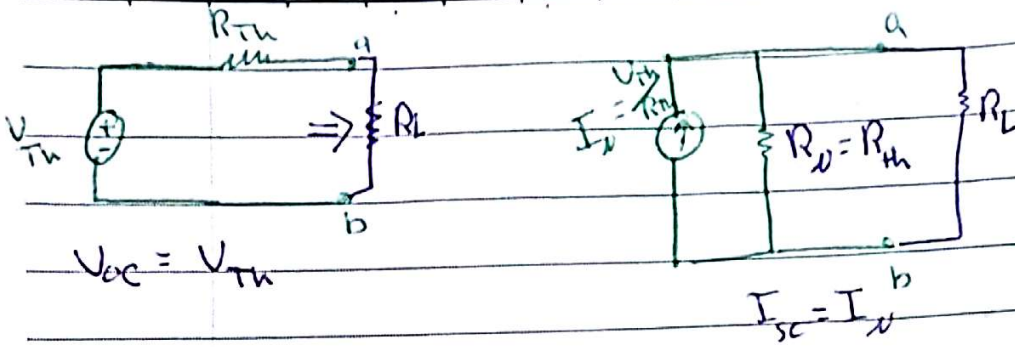
$$\vec{I}_5 = \frac{V_2}{-j20} = 1.72 + j4.8 \text{ A}$$




independent sources only

independent and dependent

dependent sources only



$$R_{Th} = \frac{V_{Th} - V_{oc}}{I_N - I_{sc}}$$

$V_{Th}$  doesn't exist only  $R_{Th}$


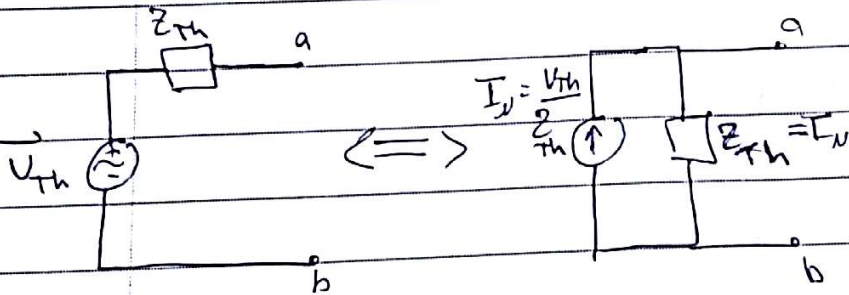




No. \_\_\_\_\_

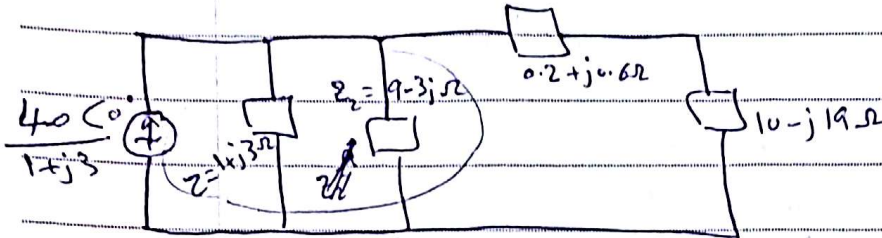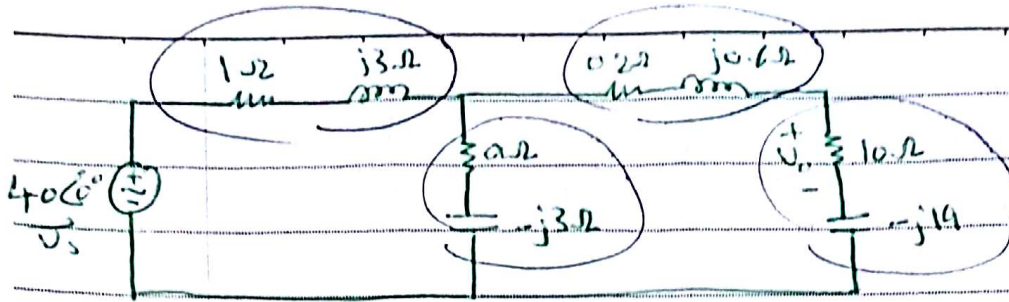
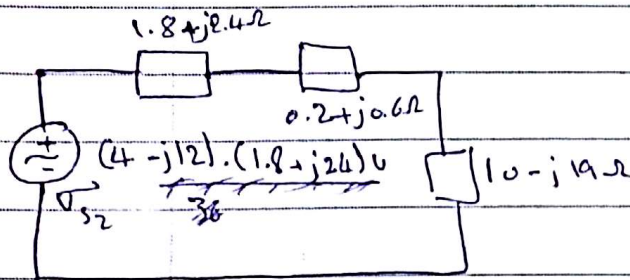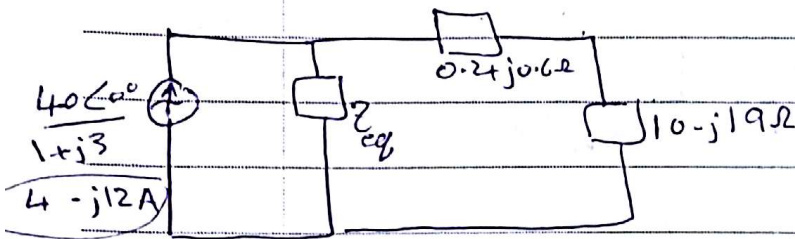
$$Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(1+j3)(9-j3)}{1+j3+9-j3} = 1.8 + j2.4 \Omega$$



$$V_{s2} = 36 - j12 \text{ V}$$



$$Z_{eq2} = 1.8 + j2.4 + 0.2 + j0.6 = 2 + j3 \Omega$$

$$V_o' = \frac{Z_L}{Z_L + Z_{eq2}} \cdot V_{s2}$$


$$V_o = \frac{10}{10 + (-j19)} \cdot V_o'$$

$$= \frac{10 - j14}{10 - j19 + 2 + j3} \cdot (36 - j12) = 36.12 - j18.84 \text{ V}$$

No.

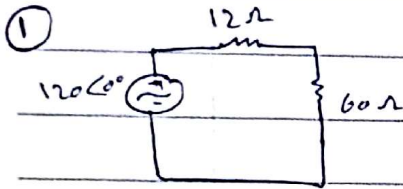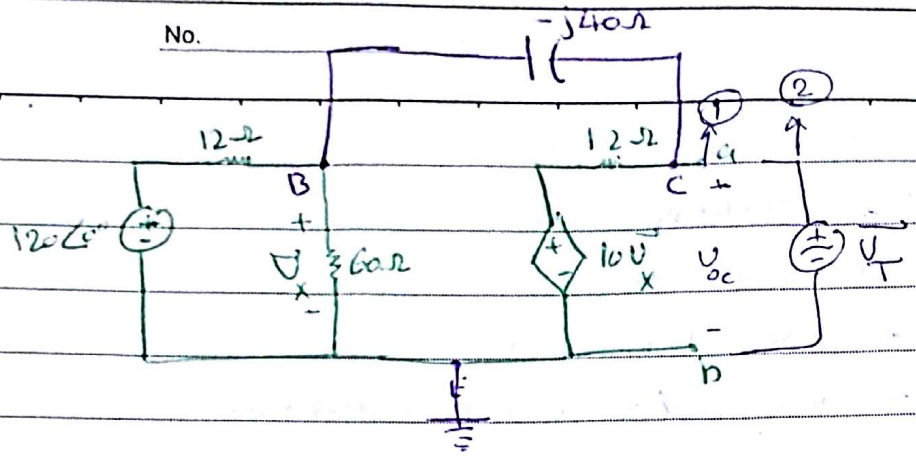
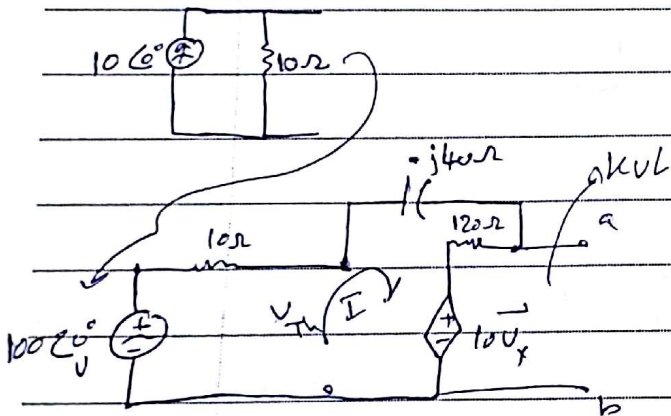
$$= 10 \angle 0^\circ = \frac{120 \angle 0^\circ}{12} \Rightarrow \frac{60 \times 12}{60 + 12} = \frac{720}{72} = 10 \Omega$$



$$-10 \vec{V}_x - 120 \vec{I} + \vec{V}_{Th} = 0$$

$$-V_s + 10\vec{I} - j40(\vec{I}) + 120\vec{I} + 10\vec{V}_x = 0$$

$$-V_s + 10\vec{I} - 40j\vec{I} + 120\vec{I} + 10[100 - 10\vec{I}] = 0$$

$$\vec{V}_{Th} = 10 \vec{V}_x + 120 \vec{I}$$

$$\vec{I} = \frac{900}{-30 + j40} \quad A = \frac{-10.8 - j14.4}{1}$$




$$\vec{V}_{Th} = 10 [100 - 10\vec{I}] + 120\vec{I} = 1000 - 100\vec{I} + 120\vec{I} = 1000 + 20\vec{I}$$

$$\vec{V}_{Th} = 1000 + 20\vec{I}$$

$$= 18 \angle -26.87^\circ A$$





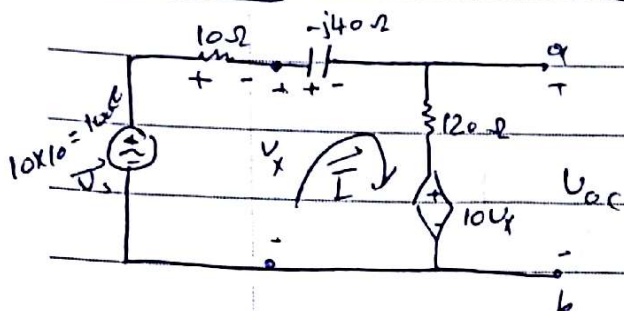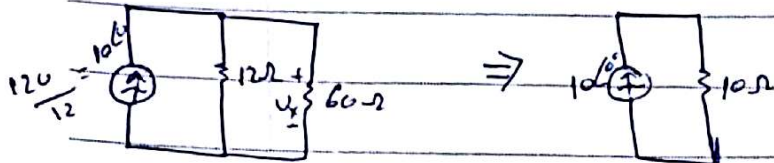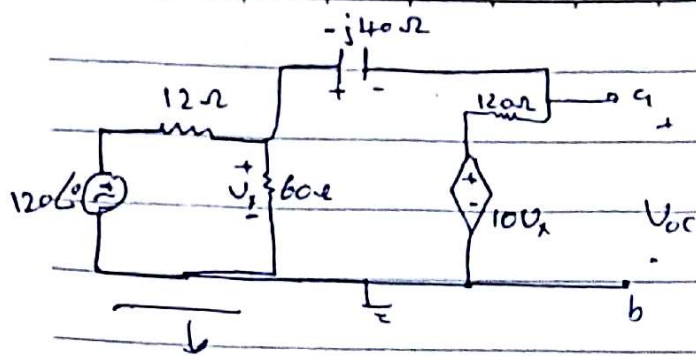

$$\text{KVL: } -10V_x - 120\vec{I} + V_{oc} = 0$$

$$V_{oc} = 10V_x + 120\vec{I}$$

$$\text{but } V_x = 100 < 0 - 10\vec{I}$$

$$\text{So } V_{oc} = 10(100 - 10\vec{I}) + 120\vec{I}$$

$$= 1000 + 20\vec{I} \dots \textcircled{1}$$

$$\text{KVL: } -100 + 10\vec{I} - j40\vec{I} + 120\vec{I} + 10(100 - 10\vec{I}) = 0$$

$$-100 + 130\vec{I} - j40\vec{I} + 1000 - 100\vec{I} = 0$$

$$\vec{I}(30 - j40) = -900$$

$$\vec{I} = -10.8 - j14.4 \text{ A} \dots \textcircled{2}$$

Substituting ② in ①

$$V_{oc} = V_{Th} = 1000 + 20(-10.8 - j14.4)$$

$$= 1000 - 216 - j288$$

$$V_{Th} = 784 - j288 \text{ V}$$


Nodal voltage method :-

① \* of equations


\* of nodes : n

\* of essential nodes : n<sub>e</sub>



\* of inde. and dep. voltage sources : m

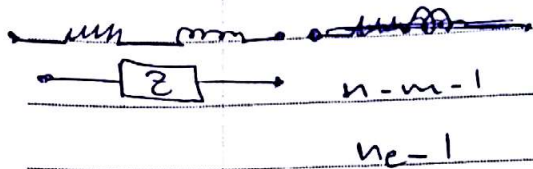

② every branch has inde impedance

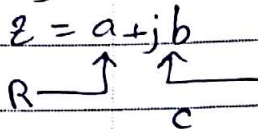
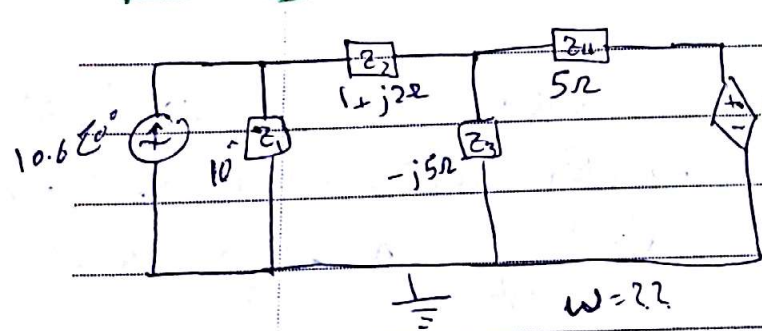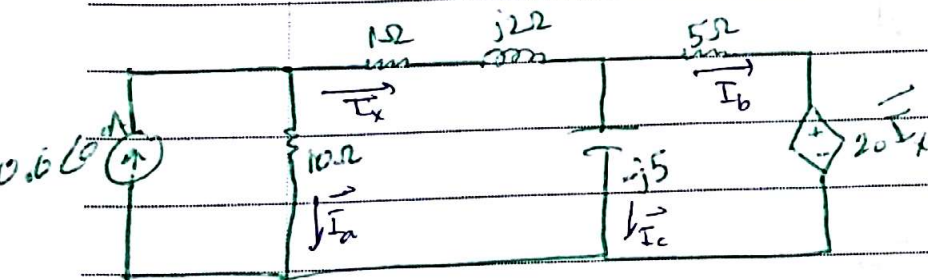
$$Z = R + j\omega L + \frac{1}{j\omega C}$$



$$n_e = 3 \quad n = 4 \quad m = 1$$

$$n_e - 1 = 3 - 1 = 2$$

$$n - m - 1 = 4 - 1 - 1 = 2$$

$$+10.6 - \frac{\vec{V}_a}{Z_1} - \frac{\vec{V}_a - \vec{V}_b}{Z_2} = 0$$


$$10.6 - \frac{\vec{V}_a}{10} - \frac{\vec{V}_a - \vec{V}_b}{1 + j2} = 0$$

$$10.6 + 0.1 \frac{\vec{V}_a}{1 + j2} = \frac{\vec{V}_a - \vec{V}_b}{1 + j2} = 0$$

$$10.6(1 + j2) - 0.1 \frac{\vec{V}_a}{1 + j2} (\vec{V}_a - \vec{V}_b) = 0$$
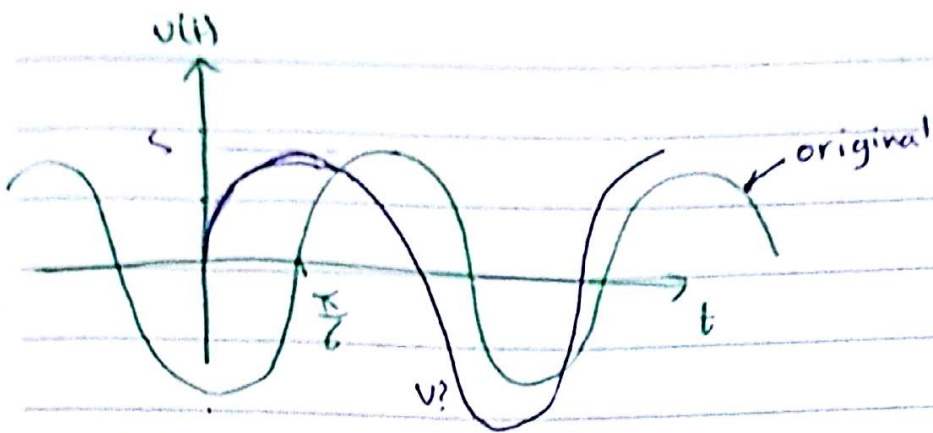
$$25j \vec{V}_a + (3 - 24j) \vec{V}_b = 0 \dots \textcircled{1}$$






$v'(t)$

$$v(t) = 5 \sin(\omega t + \phi)$$

$$= 5 \sin(\omega t + -\frac{\pi}{6})$$

$$= 5 \sin(\omega t - \frac{\pi}{6} - \frac{\pi}{2})$$

$$= 5 \cos(\omega t - \frac{4\pi}{6})$$

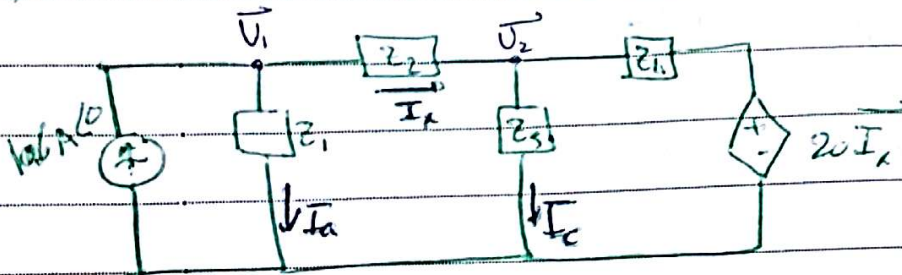

$$Z_1 = 10 \Omega \quad Z_2 = 1 + j2 \Omega \quad Z_3 = -j5 \Omega \quad Z_4 = 5 \Omega$$

$$n_e = 3$$

$$n_e - 1 = 3 - 1 = 2$$

$$n = 4$$

$$m = 1$$

$$n - m - 1 = 4 - 1 - 1 = 2$$

$$\textcircled{1} 10.6 = \frac{\vec{V}_1 - \vec{V}_2}{1 + j2} - \frac{\vec{V}_1}{10} = 0$$

$$\textcircled{2} \frac{\vec{U}_1 - \vec{U}_2}{1+j2} - \frac{\vec{U}_2}{-j5} - \frac{\vec{U}_2 - 20\vec{I}_x}{5} = 0$$


$$\vec{U}_2 = 68 - j26 \text{ V}$$

$$\vec{U}_1 = 68.40 - j16.8 \text{ V}$$

$$\vec{I}_x = 3.76 + j1.68 \text{ A}$$

$$\vec{I}_b = -1.44 - j11.92 \text{ A}$$

$$\vec{I}_c = 5.2 + j13.6 \text{ A}$$

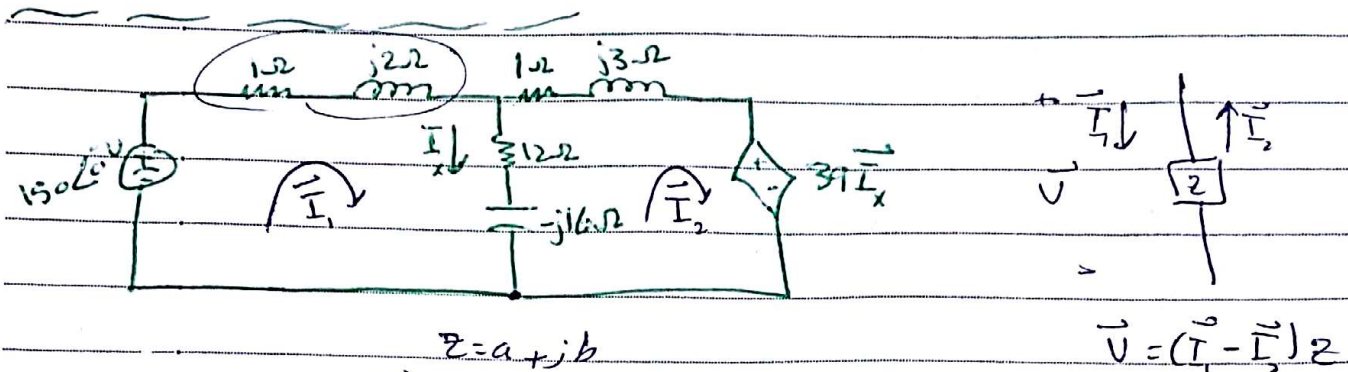

$$\vec{U} = (\vec{I}_1 - \vec{I}_2) Z$$

$$\rightarrow -150 + (1+j2)\vec{I}_1 + (12-j16)(\vec{I}_1 - \vec{I}_2) = 0$$

$$-(\vec{I}_1 - \vec{I}_2)(12-j16) + \vec{I}_2(1+j3) + 39\vec{I}_x = 0$$

$$\vec{I}_x = \vec{I}_1 - \vec{I}_2$$

$$\vec{I}_x = -2 + 6j \text{ A}$$

$$\vec{I}_1 = -26 - 52j \text{ A}$$

$$\vec{I}_2 = -24 - j58 \text{ A}$$


$$\vec{U}_1 = (1+j2)\vec{I}_1 = 78 - j104 \text{ V}$$

$$\vec{U}_2 = (12+j16)\vec{I}_x = 72 + j104 \text{ V}$$

$$\vec{U}_3 = (1+j3)\vec{I}_2 = 150 - j130 \text{ V}$$




### Example 2-

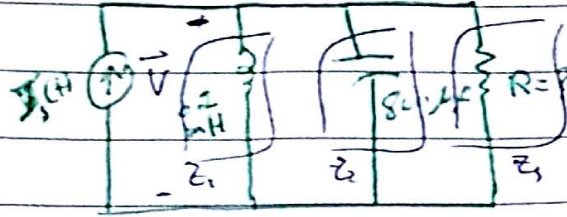

Use phasor diagram to find R?!


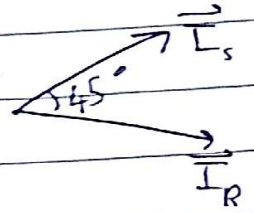
which cause the current through the resistor to lag the source current by  $45^\circ$   $\omega = 5 \text{ k rad/sec}$



$$\begin{aligned} \text{Sol :- } Z_1 &= j\omega L \\ &= j 5000 \times 0.2 \times 10^{-3} \\ &= j1 \Omega \end{aligned}$$

$$Z_2 = \frac{1}{j\omega C}$$
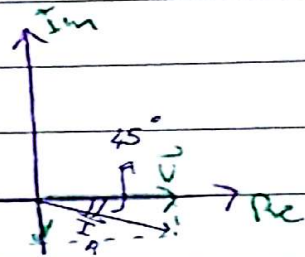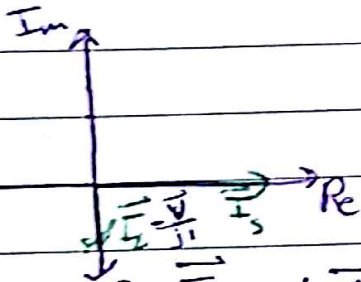
$$= -j \frac{1}{5000 \times 800 \times 10^{-6}} = -j1.25 \Omega$$




phase of  $\vec{I}_0$  and  $\vec{V}$  are the same.

$$\vec{I}_C = \frac{\vec{V}}{Z_C} = \frac{\vec{V}}{-j4} = j \frac{\vec{V}}{4}$$


$$\vec{I}_S = \vec{I}_C + \vec{I}_L + \vec{I}_R \quad \Rightarrow \quad \vec{I}_R = \vec{I}_S - (\vec{I}_L + \vec{I}_C)$$

$$\vec{I}_L = \frac{\vec{V}_s}{Z_L} = \frac{V_m \angle 0^\circ}{j\omega L} = \frac{V_m}{j5 \times 10^3 \times 0.2 \times 10^{-3}} = \frac{V_m}{j} = -jV_m$$
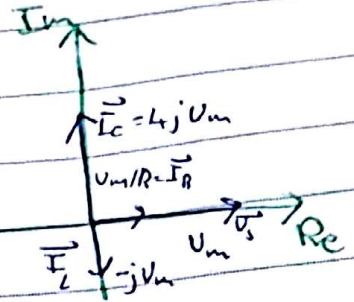
$$\vec{I}_C = \frac{\vec{V}_s}{Z_C} = \frac{V_m \angle 0^\circ}{\frac{1}{j\omega C}} = j\omega C V_m \angle 0^\circ = j5 \times 10^3 \times 800 \times 10^{-6} V_m = j4 V_m \text{ A}$$


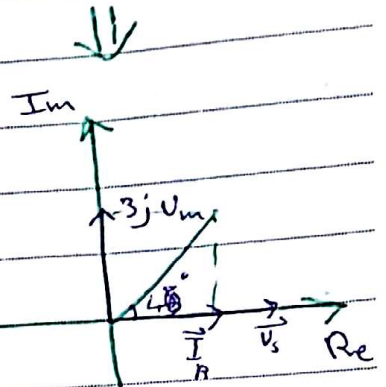
$$\vec{I}_R = \frac{\vec{V}_s}{R} = \frac{V_m \angle 0^\circ}{R} = \frac{V_m}{R}$$



$$\tan 45^\circ = \frac{3V_m}{\frac{V_m}{R}}$$

$$1 = 3R$$

$$R = \frac{1}{3}$$