

# Lap Physics2 Reports

POWERUNIT

# LAB REPORT FOR EXPERIMENT 1

**Date:** \_\_\_\_\_

Name: \_\_\_\_\_

**Partner's Name:** \_\_\_\_\_

**Registration No:-**

**Registration No:-**

**Physics Section:** \_\_\_\_\_

Instructor's Name: Dr. Yehya Rumaeeen

PHYSICS LAB EXPERIMENT 1: ELECTRIC FIELD MAPPING

## 1 PURPOSE

**1. PURPOSE**  
We'll plot several electrode configurations by determining the equipotential line and the drawing of the lines of forces

## II. DATA AND DATA ANALYSIS

## A Mapping The Equipotential Lines

- 1- Enter your data in Table 1.1 below:

Table (1.1 a)

**For one type of electrodes:**

ther type of electrodes:

Table (1.1 b)

Location of P (position of equipotential point)

P <sub>1</sub>	P <sub>2</sub>	P <sub>3</sub>	P <sub>4</sub>	P <sub>5</sub>
(-8.2, -3)	(3.2, -6.5)	(9.2, +4)		
(-8.1, -4.1)	(3.2, -3)	(9.4, -2.4)		
(-8.2, -1.2)	(3.1, -5)	(11.3, -4.3)		
(-8.2, 2.5)	(3.1, 3.3)	(9.5, 2.4)		
(-8.1, 1.6)	(3.2, -6)	(11, 3.9)		

2- Use your data of Table (1.1a) and Table (1.1 b) to plot the equipotential points on two sheets of graph paper.

3- Connect the **eight** points corresponding to each location P<sub>i</sub> with a line which is an **equipotential line**.

4- On the same graph, draw the lines of force. These are everywhere **perpendicular** to the equipotential lines, explain **why**.

$$V = qA / \epsilon_0 = F \cdot x$$

$$= qE_x$$

$$\theta = qE_x \cos A$$

$$\text{then } \cos \theta = 0$$

$$\therefore \theta = 90^\circ$$

## Measurement of The Electric Field

The data in Table (1.2) below are  $V$  in volts and  $d$  in centimeters.

Table 1.2

$V$ (volt)	$d$ (cm)
zero	zero
1	3.5
2	6
3	13.5
4	17
4.15	18

1. Plot  $V$  (as dependent variable ) versus  $d$ .

Find the slope of your graph.

$$\text{Slope} = \frac{\Delta V}{\Delta d} = C = \frac{2-1}{8.5-4.3} = \frac{1}{4.2} \text{ v/c}$$


---



---

2. How is the slope related to the electric field ?

Slope = electric field and it's constant


$$E = \frac{\Delta V}{\Delta d} = \frac{1}{4.2} \text{ volt/cm} = 0.23$$


---


3. What conclusion can you draw about the electric field in the region between the electrodes near the center?


it is constant

(Graph (1) one type of electrodes)

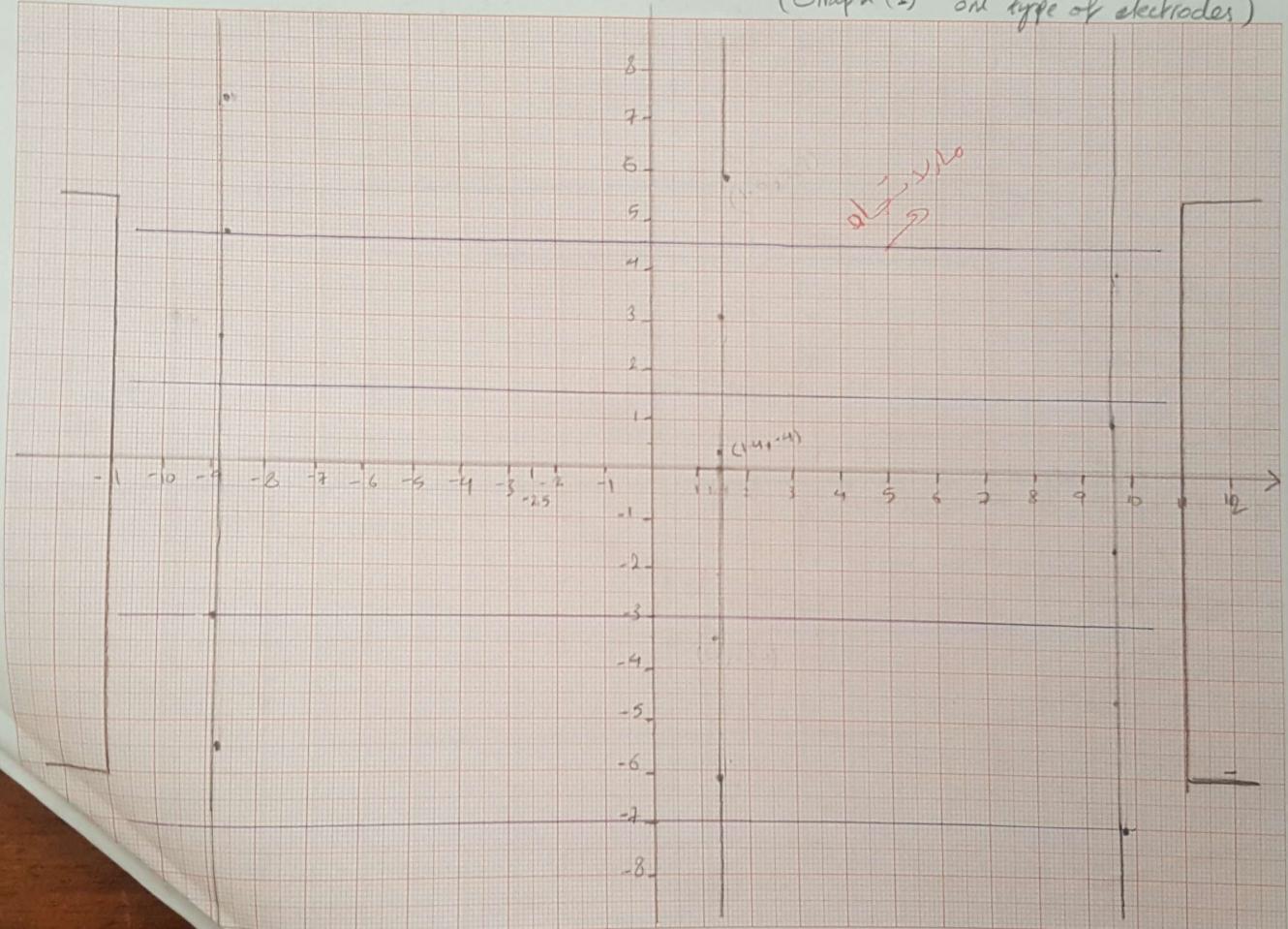

graph 2 (different diodes)

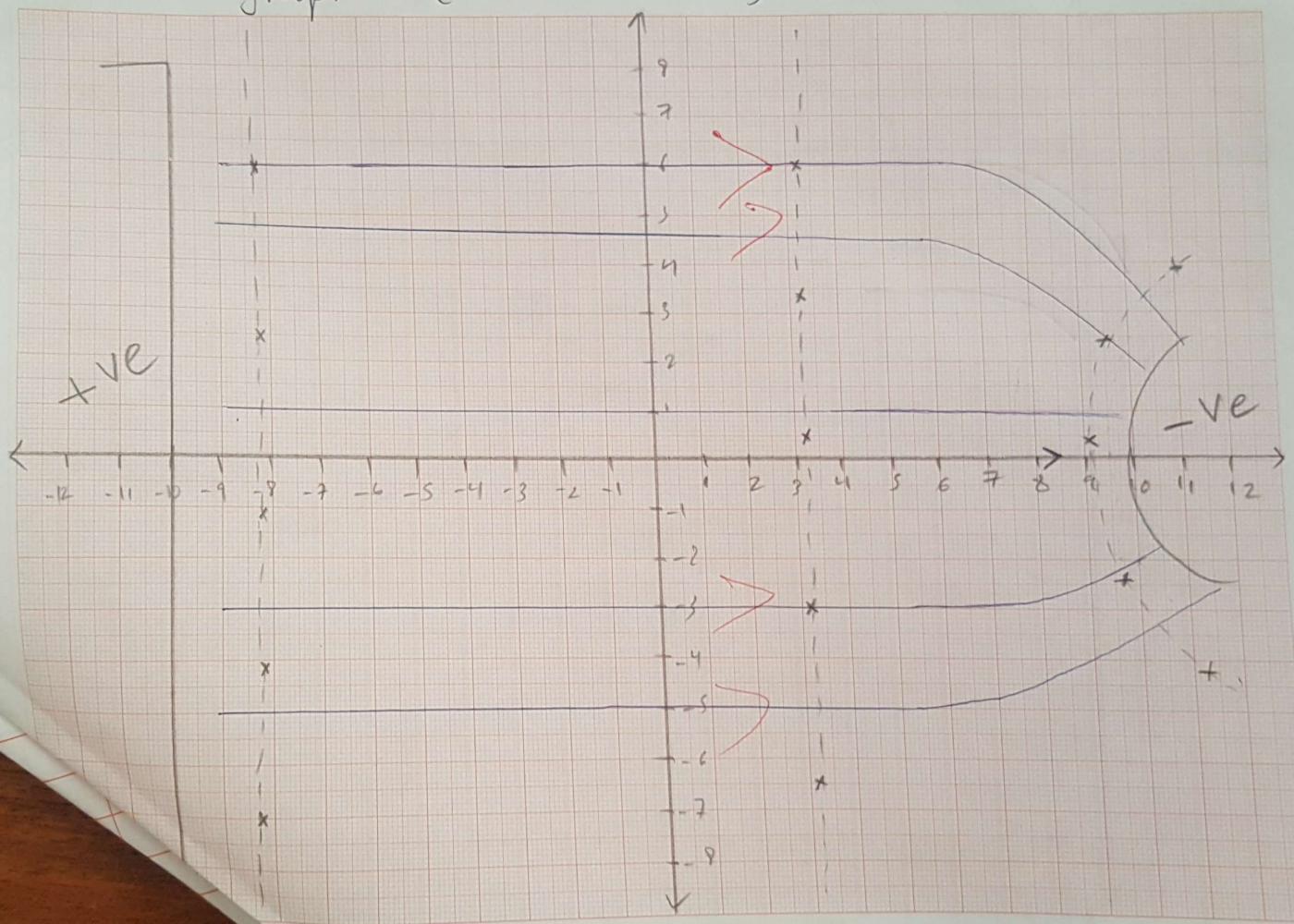

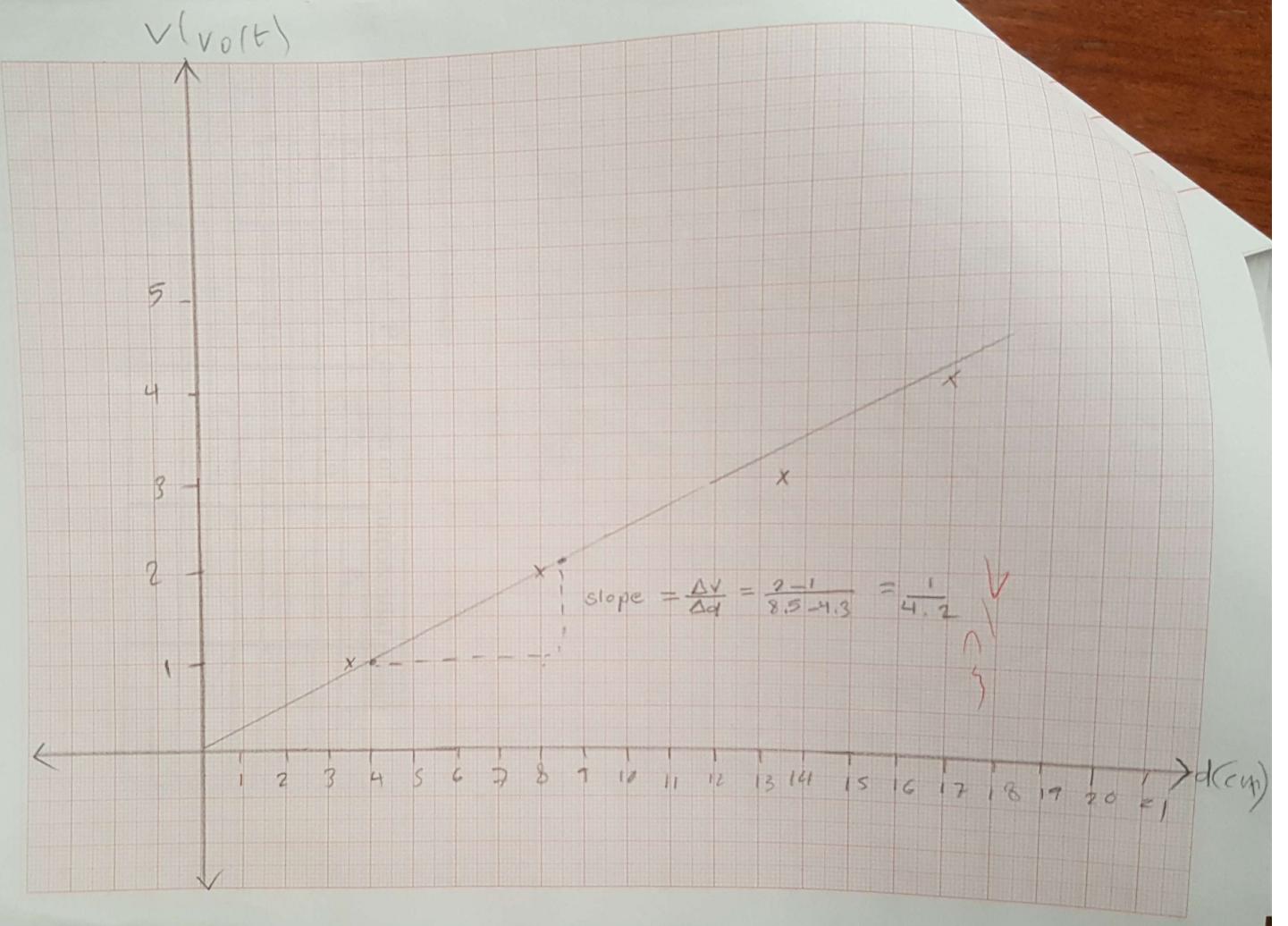

## LAB REPORT FOR EXPERIMENT 2

Name: \_\_\_\_\_

Date: \_\_\_\_\_

Registration No: \_\_\_\_\_

Partner's Name: \_\_\_\_\_

Physics Section: \_\_\_\_\_

Registration No: \_\_\_\_\_

Instructor's Name: Dr. Yehya

### PHYSICS LAB EXPERIMENT 2: SPECIFIC CHARGE OF COPPER IONS

#### I. PURPOSE

Determine the specific charge  $k$  (Coul/kg) of copper ions also we calculated the charge relations.

#### II. DATA AND DATA ANALYSIS

- Enter your data of the masses,  $m_1$  and  $m_2$  in kg as related to the current,  $I$ , in Ampere and time,  $t$ , in minutes in Table 2.1 below:

Table(2.1) *electron*

Current(I) (A)	Time (t) (min)	Amount of charge (It) (Coulomb)	$m_1$ (Kg)	$m_2$ (Kg)	Deposited mass $M_{Cu} = (m_2 - m_1)$ (Kg)
0.8A .8	20 10	$600 \times .8 = 480$	31.52 mkg	31.72 mkg	.2 mkg
0.3A .4	20 10	$600 \times .4 = 240$	31.72 mkg	31.88 mkg	.16 mkg
0.3A .4	10 5	$300 \times .4 = 120$	31.82 mkg	31.92 mkg	.1 mkg

- Use the data in Table (2.1) to plot the amount of charge (It) versus the mass of the deposited copper  $M_{Cu}$ .

3. What type of relationship do you see between  $M_{Cu}$  and  $I_t$ ?

linear and Direct relation ship

4. From your graph find the specific charge,  $K$ , of copper ions by calculating the slope.

$$\text{Slope} = \frac{Q}{m} = \frac{400 - 0}{175 - 0} = 2.3 \times 10^6 \text{ C/kg}$$

5. What are the units of  $K$ ?

Coul/kg

6. Estimate the error,  $\Delta K$ , in your value and write the result as  $K \pm \Delta K$ .

$$\frac{\Delta K}{K} = \sqrt{\left(\frac{\Delta I}{I}\right)^2 + \left(\frac{\Delta t}{t}\right)^2 + \left(\frac{\Delta M}{M}\right)^2} =$$

$$\frac{\Delta k}{2.3 \times 10^6} = \sqrt{\left(\frac{0.01}{0.8}\right)^2 + \left(\frac{0.005}{600}\right)^2 + \left(\frac{-0.0075}{0.2}\right)^2}$$

$$\Delta k = 9.92 \times 10^4 \text{ C/kg} \approx 2.3 \times 10^6 \pm 9.92 \times 10^4$$

7. Calculate the charge carried by each copper ion in the solution.

$$Q = K m_{Cu} = 2.3 \times 10^6 \times 63.6 \times 1.66 \times 10^{-27}$$

$$= 242.8 \times 10^{-21} \text{ Coul}$$

$$= 2.4 \times 10^{-19} \text{ C}$$


X  
C  
159

Column

8. Use the result above to calculate the charge of the electron  $e$ . How does it compare with the standard value?

$$\frac{Q}{c_u} = 2e \rightarrow 242.8 \times 10^{-21} \div 2 = 121.4 \times 10^{-21}$$
$$= 1.214 \times 10^{-19} \text{ coul}$$

$$P.E = \left| \frac{e_A - e_E}{e_A} \right| \times 100\% = \left| \frac{1.6 \times 10^{-19} - 1.214 \times 10^{-19}}{1.6 \times 10^{-19}} \right| \times 100\%$$
$$= 24.12\%$$

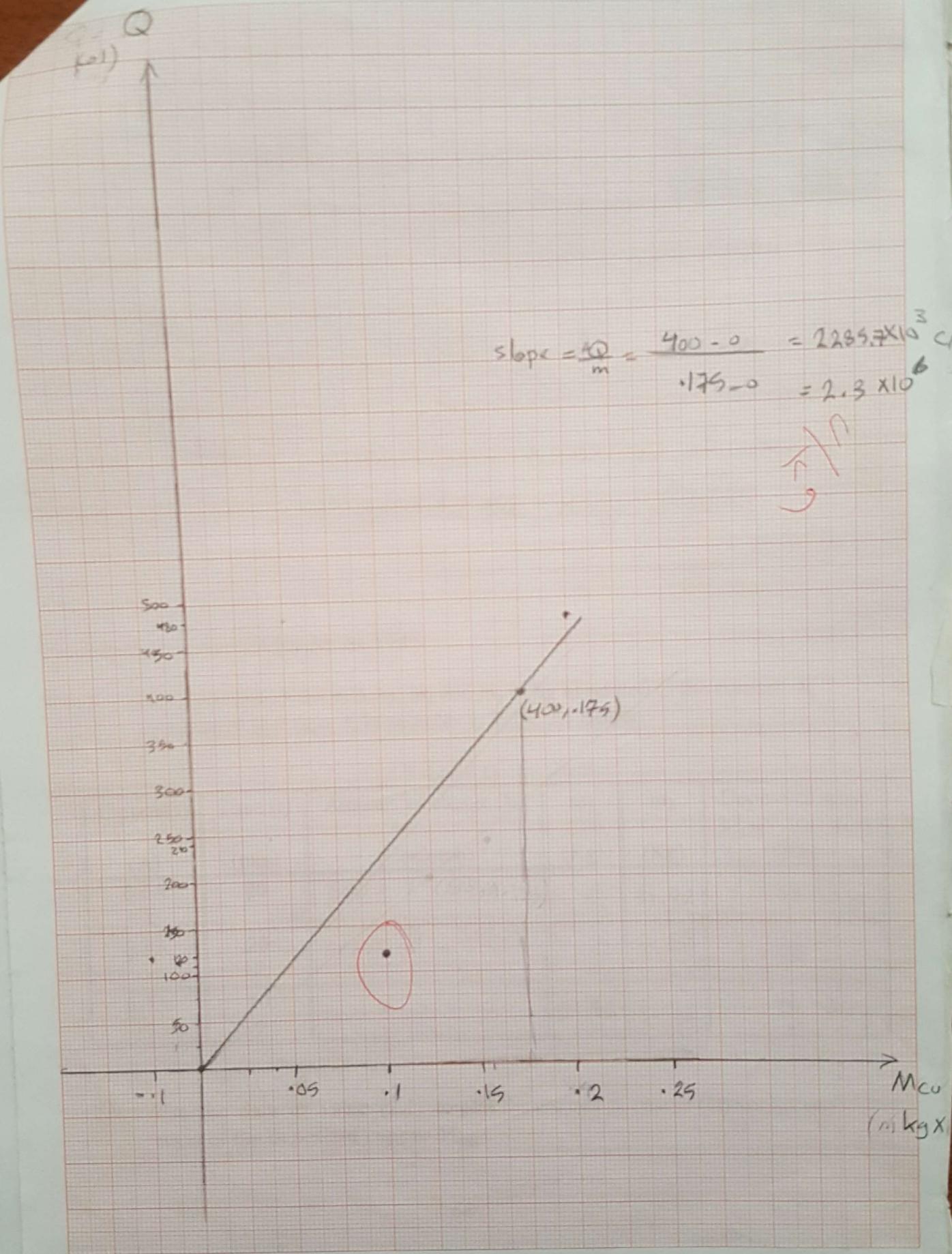

## LAB REPORT FOR EXPERIMENT 3

Date: \_\_\_\_\_ ?

Name: \_\_\_\_\_ ~~(X)~~

Partner's Name: \_\_\_\_\_

Registration No: \_\_\_\_\_ ~~(903)~~

Registration No: \_\_\_\_\_

Physics Section: \_\_\_\_\_

Instructor's Name: \_\_\_\_\_ Dr. Yousra Ramadan

### PHYSICS LAB EXPERIMENT 3: OHM'S LAW

#### 1. PURPOSE

to prove ohm's law which says if a conductor is kept at a constant temperature , the current flowing through it is directly proportional to Voltage .  $V = IR$

#### II. DATA AND DATA ANALYSIS

- Enter your data in Table 3.1

Table 3.1

R <sub>2</sub> Wire resistance Carbon		R <sub>2</sub> ! Carbon resistance Wire		R <sub>1</sub> and R <sub>2</sub> in Series		R <sub>1</sub> and R <sub>2</sub> in Parallel	
V(Volt)	I(Amp.)	V(Volt)	I(Amp.)	V(Volt)	I(Amp.)	V(Volt)	I(Amp.)
1.2	.3	1.4	.3	1.8	.2	1	.5
1.6	.4	2	.4	2.8	.3	1.2	.6
2.4	.6	3	.6	3.8	.4	1.4	.7
3.2	.8	4	.8	4.6	.5	1.6	.8
4	1	5	1	5.4	.6	1.8	.9

2- Plot graphs of voltage  $V$  as a dependent variable versus current  $I$ .

3- Determine the values of  $R$  for each **unknown resistance** as well as for the series and parallel combinations by calculating the **slopes** of your graphs.

$$R_1 = \frac{2-1}{0.5-0.25} = 4\Omega$$

$$R_2 = \frac{2-5-1.5}{0.51-0.31} = 5\Omega$$

$$R \text{ equivalent of } R_1 \text{ and } R_2 \text{ in series} = \frac{5.5-1}{0.6-0.1} = 9\Omega$$

$$R \text{ equivalent of } R_1 \text{ and } R_2 \text{ in parallel} = \frac{1.5-0.6}{1-0.3} = 1.3\Omega$$

4- From the graph of  $V$  versus  $I$  for  $R_1$ , estimate the error  $\Delta R_1$ .

$$\frac{\Delta R}{R_1} = \sqrt{\left(\frac{\Delta I}{I}\right)^2 + \left(\frac{\Delta V}{V}\right)^2} = \frac{\Delta R_1}{R_1} = \sqrt{\left(\frac{0.01}{0.1}\right)^2 + \left(\frac{0.1}{1.5}\right)^2} = 0.112$$

$$R = 5 \pm 0.112 \Omega$$

5- Using the value of  $R_1$  obtained in (3) and the **length** and **diameter** of the wire used for  $R_1$ , calculate the resistivity of the wire  $\rho$ .

$$\frac{R = \rho l}{A}, \quad \rho = \frac{A R_1}{l} = \frac{\left(\frac{4\pi}{2}\right)^2 \times \pi \times 5}{1.5} = 5.29 \times 10^{-6} \Omega \cdot \text{m}$$

$$l = 1.5, \quad D = 0.49, \quad \text{radius} = 0.25$$

6- Compare the calculated values with the experimental values you obtained for:

#### Combination of resistances in series:

- experimental value:  $9\Omega$

- calculated value:  $R_1 + R_2 = 4 + 5 = 9\Omega$

#### Combination of resistances in parallel:

- experimental value:  $1.3\Omega$

- calculated value:  $\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{4} + \frac{1}{5} = 0.2$

$V (V=16)$

$$\text{Slope (1)} [R_1 \& R_2] = \frac{5.5 - 1}{0.5 - 0.1} = 9 \quad \cancel{U/A = \Omega} \quad (\text{series})$$


$$\text{Slope (2)} [R_1] = \frac{2.5 - 1.5}{0.51 - 0.31} = 5 \quad \cancel{R_2}$$

$$\text{Slope (3)} [R_1] = \frac{2 - 1}{0.5 - 0.25} = 4 \quad \boxed{1}$$

$R_2 \quad \boxed{2}$

$$\text{Slope (4)} [R_1 // R_2] = \frac{1.5 - 0}{0.5 - 0.3} = 5 \quad \boxed{A} \quad ?$$

$$5.5 \Omega = 10.3 \Omega$$

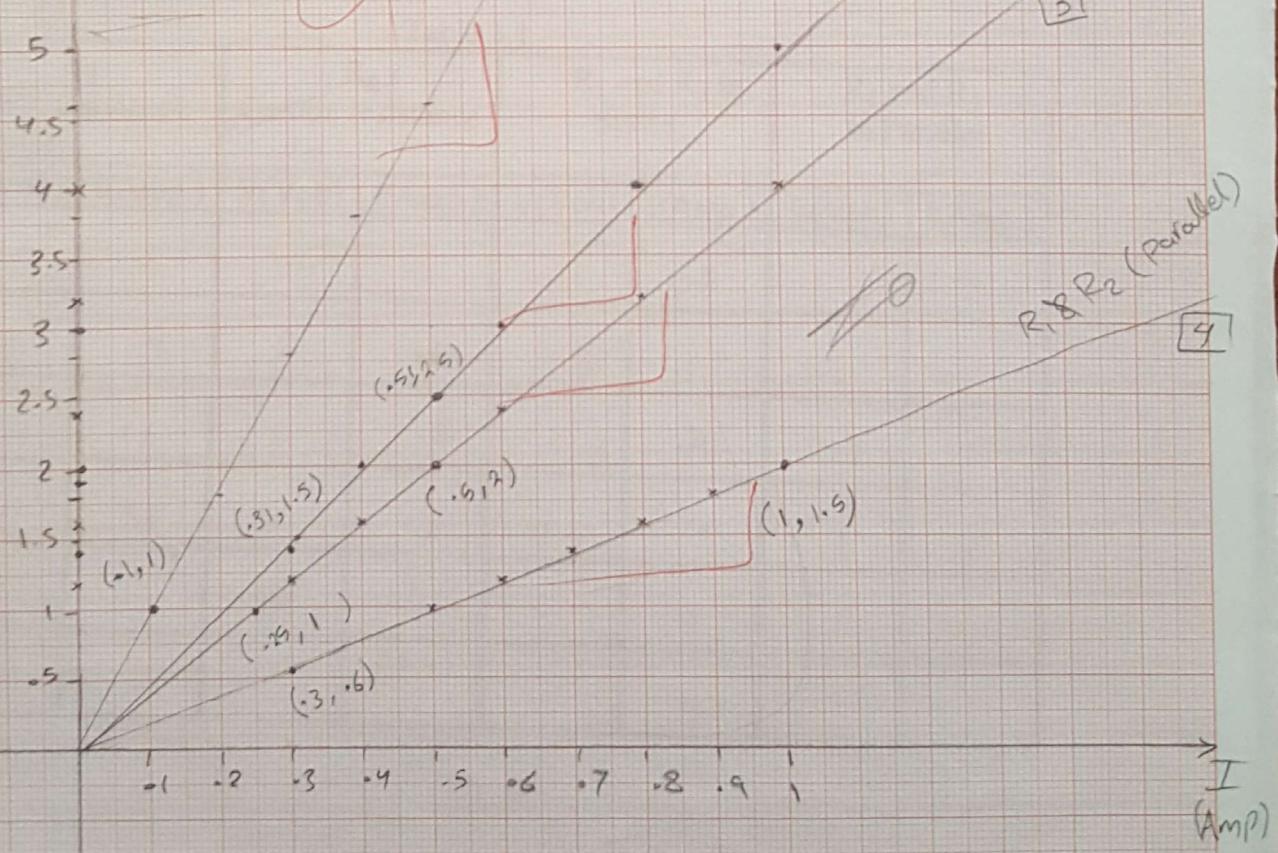

## LAB REPORT FOR EXPERIMENT 4

Date: 9-Nov-2015

Name: [Redacted]

Partner's Name: [Redacted] VO

Registration No: [Redacted]

Registration No: [Redacted]

Physics Section: 4

Instructor's Name: Dr. Yehya Ramadan

### PHYSICS LAB EXPERIMENT 4: POWER TRANSFER

#### I. PURPOSE

To investigate the condition in which maximum

power is transferred to the load resistor  $R_L$

#### II. DATA AND DATA ANALYSIS:

1. Use the equation  $P = VI$  to calculate  $P_L$  the power dissipated by the load resistor  $R_L$  and enter the calculated values in Table (4.1) below:

Table 4.1

$R_s = 100 \Omega$				
Reading	$R_L (\Omega)$	$I_L (\text{mA})$	$V_L (\text{V})$	$P_L (\text{mW})$
1	20	30	1	30
2	40	26	1.6	41.6
3	60	22	2.2	48.4
4	80	20	2.5	50
5	100	18	2.9	52.2
6	200	12	4	48
7	400	10	4.6	46
8	600	6	5	30
9	800	4	5.1	20.4

2. Plot on a graph paper the power  $P_L$  as dependent variable versus the load resistor  $R_L$ . Find the value of the load resistor for which the power dissipated is **maximum**. How is this value related to the series resistance  $R_s$ .

Maximum power at  $R_L = 100 \Omega$  where  $R_s = R_L = 100 \Omega$

3. For what value of the load resistance  $R_L$  was:

1) The load current a maximum?  $R_L = 20 \Omega$   $R_L \propto \frac{1}{I}$

2) The load voltage a maximum?  $R_L = 80 \Omega$   $R_L \propto V_L$

4. Using the expression for  **$P_L$  power dissipated in the load resistance** as a function of the load resistance  $R_L$ , determine the condition for the **maximum** power (differentiate  $P_L$  with respect to  $R_L$  and set  $\frac{dp_L}{dR_L} = 0$ )

$E_s = I_L (R_s + R_L)$   $\therefore P = I_L V_L$

$$P_L = \frac{E_s^2 R_L}{(R_s + R_L)^2} \quad \text{now } \frac{dP_L}{dR_L} = 0 \rightarrow (R_s + R_L)^2 \cancel{\times E_s^2} - E_s^2 \cancel{2(R_s + R_L)} = 0 \\ (R_s + R_L)^2 - R_s^2 = 0 \quad (R_s + R_L)^2 = R_s^2 \quad R_L = R_s$$

$(R_s + R_L)^2 - R_s^2 = 0$

$R_s^2 + 2R_s R_L + R_L^2 = 2R_s R_s + 2R_s^2$

- 5- Compare the value of  $R_L$  at maximum power found in (2) with that found in (4) above.

$R_L = 100 \Omega = R_s$ , they're equal

- 6- If the internal resistance,  $R_s$ , is larger than the load resistance  $R_L$ , which resistance will dissipate more power?

$R_s$  dissipates more


$\frac{P_{max}}{R_s}$

$P = I^2 R$

$\therefore$  Power according to the graph.

the smaller
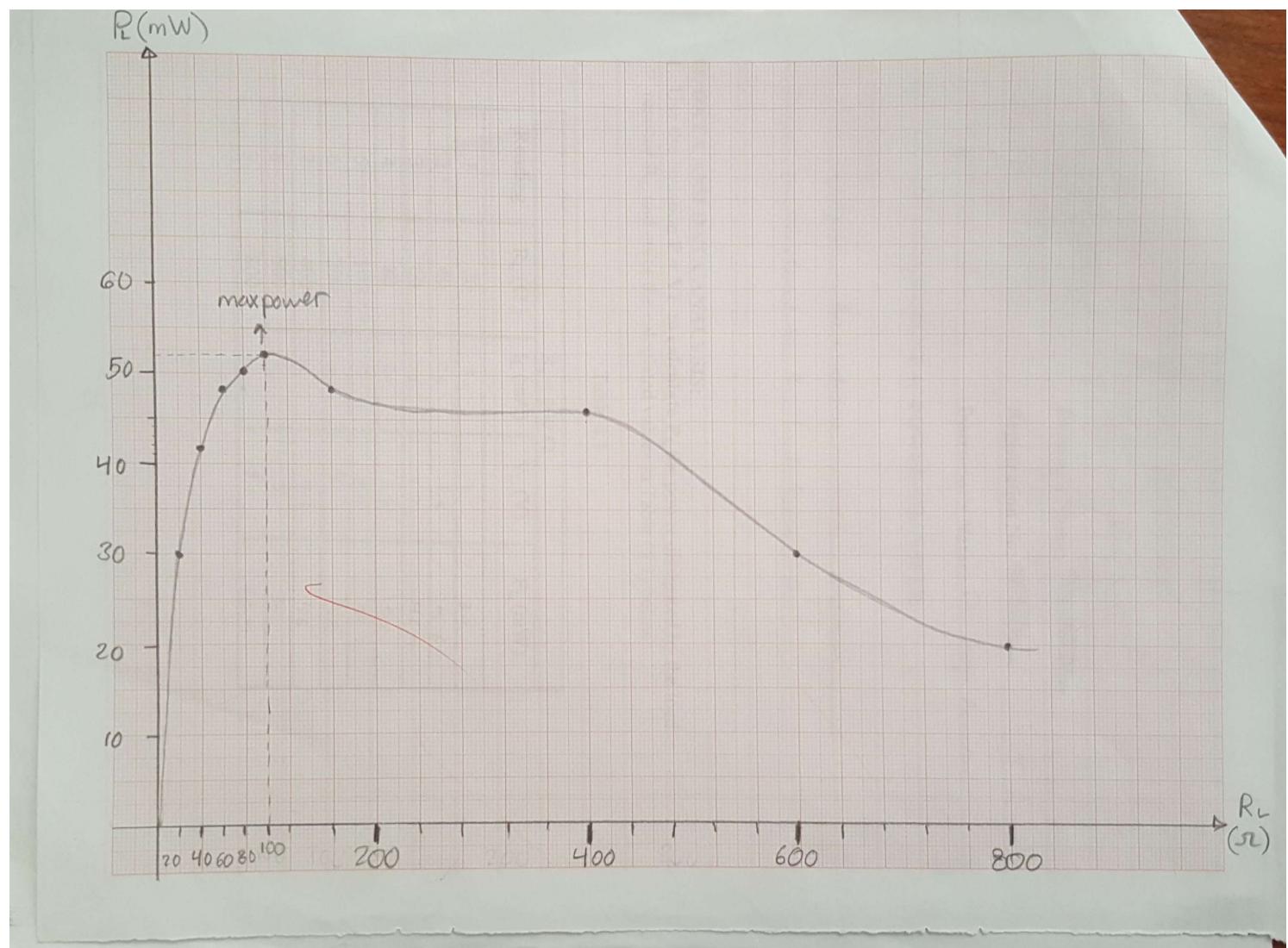
$$\begin{aligned} I_L &= I_s \\ R_s &> R_L \\ \therefore P_s &> P_L \end{aligned}$$



## LAB REPORT FOR EXPERIMENT 5

Date: 2-Nov

Name: [REDACTED]

Partner's Name: [REDACTED]

Registration No: [REDACTED]

Registration No: [REDACTED]

Physics Section: 4

Instructor's Name: Dr. Yekya Ramadeen

### PHYSICS LAB EXPERIMENT 5: THE WHEATSTONE BRIDGE

#### 1. PURPOSE

To find an unknown resistance using the Wheatstone bridge which is more accurate than Ohm's law.


#### II. DATA AND DATA ANALYSIS :

1. Show that  $\frac{R_s}{R_x} = \frac{L_1}{L_2}$

$V_{ab} = V_{ad}$ ,  $R_1 R_3 = R_2 R_x$ ,  $R_x = R_3 \left( \frac{R_1}{R_2} \right)$

but  $R = \frac{\rho l}{A}$ ,  $\rho$  and  $A$  constant.

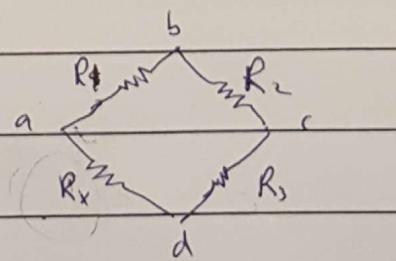$R_x = R_3 \left( \frac{L_1}{L_2} \right)$



# Resistance A

2. Record your data in Table (5.1) below:

Table 5.1

Reading	$R_1$ ( $\Omega$ )	$L_1$ (cm)	$L_2$ (cm)	$R_x$ ( $\Omega$ )	$\Delta R_x / R_x$
1	10	13	87	66.9	$3.89 \times 10^{-3}$
2	20	25	75	60	$2.1 \times 10^{-3}$
3	30	31.5	65.5	56.9	$1.63 \times 10^{-3}$
4	40	41.5	58.5	56.4	$1.47 \times 10^{-3}$
5	50	47.5	52.5	55.3	$1.41 \times 10^{-3}$
6	60	52	48	55.4	$1.417 \times 10^{-3}$
7	70	56.5	43.5	53.8	$1.45 \times 10^{-3}$
8	80	60	40	53.3	$1.5 \times 10^{-3}$
9	90	63	37	52.8	$1.56 \times 10^{-3}$
10					
$\bar{R}_x = 56.76 \Omega$					

3. Using the equation derived in (1), calculate the value of the unknown resistance  $R_x$ . Repeat for the different values of  $R_1$  and enter your calculation in table 5.1 above.

Example for one calculation:

$$R_x = R_1 \left( \frac{L_2}{L_1} \right) = 30 \times \left( \frac{65.5}{34.5} \right) = 56.9 \Omega$$

4. Calculate the relative error  $\Delta R_x / R_x$  for the different values of  $R_1$  using the equation:

$$\frac{\Delta R_x}{R_x} = \left[ \left( \frac{\Delta L_1}{L_1} \right)^2 + \left( \frac{\Delta L_2}{L_2} \right)^2 \right]^{\frac{1}{2}}$$

Example for one calculation:

$$\frac{\Delta R_x}{R_x} = \sqrt{\left( \frac{0.05}{34.5} \right)^2 + \left( \frac{0.05}{65.5} \right)^2} = 1.63 \times 10^{-3}$$

Is it essential that the battery supplies a constant current to the wire?  
Explain your answer.

No, because the galvanometer will read  
 $I=0$  at all time.

Because the balance point D<sub>1</sub>S<sub>0</sub>; I<sub>1</sub>S<sub>0</sub>

6. From the table, determine the values of  $L_1$  and  $L_2$  for which the error  $\Delta R_x / R_x$  is a minimum.

$$L_1 = \underline{47.5 \text{ cm}}$$

$$L_2 = \underline{52.5 \text{ cm}}$$



## LAB REPORT FOR EXPERIMENT 6

Name: \_\_\_\_\_ Date: \_\_\_\_\_  
Registration No: \_\_\_\_\_ Partner's Name: \_\_\_\_\_  
Physics Section: \_\_\_\_\_ Registration No: \_\_\_\_\_  
Instructor's Name: \_\_\_\_\_ Dr Yehya .

### PHYSICS LAB EXPERIMENT 6: THE POTENTIOMETER

#### I. PURPOSE:

To Calibrate the potentiometer using a voltmeter instead of the standard cell  $E_B$ ; then use it to measure an unknown emf  $E_x$ .

#### II. DATA AND DATA ANALYSIS :

##### A. Calibration of the Potentiometer

- 1- Record your measurements of the reading  $V_x$  of the voltmeter at any point on the wire and the corresponding distance  $L_x$  in Table (6.1)below:

Table (6.1)

Reading	$V_x$ (V)	$L_x$ (cm)
1	.5	17
2	.9	30
3	1.5	51
4	2.0	70
5	2.5	90
6		

Plot a graph of  $V_x$  versus  $L_x$ . State your conclusion.

$V_x$  and  $L_x$  have direct and linear relationship.

- 3- If the wire is uniform derive a simple relation between the voltmeter reading  $V_x$  at any point on the wire and the corresponding distance  $L_x$ .

$$I = \frac{V}{R} = \frac{E}{\rho \frac{l}{A}}$$

$$V_x = IR_x$$

$$V_x = E_s \frac{\rho l}{A}$$

$$= E_s \frac{l}{l_{tot}}$$

$$R_x = \rho \frac{l}{A}$$

#### B. Measurement of an Unknown EMF

- 1- Calculate and record  $\bar{L}_x$ , the average value of  $L_x$ .

Trial	$L_x$ (cm)
1	51
2	51
3	51
$\bar{L}_x$	51 cm

- 2- Use your graph of part A to find the value of  $E_x$  corresponding to  $\bar{L}_x$ .

$$E_x = m \cdot \bar{L}_x = 0.028 \times 51 = 1.47 V$$

or from the graph  $E_x = V_x = 1.5 V$

What is the current flowing through  $E_x$  when pointer touches the potentiometer wire at the balance point?

Current = 0, G = 0

- 4- What happens to the balance point when a small resistor is connected in series between  $E_x$  and the galvanometer? Explain the result you observe.


When  $G = 0, I = 0$

$V_x = E_x$

$V_x = E_x$  if we added a resistor  $V_x = E_x + IR$ .

then  $V_x = E_x$

(the current flowing is zero).

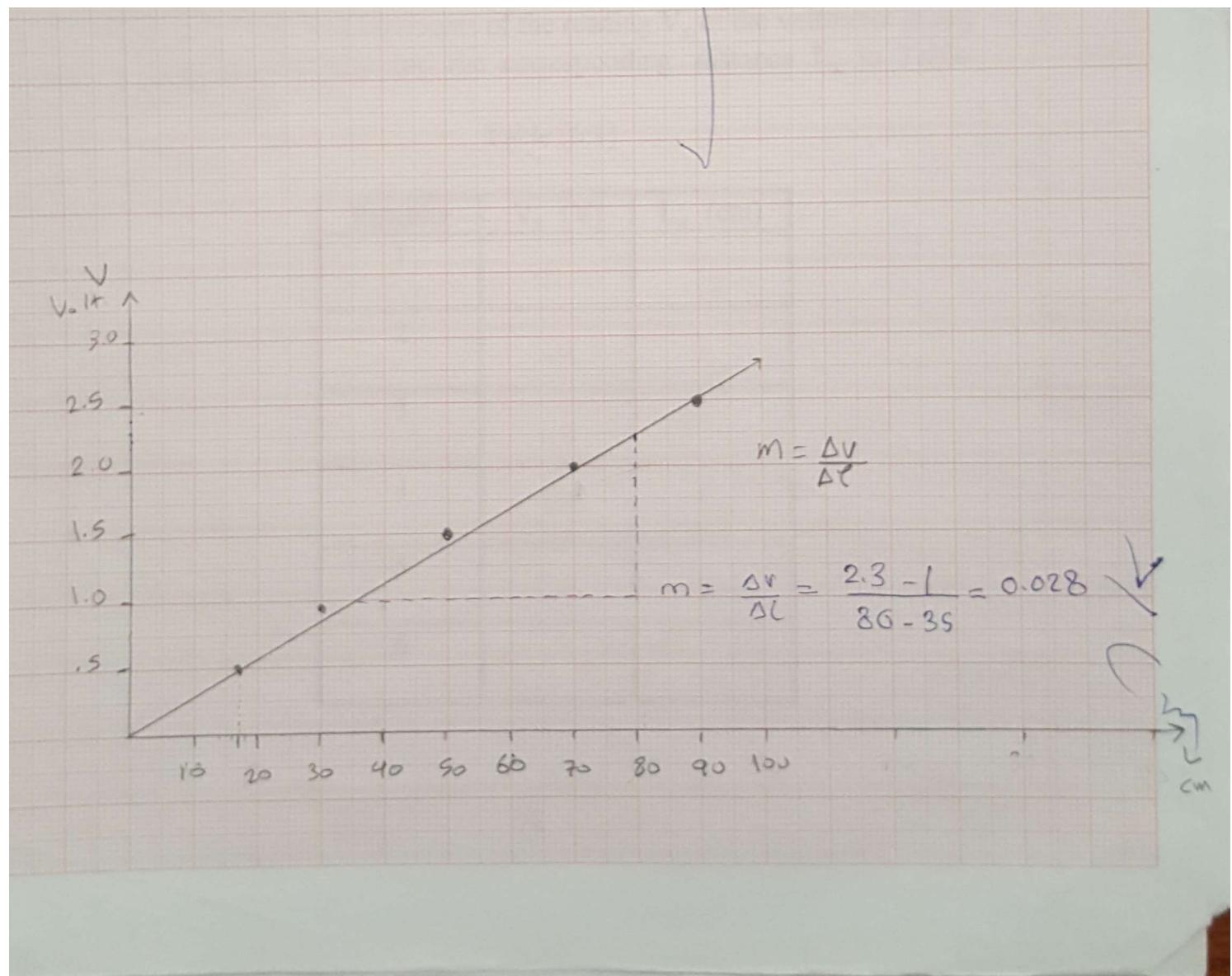

## LAB REPORT FOR EXPERIMENT 7

Date: 23 - Nov - 2015

Name: [REDACTED]

Partner's Name: [REDACTED]

Registration No: [REDACTED]

Registration No: [REDACTED]

Physics Section: 4

Instructor's Name: Dr. Yekya Ramakrishnan

### PHYSICS LAB EXPERIMENT 7 : THE RC TIME CONSTANT

#### 1. PURPOSE

To determine the time constant for an RC circuit ~~and~~ by measuring the changing current as a function of time.

#### IV. DATA AND DATA ANALYSIS:

- Enter your data of the **charging current**, the corresponding **time** and the measured voltage source  $V_t$  in Table 7.1 below:

6.160002

Table 7.1

- 2- Plot the **charging current** as dependent variable versus **time** as independent variable **for case 1**. Is the plot linear? What can you say about the shape of your graph?

It's not linear, it's exponential relationship.

and it's decaying (decreasing).

- 3- From the data of charging current versus time, determine the value of the initial charging current  $I_0$ . This is the value of the current at  $t = 0$ . Record the value in table 7.1 .

- 4- Plot  $\ln(I/I_0)$  as the dependent variable versus time. Here,  $I$  is the charging current and  $I_0$ , the initial current determined in step (3) above. Is the plot linear?

Yes it's linear and it's decaying. decreasing

- 5- Draw the straight line that best fits the data and determine the slope of the line. Record the value of the slope in table 7.1 .

- 6- Repeat steps 3,4 and 5 above for the second case.

- 7- Determine the time constant for each case from the equation:

$$\tau = \frac{-1}{\text{slope}}$$

and record it in table 7.1.

$$\tau_1 (\text{experimentally}) = \frac{\text{slope}}{-0.063 \text{ sec}^{-1}} \text{ then } T_1 = \frac{-1}{\text{slope}} = \frac{1}{-0.063} = +15.87 \text{ sec}$$

$$\tau_2 (\text{experimentally}) = \frac{-1}{-0.036} = +27.78 \text{ sec}$$


- 8- From the known values of C and R for each case, calculate  
 $\tau_1 = RC_1$  and  $\tau_2 = RC_2$  and compare these values with those obtained in step (6).

$$\tau_1 (\text{Calculated}) = \underline{RC_1 = 61.6 \times 10^3 \times 190 \times 10^{-6} = 11.704 \text{ sec}}$$

$$\tau_2 (\text{Calculated}) = \underline{RC_2 = 61.6 \times 10^3 \times 437 \times 10^{-6} = 26.919 \text{ sec}}$$

- 9- From the known values of  $V_o$  and R, , calculate  $I_o = \frac{V_o}{R}$  which is the same for both cases. Compare this value with the one obtained in step (3) above.
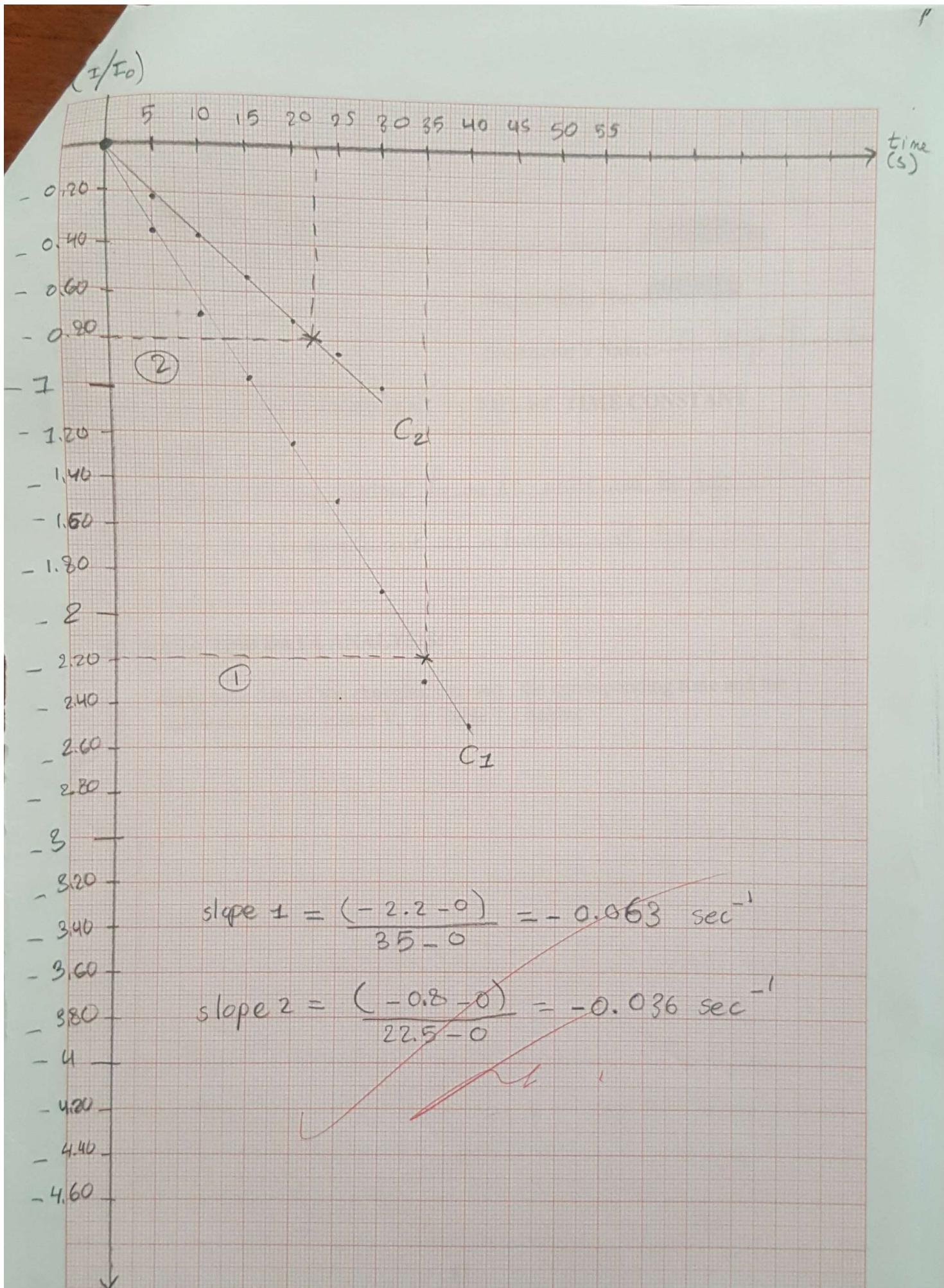
$$I_o(\text{calculated}) = \underline{\frac{6.46}{61.6 \times 10^3} = 1.07 \times 10^{-4} = 107 \mu A}$$



## LAB REPORT FOR EXPERIMENT 8

Name: \_\_\_\_\_

Date: 16-11-2015

Registration No: \_\_\_\_\_

Partner's Name: \_\_\_\_\_

Physics Section: 4

Registration No: \_\_\_\_\_

Instructor's Name: Dr. Yehya Ramadseen

### PHYSICS LAB EXPERIMENT 8: THE MAGNETIC FIELD OF A CURRENT

#### I. PURPOSE

To investigate the dependence of the direction & magnitude of the magnetic field ( $H_E$ ) on the current that produces it, & to find the reduction factor  $(k)$  of the galvanometer

#### II. DATA AND DATA ANALYSIS:

1. Enter your data in Table 8.1 below:

Table 8.1

$\theta$	I(mA)	$\theta_1$	$\theta_2$	$\theta_3$	$\theta_4$	$\bar{\theta}$	$\tan \bar{\theta}$
1	20	21	20	19	22	20.5	.37
2	30	25	24	25	25	24.75°	.46
3	35°	35	35	36	34°	35°	.7
4	50	44°	43°	42°	40°	42.5	.91
5	60	49°	50°	50°	51°	50	1.19
6	70	53°	54°	54°	55°	53.5	1.35
7	80	55°	55°	55°	56°	55.25	1.44
8	90	56°	55°	60°	60°	57.75	1.58
radius of the coil = 7.25 cm				N=50 turns			

- 2- Using Table 8.1 plot a graph between the values of  $I$  as a dependent variable against the corresponding values of  $\tan \bar{\theta}$  as the independent variable.
- 3- Use your graph to find the value of the reduction factor  $K$  and the error  $\Delta K$ .


$$K = \frac{\Delta I}{\Delta \tan \bar{\theta}} = \frac{(70 - 0) \times 10^3}{1.25 - 0} = 56 \times 10^3 \text{ A}$$

$$K \pm \Delta K =$$

ng the above value of  $K \pm \Delta K$ , find the value of  $H_E \pm \Delta H_E$ .  $K = \frac{10 \text{ aH}}{2\pi N}$

$$56 \times 10^3 = 10 \times 7.25 \times 10^2 H_E, H_E = 24.26 \text{ Gauss}$$
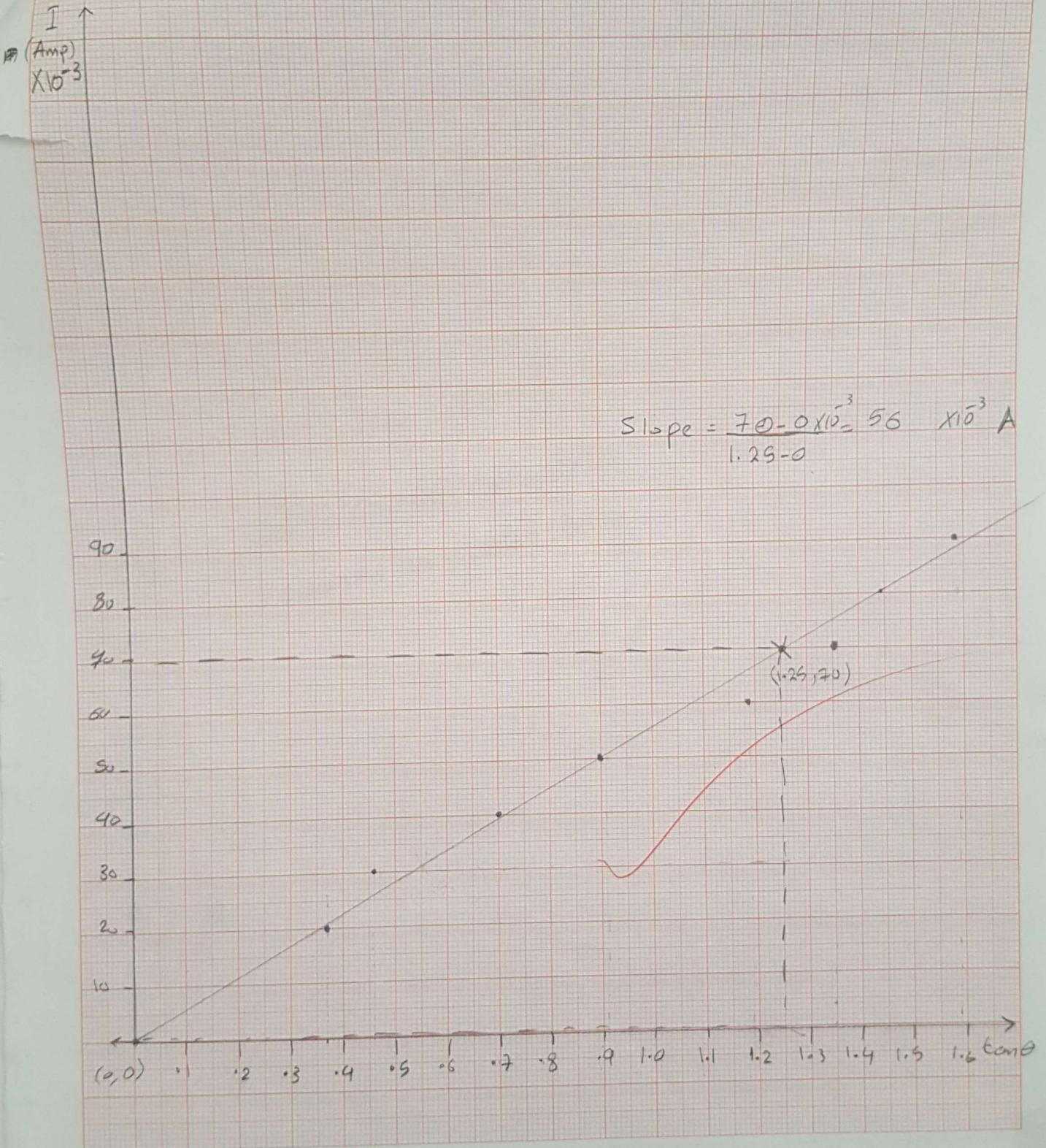
$$H_E \pm \Delta H_E = 24.26 \text{ Gauss}$$



## LAB REPORT FOR EXPERIMENT 9

### KIRCHHOFF'S LAWS

Date: 14/12/2015

Name: \_\_\_\_\_

Partner's Name: \_\_\_\_\_

Registration No: \_\_\_\_\_

Registration No: \_\_\_\_\_

Physics Section: 4

Instructor's Name: Dr. Yehya Ramadeen

### PHYSICS LAB EXPERIMENT 9 : KIRCHHOFF'S LAWS

#### 1. PURPOSE :

Apply Kirchhoff's first and second laws to analyze the electric networks and compare the results with the experimental values.

#### II. DATA AND DATA ANALYSIS:

##### A. DATA:

1. Record the measured values of  $V_1$ ,  $V_2$ ,  $V_{R_1}$ ,  $V_{R_2}$  and  $V_{R_3}$  and their polarities on diagram 1 shown below.
2. Record the measured values of  $I_1$ ,  $I_2$ , and  $I_3$  and their direction of flow on diagram 1.


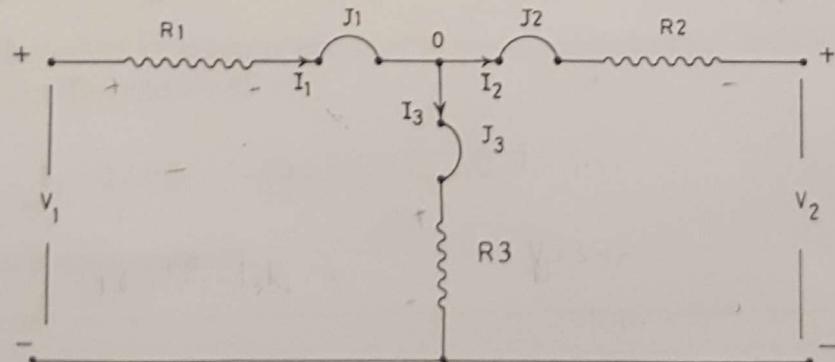


diagram 1

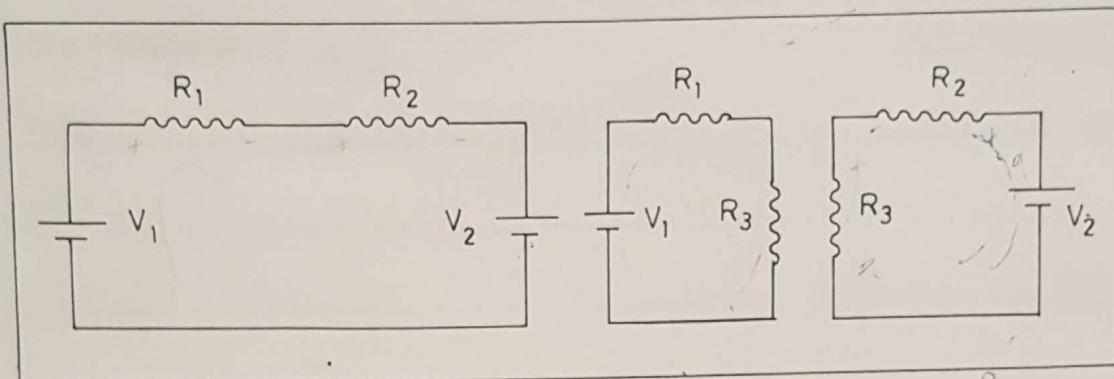- B.** Using the values obtained in part A, calculate the sum of voltage drops around the three loops shown below:



$$VR_1 = 2.2 \text{ V}, VR_2 = 0.7 \text{ V}, VR_3 = 2.6 \text{ V}$$

$$IR_1 = 6.2, IR_2 = 1.2 \text{ A}, IR_3 = 5 \text{ A}$$

$$R_1 = 360 \Omega$$

$$R_2 = 470 \Omega$$

$$R_3 = 680 \Omega$$

$$V_1 + V_{R_1} + V_{R_3} = 6 + 2.2 - 3.6 = 4.6 \text{ volt}$$

$$V_2 + V_{R_2} + V_{R_3} = 3 + 0.7 - 3.6 = 0.1 \text{ volt}$$

$$V_1 + V_{R_1} + V_{R_2} - V_2 = 6 - 2.2 - 0.7 - 3 = 2.1 \text{ volt}$$

Are the sums shown above equal to zero?

Yes

- C.** Using the values of currents obtained in part A, calculate the total sum of currents at the junction O

$$I_1 + I_2 + I_3 = 6 + 2 - 1.5 - 1.2 = 5$$

Is the sum equal to zero?

Yes

D. Using the values of  $V_1$  and  $V_2$  and the values of  $R_1$ ,  $R_2$ , and  $R_3$ , set up the **loop** and **branch** equations, and solve them to determine the values of  $I_1$ ,  $I_2$  and  $I_3$  and compare with the values obtained **experimentally** in part A.

**Loop equations:**

$$\text{loop } +V_1 + -I_1 R_1 - I_2 R_2 - V_2 = 0 \quad (1) \quad 6 - 36I_1 - 470I_2 - 3 = 0$$

$$\text{loop } V_1 - I_1 R_1 - I_3 R_3 = 0 \quad (2) \quad 6 - 36I_1 - 680I_3 = 0$$

$$\text{loop } -V_2 + I_2 R_2 - I_3 R_3 = 0 \quad (3) \quad 3 + 470I_2 - 680I_3 = 0$$

$$I_1 = I_2 + I_3 \quad I_3 = 5.3 \text{ mA}, \quad I_1 = 6.6 \text{ mA}, \quad I_2 = 1.3 \text{ mA}$$

**Branch equations:**

$$I_1 = I_2 + I_3 \quad 6.6 = 1.3 + 5.3$$

**Calculated values:**

$$I_1 = 6.6 \text{ mA} \quad \text{Ampere}$$

$$I_2 = 1.3 \text{ mA} \quad \text{Ampere}$$

$$I_3 = 5.3 \text{ mA} \quad \text{Ampere}$$

**Experimental values:**

$$I_1 = 6.2 \text{ mA} \quad \text{Ampere}$$

$$I_2 = 1.2 \text{ mA} \quad \text{Ampere}$$

$$I_3 = 5.1 \text{ mA} \quad \text{Ampere}$$

## LAB REPORT FOR EXPERIMENT 10

Date: 14 December

Name: [Redacted] VP

Partner's Name: [Redacted]

Registration No: [Redacted]

Registration No: [Redacted]

Physics Section: 4

Instructor's Name: Dr. Yahya Ramadhan

### PHYSICS LAB EXPERIMENT 10: ELECTROMAGNETIC INDUCTION

#### I. PURPOSE:

To investigate the conditions required to produce an induced current.

#### II. DATA AND DATA ANALYSIS:

Enter, in Table 10.1 below your observations and deductions on the investigated cases of induced current production.

Table 10.1

Action	Direction of Current		Size of deflection and comments
	Primary	Secondary	
(a)	C.W	C.C.W	small 4
(b)	C.W	C.W	4
(c)	C.W	C.C.W	2
(d)	C.W	C.W	2
(e)	C.W	C.W	4
(f)	C.W	C.C.W	4
(g)	C.W	C.C.W	4 → greater than 50
(h)	C.W	No change	No change
(i)		C.W	29
(j)		C.C.W	26
(k)		C.C.W	24
(L)		C.W	24

- 1- From the directions of the secondary current in case **a** and **b** determine whether Lenz's law is obeyed. Explain.

Case a:

Yes the Lenz's law is obeyed because when we turn on the switch with primary solenoid the secondary solenoid has an increasing in the magnetic flux so it will opposes this increase

Case b:

when the switch turns off the secondary

solenoid will oppose this decreasing.

- 2- Explain the reason for the difference in deflection of the galvanometer in case g when a soft iron rod is inserted in the winding.

When we put an iron rod in the first solenoid  
the deflection will increase because the iron has  
magnetic properties (materials) that will increase  
that the change in magnetic flux.

- 3- Explain what happens to the size of deflection of the galvanometer when a brass rod is inserted in the windings.

It will not change the size of deflection because  
brass doesn't have magnetic properties.  
(paramagnetic)

## LAB REPORT FOR EXPERIMENT 11

Date: 14/01/2015

Name: Rashed

Partner's Name: Ali

Registration No: 1111111111

Registration No: 1111111111

Physics Section: 4

Instructor's Name: Dr. Yousra Ramadeen

### PHYSICS LAB EXPERIMENT 11: THIN LENSES

#### 1. PURPOSE :

To study the relation between the object distance, image distance and focal length of converging and diverging lenses.

#### II. DATA AND DATA ANALYSIS:

##### A. CONVERGING LENS (CONVEX):

- Enter your data in Table 11.1 below:

Table 11.1

Trial No.	O (cm)	i (cm)	f (cm)	M	Characteristics of the image	
					Real or virtual	Erect or inverted
f <sub>1</sub>	30	14	9.51	- .46	real	inverted
f <sub>2</sub>	35	13	9.47	- .37	real	inverted
f <sub>3</sub>	23	17	9.77	- .73	real	inverted
f <sub>4</sub>						
f <sub>5</sub>						
$\bar{f} = 9.58 \text{ cm}$				$\Delta \bar{f} = \pm .09 \text{ cm}$		

- From the values of O and i calculate f the focal length of the lens in each case and then calculate  $\bar{f}$  and enter the results in Table 11.1.

example of one case:  $O = 30, I = 14, \frac{1}{f} = \frac{1}{30} + \frac{1}{14} - \frac{11}{105}$

$$f = 9.5 \text{ cm}$$

- 3- Calculate the error  $\Delta \bar{f}$  using the standered deviation method.

$$\Delta f = \pm \sqrt{\frac{\sum (f - \bar{f})^2}{n(n-1)}} = \pm \sqrt{\frac{(9.5) - 9.58)^2 + (9.47 - 9.58)^2 + (9.77 - 9.58)^2}{(3 \times 2)}}$$

$$\Delta f = .09 \text{ cm}$$

- 4- Calculate the magnification  $M$ , using the height of the object and the height of the image, or using equation 11.2 and enter the results in Table 11.1 ..

example of one case:  $M = -\frac{1}{0} = -\frac{1}{30} = -46.6$

- 5- Compare the experimental value of  $\bar{f}$  with the **actual value** of focal length printed on the lens.

Experimental value:  $\bar{f} = 9.58 \text{ cm}$ .

Actual value:  $f = 10 \text{ cm}$ .

## B. DIVERGING LENS (CONCAVE):

### 1. Enter the data in Table 11.2

Table 11.2

Trial No.	$O'$ (cm)	$i'$ (cm)	$f$ (cm)	$M$	Characteristics of the image
$f_1$	-18	26	-98.5	1.44	real erect
$f_2$	-22	42	-46.2	1.91	real erect
$f_3$	-14	21	-42	1.5	real erect.
$f_4$		.			real
$f_5$					
$\bar{f} = -48.9$	(cm)			$\Delta \bar{f} = \pm 4.95$	(cm)

- 2- From the recorded values of  $O'$  and  $i'$ , calculate the focal length  $f$  of the diverging lens in each case. Note that  $O'$  is negative as it represents the distance of a virtual object and enter the results in Table 11.2.

example of one case:

$$\frac{1}{f} = \frac{1}{O'} + \frac{1}{I'} = \frac{-1}{18} + \frac{1}{26} = -\frac{1}{58.5}$$

$$-\frac{1}{58.5} = -58.5 \text{ cm}$$

- 3- Calculate  $\bar{f}$  and enter the results in Table 11.2. Compare the experimental value of  $\bar{f}$  with the actual value of the focal length printed on the lens.

$$\bar{f} = \frac{-58.5 - 46.2 - 42}{3} = -48.9 \text{ cm}$$

Experimental value:

$$\bar{f} = -48.9 \text{ cm}$$

Actual value:

$$f = -50 \text{ cm}$$

4. Calculate the error  $\Delta \bar{f}$  using the standard deviation method

$$\Delta \bar{f} = \frac{|F_{\text{actual}} - F_{\text{exp}}|}{F_{\text{actual}}} \times 100\% = 2.2\%$$

$$\Delta \bar{f} = \sqrt{\frac{(-58.5 + 48.9)^2 + (-46.2 + 48.9)^2 + (-42 + 48.9)^2}{6}} = \pm 4.95 \text{ cm}$$

- 5- Calculate the magnification  $M$ , using the height of the object and the height of the image, or using equation 11.2 and enter the results in Table 11.2

example of one case:

$$M = -\frac{i'}{O'} = -\frac{+26}{-18} = 1.44$$