

Spring 017



Dr. Deefallah Aldalabeeh

BY:

Mohammed Abuhashieh

Powerunit-ju.com

Electrical
Machines (I)

Second
Semester
(2017)

Dr. Daifallah Dalabeih.

* Mohammad
Abu Hashia. *




* Magnetic Fields:

Why ?? → Because it is fundamental for operation of Transformers & Machines as follow:


Principle 1: Any current (i), generates Magnetic Field (ϕ) where $\phi \propto i \implies$ That is for DC current ϕ will not change with time. also for AC current ϕ will change with time.

* where ϕ is represented by closed lines.

\implies its direction can be found by mean of RHR.
 \hookrightarrow "Right Hand Rule"

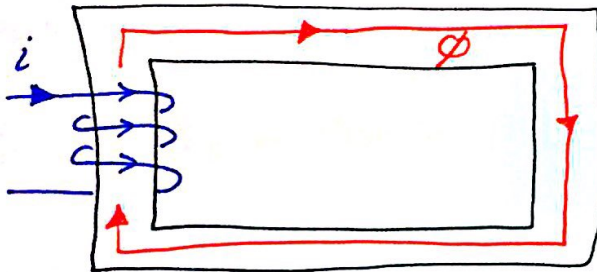

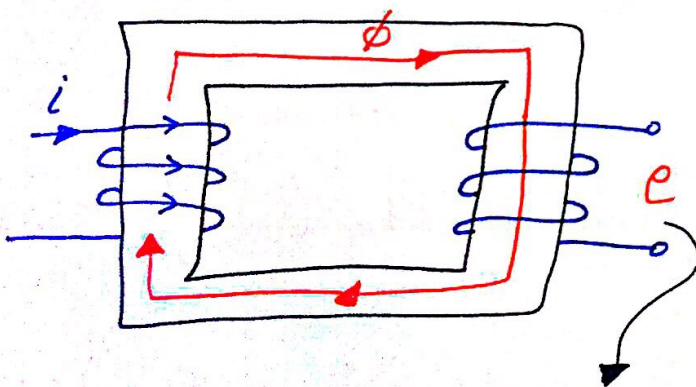
Principle 2: If the generated ϕ links or cut another conductor it will induce a voltage (e) in it.



" This is the basic principle of transformer action. "

Determine the polarity by using Dot Convention.

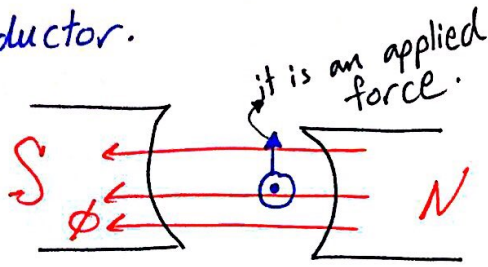Principle [3]: If the conductor cut or move through a magnetic field then a voltage will be induced in the conductor.




"This is the generator" action.

determine the polarity by using RHR.

Principle [4]: the current carrying conductor in a magnetic field will experience a force (F).

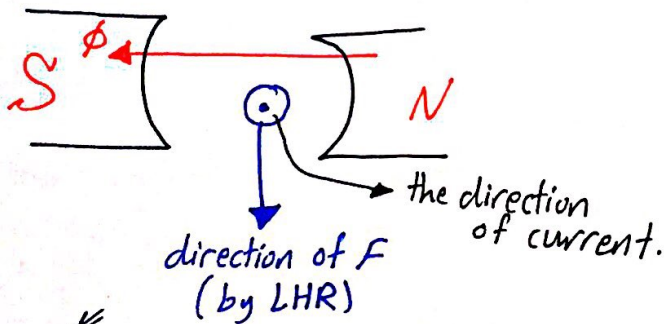* Determine the direction of (F) by using LHR
 ↳ Left Hand Rule.



"This is the" motor action.

↳ it is a generated force.

* Basic Mathematical Laws & Concepts:


[1] Amper's Law:

$$\oint \vec{H} \cdot d\vec{l} = Ni$$

* for the mean length (l_c) of flux path:

$$H l_c = Ni$$

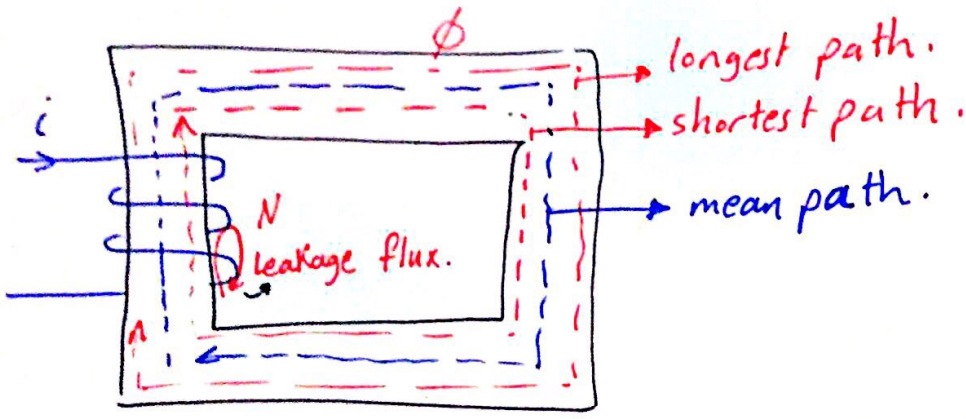- H: Magnetic field intensity.
- l : length of a closed loop.
- Ni: Total current enclosed by l :
- $i \equiv$ Applied Current.
- $N \equiv$ Number of Turns.



2 Flux Density (B):

$\int \vec{B} \cdot d\vec{A} = \phi$ A: Cross section Area on which ϕ is \perp .

$BA = \phi \Rightarrow$ unit of B is Wb/m^2 or Tesla.

$B = \mu H$ $\mu \equiv$ Permeability.

$\mu = \mu_0 \mu_r$ $\mu_r \equiv$ Relative permeability of magnetic material being used.
 $\mu_0 \equiv$ free space permeability
 $= 4\pi * 10^{-7}$

$Ni = Hl = \frac{B}{\mu} l$

$\therefore Ni = \frac{\phi}{\mu} l = \phi \left(\frac{l}{\mu} \right)$

$Ni = \phi R$

where: $R = \frac{l}{\mu}$ called Reluctance.

* Typical values of μ_r : (2000 \rightarrow 6000).

* $\phi = \frac{Ni}{R} \Rightarrow$ Hence, for a given mmf (i.e Ni) the higher the value of R the smaller the value of produced ϕ .

Note: since air has a very high R then in electrical Machines \Rightarrow the air gap between stator & Rotor should be small as possible (i.e just a clearance to make rotation possible).

* Analogy between electrical & magnetic circuits:

electrical	magnetic
emf, e	mmf, Ni
i	ϕ
R	R

∴ KCL & KVL: series & parallel combination laws are applicable to magnetic cKts.


* However: the solution obtained by magnetic ckt concept is approximate.

why??

Because:

- ① Not all the generated flux flow in the core. There is some flux flow in the surrounding air called "leakage flux".
- ② Mean length of flux path is used.
- ③ In solving one use $B = \mu H$ which assumes that μ is constant which is not in the real case as will be shown.

* Magnetic Circuits with Airgap:

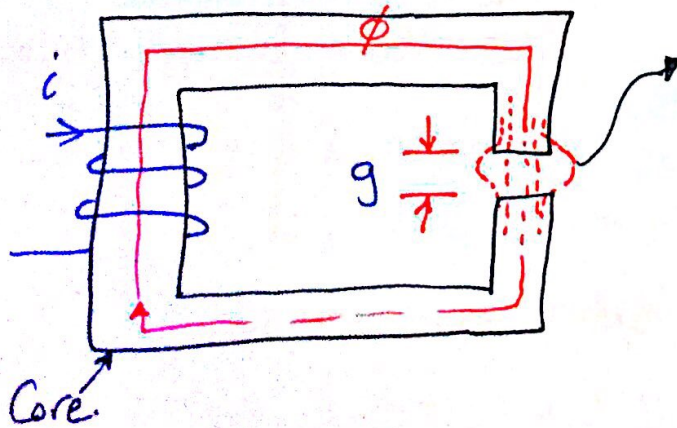

This called: Fringing field.

* Due to fringing field, then:

$$B_g = \frac{\phi}{A_g}$$

$B_g, A_g \equiv$ flux density and Area of the air gap.

$$\Rightarrow B_c = \frac{\phi}{A_c}$$

$B_c, A_c \equiv$ flux density and Area of the core.

$\Rightarrow g \equiv$ length of Airgap.

* One of the empirical methods of calculating A_g is to add g to the length of sides which make A_c .
 \Rightarrow if $A_c = a * b$ then $A_g = ([a+g] * [b+g])$


OR: $A_g = \text{a factor} * A_c$

* For e.g assume that A_g is increased by 5% :

$\therefore A_g = 1.05 * A_c$

* Characteristic of Magnetic Material:

Consider the following structure:

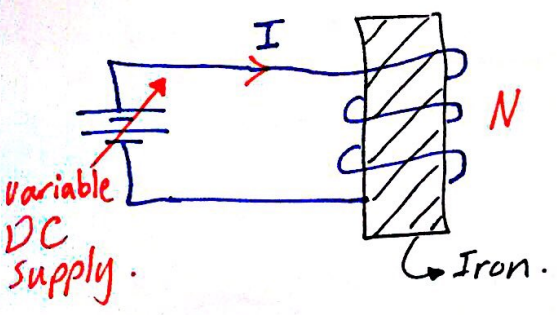


* Gradually Increase I , then measure the generated flux. Assuming initially there is No flux in the Iron.

The result will be as follows:



(Here all the domains are oriented in the direction of applied magnetic field).

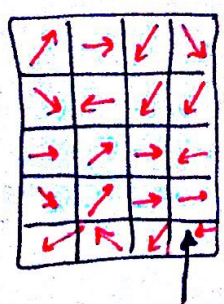\Rightarrow This curve called: "Magnetization Curve."



Domain.

* Each Domain can be considered as a permanent magnet.

$\nearrow \equiv$ Direction of magnetic field in each domain.


since $\phi = BA$, $\therefore B = \frac{\phi}{A} \Rightarrow Ni = Hl$ (6)
 $\Rightarrow \therefore H = \frac{Ni}{l}$

so the curve could be for:

ϕ OR B & Ni OR H


Consequently, The curve is called "B-H curve."

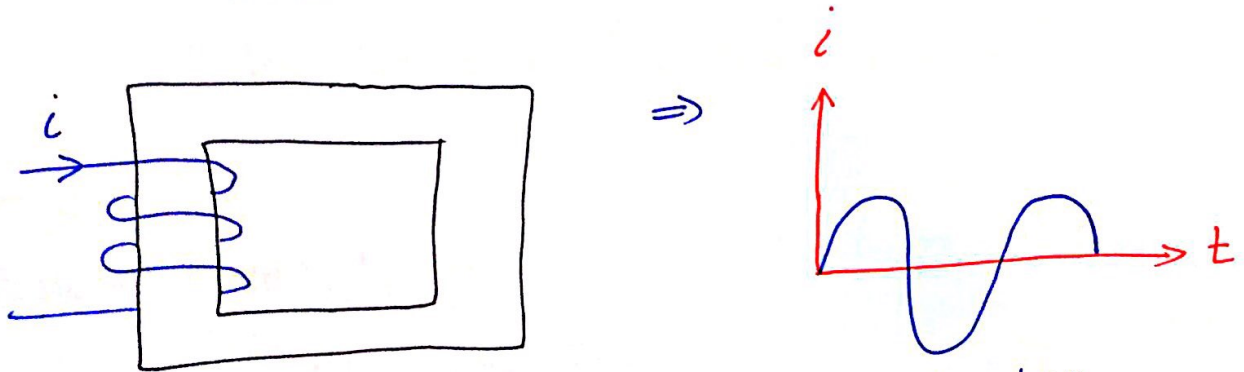* Losses in Magnetic Materials [Due to Magnetic Effect].



in the case of sinusoidal current the relationship between B and H is expressed in terms of Hysteresis loop as follow:

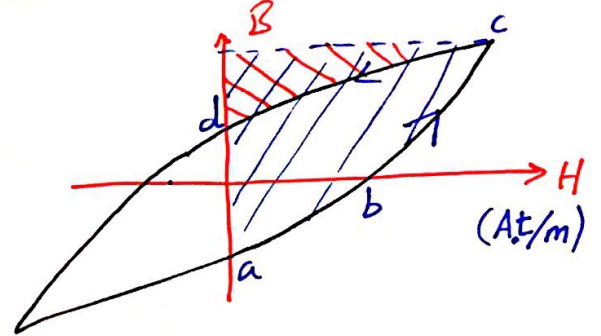\therefore For each cycle of i there is one hysteresis loop.



Area of H-loop $\iint H dB$

$\Rightarrow \int_{B_a}^{B_c} H dB \equiv$ Energy supplied by the source to magnetic material. [1]

\hookrightarrow it is the blue dashed area.

$\Rightarrow \int_{B_c}^{B_d} H dB \equiv$ Energy Returned to the supply. [2]

\hookrightarrow it is the red dashed area.

⇒ ∴ Difference between ① & ② gives the Area of ⑦
 $\frac{1}{2}$ H-loop which is equivalent to $\frac{1}{2}$ cycle of applied current.

* This difference represent the energy lost in the magnetic material due to the Domain's orientation.

∴ The Area of H-loop represent the energy lost due to one cycle applied current.

↳ This called "Hysteresis Losses."

* Analysis :

Area of H-loop: $A_h = HB$ --- ① $H \equiv A \cdot t / m$ --- ②

$$F = BIL \implies B = \frac{F}{IL} \equiv \left[\frac{N}{A \cdot m} \right] \text{ --- ③}$$

substitute ② & ③ into ①, to find unit or dimension of A_h .

$$A_h \equiv \frac{A \cdot t}{m} \cdot \frac{N}{A \cdot m} = \frac{N}{m^2} \text{ --- ④} \quad \Rightarrow \text{But } J \equiv N \cdot m.$$

so $N = \frac{J}{m} \text{ --- ⑤}$

Now sub. ⑤ into ④:

$$\underline{\underline{A_h = \frac{J}{m^3}}} \text{ --- ⑥} \quad \therefore \text{ i.e Area of H-loop represent: "Energy density"}$$

Now ⑥ can be expressed as follows:

$$A_h = \frac{\text{Total Energy Lost}}{\text{Volume of ferro-magnetic material} * \text{Number of cycles.}}$$

$$\therefore A_h = \frac{P_h * \text{Time (seconds)}}{V * \text{No. of cycles.}}$$

where:
 $P_h \equiv$ hysteresis losses
 (Watt).

$$\Rightarrow A_h = \frac{P_h}{V * \left(\frac{\text{No. of cycles}}{\text{seconds}} \right)}$$

f → it is the frequency of the applied current.

$$\Rightarrow P_h = A_h V f$$

* By performing various experiments A_h is expressed as:

$$A_h = K_h B_m^n$$

where:

$B_m \equiv$ Maximum or Peak value of flux density.

n & $K_h \equiv$ Constants depend on the type of ferromagnetic material.

* typically: $1.5 \leq n \leq 2.5$

$$\therefore P_h = K_h B_m^n V f$$

* Eddy Current Losses:

if i is sinusoidal \Rightarrow generates sinusoidal ϕ in the core

$\Rightarrow \phi$ induces a voltage e in the core, where $e \propto B_m f$

\Rightarrow since the core is made of conducting material then

a current i_e will flow within the core, it flows in circular direction, hence it is called "Eddy Current."

$$\Rightarrow i_e \propto e \propto B_m f.$$

Hence the so called Eddy current, losses P_e will be generated within the core $\Rightarrow P_e \propto i_e^2, B_m^2 f^2$

* P_e can be reduced by manufacturing the core of laminations between which there is an insulating material in order to reduce i_e .

\Rightarrow Where the laminations are installed parallel to flux direction. \rightarrow Consequently the stacking factor is introduced and defined as:

$$\text{Stacking factor} = \frac{\text{Volume of ferromagnetic material}}{\text{Total volume of the core}}$$

$\therefore P_e$ can be expressed in terms of:

$\tau \equiv$ Lamination Thickness.

$K_e \equiv$ Constant depend on the material.

$V \equiv$ volume of ferromagnetic material.

$B_m, f \equiv$ max. flux & frequency.

* Eddy current losses P_e can be expressed as:

$$P_e = K_e \tau^2 V B_m^2 f^2$$

* The sum of P_e & P_h is called "Core Losses".

$$P_{\text{core}} = P_h + P_e$$

ex. A given magnetic material has a core losses of 1800 W when the frequency is 60 Hz. if the frequency is increased by 50% and at the same flux density core losses become 3000 W Find P_e & P_h at each frequency?

Solution:

since B_m is kept constant and for the same core.

$\therefore P_h \propto f \quad P_e \propto f^2$

$\therefore P_h = K_1 f, \quad P_e = K_2 f^2$

for $f = 60 \text{ Hz}$: $K_1 \cdot 60 + K_2 \cdot 3600 = 1800$ --- ①

for $f = 90 \text{ Hz}$: $K_1 \cdot 90 + K_2 \cdot 8100 = 3000$ --- ②

\Rightarrow solving: $K_2 = \frac{1}{9}$

f	P_e	P_h
60	$\frac{1}{9} * 60 * 60 = 400$	$1800 - 400 = 1400$
90	$\frac{1}{9} * 90 * 90 = 900$	$3000 - 900 = 2100$

*** Self Inductance:**


due to ϕ which is generated by i a voltage "e" is induced in the coil.

\Rightarrow By Faraday's Law:

$e = -N \frac{d\phi}{dt}$

Introduced to find the polarity of e.

Number of turns of the coil.

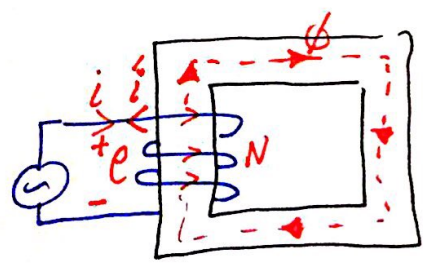

$$\therefore e = N \frac{d\phi}{dt} \dots \text{--- [1]}$$

$$Ni = R\phi \quad \therefore \phi = \frac{Ni}{R} \dots \text{--- [2]}$$

substitute [2] into [1]:

$$e = N \frac{N}{R} \frac{\partial i}{\partial t} = \frac{N^2}{R} \frac{\partial i}{\partial t} = L \frac{\partial i}{\partial t}$$


$$L = \frac{N^2}{R} = \frac{N^2 \mu A}{l} \Rightarrow \text{self inductance.}$$

* Application of Magnetic ccts to Electrical Machines:


* In Electrical Machines, Magnetic field is produced by Electromagnets as follows:

The polarity of the poles can be identified by mean of RHR.

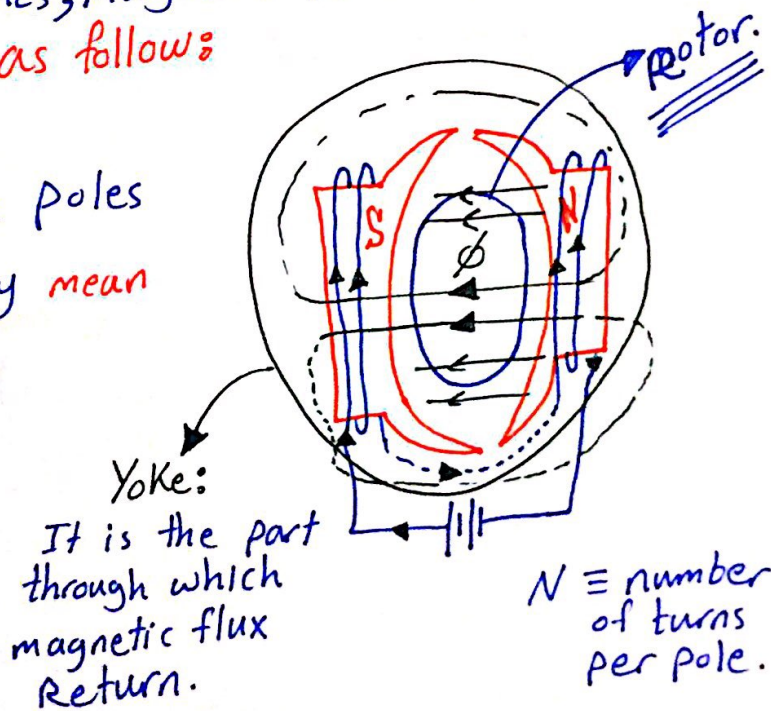remember:
* Always flux leaving the (N) and entering the (S).



* Consider a 4 poles Machine:

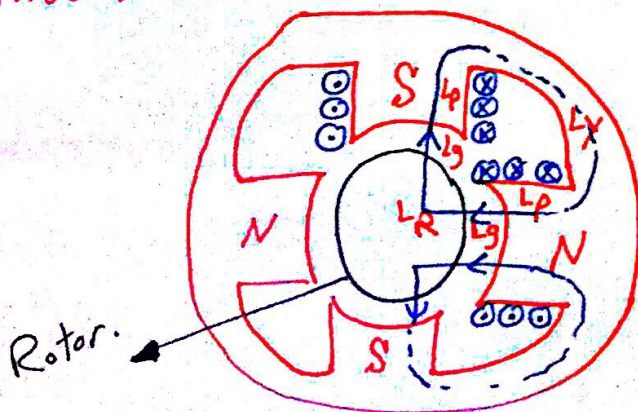

$L \equiv$ length of flux path.

subscripts:

$P \equiv$ Pole

$g \equiv$ Airgap.

$R \equiv$ Rotor.

$Y \equiv$ Yoke.

⇒ Apply Amper's Law:

$$\oint H \cdot dl = NI \Rightarrow H_p L_p + H_g L_g + H_R L_R + H_g L_g + H_p L_p + H_y L_y = NI + NI$$

$$\Rightarrow 2H_p L_p + 2H_g L_g + H_R L_R + H_y L_y = 2NI$$

$$\therefore \underline{NI} = H_p L_p + H_g L_g + \frac{1}{2} H_R L_R + \frac{1}{2} H_y L_y \quad \dots \text{--- (1)}$$



↳ Amper-turns per pole.

**** Procedure:**

For the given specified flux density, then one from the given magnetization curve, then one can determine from the curve H_p, H_R and H_y .

Also given B_g since $B_g = \mu_0 H_g$, then H_g can be calculated.

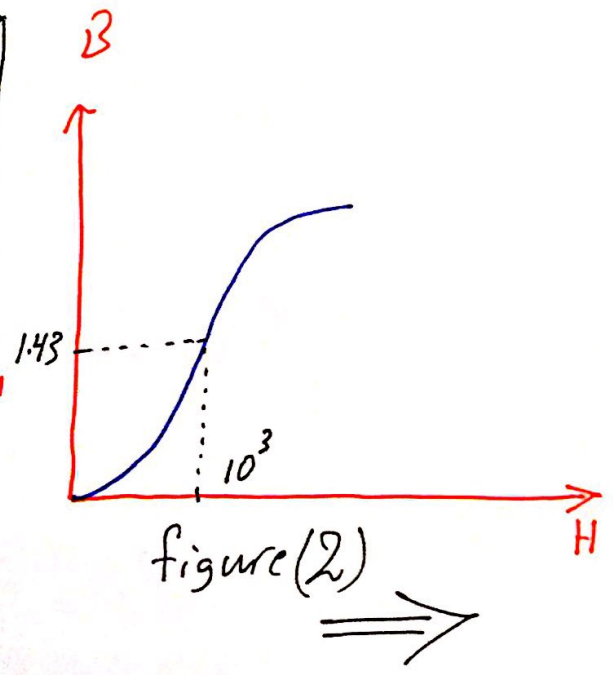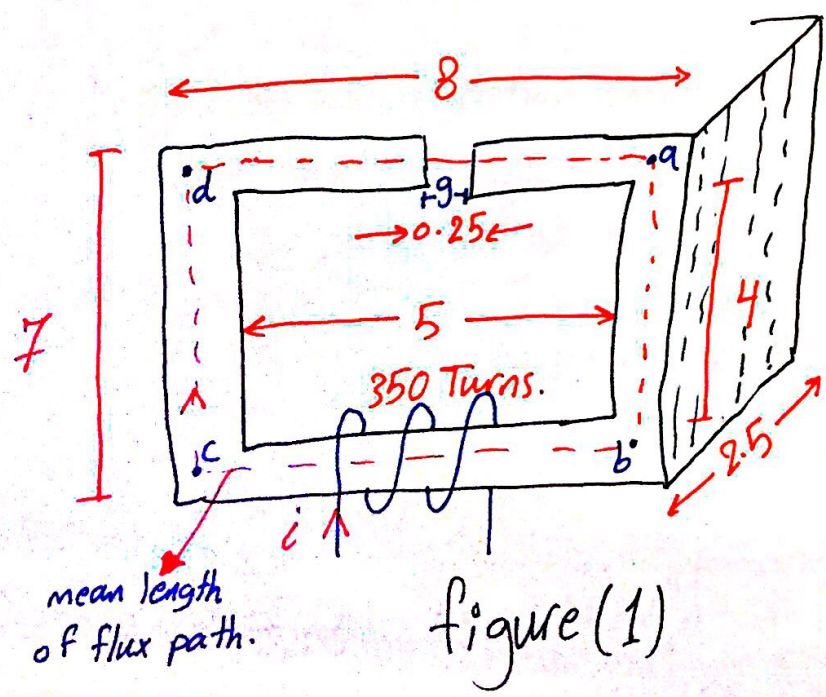Knowing L_p, L_g, L_R and L_y ∴ From (1), Required NI can be calculated.




(ex.) For the magnetic ckt. shown in Figure (1) is made of laminated steel core. It has the given magnetization curve shown in figure (2)

The stacking factor = 0.93

All dimensions in cm.

* Calculate the required exciting current i , To produce a flux of 5×10^{-4} Wb in the core? [Neglect leakage flux].

Solution:

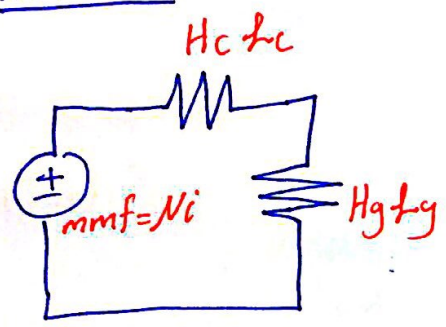

* Net Area of the core = $(1.5 \times 10^{-2} \times 2.5 \times 10^{-2} \times 0.93)$
= $3.49 \times 10^{-4} \text{ m}^2$

* mean length of flux path in steel. = $(ab + cd) + cb + (ad + g)$
= $2(4 + \frac{1.5}{2} + \frac{1.5}{2}) + (5 + \frac{1.5}{2} + \frac{1.5}{2})$
+ $(5 + \frac{1.5}{2} + \frac{1.5}{2} - 0.25)$
= 0.2375 m .

* Flux density in the steel. = $\frac{\phi}{A}$
= $\frac{5 \times 10^{-4}}{3.49 \times 10^{-4}} = 1.43 \text{ Tesla}$.

* ∴ from the magnetization curve, for $B = 1.43 \text{ T}$. ⇒ it can be found that:

$H = 10^3 \text{ A.t/m}$

⇒ $B_g = \frac{\phi}{A_g}$; $A_g = (1.5 + 0.25) \times (2.5 + 0.25) \times 10^{-4} = 4.81 \times 10^{-4} \text{ m}^2$

* $B_g = \frac{5 \times 10^{-4}}{4.81 \times 10^{-4}} = 1.04 \text{ T}$

* $B_g = \mu_0 H_g \Rightarrow H_g = 8.28 \times 10^5 \text{ A.t/m}$

⇒
Continue.

⇒ ∴ By substitution:

$$\text{Total mmf} = Ni = \sqrt{\text{steel}} + \sqrt{\text{gap}} = H_c L_c + H_g g$$

$$\Rightarrow Ni = 2307.5$$

so $i = 6.6$ Amp.

End of CH1.

CHAPTER(2):

* Transformer:

What?! ⇒ it is a device or Equipment which can be used to step-up or step-down a voltage or current.

(Voltage/Potential transformer) or (current transformer)

Why?! *Objective:

→ 1) It can be used in the process of transmitting and distributing electrical energy with minimum losses. In this case it is called: "Power Transformer".

⇒ 2) It can be used in the process of measuring High currents & voltages. In this case it is called: "Instrument Transformer".

* There are 2 types: ① voltage or Potential transformer (VT or PT).
② Current transformer (CT).

⇒ Here we are concerned with: "Power Transformer".

* Power Transformer:

Construction:


It consists of:

- ① Core .
- ② A number of windings .

* * Core: Basically There are:

1] Core Type: This is a rectangular core.


2] Shell Type: This is a 3-leg. Core.

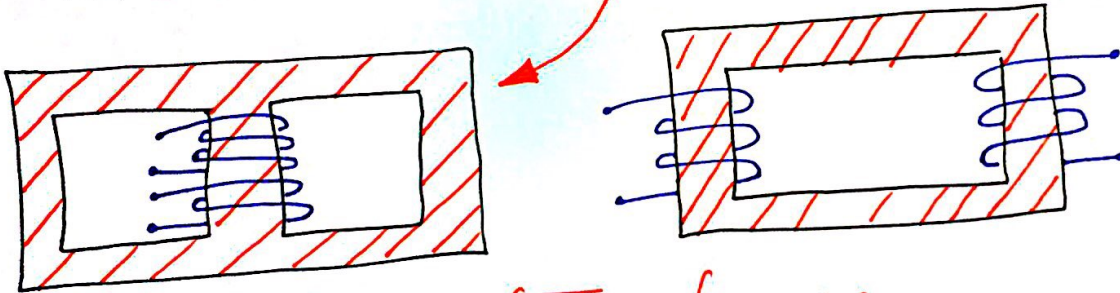

* Classification of Transformers:

- 1) Unit Transformer: This is at the power station used to step-up voltage for Transmission.
- 2) Substation Transformer: This is at the end of a transmission line and used to step-down voltage.
- 3) Distribution Transformer: This is used to step-down the voltage for various consumers.

→
continue for
the figure.

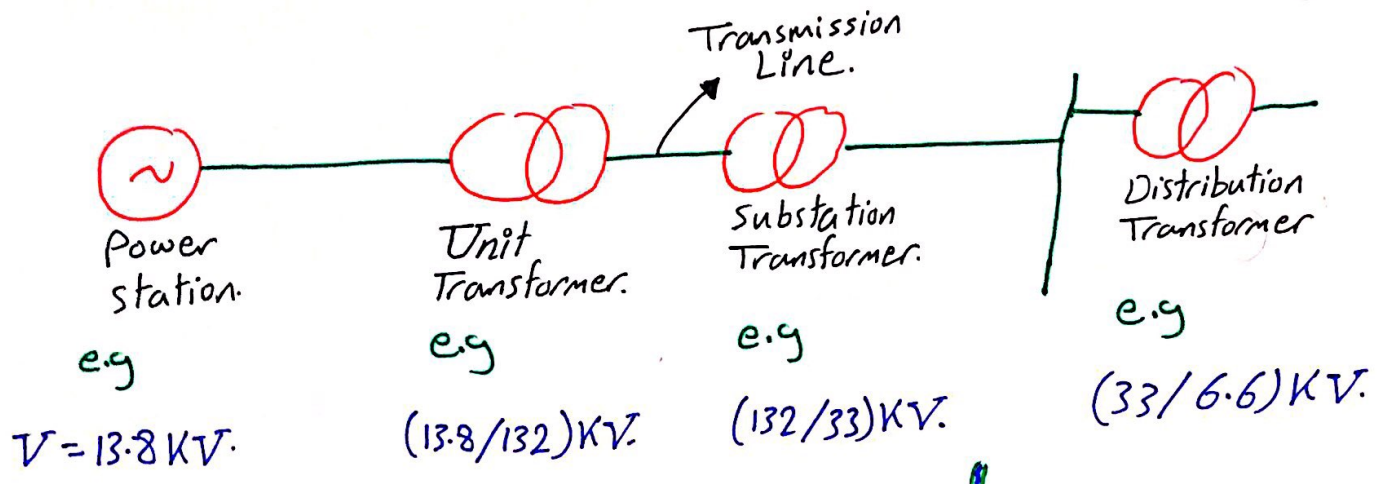


Note:

In Jordan 2-transmission Levels:
[132 and 400] KVolt.

This figure
Called:
Single Line
Diagram
Representation.

How?! (Analysis)

* Single-phase Transformer:

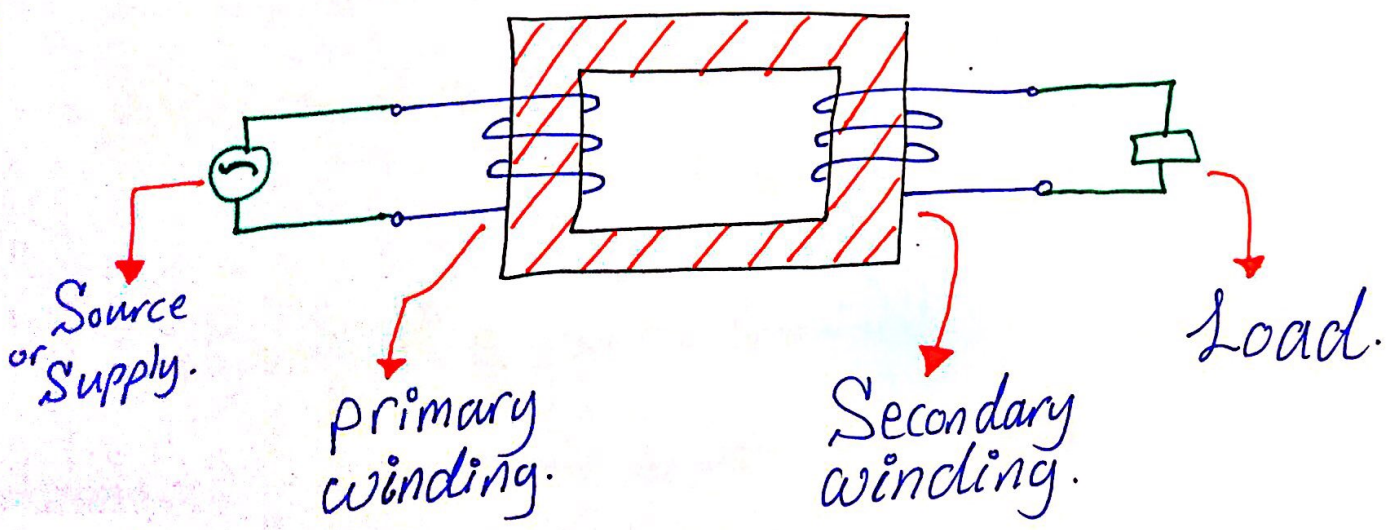

*Analysis of 1-ph Transformer:

* Ideal Transformer:

⇒ Assumptions:

- 1] Lossless Transformer. (i.e. No core losses & No Electric Losses.)
- 2] No Leakage Flux.

⇒ Objectives:


- To find voltage, current and power Relationship for this transformer.

⇒ Procedure:

$V_p \equiv$ Primary Applied Voltage.

$i_p \equiv$ Primary Current.

* i_p generates ϕ .

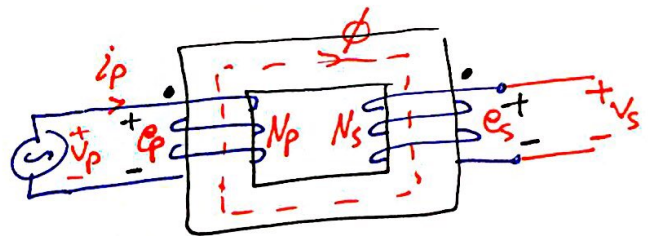

$e_p, e_s \equiv$ The induced voltage in the primary & the secondary due to ϕ .

*** Polarity of e_p can be found by "Lenz's Law."



*** Polarity of e_s can be found by "Dot Convention."

* if the current enter the left dot will make the other dot (+).

* if the current enter the undotted it will make the other undotted (+).



$N_p, N_s \equiv$ Number of turns of primary & secondary windings.

(18)

by Faraday's Law $e \triangleq N \frac{d\phi}{dt}$

$V_s \equiv$ Called secondary Terminal voltage.

$\therefore V_p = e_p = N_p \frac{d\phi}{dt}$ [1]

$V_s = e_s = N_s \frac{d\phi}{dt}$ [2]


\therefore divide [1] over [2]:

$$\frac{V_p}{V_s} = \frac{e_p}{e_s} = \frac{N_p}{N_s}$$

* Up to know i_p is called "No-load Primary Current".

* Loading Condition:

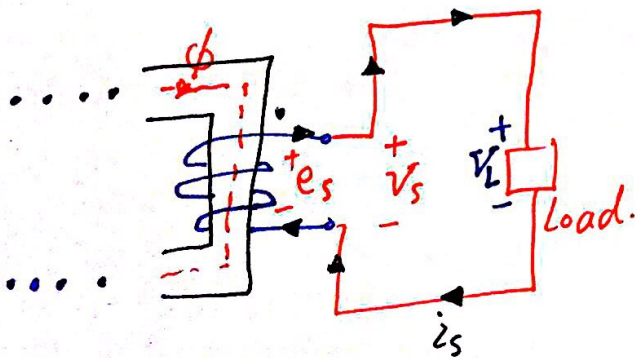\Rightarrow Connect a load to the secondary.



\hookrightarrow Then i_s is going to flow according to the convention of current flow in a source.

(i.e. The current is going to flow out from the Dot.)



⇒ i_s is going to generate (ϕ_s) → This ϕ_s opposes the main ϕ → Consequently, Resultant flux in the core is going to be Reduced

→ Consequently, $e_p \downarrow$ Hence i_p is going to increase by an amount (i_{pL}) in such a way to produce additional mmf to oppose that produced by i_s
⇒ in order to maintain the same flux in the core.

$i_{pL} \equiv$ Load component of primary current.

∴ $i_{pL} N_p = i_s N_s$ [3]

∴ In general: $i_p \equiv$ No Load component (i_0) + Load Component (i_{pL}).

However: $i_{pL} \gg i_0$ [4]

∴ $i_p = i_{pL}$

⇒ Substitute [4] in [3]: [5]

∴ $i_p N_p = i_s N_s$

⇒ $\frac{i_p}{i_s} = \frac{N_s}{N_p}$

∴ $\frac{e_p}{e_s} = \frac{i_s}{i_p} = \frac{N_p}{N_s}$

This called: Current-Voltage Relation.

⇒ $a = \frac{N_p}{N_s}$

↳ a "Turns Ratio"

$$* \quad a = \frac{V_p}{V_s} = \frac{e_p}{e_s} = \frac{i_s}{i_p} = \frac{N_p}{N_s}$$

since a is Real, Then e_p & e_s are "in-phase".
Also i_p & i_s are "in-phase".

\therefore phase angle of Primary & Secondary ccts are equal.

$$\therefore \frac{V_p}{V_s} = \frac{I_s}{I_p} = a \quad \text{where } V_s I_s \equiv \text{phasor voltages.} \\ \text{ \& currents.}$$

\Rightarrow we can reach that:

$$|V_p| |I_p| = |V_s| |I_s|$$

Then you can reach that
primary & secondary have the
Same apparent power (VA).

$$* \quad \left[\begin{array}{l} P_p = V_p I_p \cos \theta_p \\ P_s = V_s I_s \cos \theta_s \end{array} \right]$$

and we know $\theta_p = \theta_s$


$$\Rightarrow \underline{\underline{P_p}} = (a V_s) * \left(\frac{I_s}{a} \right) \cos \theta_s = \underline{\underline{P_s}}$$

$$\therefore \text{For Ideal Transformer, } \eta = \frac{P_{out}}{P_{in}} = \frac{P_s}{P_p} = \frac{P_p}{P_s} = 1 = 100\%$$

efficiency.

* Impedance Reflection:

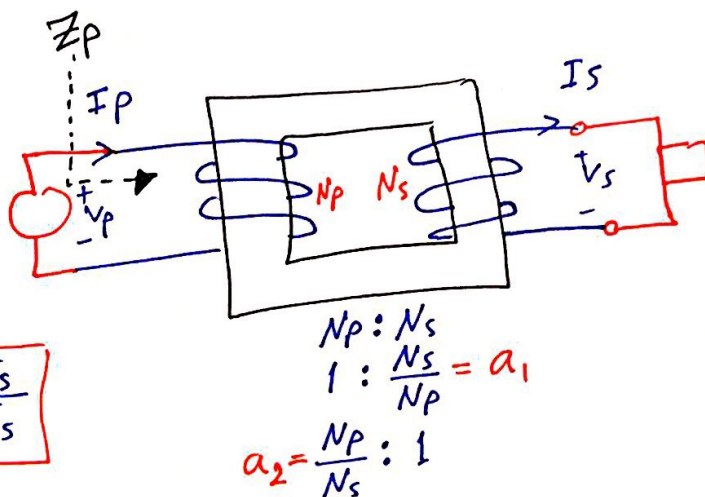$Z_P \equiv$ Impedance of Transformer seen from Primary Terminal.




$$Z_P = \frac{V_P}{I_P} \quad , \quad Z_S = \frac{V_S}{I_S}$$

$$\Rightarrow Z_P = \frac{V_P}{I_P} = \frac{a V_S}{\frac{I_S}{a}} = a^2 \frac{V_S}{I_S} = a^2 Z_S$$

$$\Rightarrow Z_P = a^2 Z_S$$

OR

$$Z_S = \frac{Z_P}{a^2}$$

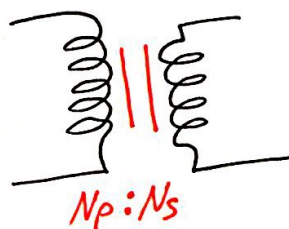

$$a = \frac{N_p}{N_s} : 1$$

This called: (a) side

This called: (one) side.

** To Reflect an Impedance to a-side multiply it by a^2 .

** To Reflect an Impedance to 1-side divide it by a^2 .


* Real/Practical Transformer:

* since each turn doesn't have the same flux,

Then the concept of Flux linkage (λ) and defined as follow:

$$\lambda = \sum_{i=1}^N \phi_i$$

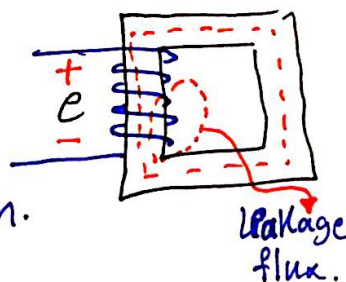$\phi_i \equiv$ flux passing through i^{th} turn.
 $N \equiv$ Number of turns.



∴ Average flux Per turn ($\bar{\phi}$):

$$\bar{\phi} = \frac{\lambda}{N}$$


∴ Voltage induced (e):

by Faraday's Law:

$$e = \frac{d\lambda}{dt}$$

$$\therefore e = \frac{d\lambda}{dt} = \frac{d(N\bar{\phi})}{dt}$$

$$* e = N \frac{d\bar{\phi}}{dt} *$$

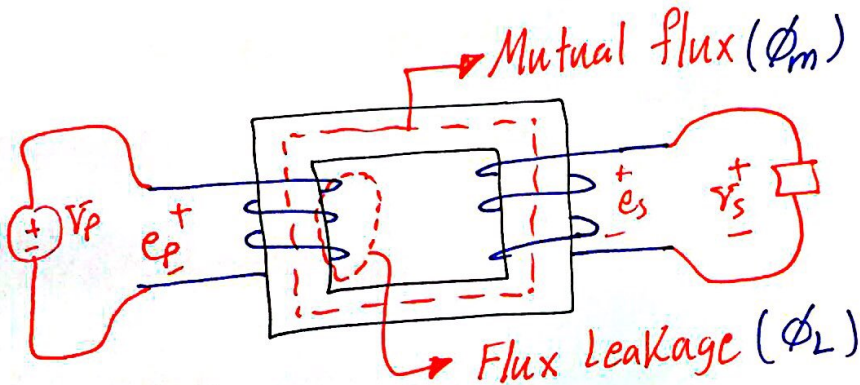

* For the primary:

$$\therefore \bar{\phi}_p = \phi_m + \phi_{LP}$$

$\bar{\phi}_p \equiv$ Average flux in the primary.
 $\phi_m \equiv$ Mutual flux.
 $\phi_{LP} \equiv$ primary leakage flux.

* For the secondary:

$$\therefore \bar{\phi}_s = \phi_m + \phi_{LS}$$

$\bar{\phi}_s \equiv$ Average flux in the secondary.
 $\phi_{LS} \equiv$ Leakage flux in the secondary.

$$\Rightarrow \begin{cases} e_p = N_p \frac{d\bar{\phi}_p}{dt} = \left(N_p \frac{d\phi_m}{dt} \right) + \left(N_p \frac{d\phi_{LP}}{dt} \right) \\ e_s = N_s \frac{d\bar{\phi}_s}{dt} = \left(N_s \frac{d\phi_m}{dt} \right) + \left(N_s \frac{d\phi_{LS}}{dt} \right) \end{cases}$$

Labels: e_{pm} (pointing to the mutual flux term in the primary equation), e_{pL} (pointing to the primary leakage term), e_{sm} (pointing to the mutual flux term in the secondary equation), and e_{sL} (pointing to the secondary leakage term).

$$\therefore \begin{cases} e_p = e_{pm} + e_{pL} \\ e_s = e_{sm} + e_{sL} \end{cases}$$

$$\frac{e_{pm}}{e_{sm}} = \frac{N_p}{N_s}$$

Turns Ratio is equal to the ratio of induced voltage in secondary & primary due to mutual flux.

If:


- 1) Resistance of the windings are neglected.
- 2) For a well designed Iron Transformer, ϕ_{LP} & ϕ_{LS} are very small, Then:

$$\begin{aligned} V_p = e_p &= N_p \frac{d\phi}{dt} \\ V_s = e_s &= N_s \frac{d\phi}{dt} \end{aligned} \Rightarrow \therefore \frac{V_p}{V_s} = \frac{e_p}{e_s} = \frac{N_p}{N_s}$$

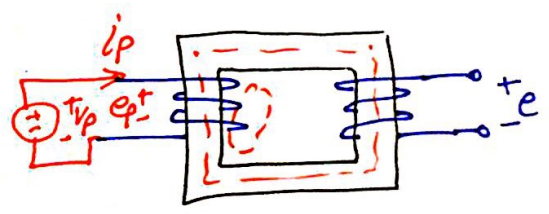*** Current Relationship:**

* Consider No-load Condition:

i_p in this case is called (Excitation Current)



=> For practical transformer, There is losses:

Losses = core losses + electrical losses.

$$= (P_h + P_e) + i_p^2 R_p$$

$R_p \equiv$ Resistance of primary windings.

usually $P_e + P_h \gg i_p^2 R_p$

$\therefore i_p$ has two functions:

- 1) To generate flux. $\Rightarrow i_m$.
- 2) To supply or account for core losses. $\Rightarrow i_c$.

$\therefore i_p = i_m + i_c$ → Loss Component.
 ↓
 Magnetization Component.

* Objective:

To find the wave shape of i_p .

- 1) find waveshape of i_m .
- 2) find wave shape of i_c .
- 3) Sum of the two waves.

$v = N \frac{d\phi}{dt} \Rightarrow \therefore \phi = \frac{1}{N} \int v dt.$

if $v = V_m \cos \omega t$, Then $\phi = \phi_m \sin \omega t.$

\Rightarrow since $N i_m = R \phi$

Then by using Figure (1), (2)

& the magnetization curve (ϕ vs i_m)

\Rightarrow one can graphically deduce the wave shape of i_m .

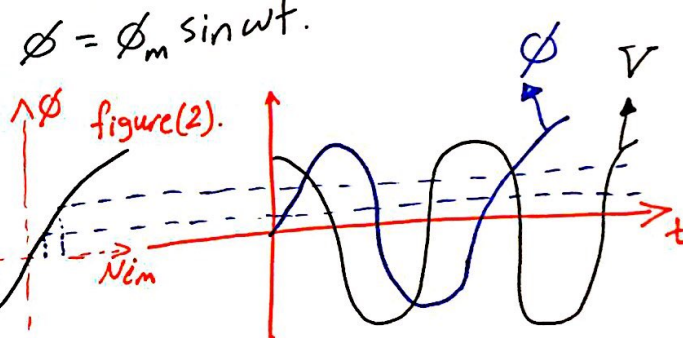


figure (1).

It can be found the shape will be as follows: \Rightarrow figure (3)


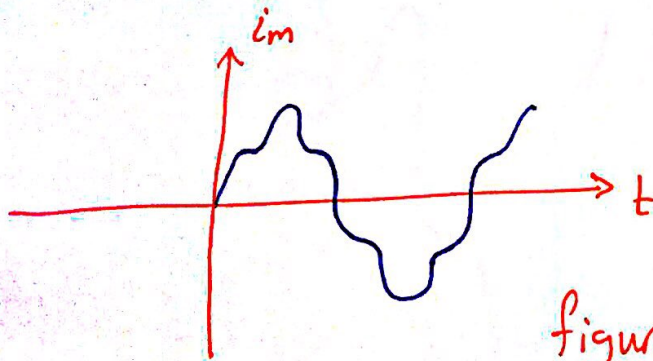


figure (3).

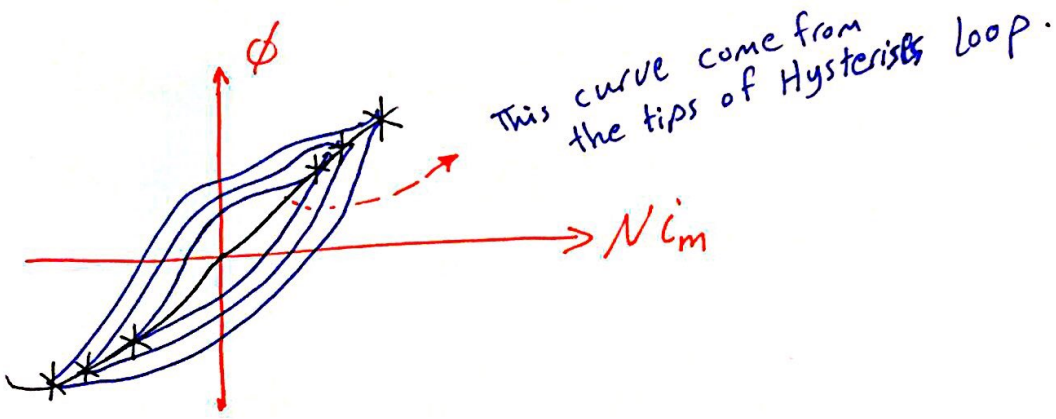$\Rightarrow i_m$ is Non-Pure sinusoidal
 i.e. distorted.




i_c : To represent eddy + hys. losses.

$$i_{eddy} \propto C_{eddy} \propto \frac{d\phi}{dt}$$


$\therefore P_e$ is maximum when $\phi = 0$

Since $P_{eddy} \propto i_{eddy}^2$

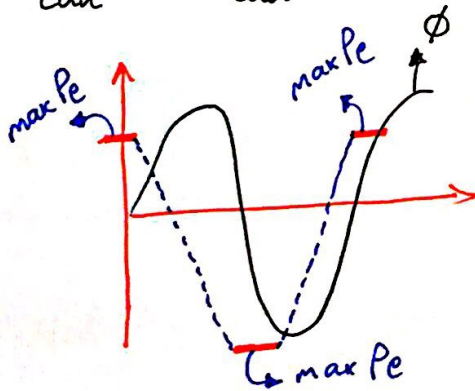

** P_{phys} is a non-linear complex function of Applied voltage.

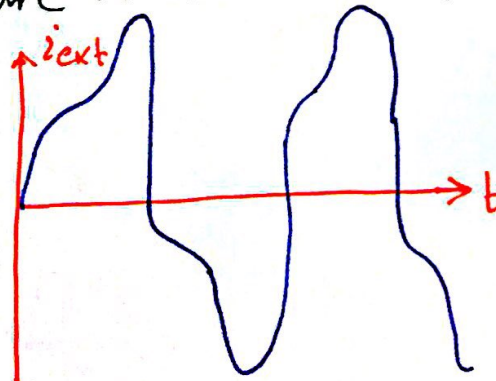When i_m & i_c are added the shape of i_{ext} will be as follow:



* i_{ext} is a periodic Non-sinusoidal current.

Comment:

By using Fourier Series, any periodic waveform can be written as sum of cos & sin terms:

$$i_{\text{ext}} = \underbrace{I_{m_1} \cos \omega t}_{\text{Fundamental Component}} + \underbrace{I_{m_2} \cos 2\omega t + I_{m_3} \cos 3\omega t + I_{m_4} \cos 4\omega t + \dots}_{\text{Harmonics}}$$

⇒ If (+ve) & (-ve) cycles are Identical, then the expression has only odd harmonics.


$$\therefore i_{\text{ext}} = I_{m_1} \cos \omega t + I_{m_3} \cos 3\omega t + I_{m_5} \cos 5\omega t + \dots$$

* Equivalent circuit of Real Transformer:

The equivalent ckt should take the followings into account:

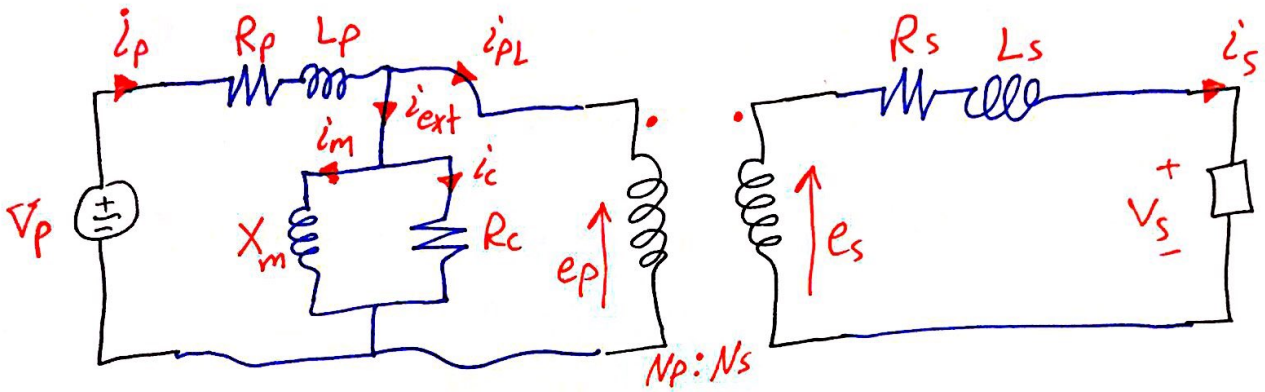- 1] Electrical losses in the primary & secondary windings. (I^2R).
- 2] Core losses.
- 3] Leakage flux. (i.e. $N \frac{d\phi_L}{dt}$).





$R_p, R_s \equiv$ To represent electrical losses in primary & Secondary.

$L_p, L_s \equiv$ To represent Leakage flux in primary & Secondary.

$R_c \equiv$ To represent Core Losses.

$X_m \equiv$ To represent generated flux by i_m .

$i_{PL} \equiv$ Load component of primary current.

$i_{ext} \equiv$ No-load. $i_p = i_{ext} + i_{PL}$

$e_p, e_s \equiv$ Induced voltages in primary & secondary.

$V_p \equiv$ Primary applied voltage.

$V_s \equiv$ Terminal Secondary voltage.




This circuit called

"Exact equivalent Circuit"


⇒ Since $I_{ext} \ll i_{pL}$ & the voltage drop in R_p & L_p is very small, then:

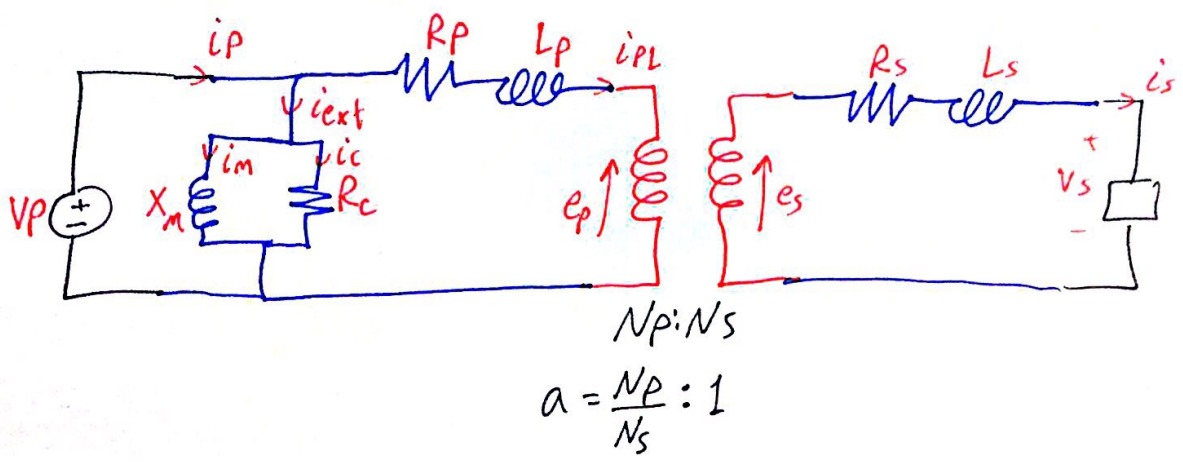The parallel branch ($X_m // R_c$) can be shifted to the input.



⇒ one can Reflect Primary to secondary or other way round.

* Reflection to Primary:

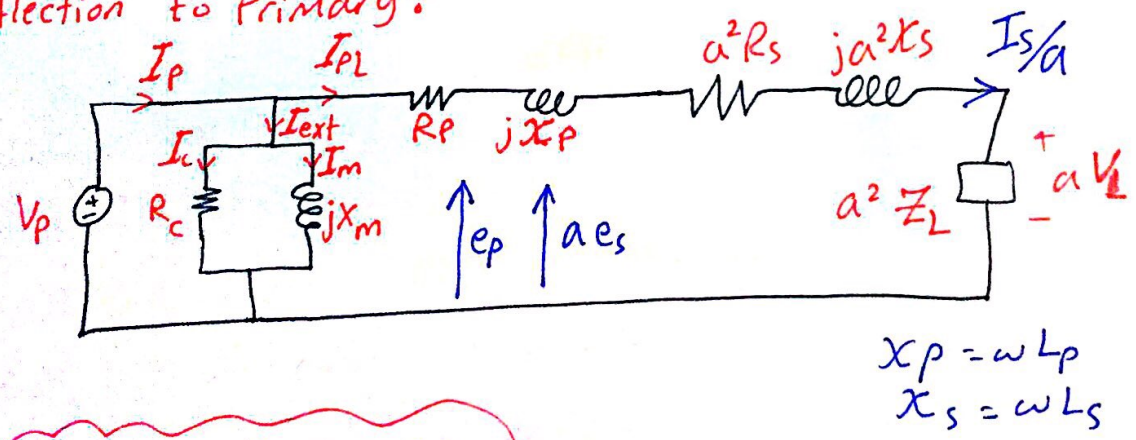


$$R_{eq(p)} = R_p + a^2 R_s$$

$$X_{eq(p)} = X_p + a^2 X_s$$

$$I_{ext} = I_c + I_m$$

$R_{eq}, X_{eq} \equiv$ Equivalent Resistance & Reactance of the transformer. (series).

* Now Reflection to Secondary:

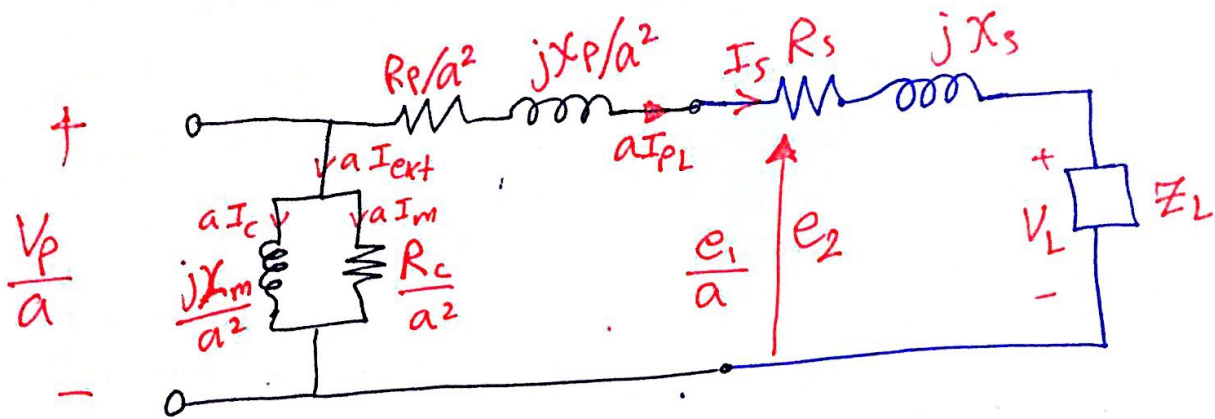

$$R_{eq(s)} = R_p/a^2 + R_s$$

$$X_{eq(s)} = X_p/a^2 + X_s$$

* Notice that:
 In Ω $R_{eq(p)} \neq R_{eq(s)}$
 $X_{eq(p)} \neq X_{eq(s)}$

* But However as will be shown later in PU system R_{eq} & X_{eq} is the same irrespective of the reflection side.


$$Z_{eq} = R_{eq} + jX_{eq}$$

* Evaluation of Transformer Parameter:

- What?! \Rightarrow To measure R_{eq}, X_{eq}, X_m & R_c .
- Why?! \Rightarrow Because these parameters are required in the process of Transformer analysis.
- How?! \Rightarrow By Performing o/c & s/c Test on the Transformer.

* O/C Test :

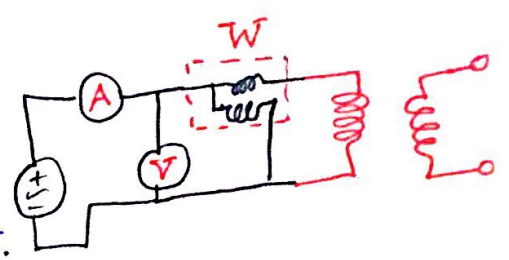- 1] o/c the secondary (i.e. $Z_L = \infty$).
- 2] Apply Rated Voltage to the Primary & take the readings of input voltage, current & power. (i.e. A, V, W)



* Illustration :

e.g. Transformer Rating (132/33) kV.


Note: As a Convention in the o/c test the low voltage side is made as primary because it is easier to measure its rating voltage. Hence, Readings are taken on LV side.

* Analysis :

This can be performed by using the eqn. cct. of $S \rightarrow P$.

$$\therefore \frac{I_s}{a} = I_{PL} = 0$$

$$\therefore I_p = I_{ext} = I_c + I_m$$

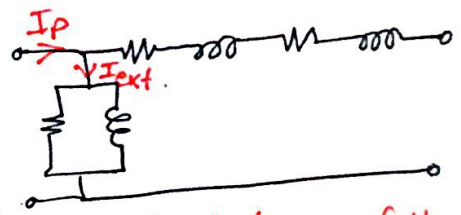

\therefore In the o/c test R_c & X_m can be evaluated as follows:

$I_p \equiv$ Ammeter Reading.

$V_p \equiv$ Voltmeter Reading.

Wattmeter Reading \equiv losses in the cct. \equiv losses in R_c

** Calculations :

$$\text{Wattmeter reading } P_{oc} = \frac{V_{oc}^2}{R_c} = \frac{(\text{voltmeter reading})^2}{R_c}$$

$$\therefore R_c = \frac{V_{oc}^2}{P_{oc}}$$

$$\text{Admittance } |Y| = \frac{\text{Ammeter reading}}{\text{voltmeter reading}}$$



$$\Rightarrow Y = \frac{1}{R_c} + \frac{1}{j X_m} \Rightarrow |Y| = \sqrt{\left(\frac{1}{R_c}\right)^2 + \left(\frac{1}{X_m}\right)^2}$$

$$\therefore \frac{1}{X_m} = \sqrt{|Y|^2 - \left(\frac{1}{R_c}\right)^2}$$

Another way to find X_m :

$$Y = |Y| \angle -\theta$$


$$P_{oc} = V_{oc} I_{oc} \cos \theta$$

$$\Rightarrow \theta = \cos^{-1} \left[\frac{P_{oc}}{I_{oc} V_{oc}} \right]$$

\Rightarrow find Y then: $Y = \frac{1}{R_c} + \frac{1}{j X_m}$
 \Rightarrow find X_m .

S/C Test:

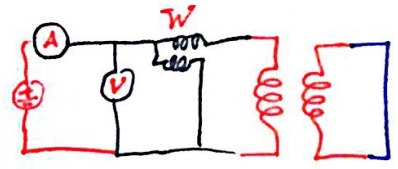- 1] S/c the terminal of the secondary.
- 2] Apply Rated current to the primary and take the Reading of W, V & A (i.e. P_{sc} , V_{sc} & I_{sc})



As a Convention the HV is made primary.

* Analysis:

using equivalent circuit:

since $I_{pl} \gg I_{ext}$ (i.e. core losses are neglected)

$$\therefore I_{pl} = I_p = \text{Ammeter Reading} \equiv I_{sc}$$

$$\therefore Z_{eq} = R_{eq} + j X_{eq}$$

Wattmeter reading $P_{sc} = I_{sc}^2 R_{eq}$

$$\therefore R_{eq} = \frac{P_{sc}}{I_{sc}^2}$$

$$\underline{|Z_{eq}| = \frac{V_{sc}}{I_{sc}} = \sqrt{R_{eq}^2 + X_{eq}^2}}$$

$$\therefore X_{eq} = \sqrt{|Z_{eq}|^2 - R_{eq}^2}$$

$\Rightarrow \underline{OR}: Z_{eq} = |Z_{eq}| \angle \theta \Rightarrow \theta = \cos^{-1} \left[\frac{P_{sc}}{V_{sc} I_{sc}} \right]$

(ex.) 1380 VA, 230/115 V Transformer has been tested to determine its equivalent cct. The results were as follows:

O/C Test

$V = 230 \text{ Volt.}$
 $I = 0.45 \text{ A.}$
 $P = 30 \text{ W.}$


S/C Test

$V = 13.2 \text{ Volt.}$
 $I = 6 \text{ A.}$
 $P = 20.1 \text{ W.}$

* Find the equivalent cct referred to Low voltage side?

Solution:

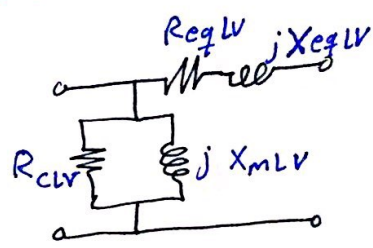* since in o/c test the applied voltage should be the rated one.



∴ In this example the applied voltage is that of HV.
 ∴ In the o/c Test the HV was primary.

* in s/c test, Rated current should be applied.

$I_{rated, HV} = 1380/230 = 6 \text{ A}$
 $I_{rated, LV} = 1380/115 = 12 \text{ A.}$

from the given results it can be deduced that in the s/c test primary was HV.

* O/C test results:

Here R_{CHV} & X_{mHV} can be evaluated as follows:

$P_{oc} = \frac{V_{oc}^2}{R_c} \Rightarrow R_c = \frac{V_{oc}^2}{P_{oc}} = \frac{230^2}{30} \Rightarrow R_{CHV} = 1763.3 \Omega$

$|Y| = \sqrt{\left(\frac{1}{R_c}\right)^2 + \left(\frac{1}{X_m}\right)^2} \Rightarrow |Y| = \frac{I_{oc}}{V_{oc}} = \frac{0.45}{230} \Rightarrow |Y| = 0.001957 \text{ S}$

→ solving: $X_{mHV} = 533.9 \Omega$

continue →

$$\Rightarrow \text{or use: } \gamma = |\gamma| \angle \theta, \theta = \cos^{-1} \left[\frac{P_{os}}{\sqrt{oc} I_{oc}} \right]$$

(33)

* S/C test results:

Here $R_{eq_{HV}}$ & $X_{eq_{HV}}$ are evaluated as follows:

$$Z_{eq} = R_{eq} + j X_{eq}$$

$$P_{sc} = I_{sc}^2 * R_{eq}$$


$$\Rightarrow R_{eq} = \frac{P_{sc}}{I_{sc}^2} = \frac{20.1}{36}$$

$$\Rightarrow R_{eq_{HV}} = 0.558 \Omega$$

$$|Z_{eq}| = \frac{V_{sc}}{I_{sc}} = \sqrt{R_{eq}^2 + X_{eq}^2} = \frac{13.2}{6} = 2.2$$

↳ solving:

$$X_{eq_{HV}} = 2.128 \Omega$$

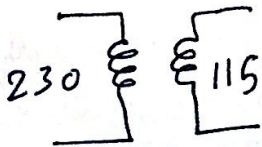

$$N_{HV} = 230, N_{LV} = 115$$

$$a_1 = \frac{230}{115} : 1$$

$$a_1 = 2 : 1$$

OR

$$1 : \frac{115}{230} = 0.5 = a_2$$

$$R_{CLV} = \frac{R_{CHV}}{a_1^2} \quad \& \quad X_{mLV} = \frac{X_{mHV}}{a_1^2}$$

$$R_{eq_{LV}} = \frac{R_{eq_{HV}}}{a_1^2} \quad \& \quad X_{eq_{LV}} = \frac{X_{eq_{HV}}}{a_1^2}$$

or if we use a_2
multiply by a_2^2 .

as a final answer:

$$R_{CLV} = 440.8 \Omega, \quad X_{mLV} = 133.3 \Omega, \quad R_{eq_{LV}} = 0.139 \Omega, \quad X_{eq_{LV}} = 0.532 \Omega$$

* Per Unit (PU) system:

What?! **Definition:** Here the basic quantities V, I, Z & S are not expressed by units of voltage, current, ohm, VA but they are expressed as a Fraction of a Reference or Base value.

$$\text{PU value} = \frac{\text{Actual Value}}{\text{Base OR Reference value.}}$$

PU it is dimensionless & Real +ve value.

⇒ Actual value : could be Complex.

(34)

∴ PV value & Actual value : have the same value of angle.

Why?! Advantages:

1] As will be shown, it simplifies the process of solving system with many transformers.

Ex. R_{eq}, X_{eq}, R_c, X_m have the same value irrespective of the reflection side.

2] The Parameters of generators & transformers (i.e. R, X) have the same range of values.

3] It simplifies the solution of 3-ph system, where $\sqrt{3}$ does not appear.

How?! Procedure:

since there are 4 quantities V, I, Z & Power, Then one may select the Base values for any Two quantities, Then Calculate the Base values for other two quantities.

* Usually, The base values of V & S are selected (i.e. V_b & S_b)

$$\therefore \underline{\underline{I_b}} = \frac{S_b}{V_b} \quad \underline{\underline{Z_b}} = \frac{V_b}{I_b} = \frac{V_b}{S_b/V_b} = \underline{\underline{\frac{V_b^2}{S_b}}}$$


* Usually, Selected base values are the Rating of a component in the system.

*** Note:**

since a transformer has the same S for its HV & LV sides, Then S_b does not change one move from one side to other.
 However, the voltage changes when one move from one side to other side.

This change should be according to voltage or Turns Ratio.

*** Illustration:**

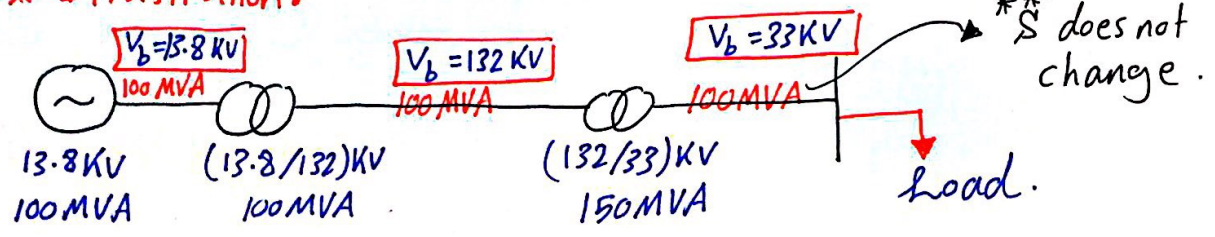

let $S_b = 100 \text{ MVA}$.
 $V_b = 13.8 \text{ kV}$.

*** $Z_{eq}(\text{pu})$ For Transformer:**

⇒ reflect to a-side:

$R_{eq} = r_1 + a^2 r_2$

$X_{eq} = x_1 + a^2 x_2$


* let Base voltages be V_1, V_2 .

where $\frac{V_1}{V_2} = a$

* let Base Power = S .

∴ $Z_b = \frac{V_1^2}{S}$

$Z_{2b} = \frac{V_2^2}{S}$

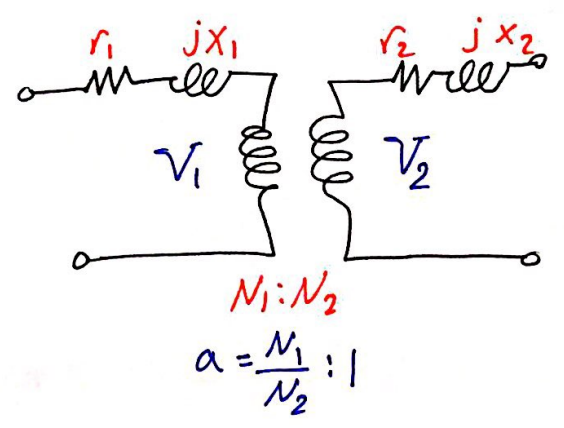

∴ $R_{eq}(\text{pu}) = \frac{R_{eq1}}{Z_b} = \frac{R_{eq1} S}{V_1^2}$



$$\therefore R_{eq1}(PU) = (r_1 + a^2 r_2) \frac{S}{V_1^2} \text{ --- (1)}$$

$$X_{eq1}(PU) = (X_1 + a^2 X_2) \frac{S}{V_1^2} \text{ --- (2)}$$

* Reflect to (1)-side :

$$R_{eq2} = \frac{r_1}{a^2} + r_2$$

$$X_{eq2} = \frac{X_1}{a^2} + X_2$$

$$\Rightarrow \therefore R_{eq2}(PU) = \frac{R_{eq2}}{Z_{b2}}$$

$$R_{eq2}(PU) = \left(\frac{r_1}{a^2} + r_2 \right) \frac{S}{V_2^2} \text{ --- (3)}$$

since $\frac{V_1}{V_2} = a, \therefore V_2 = \frac{V_1}{a}$ --- (4)

\Rightarrow Substitute (4) into (3):

$$R_{eq2}(PU) = \left(\frac{r_1}{a^2} + r_2 \right) \frac{S a^2}{V_1^2}$$

$$\therefore R_{eq2}(PU) = (r_1 + a^2 r_2) \frac{S}{V_1^2} \text{ --- (5)}$$

* similarly :

$$X_{eq2}(PU) = (X_1 + a^2 X_2) \frac{S}{V_1^2} \text{ --- (6)}$$

**** Conclusion :**

By Comparing (1) with (5) $\Rightarrow R_{eq1}(PU) = R_{eq2}(PU)$

By Comparing (2) with (6) $\Rightarrow X_{eq1}(PU) = X_{eq2}(PU)$

$\therefore R_{eq}(PU)$ & $X_{eq}(PU)$ are the same irrespective of the side reflection.

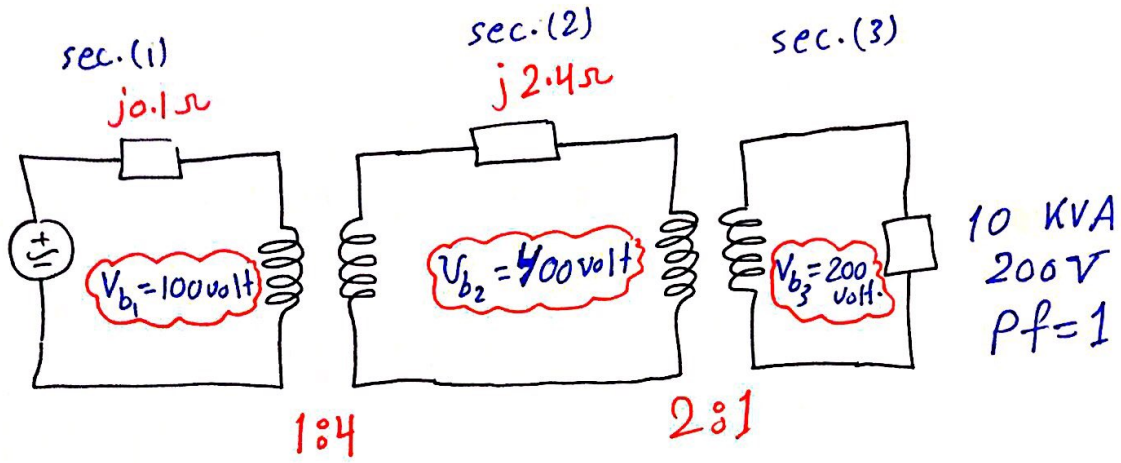


Figure (1).

(ex.) Find the PU equivalent cct of the cct shown in figure (1). Take the rating of the load as Base values: $\therefore V_b = 200 \text{ Volt.}$
 $S_b = 10 \text{ KVA.}$

$\Rightarrow S_b = 10 \text{ KVA}$ for all sections.

Next, Calculate Z_b for each section $Z_b = V_b^2 / S_b$

$$Z_{b1} = \frac{(100)^2}{10 * 10^3}$$

$$Z_{b2} = \frac{(400)^2}{10 * 10^3}$$

$$Z_{b3} = \frac{(200)^2}{10 * 10^3}$$

\Rightarrow

$$\begin{aligned} Z_{b1} &= 1 \Omega \\ Z_{b2} &= 16 \Omega \\ Z_{b3} &= 4 \Omega \end{aligned}$$


Now the PU values:

$$j0.1 \Omega \Rightarrow \frac{j0.1}{1} = \boxed{j0.1 \text{ PU.}}$$

$$j2.4 \Omega \Rightarrow \frac{j2.4}{16} = \boxed{j0.15 \text{ PU.}}$$

$$Z_L = \frac{V^2}{S} = 4 \Omega \quad (\underline{Z_{b3} = Z_L}) \Rightarrow \boxed{Z_{L(PU)} = 1 \text{ PU}}$$

* PU equ. cct:

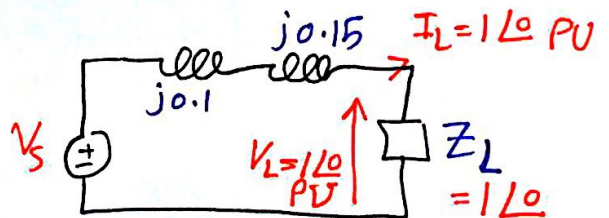

why!?

Because its rating were selected as Base value. \Rightarrow

⇒ for I_L :

$$I_L = \frac{10^4}{200} \angle 0^\circ \text{ A} \Rightarrow I_{Lb} = \frac{10^4}{200}$$

$$I_L(\text{PU}) = \frac{I_L}{I_{Lb}} = \boxed{1 \angle 0}$$

for V_s :

$$V_s(\text{PU}) = 1 \angle 0 (j0.1 + j0.15) + 1 \angle 0$$

$$\Rightarrow \boxed{V_s(\text{PU}) = 1.0308 \angle 0.24^\circ}$$

Comment:

Given an impedance, say Z if the base value is


$$Z_{b_{\text{old}}} = \frac{V_{\text{old}}^2}{S_{\text{old}}} \therefore Z(\text{PU}) = \frac{Z}{Z_{b_{\text{old}}}} = \frac{Z S_{\text{old}}}{V_{\text{old}}^2} \dots \boxed{1}$$

If the base value of Z is changed, say $Z_{b_{\text{new}}} = \frac{V_{\text{new}}^2}{S_{\text{new}}}$

$$\Rightarrow Z_{\text{new}}(\text{PU}) = \frac{Z S_{\text{new}}}{V_{\text{new}}^2} \dots \boxed{2}$$

$$\Rightarrow \frac{\boxed{2}}{\boxed{1}} \Rightarrow \frac{Z_{\text{new}}(\text{PU})}{Z_{\text{old}}(\text{PU})} = \frac{S_{\text{new}}}{S_{\text{old}}} * \frac{(V_{\text{old}})^2}{(V_{\text{new}})^2}$$
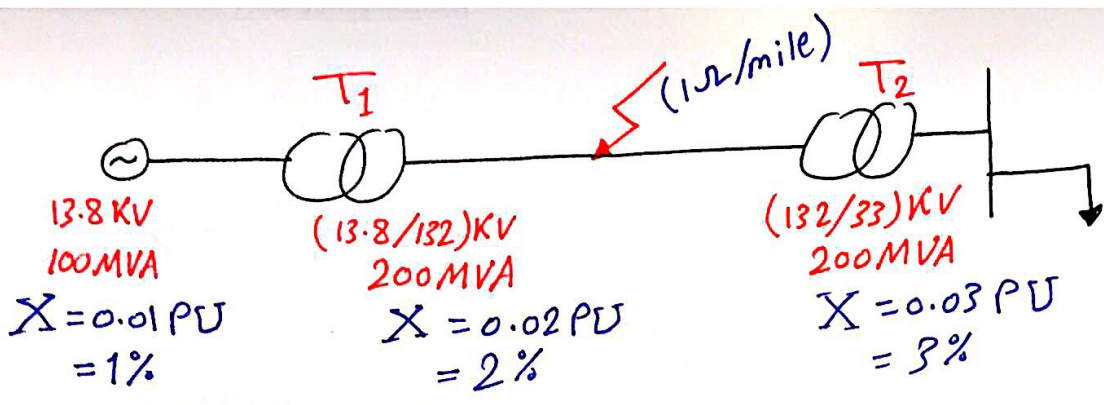
$$\therefore \boxed{Z_{\text{new}}(\text{PU}) = Z_{\text{old}}(\text{PU}) * \left(\frac{V_{\text{old}}}{V_{\text{new}}}\right)^2 * \left(\frac{S_{\text{new}}}{S_{\text{old}}}\right)}$$



for example: let the base value be:

$V_b = 13.8 \text{ KV}$ & $S_b = 100 \text{ MVA}$.


for T_1 : $X_{\text{new}} = X_{\text{old}} * \left(\frac{V_{\text{old}}}{V_{\text{new}}}\right)^2 * \left(\frac{S_{\text{new}}}{S_{\text{old}}}\right)$
 $= 0.02 (1)^2 * \left(\frac{100}{200}\right) \Rightarrow X_{\text{new}} = 0.01$

end of first material.

* Voltage Regulation:

This is a measure to indicate the amount of voltage drop at the load due to the equivalent impedance of the Transformer.

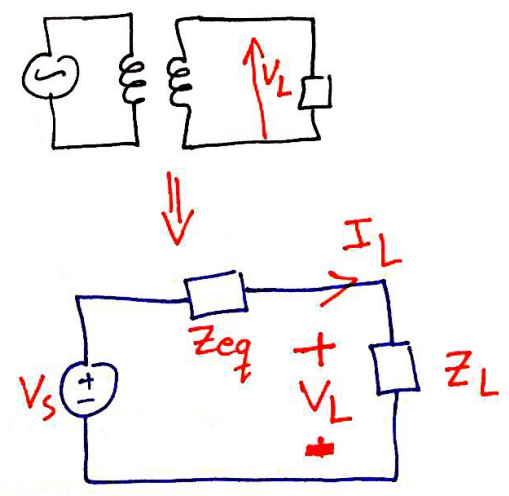**
 $\Rightarrow V_L = V_s - I_L Z_{eq}$
 $= V_s - I_L (R_{eq} + j X_{eq})$



* Voltage Regulation: ↗ magnitude.

$$V_R \% \triangleq \frac{|V_L(NL)| - |V_L(FL)|}{|V_L(FL)|} * 100\%$$

⇒ $V_L(NL)$ means $I_L = 0$

$$\therefore V_L(NL) = V_s$$

* Sometimes V_L is called V_R .
↳ Receiving.

* Objective:

Is to see the magnitude of V_R for various loading conditions (i.e. Inductive, Resistive, Capacitive)


By keeping $|V_L|$ & $|I_L|$ constants.

The PF angle is changed in order to find required E_s .

* Procedure:

By using the concept of phasor diagram.
taking V_s as Reference.

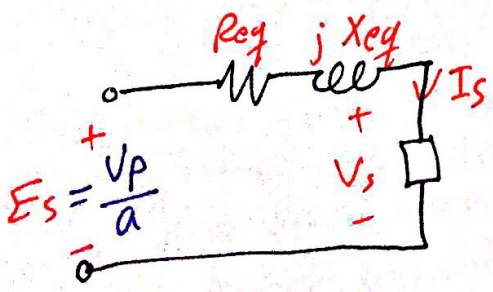* Voltage regulation: Here usually the equivalent ckt Reflected to secondary is used.




* Note: $V_s(NL) = E_s = \frac{V_p}{a}$

$$a = \frac{N_p}{N_s}$$

$$E_s = I_s (R_{eq} + jX_{eq}) + V_s$$


↳ Z_{eq} .

* Inductive:

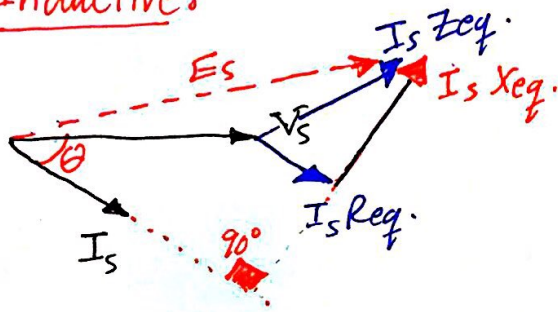


$\therefore |E_s| > |V_s|$
 so we can reach that:
 V_R is +ve.

* Resistive:

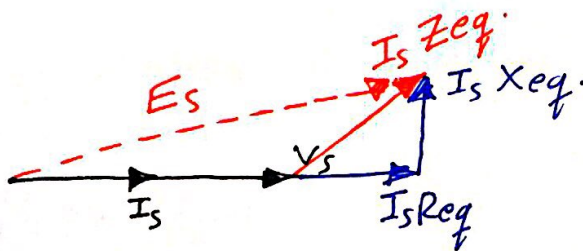

$|E_s| > |V_s| \therefore \underline{V_R}$ is +ve.
But:
 $|E_s|_{\text{resistive}} < |E_s|_{\text{inductive}}$

* Capacitive:

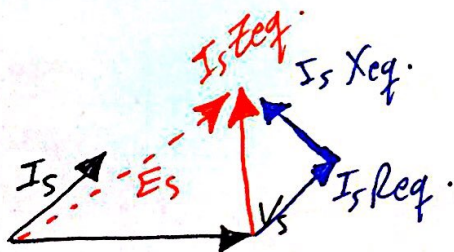

$|E_s| < |V_s|$
 $\therefore \underline{V_R}$ is -ve.

* Definition:

\Rightarrow Ferranti Effect:

it is the increase in voltage occurring at the receiving end of along Transmission Line above the voltage at the sending end and it is more pronounced as how much the longer the line & the higher the voltage applied, also more pronounced in underground cables.

ex. A 10 KVA, 60 Hz, (4800/240)V transformer is tested by CONVENTIONAL procedure with the following results:

O/C : 240 V, 1.5 A, 60 W.

S/C : 180 V, rated A, 180 W.

Find the VR of this step-down Transformer, at unity pf at full load? (full load → it is the quantity of current = $\frac{\text{apparent power}}{\text{voltage}}$)

since step-down ⇒ secondary is LV.

By using calculations it can be found: $R_{eq_{LV}} = 0.104 \Omega$

$X_{eq_{LV}} = 0.19 \Omega$


∴ $V_s = 240 \angle 0^\circ$ volt.

$I_s = \frac{10 \times 10^3}{240} \angle 0^\circ$

∴ $E_s = I_s(0.104 + j0.19) + 240 \angle 0$


⇒ $E_s = 244.17 + j7.92$ volt. ⇒ $|E_s| = 244.3$ volt.

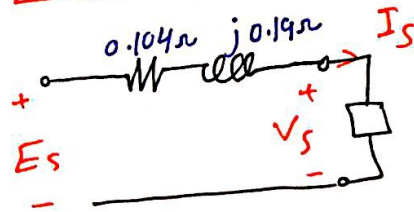∴ $VR = \frac{244.3 - 240}{240} * 100\% \Rightarrow VR = 1.8\%$



* Efficiency: (η)

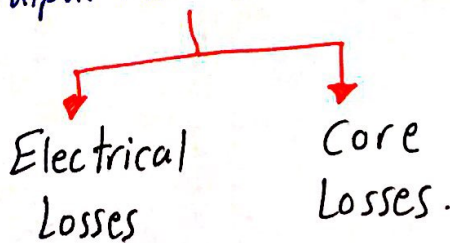$\eta \triangleq \frac{\text{output}}{\text{input}} = \frac{\text{output}}{\text{output} + \text{Losses}}$




continue. →

* for the last (ex):

2) Evaluate η of the transformer at full load
 & Pf = 0.9 lagging ?

$$\begin{aligned} \text{output} &= |V_s| |I_s| \cos \theta \\ &= 240 * \left(\frac{10 * 10^3}{240} \right) * 0.9 \\ &= \boxed{9 \text{ kW}} \end{aligned}$$

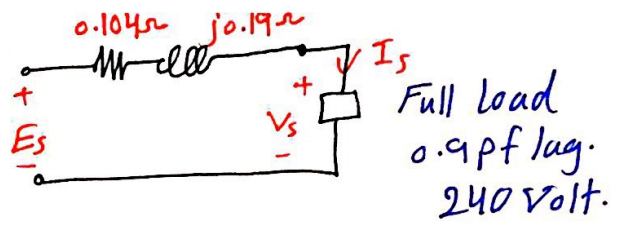

Losses: Electrical = $P_{sc} = 180 \text{ W}$. & Core = $P_{oc} = 60 \text{ W}$.
 ↓
 This happen just at full load.

∴ By substitution: $\eta = 97.4\%$


* Auto transformer:

* This is basically used when the voltage ratio is around 1.

* Construction:

It consists of 2 coils, electrically connected, with Polarity aiding.

connect +ve with -ve.

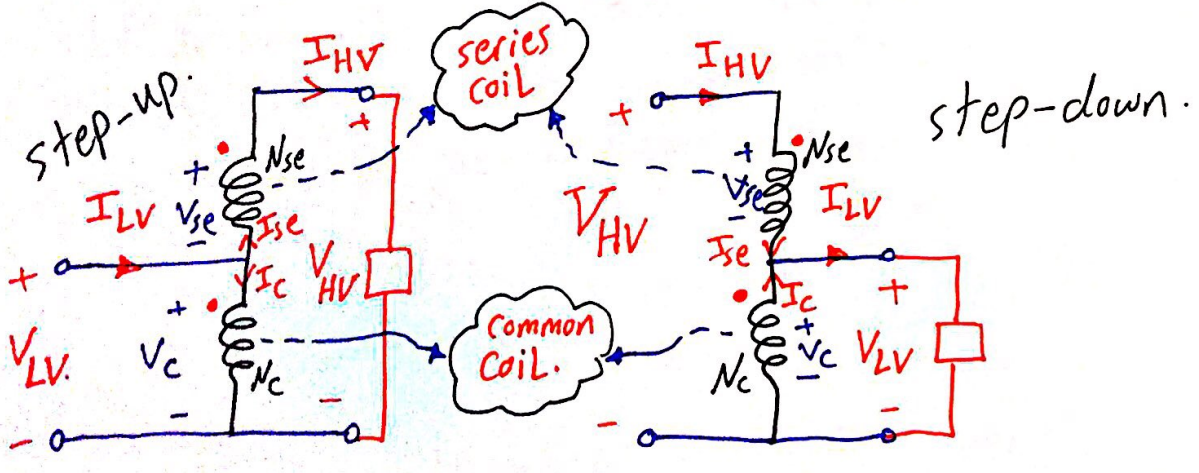

⇒ Objective: is to find voltage & current relationships at transformer terminals.

* Characteristics:

$$I_c N_c = I_{se} N_{se} \dots \dots \dots [1]$$

$$\frac{V_c}{V_{se}} = \frac{N_c}{N_{se}} \dots \dots \dots [2]$$

⇒ Consider Step-up Transformer:

$$V_{HV} = V_{se} + V_c \dots \dots \dots [3]$$

$$\Rightarrow V_{HV} = V_{se} + V_{LV} \Rightarrow \text{from [2]: } V_{se} = V_c \frac{N_{se}}{N_c}$$

$$\therefore V_{HV} = V_c \frac{N_{se}}{N_c} + V_{LV} = V_{LV} \left(\frac{N_{se} + N_c}{N_c} \right)$$

∴ $\frac{V_{HV}}{V_{LV}} = \frac{N_{se} + N_c}{N_c}$ voltage relationship.

Now for the current:


$$I_{LV} = I_c + I_{se} = I_c + I_{HV} \Rightarrow \text{from [1]: } I_{LV} = I_{se} \frac{N_{se}}{N_c} + I_{HV}$$

∴ $I_{LV} = I_{HV} \left(\frac{N_{se} + N_c}{N_c} \right)$ ∴ $\frac{I_{LV}}{I_{HV}} = \frac{N_{se} + N_c}{N_c}$

current relationship.

* Apparent Power Advantage:

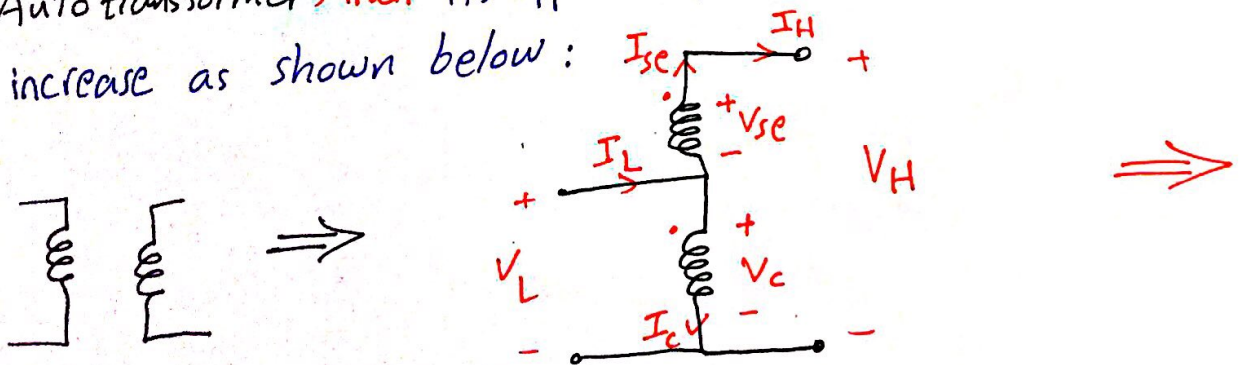if the conventional transformer converted to Auto transformer, Then its apparent power will increase as shown below:



$\therefore S_i = V_L I_L \dots \dots \boxed{1}$ $S_i \equiv$ input apparent power.
 $S_o = V_H I_H \dots \dots \boxed{2}$

It was shown before that:

$\frac{V_H}{V_L} = \frac{I_L}{I_H} = \frac{N_c + N_{se}}{N_c} \dots \dots \boxed{3}$

\Rightarrow find the relationship between S_i & S_o :

\therefore By substituting $\boxed{3}$ into $\boxed{2}$:

$S_o = \left(V_L \frac{N_c + N_{se}}{N_c} \right) * \left(I_L \frac{N_c}{N_c + N_{se}} \right) = V_L I_L = S_i$

$\therefore S_o = S_i = S_{io}$

* However the apparent power of transformer winding:

$S_{sw} = V_c I_c = V_L (I_L - I_H) = V_L \left(I_L - I_L \frac{N_c}{N_c + N_{se}} \right)$
 \downarrow
 $V_c = V_L$
 $= \left(V_L I_L \right) \left(\frac{N_{se}}{N_c + N_{se}} \right)$
 \downarrow
 S_{io}

$\Rightarrow \frac{S_{io}}{S_{sw}} = \frac{N_c + N_{se}}{N_{se}}$

\Rightarrow Apparent Power Advantage.


* it can be shown that if a conv. Trans. converted to Auto trans.

Then: its $Z_{eq}(PU)$ will be reduced by a factor = $\frac{N_c + N_{se}}{N_{se}}$

in Auto transformer
divide the $Z_{eq}(PU)$
by this factor.

ex. A 5000 VA, (480/120)V. conventional Transformer is to be used to supply power from 600V source to 120V load. Consider the transformer to be ideal, and assume that all insulation can handle 600V.

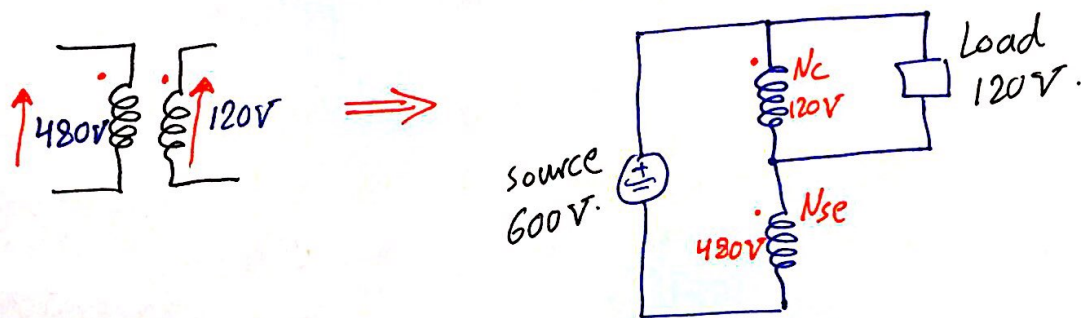1) Sketch the transformer connections that will do the required job?



2) Find the KVA rating of the produced AutoTransformer?

we have: $N_c \propto V_c, N_{se} = V_{se}$
 $\Rightarrow S_w = 5000 \text{ VA.}$

$\therefore S_{io} = S_w \left(\frac{N_c + N_{se}}{N_{se}} \right) \Rightarrow S_{io} = 6250 \text{ VA}$

3) Find the max. primary & secondary currents of the Autotrans.?

$I_{p_{max}} = \frac{6250}{600} \quad \& \quad I_{s_{max}} = \frac{6250}{120} \Rightarrow$

$I_{p_{max}} = 10.4 \text{ Amp.}$
 $I_{s_{max}} = 52.1 \text{ Amp.}$

4) If $Z_{pu}(\text{conv.}) = 0.01 + j0.08$ find $Z_{pu}(\text{Auto})$?

$\therefore Z_{pu}(\text{Auto}) = (0.01 + j0.08) / \left(\frac{6250}{5000} \right) \rightarrow 1.25$


$\Rightarrow Z_{pu}(\text{Auto}) = 0.008 + j0.064$

*Note: See the Advantages & Disadvantages in the Book.

* Current Inrush:

This is a transient condition which may occur when a transformer is energized (i.e. primary connected to source).

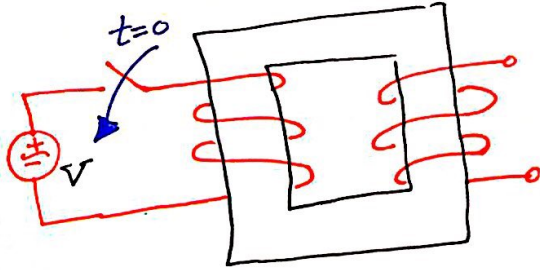* Let $V = V_m \sin(\omega t + \theta)$
 $\theta \equiv$ phase angle of applied voltage.



* Let $\theta = 0^\circ \therefore V = V_m \sin \omega t$

\Rightarrow find the value of ϕ over a half-cycle:

$$\omega = 2\pi f = \frac{2\pi}{T} \therefore T = \frac{2\pi}{\omega} \Rightarrow \text{half-cycle} = \frac{\pi}{\omega}$$


$$\Rightarrow \phi = \frac{1}{N} \int_0^{\pi/\omega} V dt = \frac{1}{N} \int_0^{\pi/\omega} V_m \sin \omega t dt$$
$$= \frac{-V_m}{\omega N} [\cos \omega t]_0^{\pi/\omega} \Rightarrow \phi = 2 \left(\frac{V_m}{\omega N} \right) \phi_m$$

$\phi_m \equiv$ Normal max. value of flux.

\therefore in this case $\phi = 2\phi_m$

\therefore Under this condition, the primary will draw a very high current $\gg I_{rated}$.

This will occur if $V=0$ at $t=0$.

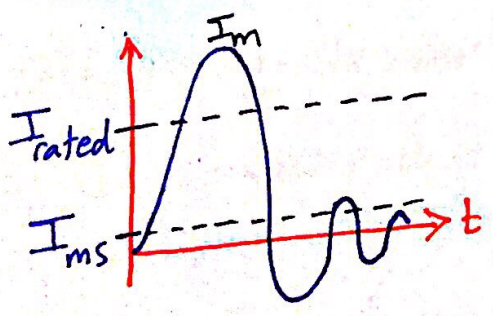

* Three-Phase Transformer :


since electrical energy is generated, transmitted and distributed in 3-ph AC voltage, then 3-ph transformers are required for step-up & step-down.

* Note: see the advantages & disadvantages of 3-ph supply over 3-ph & single phase

* Construction :


It can be one of two:

1] Using 3 1-ph Transformers.

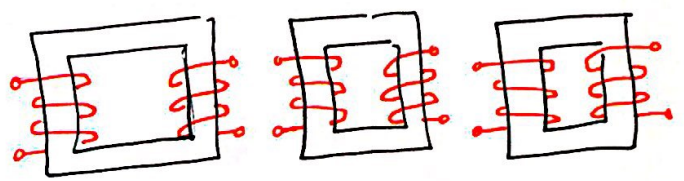

This called: "3-ph Transformer Bank."

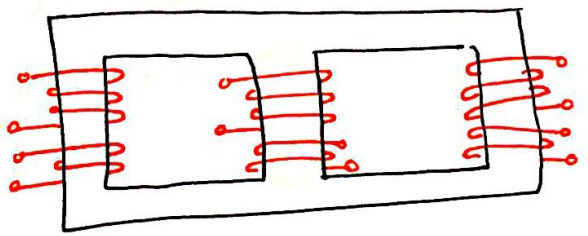2] A single core with 3 pairs of windings.



* The only advantage of first type on second type: each unit in the bank could be replaced individually in the event of trouble. (saving money).

* Note: What is the advantages & disadvantages of these types?

* From Connection Point of view there are 4-types:

- 1] Y-Y
- 2] Y-Δ
- 3] Δ-Y
- 4] Δ-Δ

* Objective:

- 1] Find voltage ratio.
- 2] phase angle shift.
- 3] Advantages & Disadvantages of each type.

* The advantage of using single 3-ph is:

Lighter, smaller, cheaper and slightly more efficient.

* Advantages of Autotransformer:

1] Gives more apparent power than the conventional as shown in the relation $\frac{S_{io}}{S_w} = \frac{N_{se} + N_c}{N_{se}}$

2] It is very advantageous to build transformers between two nearly equal voltages as auto transformers.

* Disadvantages of Autotransformer:

1] There is a direct physical connection between the primary & the secondary circuits so the electrical isolation of the two sides is lost.

2] The effective PV impedance for Autotransformer is smaller by a factor equal to the reciprocal of the power advantage of auto transformer connection ($\frac{N_{se} + N_c}{N_{se}}$).

* Introduction:

HV is represented by Capital Letters (e.g. A, B, C, Y, D).

LV is represented by small letters (e.g. a, b, c, y, d)

Y-Y connection:


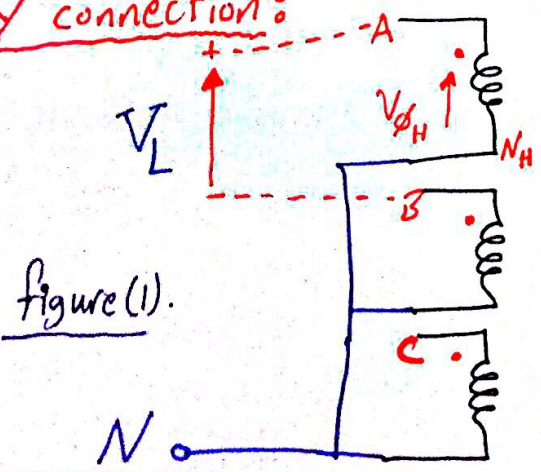


Figure (1).

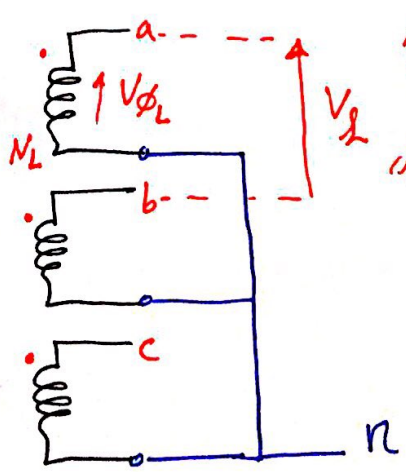

This called: "Wiring" or "Connection" Diagram

$V_L, V_L \equiv$ Line voltage of HV & LV sides.



$V_{\phi_H}, V_{\phi_L} \equiv$ phase voltage of HV & LV sides.

$N_H, N_L \equiv$ Number of Turns of HV & LV sides.

$$\frac{|V_L|}{|V_L|} = \frac{\sqrt{3} |V_{\phi_H}|}{\sqrt{3} |V_{\phi_L}|} = \frac{|V_{\phi_H}|}{|V_{\phi_L}|} = a$$

$a \equiv$ Ratio of Phase voltages.

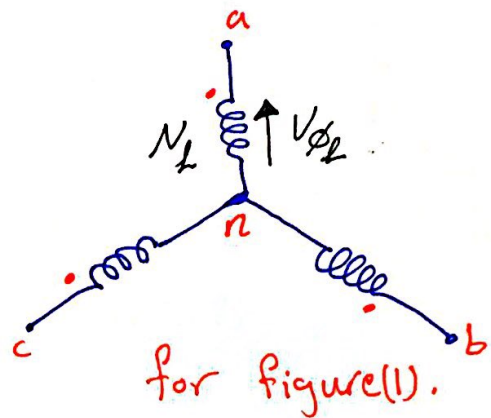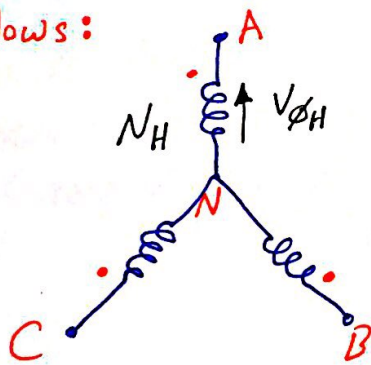* **Wiring Diagram** is represented by a symbol where the windings of each phase are drawn parallel to each other as follows:




⇒⇒ Connection Designation:

- 1] First write the letter symbol of HV.
- 2] Next write the letter symbol of LV.
- 3] Indicate the phase of the low voltage with respect to High voltage.
 - ↳ By using the clock arms:

* a) Hour arm always pointing at the 12:00 position to represent HV.

b) Minutes arm is used to represent LV.

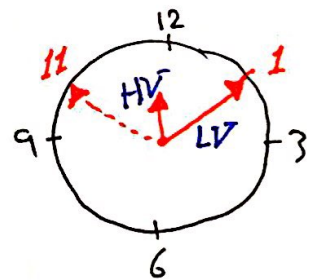

(ex.) Find the Connection Designation for figure (1) in page (49)?

(51)

$YNyn0$ → zero since No shift between the voltages.
 ↙ we write it since the neutral is accessible.

** In figure (2) just reverse the connection of the low voltage side

In this case:

there is a phase shift of 180° between HV & LV sides. (i.e. Between corresponding voltages).


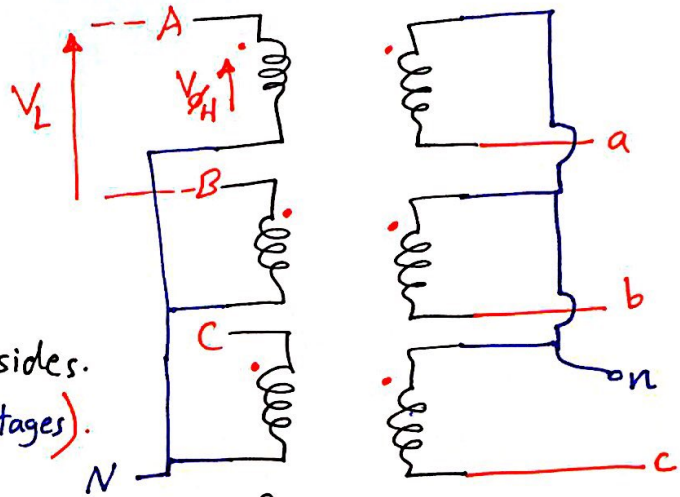


Figure (2).

for figure (2):

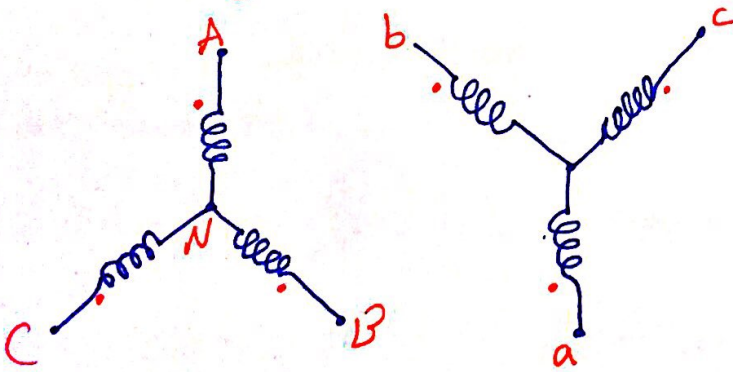


⇒⇒ Connection Designation:


$YNyn6$

↙ six since the phase shift is 180° .


* By reversing the connections:

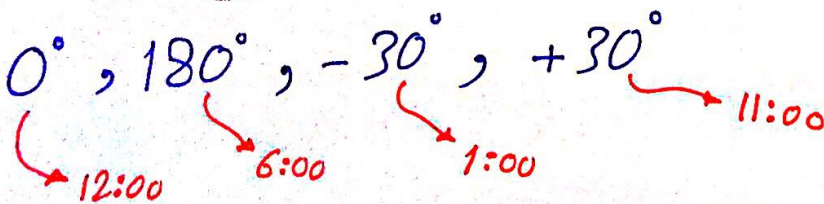There are only 4 possible cases for the phase shifts:



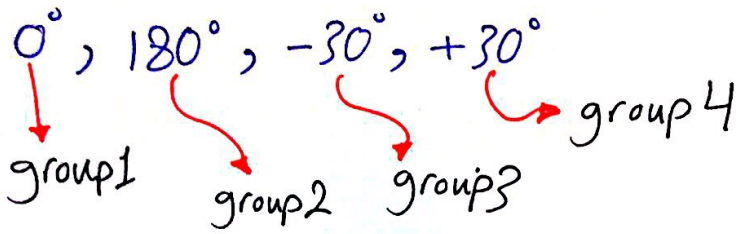

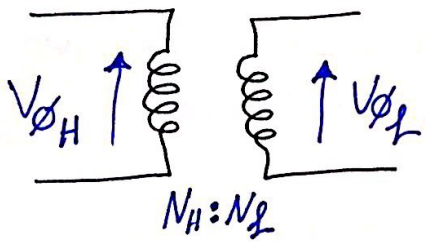* The Per-Phase cct of the Y-Y connection will be as follows:



$$a = \frac{V_{\phi_H}}{V_{\phi_L}} = \frac{N_H}{N_L}$$

Y-Δ Connection:


$$\frac{|V_L|}{|V_2|} = \frac{\sqrt{3}|V_{\phi_H}|}{|V_{\phi_L}|} = \sqrt{3} \frac{|V_{\phi_H}|}{|V_{\phi_L}|} = \sqrt{3} a$$

* By similar approach, it can be found for:

$$\Delta-Y: \frac{|V_L|}{|V_2|} = \frac{a}{\sqrt{3}}$$

$$\Delta-\Delta: \frac{|V_L|}{|V_2|} = a$$

figure (3).

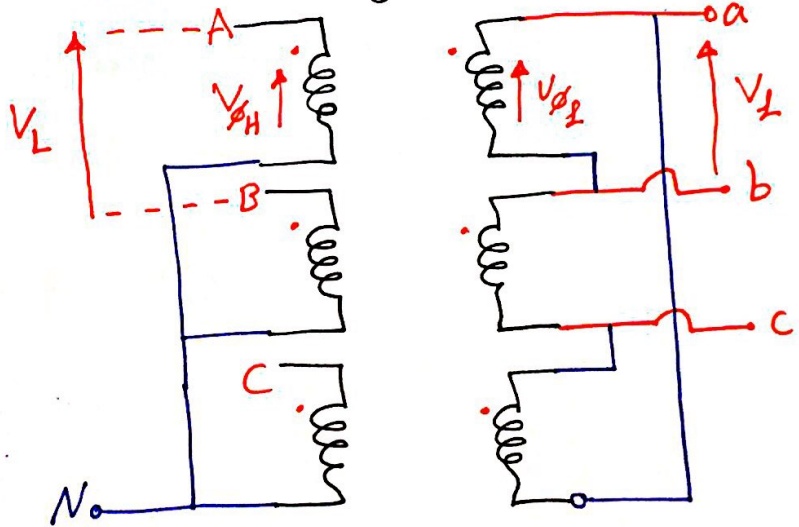

* * if he ask to derive a relation for any type: DRAW the figure and put the variables on it then derive the needed relation.

*in Y-Δ connection, there is a phase shift of 30° between corresponding voltages.

⇒ As a Convention:

* The terminal markings are made in such way that HV leads LV by 30° in the case of +ve phase sequence.

* The terminal markings are made in such way that HV lags LV by 30° in the case of -ve phase sequence.

** Illustration: consider figure(?).

⇒ assume +ve phase sequence.


Let $\angle V_{AN} = \text{Zero}$. $\therefore \angle V_{AB} = +30^\circ$

But V_{AN} & V_{ab} are in phase $\Rightarrow \angle V_{ab} = \angle V_{AN} = 0^\circ$

$\therefore V_{AB}$ (ie HV) leads V_{ab} (ie LV) by 30° .

* Find the Per-phase cct for Y-Δ:

discussed
in the
Next page.


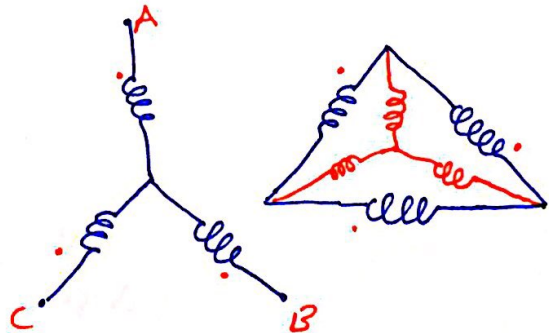


* Effective Turns Ratio:

consider a Y-Δ Transformer:


$$\frac{V_{\phi L}}{V_{LL}} = \frac{N_H}{N_L} \dots\dots [1]$$
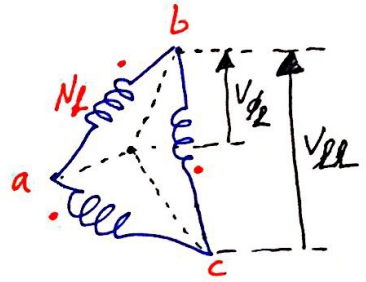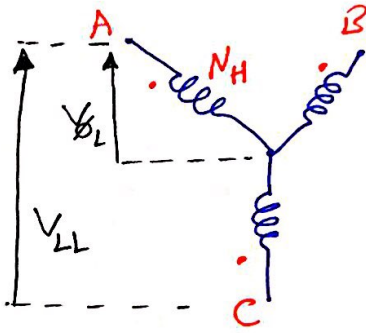
$$\frac{V_{\phi L}}{\sqrt{3} V_{\phi_2}} = \frac{N_H}{N_L} \dots\dots [2]$$



$$\therefore \frac{V_{\phi L}}{V_{\phi_2}} = \frac{N_H}{N_L/\sqrt{3}} \dots\dots [3]$$

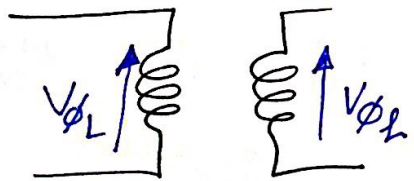$\therefore [3]$ can be used to find per phase equivalent cct:



$N_H : N_L/\sqrt{3}$

$$a_{eff} \left(\frac{N_H}{N_L/\sqrt{3}} \right) : 1$$

$$\therefore a_{eff} = \frac{N_H}{N_L/\sqrt{3}}$$

Effective Turns Ratio.

$\Rightarrow [1]$ can be written as follows:

$$\frac{V_{LL}/\sqrt{3}}{V_{LL}} = \frac{N_H}{N_L} \Rightarrow \therefore \frac{V_{LL}}{V_{LL}} = \frac{N_H}{N_L/\sqrt{3}} \equiv a_{eff} \equiv \text{Ratio of Line Voltage.}$$

** Conclusion:



Irrespective of the type of 3-ph Transformer windings

$$a_{eff} \triangleq \text{Ratio of Line Voltages.}$$

ex. A (132/33) KV Transformer is D-Y connected.
 a balanced Y-connected resistive Load of 15Ω
 is connected to LV side.

Find how this load is seen from HV side ?

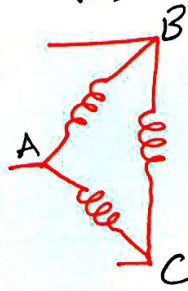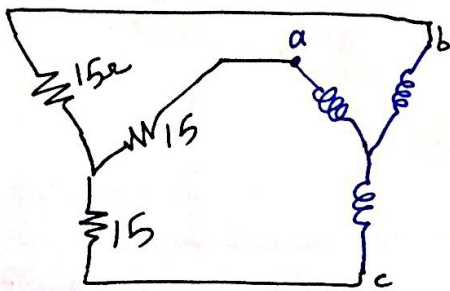from connection designation: $132/33$
 \downarrow $\rightarrow y$
 D (Δ) (Y)



\therefore load seen from HV side:

$$15 * a_{eff}^2 = 15 * \left(\frac{132}{33}\right)^2 = \underline{\underline{240\Omega}}$$

(33 : 132) KV

$$1 : \frac{132}{33} = a_{eff}$$

*Note: if the load was (Δ) with 45Ω :

first we convert $\Delta \rightarrow Y \Rightarrow \frac{45}{3} = 15\Omega$

Then load seen from HV side: $= 15 * \left(\frac{132}{33}\right)^2 = \underline{\underline{240\Omega}}$

\Rightarrow We convert from $\Delta \rightarrow Y$:


since we deal with single-per-phase circuit.

* Application of O/C & S/C Tests To 3-ph Transformer:

In O/C Rated voltage is applied.
In S/C Rated current is applied.

Conventional Test: \rightarrow O/C LV is primary.
 \rightarrow S/C HV is primary.

O/C Test:

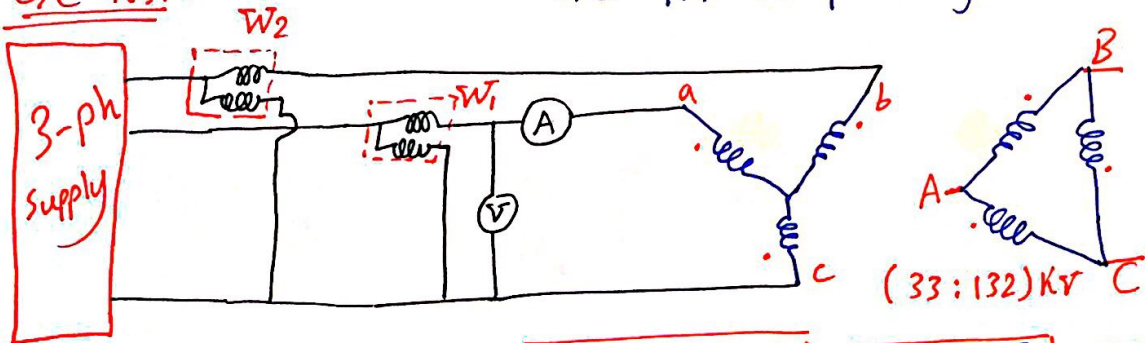

$$P_{3\phi} = W_1 + W_2$$


$$P_{oc} = \frac{W_1 + W_2}{3}$$

$$V_{oc} = \frac{V}{\sqrt{3}}$$

$$I_{oc} = A$$

in this figure: Applied voltage = $V = 33$ K Volt.

S/C Test:

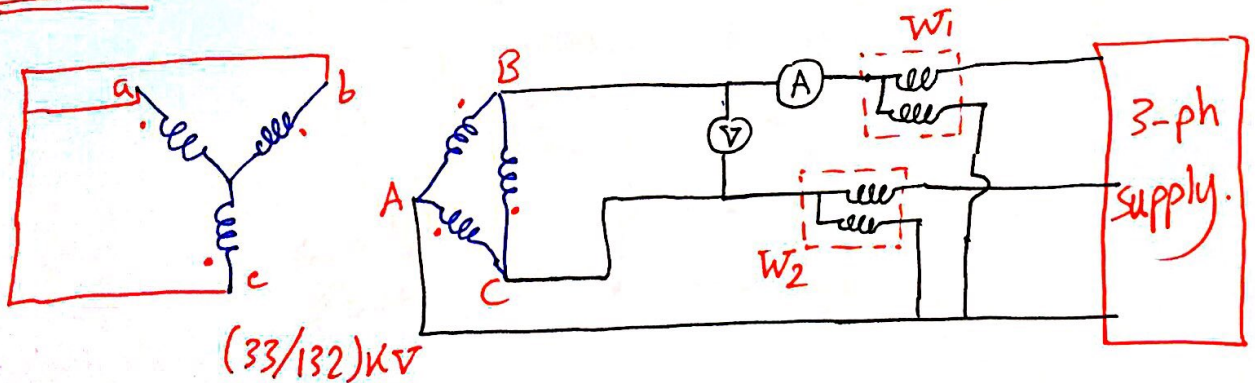

for example: 100KVA, (33/132)KV

$$|S| = \sqrt{3} |V| |I| \Rightarrow 100 * 10^3 = \sqrt{3} * 132 * 10^3 * |I|_{rated}$$

$$I_{sc} = |I|_{rated} = A$$

$$V_{sc} = \frac{V}{\sqrt{3}}$$

$$P_{sc} = \frac{W_1 + W_2}{3}$$

⇒ ∴ Req & Xeq can be calculated as before.

* PU system in 3-ph Transformer:

Let $S_{3\phi} \equiv$ Apparent power of 3-ph (Base).
 $V_{LL} \equiv$ Lin voltage.


∴ For per-phase circuit: $S_{1\phi} = \frac{S_{3\phi}}{3}$, $V_{1\phi} = \frac{V_{LL}}{\sqrt{3}}$

Now for Z_b :

$Z_b = \frac{(V_{1\phi})^2}{S_{1\phi}} = \frac{(V_{LL}/\sqrt{3})^2}{S_{3\phi}/3} \Rightarrow Z_b = \frac{V_{LL}^2}{S_{3\phi}}$

Base Impedance of per-phase circuit.

* Parallel Operation of Transformers:

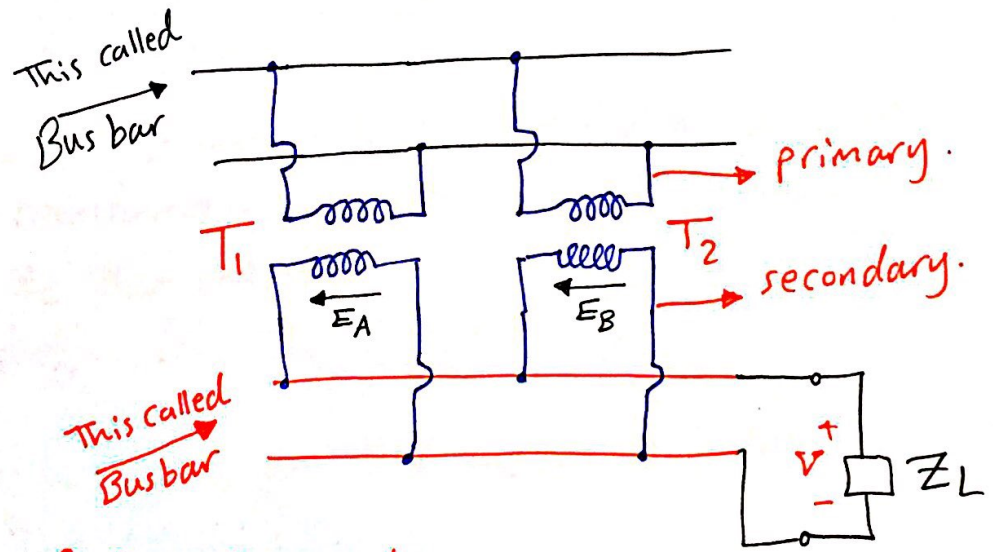


*** ⇒ Condition of Parallel operation:

- 1) Same voltage ratio & turns ratio.
- 2) Same percentage impedance & $\frac{X}{R}$ ratio.
- 3) Identical Position of Tap Changer.
- 4) Same KVA ratings.
- 5) Same vector group.
- 6) same frequency rating.
- 7) same Polarity.
- 8) same phase sequence.

* Equivalent circuit:

For Two-Transformers in parallel.

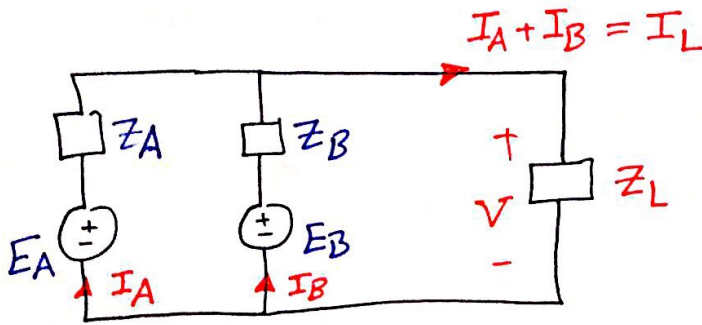

KVL: $E_A = I_A Z_A + V = I_A Z_A + (I_A + I_B) Z_L \dots\dots [1]$

$E_B = I_B Z_B + V = I_B Z_B + (I_A + I_B) Z_L \dots\dots [2]$

\Rightarrow By using [1] & [2] you can find expressions for I_A , I_B & V .

By rearrangement & substitution it can be found that:

$$V = \frac{\frac{E_A}{Z_A} + \frac{E_B}{Z_B}}{\frac{1}{Z_A} + \frac{1}{Z_B} + \frac{1}{Z_L}} \dots\dots [1^*]$$

Advantages of [1*] is that it can be modified for any number of parallel transformers. For example for a 3rd Transformer with E_C & Z_C Then one add to:

The numerator $\frac{E_C}{Z_C}$ & The dominator $\frac{1}{Z_C}$

* when V is found one can find the current in any transformer:

For e.g. $I_A = \frac{E_A - V}{Z_A}$

* For the special case where $E_A = E_B$, Then:

$I_A Z_A = I_B Z_B$ since $\Rightarrow I_L = I_A + I_B$

$\therefore I_A = I_L \left(\frac{Z_B}{Z_A + Z_B} \right)$ $\therefore I_B = I \left(\frac{Z_A}{Z_A + Z_B} \right) \Rightarrow$

$$I_A * V = I * V \left(\frac{Z_B}{Z_A + Z_B} \right), \quad I_B * V = I * V \left(\frac{Z_A}{Z_A + Z_B} \right)$$

apparent power of load.

"sharing of apparent power" between Transformers.

ex.) Two Parallel Transformers have the following Data:

	<u>T_A</u>	<u>T_B</u>
Rated current (A)	200	600
Z _{eq} (pu)	0.02 + j0.05	0.025 + j0.06
No load emf (V)	245	240

Calculate the terminal voltage when they are connected to $Z_L = 0.25 + j0.1 \Omega$?

Solution:

$$Z_A = (0.02 + j0.05) \frac{245}{200} \Rightarrow Z_A = 0.0245 + j0.0613 \Omega$$

$$Z_B = (0.025 + j0.06) \frac{240}{600} \Rightarrow Z_B = 0.01 + j0.024 \Omega$$

By substitution:


using $E_A = 245 \angle 0^\circ$ & $E_B = 240 \angle 0^\circ$
 it can be found: $V = 230 \angle -3^\circ$ volt.

End of CH2.

* * * *

CHAPTER (3):

* Electrical Machines :

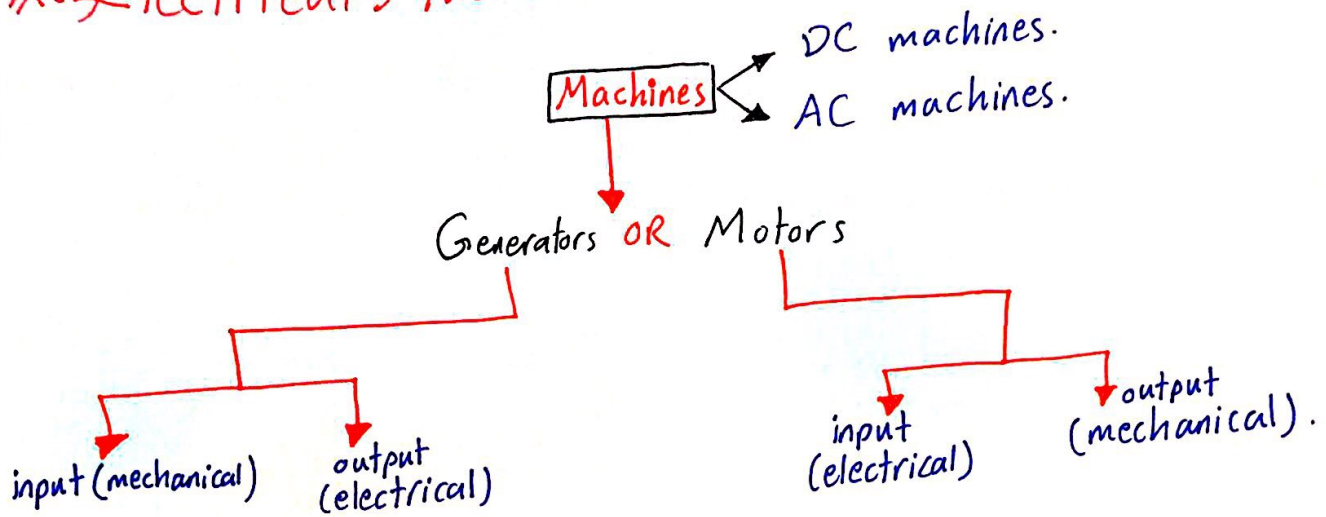



* Fundamental of machines :

in machines there are 3 requirements:

- 1] Magnetic Field. (Electromagnet).
- 2] Conductors.
- 3] Relative motion between 1] & 2].

* Voltage Induced in a single turn coil :

Consider the following structure:

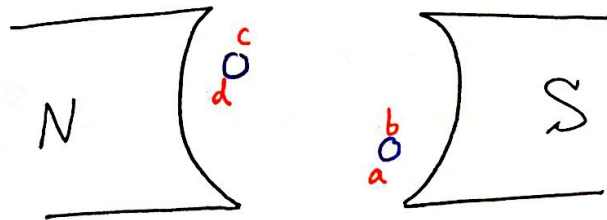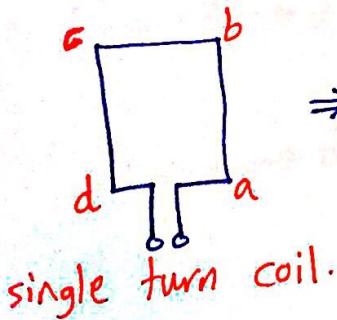

In this case: magnetic field is the "STATOR", and the coil is "Rotating ROTOR".

$$e \triangleq (V \times B) \cdot L$$

$V \equiv$ linear velocity of the conductor.

$e \equiv$ Induced voltage in a conductor

$B \equiv$ flux density.

$L \equiv$ Active length of the conductor


* To find the direction of the induced voltage one may use RHR.

(61)


Fore finger \equiv Direction of magnetic Field.

Thumb \equiv Direction of Applied Force.

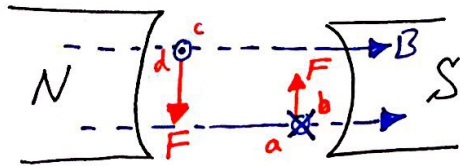Middle finger \equiv Direction of Induced or Generated voltage.




$F \equiv$ applied Force.

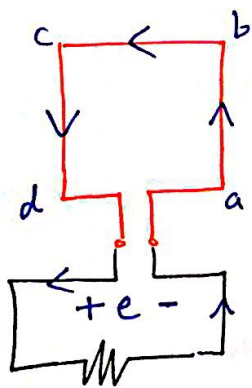


* If a load is connected to the coil, then a current will flow in the same direction of Induced voltage.

* Magnitude of e :
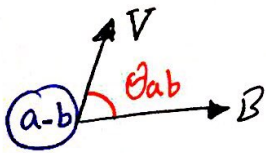
$$\Rightarrow \underline{\underline{e_{ab} = v B l \sin \theta_{ab}}}$$


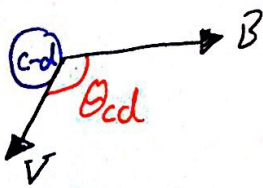
$$\Rightarrow \underline{\underline{e_{cd} = v B l \sin \theta_{cd}}}$$




* However, No induced voltage in bc & da.

$$\theta_{ab} + \theta_{cd} = 180^\circ$$

$$\therefore e = e_{ab} + e_{bc} + e_{cd} + e_{da} = v B l \sin \theta_{ab} + v B l \sin \theta_{cd}$$

But: $\theta_{cd} = 180 - \theta_{ab} \Rightarrow e = v B l (\sin \theta_{ab} + \underbrace{\sin(180 - \theta_{ab})}_{= \sin \theta_{ab}})$

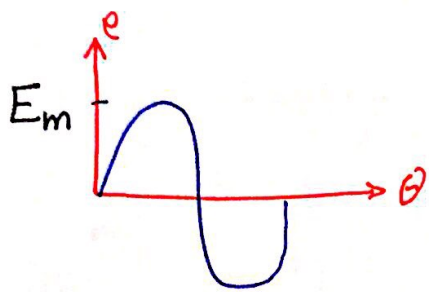
$$\Rightarrow \underline{\underline{e = 2 v B l \sin \theta_{ab}}}$$



$$e = 2vBl \sin \theta_{ab}$$

\downarrow
 E_m

$$E_m = 2vBl$$

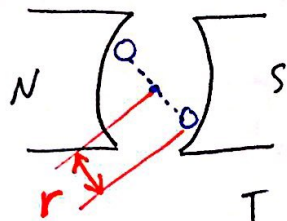


$$\Rightarrow \underline{v = \omega r}$$

$$E_m = 2vBl = 2\omega rBl$$

$$= AB\omega$$


remember: $\phi_m = AB$

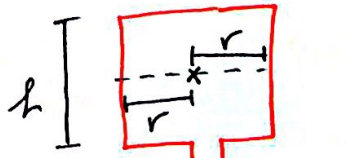

Area = $2rl$
Plane Area of the coil.

$$E_m = \phi_m \omega$$

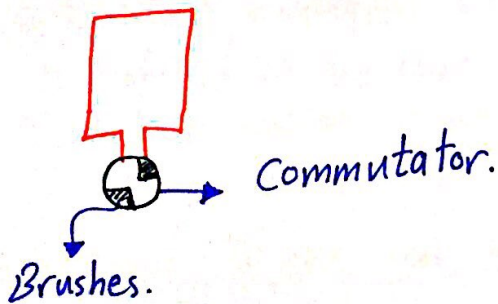this is for single turn coil, if there is more than one turn \Rightarrow multiply by number of turns.




* Comment: The internal AC induced voltage is converted to a DC voltage by means of commutator segments (connected to) is contact with Fixed brushes, This called "Commutation".


\therefore The equivalent circuit will be as follows:

$R_a \equiv$ Internal Resistance of the Rotor windings called "Armature windings".


$I_a \equiv$ Armature Current.

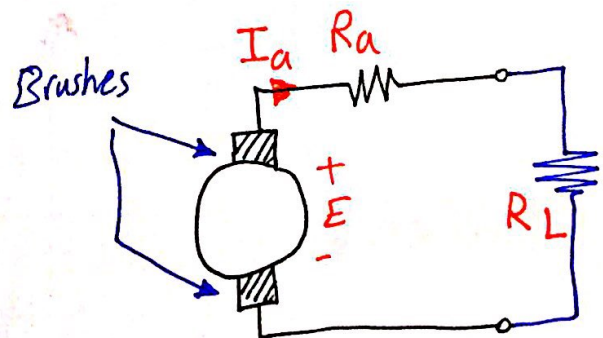

"Armature Circuit."

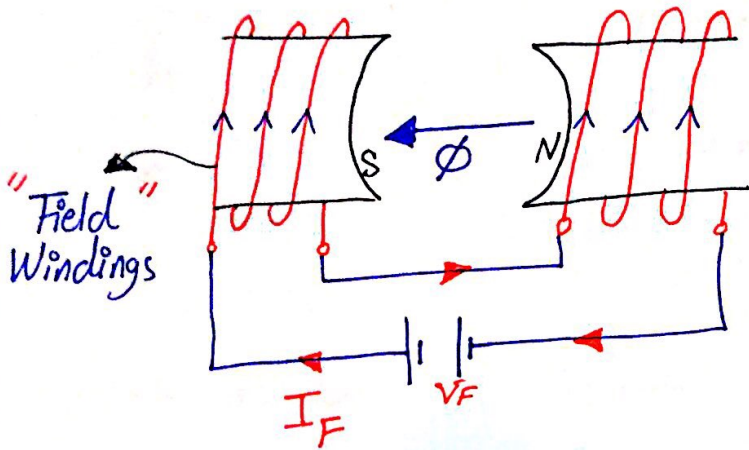


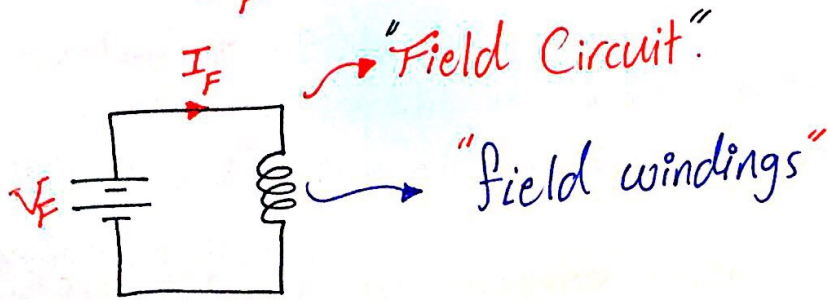
$I_F \equiv$ Field Current.
(i.e. current required to generate magnetic field.)



* **Armature Windings:** They are the windings in which a voltage is induced in the case of generator, OR the windings into which a current is applied in the case of Motor.

* **Induced Torque in a single turn coil:**

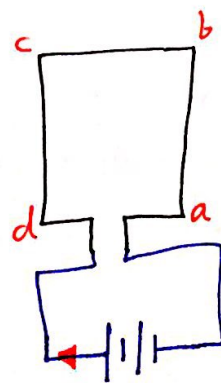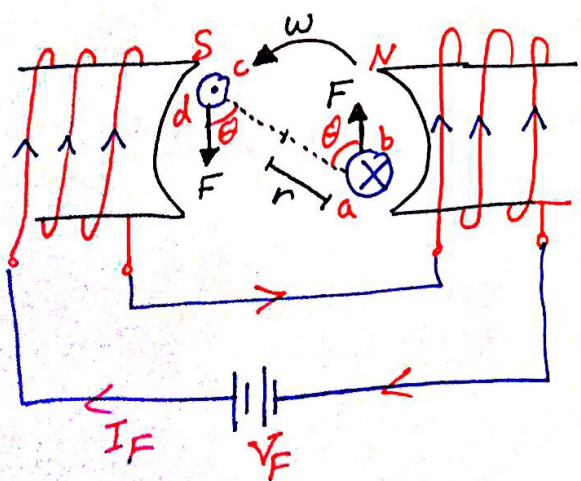
In this case A current is applied to Armature Windings.



I_a Applied Current.

⊙, ⊗ \equiv Direction of Applied Current.

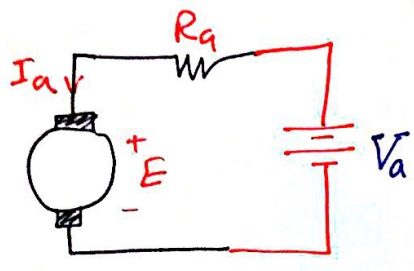$\omega \equiv$ Direction of Developed Angular Speed.



Consequently, Force \$F\$ will be developed on the Armature conductors.

where:

$$F = (B * l) I_a$$

* The direction of \$F\$: By means of LHR.

forefinger \$\equiv\$ Field Direction.

middle finger \$\equiv\$ Direction of Applied Current.

Thumb \$\equiv\$ Direction of generated or developed Force.

* Only Torques are developed on the sides \$ab\$ & \$cd\$.
(i.e No Torques on \$bc\$ & \$da\$).

$$\tau_{ab} = F * r \sin\theta = B I_a l r \sin\theta$$

$$\tau_{cd} = F * r \sin\theta = B I_a l r \sin\theta$$

\$\therefore\$ Developed Torque:

$$\tau = \tau_{ab} + \tau_{cd}$$


$$\therefore \underline{\underline{\tau = 2 B I_a l r \sin\theta}}$$

$$\Rightarrow \boxed{\tau = A B I_a \sin\theta} \dots \dots \square$$

\$\Rightarrow \square\$ can be rewritten in another form:

$$\underline{\underline{\tau = A B_s I_a \sin\theta}}$$

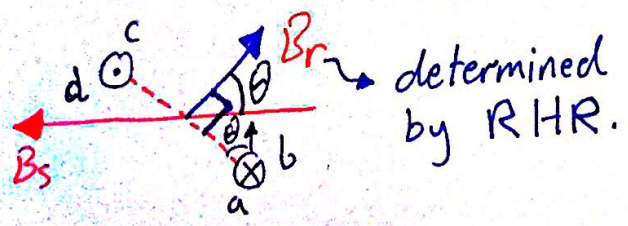\$B_s \equiv\$ This is to indicate the flux density produced by field or stator windings.



\$B_r\$ determined by RHR.



$\Rightarrow NI_a = R \Phi_R = R B_p A_R$ $G \equiv \text{constant.}$

$NI_a = \frac{l}{\mu A_R} B_p A_R \Rightarrow I_a = \left(\frac{l}{N}\right) \cdot \frac{B_p}{\mu}$

$I_a = \frac{G B_p}{\mu} \dots [2]$

* Substitute [2] in [1]:


$\tau = A B_s \frac{G B_p}{\mu} \sin \theta = K B_s B_p \sin \theta$

$\tau = K (B_s \times B_p)$


$K \equiv \text{constant.}$
 ↳ Related to the construction of the machine.

- * In a generator action there is a motor action.
- * In a motor action there is a generator action.

Gen.

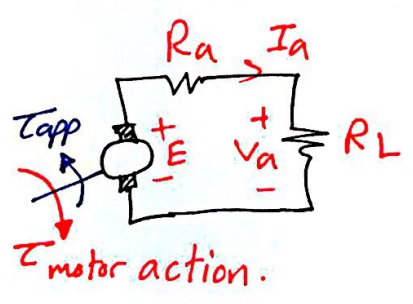



Motor.

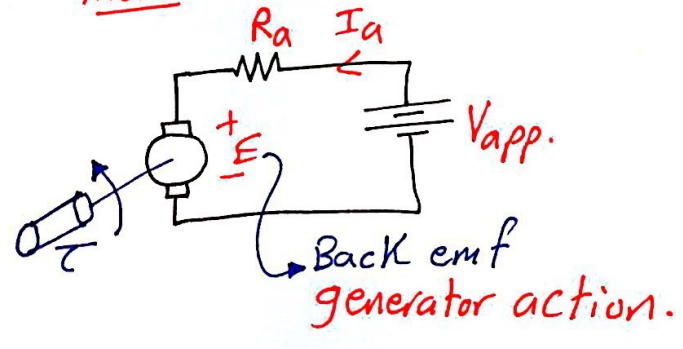

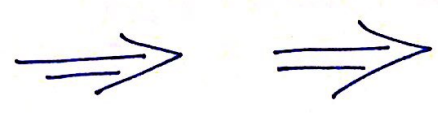*** Rotating magnetic field:**

If a Balanced 3-ph voltage is applied to a 3-ph winding located on the **Stator**, Then a Rotating magnetic field is produced within the **stator**, as follows:



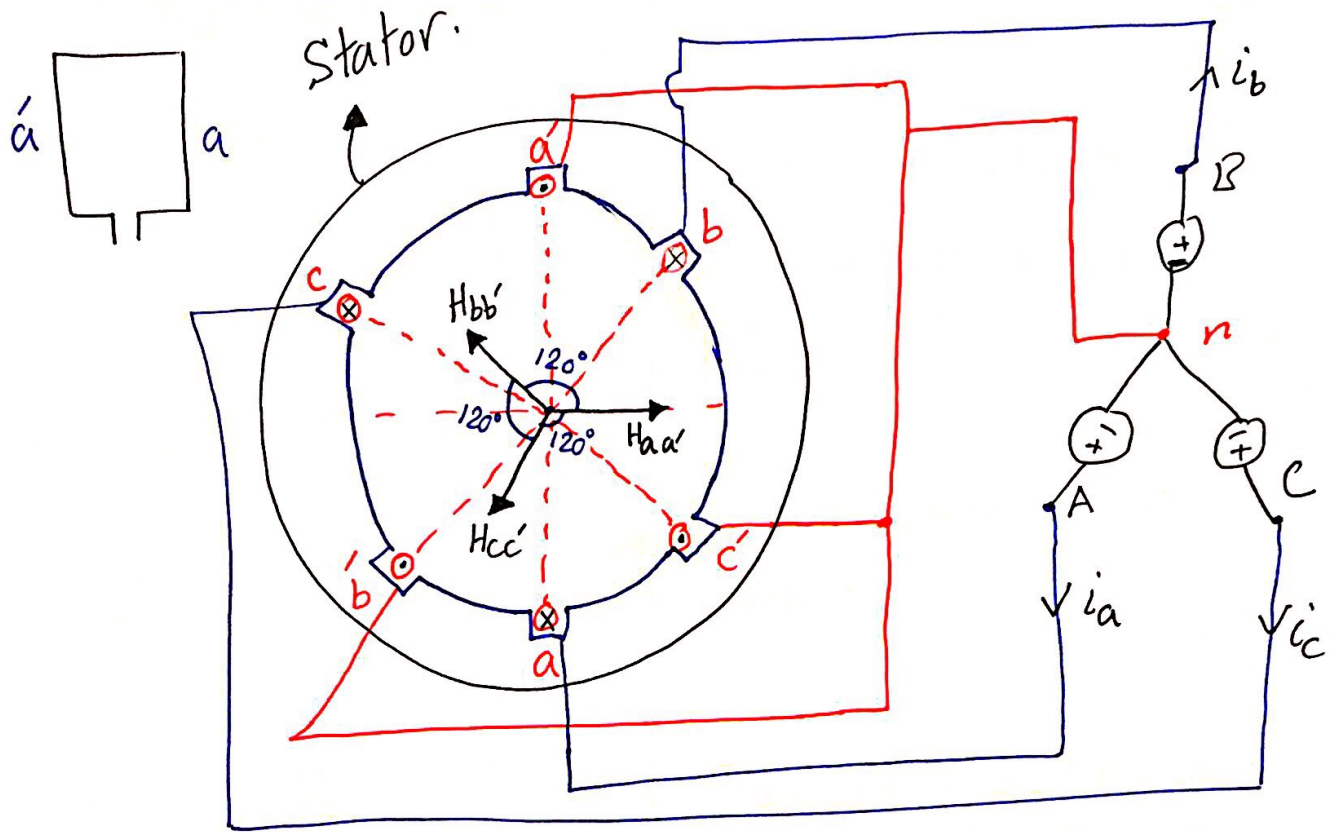

* Consequently, Balanced 3-ph currents will flow to the terminals i_a, i_b, i_c

∴ $i_a = I_m \sin(\omega t)$
 $i_b = I_m \sin(\omega t - 120^\circ)$
 $i_c = I_m \sin(\omega t - 240^\circ)$

* Each current will generate its magnetic field whose:

- 1] magnitude \propto current.
- 2] Direction can be found by RHR.

since $\vec{B} = \mu \vec{H}$

∴ $H_{aa'} = H_m \sin(\omega t) \angle 0^\circ$
 $H_{bb'} = H_m \sin(\omega t - 120^\circ) \angle 120^\circ$
 $H_{cc'} = H_m \sin(\omega t - 240^\circ) \angle 240^\circ$

∴ $B_{aa'} = B_m \sin(\omega t) \angle 0^\circ$
 $B_{bb'} = B_m \sin(\omega t - 120^\circ) \angle 120^\circ$
 $B_{cc'} = B_m \sin(\omega t - 240^\circ) \angle 240^\circ$

∴ Resultant flux density:

(67)

$$B_R = B_{aa'} + B_{bb'} + B_{cc'}$$

$$\Rightarrow B_R = B_m \sin(\omega t) \angle 0^\circ + B_m \sin(\omega t - 120^\circ) \angle 120^\circ + B_m \sin(\omega t - 240^\circ) \angle 240^\circ$$

* By converting to cartesian form it can be found that:

$$B_R = 1.5 B_m (\sin(\omega t) - j \cos(\omega t))$$

∴ $|B_R| = 1.5 B_m$

Next investigate the direction of B_R as ωt changes.

ωt	B_R
0°	$-j1.5 B_m = 1.5 B_m \angle 90^\circ$
90°	$1.5 B_m = 1.5 B_m \angle 0^\circ$
180°	$j1.5 B_m = 1.5 B_m \angle 90^\circ$
270°	$-1.5 B_m = 1.5 B_m \angle 180^\circ$
360°	$-j1.5 B_m = 1.5 B_m \angle -90^\circ$

* hence in this case when the current make one electrical cycle, the Rotating magnetic field makes one mechanical Rotation.

Next consider the following case

$\omega t = 90^\circ$


Then: $i_a = I_m \sin(\omega t) = +ve$

$i_b = I_m \sin(\omega t - 120) = -ve$

$i_c = I_m \sin(\omega t - 240) = -ve$

* let +ve current represented by \otimes

* let -ve current represented by \odot

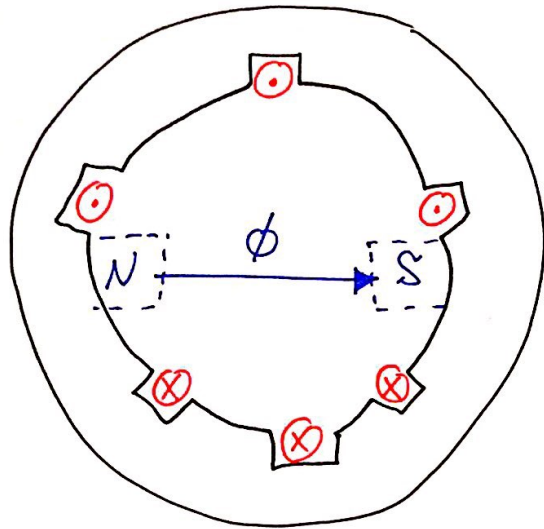


*hence this type of stator windings represent 2-pole winding.

*The sequence of this winding is a c b a c b

(i.e span between coil sides of each sides of each phase $(a \rightarrow a') = 180^\circ$ and the span between phases (i.e $a \rightarrow b = 120^\circ$)

⇒ However, the sequence is repeated twice a c b a c b a c b a c b

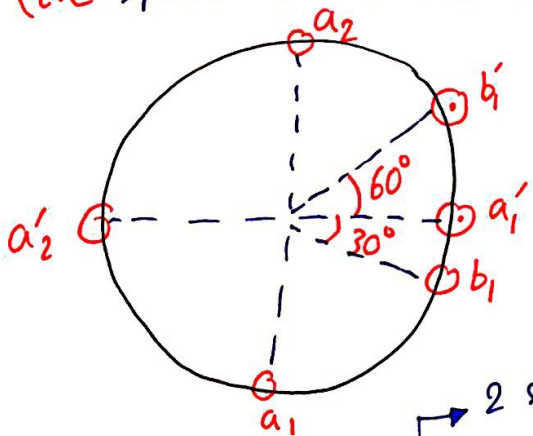(i.e span between coil sides = 90° & span between phases = 60°)



see Text Book.



2 seq. & 4 poles.

⇒ Then in the previous case electrical freq. = 2 * Mechanical Freq.

in general: $f_e = P f_m$

f_e ≡ electrical freq. of applied current.
 f_m ≡ mechanical freq. of rotating flux.
 P ≡ Number of pole-pairs of stator windings.

* End of Second Material *

* Voltage Induced in AC machines: (such as synchronous generator).

Here the field windings are located on the Rotor and the Armature windings are located on the Stator.



* The field current is supplied from External DC source to fieldwindings through sliprings & brushes.

* The Field Windings are designed in such away a sinusoidal flux is generated.

⇒ This flux is going to cut or Link Armature Windings. Consequently a voltage is induced, whose magnitude is derived as follows:

* voltage induced (ie magnitude):

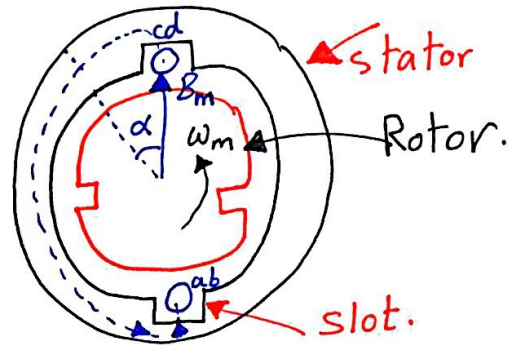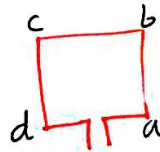Consider a single turn coil located in 2 slots.



⇒ flux generated can be expressed as:



θ ≡ Position at Stator.

⇒ As a Reference: Let Bm along +ve y direction.

⇒ At a given location or position on the stator with angle α, Then: $B = B_m \cos \alpha$


* If the Rotor is rotating at angular speed ω_m

↳ m stands for mechanical.

∴ $B = B_m \cos(\omega_m t - \alpha)$

↳ This is for outward direction of flux.

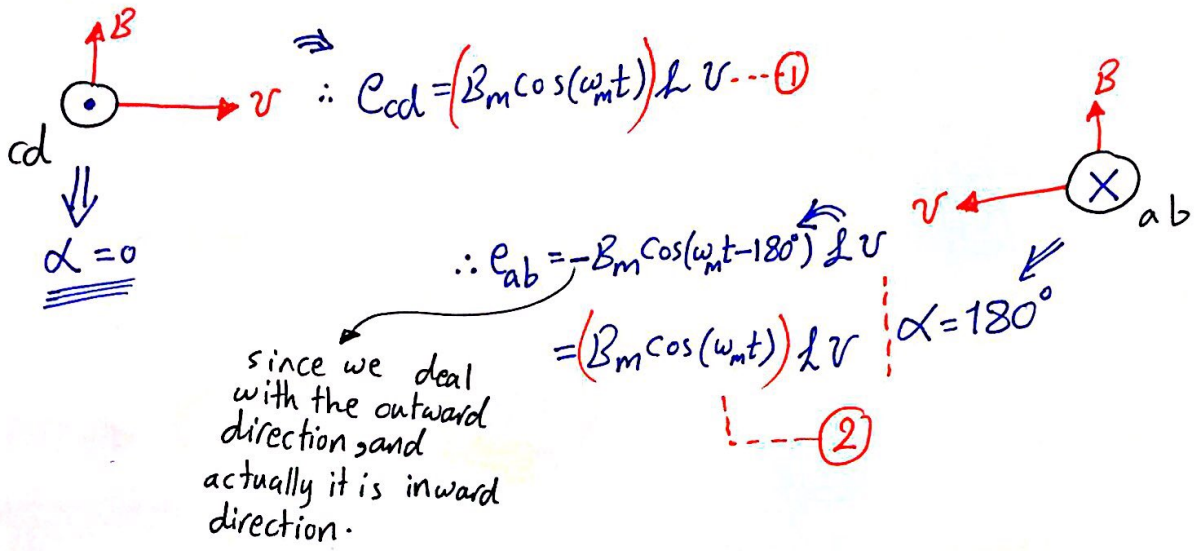⇒ voltage induced can be found by using RHR.
 (However this was applied when the field is stator).
 to apply it here, then to simulate that the field is the stator, then the observer sit on the Rotor and then look at Armature windings as follows:




As before there is No induced voltage in cb & da
 ∴ the Total induced voltage in the single turn coil:

(1) + (2) ⇒ $e = 2 B_m \cdot l \cdot v \cdot \cos(\omega_m t)$

∴ Amplitude of Induced voltage is: $E_m = 2 B_m \cdot l \cdot v$
 $= 2 B_m \cdot l \cdot \omega_m r$

since $\omega_e = \frac{P}{2} \omega_m$ $P \equiv$ Number of poles.
 electrical ⇒ ∴ $\omega_m = \frac{2 \omega_e}{P}$ ⇒ $E_m = \frac{4 B_m \cdot l \cdot \omega_e r}{P} \dots (1)$

* Average value of flux under a pole:

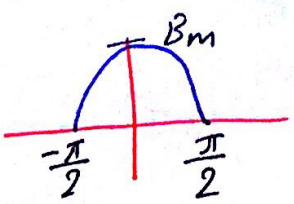

$B_{av} = \frac{1}{\pi} \int_{-\pi/2}^{\pi/2} B_m \cos \alpha \, d\alpha = \frac{1}{\pi} [B_m \sin \alpha]_{-\pi/2}^{\pi/2}$
 $= \frac{2 B_m}{\pi}$

* But surface area of a pole, $A_p = \frac{2\pi r l}{P}$

\therefore flux per pole, $\phi = B_{av} * A_p = \frac{2B_m}{\pi} * \frac{2\pi r l}{P}$
 $= \frac{4B_m r l}{P} \dots \dots$ (2)

\therefore Substitute (2) in (1):

$\Rightarrow E_m = \phi \omega_e$

** For N-turns coil:
Then, $E_m = N \phi \omega_e$

or in RMS:

$E_{rms} = \frac{E_m}{\sqrt{2}} = \frac{N \phi \omega_e}{\sqrt{2}} = \frac{N \phi (2\pi f)}{\sqrt{2}}$

$\Rightarrow E_{rms} = 4.44 N \phi f \dots \dots$ (4)

* in deriving (3) & (4) the following were assumed:

- 1] Flux is Sinusoidal, which isn't the case.
This is taken into account by introducing Pitch Factor (K_p).
- 2] That the turns are concentrated in a pair of slots.
However in practice, the coils are Distributed
This is taken into account by a Distribution Factor (K_d)

\therefore The general expression for induced voltage:

$E_{rms} = 4.44 K_p K_d N \phi f$
 \downarrow
 K_w

$K_w \equiv K_p K_d$ and called Winding Factor, defined as follows:

$K_p \triangleq \sin(P/2)$
 $P \equiv$ coils Pitch in electrical degree.



$$K_d = \frac{\sin\left(\frac{n\gamma}{2}\right)}{n \sin\left(\frac{\gamma}{2}\right)}$$


$\gamma \equiv$ slot Pitch in electrical degree.

$n \equiv$ Number of phase belts

$$\Rightarrow n = \frac{\text{Number of slots}}{3 * P}$$



number of poles.

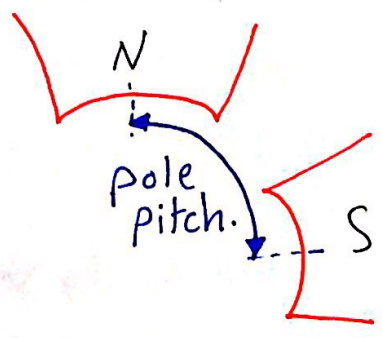Pole Pitch \equiv Distance between adjacent Poles.



ex. A 3-ph, 4-pole synchronous generator has 96 slots. The slot contain a double layer winding with 4 turns per coil. The coil pitch is $\frac{19}{24}$, Evaluate the following:

\therefore Each coil has 2 coil sides.

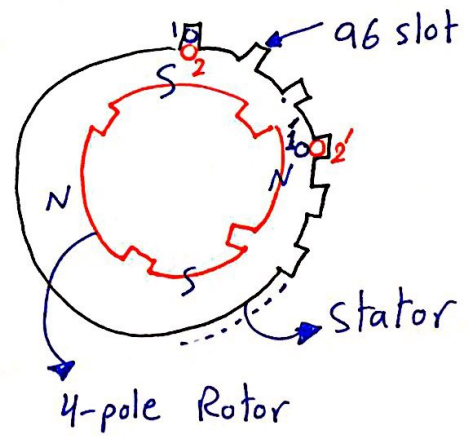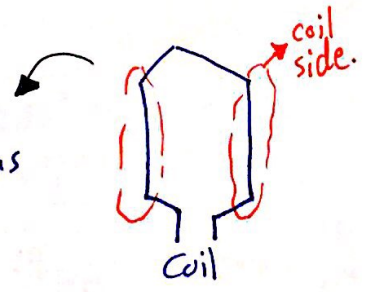


\Rightarrow Double Layer windings: means that each slot has 2 coil sides. \equiv equal to one coil.

\rightarrow side connected at the bottom of the slot & the other side connected at the top of the slot.

\therefore Total Number of coils \equiv Number of slots.

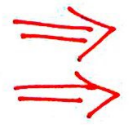\therefore Total Number of turns \equiv Number of slots * Number of turns per coil \Rightarrow



⇒ Now for the coil pitch: it is the distance or span between coil sides of a given coil.


ex. ⇒ on the figure: span between (1 & 1') OR (2 & 2')

Note: The Span is measured in mechanical degree or in electrical degree.

* Important Definitions:

→ Full Pitch Coil: if a coil side is under the center of a S-pole, then its other side will be under the center of adjacent North pole. ⇒ This is equal to pole's pitch.

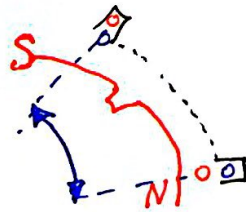→ Fractional Pitch Coil: if the coils pitch is < Full-pitch.



∴ Pole's Pitch = $\frac{360^\circ \text{ mech.}}{P}$

↳ Number of poles.

always:


Pole's pitch = 180° electrical

* In this example:

1) Coil's pitch = $\frac{19}{24}$ means: $\frac{19}{24} * \text{Full Pitch}$.

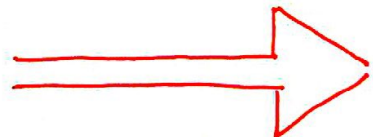2) Pole's Pitch = $\frac{360^\circ}{4} = 90^\circ$ mechanical. OR Pole's Pitch = 180° electrical.

⇒ ∴ $1^\circ \text{ mech} \equiv 2^\circ \text{ elect}$.



Continue.

NOW BACK TO the Example:

(74)

1} Find slot & coil pitch in electrical degrees?

* slot pitch, $\gamma \equiv \frac{360^\circ}{96} = 3.75^\circ \text{ mech.} = 3.75 * 2 = \underline{\underline{7.5^\circ \text{ elect.}}}$

* Coil pitch, $\rho = \frac{19}{24} * \text{Pole's Pitch} = \frac{19}{24} * 90^\circ \text{ mech.} = \underline{\underline{71.25^\circ \text{ mech.}}}$
 $= \frac{19}{24} * 90^\circ * 2 = \underline{\underline{142.5^\circ \text{ elect.}}}$

2} Find Pitch, distribution and winding factors?

* $K_p = \sin\left(\frac{\rho}{2}\right) = \sin\left(\frac{142.5}{2}\right) \Rightarrow \boxed{K_p = 0.947}$

* $K_d = \frac{\sin(n\gamma/2)}{n \sin(\gamma/2)}$; $n = \text{Number of phase belts} = \frac{\text{No. of slots}}{3 * p} = \frac{96}{3 * 4} = \underline{\underline{8}}$

$\Rightarrow \boxed{K_d = 0.956}$

* $K_w = K_p K_d \Rightarrow \boxed{K_w = 0.905}$

3} If flux per pole is 0.06 Wb and speed of Rotor is 1800 rpm, Find the magnitude of gen. voltage per phase?

$E_{rms} = 4.44 K_w N \phi f$
 $f = f_e = \frac{p}{2} n \text{ (rps)}$
 $= \frac{4}{2} * \frac{1800}{60} = \underline{\underline{60 \text{ Hz}}}$

; $N \equiv \text{Number of turns per phase.}$
 $= \frac{96 * 4}{3} = \underline{\underline{128}}$ → Number of Turns/coil.
Total Number of coils. → Number of phases.

$\Rightarrow E_{rms} = (4.44) (0.905) (128) (0.06) (60)$

$\Rightarrow \boxed{E_{rms} = 1851.59 \text{ volt}}$

* * *

Three-phase Synchron. Generator:

(75)

* Construction: explained before.

⇒ But Rotor could be of Two Types:

- 1] Cylindrical or Non-salient (i.e. 2-poles Rotor).
- 2] Non-Cylindrical or Salient (i.e. more than 2-poles).

$$f = nP \rightarrow \text{No. of pair poles.}$$

S.T ⇒ $n = 3000 \text{ rpm}$

$f = 50 \text{ Hz.}$

$$\therefore 50 = \frac{3000}{60} * P \Rightarrow \underline{\underline{P=1}}$$

∴ Cylindrical Rotor is used.



Hydro $n = (1000 - 1400) \text{ rpm.}$

∴ required poles > 2


∴ Salient Rotor is used.

* Equivalent cct of gen.:

since the gen. has 3-phases:

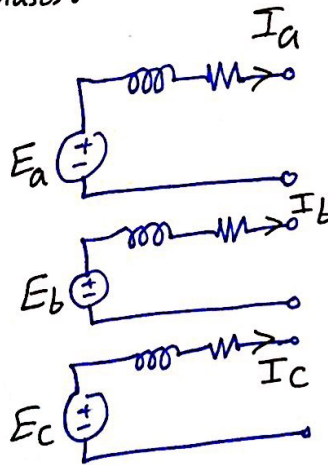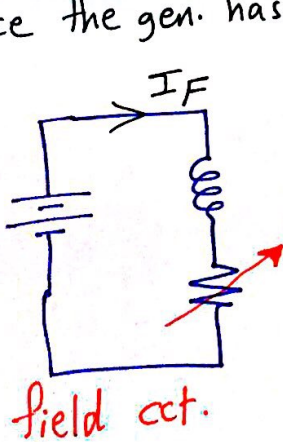

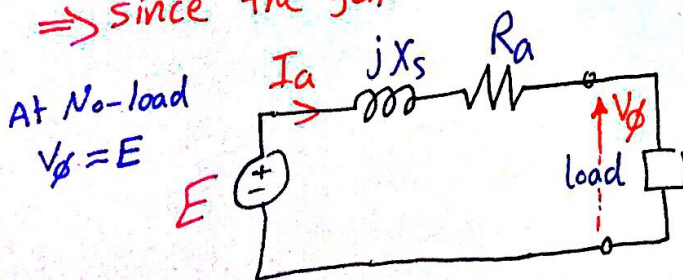⇒ since the gen. is **Balanced**, then one use per-phase cct:



$E, V_\phi \equiv$ generated & Terminal phase voltages.
 $X_s \equiv$ Synchron. Reactance, whose components will be explained later.

$R_a \equiv$ Armature winding Resistance.

$I_a \equiv$ Armature Current.

*** Armature Reaction:**


The flux produced by Armature current effect the main flux which is produced by Field windings, causing its reduction since $E = k\phi\omega$, then E will be reduced.

∴ The effect of A.R is represented by a Reactance X_a .
 ⇒ *since Armature winding has a self inductance, $L_a \Rightarrow X_a$
 The sum of X & X_a is called "Synchronous Reactance", X_s

$X_s = X + X_a$

*** Phasor Diagram of Synch. Gen.:**

⇒ Here one uses the per-ph equ. cct.

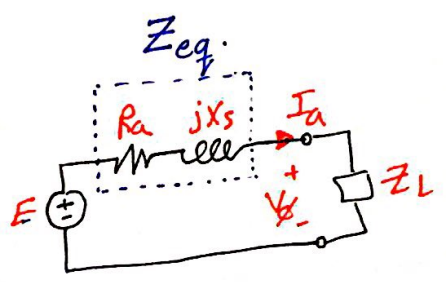


- Objective: To find voltage & current relationships under various loading condition.

This is the condition of generator operating alone.


- Procedure: Keep $|V_\phi|$ & $|I_a|$ constants & vary PF Angle of the load.

- Inductive Load:

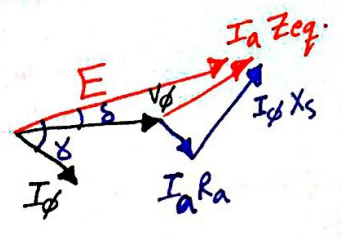


$E = I_a Z_{eq} + V_\phi$
 $\delta \equiv$ angle between E & I_ϕ
 $\phi \equiv$ angle between E & V_ϕ

- Resistive Load:

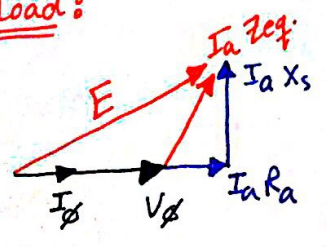

- Capacitive Load:

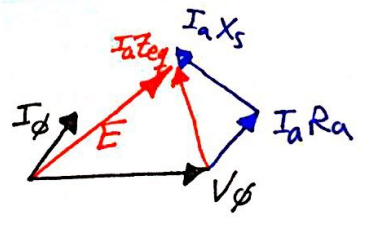


∴ $|E_L| > |E_R| > |E_C|$
 & $|E_C|$ could be $< |V_\phi|$

* Since $V_R = \frac{|E| - |V_\phi|}{|V_\phi|}$ ∴ V_R for inductive load has high +ve magnitude than Resistive Load.

* However, it can be deduced if $|E|$ is kept constant

Then as the load changes $|I_a|$ is varied then $|V_{\phi 2}| < |V_{\phi 1}| < |V_{\phi C}|$

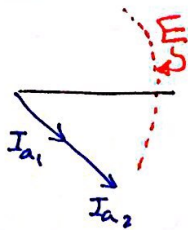Note: see the corresponding phasor diagram in the Text book.




\Rightarrow here in this case $|V_{\phi 2}| < |V_{\phi 1}|$

* Comment: As load increases (i.e. $I_a \uparrow$) \rightarrow Then voltage drop (i.e. $I_a Z_{eq} \uparrow$)

\rightarrow then $V_{\phi} \downarrow$ ($V_{\phi} = E - I_a Z_{eq}$)


Hence to maintain V_{ϕ} at a constant value then one should $E \uparrow$

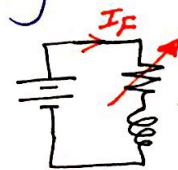\rightarrow since $E = K\phi\omega$ here one may $\uparrow \phi$ or $\uparrow \omega$ \rightarrow But ω can NOT be increased in order to maintain f at specified value, Therefore one $\uparrow \phi$ by $I_F \uparrow$ by reducing the variable resistance in the field windings.



* Power & Torque Relationships in 3-ph Synch. Gen. :

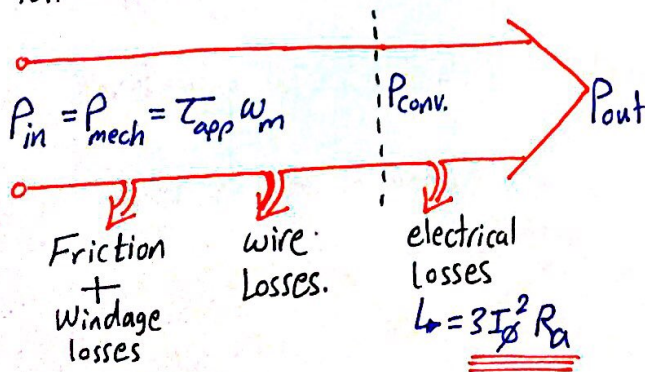This can be introduced by using power flow diagram as follows :



$P_{conv.} \equiv$ Amount of power converted to electrical.

$$P_{conv} = 3 |E| |I_{\phi}| \cos \delta$$

$$= \sqrt{3} |E| |I_{\phi}| \cos \delta$$

$$P_{out} = 3 V_{\phi} I_{\phi} \cos \theta$$

$$= \sqrt{3} V I_{\phi} \cos \theta$$

$\theta \equiv$ pf angle of load.

$$P_{conv} = T_{ind} \omega_m$$

$$\therefore T_{ind} = \frac{P_{conv}}{\omega_m}$$


⇒ ⇒ Approximate Expression for P & T :

* Here R_a is neglected.

∴ The phasor diagram will be as follows :

∴ $P_{conv} = P_{out}$

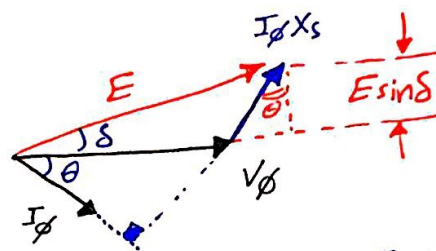since $P_{out} = 3V_{\phi} I_{\phi} \cos \theta \dots \dots \dots [2]$



⇒ $E \sin \delta = I_{\phi} X_s \cos \theta \dots \dots \dots [1]$

Sub. ① into ② :

$P_{out} = \frac{3V_{\phi} E \sin \delta}{X_s} \dots \dots \dots [3]$

since $P_{conv} = P_{out} = T_{ind} \omega_m$

∴ $T_{ind} = P_{out} / \omega_m$

⇒ $T_{ind} = \frac{3V_{\phi} E \sin \delta}{\omega_m X_s} \dots \dots \dots [4]$

* Comment :

from [3] it can be observed that $P_{out(max)}$ is when $\delta = 90^\circ$.

∴ $P_{out(max)} = \frac{3V_{\phi} E}{X_s} \Rightarrow$ This called: Static Stability Limit.

* in practice, δ never reach 90° usually it is in the Range of 20°-30°


What?!

* Measurement of R_a & X_s :

Why?! Because there values are required in the performance analysis of the generator.

How?! By Performing DC, O/C & S/C Tests on the generator.

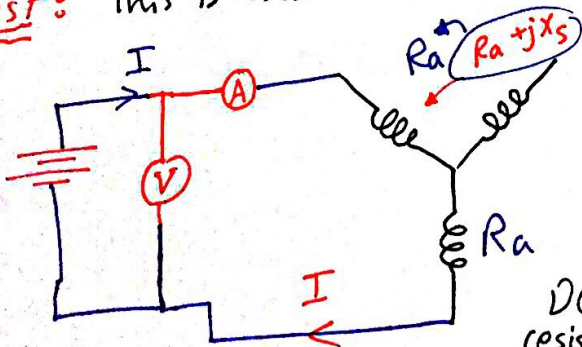* DC Test : This is used to measure R_a .



Armature winding usually Y-connected.

∴ $2R_a = \frac{\text{voltmeter reading}}{\text{Ammeter reading}}$


∴ $R_a = \frac{1}{2} \frac{V}{A}$

DC resistance. $R_{a,ac} = \text{factor} * R_{a,dc}$

* o/c Test:



⇒ Procedure: with terminals o/c, run the gen. at constant speed and then vary the field current. Taken the readings of terminal voltage & field current.

I_F	I_1 I_n
V	V_1 V_n

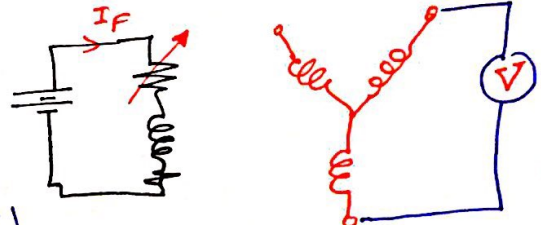

∴ In o/c V Reading \equiv Generated Voltage (E).

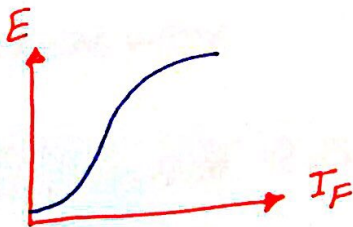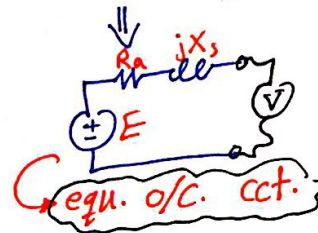since $E = k\phi n$ (constant speed).
 $\Rightarrow E = k'\phi$ * But ϕ is generated by I_F .





⇒ This is "o/c char. of the gen." OR "Magnetization Curve."

* S/c Test:


⇒ short circuit the terminals of the generator. Then, vary I_F & take the corresponding Reading of I_a .


I_F	I_{F1} I_{Fn}
I_a	I_{a1} I_{an}

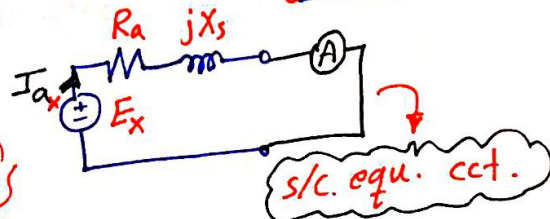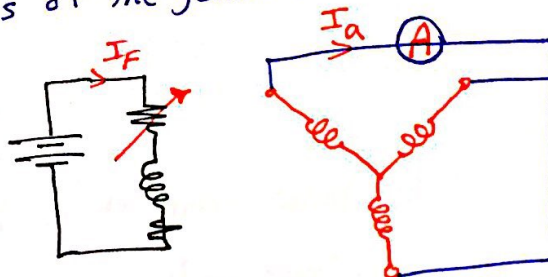

$\Rightarrow I_a = \frac{E}{R_a + jX_s} \Rightarrow I_a = \frac{E}{Z_{eq}}$

$\Rightarrow |I_a| = \frac{|E|}{|Z_{eq}|}$

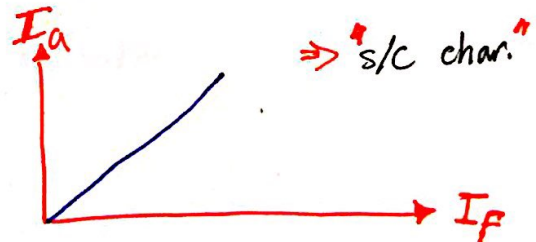

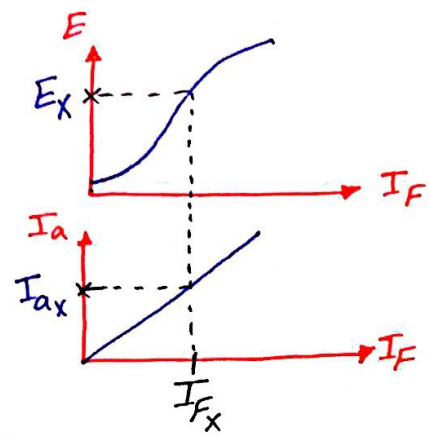

** For a given I_{Fx} , one would obtain from o/c & s/c characteristics the corresponding E & $I_a \Rightarrow$ say E_x, I_{ax}

$\therefore \frac{E_x}{I_{ax}} = |Z_{eq}|$

\Rightarrow since $Z_{eq} = R_a + jX_s \Rightarrow \therefore |Z_{eq}| = \sqrt{R_a^2 + X_s^2}$
 so $X_s = \sqrt{|Z_{eq}|^2 - R_a^2}$

* Name Plate of a generator contain the following:
 1) Rated voltage 2) Rated current. 3) Frequency

* Short circuit Ratio (SCR):

SCR \triangleq $\frac{\text{The field current which produces Rated voltage at o/c.}}{\text{The field current which produces Rated armature current at s/c}}$

$\Rightarrow \text{SCR} = \frac{I_{Fv}}{I_{FI}}$

* It can be found that:
 $\text{SCR} = \frac{1}{X_s \text{ (pu)}}$

* Generator could be operated on its own called "Alone Generator".
 OR * Generator could be working with other generators called "Parallel Generators".

What? why? * Parallel operation of 3-ph generator:


Objectives or Advantages:

- 1] More economical from operation Point of view.
- 2] More Reliable.

How?! A generator could be connected in parallel with other generator OR Connected in parallel with a power system.
(i.e National Grid).

* Conditions for Parallel operation:

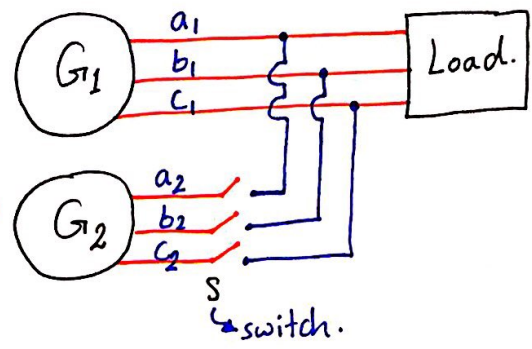G_2 is to be connected with G_1 which is already supplying load.



* G_2 is called: "Oncoming Generator."

⇒ Condition of Parallel operation:

(i.e what should be done before closing S)

1) G_1 & G_2 should have the same voltage (i.e magnitude & phase angle).

The magnitude of G_2 Can be checked by means of VOLTMETER.


2) They should have the same sequence.

⇒ This could be checked by:

a) using a small 3-ph induction motor ⇒ first connected to G_1 and then to G_2 , observe direction of rotation.

- if same direction, then same phase sequence.
- otherwise, reverse the connection of 2-phases in G_2 .

b) Using 3-bulb method.

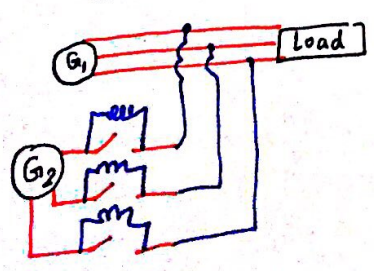

⇒ The brightness of the lamp depends on the phase shift between its terminals.

→ when 3-bulbs light-up & dim-down simultaneously together, then G_1 & G_2 have the same phase sequence.

→ when 3-bulbs dim-down, then they are in-phase.

3) Frequency of G_2 should be slightly higher than G_1

⇒ for stability reasons.

* This process of Parallel operation is called: "Synchronization."

ex. "Example 4-1 in Text Book".

200 KVA, 480 volt, 50 Hz. Y-connected synch. Gen. with rated field current 5A was tested, and the following were taken:

$V_{T,sc}$ at rated $I_F = 540$ volt.

$I_{L,sc}$ at rated $I_F = 300$ A.

when a DC volt 10-V was applied a 25A was measured.

Find R_a & X_s ?

From the DC Test one can obtain R_a :

$\rightarrow R_a = \frac{1}{2} \left(\frac{\text{Voltmeter}}{\text{Ammeter}} \right) = \frac{1}{2} \left(\frac{10}{25} \right) \Rightarrow R_a = 0.2 \Omega$

from the o/c Test one can obtain E_A :


since it is Y-connected: $E_A = \frac{V_{T,sc}}{\sqrt{3}} = \frac{540}{\sqrt{3}} \Rightarrow E_A = 311.8 \text{ volt.}$

from the s/c Test one can obtain I_a :

since it is Y-connected: $I_a = I_{L,sc} = 300 \text{ A.}$

Now: $|Z_{eq}| = \frac{E_A}{I_a} = \frac{311.8}{300} = 1.04 \Omega = \sqrt{R_a^2 + X_s^2}$


so $X_s = 1.021 \Omega$

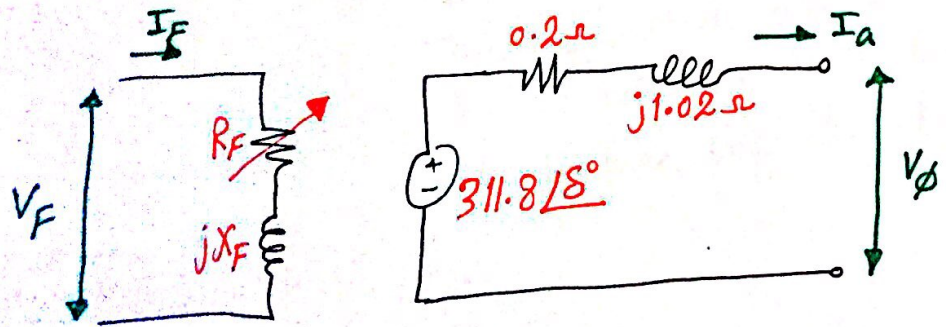

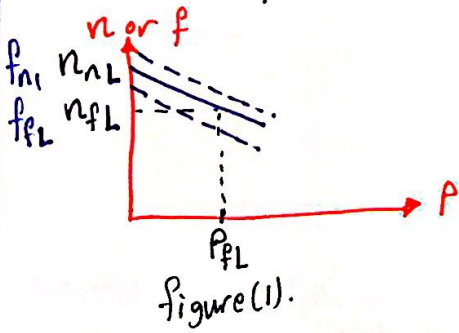*** Power-frequency & voltage - Reactive power Relationships:**

As the load (i.e P) on the gen \uparrow the speed (i.e n) \downarrow due to the rotating torque.

This decrease is non-linear, but by using a Governor Mechanism the drop is made linear.



$$\therefore \text{speed drop} = \frac{n_{nL} - n_{fL}}{n_{fL}}$$

since $f = n \cdot p$.

\therefore since drop is linear, then the output of the gen. can be expressed as:


$$P = S_p (f_{nL} - f_{fL})$$

where S_p unit is: MW/Hz.

* By means of the Governor, the no-load set-point can be changed. \therefore characteristics can be shifted up or down.

* Application of this characteristics: is that it can be used to find load sharing between parallel generators as will be illustrated by an example.

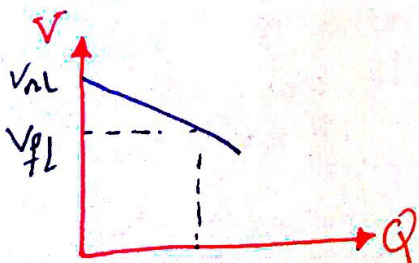* It was found before by using phasor diagram that as the inductive load increases (i.e Reactive Power increases) then terminal voltage \downarrow . By means of a voltage Regulator, this decrease is made linear.




figure(2).

Figure(1) & figure(2):


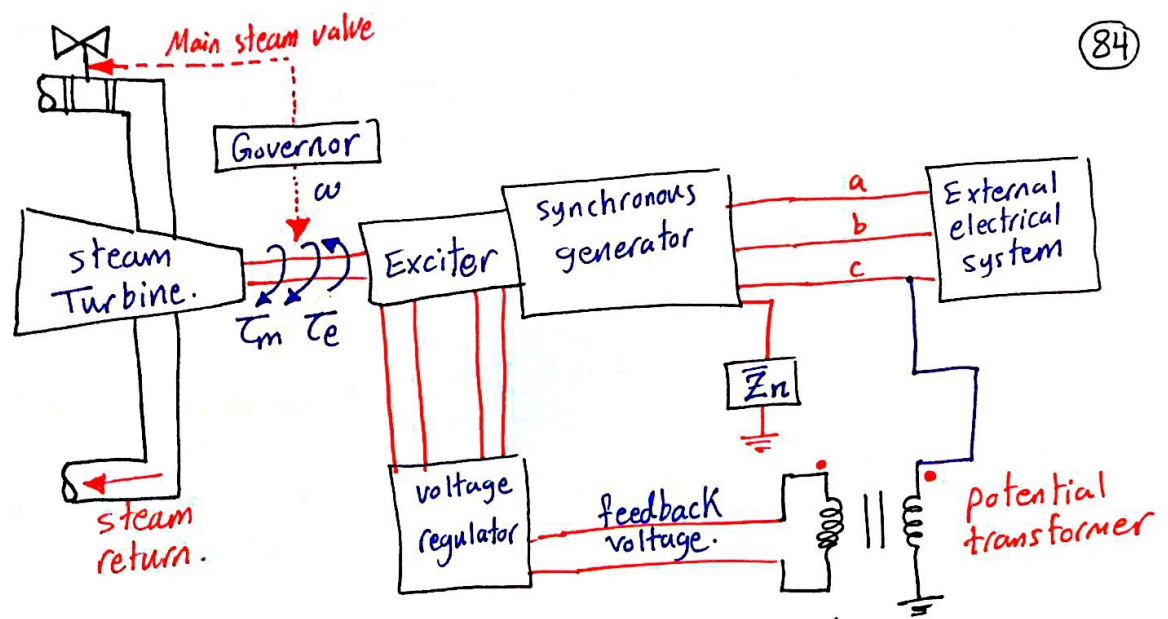
These 2 controls are illustrated by the following block diagram of Turbine-Generator-Exciter system.





* Power sharing between 2 generators can be solved by drawing their characteristics Back-to-Back.

This called: "Housing Diagram"

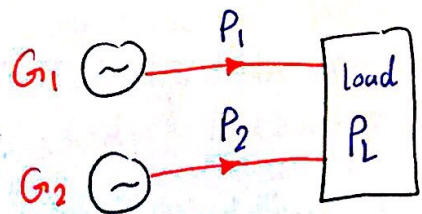
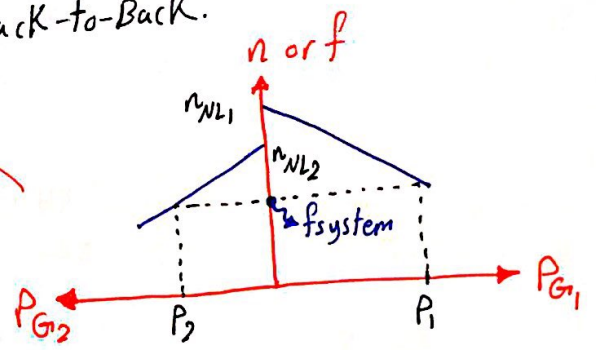


$$P_1 + P_2 = P_L$$

$$S_{P1} (f_{NL1} - f_{sys}) + S_{P2} (f_{NL2} - f_{sys}) = P_L$$

* Connecting a Generator to infinite system:

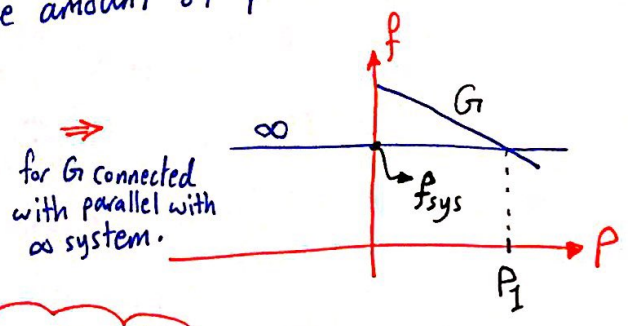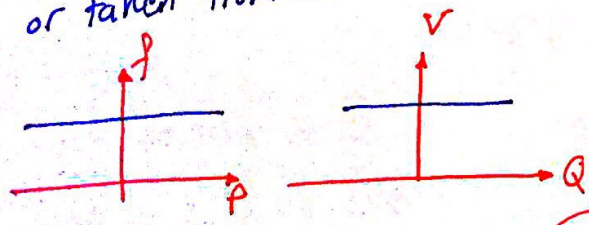• Definition: ∞ system it is a large power system whose frequency and voltage, does not change by the amount of power supplied to it or taken from it.



for G connected with parallel with ∞ system.

$$P_{\infty} = P_L - P_1$$

(ex.) A DC, o/c, s/c Tests as explained before, were performed on 25 MVA, 12.2 KV, 0.9 pf Lagging 3-ph Δ -connected generator with the following Results: (85)

DC Test: $V=12$ volt & $I=10$ A.

o/c Test:

I_F (A)	320	365	380
V (KV)	15.4	17.5	18.3

s/c Test:

I_F (A)	320	365	380
I_a (A)	1040	1190	1240

Find the parameters of generator?

* Rated pf: This is the lowest acceptable pf of the gen. when it is operating at its rated apparent power.

$$R_{dc} = \frac{1}{2} \left(\frac{12}{10} \right) \Rightarrow R_{dc} = 0.6 \Omega$$

$$|Z| = \frac{V_{oc}}{I_{sc}} = \frac{(15.4/\sqrt{3}) * 10^3}{1040} = 8.55 \Omega$$

we take any one from table.
since we need phase voltage.

$$\Rightarrow X_s = \sqrt{|Z|^2 - R^2} \Rightarrow X_s = 8.53 \Omega$$

(ex.) a 480 volt, 200 KW, 2 pole, 3 ph, 50 Hz synch. gen. with its turbine has $n_{NL} = 3040$ rpm and $n_{FL} = 2975$ rpm, is in parallel with

480V, 150 KW, 4 pole, 3-ph, 50 Hz synch. gen. with its turbine has $n_{NL} = 1500$ rpm & $n_{FL} = 1485$ rpm in order to supply a load of $P_L = 200$ KW at 0.85 pf lagging.

1) Find speed Droop (SD) for each gen?

\therefore By substitution $SD_{G_1} = 2.18\%$, $SD_{G_2} = 1.01\%$

2) Find the operating frequency of the system (i.e f_{sys}) and then load sharing?

$f = nP$, by using this:

	G_1	G_2
f_{NL}	50.67 Hz	50 Hz
f_{FL}	49.58 Hz	49.5 Hz

$$SP_1 = \frac{200}{50.67 - 49.58} = 183.5 \text{ KW/Hz}$$

$$SP_2 = \frac{150}{50 - 49.5} = 300 \text{ KW/Hz}$$

$$\therefore 200 = 183.5 (50.67 - f_{sys}) + 300 (50 - f_{sys})$$

P_{G_1} P_{G_2}

$$\rightarrow f_{sys} = 49.84 \text{ Hz}$$

$$P_{G_1} = 152.3 \text{ KW}$$

$$P_{G_2} = 47.7 \text{ KW}$$

* DC Machines:

* Construction: It was explained during Fundamentals of electrical machines \Rightarrow Field windings are located at the stator.
Armature windings are located at the Rotor.


* Classification:

According to the source of field current (I_f), DC Machines are classified into:

1] Separately Excited Machine.
 I_f is supplied from External DC source.

2] Self-Excited DC Machine.
 I_f depends on residual magnetism in the poles of the machine and classified into:

a) Shunt DC Machines.

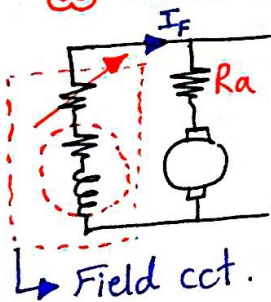

field cct should be high for I_f to be small.

* Number of turns (N) in series is less than in shunt.

b) Series DC Machines.




field cct should be small for voltage drop to be small


c) Compound DC Machines.

It has 2 field windings (i.e. series & shunt)

There are 2 possible connection:

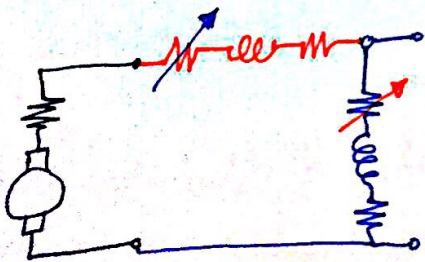

"long shunt Compound DC Machines."

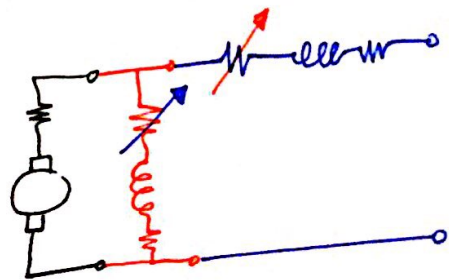


"short shunt compound DC Machines."

- * If the series field aid shunt field the machines is called "Cumulative Compound Machine".
- * If the series field opposes shunt field the machines is called "Differential Compound Machine".

- * If we need the machine Generator \Rightarrow Connect R_L .
- * If we need the machine Motor \Rightarrow Connect a voltage source.

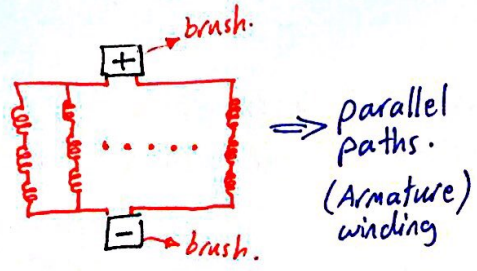Introduction to the types of Armature Winding:



$a \equiv$ Number of parallel paths between +ve & -ve brushes.
 $a \Rightarrow$ depends on the type of Armature windings.

$a = mP$ for Lap winding.
 $a = 2m$ for Wave winding.

$m \equiv$ Multiplicity of Armature winding.

- $m=1$ for simplex.
- $m=2$ for Duplex.
- $m=3$ for Triplex.

$P \equiv$ Number of poles.

* Illustration:

consider a double layer Armature winding with 36 slots, let the machine has 4 poles. If the machine (type of winding) is a simplex Lap winding.


$a = mP = 1 * 4 = 4$

\Rightarrow since it is a double layer
 so No. of coils = No. of slots.
 No. of coils = 36

\Rightarrow No. of coils/path = $36/4 = 9$

if induced voltage per coil = e

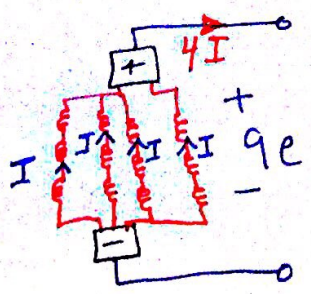\therefore generated voltage (voltage between brushes) = $9e$



if the rated current of coil = I

\therefore Rated current of the machine $\equiv a * I = 4I$




⇒ ∴ Rated power of the machine = $9e * 4I$
 $= \boxed{36eI}$

* If the type of winding is a simplex wave winding.

⇒ $a = 2 * m = 2 * 1 = \boxed{2}$ } produced current = $I_a = \underline{2I}$
 No. of coils/path = $36/2 = \boxed{18}$ } Rated power = $18e * 2I = \underline{36eI}$
 voltage between brushes = $\underline{18e}$

⇒ Conclusion :

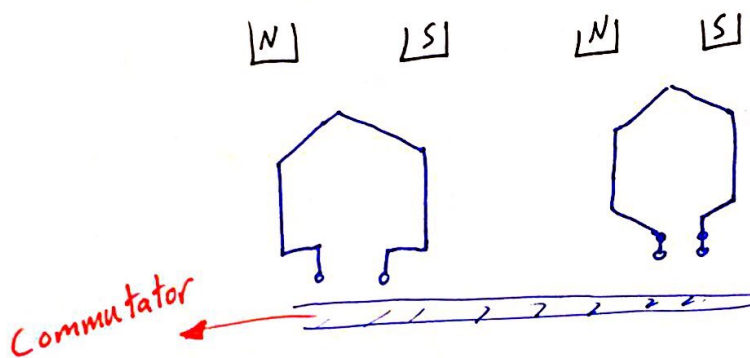- * Lap winding used for Low voltage & High current application.
- * Wave winding used for High voltage & Low current application.



see the Text Book for full figure.

* Voltage Induced in DC Generator (i.e voltage between brushes):

It was found before that the voltage induced in a single turn $e = 2Blv$ where a turn consists of 2 conductors.

① ∴ $e = 2Blv$ But Area per pole: $A_p = \frac{2\pi r^2}{P} \dots \dots \textcircled{2}$
 ∴ flux per pole: $\phi = BA_p = \frac{B * 2\pi r^2}{P}$ ∴ $2Blv = \frac{P\phi}{\pi} \dots \dots \textcircled{3}$

substitute ③ into ①:

⇒ $e = \frac{P\phi\omega}{\pi}$ "voltage induced in a single turn".

* If the total Number of Armature conductors = Z .

∴ Total Number of Armature Turns = $Z/2$

∴ Number of Turns per path = $\frac{Z}{2a} \dots \dots \textcircled{4}$

∴ Voltage generated across brushes, $E = \text{voltage per path} = \textcircled{4} * \textcircled{5}$

$\therefore E = \frac{P\phi\omega}{\pi} * \frac{Z}{2a}$ But $\omega = 2\pi n$ $n \equiv$ speed r.p.s.

$\Rightarrow E = \frac{P\phi Zn}{a}$

$K = \frac{PZ}{a}$

* For a given machine P, Z, a are constants so $\Rightarrow E = K\phi n$

- ** For a generator, E is called "generated voltage".
- ** For a Motor, E is called "Back emf".

*** Induced Torque in DC Machine :**


It was found before that the torque induced in a single turn $\tau_{ind} = 2B l I r$, $I \equiv$ current passing through turn. $\dots \textcircled{6}$

* Sub. $\textcircled{3}$ into $\textcircled{6}$: $\tau_{turn} = \frac{P\phi I}{\pi}$

\therefore Total Torque produced, $T = \tau_{turn} * \text{Total Number of Turns.}$

so, $T = \frac{P\phi I}{\pi} * \frac{Z}{2}$

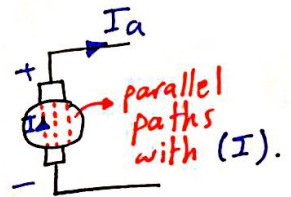* if the armature current is I_a , $I = \frac{I_a}{a}$



$\Rightarrow T = \frac{P\phi Z I_a}{2\pi a}$

* For a given machine P, Z, a constants : $\Rightarrow T = K'\phi I_a$

$K' = \frac{PZ}{2\pi a}$

** For a DC Motor, T is called "Developed or Generated" Torque.

** For a DC generator, T is called "Opposing or Retarding Torque".


*** Characteristics of DC Generator :**

* Objective: To find No-load & load char.



● **Separately Excited:**

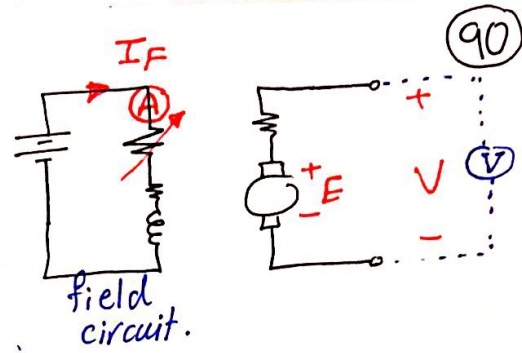- No-load: $I_F \equiv$ field current.
 $E, V \equiv$ Generated & Terminal voltages.




* Procedure:

Run generator at constant speed then vary I_F , and take the reading of V .

\Rightarrow Then plot V vs. I_F

since $E = K\phi\omega$.

I_F	I_1	\dots	I_n
V	V_1	\dots	V_n

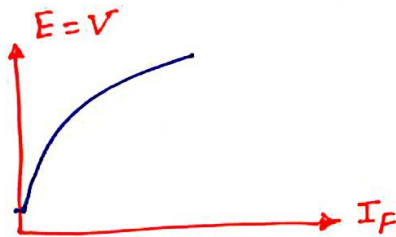


\Rightarrow This called: Magnetization Curve.
 OR No-load char.


● Load Characteristic:

* procedure: Run generator at constant speed and for a given I_F , vary R_L , & record the readings of V_L & I_L .

\Rightarrow Then plot V_L vs. I_L .

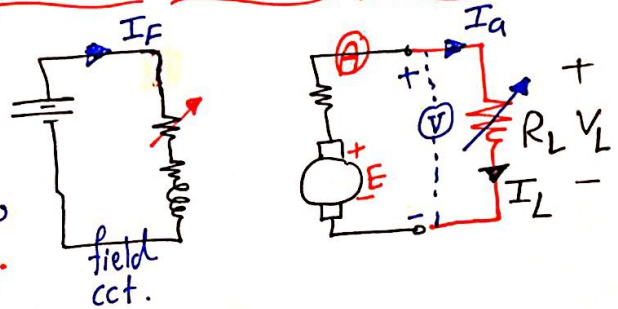


* when $I_L = 0$, (No-load) ; $V_L = E$.

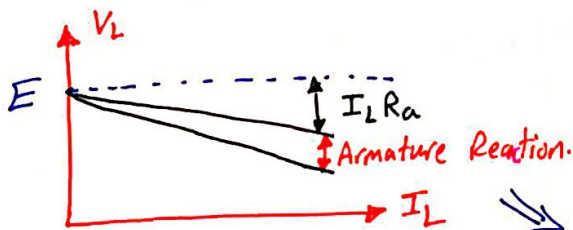

* using KVL: $V_L = E - I_L R_a$
 $R_a \equiv$ Equivalent Armature Resistance

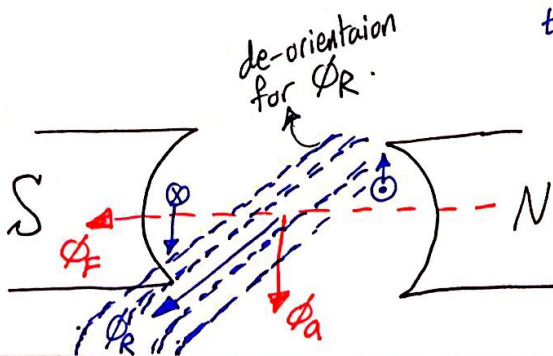\Rightarrow so we have two types of drop.





$\Rightarrow \phi_a$ cause a de-orientation for the resultant flux.

● Self-excited:

● shunt generator:
No load:


* Run gen. at constant speed.

since $E = k\phi n$.

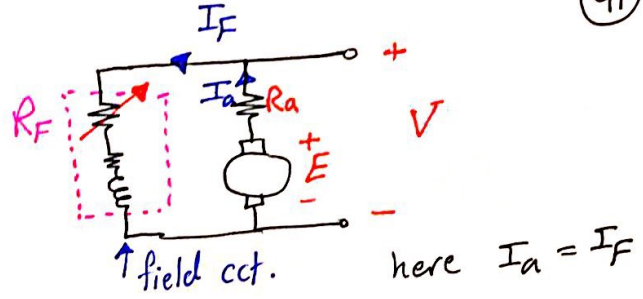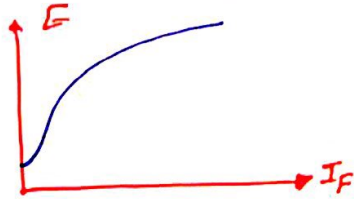

⇒ This called: Build-up of voltage.
 due to Residual Magnetism

$$I_a = I_F = \frac{E}{R_a + R_F}$$

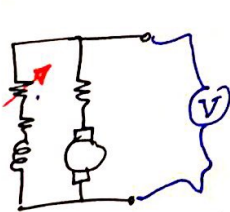


→ if the voltmeter reads zero, we say voltage is failed to Build-up.

* Causes of failure to Build-up:


- 1] Lack of Residual Magnetism.
- 2] Field windings are connected in such a way to cancel Residual Magnetism.
- 3] open circuit in the field or Armature Windings.

Load:

$$\Rightarrow V_L = E - I_a R_a$$

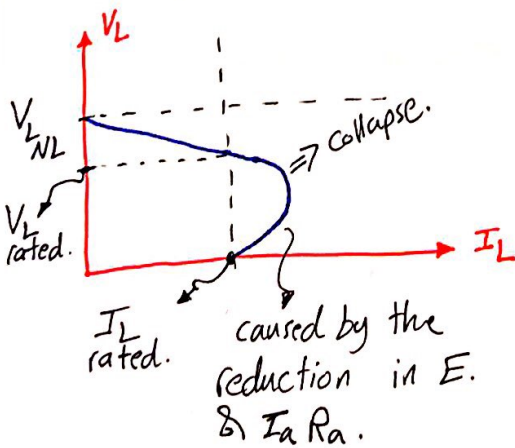
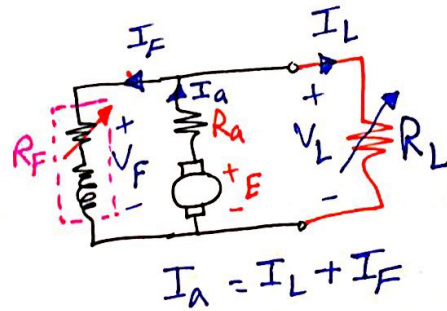
$$\begin{aligned} \Rightarrow I_L \uparrow &\rightarrow I_a \uparrow \\ &\downarrow \\ &I_a R_a \uparrow \\ &\downarrow \\ &V_L \downarrow \end{aligned}$$



also $V_L = V_F \Rightarrow V_L \downarrow \Rightarrow V_F \downarrow$

$$I_F = \frac{V_F}{R_F}$$



$$V_F \downarrow \Rightarrow I_F \downarrow \Rightarrow \phi \downarrow \Rightarrow E \downarrow$$

"field cct Resistance.
 represent all of field cct"

● Series generator:

$$V_L = E - I_L (R_a + R_s)$$



$$I_s = I_a = I_L$$

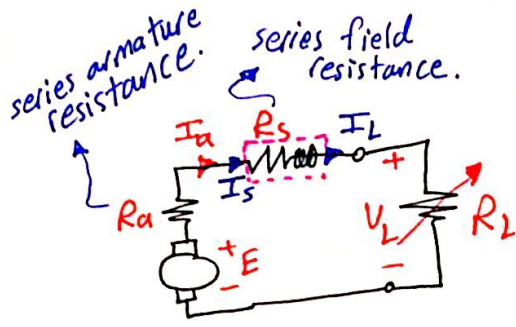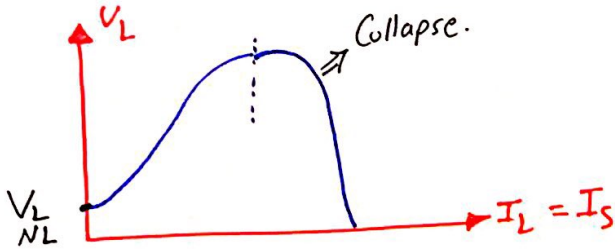

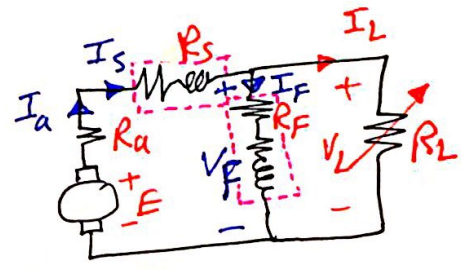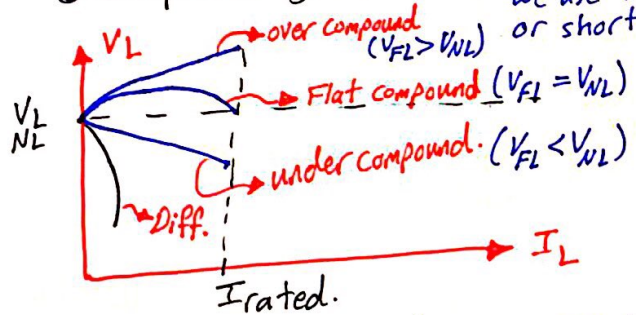(92)

$$I_L \uparrow \Rightarrow E = K\phi n \uparrow \Rightarrow I_L (R_a + R_s) \downarrow$$

● Compound generator: "No difference if we use long shunt or short shunt."



$$V_L = V_F$$

$$I_a = I_s = I_F + I_L$$

$$E = I_a (R_a + R_s) + V_F$$

$$V_L = V_F = E - I_a (R_a + R_s)$$

- $R_F \equiv$ shunt field cct resistance.
- $R_a \equiv$ Armature cct resistance.
- $R_s \equiv$ Series Field resistance.

* Commutative:

$N_s I_s$ aid $N_F I_F$
 mmf of series field mmf of shunt field.

$$I_L \uparrow \Rightarrow I_a \uparrow$$


* Depending on the amount of aiding there are \cong possible characteristics: see the above figure.

* Characteristics of DC Motors:

● Shunt Motor:

$V, I \equiv$ Applied Voltage & Current.

$E \equiv$ Back EMF.

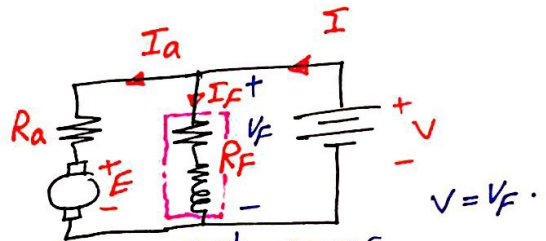

* Objective: To find various relationships of voltage, current, power and load characteristics.

* Procedure: $E = V - I_a R_a \dots \dots \textcircled{1} \Rightarrow$ Multiply $\textcircled{1}$ by I_a :

$\Rightarrow E I_a = V I_a - I_a^2 R_a \dots \dots \textcircled{2} ; (I_a = I - I_f) \dots \dots \textcircled{3}$

* sub. $\textcircled{3}$ into $\textcircled{2}$:

$$E I_a = V I - V I_f - I_a^2 R_a \rightarrow \text{Armature ckt losses.} \Rightarrow E I_a = V I - (V I_f + I_a^2 R_a)$$

\downarrow input to motor. \downarrow field ckt losses. \downarrow input. \downarrow Electrical Losses.
 Converted Power ($P_{conv.}$).

* Note:

It can be found that for ALL TYPES of motors that:

$P_{conv.} = E I_a$; $P_{conv} = \tau_{ind} \cdot \omega_m = E I_a \Rightarrow \tau_{ind} = \frac{E I_a}{\omega_m}$

* We could be asked to prove $P_{conv.} = E I_a$ for any Type.

* Speed Equation:

$E = V - I_a R_a \Rightarrow K \phi \omega = V - I_a R_a \Rightarrow \therefore \omega = \frac{V - I_a R_a}{K \phi}$ speed equation (SE).

This SE. shows the 3 methods of controlling the speed of shunt motor:

- 1] By varying applied voltage (V), (Armature Control).
- 2] By varying flux (ϕ), (Field Control).
- 3] By varying Armature ckt. Resistance. (Rarely being used).

*** Field Control:**

⇒ Vary R_F .

for ex. if $R_F \uparrow \Rightarrow I_F = \frac{V}{R_F} \downarrow \Rightarrow \phi \downarrow \Rightarrow E \downarrow$

since $I_a = \frac{V - E}{R_a} \Rightarrow E \downarrow \Rightarrow$ so $I_a \uparrow$ But $T_{ind} = K \phi I_a$

⇒ increasing in I_a > decreasing in ϕ


so $T_{ind} \uparrow \Rightarrow \omega \uparrow$ As $\phi \downarrow \Rightarrow \omega \uparrow$

**** For shunt motor** (Never ever open suddenly the shunt field ckt) since $I_F = 0$ so $\phi = 0$ which lead to $\omega = \infty$.

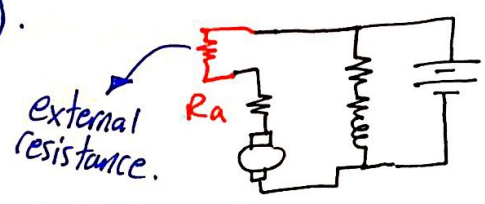*** Armature Control:**

⇒ vary the applied voltage.

*** Varying Armature ckt. resistance:** (By adding an external resistance to R_a).




(ex.) A 10kW, 250V, DC shunt gen. is driven at 1000 rpm and given $R_a = 0.15 \Omega$ & $I_F = 1.64A$. IF Rotational losses = 540W.
Find at Rated Conditions: 1] Generated Voltage. 2] Efficiency.

1] By KVL:

$$E = I_a R_a + V_L \quad ; \quad V_L = 250 \text{ volt} \quad \& \quad R_a = 0.15 \Omega$$
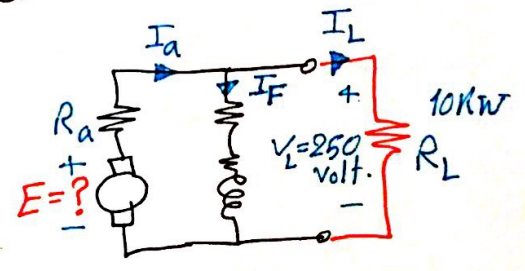
$$\Rightarrow I_a = I_F + I_L = 1.64 + \frac{10 \times 10^3}{250} = 41.64A$$



Substitute: $E = 256.25 \text{ Volt.}$

2] $\eta = \frac{P_{out}}{P_{out} + P_{losses}} * 100\%$, $P_{out} = P_L = 10 \times 10^3 W$, $P_{losses} = \text{electrical} + \text{mechanical}$.
 ↳ \equiv Rotational losses.

Electrical = Losses of Armature + losses of field = $I_a^2 R_a + V_F I_F = 670.08 W$.

Substitute: $\eta = 89.2\%$



ex. A 7.5 hp (horse Power), 120 V DC series Motor has (95)
 $R_a = 0.2 \Omega$, $R_s = 0.16 \Omega$. At Full load the current input is 58 A.
 at the rated speed of 1050 rpm. Given Core Losses = 200 W.
 \rightarrow mechanical losses = 240 W At full load. Assume mechanical
 losses is proportional with the cube of motor's speed. ($P_{mech.} \propto \omega^3$)
 & the Core losses are constant.

Also given from the magnetization curve which produced at $n = 1200$ rpm
 the followings:

$I_f = 35 \text{ A} \rightarrow E = 115 \text{ V}.$
 $I_f = 58 \text{ A} \rightarrow E = 134 \text{ V}.$

* Analysis for the Givens :

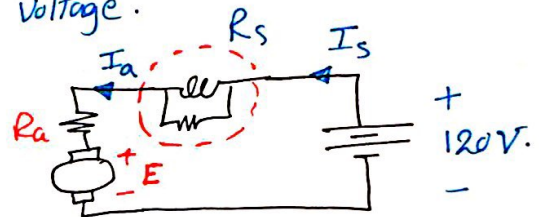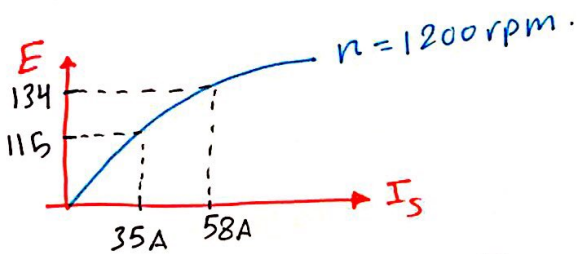120 V in the example \Rightarrow it is a Terminal voltage.



* Find the speed & efficiency of the motor if it is operating
 at Armature current 35 A ?

Solution:

$I_a = I_f$
 $R_a = 0.2 \Omega$
 $R_s = 0.16 \Omega$

$\Rightarrow E = V - I_a (R_a + R_s)$
 for $I_a = 35 \text{ A} \Rightarrow E_1 = 107.4 \text{ volt}$
 $I_a = 58 \text{ A} \Rightarrow E_2 = 99.1 \text{ volt}.$

remember: E here is called back emf.

Since $E = K \phi n \Rightarrow \therefore \frac{E_1}{E_2} = \frac{\phi_1 n_1}{\phi_2 n_2} \dots [1]$

* Ratio $\frac{\phi_1}{\phi_2}$ can be evaluated from the given information as follows.

$E_1' = 115 \text{ volt for } I_s = 35 \text{ A, } n = 1200 \text{ rpm}.$

$E_2' = 134 \text{ volt for } I_s = 58 \text{ A, } n = 1200 \text{ rpm}.$

$\therefore \frac{E_1'}{E_2'} = \frac{115}{134} = \frac{\phi_1 1200}{\phi_2 1200} \therefore \frac{\phi_1}{\phi_2} = \frac{115}{134} \dots [2]$

Continue.

⇒ ∴ substituting ② into ①:

$\frac{107.4}{99.1} = \frac{115}{134} \cdot \frac{n_1}{1050} \Rightarrow n_1 = 1326 \text{ rpm}$

Now for the efficiency:

$\eta = \frac{P_{out}}{P_{in}} * 100\%$

for the input: $P_{in} = (35)(120) \Rightarrow P_{in} = 4200W$

for the output: $P_{out} = P_{conv} - (P_{core} + P_{mech}) \Rightarrow$ Always put in mind the power flow diagram.

$\Rightarrow P_{conv} = E I_a = (107.4)(35)$

$\Rightarrow P_{conv} = 3759W$

$P_{core} = 200W$

$P_{mech} = 240W @ n = 1050 \text{ rpm}$

$P_{mech} = ?W @ n = 1326 \text{ rpm}$

so $P_{mech} = 240 \left(\frac{1326}{1050}\right)^3 = 483.4W$

Now substituting: $\Rightarrow P_{out} = 3759 - (483.4 + 200) \Rightarrow P_{out} = 3075.6W$

so $\eta = \frac{P_{out}}{P_{in}} * 100\% \Rightarrow \eta = 73.2\%$

*** Always Draw the circuit before you start to solve.


* Load Characteristic of DC Motors:

This give Relationship between tw output of the Motor.
 ⇒ speed (n or ω) & Torque.

* Illustration:

For example, consider shunt Motor:

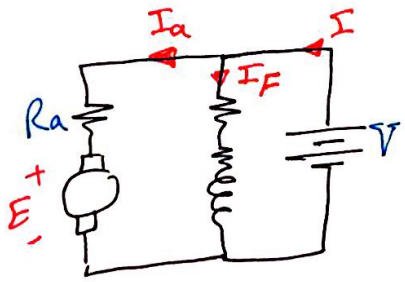$E = V - I_a R_a$; $E = K \phi \omega$, $T = K' \phi I_a$




Continue.

⇒ Substitute ②, ③ into ①:

$$K\phi\omega = V - \frac{I}{K'\phi} R_a \Rightarrow \therefore$$

$$\omega = \left(\frac{V}{K\phi} \right) - \left(\frac{R_a}{KK'\phi^2} \right) T$$

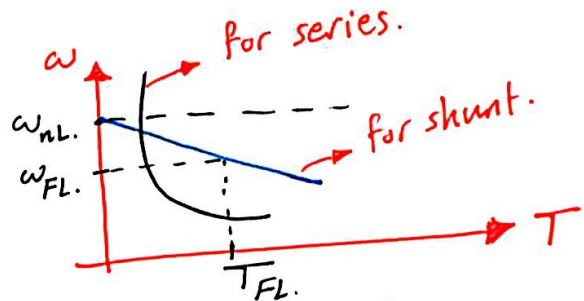V is constant ⇒ I is constant ⇒ φ is constant.
 also I_f constant.



when T increased ⇒ ω decreased.

* speed Regulation:

$$SR = \frac{\omega_{NL} - \omega_{FL}}{\omega_{FL}}$$


* Solution of Armature Reaction Problem:

• To illustrate Consider a DC Generator:

Armature Reaction: Intersection between φ_a & φ. where φ ∝ I_a

Solution → is to eliminate or Reduce φ_a.

By using for example: Interpoles.

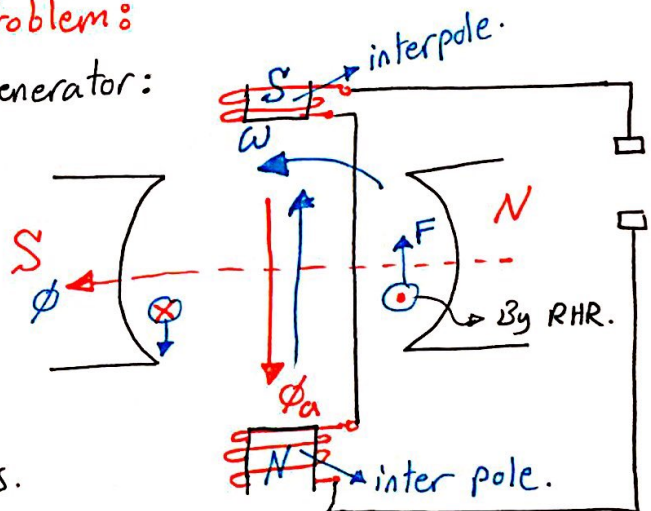

⇒ These interpoles generate flux opposing φ_a.

hence they are connected in series with Armature windings.


* polarity of interpole = Polarity of adjacent Main pole when moving in the direction of Rotation.

$$* \text{Armature Resistance} = R_a + \text{interpole resistance.}$$

• For DC Motor:

The same procedure for DC generator.

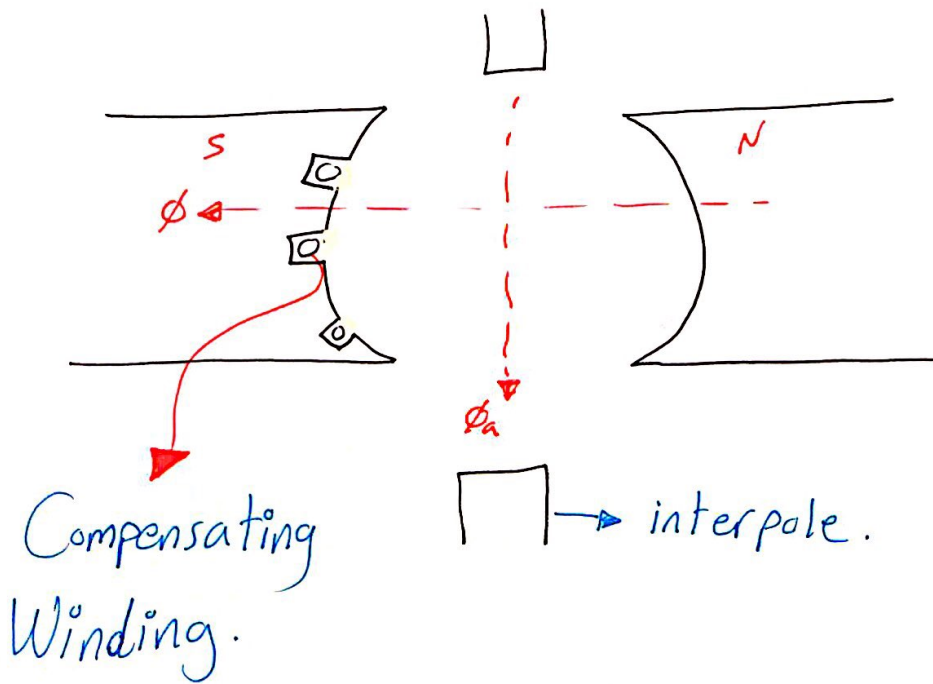⇒ * Some times it could be with Compensating winding. 98



* Here in this case, the total armature resistance would be as follows:

$$\text{Armature Resistance} = R_a + \text{interpole Winding} + \text{Compensating Winding}.$$

* End of Material. *

😊 Best of Luck. 😊