


Machines2

Summer017



Dr. **E**yad **A**bu **A**l**F**ilat ⚡

⚡ By: **M**hmd **A**buhashieh

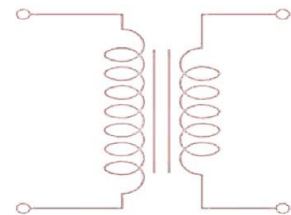

Powerunit-ju.com

Electrical Machines II

Dr. Eyad Abu Al-Feilat.

Summer
Semester
2017

Note book

By. Mohammad Abu Hashia.



Electrical Machines :

* Review :

synchronous generators. } 3-ph AC machines.
 sync. motors. }



induction motors } 3-ph AC machines.
 induction gen. }

1-ph induction motor {
 → split-phase.
 → capacitor start.
 → capacitor run.
 → capacitor start capacitor run.

special purpose machines {
 → Reluctance motor.
 → stepper motor.
 → universal → DC AC
 → DC motors → Brushless.


* Machine (M/C) : Energy Conversion Device.

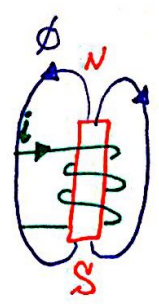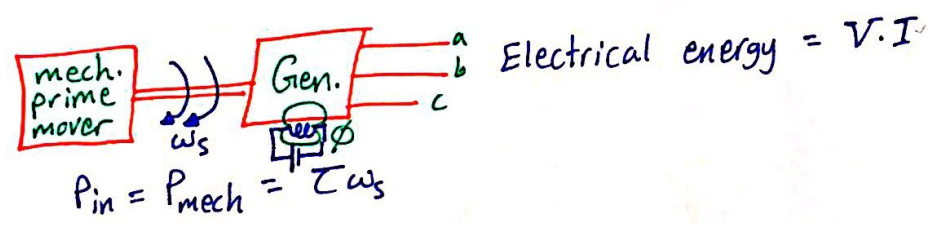* Electrical machines {
 → motors.
 → generators.



** Any current will generate a magnetic field.

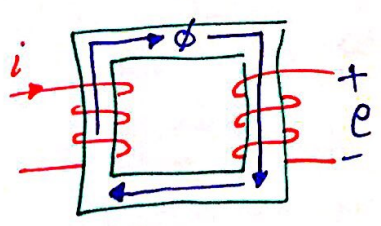** Transformer Action: if the flux cut or link another conductor it will induce a voltage in it.



$$e = -N \frac{d\phi}{dt} \quad \text{if } \phi = \phi_m \sin \omega t$$

$$\Rightarrow e = N \phi_m \omega \cos \omega t$$

$$E_m = N \phi_m \omega \Rightarrow E_m = \frac{N \phi_m (2\pi f)}{\sqrt{2}}$$




$$\Rightarrow E_m = 4.44 N_{ph} \phi f$$

$B = \mu H \Rightarrow H = \frac{B}{\mu}$



for material with small $\mu \Rightarrow$ need High H to magnetized.
 for material with High $\mu \Rightarrow$ need Low H to magnetized.


* Electrical cycle = $\frac{P}{2}$ * mechanical cycle. ; where $P \equiv$ Number of poles.

Y-Connection:

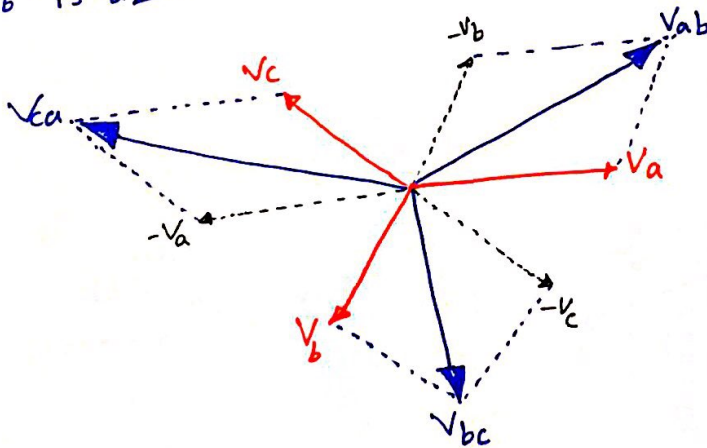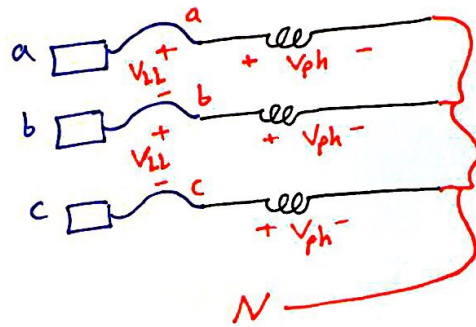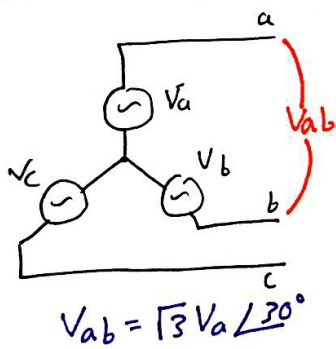

Δ -Connection: (Two ways of connection)

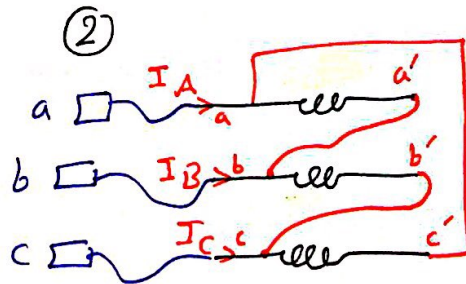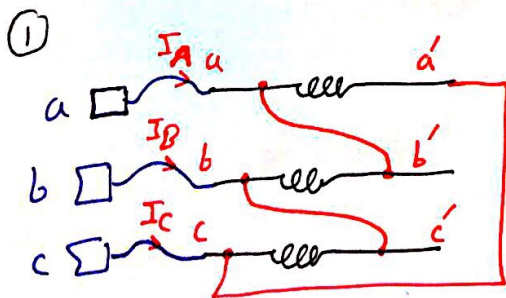


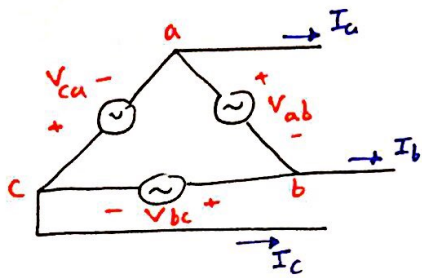


$V_{LL} = V_{ph}$

$|I_L| = \sqrt{3} |I_{ph}|$

↳ for I_L & I_{ph} lead or lag depends on the way of connection.



* for way ①:

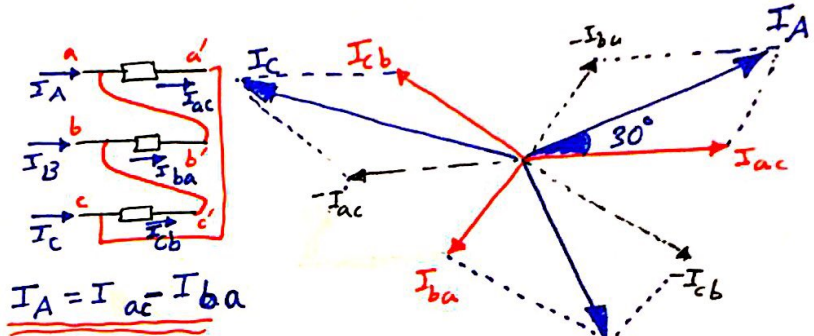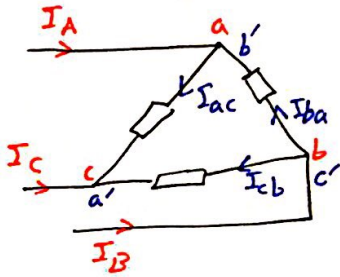


$I_A = I_{ac} - I_{ba}$

Here: I_L leads I_{ph} By 30° .

* for way ②:

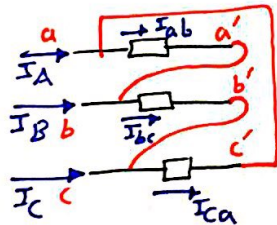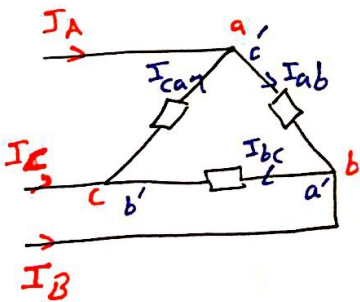


$I_A = I_{ab} - I_{ca}$

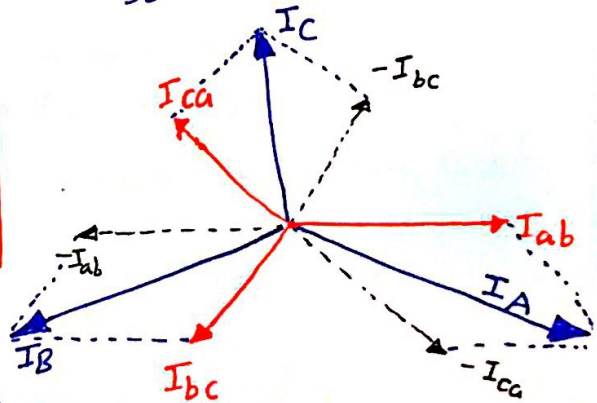


Here: I_L lags I_{ph} By 30° .
"Default situation".


* In loaded stator:

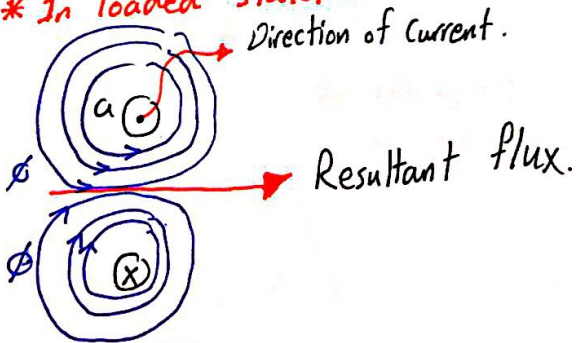

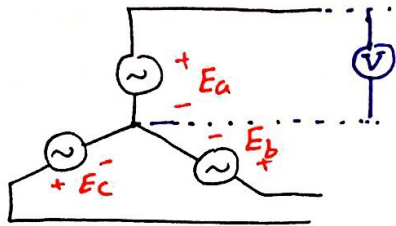⇒ Determine the direction of flux by RHR.



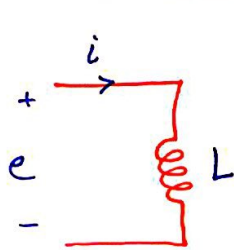we can measure E_a if only it was open circuit.



$$L = \frac{\lambda}{i} = \frac{N\phi}{i}$$

$$e = N \frac{d\phi}{dt} = L \frac{di}{dt}$$

if $i(t) = I_m \sin \omega t$


Then:

$$e = (\omega L) I_m \cos \omega t$$


$X_L \equiv$ Reactance.

$$\Rightarrow e = X_L I_m \cos \omega t$$

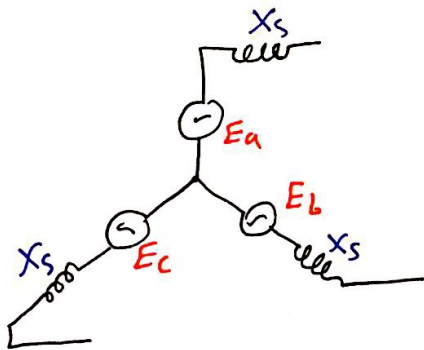* We add sync. reactance to the 3-ph gen.:







* per-phase circuit:

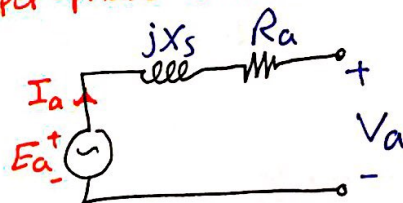

$$V_a = E_a - I_a (R_a + jX_s)$$

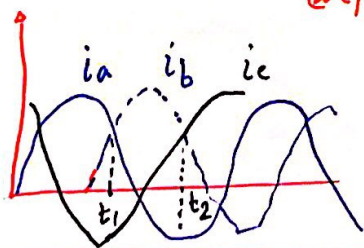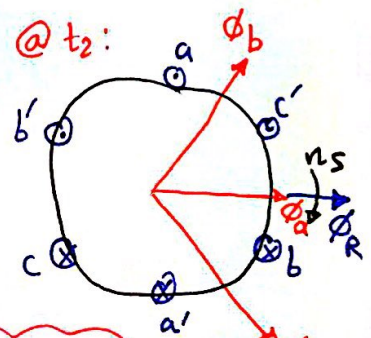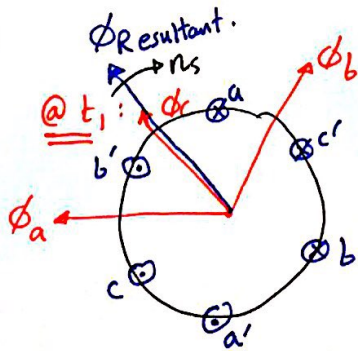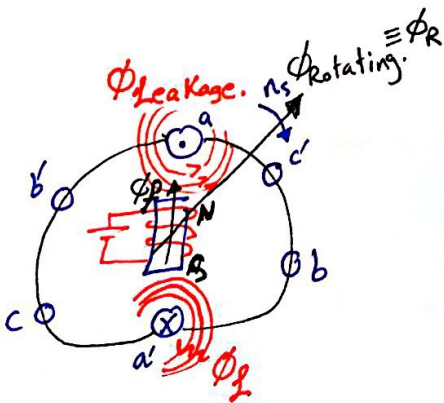$\hookrightarrow V_a$ is Highest when open circuit.



@ t_1 , i_a & i_b +ve.
 i_c -ve.


$$n_s = \frac{120}{p} f \text{ rpm}$$

$$f_e = \left(\frac{p}{2}\right) f_m$$

\rightarrow # of poles

- * E_f leads V_t when the ^{reactive} power coming from the machine toward the terminals. (+ve δ°) \Rightarrow gen. case.
- * E_f lags V_t when the ^{reactive} power coming from the terminals toward the machine. (-ve δ°) \Rightarrow motor case.
- * Reactive power Bi-directional.
- * Active Power Uni-directional "Always from the machine toward the terminals."

**** Power flow diagram:**

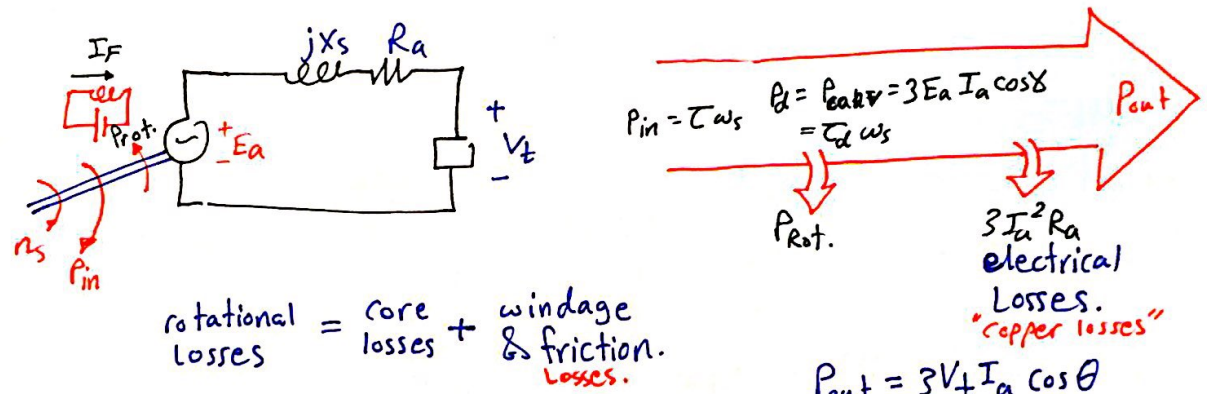

rotational losses = core losses + windage & friction losses.

- $\delta^\circ \equiv$ Angle between E_a & V_t .
- $\theta^\circ \equiv$ Angle between V_t & I_a .
- $\gamma^\circ \equiv$ Angle between E_a & I_a .

$\omega_s = \frac{2\pi N_s}{60}$ rad/s

$\eta = \frac{P_{out}}{P_{in}}$

**** Evaluation of parameters:**

*** DC Test:**

$R_{ac} > R_{dc} \Rightarrow R_{ac} = (1.1 - 1.5) R_{dc}$
 given. \Rightarrow if it is NOT given assume $R_{ac} = R_{dc}$.


in Y-connection:

$2R_a = \frac{V_{dc}}{I_{dc}} \Rightarrow R_a = \frac{1}{2} \frac{V_{dc}}{I_{dc}}$

in Δ -connection:

$\frac{2R_a}{3} = \frac{V_{dc}}{I_{dc}} \Rightarrow R_a = \frac{3}{2} \frac{V_{dc}}{I_{dc}}$

* O/C & S/C Tests:

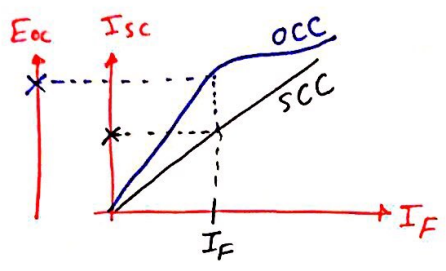


we obtain Z_s :
 $Z_s = \frac{E_a}{I_{sc}}$ → phase voltage.

* Modes of operation of sync. Gen.:


- 1) Stand alone (Isolated) ⇒ off-Grid.
- 2) S.G connected to infinite Bus ⇒ ON-Grid

* Stand Alone:

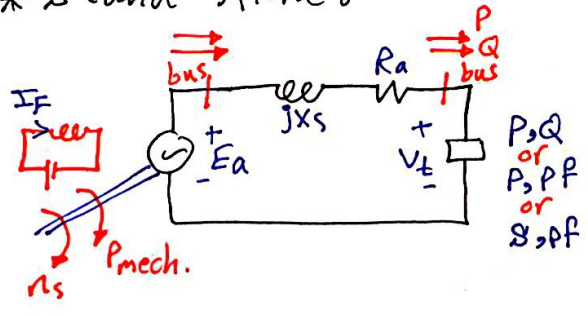

for. ex.: $f = 50\text{Hz}$
 $p = 2$
 $\Rightarrow n_s = 3000\text{rpm}$

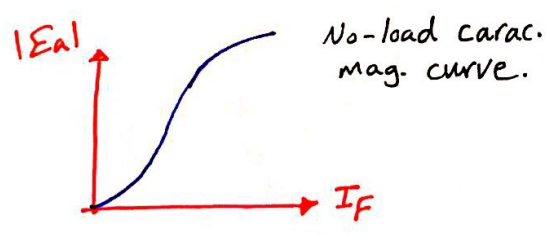$E_a = 4.44 f N \phi$
 $n_s = \text{constant}, f = \text{constant}$
 $E_a \propto I_f$
 $E_a = V_t + I_a (R_a + jX_s)$



@ No-load: $|V_t| = |E_a|$
 $V_t = E_a - I_a (R_a + jX_s)$
 Graph showing terminal voltage V_t versus load current $I_L = I_a$ for different power factors: lead PF, 1.0 PF, and lag PF. The rated voltage is indicated by a dashed line. The full load current I_{FL} is marked on the x-axis.
 There is three cases for it.

* Pure resistive load:


$$V_t = |E_a| \angle \delta^\circ - |I_a| \angle \theta (R_a + jX_s)$$

* Reactor: we mean by reactor ⇒ Inductor.

* if a fault occur at the load:

we want small fault current so that they use bigger synchronous impedance. (To reduce the fault current if it is existed).

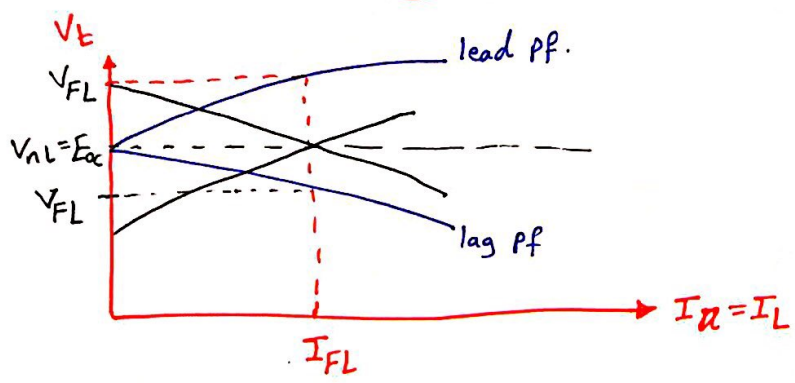
** $VR_{FL} \% = \frac{V_{nl} - V_{tfl}}{V_{tfl}} * 100\%$




** if $|Ea| > |Vt| \Rightarrow$ we say: over excited generator.
 \Rightarrow lagging pf (supply VAR).

** if $|Ea| < |Vt| \Rightarrow$ we say: under excited generator.
 \Rightarrow Leading pf (absorbe VAR).

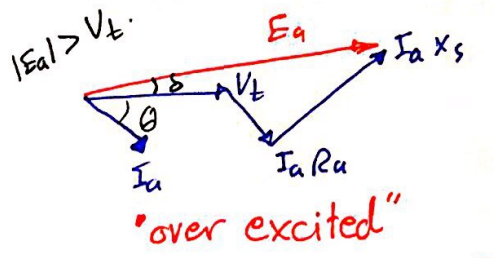
* Ea could be obtained: from $Ea = Vt + Ia(Ra + jXs)$
 OR as follows:



\Rightarrow

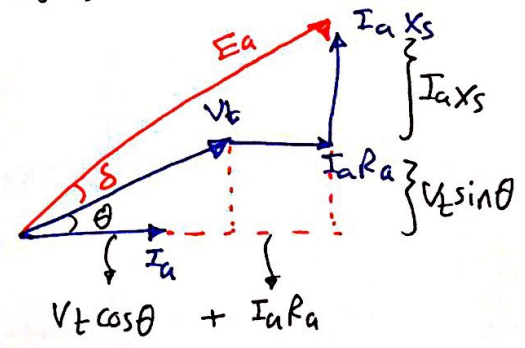


$\Rightarrow |Ea| = \sqrt{(Vt \cos \theta + IaRa)^2 + (Vt \sin \theta + IaXs)^2}$ "lagging case".


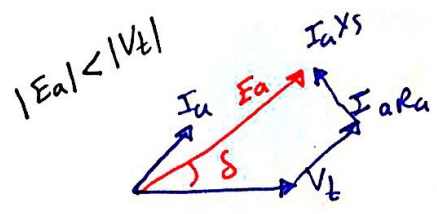


\Rightarrow

$|Ea| = \sqrt{(Vt \cos \theta + IaRa)^2 + (Vt \sin \theta - IaXs)^2}$ "leading case".

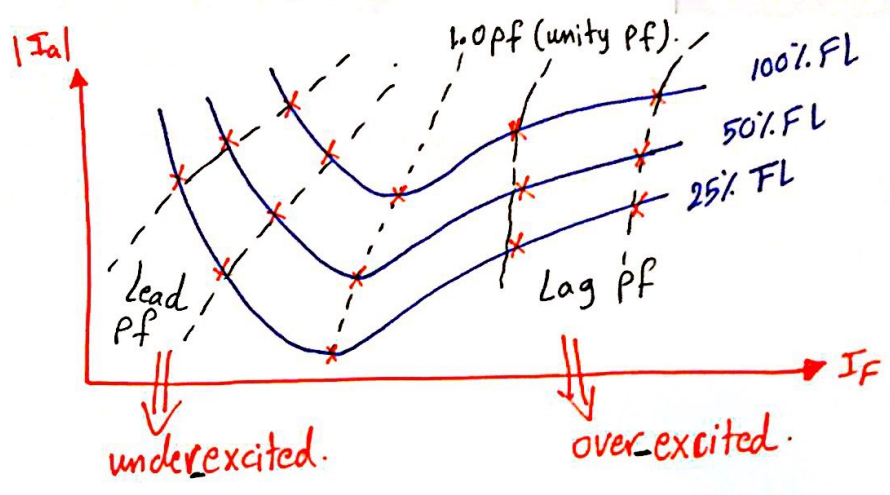

Example (2) in slides:

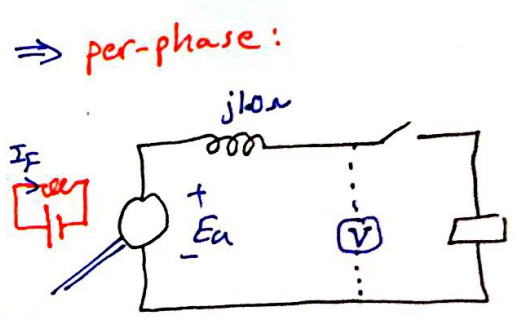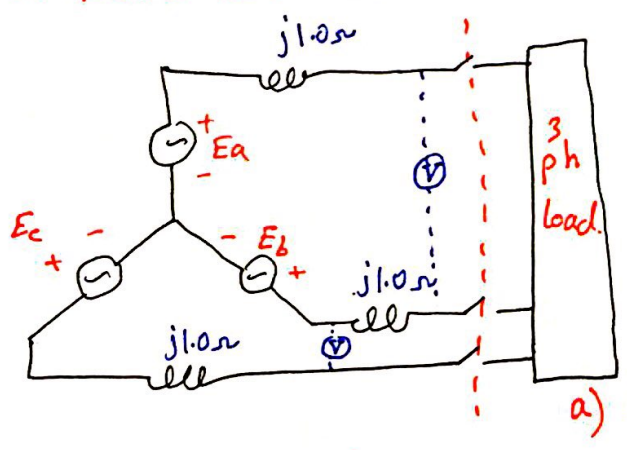

a) $\frac{120f}{P} = n_s = \frac{120 * 60}{6} = 1200 \text{ rpm.}$

b)

P	ns	
	50Hz	60Hz
2	3000	3600
4	1500	1800
6	1000	1200
8	750	900
⋮	⋮	⋮

$|E_a| = \frac{440}{\sqrt{3}} = 277 \text{ volt.}$
 for 0.8 pf lag:
 $V_t = E_a - jX_s I_a = 277 \angle \delta - 60 \angle -36.87^\circ (1 \angle 90^\circ)$

Two unknown variables, so we use the equation:

$$|E_a| = \sqrt{(V_t \cos \theta + I_a R_a)^2 + (V_t \sin \theta + I_a X_s)^2}$$


$$\Rightarrow (277)^2 = (V_t * 0.8 + 60 * 0)^2 + (V_t * 0.6 + 60 * 1)^2$$

solve for V_t : $V_t = 236.8 \text{ volt}$ phase voltage.

$V_t = \sqrt{3} (236.8) \Rightarrow V_t = 410 \text{ volt.}$ line voltage

⇒ Always make the answers line to line values.

Continue. →

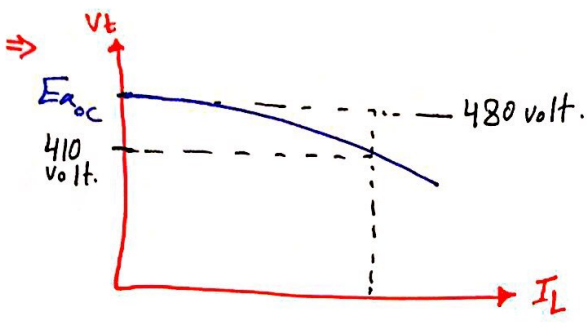

Now @ pf=1:
 $\Rightarrow \theta = 0^\circ$ $|Ea| = 277$ volt.

Do the same:

$$\Rightarrow \begin{cases} V_t = 270.4 \text{ volt} \\ V_t = 468.4 \text{ volt} \end{cases}$$

Now for pf=0.8 Leading:


$$\Rightarrow \theta = 36.87^\circ$$

$$|Ea| = \sqrt{(V_t \cos \theta)^2 + (V_t \sin \theta + I_a X_s)^2}$$

solving:

$$\begin{cases} E_t = 308.8 \text{ volt} \\ V_t = 535 \text{ volt} \end{cases}$$

c) $S_{3-ph} = \sqrt{3} V_{LL} I_L = 49.9 \text{ KVA}$

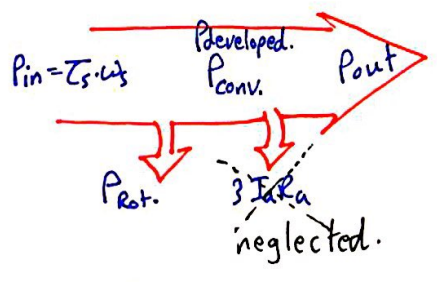

for 0.8 pf lagging:

OR $P_{out} = \sqrt{3} V_t \times 60 \times 0.8$
 $P_{out} = 3 V_p I_a \cos \theta = 34.1 \text{ KW}$

$$P_{in} = P_{out} + \text{elec.} + \text{mech.} + \text{core.} = 36.6 \text{ KW}$$

$$\Rightarrow \eta = \frac{P_{out}}{P_{in}} \times 100\% \Rightarrow \eta = 93.2\%$$

$$\omega_m = \frac{2\pi n_s}{60} = \frac{2\pi (1200)}{60} \Rightarrow \omega_m = 125.7 \text{ rad/sec}$$

d) $T_{app} = \frac{P_{in}}{\omega_m} = \frac{36.6 \text{ K}}{125.7} \Rightarrow T_{app} = 291.2 \text{ N.m}$; $T_{ind} = \frac{P_{conv}}{\omega_m} = \frac{34.1 \text{ K}}{125.7} \Rightarrow T_{ind} = 271.3 \text{ N.m}$

e) $VR\% = \frac{V_{nl} - V_{fl}}{V_{nl}} \times 100\%$

Leading pf: $VR = -10.3\%$


unity pf: $VR = 2.6\%$

Lagging pf: $VR = 17.1\%$


* Sync. Gen. on infinite bus

Infinite bus \equiv means constant voltage & constant frequency.

$$R_a \ll X_s$$

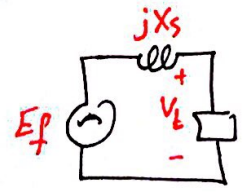
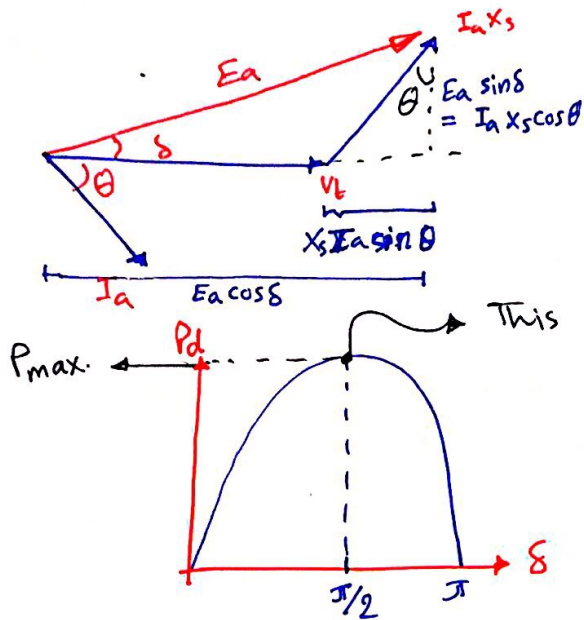
$$\begin{cases} E_f = V_t + j I_a X_s \\ P = 3 V_t I_a \cos \theta \\ Q = 3 V_t I_a \sin \theta \end{cases}$$



$$\Rightarrow E_a \sin \delta = I_a X_s \cos \theta$$

$$P_{out} = P_d = 3 V_t I_a \cos \theta$$

$$\Rightarrow P_{out} = P_d = 3 \frac{V_t E_a \sin \delta}{X_s}$$

This Called: "steady state stability" limit.

$$P_{max} = \frac{3 V_t E_a}{X_s} @ \delta = 90^\circ$$

$$\Rightarrow E_a \cos \delta = V_t + I_a X_s \sin \theta$$

$$(E_a \cos \delta - V_t) = I_a X_s \sin \theta$$

$$3 V_t \frac{1}{X_s} (E_a \cos \delta - V_t) = 3 I_a \sin \theta$$

$$\Rightarrow 3 V_t I_a \sin \theta = 3 \left[\frac{E_a V_t \cos \delta}{X_s} - \frac{3 V_t^2}{X_s} \right]$$


$$\Rightarrow Q = \frac{3 V_t}{X_s} [E_a \cos \delta - V_t]$$

if $E_a \cos \delta > V_t$
overexcited
Q is supplied.
Lag Pf.

if $E_a \cos \delta < V_t$
under excited.
Q is absorbed.
Lead Pf.

* Tutorial Solutions:

Q1 a) $|V_t|_{nl} = |E_a| = 4.44 f N \phi$

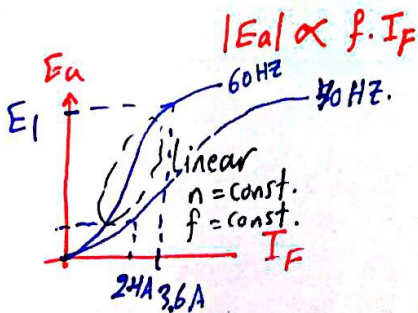

$$\frac{E_{a1}}{E_{a2}} = \frac{f_1 I_{f1}}{f_2 I_{f2}}$$

$$\Rightarrow E_{a2} = \frac{I_{f2} f_2 E_{a1}}{f_1 I_{f1}}$$

$$= \frac{(40)(2.4)(360)}{(60)(3.6)} \Rightarrow |E_{a2}| = 160 \text{ V}$$

Q1) b) $|V_{tNL}| = |E_a| = 620 \text{ volt}$
 $f = 60 \text{ Hz}$

if $\phi_2 = 0.85 \phi_1 \Rightarrow I_{F2} = 0.85 I_{F1}$ II
 $n_2 = 1.1 n_1 \Rightarrow f_2 = 1.1 f_1$

$\Rightarrow f_2 = 1.1 (60) = 66 \text{ Hz}$


$|E_2| = \frac{f_2 I_{F2}}{f_1 I_{F1}} E_1 = (1.1)(0.85)(620) \Rightarrow \boxed{E_2 \approx 580 \text{ volt}}$

Note: if the # of poles & frequency weren't given \Rightarrow we write the table for 50Hz & 60Hz & we find # of poles from the given (n_s).

Q2) assume P wasn't given:


P	n_s (rpm)	
	50Hz	60Hz
2	3000	3600
4	1500	1800
6	1000	1200
8	750	900

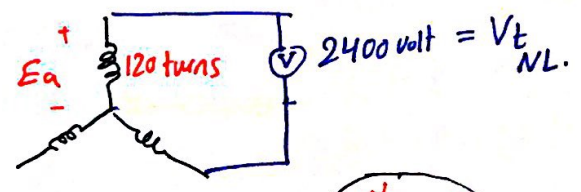$n_s = \frac{120}{P} f$
 \rightarrow so $f = 60 \text{ Hz}$ & $P = 8$




$E = 4.44 K_w f N \phi$

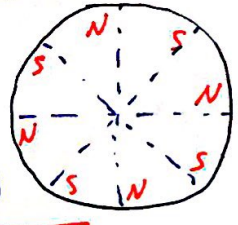$\phi = \frac{2400/\sqrt{3}}{4.44(0.9)(120)(60)}$




$\Rightarrow \boxed{\phi = 48.2 \text{ mWb}}$

Q3)

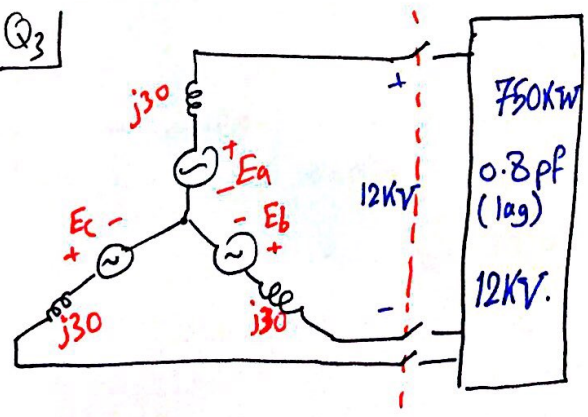

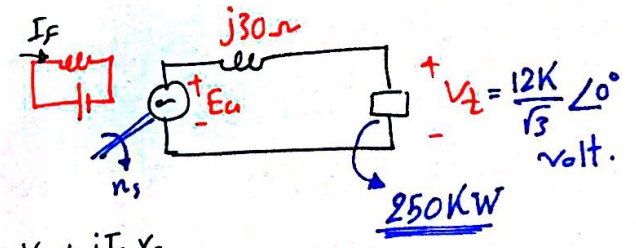$VR\% = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$



$E_a = V_L + j I_a X_s$
 $= \frac{12000}{\sqrt{3}} \angle 0^\circ + (j30) \left(\frac{9375K}{\sqrt{3}(12K)} \right)$ since Y: $I_L = I_{ph}$



$\theta = \cos^{-1}(0.8) = 36.87^\circ$

$P = S \cdot pf$


$\Rightarrow \boxed{S = 9375KVA}$

$I_a = 45.1 \angle -36.9^\circ$
 $E_a = 7816 \angle 7.9^\circ \text{ volt}$
 $|E_a|_{LL} = 13.5 \text{ KV}$
 $\Rightarrow VR = \frac{13.5 - 12}{12} \times 100\%$
 $\Rightarrow \boxed{VR = 12.5\%}$


⇒ phasor diagram for Q_3 :

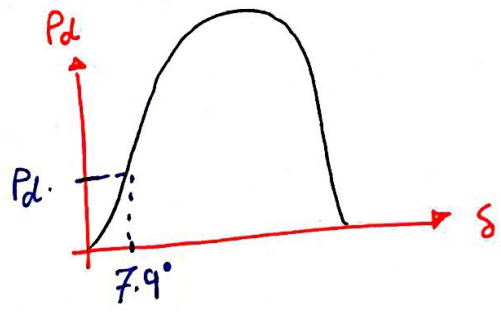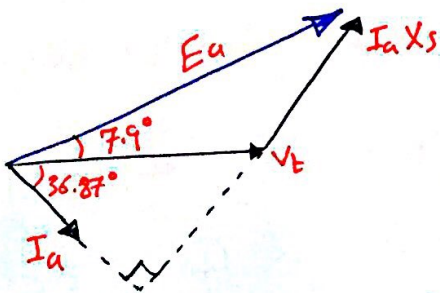


Q4 @ PF = 1:
 $I_a = 524.9 \angle 0^\circ A$
 $E_a = 6412.7 \angle 3.1^\circ \text{ volt.}$
 $|E_a|_{LL} = 11.1 K \text{ volt.}$
 ⇒ $VR = 0.9\%$

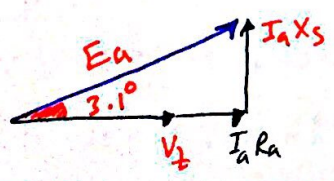


@ 0.8 pf lag:
 $I_a = 656.1 \angle -36.9^\circ A.$
 $E_a = 6670.4 \angle 2.6^\circ \text{ volt.}$
 $|E_a|_{LL} = 11.5 K \text{ volt.}$
 ⇒ $VR = 4.55\%$

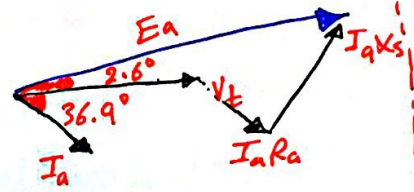

@ 0.8 pf lead:
 $I_a = 656.1 \angle +36.9^\circ A$
 $E_a = 6155.4 \angle 3.6^\circ \text{ volt.}$
 $|E_a|_{LL} = 10.7 K \text{ volt.}$
 ⇒ $VR = -2.73\%$

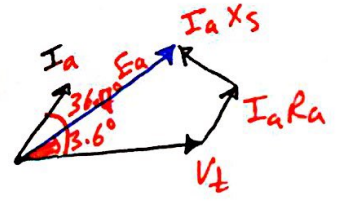

Q5

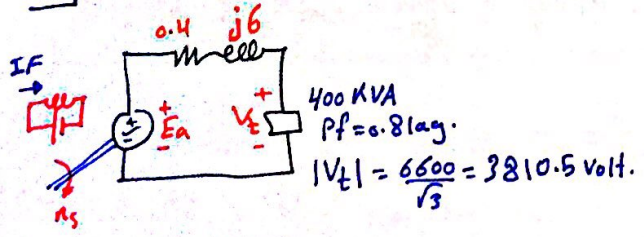


$$|I_a| = |I_L| = \frac{S_{3\phi}}{\sqrt{3} V_L} = \frac{1200 \times 10^3}{\sqrt{3} (6600)} = 105 A.$$

$$\Rightarrow E_a = V_t + I_a (R_a + jX_s) = 3810.5 \angle 0^\circ + 105 \angle -36.9^\circ (0.4 + j6)$$

$$E_a = 4949.4 \angle 6.6^\circ \text{ volt.}$$

$$\Rightarrow |E_a|_{LL} = 7960 \text{ volt.}$$

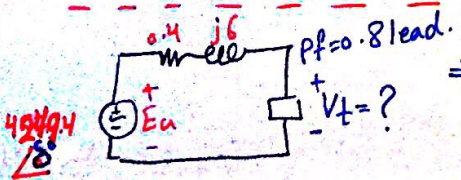

$$\Rightarrow V_t = E_a - I_a (R_a + jX_s) \text{ Two unknowns.}$$

$$\Rightarrow |E_a|^2 = (V_t \cos \theta + I_a R_a)^2 + (V_t \sin \theta - I_a X_s)^2$$

$$(4949.4)^2 = (V_t \cdot 0.8 + 105 \times 0.4)^2 + (V_t \cdot 0.6 - 105 \times 6)^2$$


$$\Rightarrow |V_t| = 4652.7 \text{ volt.} \Rightarrow |V_t|_{LL} = 8058.7 \text{ volt.}$$

Q6

O/C Test: $I_f = 125A, V_{t_{oc}} = 8000V, n = n_s$.

S/C Test: $I_f = 125A, I_{sc} = 800A, n = n_s$.

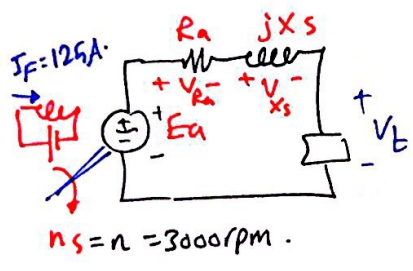
@ rated Full-load: $V_{drop} = V_{Ra} = 3\%$ of the rated phase voltage.



$$|Z_s| = \frac{|E_{oc}|_{ph}}{I_{sc}}$$

$$|Z_s| = \sqrt{R_a^2 + X_s^2} = 5.7 \Omega$$
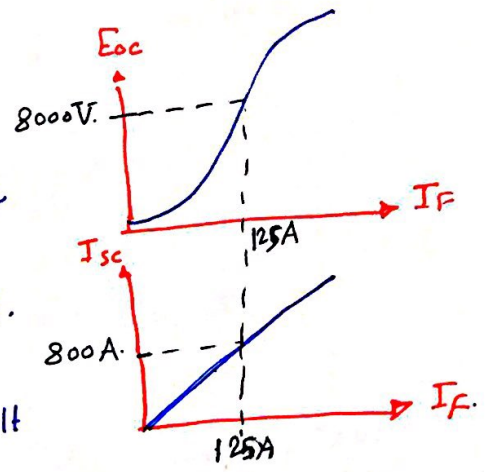
$$I_{a_{FL}} = \frac{6000 \times 10^3}{\sqrt{3} (6.6) \times 10^3} = 524.8A$$



$$\Rightarrow V_{real} = R_a I_{a_{FL}} = \frac{3}{100} \times \frac{6600}{\sqrt{3}} = 114.3 \text{ volt}$$

$$\Rightarrow R_a = \frac{114.3}{524.8} \Rightarrow R_a = 0.22 \Omega$$

$$\Rightarrow X_s = \sqrt{|Z_s|^2 - R_a^2} \Rightarrow X_s = 5.69 \Omega$$

$$VR = \frac{|E_a| - |V_t|}{|V_t|} \times 100\%$$

$$\Rightarrow VR = \frac{10650 - 6600}{6600} \times 100\% \Rightarrow VR = 61\%$$


$$\Rightarrow E_a = \frac{6600}{\sqrt{3}} \angle 0^\circ + 524.8 \angle -36.9^\circ (0.22 + j5.69)$$

$$\Rightarrow E_a = 6148 \angle 22.1^\circ \text{ volt.}$$

$$|E_a|_{LL} = 10650 \text{ volt.}$$

* For $X_{s_{pu}}$: $X_{base} = \frac{(kV)^2}{S_{3\phi}} = \frac{(6.6)^2}{6} = 7.26 \Rightarrow X_{s_{pu}} = \frac{X_{s_{\Omega}}}{X_{base}} = 78.4\%$

Q7


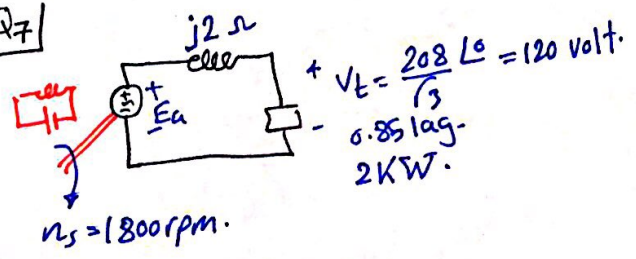


$$\Rightarrow E_a = V_t + j I_a X_s$$

$$|I_a| = \frac{6000}{\sqrt{3} \times 208 \times 0.85} = 19.6A$$

$$\Rightarrow E_a = 120 \angle 0^\circ + 19.6 \angle -31.8^\circ \times 2 \angle 90^\circ$$

$$|E_a|_{LL} = 250.5 \text{ volt.} = 144.6 \angle 13.8^\circ \text{ volt.}$$

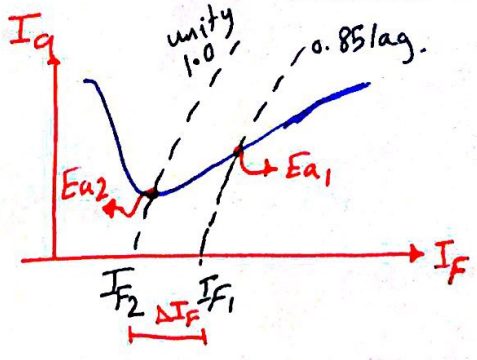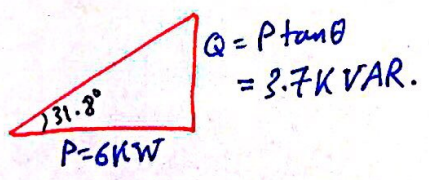


Continue.

$\Rightarrow E_a \propto I_f$ $n = \text{const.}$ $\Rightarrow E_{a2} = 120 \angle 0^\circ + 16.7 (2 \angle 90^\circ)$

$\Rightarrow E_{a2} = 124.8 \angle 15.6^\circ$


$I_a = \frac{6000}{\sqrt{3} (208) (1)} = 16.7 \text{ A}$

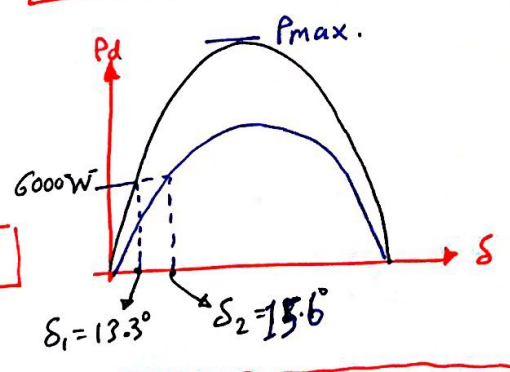$\frac{\Delta I_f}{I_{f1}} = \frac{I_{f2} - I_{f1}}{I_{f1}} = \frac{E_{a2} - E_{a1}}{E_{a1}}$
 $= \frac{124.8 - 144.6}{144.6} \times 100\% = -13.8\%$




Q8

- find:
 a) E_a at rated conditions, $\text{Pf} = 0.8 \text{ Lag.}$?
 b) $I_{f2} = 1.2 I_{f1} \Rightarrow |E_{a2}| = 1.2 |E_{a1}|$
 find I_{a2}, Pf_2, Q_2 ?
 c) $I_{f3} = I_{f1}$ find $\text{max} = \frac{3V_t E_a}{X_s}$, Pf_3, I_{a3}, Q ?

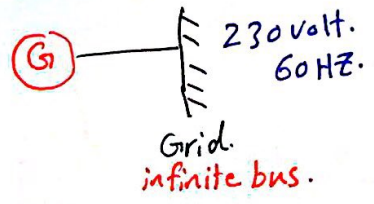


solutions:


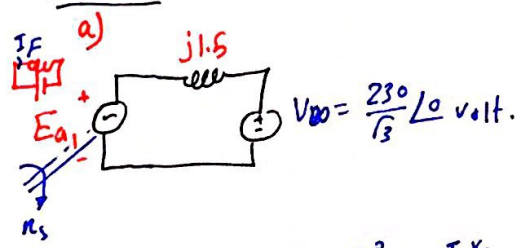


$E_a = V_t + j I_a X_s$ $|I_a|_{FL} = \frac{S_{3\phi}}{\sqrt{3} V_L} = 62.8 \text{ A}$
 $\Rightarrow I_{a1} = 62.8 \angle -36.9^\circ$

$E_{a1} = 132.8 \angle 0 + 62.8 \angle -36.9^\circ * 1.5 \angle 90^\circ$
 $\Rightarrow E_{a1} = 203.8 \angle 21.7^\circ \text{ volt}$
 $|E_{a1}|_{LL} = 353 \text{ volt}$

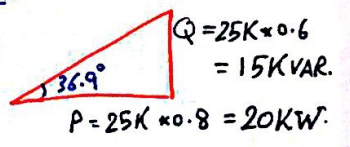

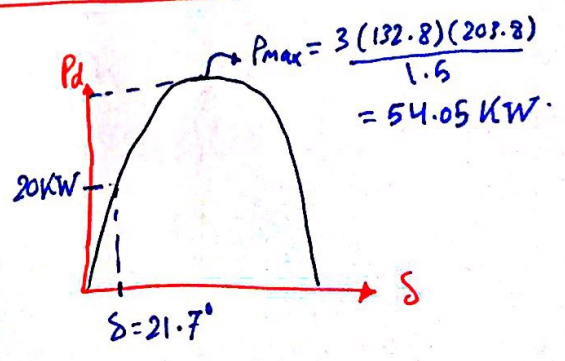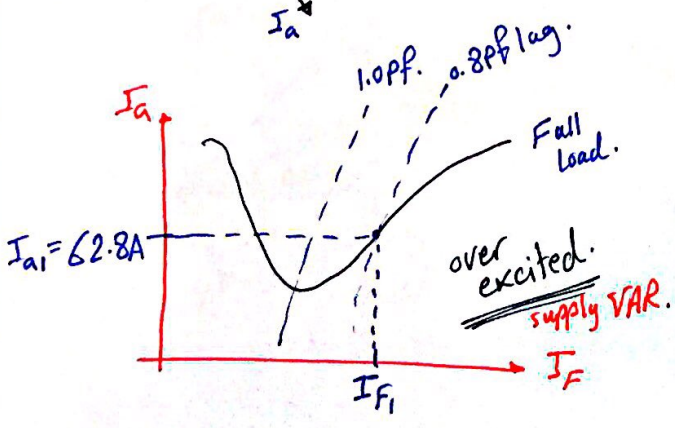$Q = 25 \text{ K} * 0.6 = 15 \text{ KVAR}$
 $P = 25 \text{ K} * 0.8 = 20 \text{ KW}$



$P_d = \frac{3V_t E_a}{X_s} \sin \delta = P_{out} = 3V_t I_a \cos \theta$

b) $P_{d1} = P_{d2}$
 $E_{a2} = 1.2 E_{a1} = \boxed{244.6 \text{ volt.}}$

$\Rightarrow P_{d1} = P_{d2} = 20 \text{ kW} = \frac{3 (132.8) (244.6)}{1.5} \sin \delta_2$ 15

$\Rightarrow \boxed{\delta_2 = 17.9^\circ}$

$\Rightarrow \underline{\underline{E_a = 244.6 / 17.9^\circ}}$

for I_{a2} :

$I_{a2} = \frac{E_{a2} - V_t}{jX_s} \Rightarrow \boxed{I_{a2} = 83.4 \angle -53.1^\circ}$

$P_{d1} = P_{d2} \Rightarrow \frac{3V_t E_{a1} \sin \delta_1}{X_s} = \frac{3V_t E_{a2} \sin \delta_2}{X_s} = 1.2 E_{a1} \sin \delta_2 \Rightarrow \boxed{\sin \delta_1 = 1.2 \sin \delta_2}$

we could also use it to find δ_2 .

for Q:


method (1):

$Q_2 = 3V_t I_{a2} \sin \theta = P_2 \tan \theta_2 = 26.5 \text{ KVAR.}$


method (2):

$Q_2 = \frac{3V_t}{X_s} [E_{a2} \cos \delta_2 - V_t] = 26.5 \text{ KVAR.}$

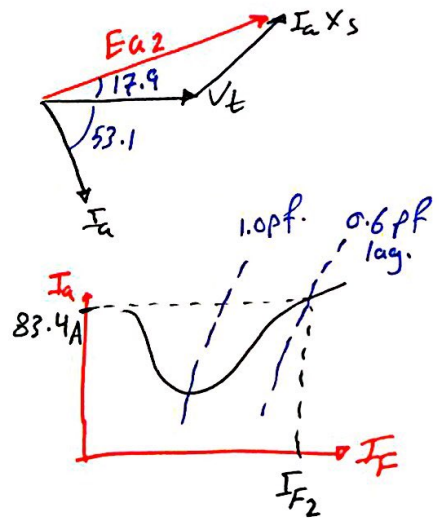for pf: $\Rightarrow \text{pf}_2 = \cos(53.1^\circ) = 0.6 \text{ lagging.}$



c)

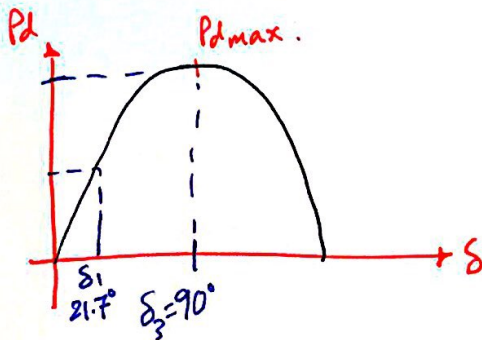


$|E_{a3}| = |E_{a1}| = 203.8 \text{ volt}$

$\Rightarrow \boxed{E_{a3} = 203.8 \angle +90^\circ}$

$\Rightarrow I_{a3} = \frac{E_{a3} - V_t}{jX_s} = \frac{203.8 \angle 90^\circ - 132.8 \angle 0^\circ}{1.5 \angle 90^\circ} = \boxed{162.2 \angle 33.1^\circ \text{ A}}$

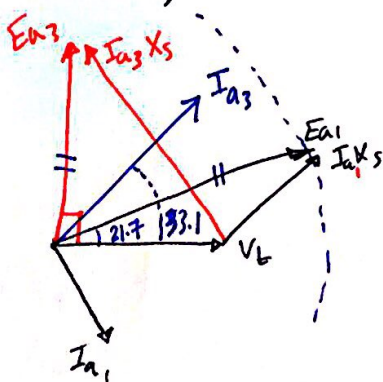$\text{pf}_3 = \cos(33.1) = 0.838 \text{ leading.}$



$Q_3 = 3 V_t I_{a3} \sin \theta$
 $= 3 (132.8) (162.2) \sin(-33.1^\circ)$

$\boxed{Q_3 = -35.3 \text{ KVAR}}$

underexcited
 \Rightarrow absorbing Q.

\Rightarrow continue

⇒ if I_F is reduced without using steady state stability 16
 Limit (until reach 20kW).
 Find I_{a4} & P_{F4} & Q_4 ?

$$I_a = \frac{E_{a4} - V_t}{jX_s}$$

we have to find E_{a4} ?!

$$P_{max} = 20kW = \frac{3(132.8) E_{a4}}{1.5}$$

$$\text{so } |E_{a4}| = 75.3 \text{ volt.}$$

$$\Rightarrow \boxed{E_{a4} = 75.3 \angle 90^\circ \text{ volt.}}$$

Now for I_{a4} :
$$I_{a4} = \frac{(75.3 \angle 90^\circ) - (132.8 \angle 0^\circ)}{j1.5} \Rightarrow \boxed{I_{a4} = 101.8 \angle 60.4^\circ \text{ A}}$$


$$P_{F4} = \cos(60.4^\circ) \Rightarrow \boxed{PF = 0.494} \text{ leading.}$$

Now for Q_4 :

$$Q_4 = 3 V_t E_{a4} \sin \theta = 3(132.8)(101.8) \sin(-60.4) \Rightarrow \boxed{Q_4 = -353 \text{ KVAR}}$$

Q9) a)
$$P_{max} \Big|_{\delta=90^\circ} = \frac{3V_t E_a}{X_s} = \frac{V_{LL} E_{LL}}{X_s}$$
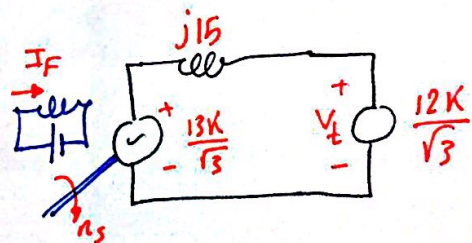
$$P_{max} = \frac{12 \times 13 \times 10^6}{15} = \boxed{10.4 \text{ MW.}}$$



$$\tau_{d_{max}} = \frac{P_{max}}{\omega_s} = \frac{60}{2\pi} \frac{P_{max}}{n_s}, \quad n_s = 1800 \text{ rpm.} \Rightarrow \boxed{\tau_{d_{max}} = 55.1 \text{ kN.m.}}$$

b)
$$I_a = \frac{E_a - V_t}{jX_s} = \frac{\frac{13k}{\sqrt{3}} \angle 90^\circ - \frac{12k}{\sqrt{3}} \angle 0^\circ}{15 \angle 90^\circ} \Rightarrow \boxed{I_a = 680.9 \angle 42.7^\circ \text{ A.}}$$

for PF:
$$PF = \cos(42.7^\circ) = \boxed{0.7349} \text{ leading.}$$

Q₁₀

$$I_a = \frac{\frac{2300}{\sqrt{3}} \angle 15^\circ - \frac{2300}{\sqrt{3}} \angle 0^\circ}{4 \angle 90^\circ}$$



$$\Rightarrow I_a = 86.6 \angle 7.5^\circ \text{ A.}$$

for pf: $pf = \cos(7.5) = 0.991$ leading.

$$P_{out} = \frac{3V_t E_a \sin \delta}{X_s} = 3V_t I_a \cos \theta$$

$$Q_{out} = \frac{3V_t}{X_s} [E_a \cos \delta - V_t] = 3V_t I_a \sin \theta$$

$$I_a |_{\delta=90^\circ} = \frac{\frac{2300}{\sqrt{3}} \angle 90^\circ - \frac{2300}{\sqrt{3}} \angle 0^\circ}{4 \angle 90^\circ} = 469.5 \angle 45^\circ \text{ A}$$

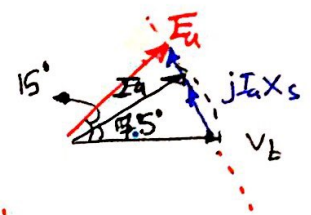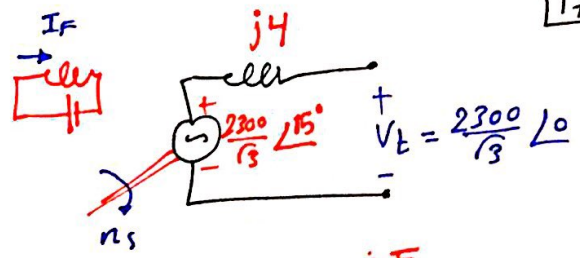


Solving:

$$P_{out} = 0.34 \text{ MW.}$$

$$Q_{out} = -45.03 \text{ KVAR.}$$

$$P_{max} = 1.32 \text{ MW.}$$


Q₁₁

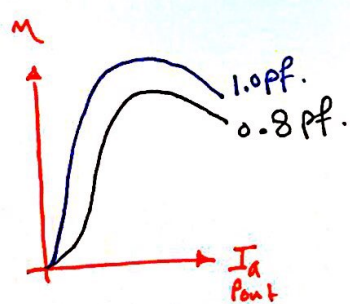

$$I_{aFL} = \frac{10 \times 10^6}{\sqrt{3} \times 12 \times 10^3} = 481.1 \text{ A.}$$

$$P_{sc} = 3I_a^2 R_a = 60 \text{ KW.}$$

$$P_{core} = 75 \text{ KW.}$$

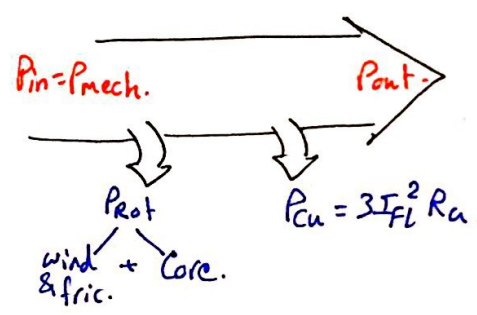


$$P_{out} = S_{rated} * pf = 8 \text{ MW}$$

$$P_{in} = P_{out} + P_{cu} + P_{rot} = P_{out} + \sum P_{losses}$$

$$\eta = \frac{P_{out}}{P_{in}} * 100\% \Rightarrow \eta = 97.6\%$$


Q₁₂

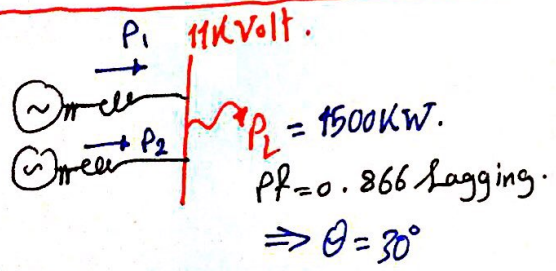

$$P_L = 500 \text{ KW.}$$

$$pf = 0.866 \text{ lagging.}$$

$$\Rightarrow \theta = 30^\circ$$

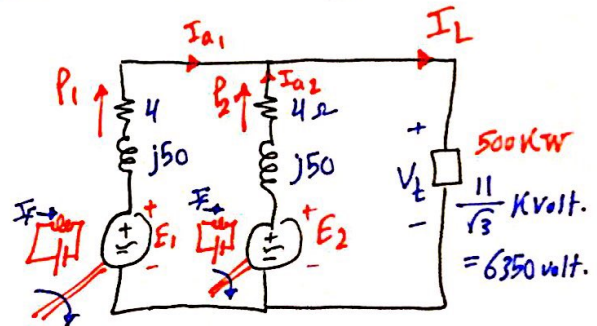

since they share the load equally:

$$P_1 = P_2 = \frac{P_L}{2}$$

continue.

$$\Rightarrow |I_L| = \frac{S_L}{\sqrt{3} V_{LL}} = \frac{P_L / \text{pf}}{\sqrt{3} V_{LL}} = \frac{1500 \text{ kW} / 0.866}{\sqrt{3} \times 11 \text{ kV}} = 90.9 \text{ A.}$$

$$\Rightarrow I_L = 90.9 \angle -30^\circ ; I_L = I_1 + I_2$$

$$P_1 = \sqrt{3} V_L I_1 \cos \theta_1 = \sqrt{3} V_L I_1 \cos \theta_1 = 750 \text{ kW} \Rightarrow \cos \theta_1 = \text{pf}_1 = 0.7873$$

$$\theta_1 = \cos^{-1}(0.7873) \Rightarrow \theta_1 = 38.1^\circ$$

lagging.

$$\text{So } I_2 = 90.9 \angle -30^\circ - 50 \angle -38.1^\circ \Rightarrow$$

$$I_2 = 42 \angle -20.3^\circ \text{ A.}$$

$$\text{pf}_2 = \cos(20.3) = 0.937$$

lagging.

Check for the answers by:

$$I_1 \cos \theta_1 \stackrel{?}{=} I_2 \cos \theta_2$$

$$50 \times 0.787 \stackrel{?}{=} 42 \times 0.937 \text{ (yes, equal each other).}$$

$$E_{a1} = V_t + I_{a1} (R_a + jX_s) = 6350 \angle 0 + 50 \angle -38.1^\circ (4 + j50)$$

$$\Rightarrow E_{a1} = 8258.5 \angle 12.9^\circ \text{ volt.}$$

$$\text{VR\%} = \frac{8258.5 - 6350}{6350} \times 100\%$$

$$\Rightarrow \text{VR\%} = 30.1\%$$

* * *

* Example on Δ -connection:

$V_{LL} = 480 \text{ v.}$, $P = 4$, $f = 60 \text{ Hz}$, Δ -connected S.G. has the o.c.c



shown below:

$$X_s = 0.1 \ \Omega / \text{ph.}$$

$$R_a = 0.015 \ \Omega / \text{ph.}$$



@ Full-load, $I_{LFL} = 1200 \text{ A}$
& $\text{pf} = 0.8$ lagging
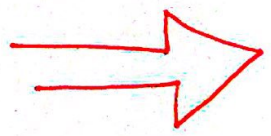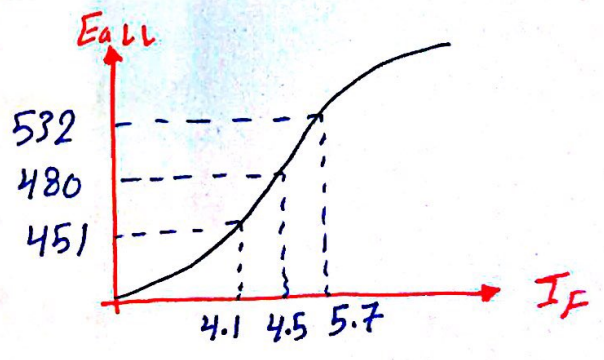
$$P_{F\&W} = 40 \text{ kW}, P_{\text{core}} = 30 \text{ kW.}$$



*find the following:

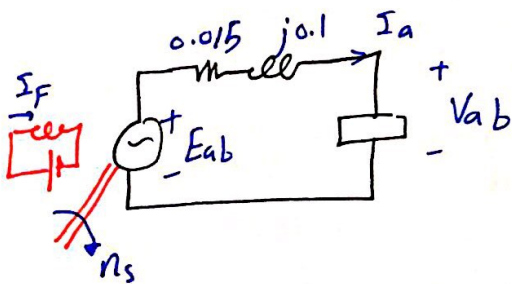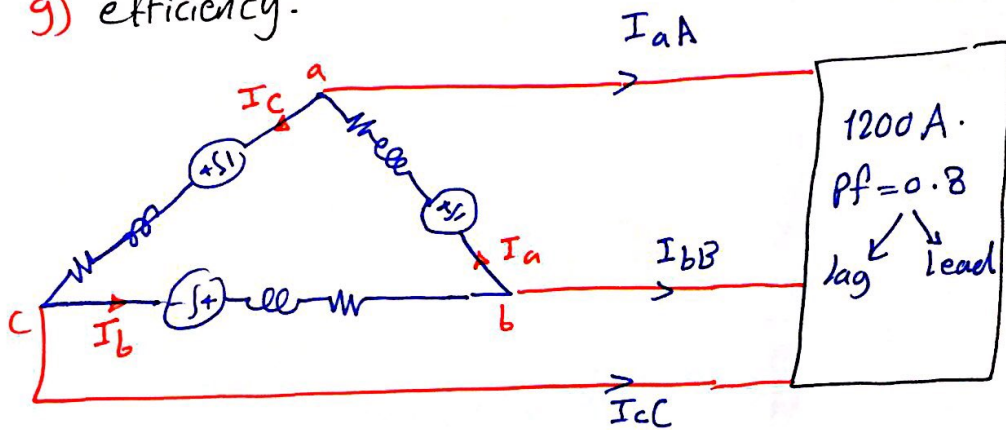- a) n_s c) $I_F \Rightarrow V_t = 480 \text{ volt @ Full-load condition.}$
- b) $I_F \Rightarrow V_t = 480 \text{ volt @ No-load condition.}$
- d) P_{out}, Q_{out} @ Full-load condition.
- e) V_t , if the load is suddenly disconnected.
- f) I_F , to keep V_t @ rated voltage, if full load, 0.8 PF leading is supplied.
- g) efficiency.



a) $n_s = \frac{120f}{P} = \frac{120 \times 60}{4} \Rightarrow n_s = 1800 \text{ rpm}$

b) from the graph:
For $E_{oc} = 480 \text{ volt} \Rightarrow I_F = 4.5 \text{ A.}$


c) $I_L = 1200 \text{ A} \Rightarrow |I_{ph}| = \frac{1200}{\sqrt{3}} = 692.8 \text{ A.}$

$V_{tLL} = 480 \text{ V}$

$E_{ab} = V_{ab} + I_a(R_a + jX_s)$
 $= 480 \text{ V} + 692.8 \angle -36.9^\circ (0.015 + j0.1)$

$\Rightarrow E_{ab} = 532 \angle 5.3^\circ$

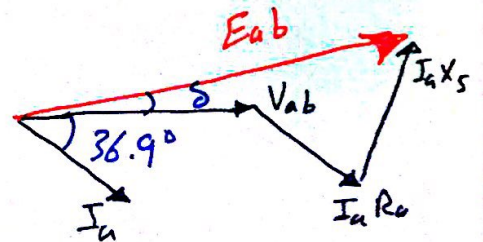
from graph: $\Rightarrow I_F = 5.7 \text{ A}$



d) $P_{out} = \sqrt{3} V_L I_L \cos \theta = \sqrt{3} (480) (1200) (0.8)$
 $Q_{out} = \sqrt{3} V_L I_L \sin \theta = \sqrt{3} (480) (1200) (0.6)$
 $\Rightarrow \begin{cases} P_{out} = 798 \text{ kW} \\ Q_{out} = 600 \text{ kVAR} \end{cases}$

e) $|V_{tLL}| = |E_{oc}|_{LL} = 532 \text{ volt.}$
 if he asked for VR: $VR\% = \frac{532 - 480}{480} \times 100\%$
 $\Rightarrow \boxed{VR\% = 10.8\%}$

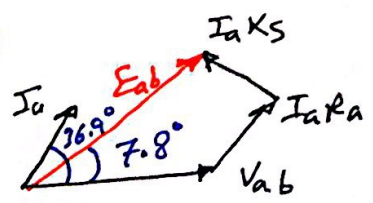
f) $V_t = 480 \text{ volt}$, $Pf = 0.8 \text{ Lead.}$
 $E_{ab} = 480 \angle 0^\circ + 692.8 \angle 36.9^\circ (0.015 + j0.1)$
 $\Rightarrow \boxed{E_{ab} = 450.3 \angle 7.8^\circ \text{ volt.}}$



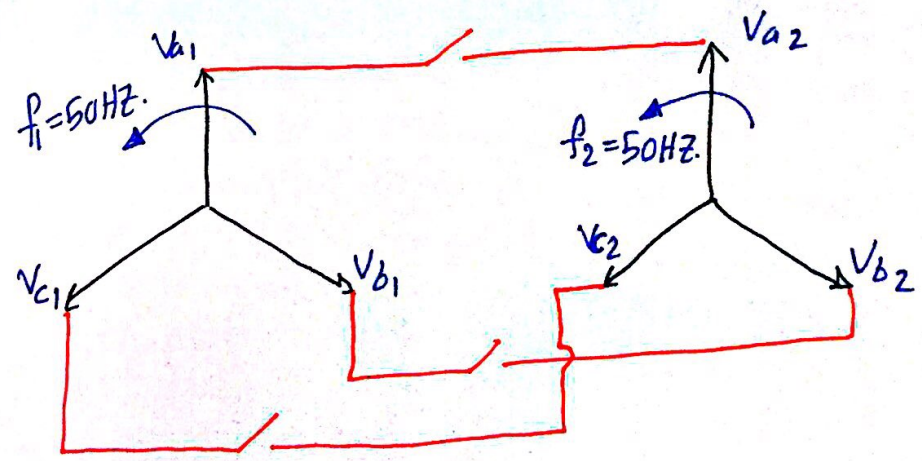g) $\eta = \frac{P_{out FL}}{P_{out} + P_{cu} + P_{core} + P_{F\&W}}$
 $\begin{cases} P_{out} = 798 \text{ kW} \\ P_{cu} = 3 I_a^2 R_a = 3 (692.8)^2 (0.015) \\ \Rightarrow \boxed{P_{cu} = 21.6 \text{ kW}} \end{cases}$
 $\begin{cases} P_{core} = 30 \text{ kW} \\ P_{F\&W} = 40 \text{ kW} \end{cases}$
 $\Rightarrow \boxed{\eta = 89.7\%}$

end of First Material. * * * * * end of First Material

Parallel operation of synchronous Generator:



*** synchronous motor:**

* If we took V_t as a reference; the angle for E_f would be -ve ($-\delta$).

*** in case lagging PF:**

The terminal will see the circuit as inductive load.
 \Rightarrow under excited (absorbing VAR).


*** in case leading PF:**

The terminal will see the circuit as capacitive load.
 \Rightarrow Over excited (supplying VAR).


*** Reactive Power in Motor Case:**


$$Q = \frac{3V_t}{X_s} [V_t - E_f \cos\delta]$$

*** Effect of field current changes:**

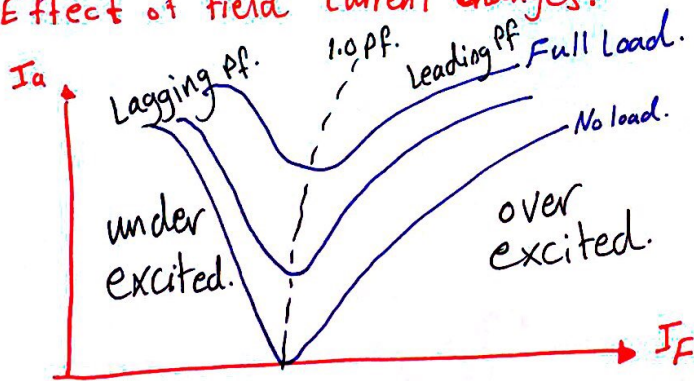

Example: slide (34): Let us consider

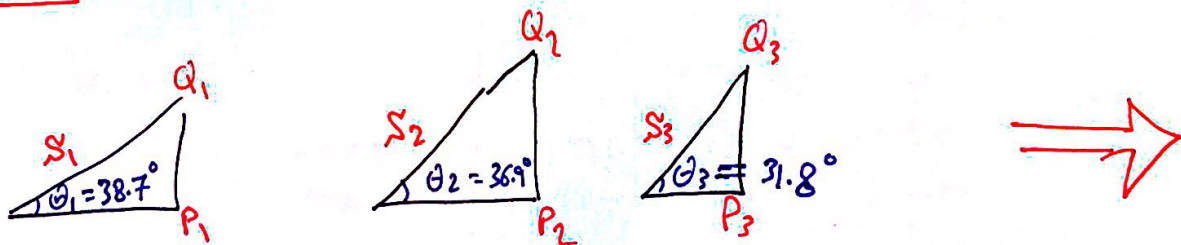

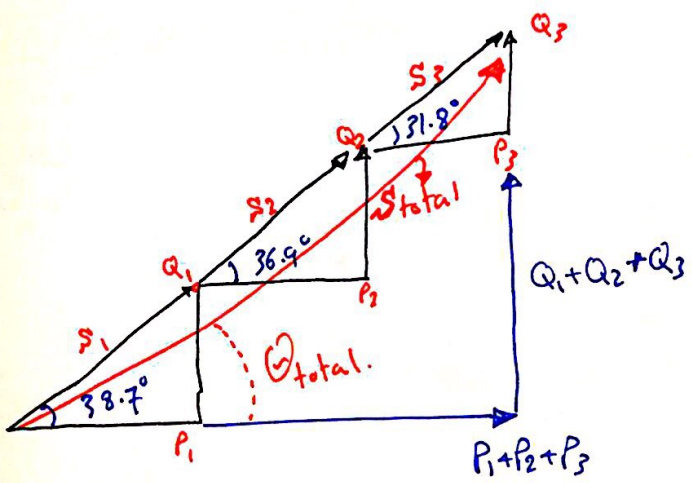

$$S_{tot} = S_1 + S_2 + S_3$$

$$= (P_1 + jQ_1) + (P_2 + jQ_2) + (P_3 + jQ_3)$$

$$S_{tot} = (P_1 + P_2 + P_3) + j(Q_1 + Q_2 + Q_3)$$

$$P_{f_{total}} = \cos \tan^{-1} \frac{Q_{tot}}{P_{tot}}$$

$$Q_1 = 80.2 \text{ KVAR.}$$

$$Q_2 = 150 \text{ KVAR}$$

$$Q_3 = 93 \text{ KVAR.}$$

$$\Rightarrow P_{tot} = 450 \text{ KW}$$



$$Q_{tot} = 323.2 \text{ KVAR.}$$

* Tutorial (2) Solutions :

$$1 \text{ hp} = 746 \text{ W.}$$

Q1

Equivalent cct:

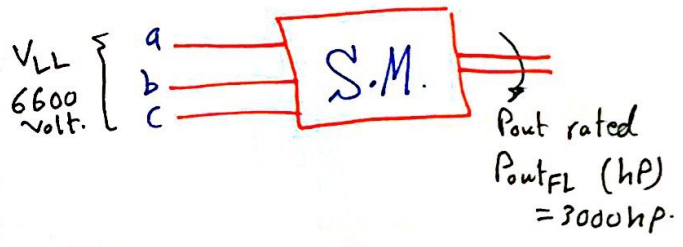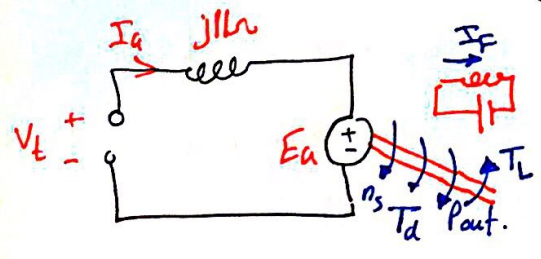

$$\Rightarrow S_{3\phi} = \frac{3M}{0.8} \Rightarrow S_{3\phi} = 3.75 \text{ MVA.}$$

$$S_{3\phi} = \frac{P_{3\phi in}}{PF}$$

$$\Rightarrow P_{3\phi in} = \frac{P_{out FL}}{\eta}$$

$$= \frac{3000 * 746}{0.746}$$

$$P_{3\phi in} = 3 \text{ MW.}$$

$$S_{3\phi} = 3V_{\phi} I_{\phi} = \sqrt{3} V_L I_L$$


$$S_{\phi} = V_{ph} \cdot I_{ph} = 1.25 \text{ MW.}$$

in Y-con. $(I_L) = |I_{ph}|$.

$$|I_L| = \frac{S_{3\phi}}{\sqrt{3} V_L} = \frac{3.75 \text{ M}}{\sqrt{3} * 6600} = |I_{ph}| = 328$$

$$\text{so } I_a = 328 \angle +36.87^\circ \text{ A.}$$

⇒ *phasor diagram:

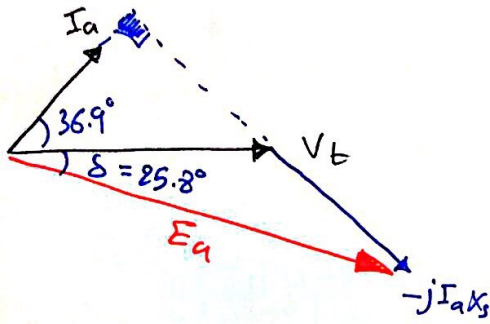


$$E_a = \frac{6600}{\sqrt{3}} \angle 0^\circ - 328 \angle 36.9^\circ \times 11 \angle 90^\circ$$

$$E_{a,ph} = 6636.8 \angle -25.8^\circ \text{ volt.}$$


$$|E_a|_{LL} = 11493.7 \text{ volt.}$$

Q2 | $P = 4$, $f = 60 \text{ Hz}$, Y-conn, $|V_t|_{LL} = 3980 \text{ volt.}$

Equ. cct:

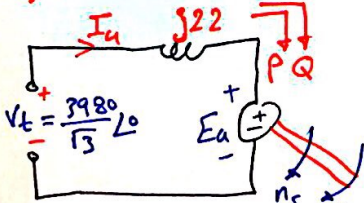

$n_s = 1800 \text{ rpm.}$

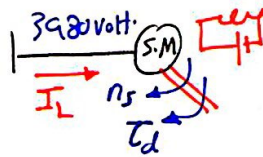

$$E_{a,LL} = 3100 \text{ volt.}$$

$$I_F = 25 \text{ A.}$$

$$a) I_{ph} = I_L = \frac{V_t - E_a}{jX_s} = \frac{\frac{3980}{\sqrt{3}} \angle 0^\circ - \frac{3100}{\sqrt{3}} \angle 30^\circ}{22 \angle 90^\circ}$$

$$\Rightarrow I_L = 53 \angle -40^\circ \text{ A.}$$

b) $Pf = \cos(40^\circ) \Rightarrow Pf = 0.766$ lagging.


c) $\omega_s = \frac{2\pi n_s}{60} = 188.5 \text{ rad/sec.}$

$$P_d = P_{in} = \sqrt{3} I_L V_t \cos \theta = \frac{3 E_a V_t}{X_s} \sin \delta$$


$R_a = 0$ $P_d = 280.4 \text{ kW.}$

$$T_d = \frac{P_d}{\omega_s} = \frac{280.4 \times 10^3}{188.5} \Rightarrow T_d = 1487 \text{ N.m.}$$

*phasor diagram:

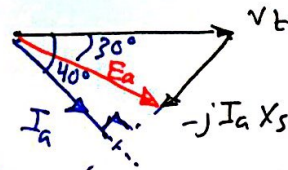

Q3 |

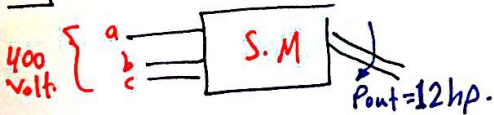


$$\sum P_{loss} = 1200 \text{ W.}$$

$$P_{in} = P_{out} + \sum \text{losses} = 12 \times 746 + 1200 = 10152 \text{ W.}$$


$$\eta = \frac{P_{out}}{P_{in}} = \frac{12 \times 746}{10152} \Rightarrow \eta = 88\%$$

* Remember the following relation:

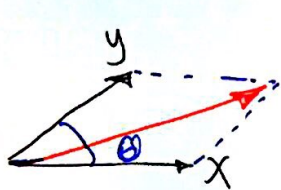


$$|x+y| = \sqrt{x^2 + y^2 + 2xy \cos \theta}$$

Q4

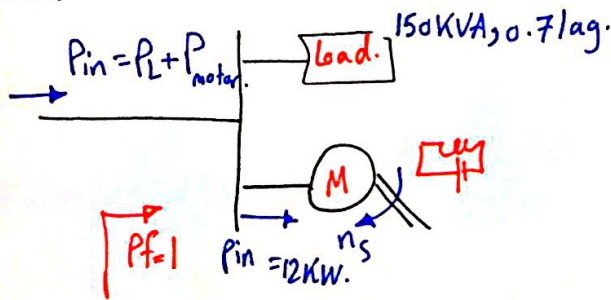

over excited:

\Rightarrow leading Pf.
& $|E_a| > V_t$.

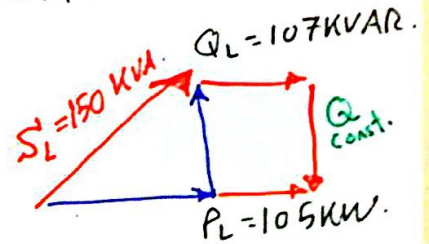

$Q_m = Q_L = 107 \text{ KVAR.}$


$|S_m| = \sqrt{P_m^2 + Q_m^2} = \sqrt{12^2 + 107^2} \Rightarrow |S_m| = 107.6 \text{ KVA.}$

$P_{fm} = \cos \left[\tan^{-1} \frac{Q_m}{P_m} \right] = \cos \left[\tan^{-1} \frac{107}{12} \right] \Rightarrow \boxed{Pf = 0.111} \text{ leading.}$

$P_{in} = \frac{100 \times 746}{0.9} = 82.9 \text{ KW.}$

$S_m = \sqrt{(82.9)^2 + (107)^2} = 135.4 \text{ KVA.}$

Q5

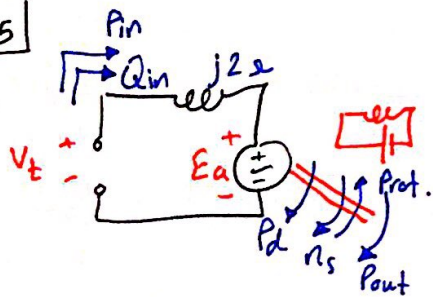

b) $E_a = V_t - j I_a X_s$

$= \frac{6600}{\sqrt{3}} \angle 0 - 43.7 \angle -36.9^\circ \times 2 \angle 90^\circ$

$\Rightarrow \boxed{E_a = 3758.6 \angle -1^\circ \text{ volt.}}$

$|E_a|_{LL} = 6510 \text{ volt.}$

I. a) $P_{in} = \sqrt{3} V_t I_L \cos \theta$

$\Rightarrow 400 \text{ K} = \sqrt{3} \times 6.6 \text{ K} \times I_L \times 0.8$

$\Rightarrow |I_L| = |I_a| = 43.7 \text{ A}$


so $\boxed{I_a = 43.7 \angle -36.9^\circ \text{ A.}}$

c) $T_{max} = \frac{P_{dmax}}{\omega_s}$

$P_{dmax} = \frac{3 V_t E_a}{X_s} = 21.4 \text{ MW.}$

$T_{dmax} = \frac{9.55 P_{dmax}}{n_s} = \frac{9.55 \times 21.4 \times 10^6}{1000}$

$\boxed{T_{dmax} = 205.2 \text{ KN.m.}}$

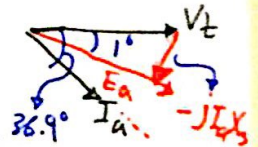

II. $I_{f2} = 1.25 I_{f1} \Rightarrow E_{a2} = 1.25 E_{a1} = 1.25 * 3758.6$

$E_{a2} = 4698.25 \text{ volt.}$

a) $P_{d1} = P_{d2}$

$\frac{3V_t E_{a1}}{X_s} \sin \delta_1 = \frac{3V_t E_{a2}}{X_s} \sin \delta_2 \Rightarrow E_{a1} \sin \delta_1 = 1.25 E_{a1} \sin \delta_2$

$\sin \delta_2 = \frac{\sin \delta_1}{1.25} = \frac{\sin(1)}{1.25} \Rightarrow \delta_2 = 0.8^\circ$

b) $I_{a2} = \frac{V_t - E_{a2}}{jX_s} = \frac{3810.5 \angle 0^\circ - 4698.25 \angle -0.8^\circ}{2 \angle 90^\circ} \Rightarrow I_{a2} = 445 \angle +85.8^\circ \text{ A}$


c) $Pf = \cos \theta_2 = \cos(85.8) \Rightarrow Pf = 0.077 \text{ Leading.}$

d) $P_{max2} = 1.25 P_{max1} = 1.25 * 21.4 \text{ M} \Rightarrow P_{max2} = 26.7 \text{ MW.}$

$P_1 = 400 \text{ kW.}$

$Q_1 = \frac{P}{Pf} \sin \theta = \frac{400 \text{ K}}{0.8} * 0.6 = 300 \text{ KVAR.}$



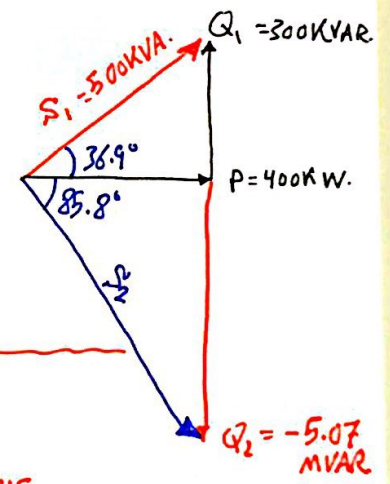
$Q_2 = \sqrt{3} I_a V_L \sin \theta_2 = \sqrt{3} (6600) (445) \sin(-85.8)$
 $= -5.07 \text{ MVAR.}$



Q6 3.3kV, 50Hz, P=2, Y-con., $X_s = 15 \Omega$
 $|E_a| = |V_t| = 3.3 \text{ K volt.}$

a) $P_{max} |_{\delta=90^\circ} = \frac{3.3 \text{ K} * 3.3 \text{ K}}{15} = 726 \text{ kW.}$

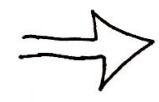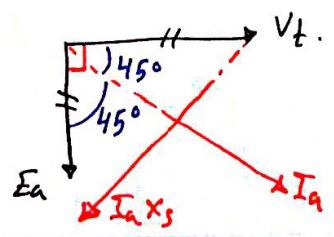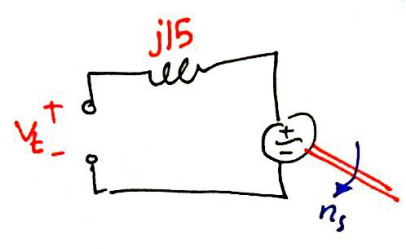$T_{max} = \frac{P_{max}}{\omega_s} = \frac{726 \text{ K}}{314} = 2310.9 \text{ N.m.}$



b) $I_a = \frac{V_t - E_a}{jX_s} = \frac{\frac{3300}{\sqrt{3}} \angle 0^\circ - \frac{3300}{\sqrt{3}} \angle -90^\circ}{15 \angle 90^\circ} \Rightarrow I_a = 179.6 \angle -45^\circ \text{ A.}$

$Pf = \cos \theta \Rightarrow Pf = \cos 45 \Rightarrow Pf = 0.707$ Lagging.

$Q = \sqrt{3} V_L I_L \sin \theta$ (absorbed). $= \sqrt{3} * 3.3 \text{ kV} * 179.6 * 0.707$
 $\Rightarrow Q = 726 \text{ KVAR.}$


c) $E_{a2} = 1.2 E_{a1} = 1.2 * \frac{3300}{\sqrt{3}} \Rightarrow E_{a2} = 2286 \text{ volt.}$

$\delta_2 = \sin^{-1} \left(\frac{\sin \delta_1}{1.2} \right) = \sin^{-1} \left(\frac{\sin 90}{1.2} \right) \Rightarrow \delta_2 = 56.4^\circ$

$I_{a2} = \frac{\frac{3300}{\sqrt{3}} \angle 0^\circ - 2286 \angle -56.4^\circ}{15 \angle 90^\circ} \Rightarrow I_a = 134 \angle -18.6^\circ \text{ A.}$

$Pf = 0.948$
Lagging.

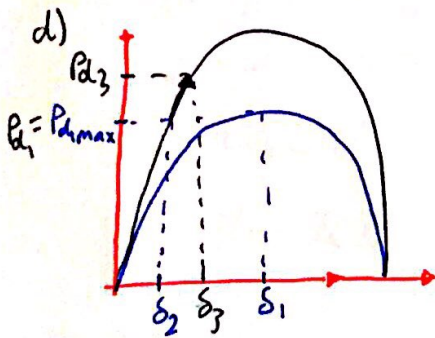$Q_2 = \sqrt{3} * 3300 * 134 \sin(18.6) \Rightarrow Q_2 = 244.3 \text{ KVAR.}$



$P_{d3} = 1.1 P_{d1 \text{ max}} = 1.1 * 726 \text{ K} = 798.6 \text{ KW.}$

$P_{d3} = 3 \frac{V_t E_{a3}}{X_s} \sin \delta_3$

$798.6 * 10^3 = \frac{3 * \frac{3300}{\sqrt{3}} * 2286}{15} \sin \delta_3$

$\Rightarrow \delta_3 = 66.5^\circ$

$I_a = 154.7 \angle -25.4^\circ \text{ A}$, $Pf = 0.908$ Lagging, $Q_3 = 379.3 \text{ KVAR.}$

Q7 | $V_t = 208 \text{ volt, } 45 \text{ KVA.}$


0.8 pf lead.

Δ -connected.

$f = 60 \text{ HZ}$ & $X_s = 2.5 \Omega$

$P_{F\&W} = 1.5 \text{ KW}$, $P_{core} = 1 \text{ KW.}$

$P_{out} = 15 \text{ hp.}$

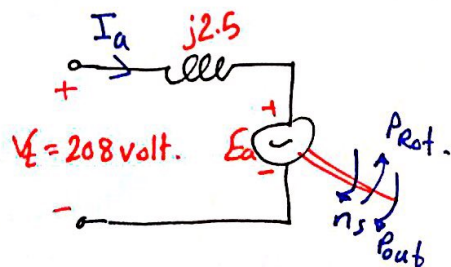

$$\Rightarrow P_{in} = P_d = P_{rot} + P_{out} = (1.5 + 1 + 11.2) \text{ kW} = 13.7 \text{ kW}$$

$$I_d = \frac{P_{in}}{3 V_{ph} \cos \theta} = \frac{13.7 \times 10^3}{3 \times 208 \times 0.8} = 27.4 \text{ A}$$

$$\Rightarrow I_a = 27.4 \angle 36.9^\circ \text{ A} \Rightarrow |I_L| = \sqrt{3} |I_{ph}| \Rightarrow |I_L| = 47.5 \text{ A}$$

$$P_{in2} = P_{out2} + P_{rot} = 22.4 + 2.5 = 24.9 \text{ kW}$$

$$P_{in2} = \frac{3 V_t E_{a2} \sin \delta_2}{X_s}$$

$$\Rightarrow I_{a2} = \frac{V_t - E_{a2} \angle \delta}{j X_s}$$


$$\Rightarrow \delta_2 = 23^\circ$$

$Pf = 0.966$ leading.

$$\Rightarrow I_{a2} = 41.3 \angle 15^\circ \text{ A}$$

$$|I_L| = 71.5 \text{ A}$$
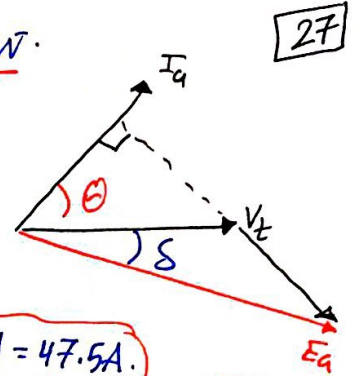
$$E_a = 255 \angle -12.4^\circ \text{ volt}$$



Q8

$$a) n_s = \frac{120}{p} * f = \frac{120}{8} * 60 \Rightarrow n_s = 900 \text{ rpm}$$

$$b) P_{in} = P_{out} = 400 * 746 \Rightarrow P_{in} = 298.4 \text{ kW}$$

$$P_{in} = 3 V_t I_a Pf \Rightarrow I_a = \frac{298.4 \text{ kW}}{3 * 480 * 0.8} \Rightarrow I_a = 259 \angle -36.9^\circ \text{ A}$$

$$E_a = V_t - I_a (j X_s) = 480 \angle 0^\circ - (259 \angle -36.9^\circ) * 0.6j \Rightarrow E_a = 406.2 \angle -17.8^\circ \text{ volt}$$

$$c) \delta = 17.8^\circ \quad \tau = \frac{P_{in}}{\omega_s} = \frac{298.4 \text{ kW}}{2\pi * \frac{900}{60}} \Rightarrow \tau \approx 3166 \text{ N.m}$$

$$P_{in \max} = \frac{3 V_t E_g}{X_s} = \frac{3 * 480 * 406.2}{0.6} = 974.88 \text{ kW}$$

$$\tau_{\max} = \frac{P_{\max}}{\omega_s} \Rightarrow \tau_{\max} \approx 10344 \text{ N.m}$$

τ is 30.6% of τ_{\max} .

$$d) E_{a2} = 1.3 E_{a1} \Rightarrow |E_{a2}| = 528 \text{ volt}$$

$$\sin \delta_2 = \frac{\sin \delta_1}{1.3} = \frac{\sin 17.8}{1.3} \Rightarrow \delta_2 = 13.6^\circ$$

$$I_a = \frac{V_t - E_a \angle \delta}{j X_s} \Rightarrow I_a = 214.2 \angle 15^\circ \text{ A}$$


$Pf = 0.966$ leading

*

*


*

⇒

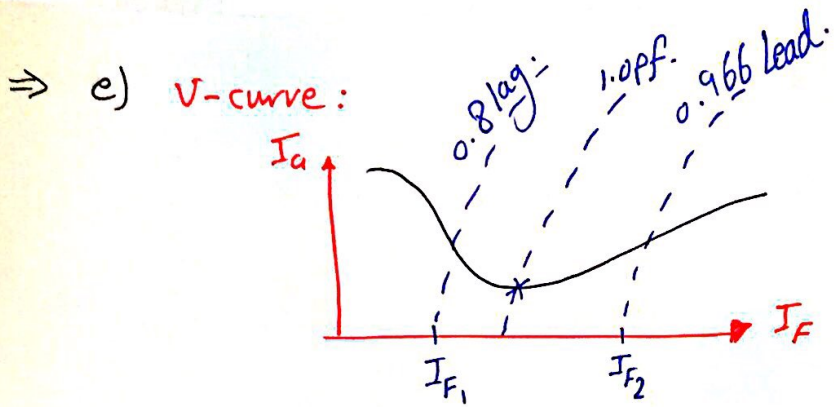

* * *

* Induction Motor:

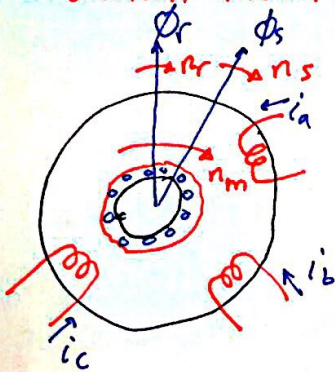

$$n_r < n_s$$

$$n_m = (1-s) n_s$$

$$s = \frac{n_s - n_m}{n_s} \Rightarrow \text{slip.}$$

$$n_r = n_s - n_m \text{ rpm.}$$

$$n_r = s n_s$$


EX.

for $s = 0.03$, $n_s = 3000 \text{ rpm}$, $n_m = ?$

$$n_m = (1-s) n_s = (1-0.03) * 3000 = \underline{\underline{2910 \text{ rpm}}}$$

* In Motor, E_a called Back EMF.

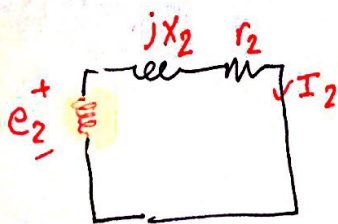* We use phase analysis only if the circuits have the same frequency.



$$\Rightarrow e_{rms} = 4.44 f_m N_{ph} \phi$$

@ standstill ($n_m = 0$)

$$E_2 = e_{rms} = 4.44 f_s N_2 \phi$$

$$f_r = s f_s$$



$\Rightarrow E_2 = sE_1$

$I_2 = \frac{E_2}{\sqrt{R_2^2 + X_2^2}} = \frac{sE_1}{\sqrt{R_2^2 + X_2^2}} = \frac{E_1}{\sqrt{\left(\frac{R_2}{s}\right)^2 + \left(\frac{X_2}{s}\right)^2}}$

$\Rightarrow I_2 = \frac{E_2}{\sqrt{\left(\frac{R_2}{s}\right)^2 + X_2^2}}$

$x_2 = sX_2$

$\frac{R_2}{s} = R_2 + \frac{sR_2 - sR_2}{s}$

$\Rightarrow \frac{R_2}{s} = R_2 \frac{(1-s)}{s} + R_2$

Example: 480 volt, 60 Hz, 6-pole, 3-ph Δ -connected. Induction motor with the following parameters:

$R_1 = 0.461 \Omega$ $R_2 = 0.258 \Omega$ $X_1 = 0.507 \Omega$ $X_2 = 0.309 \Omega$
 $X_m = 30.74 \Omega$, $P_{rot} = P_{\Delta W} + P_{core} = 2450 W$.

If the motor runs at a full-load $s=5\%$, find the following:

- 1) the magnitude of Line current drawn by the motor.
- 2) the motor pf.
- 3) the real & reactive power drawn by the motor.
- 4) the motor output horse power (hp).
- 5) the motor efficiency.
- 6) the motor's starting current.

$s_{FL} = \frac{n_s - n_m}{n_s} = 0.05$

$n_s = \frac{120 f}{P} = \frac{120 * 60}{6} = 1200 \text{ rpm}$


$n_m = (1 - 0.05) * 1200 = 1140 \text{ rpm}$

$Z_{eq}(s) = \left(\frac{R_2'}{s} + jX_2'\right) // (jX_m) + (R_1 + jX_1)$

$Z_{FL}(s=0.05) = \frac{(5.16 + j0.309) * j30.74}{5.16 + j(0.309 + 30.74)} + (0.461 + j0.507)$


$\Rightarrow Z_{eq} = 5.6 \angle 16.9^\circ \Omega$

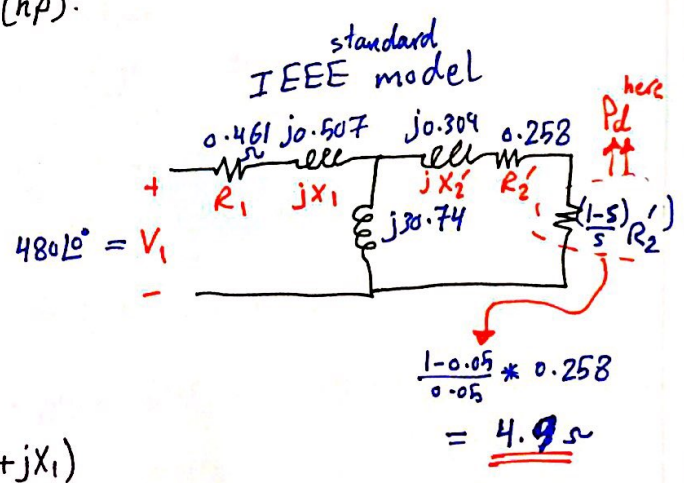$I_{1FL} = \frac{480 \angle 0^\circ}{5.6 \angle 16.9^\circ} = 85.7 \angle -16.9^\circ A$



* Always the induction motor (lagging).

①

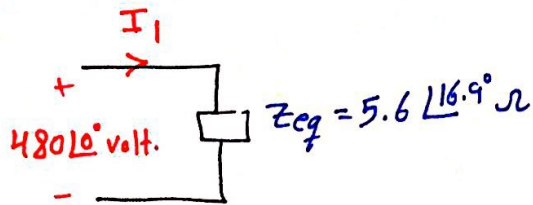

$$I_L = \sqrt{3} I_{ph}$$

$$|I_L| = \sqrt{3} * 85.7$$

$$\Rightarrow |I_L| = 148.4 \text{ A}$$

② $PF = \cos(16.9^\circ) \Rightarrow PF = 0.9568$ Lagging.

③ $P_{in} = \sqrt{3} V_L I_L \cos\theta = \sqrt{3} * 480 * 148.4 * 0.9568 = 118.05 \text{ KW}$

or using: $Z_{eq} = 5.4 + j1.6 \Omega$

$$P_{in} = 3 |I_1|^2 R_{eq} = 3 (85.7)^2 * 5.4 = 118.98 \text{ KW}$$


$$Q_{in} = \sqrt{3} V_L I_L \sin\theta = \sqrt{3} * 480 * 148.4 * \sin(16.9^\circ) = 35.9 \text{ KVAR}$$

or using:

$$Q_{in} = 3 |I_1|^2 X_{eq} = 3 (85.7)^2 * 1.6 = 35.3 \text{ KVAR}$$

To assure PF value $\Rightarrow PF = \cos\left[\tan^{-1}\left(\frac{Q_{in}}{P_{in}}\right)\right] = 0.9567$ Lag.

④

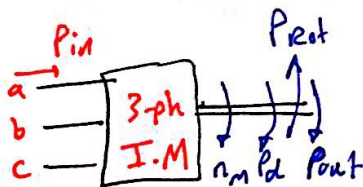

$$P_{out} = P_d - P_{rot}$$

$$P_d = 3 |I_2'|^2 \frac{(1-s)}{s} R_2'$$

$$I_2' = I_1 * \frac{jX_m}{\frac{R_2'}{s} + j(X_2' + X_m)} = \frac{(85.7 \angle -16.9^\circ) * j30.74}{5.16 + j(0.309 + 30.74)}$$

$$\Rightarrow I_2' = 83.7 \angle -7.5^\circ \text{ A} \Rightarrow P_d = 3 (83.7)^2 * 4.9 = 102.9 \text{ KW}$$

$$P_{out} = 102.9 \text{ K} - 2.45 \text{ K} \Rightarrow P_{out} = 100.45 \text{ KW} \Rightarrow P_{out} = \frac{100.45 * 10^3}{746}$$

$$P_{out} = 134.7 \text{ hp}$$

⑤ $\eta_{FL} = \frac{P_{out}}{P_{in}} * 100\% = \frac{100.45}{118.05} * 100\% \Rightarrow \eta = 85.1\%$

⑥ @ full load $s = 0.05$
@ starting $r_m = 0 \Rightarrow s = 1$


$$Z_{eq}(s=1) = (0.461 + j0.507) + \frac{j30.74 * (0.258 + j0.309)}{0.258 + j(0.309 + 30.74)}$$

$$\Rightarrow Z_{eq} = 1.1 \angle 48.8^\circ \Omega$$

$$\Rightarrow I_{1 \text{ starting}} = \frac{480}{1.1 \angle 48.8^\circ}$$

$$I_1 = 436.4 \angle -48.8^\circ \text{ A}$$

* Approximate equivalent cct :

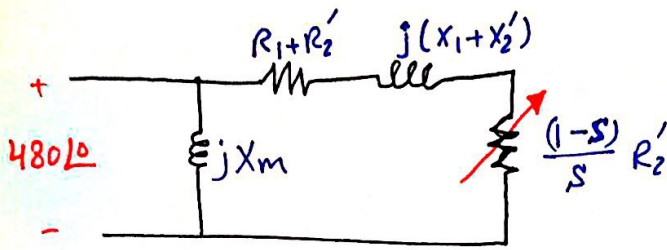


we use it if it is allowed since it is more easier.

$$V_{th} = V_{oc} = \frac{V_1 * jX_m}{R_1 + j(X_1 + X_m)} = \frac{480 \angle 0 * j30.74}{0.461 + j(0.507 + 30.74)} = 472.2 \angle 0.8^\circ \text{ V.H.}$$

$$Z_{th} = jX_m \parallel (R_1 + jX_1) = \frac{(0.461 + j0.507) * j30.74}{0.461 + j(0.507 + 30.74)} = 0.67 \angle 48.6^\circ \Omega$$

$$= 0.45 + j51 \Omega$$


The cct become :

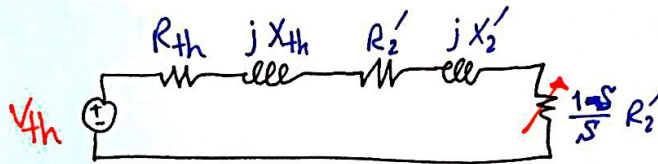

& we find what he want.

* Power flow in I.M :

Consider the exact equ. cct :

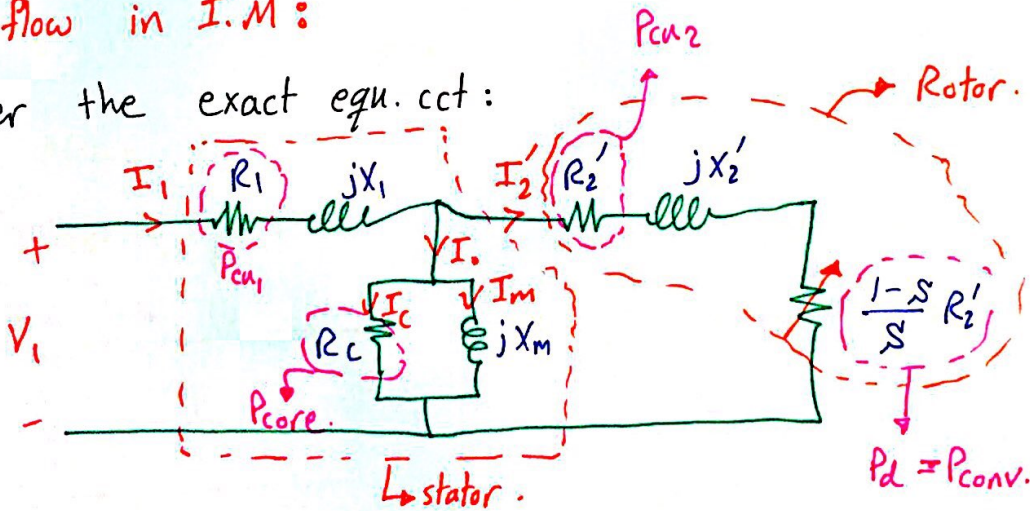

$$P_{in} = \sqrt{3} V_L I_L \cos \theta$$

$$P_{in} = 3 V_1 I_1 \cos \theta$$

$$P_g = 3 |I_2'|^2 \frac{R_2'}{s}$$

$$P_d = P_{conv} = 3 |I_2'|^2 \frac{1-s}{s} R_2' = T_d \cdot \omega_m$$

$$P_{out} = P_{shaft} = T_o \cdot \omega_m$$

$$\eta = \frac{P_{out}}{P_{in}}$$

$$P_{cu1} = 3 I_1^2 R_1$$

stator copper losses.

air gap power.

$$P_{cu2} = 3 I_2'^2 R_2'$$





rotor copper losses.

PF&W.

$\Rightarrow P_g = \frac{P_{cu2}}{s} \Rightarrow P_{cu2} = s P_g$


$P_d = (1-s) P_g$ as $n_m = (1-s) n_s \Rightarrow \omega_m = (1-s) \omega_s$

$T_d = \frac{P_d}{\omega_m} = \frac{(1-s) P_g}{(1-s) \omega_s} \Rightarrow T_d(s) = \frac{P_g}{\omega_s} = \frac{3 |I_2'|^2 R_2'/s}{\omega_s}$

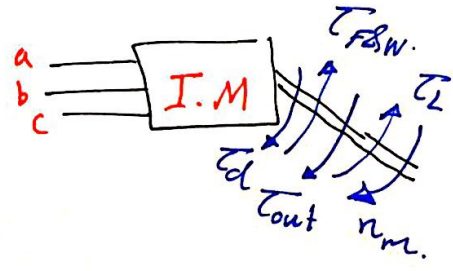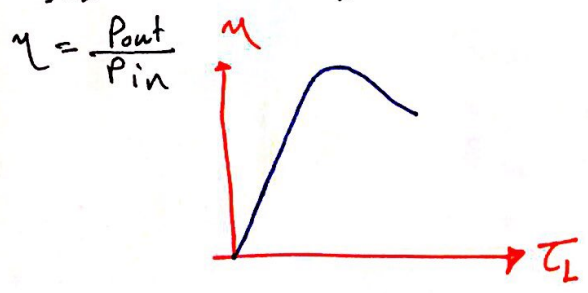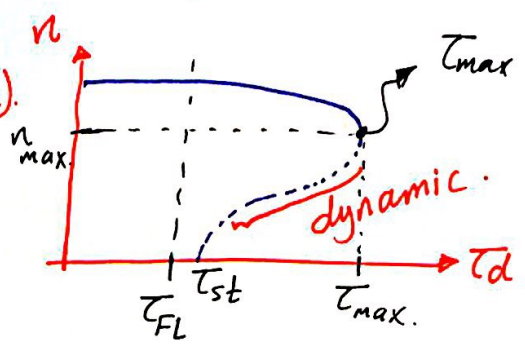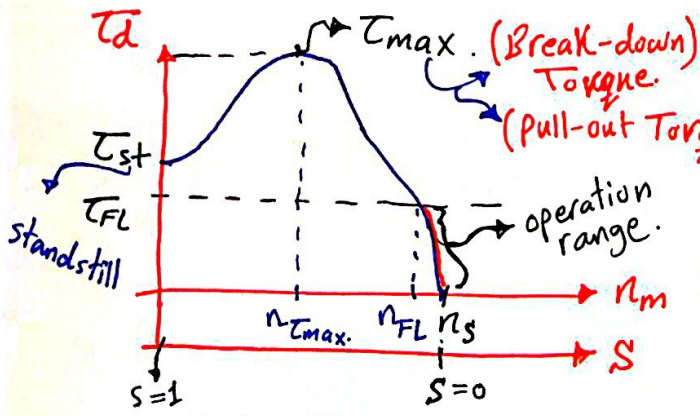


* To obtain I_2' :

• By Thevenin Equivalent:

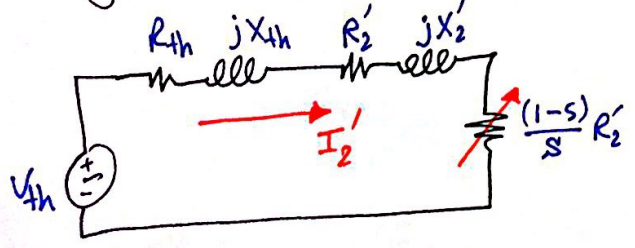

$I_2' = \frac{V_{th}}{(R_{th} + \frac{R_2'}{s}) + j(X_{th} + X_2')}$

• By Approximate circuit:

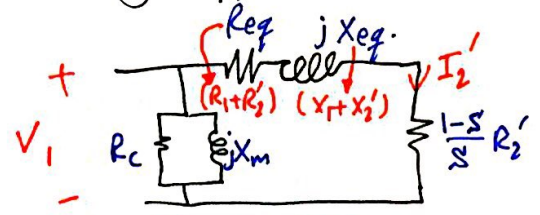

$I_2' = \frac{V_1}{(R_1 + \frac{R_2'}{s}) + j(X_1 + X_2')}$

$\Rightarrow |I_2'| = \frac{|V_{th}|}{\sqrt{(R_{th} + \frac{R_2'}{s})^2 + (X_{th} + X_2')^2}}$

$T_d(s) = \frac{3 |V_{th}|^2 R_2'/s}{\omega_s [(R_{th} + \frac{R_2'}{s})^2 + (X_{th} + X_2')^2]}$

- * @ starting $n_m = 0 \Rightarrow S = 1$
- * @ No-load $n_m \approx n_s \Rightarrow S = 0$

$$\tau_{d_{st}} (S=1) = \frac{3|V_{th}|^2}{\omega_s} * \frac{R_2'}{(R_{th}+R_2')^2 + (X_2'+X_{th})^2}$$


OR. $\tau_{d_{st}} (S=1) = \frac{3|V_1|^2}{\omega_s} * \frac{R_2'}{R_{eq}^2 + X_{eq}^2}$

$$\tau_{d_{FL}} (S=S_{FL}) = \frac{3|V_{th}|^2}{\omega_s} * \frac{R_2'/S_{FL}}{(R_{th} + \frac{R_2'}{S_{FL}})^2 + (X_{th} + X_2')^2}$$

$$\tau_{d_{max}} (S=S_{max}) = \frac{3|V_{th}|^2}{\omega_s} * \frac{R_2'/S_{max}}{(R_{th} + \frac{R_2'}{S_{max}})^2 + (X_{th} + X_2')^2}$$

$S_{max} = \frac{n_s - n_{T_{max}}}{n_s}$
"max slip".

* Max Power Transfer:

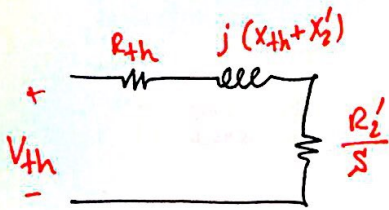

$$\tau_{d_{max}} = \frac{P_{g_{max}}}{\omega_s}$$

$$\frac{R_2'}{S_{max}} = |R_{th} + j(X_{th} + X_2')| = \sqrt{R_{th}^2 + (X_{th} + X_2')^2}$$

$$S_{max} = \frac{R_2'}{\sqrt{R_{th}^2 + (X_{th} + X_2')^2}}$$

S_{max} depends on the machine parameters

$$\tau_{d_{max}} (S_{max}) = \frac{3|V_{th}|^2 R_2'/S_{max}}{\omega_s [(R_{th} + \frac{R_2'}{S_{max}})^2 + (X_{th} + X_2')^2]}$$

↳ After simplify it:

$$\tau_{d_{max}} = \frac{3|V_{th}|^2}{2\omega_s} * \frac{1}{R_{th} + \sqrt{R_{th}^2 + (X_{th} + X_2')^2}}$$

$$\tau_d (S) = \frac{3|V_1|^2}{\omega_s} * \frac{R_2'/S}{(R_1 + \frac{R_2'}{S})^2 + (X_1 + X_2')^2}$$

$$\Rightarrow \tau_d \propto |V|^2 \Rightarrow \frac{T_2}{T_1} = \left| \frac{V_2}{V_1} \right|^2$$

$$\tau_d \propto P$$


when S very small

$$\tau_d \approx \frac{3|V_1|^2}{\omega_s} * \frac{R_2'/S}{(R_2'/S)^2} = \frac{3|V_1|^2}{\omega_s} * \frac{S}{R_2'}$$

$$\tau_d = \frac{3|V_1|^2}{\omega_s} * \frac{(R_2' + R_{ext})/s}{\left[R_1 + \frac{(R_2' + R_{ext})}{s}\right]^2 + [X_1 + X_2']^2}$$

external resistance.

34

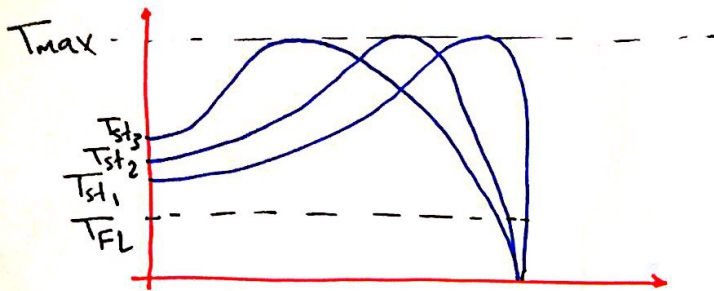

could ask to find external resistance that adjust max. Torque.

Tutorial #3:

Q₁ | solved.

Q₂ | additional parts:

$$\tau_{st} = \frac{3|V_1|^2 R_2'}{\omega_s [(R_1 + R_2')^2 + X_{eq}^2]} = \frac{3 * \left(\frac{480}{\sqrt{3}}\right)^2 * 0.5}{20\pi * [(1.5)^2 + 100]} = \underline{\underline{17.9 \text{ N.m.}}}$$

$$\tau_{dFL} = \frac{3|V_1|^2}{\omega_s} * \frac{R_2'/s_{FL}}{(R_1 + \frac{R_2'}{s_{FL}})^2 + X_{eq}^2} = \frac{(480)^2}{20\pi} * \frac{0.5/0.05}{\left(1 + \frac{0.5}{0.05}\right)^2 + 100}$$

Q₃ | 3-ph, 30 hp, 480 V, 60 Hz.

$P_{tot} = P_{core} + P_{F\&W} = 1250 \text{ W.}$


$V_{LL} = 440 \text{ volt.}$

$s = 8.5\%$

using IEEE model:


$$n_m = (1-s)n_s = (-0.085) * \frac{120 * 60}{4}$$

$n_m = 1737 \text{ rpm.}$

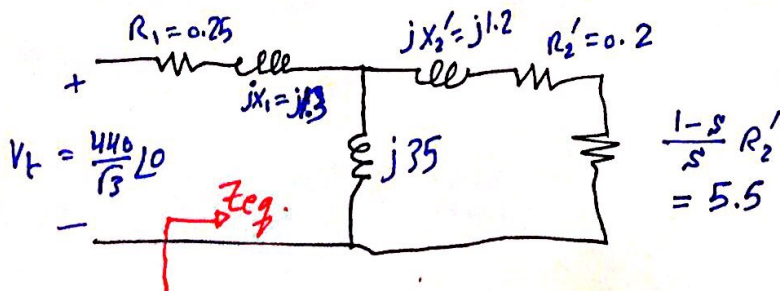


$$\Rightarrow Z_{eq} = R_1 + jX_1 + (jX_m) \parallel \left(\frac{R_2'}{s} + jX_2' \right)$$
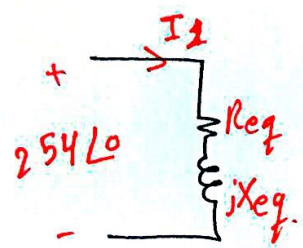
$$= 0.25 + j1.3 + \frac{j35 * (5.7 + j1.2)}{5.7 + j36.2} = 6.36 \angle 31^\circ \Omega$$



$$I_1 = \frac{254 \angle 0^\circ}{6.36 \angle 31^\circ} = 39.94 \angle -31^\circ \text{ A}$$
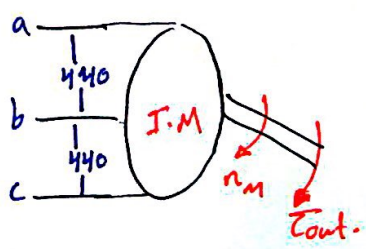
$$PF = \cos(31^\circ) = 0.8572 \text{ Lagging}$$



$$P_{in} = \sqrt{3} V_L I_L = 3 V_t I_a \cos \theta = 3 |I_a|^2 R_{eq}$$

$$= \sqrt{3} * 440 * 39.9 * 0.857 = 26.092 \text{ kW}$$

$$T_{out} = \frac{P_{out}}{\omega_m} = \frac{9.55 P_{out}}{n_m}$$

$$P_{out} = P_{in} - \sum \text{losses}$$

$$= P_{in} - P_{cu1} - P_{cu2} - P_{rot}$$

$$P_{cu1} = 3 |I_1|^2 R_1, P_{cu2} = 3 |I_2'|^2 R_2'$$

$$I_2' = I_1 * \frac{jX_m}{\frac{R_2'}{s} + jX_2' + jX_m} = (39.94 \angle -31^\circ) * \frac{j35}{5.7 + j36.2} = 38.1 \angle -22.1^\circ \text{ A}$$

$$P_{cu1} = 3 (39.9)^2 * 0.25 = 1200 \text{ W}$$



$$P_{cu2} = 3 (38.1)^2 * 0.25 = 875.5 \text{ W}$$

$$P_{out} = 22.8 \text{ kW}$$

$$\Rightarrow T_{out} = \frac{9.55 * 22.8 \text{ kW}}{1737} = 125.4 \text{ N.m}$$


$$\eta_m = \frac{22.8}{26.1} * 100\% = 87.4\%$$

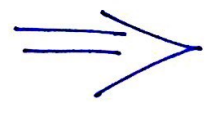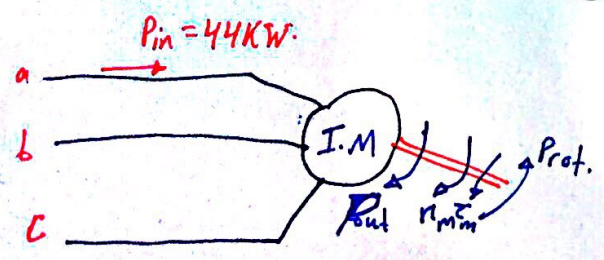Q4] 3-ph, I.M, $n_m = 1752 \text{ rpm}$, $f = 60 \text{ Hz}$, $P = 4 \Rightarrow n_s = 1200 \text{ rpm}$.



$$s = \frac{n_s - n_m}{n_s} = \frac{1200 - 1152}{1200} * 100\%$$

$s = 4\%$

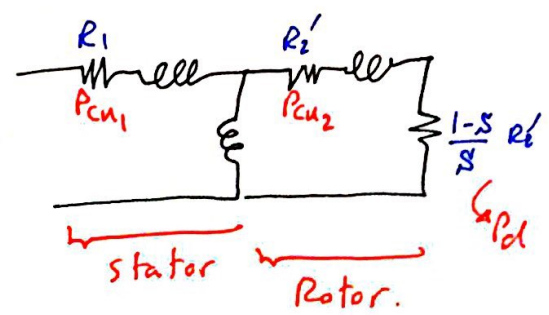

$$P_g = P_{in} - P_{cu1} = 44K - 1.6K \Rightarrow P_g = 42.4KW$$

$$P_{cu2} = P_g - P_d \Rightarrow P_d = (1-s) P_g$$

$$P_{cu2} = s P_g = 0.04 * 42.4K \Rightarrow P_{cu2} = 1.7KW$$

$$\tau_d = \frac{P_d}{\omega_m} = \frac{P_g}{\omega_s} = \frac{9.55 P_g}{n_s} = \frac{9.55 * 42.4 * 10^3}{1200} \Rightarrow \tau_d = 337.4 N.m$$

$$P_d (hp) \Rightarrow P_d = (1 - 0.04) * 42.4K = 40.7KW$$

$$P_{d_{hp}} = \frac{40.7 * 10^3}{746} \Rightarrow P_{d_{hp}} = 54.6 hp$$

$$P_{out} = P_d - P_{rot} = 40.7K - 0.5K = 40.2KW$$

$$P_{out_{hp}} = \frac{40.2K}{746} \Rightarrow P_{out_{hp}} = 53.9 hp$$

$$\tau_{out} = 9.55 \frac{P_{out}}{n_m} = \frac{9.55 * 40.2K}{1152}$$


* friction Torque = $\tau_{out} - \tau_d$

$$\Rightarrow \tau_{out} = 333.3 N.m$$

Q5 | 3-ph, 10hp, $V_{LL} = 230$ volt, $P = 4$, $f = 60$ Hz, Y-conn.


$S_{FL} = 0.045$, $P_{rot} = 0$.

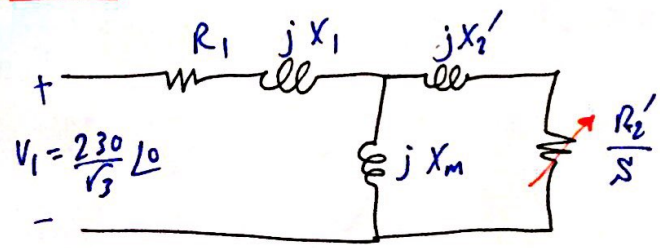- $R_1 = 0.35$
- $X_1 = 0.5$
- $X_2' = 0.5$
- $X_m = 15$



$$P_d = P_{out} = 10 * 747 = 7460 W$$
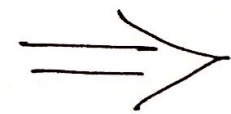
$$\tau_d = \frac{P_d}{\omega_m} = \frac{P_g}{\omega_s}$$




$$\Rightarrow T_d(s) = \frac{3 |V_{th}|^2}{\omega_s} * \frac{R_2' / s}{(R_{th} + \frac{R_2'}{s})^2 + (X_{th} + X_2')^2}$$

$$= \frac{9.55 \text{ Pd}}{n_m} = \frac{9.55 * 7460}{1719} = \underline{41.4 \text{ N.m.}}$$

$n_s = \frac{120 * 160}{4} = 1800 \text{ rpm.}$

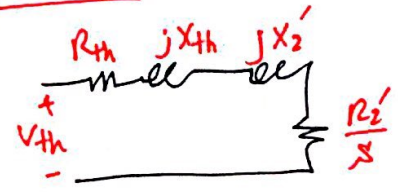$n_m = (1 - 0.045) n_s = 1719 \text{ rpm.}$



$$\Rightarrow V_{th} = V_{oc} = \frac{V_1 * j X_m}{R_1 + j(X_1 + X_m)} = \frac{230 \angle 0}{\sqrt{3}} * \frac{j 15}{0.35 + j 15.5}$$

$V_{th} = 128.5 \angle 13^\circ \text{ Volt.}$

$$Z_{th} = jX_m // (R_1 + jX_1) = j 15 * \frac{(0.35 + j 0.5)}{0.35 + j 15.5} = \underline{0.33 + j 0.5} \Omega$$

$\omega_s = \frac{2\pi n_s}{60} = 188.5 \text{ rad/s.}$

$$T_d(0.045) = \frac{3 (128.5)^2}{188.5} * \frac{R_2' / 0.045}{(0.33 + \frac{R_2'}{0.045})^2 + j(0.5 + 0.5)^2} = 41.4$$

solve for R_2'



OR more easier:

Use: $T_d \approx \frac{3 |V_1|^2}{\omega_s} * \frac{s}{R_2'}$

$$41.4 = \frac{3 (128.5)^2}{188.5} * \frac{0.045}{R_2'}$$

$R_2' = 0.286 \Omega.$

$$\Rightarrow T_{1/2 FL} = \frac{3 |V_1|^2}{\omega_s} * \frac{s_{1/2}}{R_2'}$$

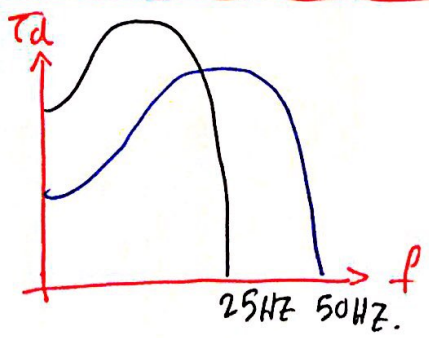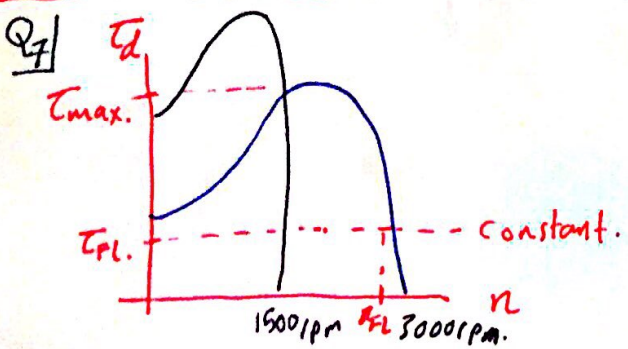

440 volt, 25 hp, 60 Hz, 1750 rpm $\rightarrow n_s = 1800$ rpm.

38

P=4. WRIM.

$$R_1 = 0.2$$

$$R_2 = 0.15$$

$$X_1 = 1.0$$

$$X_2 = 0.8$$

$$X_m = 30$$

$$\frac{R_2' + R_{ext}}{s} = \sqrt{R_1^2 + (X_1 + X_2')^2}$$


OR

$$\frac{R_2' + R_{new}}{1} = \sqrt{R_{th}^2 + (X_{th} + X_2')^2}$$

$$R_{new} = \sqrt{(0.2)^2 + (1.8)^2} - 0.15 = 1.7 \Omega$$

$$T_m = \frac{3|V|^2}{2\omega_s} * \frac{1}{R_1 + \sqrt{R_1^2 + X_{eq}^2}}$$

* T_{max} independent on R_2'

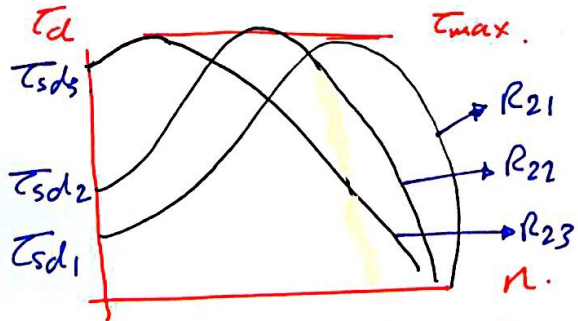


$$R_{23} > R_{22} > R_{21}$$

$$n_{T_{max}} = (1 - s_{max}) n_s$$

$$s_{max} = \frac{R_2'}{\sqrt{R_1^2 + X_{eq}^2}} = \frac{0.15}{\sqrt{(0.2)^2 + (1.8)^2}} \Rightarrow s_{max} = 0.08$$


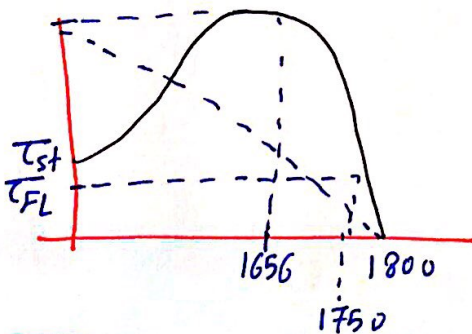
$$n_{T_{max}} = (1 - 0.08) * 1800 \Rightarrow n_{T_{max}} = 1656 \text{ rpm.}$$



* * *


Second Material.

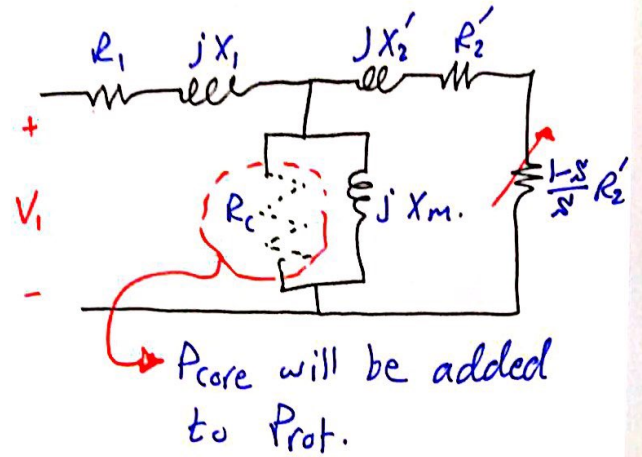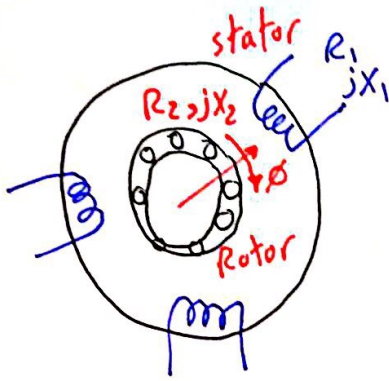* Determination of I.M Parameters of IEEE Model:



• DC Resistance Test:


* For Y-connected armature:

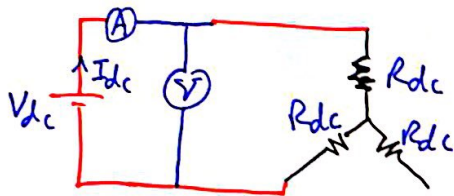

$$\frac{V_{dc}}{I_{dc}} = 2 R_{dc} \Rightarrow R_{dc} = \frac{1}{2} \frac{V_{dc}}{I_{dc}}$$

V_{dc}	x	V given. $A.$
I_{dc}	y	

* for Δ -connected armature:

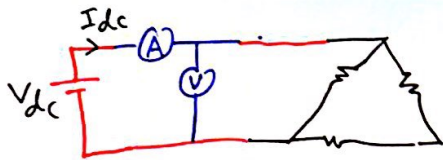

when the M/C is a standstill
 $n_m = 0, s = 1$

$$R_{dc} = \frac{3}{2} \frac{V_{dc}}{I_{dc}}$$

• Blocked (locked) Rotor Test:

$$\begin{matrix} n_m = 0 \\ s = 1 \end{matrix} \quad (R_2 + jX_2') \leq (R_c // jX_m)$$



V_{BL}	x	V
I_L	y	A
P_{BL}	z	$W.$

* Small voltage applied such that the current doesn't exceed the rated armature winding current.

$$|Z_{BL}| = |R_{eq} + jX_{eq}| \Rightarrow Z_{BL} = \sqrt{R_{eq}^2 + X_{eq}^2}$$

$$R_1 = R_{dc} \Rightarrow R_{eq} = R_1 + R_2'$$

$$Z_{BL} = \frac{V_{BL}}{I_{BL}}$$

$$P_{3\phi} = W_1 + W_2$$

$$P_{BL} = 3 |I_{BL}|^2 R_{BL}$$

$$R_{BL} = R_{eq}$$

we find R_{BL} :

$$R_{BL} = \frac{P_{BL}}{3 |I_{BL}|^2}$$

$$R_{BL} = R_1 + R_2' = R_{eq}$$


$$R_2' = R_{BL} - R_1$$

$$|X_{BL}| = \sqrt{\frac{Z_{BL}^2}{3} - R_{BL}^2} = X_1 + X_2' = X_{eq}$$

* Practically, according to the IEEE Model standard the Blocked rotor test is conducted at reduced frequency $f_{test} = \frac{1}{4} f_{rated}$ \Rightarrow for 60Hz $\Rightarrow f_{test} = 15Hz$
 for 50Hz $\Rightarrow f_{test} = 12.5Hz$.

* Actual Reactance:

$$\text{of } X_1 \text{ \& } X_2 \Rightarrow \frac{|X_1 + X_2|}{f_{rated}} = \frac{f_{rated}}{f_{test}} * X_{BL}$$

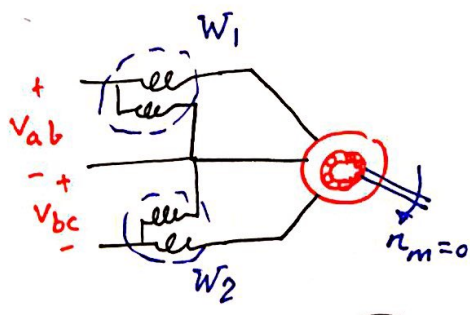

* for Y-con.:
 $Z_{BL} = \frac{|V_{BL}|}{\sqrt{3} I_{BL}}$
 * for Δ -con.:
 $Z_{BL} = \frac{V_{BL}}{\frac{|I_{BL}|}{\sqrt{3}}}$

** Study the classes of SCIM \Rightarrow Summarize them.



\Rightarrow see the slides.

• No - Load Test: (frated).

Rated Voltage is applied.

$n_m \approx n_s, \Sigma = 0.0$

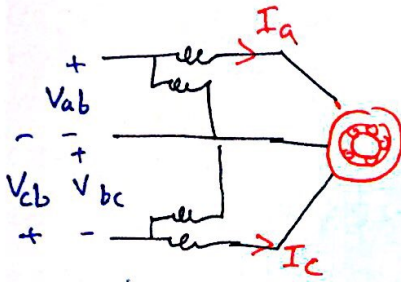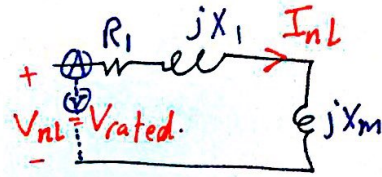$\frac{(1-\Sigma)}{\Sigma} R_2' \rightarrow \infty$



$W_1 = V_L I_L \cos(\theta_{V_{ab}} - \theta_{I_a})$
 $W_2 = V_L I_L \cos(\theta_{V_{cb}} - \theta_{I_c})$

*for Y-con.:

$\frac{V_{nl}/\sqrt{3}}{I_{nl}} = |Z_{nl}| = |R_1 + j(X_1 + X_m)|$
 $= \sqrt{R_1^2 + (X_1 + X_m)^2}$

$R_{nl} = R_1 = \frac{P_{nl}}{3 I_{nl}^2}$

$P_{cu1} = 3 I_{nl}^2 R_1 \Rightarrow P_{rot} = P_{nl} - 3 I_{nl}^2 R_1$
 P_{FSW} P_{core}

$(X_1 + X_m) = \sqrt{|Z_{nl}|^2 - R_1^2}$

* No-load Test determine the rotational losses. find X_m .

Example: $V_{LL} = 460V, f = 60Hz, Y-con., 40hp, Design B.$

The following data were obtained:

$I_L \text{ rated} = 57.8 A.$

$f_{test} = 15 Hz.$

Blocked Rotor

V_{BL}	38.2	V
I_{BL}	58	A
P_{BL}	2573.4	W

No load Test.

V_{nl}	460	V
I_{nl}	32.7	A
P_{nl}	4604.4	W

DC Test

V_{dc}	12 V
I_{dc}	59 A.



* DC Test:

$$R_{dc} = R_1 = \frac{1}{2} \frac{V_{dc}}{I_{dc}} = \underline{0.1 \Omega}$$

see class B.

$$\begin{aligned} \rightarrow X_1 &= 0.4 \text{ Xeq.} \\ X_2' &= 0.6 \text{ Xeq.} \end{aligned}$$

* BL Rotor:

$$Z_{BL} \Big|_{15\text{Hz}} = \frac{V_{BL}/\sqrt{3}}{I_{BL}} = \frac{36.2/\sqrt{3}}{58} = \underline{0.36 \Omega}$$

$$X_{BL} \Big|_{15\text{Hz}} = \sqrt{Z_{BL}^2 - (R_1 + R_2')^2}$$

$$R_1 + R_2' = \frac{P_{BL}/3}{(I_{BL})^2} = 0.255 \Omega/\text{ph.}$$

$$= \sqrt{(0.36)^2 - (0.255)^2} = \underline{0.254 \Omega @ f=15\text{Hz.}}$$

$$\begin{aligned} R_2' &= 0.255 - 0.1 \\ &= \underline{0.155 \Omega} \end{aligned}$$

* No-load Test:

$$\begin{aligned} (X_1 + X_2') \Big|_{60\text{Hz}} &= 4 * 0.254 \\ &= 1.016 \Omega/\text{ph.} \end{aligned}$$

$$P_{nl} = 3|I_{nl}|^2 R_{nl} = P_{cu1} \Big|_{nl} + P_{rot}$$

or using:

$$S_{nl,ph} = V_{nl} I_{nl} = \frac{460 * 32.7}{\sqrt{3}} = \underline{8684.5 \text{ VA.}}$$

$$Q_{nl} = \sqrt{S_{nl,ph}^2 - P_{nl,ph}^2} = \sqrt{(8684.5)^2 - (1554.8)^2} = \underline{8544.2 \text{ VAR.}}$$

$$Q_{nl,ph} = |I_{nl}|^2 (X_1 + X_m) \Rightarrow X_1 + X_m = \frac{8544.2}{(32.7)^2} = \underline{8 \Omega}$$

$$P_{rot} = P_{nl} - 3|I_{nl}|^2 R_1$$

$$= 4664.4 - 3(32.7)^2(0.1) = \underline{4325 \text{ W.}}$$

$$\text{so } X_m = 8 - 0.407$$

$$X_m = \underline{7.58 \Omega}$$

* Induction Generator (I.G.):

$$n_m > n_s$$


$$s = \frac{n_s - n_m}{n_s} < 0$$


$$P_d = 3|I_2'|^2 \frac{(1-s)R_2'}{s}$$

when $s < 0$:

$$P_d < 0$$


This means that the M/C work as Gen.

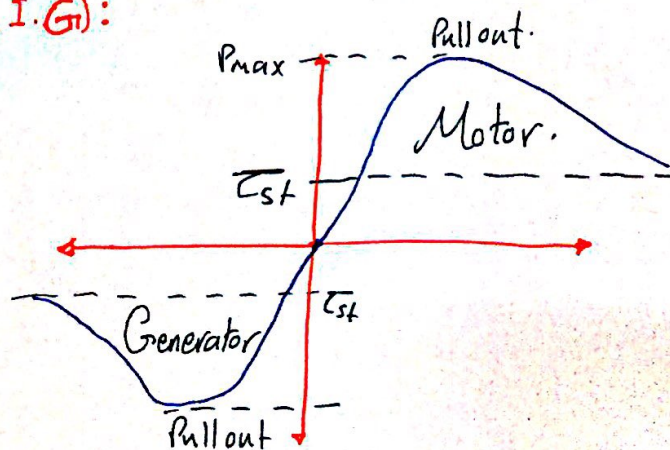

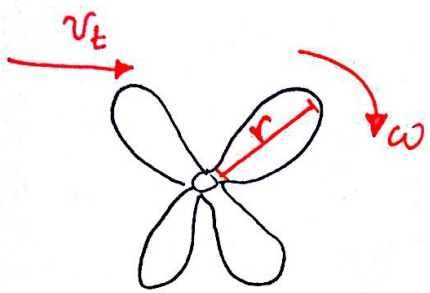


$v_t \equiv$ Tangential Speed
 $w \equiv$ Angular Speed.

$v_t = w \cdot r$

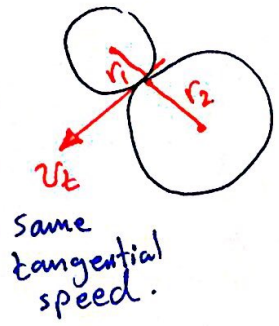


$w_1 r_1 = w_2 r_2$
 $\frac{w_1}{w_2} = \frac{r_2}{r_1} \Rightarrow w_1 = \frac{r_2}{r_1} w_2$

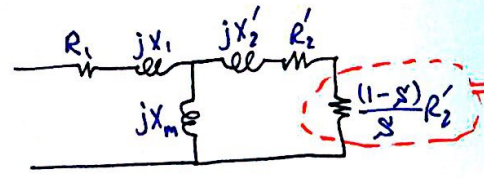
* we can increase the speed of the motor by increasing the size of gears.



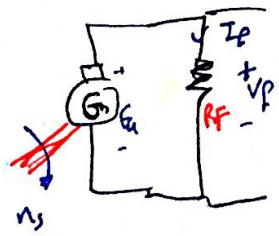
(-ve) Resistance.
 it will generate a real active power.



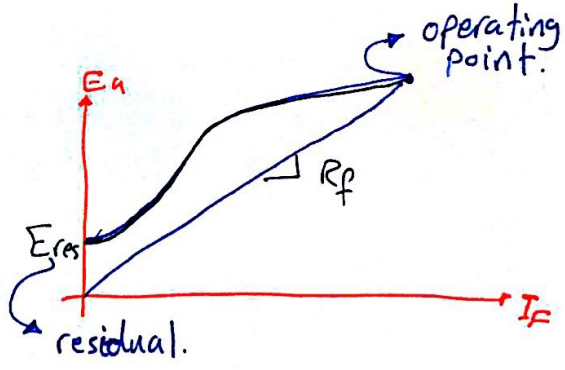
$E_a = K_a \phi \omega$
 $E_a = K I_f \phi$
 $E \propto I_f$





* Capacitor Bank:

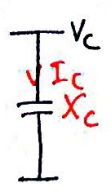

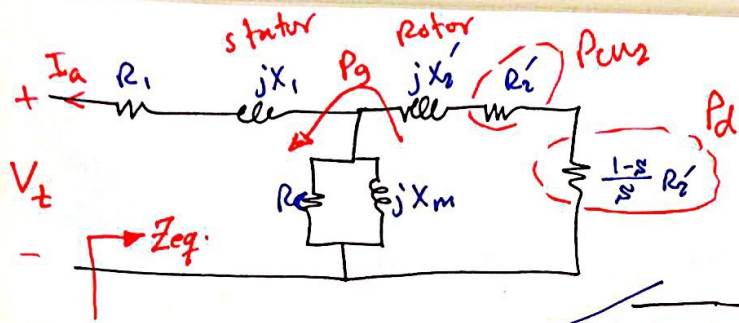$Q_{c,ph} = \frac{V_c^2}{X_c} = \frac{V_c^2}{\frac{1}{\omega C}} = \omega C V_c^2$



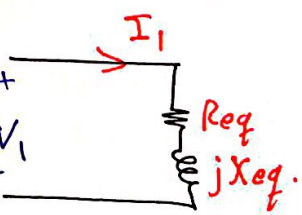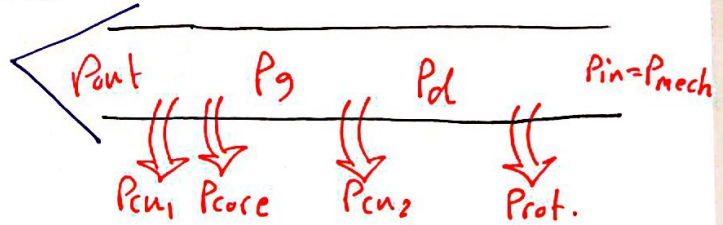
$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$



$$\Rightarrow P_{in} = 3|I_1|^2 Re_{eq} \quad (-ve \text{ power})$$

* * *


* Single phase I.M :

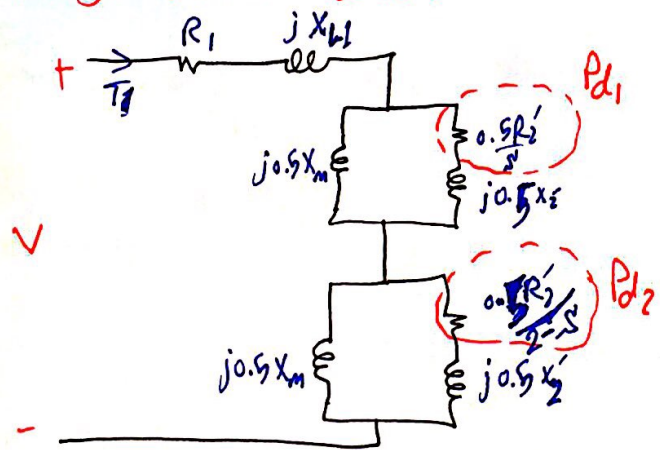

$$P_{d \text{ total}} = P_{d1} + P_{d2}$$

Very important.

• No-load Test :

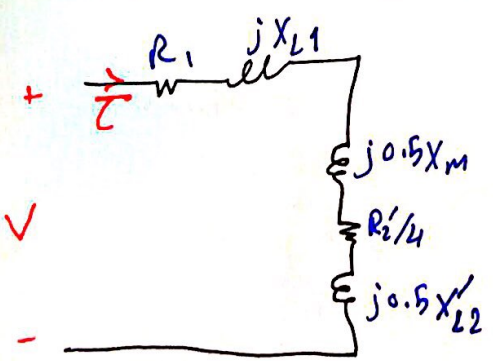

$$Z_{NL} = \frac{V_{NL}}{I_{NL}} = \sqrt{R_{NL}^2 + X_{NL}^2}$$

$$= \sqrt{\left(R_1 + \frac{R_2'}{4}\right)^2 + \left(X_1 + \frac{X_2'}{2} + \frac{X_m}{2}\right)^2}$$






$$\cos \theta_{nL} = \frac{P_{nL}}{V_{nL} I_{nL}} \Rightarrow X_{nL} = Z_{nL} \sin \theta_{nL}$$

So, $X_{nL} = X_1 + 0.5X_2' + 0.5X_m$


$$\Rightarrow X_m = 2(X_{nL} - X_1 - 0.5X_2')$$

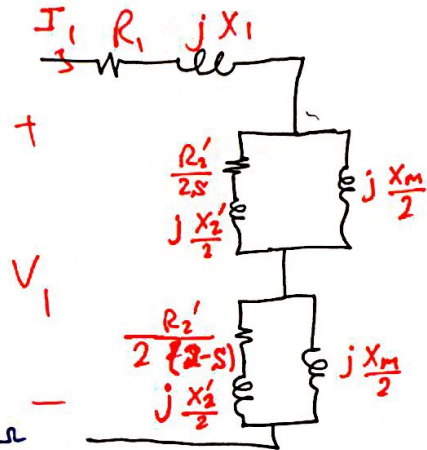Example (in slides):

$V_{BL} = 36 \text{ volt.}$ $V_{nL} = 110 \text{ volt.}$
 $I_{BL} = 5 \text{ A.}$ $I_{nL} = 4 \text{ A.}$
 $P_{BL} = 100 \text{ W.}$ $P_{nL} = 90 \text{ W.}$
 $R_1 = 1.8 \Omega$



* Blocked Test:

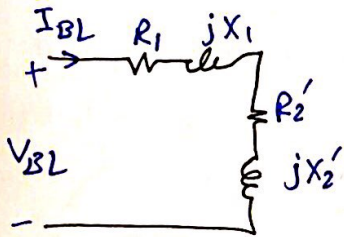

$$Z_{BL} = \frac{V_{BL}}{I_{BL}} = \frac{36}{5} = 7.2 \Omega$$

$$\cos \theta = \frac{P_{BL}}{I_{BL} V_{BL}} = \frac{100}{36 * 5} \Rightarrow \theta = 56.25^\circ$$


$$Z_{BL} \angle \theta = 7.2 \angle 56.25^\circ = 4 + j6 = R_{BL} + jX_{BL}$$

$$\Rightarrow R_1 + R_2' = 4 \Rightarrow R_2' = 2.2 \Omega$$

$$X_1 + X_2' = X_{BL} = 6$$

$$X_1 = X_2' = \frac{X_{BL}}{2} = 3 \Omega$$

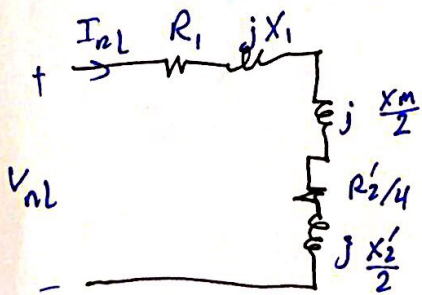* No Load Test: $n_m \approx n_s \Rightarrow S=0$




$$Z_{nL} = \frac{V_{nL}}{I_{nL}} = \frac{110}{4} = 27.5 \Omega$$

$$\cos \theta_{nL} = \frac{P_{nL}}{V_{nL} I_{nL}} \Rightarrow \theta_{nL} = 78.2^\circ$$

$$Z_{nL} \angle \theta_{nL} = 27.5 \angle 78.2^\circ = 5.6 + j26.9 \Omega$$

$$X_m = 2(X_{nL} - X_1 - 0.5X_2') = 2(26.9 - 3 - 3/2) \Rightarrow X_m = 44.8 \Omega$$
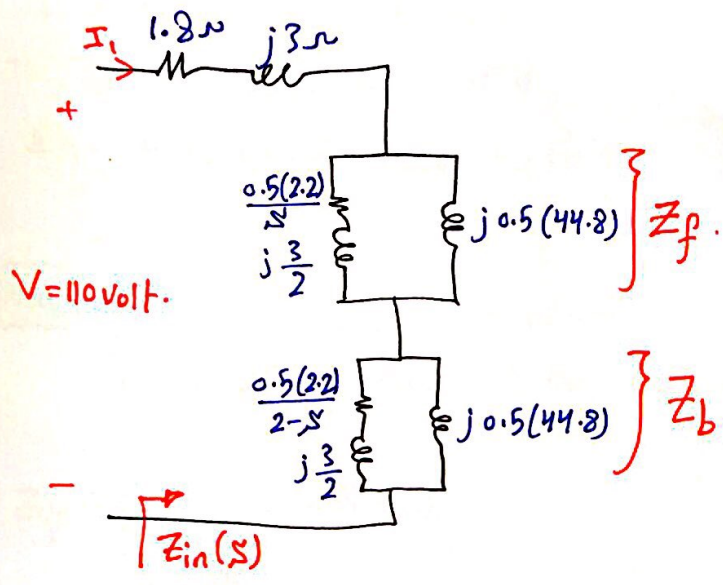
$$P_{rot} = P_{nL} - [I_{nL}]^2 (R_1 + \frac{R_2'}{4}) = 52.4 \text{ W}$$



$$S_{FL} = \frac{n_s - n_m}{n_s} = \frac{1000 - 950}{1000} = 5\%$$

$$Z_{in} = R_1 + jX_1 + Z_f + Z_b$$

substitute:

$$Z_{in} = 12.76 + j15.45 = 20 \angle 50.4^\circ \Omega$$

$$I_{in} = \frac{110 \angle 0}{20 \angle 50.4} = \underline{\underline{5.5 \angle -50.4^\circ A}}$$



$$Pf = \cos(50.4)$$

$$\underline{\underline{Pf = 0.6374}} \text{ lagging.}$$

* * * *



* The problem of single-phase IM that it is NOT self-started.

* 1-ph I.M:

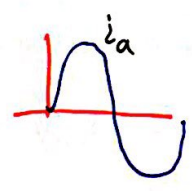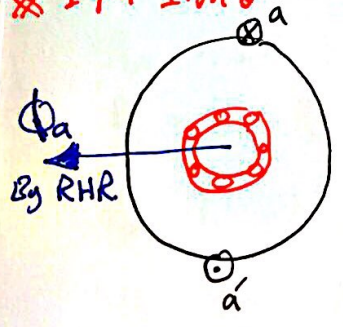

⇒ Stationary flux.
No Induction.
No Starting Torque.

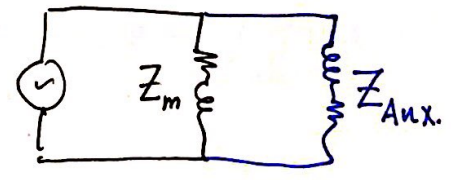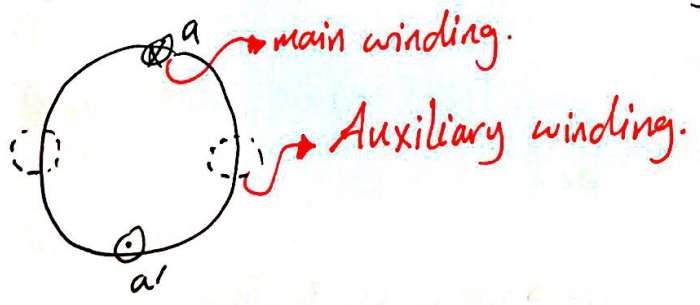To make the field Rotating, we add Auxiliary winding.



Dr. Eyad Abu-AlFeilat

47

Tutorial Solutions #4

By: Mohammad Abu-Hashia.

Q1 120 volt, $\frac{1}{4}$ hp, 60 Hz, $P=4$

$R_1=2, R_2=2.8, X_1=2.56, X_2=2.56, X_m=60.5 \Omega$.

$$Z_{eq}(s) = R_1 + jX_1 + Z_f + Z_b$$

at $s=0.05$

$$Z_{eq} = 17.1 + j17.7 \Omega$$
$$= 24.6 \angle 46.1^\circ \Omega$$

$$I_1 = \frac{V_1}{Z_{eq}} = \frac{120 \angle 0^\circ}{24.6 \angle 46.1^\circ} \Rightarrow I_1 = 4.9 \angle -46.1^\circ$$

$$PF = \cos(46.1) \Rightarrow PF = 0.6934 \text{ Lagging.}$$

$$P_{in} = V_1 I_1 \cos \theta = 120 * 4.9 * 0.693 = 407.5 \text{ W.}$$

$$P_g = P_{in} - P_{cu1} = 407.5 - 14.91^2 * 2 = 359.5 \text{ W.} = P_{gf} + P_{gb}$$

$$P_d = (1-s) P_{gnet} = (1-s) [P_{gf} - P_{gb}]$$

for P_{gf} : $P_{gf} = |I_f|^2 \frac{R_2'}{2}$

for P_{gb} : $P_{gb} = |I_b|^2 \frac{R_2'}{2}$

$$\tau_a = \frac{P_{gnet}}{\omega_s} = \frac{P_{gf} - P_{gb}}{\omega_s}$$
$$= \frac{P_{dnet}}{\omega_m} = \frac{P_{df} - P_{db}}{\omega_m}$$

Need I_f : $I_f = (4.9 \angle -46.1) \frac{j30.25}{\frac{1.4}{0.05} + j(30.25 + 1.28)} = 3.52 \angle -4.5^\circ \text{ A.}$


So Now:

$$P_{gf} = (3.52)^2 * \frac{2.8/2}{0.05} = 346.9 \text{ W.}$$

or more simple USE:



$$P_{gf} = |I_1|^2 R_f$$
$$= (4.9)^2 * 14.4$$
$$= 345.7 \text{ W.}$$

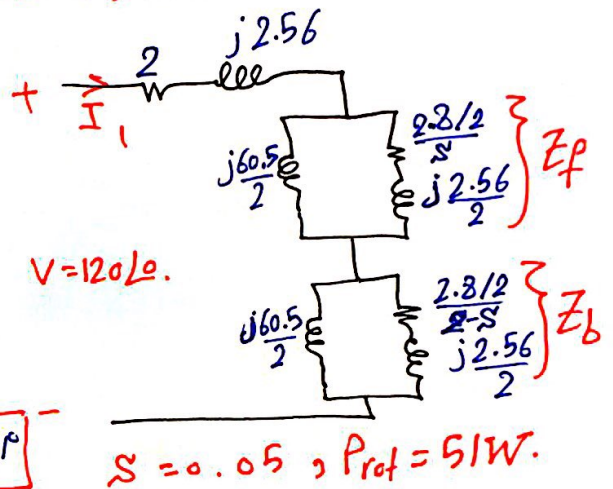

$$\Rightarrow P_{g_b} = |I_1|^2 R_b = (4.9)^2 * 0.66 = \underline{15.85 \text{ W}}$$

$$P_d = (1-s) [P_{g_f} - P_{g_b}] = (1-0.05) [345.7 - 15.85]$$

$$\underline{P_d = 313.2 \text{ W}}$$

$$\Rightarrow P_{out} = P_d - P_{rot} = 313.2 - 51$$

$$\underline{P_{out} = 262.2 \text{ W}}$$

$$\eta = \frac{P_{out}}{P_{in}} * 100\% = \frac{262.2}{407.8} * 100\% = \underline{64.3\%}$$

$$\tau_d = \frac{P_{g_{net}}}{\omega_s} = \frac{P_{d_{net}}}{\omega_m} = \frac{345.7 - 15.85}{188.5} = \underline{1.75 \text{ N.m}}$$

$$\tau_{out} = \frac{P_{out}}{\omega_m} = \frac{262.2}{(1-0.05)*188.5} = \underline{1.465 \text{ N.m}}$$

Q2 Same as question 1 with $s = 0.025$

Answers:

$$Z_f = 12.4 + j23.3 \Omega$$

$$Z_b = 0.65 + j1.24 \Omega$$

$$Z_{eq} = 15.1 + j27.1 \Omega$$

$$I_1 = 3.87 \angle -60.9^\circ$$

$$PF = 0.4863 \text{ lagging}$$

$$P_{g_f} = 185.7 \text{ W}$$

$$P_{g_b} = 9.7 \text{ W} \Rightarrow P_{g_{net}} = 176 \text{ W}$$

$$P_{d_{net}} = 171.6 \text{ W}$$

$$P_{in} = 225.8 \text{ W}$$

$$P_g = P_{in} - P_{cu1} = 195.9 \text{ W}$$

$$P_{out} = 120.6 \text{ W}$$

$$\eta = 53.4\%$$

Q3 $n_m = 400 \text{ rpm} \Rightarrow s = \frac{1800 - 400}{1800} = 0.778 = 77.8\%$

Answers:

$$Z_f = 1.65 + j1.82 \Omega$$

$$Z_b = 1.1 + j1.27 \Omega$$

$$Z_{eq} = 4.7 + j5.15 \Omega$$

$$I_1 = 17.2 \angle -47.6^\circ$$

$$PF = 0.6743 \text{ lagging}$$

$$P_{g_f} = 488.1 \text{ W}$$

$$P_{g_b} = 325.4 \text{ W} \Rightarrow P_{g_{net}} = 162.7 \text{ W}$$

$$P_{d_{net}} = 36.1 \text{ W}$$

$$P_{in} = 1391.8 \text{ W}$$

$$P_g = P_{in} - P_{cu1} = 800.12 \text{ W}$$

$$P_{out} = -14.9 \text{ W}$$

$$\eta = 1.1\%$$

Q4

$S = 0.05$

$Z_f = 15.1 + j5.9 \Omega$

$Z_b = 0.43 + j0.99 \Omega$

$Z_{eq} = 16.8 + j.8.9 \Omega$

$I_1 = 11.6 \angle -27.8^\circ A$

$Pf = 0.8846$ Lagging.

$P_{in} = 2257.5 W.$

$P_{gf} = 2031.9 W$
 $P_{gb} = 57.9 W \Rightarrow P_{gnet} = 1974 W.$

$P_{dnet} = 1875.3 W.$

$P_{out} = 1584.3 W.$

$P_g = P_{in} - P_{cu1} = 2082.6 W.$

$\tau_d = 18.8 N.m.$

$\tau_{out} = 15.9 N.m.$

$\eta = 70.2\%$



$I_1 = \frac{V_1}{Z_{eq}}$

$Pf = \cos \theta$

$P_{in} = V_1 I_1 Pf$

$P_g = P_{in} - P_{cu1}$


$P_{dnet} = (1 - s) P_{gnet}$

$P_{gnet} = P_{gf} - P_{gb}$

$P_{out} = P_{dnet} - P_{rot}$


$\tau_d = \frac{P_d}{\omega_m}$ & $\tau_{out} = \frac{P_{out}}{\omega_m}$

$\eta = \frac{P_{out}}{P_{in}} * 100\%$

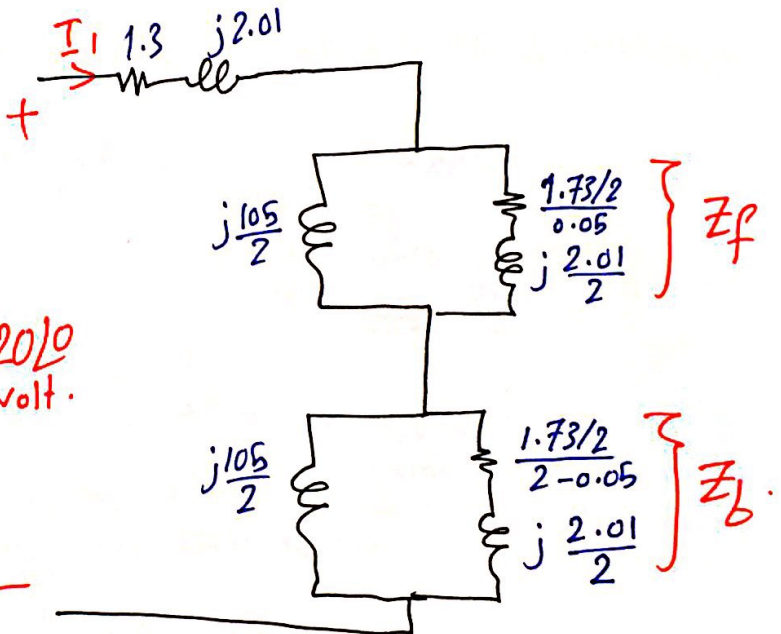

* Special Motors:

* DC Motors:

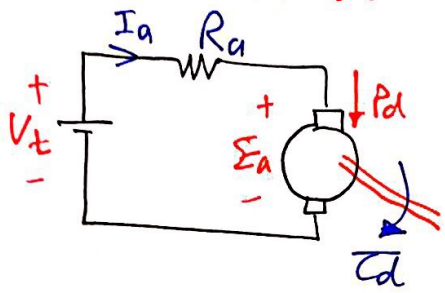

$P_d = E_a I_a$

$E_a = K \phi \omega$
 $E_a \propto n$
 $T_d = K I_a$
 $I_a = \frac{V_t - E_a}{R_a}$

* flux always take the path with less Reluctance.
 as the current which take the path with less Resistance.

• I.G: (Example) \Rightarrow Question #8 in Tutorial #3:

480V, 60Hz, 6-poles, Δ -conn. I.M with: $R_1 = 0.461, R_2 = 0.258, X_1 = 0.507, X_2 = 0.309, X_m = 30.74$
 $P_{rot} = 2.45 \text{KW}, n_m = 1224 \text{rpm}.$


a) find slip?

$\Rightarrow n_s = 1200 \text{rpm} \cdot \text{so } s = \frac{1200 - 1224}{1200} = -0.02 = -2\% \text{ (I.G.)}$

b) find I_1 ?

$Z_{eq} |_{s=-0.02} = -10.3 + j5.29 \Omega$

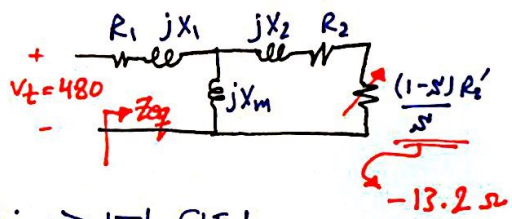$\Rightarrow I_1 = \frac{V_1}{Z_{eq}} = \frac{480}{-10.3 + j5.29} = -36.7 - j18.8 = 41.2 \angle -152.9^\circ \text{ A}$



c) find Q_1 & Q_2 ?

$P_t = \sqrt{3} I_L V_L \cos \theta$
 $Q_t = \sqrt{3} I_L V_L \sin \theta$

$\Rightarrow P_t = -53 \text{KW absorbed} \Rightarrow |I_L| = 71.7 \text{A}$
 $Q_t = 27.2 \text{KVAR} \hookrightarrow \text{or } 53 \text{KW supplied}$

d) find P_g ?

$I_2 = \frac{I_1 jX_m}{R_2 + j(X_m + X_2)} = 37.8 \angle -175.5^\circ \text{ A} \Rightarrow P_g = 3 |I_2|^2 \frac{R_2'}{s} = -55.4 \text{KW}$

e) find P_d ?

$P_d = (1-s) P_g = 1.02 * (-55.4) = -56.5 \text{KW}$

f) find P_{mech} ?

$P_{mech} = P_d - P_{rot} = (-56.5 - 2.4) \text{K} = -58.9 \text{KW}$

g) find η ?

$\eta = \frac{\text{out}}{\text{in}} * 100\% = \frac{53}{58.9} * 100\% \Rightarrow \eta = 89.9\%$

* * * End of Material * * *
 Good Luck.