

Power Unit

Grade: 20/20

University of Jordan Faculty of Engineering & Technology Electrical Engineering Department
 EE371: Electrical Machines I First Exam First Semester 2015-2016 02/11/2015 Time: 1 Hour

Student Name: [Redacted] Student ID#: [Redacted] Serial #: [Redacted]

Questions 1 (25 mark)

SHOW YOUR CALCULATIONS

$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$

In the magnetic system shown in Fig. 1,

$l_1 = 300 \text{ mm}$
 $A_1 = 200 \text{ mm}^2$
 $\mu_{r1} = 2250$

$l_2 = 100 \text{ mm}$
 $A_2 = 400 \text{ mm}^2$
 $\mu_{r2} = 1350$

$l_3 = 300 \text{ mm}$
 $A_3 = 200 \text{ mm}^2$
 $\mu_{r3} = 2250$

$I = 0.5 \text{ A}$
 $N = 25$

Draw the equivalent magnetic circuit and determine the following:

- the reluctances \mathcal{R}_1 , \mathcal{R}_2 and \mathcal{R}_3 of the paths l_1 , l_2 and l_3 .
- the flux ϕ and flux density B in the three branches of the core ϕ_1 , ϕ_2 , ϕ_3 , B_1 , B_2 , and B_3 .
- the core inductance L .

$\mathcal{R} = \frac{L}{\mu A}$

$\mathcal{R}_1 = \mathcal{R}_3 = \frac{300 \times 10^{-3}}{2250 \mu_0 (200 \times 10^{-6})}$

$\mathcal{R}_1 = \mathcal{R}_3 = 530.5 \text{ k At/wb}$

$\mathcal{R}_2 = \frac{100 \times 10^{-3}}{1350 \mu_0 (400 \times 10^{-6})}$

$\mathcal{R}_2 = 147.4 \text{ k At/wb}$

$\mathcal{F} = NI$
 $\mathcal{F} = 0.5 \times 25 = 12.5 \text{ At}$

$\phi_1 = \frac{\mathcal{F}}{\mathcal{R}_1} = \frac{12.5}{530.5} = 23.56 \mu\text{wb}$

$\phi_2 = \phi_1 \frac{\mathcal{R}_3}{\mathcal{R}_3 + \mathcal{R}_2} = 15.14 \mu\text{wb}$

$\phi_3 = \phi_1 - \phi_2 = 8.42 \mu\text{wb}$

$B = \frac{\phi}{A}$

$B_1 = \frac{8.42 \times 10^{-6}}{200 \times 10^{-6}} = 0.0421 \text{ T}$

$L \frac{d\phi}{dt} = N \frac{d\mathcal{F}}{dt}$

$L = N \frac{\phi}{\mathcal{F}}$

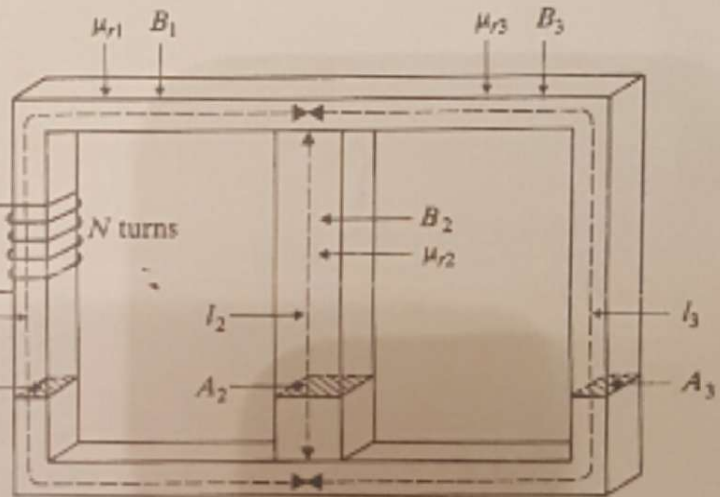


Fig. 1

$\mathcal{R}_1 =$	530.5 k At/wb
$\mathcal{R}_2 =$	147.4 k At/wb
$\mathcal{R}_3 =$	530.5 k At/wb
$\phi_1 =$	19.35 μwb
$\phi_2 =$	15.14 μwb
$\phi_3 =$	4.2 μwb
$B_1 =$	0.092 T
$B_2 =$	0.038 T
$B_3 =$	0.021 T
$L =$	2.97 mH

Question #2 (25 marks)

SHOW YOUR CALCULATIONS

25

The core loss in a certain electrical apparatus operating at its rated voltage and frequency of $V_1 = 240$ V and $f_1 = 25$ Hz is $P_{e1} = 1500$ W. When the apparatus is connected to a 50-Hz source whose voltage V_2 is adjusted such as to cause the flux density B_2 to be 70.7% of its rated value (B_1), the core loss becomes $P_{e2} = 2000$ W. Assume the Steinmetz exponent $n = 2$, determine:

- a. the new source voltage, V_2 .
- b. P_{e1} , P_{h1} , P_{e2} and P_{h2} .

$$\frac{B_2}{B_1} = 0.707 \quad \frac{V_2}{V_1} = \frac{B_2 \cdot f_2}{B_1 \cdot f_1}$$

$V_2 =$	334.36 V	
$P_{e1} =$	500 W	✓
$P_{h1} =$	1000 W	✓
$P_{e2} =$	1000 W	✓
$P_{h2} =$	1000 W	✓

$$P_{e1} = P_{m1} + P_{e1}$$

$$1500 = k_m f_1 B_1^n + k_e (f_1 B_1)^2$$

$$2000 = k_m f_2 B_2^n + k_e (f_2 B_2)^2$$

$$\frac{P_{m2}}{P_{m1}} = \frac{f_2}{f_1} \left(\frac{B_2}{B_1} \right)^n$$

$$P_{m2} = 0.5 P_{m1} \quad \text{--- (1)}$$

$$\frac{P_{e2}}{P_{e1}} = \left(\frac{f_2}{f_1} \right)^2 \times \left(\frac{B_2}{B_1} \right)^2$$

$$P_{e2} = 0.5 P_{e1} \quad \text{--- (2)}$$

Solving for (1) and (2) →

~~$$P_{m1} = 1500$$~~

$$2000 = P_{m2} + P_{e2}$$

$$1500 = P_{m1} + P_{e1}$$

$$500 = P_{e1} = 500 \text{ W} \quad P_{e2} = 1000 \text{ W}$$

$$P_{m1} = 1000 \text{ W}$$

$$P_{m2} = 1000 \text{ W}$$

$$\frac{240}{V_2} = \frac{25}{50} \cdot \frac{B_1}{B_2}$$

$$V_2 = (240) \left(\frac{50}{25} \right) \left(\frac{B_1}{B_2} \right)$$

~~$$V_2 = 480$$~~

$$V_2 = 334.36 \text{ V}$$

Power Unit

Question #3 (25 marks)

SHOW YOUR CALCULATIONS

25

The following measurements were obtained from tests carried out on a 10-kVA, 2300/230-V, 50-Hz distribution transformer:

Test	O.C.T (HV winding open)	S.C.T (LV winding shorted)
Voltage	$V_{oc} = 230 \text{ V}$	$V_{sc} = 120 \text{ V}$
Current	$I_{oc} = 0.45 \text{ A}$	$I_{sc} = 4.5 \text{ A}$
Power	$P_{oc} = 70 \text{ W}$	$P_{sc} = 240 \text{ W}$


Draw and determine the equivalent circuit parameters of the transformer referred to the low-voltage side (secondary).

O.C.T (secondary) (LV)

$R_c'' =$	769.23 Ω
$X_M'' =$	694.44 Ω
$R_{eq}'' =$	0.1185 Ω
$X_{eq}'' =$	0.2384 Ω

$$\cos \phi = \frac{P_{oc}}{I_{oc} \cdot V_{oc}}$$

$$\cos \phi = 0.676$$

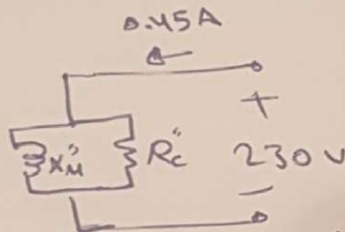

$$Y'' = \frac{I_{oc}}{V_{oc}} \angle -\phi = (1.3 + j1.44) \text{ mS}$$


$$R_c'' = \frac{1}{1.3 \text{ m}} = 769.23 \Omega$$

$$X_M'' = \frac{1}{1.44 \text{ m}} = 694.44 \Omega$$

Power Unit

S.C.T (Primary HV)
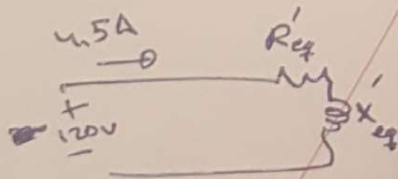
$$\text{as } I_{rated \text{ primary}} = \frac{10 \text{ kVA}}{2300} = 4.34 \text{ A}$$




$$Z' = \frac{V_{sc}}{I_{sc}} \angle \cos^{-1} \left(\frac{P}{I_{sc} V_{sc}} \right)$$

$$Z' = 11.85 + j23.89 \Omega$$

$$R_{eq}' = 11.85 \Omega \quad X_{eq}' = 23.89 \Omega$$
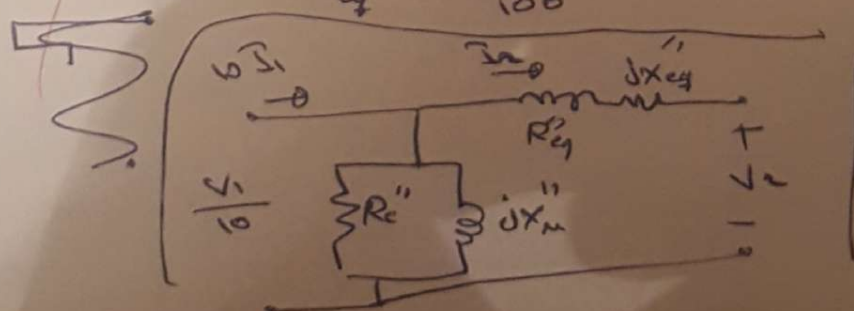
$$R_{eq}'' = \frac{11.85}{100} \Omega \quad X_{eq}'' = \frac{23.89}{100} \Omega$$



Question #4 (25 marks)

SHOW YOUR CALCULATIONS

CS


A single-phase 10-kVA, 2200/220-V transformer has the following parameters:

$R_1 = 4.0 \Omega$, $R_2 = 0.04 \Omega$, $X_1 = 5.0 \Omega$, $X_2 = 0.05 \Omega$, $R_c = 35 \text{ k}\Omega$, $X_m = 4.0 \text{ k}\Omega$

The transformer is supplying its rated load to a load at 220 V and 0.8 PF lagging.

- Draw the approximate equivalent circuit of this transformer, showing values of the elements referred to the high-voltage side (primary).
- Determine the input voltage V_1 of the transformer to meet the above load.
- Calculate the full-load voltage regulation at 0.8 PF lagging.
- Calculate the full-load efficiency at 0.8 PF lagging.

Power Unit

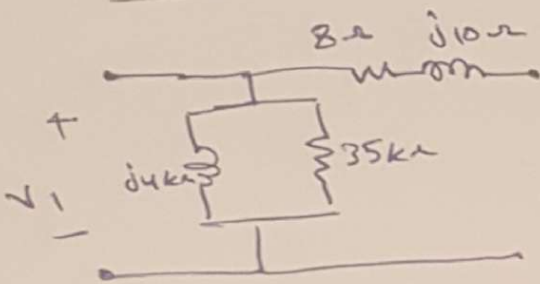


$R_{eq1} = R_1 + 100 R_2$

$X_{eq1} = X_1 + 100 X_2$

$R_c =$	35 kΩ	?
$X_m =$	4 kΩ	?
$R'_{eq} =$	8 Ω	
$X'_{eq} =$	10 Ω	
$V_1 =$	2256.4 V	
% V.R FL	2.56 %	
% η FL	96.26 %	

$P = VI \cos \phi$

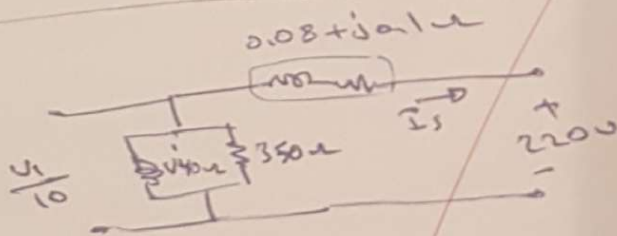

$I_s = \frac{10 \text{ kVA}}{220 \times 0.8}$

$I_s = \frac{10 \text{ kVA}}{220} \angle -\cos^{-1}(0.8)$

$I_s = 45.45 \angle -36.9^\circ \text{ A}$

$\frac{V_1}{10} = 220 + I_s (0.08 + j0.1)$

$\frac{V_1}{10} = 225.64 \angle 0.37^\circ \text{ V}$

$V_1 = 2256.4 \text{ V}$

$P_{cu} = I_s^2 \times R'_2$
 $= (45.45)^2 \times 0.08$
 $= 165.25 \text{ W}$

$\%VR = \frac{\frac{V_1}{10} - V_{FL}}{V_{FL}} \times 100\% = \frac{225.64 - 220}{220} \times 100\%$

$\%VR = 2.56\%$

$P_{core} = \frac{(\frac{V_1}{a})^2}{R_c} = 145.5 \text{ W}$

$\eta = \frac{P_{out}}{P_{out} + P_{cu} + P_{core}}$
 $= \frac{10 \text{ kVA} \times 0.8}{10 \text{ kVA} \times 0.8 + 145.5 + 165.25}$
 $= 96.26\%$