

Name (in Arabic)

المهندس محمد

Student Number 2110478

1. A single phase, 100 kVA, 2000/400V transformer, the per unit resistance of the transformer is 0.015 and the reactance is 0.025. The core resistance referred to the high voltage side is 4000Ω and the magnetizing reactance is 1000 Ω.

6 marks

- (i) Find the approximate equivalent parameters referred to the low voltage side.

$$a = \frac{2000}{400} = 5$$


in pu unit the resistance and reactance same in LV and HV.

$$R_{e1} = 4000/a^2 = \frac{4000}{25} = 160 \Omega$$

$$X_{m1} = 1000/a^2 = \frac{1000}{25} = 40 \Omega$$


$$R_{eq1} = 0.015 \times \left(\frac{400^2}{100 \times 10^3}\right) = 0.024$$
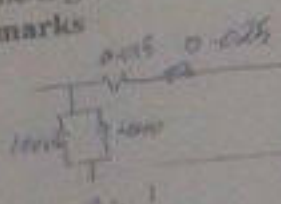
$$X_{eq1} = 0.025 \times \left(\frac{400^2}{100 \times 10^3}\right) = 0.04$$



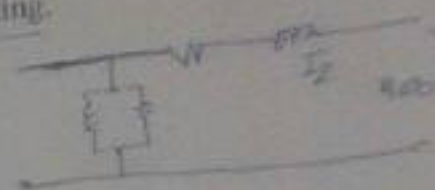- (ii) Find the voltage regulation at full load and 0.8 power factor lagging.

$$\begin{aligned} \%VR &= I_2 R_{eq} \cos \theta + I_2 X_{eq} \sin \theta \\ &= 1 [0.015 (0.8) + 0.025 (0.6)] \\ &= 2.7\% \end{aligned}$$



- (iii) Draw the phasor diagram



- (iii) Find the maximum efficiency at 0.9 power factor lagging

$$\begin{aligned} \eta_{max} &= \frac{V I_{max} \cos \theta}{V I_{max} \cos \theta + 2 P_c} = \frac{K \cos \theta}{K \cos \theta + 2 P_c} \\ &= \frac{0.916 (0.9)}{0.916 (0.9) + 2 \times \left(\frac{1}{100}\right)} = 97.34\% \end{aligned}$$

$$K = \sqrt{\frac{\frac{1}{R_{eq1}}}{\frac{1}{R_{eq2}}}} = \sqrt{\frac{1}{0.015}} = 0.816$$

- (iv) Find all day efficiency given that load is:

- 8 hours for 1/2 load at 0.9 power factor lagging
- 6 hours for full load at 0.8 power factor lagging
- 6 hours for 1/4 load at unity power factor
- 4 hours at no load

$$\text{all day } \eta = \frac{\sum \text{energy in 24 hrs}}{\sum \text{energy in 24 hrs} + \sum \text{loss in 24 hrs}}$$

$$= \frac{(8 \times \frac{1}{2} \times 0.9) + (6 \times (1) \times 0.8) + (6 \times \frac{1}{4} \times 1) \times 100}{9.9 + 24 (0.01) + (8 (\frac{1}{2})^2 + (1)^2 + 6 (\frac{1}{4})^2) \times 100} = 85.12\%$$


5

$$P_{iR} = \frac{1}{100} = 0.01$$

85.12

2. The magnetic circuit below is made of iron whose characteristics is shown below. Find the current (i) so that 4mwb flux crosses the airgap in upward direction. The fringing factor of the airgap is 1.05. Find the current i.

7 marks

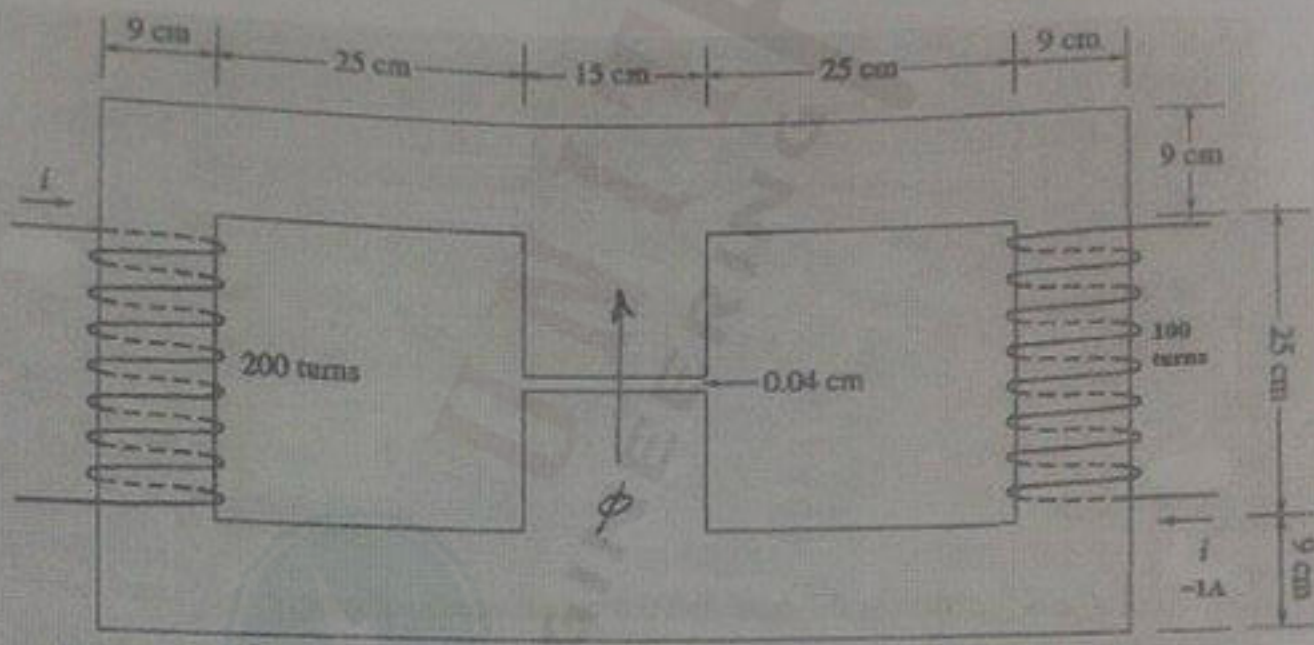


$$\Phi_g = 4 \times 10^{-3}$$

$L??$

$$\text{Fringing} = 1.05$$

Core depth 5 cm

$$H_{Lc} = N_i$$

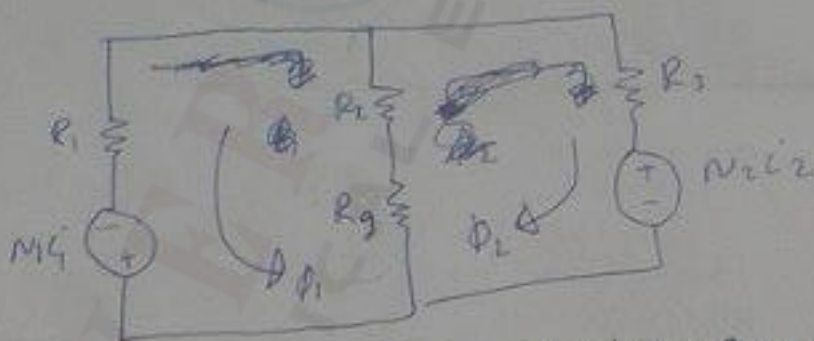

Non linear

$$R_{Lc} = \frac{L_c}{\mu_0 \mu_r} = \frac{2(25 + 9/2 + 15/2) + (25 + 9/2 + 9/2)}{\mu_0 \mu_r}$$


$$N_1 I_1 = (R_1 + R_2 + R_4) \phi_1 + (R_2 + R_3) \phi_2$$

$$N_2 I_2 = (R_2 + R_3 + R_4) \phi_2 + (R_2 + R_3) \phi_1$$

$$\phi_g = AB \rightarrow B_g = \frac{4 \times 10^{-3}}{1.05 \times 15 \times 5 \times 10^{-4}} = 0.507 \Rightarrow H = 8$$

$$H_{Lc} = N_1 I_1 + N_2 I_2$$

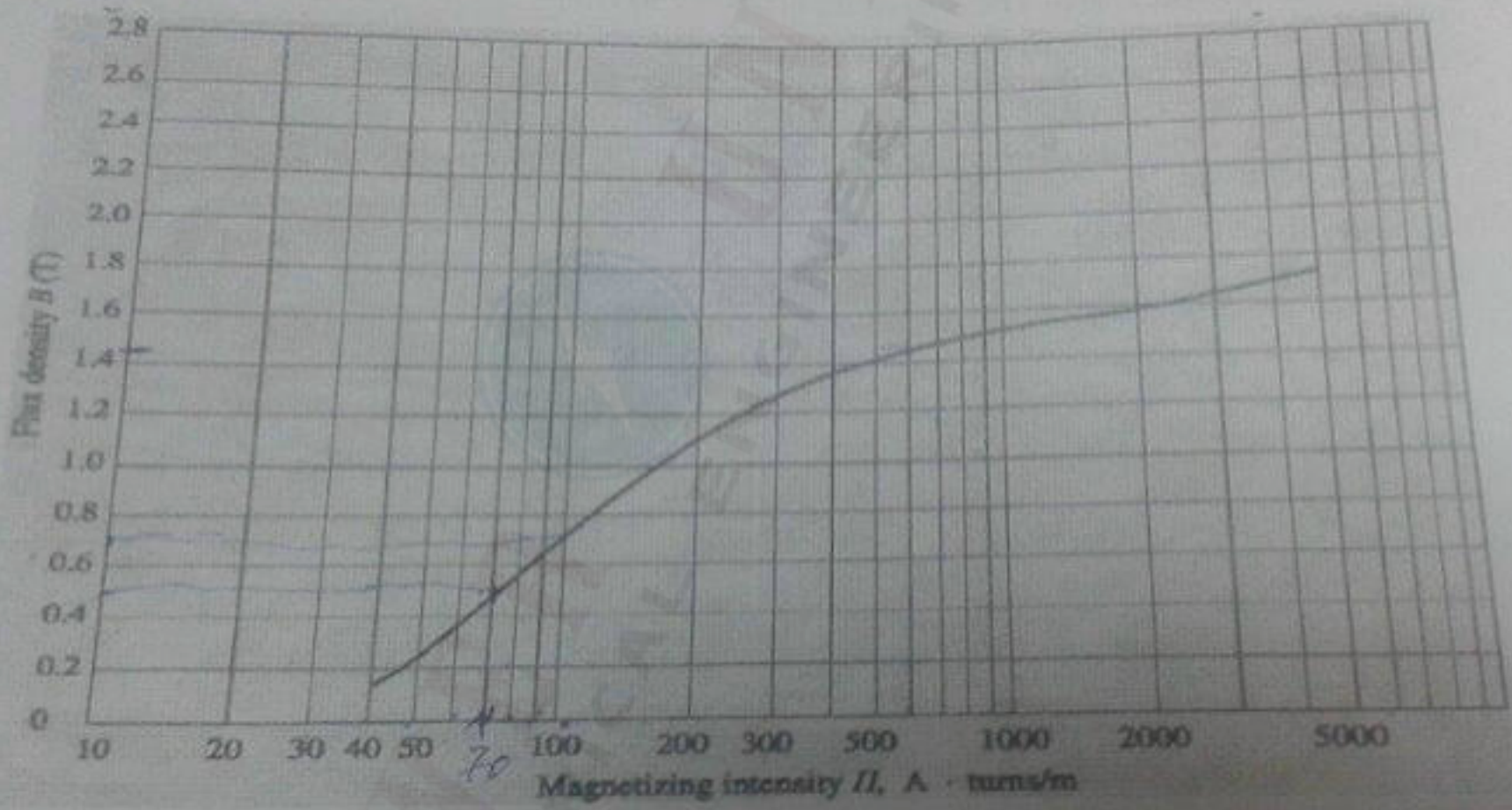
$$85 \times 34 \times 10^{-2} = 200 I_1 + 100 I_2$$




3. A power system consisting of a source, a step up transformer T1, a feeder, a step down transformer T2 and a load. The load is supplied at 250V. The load impedance is $10 + j5 \Omega$. T1 is 5kVA of 1:5 transformation ratio and an equivalent impedance referred to the low voltage side of $0.2 + j0.5 \Omega$. T2 is 5kVA of 5:1 transformation ratio and of a per unit equivalent impedance of $0.01 + j0.02$. The feeder is of $10 + j30 \Omega$.

(i) Sketch a diagram showing the system

7 marks

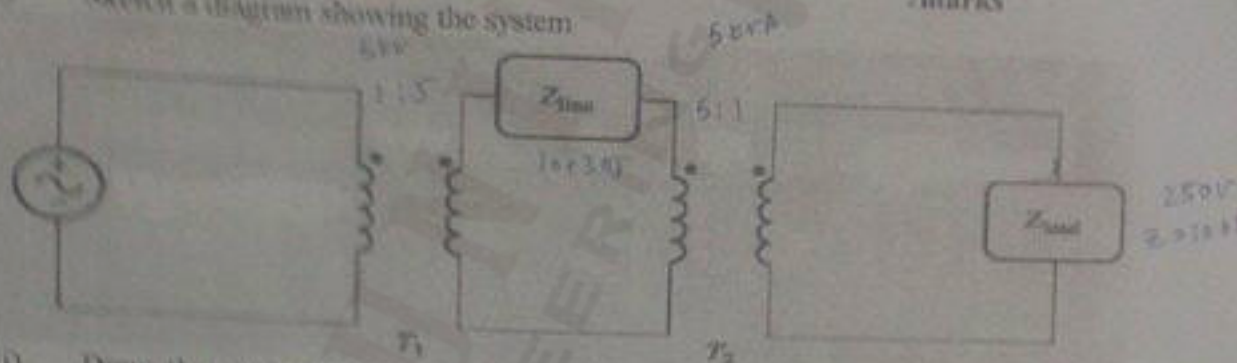

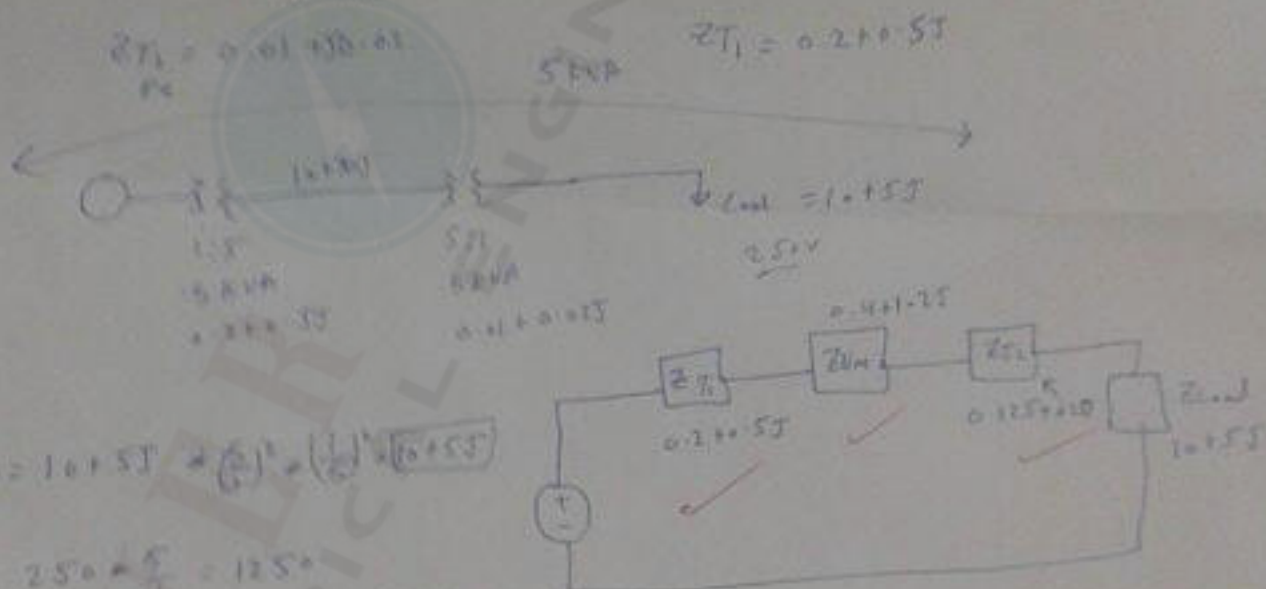(ii) Draw the equivalent circuit of the system referred to the low voltage side indicating values



$$Z_{load} = 10 + j5 \Omega \times \left(\frac{1}{5}\right)^2 = \frac{1}{25} \times (50 + j25) = 2 + j1 \Omega$$

$$V_{T2} = 250 \times \frac{1}{5} = 50 \text{ V}$$

$$Z_{T2} = 0.01 + j0.02 \times \left(\frac{50}{5000}\right) = 0.0001 + j0.0004 \Omega$$

$$Z_{T2} + \left(\frac{1}{5}\right)^2 = 0.125 + j0.25 \Omega$$

$$Z_{inc} = 10 + j30 + \frac{1}{25} = 10.04 + j30 \Omega$$

$$Z_{T1} = 0.2 + j0.5 \Omega$$

$$Z_{U_{load}} = 250 \times \frac{1}{5} = 50 \text{ V}$$

$$I_{load} = \frac{250}{10 + j5} = 22.3 \angle -26.56^\circ$$

3. A power system consisting of a source, a step up transformer T1, a feeder, a step down transformer T2 and a load. The load is supplied at 250V.

The load impedance is $10+j5 \Omega$


T1 is 5kVA of 1:5 transformation ratio and an equivalent impedance referred to the low voltage side of $0.2+j0.5 \Omega$

T2 is 5kVA of 5:1 transformation ratio and of a per unit equivalent impedance of $0.01+j0.02$

The feeder is of $10+j30 \Omega$.

7marks

(i) Sketch a diagram showing the system

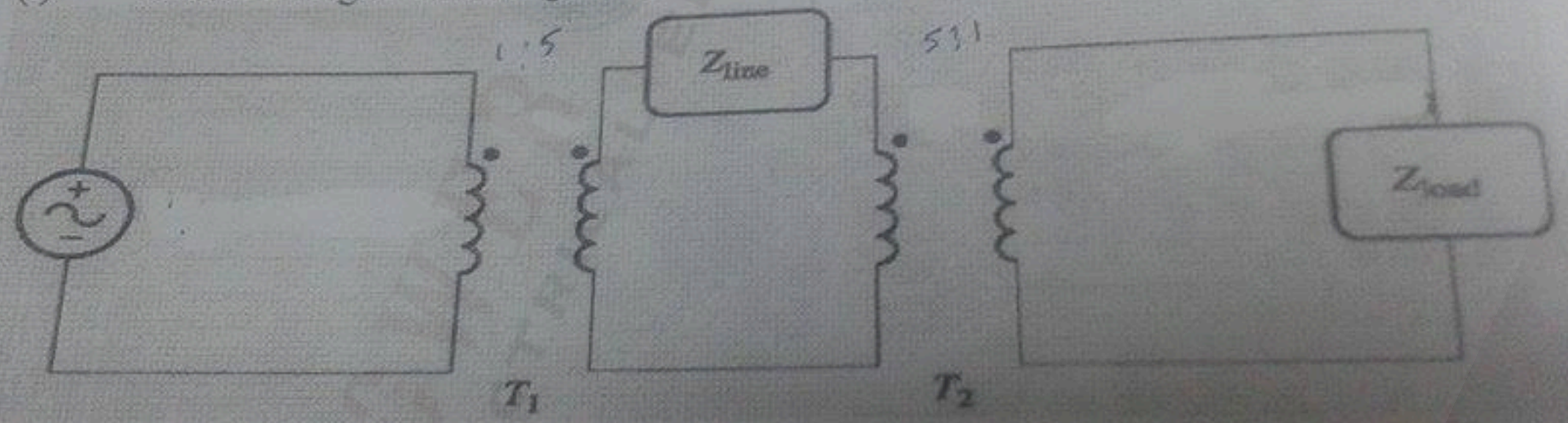

(ii) Draw the equivalent circuit of the system referred to the low voltage side indicating values

(iii) Find the supply voltage

$$V_s = 250 + 27.3 \times 26.56 (0.2 + 0.53 + 0.4 + 1.25 + 0.125 \times 25)$$

$$V_s = 285.67 \text{ V} \quad \checkmark$$

(iv) Find the power loss in the two transformers and in the feeder

$$P_{\text{loss}} = (27.3)^2 (0.2 + 0.4 + 0.125) \\ = 360.535 \quad \checkmark$$

(v) Find the efficiency of the system

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{2000}{5000 + 360.535} = \frac{22.3 \times 250 \cos(26.56)}{5000 + 360.535}$$

$$= 93.25\% \quad \checkmark$$

7