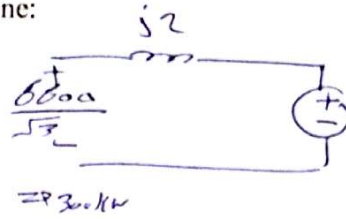


Question # 2-a (13 points)

A 6600-V, 50-Hz, 4-pole, 3-phase, Y-connected synchronous motor takes 300 kW at 0.6 PF lagging. The motor has a synchronous reactance X_s of 2 Ω /phase, negligible armature resistance R_a and rotational power loss P_{rot} (friction, windage and core losses) of 30 kW. Determine:

- The motor synchronous speed n_s ,
- The armature current I_a ,
- The induced voltage E_a and torque angle δ ,
- The reactive power absorbed/supplied by the motor Q_m ,
- The developed power P_d , and developed torque T_d ,
- The output horse power P_{out} , and the motor efficiency $\% \eta$,
- The maximum torque the motor can develop T_{dmax} ,
- The motor's armature current I_a , reactive power Q_m and power factor PF when the motor develops its maximum torque.



$n_s = 1500$ rpm	$I_a = 43.72 \angle -53.1^\circ$ A	$E_a \angle \delta = 3740.9 \angle -0.8^\circ$ V
$Q_m = 399.48$ kVAR	$P_d = 298.540$ kW	$T_d = 1900$ N.m
$P_{out} = 268.54$ kW	$\% \eta = 89.95$ %	$T_{dmax} = 136122$ N.m
$I_a = 2670.9 \angle -45.5^\circ$	$Q_m = 21777.310$ kVAR	$PF = 0.700$ lead (lag)

Question # 2-b (5 points) 1 hp = 746 W

$I_{a2} = 1.2 I_{a1} \Rightarrow |E_{a2}| = 1.2 |E_{a1}|$

If the induced voltage E_a of the machine of Question # 2-a is increased by 20% and the power input to the motor remains the same, i.e. 300 kW, find:

- The new induced voltage E_a and power angle δ ,
- The new values of armature current I_a , reactive power Q_m and the power factor PF ,
- The new maximum developed torque T_{dmax} .

$P_1 = P_2 = \frac{3V_L E_{a1} \sin \delta_1}{X_s} = \frac{3V_L E_{a2} \sin \delta_2}{X_s}$

$E_a \angle \delta = 4489 \angle -0.668^\circ$	$Q_m = 3871.931$ kVAR	$PF = 0.087$ (lead/lag)
$I_a = 340 \angle +85^\circ$ A		
$T_{dmax} = 163344.4$ N.m		

$I_a = \frac{300 \text{ kW}}{\sqrt{3} V PF}$

$E_a X_s = \sqrt{V_L^2 - \bar{I}_a (j X_s)}$
 $= 3740.9 \angle -0.8^\circ$

$Q_m = \sqrt{3} V_L I_a \sin \theta$

$P_d = \frac{3V_L E_a \sin \delta}{X_s}$

$P_{cu} = 3 I_a^2 R_a = 0$

$\eta = \frac{P_{out}}{P_{in}}$

$T_{dmax} = \frac{3V_L E_a}{\omega_s X_s} \sin 90^\circ$

$\bar{I}_a = \frac{6600 \angle 0 - 3740.9 \angle -90}{j 2}$



Question # 3 (7 points) ABET outcome 'h' Assessment

In an industrial plant, a 3-phase Y-connected load takes a total power of 300 kW at power factor of 0.60 lagging from a 380-V, 3-phase source. A synchronous motor supplying 100 hp and operating at 0.8 power factor leading and having an efficiency of 90% is added to the plant.

Determine

- The reactive and apparent powers of taken by the load Q_L and S_L
- The real, reactive, and apparent powers of taken by the motor P_m , Q_m and S_m
- The overall real, reactive, and apparent powers supplied by the system P_s , Q_s and S_s
- The magnitudes of load current, motor current, and system current I_L , I_m , and I_s
- The over all system power factor PF_s .
- Is the motor under- or over-excited.

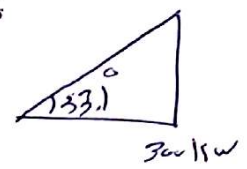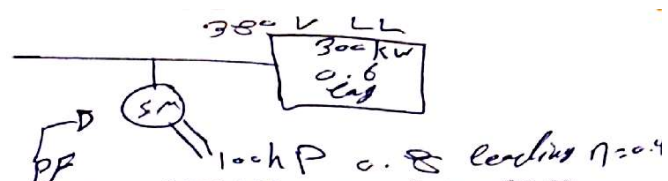Draw the power triangles to illustrate your solution.



$Q_L = 399.5$ kVAR	$S_L = 499.6$ kVA	
$P_m = 82.85$ kW	$Q_m = 62.14$ kVAR	$S_m = 103.56$ kVA
$P_s = 382.85$ kW	$Q_s = 461.64$ kVAR	$S_s = 594.73$ kVA
$I_L = 2759.53$ A	$I_m = 1570.3$ A	$I_s = 775.22$ A
$PF_{overall} = 0.754$ lead (lag)		

$100 \text{ hp} = P_{out} = 74.57 \text{ kW}$, $\eta = 0.9 = \frac{P_{out}}{P_{in}}$

$P_{in} = 82.85 \text{ kW}$

$I_L = \frac{P_{3\phi}}{\sqrt{3} V_L PF}$

$Q_L = P \tan \theta$


$S_L = \sqrt{P^2 + Q^2}$

$P_s = P_L + P_m$

$Q_s = Q_L + Q_m$

$S_s = S_L + S_m$

$I = \frac{S_{3\phi}}{\sqrt{3} V_{LL}}$

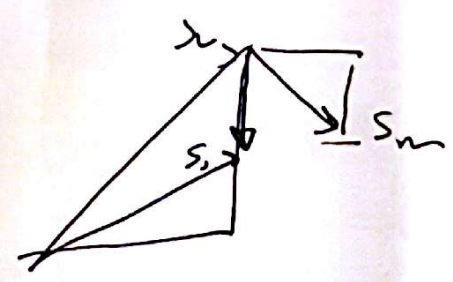



Question #4 (10 marks)

SHOW YOUR CALCULATIONS

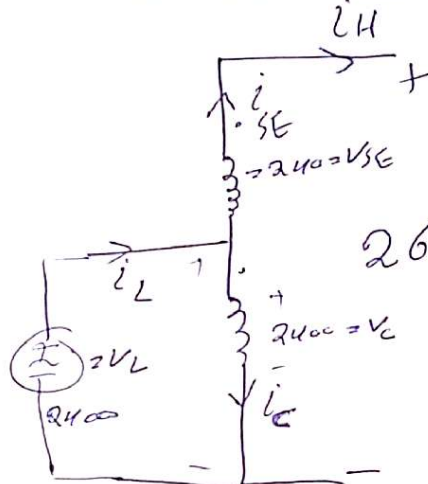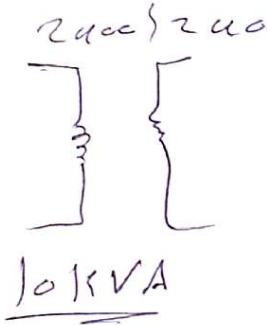8.5

A 10-kVA, 60-Hz, 2400—240-V distribution transformer is reconnected for use as a step-up autotransformer with a 2640-V output and a 2400-V input. Draw the connection diagram and determine:

- the rated primary current I_L and secondary current I_H when connected as an autotransformer.
- the advantage factor, A_f .
- the apparent-power rating S_{10} when connected as an autotransformer.
- power transferred by induction S_{ind} and conduction S_{cond} .



$I_L =$	45.87 A
$I_H =$	41.7 A
$A_f =$	11
$S_{10} =$	110080 kVA
$S_{ind} =$	100000 kVA
$S_{cond} =$	100080 kVA

$I_H = I_{SE}$

$I_L = I_{SE} + I_C$

$V_L = V_C$

$V_H = V_C + V_{SE}$

$110080 = S_{10}$
 110080

~~$V_L I_L = S_w \Rightarrow I_L = \frac{S_w}{V_C} = 41.7 A$~~

~~$I_H = I_{SE} = \frac{S_w}{V_{SE}} = 41.67 A$~~

~~$A_f = \frac{S_{10}}{S_w}, S_{10} =$~~

$I_{SE} = \frac{10k}{240} = 41.7 A = I_H$
 $\Rightarrow I_L = 45.87 A$


$I_C = 4.17 A$

$S_{10} = 110080 \Rightarrow A_f = \frac{S_{10}}{S_w} = 11$

$S_{in} = S_w$

$S_{con} = S_{10} - S_w$

$20.913 \rightarrow j0.108$

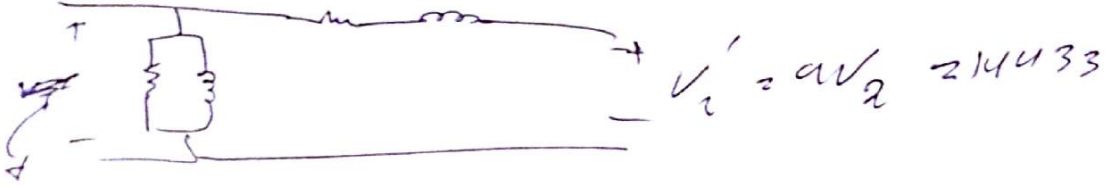

14433

