

# Power Unit

Student Name: محمد عبد الجبار Student ID#: 0142417 Serial #: 38

**Question # 1 (3 marks)**

An induction motor develops 15kW to a load at a speed of 2950 rpm. Find

1.1	the frequency of the stator current and number of poles	$f = 50$ Hz $P = 2$ poles
1.2	the motor's slip $s$ .	$s = 1.667\%$
1.3	the developed torque in the motor in N.m under these conditions.	$T_d = 48.55$ Nm
1.4	the operating speed of the motor if its torque is doubled.	$n_m =$ rpm
1.5	the power that will be supplied by the motor when the torque is doubled.	$P_d =$ kW

$$n_s = \frac{120(50)}{2} = 3000 \approx 2950$$

$$s = \frac{n_s - n_m}{n_s}$$

$$T_d = \frac{P_d}{\omega_m} = \frac{15 \text{ kW}}{308.9} \quad , \quad \omega_m = \frac{2\pi n_m}{60} = 308.9 \text{ rad/s}$$

$$= 48.5$$

$$T_{d2} = 97 \text{ N.m}$$

$$s = \frac{n_s - n_m}{n_s}$$

$$n_m = (1-s)n_s$$


**Question # 2 (4 marks)** →  $n_s = 1800 \text{ rpm}$

$I_L$  (4)

A 480-V, 4 pole, 60 Hz, 50-hp, three phase induction motor is drawing 60A at 0.85 PF lagging. The stator copper losses are 2 kW, and the rotor copper losses are 700 W. The friction and windage losses are 600 W and the core losses are 1800 W. Draw the IM power flow diagram and find the following quantities:

2.1	The input power $P_{in}$	$P_{in} = 42.4$ kW
2.2	The air-gap power $P_g$	$P_g = 38.6$ kW
2.3	The power developed $P_d$	$P_d = 37.9$ kW
2.4	The output horse power $P_{out}$	$P_{out} = 350$ hp
2.5	The efficiency of the motor $\eta$	$\% \eta = 87.97\%$
2.6	The motor speed $n_m$	$n_m = 1767.6$ rpm
2.7	The torque developed $T_d$	$T_d = 204.77$ Nm
2.8	The output torque $T_{out}$	$T_{out} = 201.5$ Nm

$P_d$        $P_{dev}$

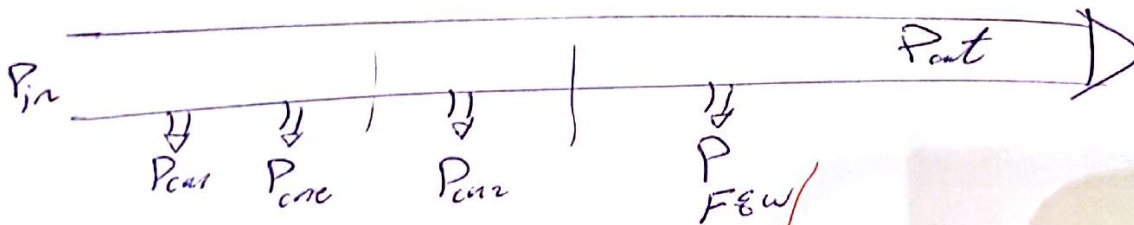

$$P_{in} = \sqrt{3} V_L I_L \cos \theta = 42400 \text{ W}$$

$$P_g = P_{in} - P_{cst} - P_{cu2} = 42400 - 2000 - 1800 = 38600$$

$$P_{dev} = P_g - P_{cu2} = 38600 - 700 = 37900$$

$$P_{out} = P_{dev} - P_{F\&W} = 37900 - 600 = 37300$$

$$P_{out} = 37.9 \text{ kW} - 600 \text{ W} = 37300 \text{ W}$$

$$P_{out} = \frac{37300}{746} = 50 \text{ hp}, \quad \eta = \frac{P_{out}}{P_{in}}$$

$$n_m = (1-s)n_s \Rightarrow P_d = (1-s)P_g \Rightarrow s = 0.018 = 1.8\%$$

$$\omega_m = (1-s)\omega_s = 185.107$$

$$T_d = \frac{P_d}{\omega_s} = \frac{37900}{188.5}$$

$$T_{out} = \frac{P_{out}}{\omega_m} = \frac{37300}{185.107}$$

**Question # 3 (10 marks)**

$n_s = 1800$

6

A 460-V, 25-hp, 60 Hz, four-pole, Y-connected wound-rotor induction motor has the following impedances in ohms per phase referred to the stator circuit:


$R_1 = 0.641 \Omega$        $R_2 = 0.332 \Omega$        $X_1 = 1.106 \Omega$        $X_2 = 0.464 \Omega$        $X_M = 26.3 \Omega$

The core loss is lumped in with the rotational losses. The total rotational losses are 1100 W and are assumed to be constant. For a rotor slip of 2.2 percent at the rated voltage and rated frequency, use the IEEE motor equivalent circuit to find the motor's

3.1	synchronous speed $n_s$ rotor speed $n_m$	$n_s = 1800$ rpm $n_m = 1760.4$ rpm
3.2	magnitude of stator current $ I_1 $ and PF <sub>1</sub> at the above slip	$ I_1  = 18.9$ A PF = 0.833
3.3	Thévenin's equivalent voltage $V_{Th}$ and Thévenin's equivalent impedance $Z_{Th}$	$V_{Th} = 254.82134$ V $Z_{Th} = 1.22 \angle 61.2^\circ \Omega$
3.4	magnitude of rotor current $ I_2 $ and PF <sub>2</sub> at the above slip	$ I_2  = 16.17$ A PF = 0.997
3.5	converted power $P_{conv}$ and airgap power $P_g$	$P_{cov} = 11.576$ kW $P_g = 11.837$ kW
3.6	developed torque $T_d$ load torque $T_L$	$T_d = 62.79$ Nm $T_L = 56.83$ Nm
3.7	the starting torque of this motor $T_{st}$ magnitude of rotor starting current $ I_{2st} $	$T_{st} = 237$ Nm $ I_{2st}  =$
3.8	the maximum torque of this motor $T_{max}$ the speed at maximum torque $n_{Tmax}$	$T_{max} = 234.9$ Nm $n_{Tmax} = 1440$ rpm
3.9	the new maximum torque of the motor $T_{maxnew}$ and the speed at which the maximum torque now occur, if the rotor resistance is doubled, $n_{Tmax}$	$T_{maxnew} = 234.9$ Nm $n_{Tmax} = 1080$ rpm
3.10	the new starting torque of the motor $T_{stnew}$ if the rotor resistance is doubled, $T_{stnew}$	$T_{stnew} = 1910$ Nm
3.11	Plot the T-Speed c/c for both cases.	

7

104  
114.14

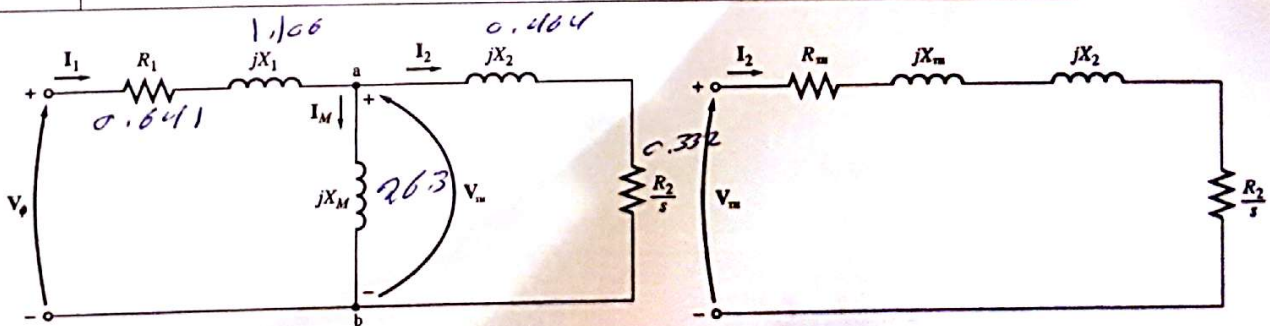

$I_L = 18.9 \angle -33.6^\circ$  A  
 $V_{Th} = V_{af} = 265 \frac{j26.3}{j26.3 + j1.106 + 0.641} = 254.82134$   
 $Z_{Th} = 1.22 \angle 61.2^\circ$

$$|I_2| = \frac{V_{Th}}{Z_{Th} + \frac{R_2'}{s} + jX_2}$$

$$P_{conv} = 3(I_2')^2 R_2' \left(\frac{1-s}{s}\right)$$

$$P_2 = 3(I_2')^2 \frac{R_2'}{s}$$

$$T_d = \frac{P_2}{\omega_s} = \frac{11837}{188.5} = 62.79$$

$$T_L = \frac{P_{out}}{\omega_m}$$

$$0.58 + j1.07$$



$$T_d)_{st} = \frac{3 V_{Th}^2}{\omega_s} \frac{R_2'}{(R_{Th} + R_2')^2 + (X_{Th} + X_2')^2}$$

$$T_{max} = \frac{3V^2}{2\omega_s} \frac{1}{\left[ R_{Th} + \sqrt{R_{Th}^2 + (X_{Th} + X_2')^2} \right]}$$

$$s_{max} = \frac{R_2'}{\sqrt{R_{Th}^2 + (X_{Th} + X_2')^2}} = \underline{\underline{0.2}}$$

$n_n =$

$$s_{max} = 0.4$$

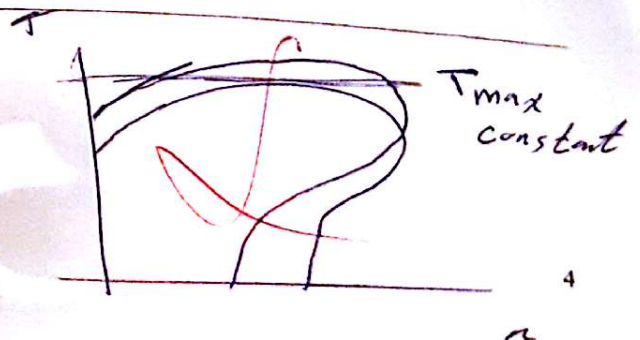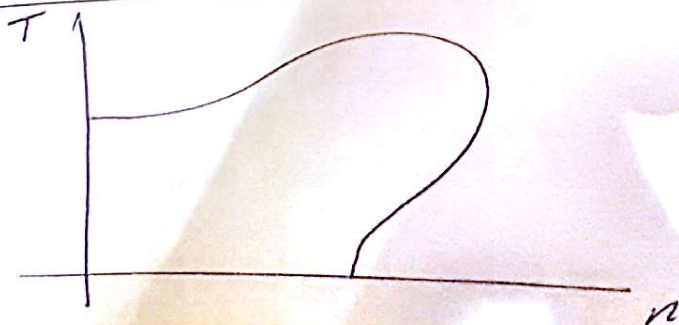


**Question # 4 (8 marks)**

The following test data were taken on a 7.5-hp, four-pole, 208-V, 60-Hz, design A, Y-connected IM having a rated current of 28 A. Find the parameters ( $R_1$ ,  $X_1$ ,  $R_2$ ,  $X_2$ , and  $X_M$ ) of the IEEE model of the IM and the rotational power loss  $P_{rot}$ .

DC Test		No-load Test ( $f = 60$ Hz)			Locked-rotor Test ( $f = 15$ Hz)		
$V_{DC}$	$I_{DC}$	$V_{nl}$	$I_{nl}$	$P_{nl}$	$V_{Bl}$	$I_{Bl}$	$P_{Bl}$
13.6 V	28.0 A	208 V	8.17 A	420 W	25 V	27.9 A	920 W

Division of blocked-rotor reactance for NEMA-design motors

	A, D	B	C	Wound Rotor
$X_1$	$0.5X_{BR}$	$0.4X_{BR}$	$0.3X_{BR}$	$0.5X_{BR}$
$X_2$	$0.5X_{BR}$	$0.6X_{BR}$	$0.7X_{BR}$	$0.5X_{BR}$

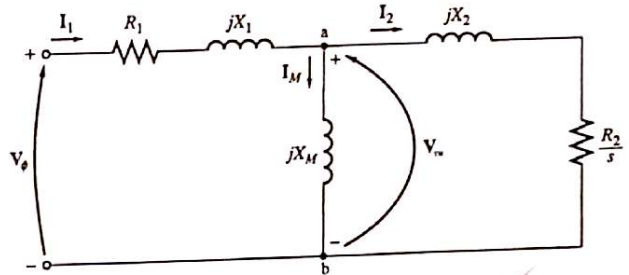

$R_1 =$	0.24	$\Omega$
$R_2 =$	0.15	$\Omega$
$X_1 =$	0.68	$\Omega$
$X_2 =$	0.68	$\Omega$
$X_M =$	<del>13.86</del>	$\Omega$
$P_{rot} =$	371.9	W

① DC  
 $R_1 = \frac{1}{2} \frac{13.6}{28} = 0.24$

② Blocked ( $s=1$ )

$$Z_B = \frac{25}{\sqrt{3}} = 0.52 \Omega$$

$$R_{eq} = \frac{920}{3} = 0.39 \Omega$$

$$X_{BL} = \sqrt{Z^2 - R^2} = 0.34 \Omega$$

$$X_B |_{60Hz} = 4(0.34) = 1.36 \Omega = (X_1 + X_2')$$

③ No-load ( $s=0$ )

$$P_{nl} = 3 I_{nl}^2 R_1 + P_{rot}$$

$$420 = 2943.3$$

$$2943.25 = 3 I_{nl}^2 (X_1 + X_M)$$

$$X_1 + X_M = 14.54 \rightarrow X_M =$$

Question # 5 (5 marks)

$n_c = 1800$

$s = 5\%$

A 460-V 100-hp four-pole  $\Delta$ -connected 60-Hz three-phase induction motor has a full-load slip of 5%, and efficiency of 92%, and a power factor of 0.87 lagging. At start-up, the motor develops 1.9 times the full-load torque but draws 7.5 times the rated current at the rated voltage. This motor is to be started with a reduced voltage starter. Find

5.1	The full-load torque $T_{FL}$ .	$T_{FL} = 416.43 \text{ Nm}$
5.2	The full-load current $I_{FL}$ .	$I_{FL} = 67.5 \text{ A}$
5.3	the starting voltage $V_{st}$ that would reduce the starting torque until it equals the rated torque of the motor	$V_{st} = 333.7 \text{ V}$ <del>192.6</del> $\checkmark$ value
5.4	the motor starting current $I_{st}$ drawn from the supply at the reduced voltage.	$I_{st} = 161.18 \text{ A}$
5.5	the new starting $T_{st}$ torque if the motor is started at rated voltage using a 50 Hz source	$T_{st} = \text{? Nm}$

$116.9 \angle -29.5$

$T_{FL} \approx \frac{T_{st}}{1.9}$ ,  $T_{st} = 1.9 T_{FL}$

$\eta = \frac{P_{out}}{P_{in}} = 0.92 = \frac{74.57}{?}$

$P_{in} = 81.05 \text{ kW}$

$I_{LL} = \frac{116.9 \angle -29.5 \text{ A}}{67.5}$

$T_{d/PL} = \frac{P_g}{\omega_m}$

$= 416.4$

$\frac{T_{FL}}{T_{st}} = \left(\frac{V_2}{V_1}\right)^2$

$\frac{V_2}{V_1} = \frac{1.9}{7.5} \Rightarrow V_2 = \frac{1.9}{7.5} \times 460 = 116.9 \text{ V}$

$\frac{1}{2}$   $\frac{1}{2}$