

Student Name: Amal Al-Shehri Student ID#: 0144235 Serial #: 17.

* Q # 1 (5)	Q # 2 (6)	Q # 3 (7)	Q # 4 (4)	Q # 5 (3)	GRADE
3.5	4	7	1.5	3	21 <u>19/25</u>

Question # 1 (5 marks) ABET Outcome h Assessment SHOW YOUR CALCULATIONS

A small industrial plant has a total electrical load of 500 kVA at 0.60 PF lagging. A 100 hp water pump is to be installed. A synchronous motor operating at 0.60 PF leading is selected to drive the pump. Neglect all losses in the synchronous motor. Draw the power triangles for the load, motor and source, and then calculate

		1 hp = 746 W
a.	the total real and reactive powers supplied by the source before installing the pump.	$P_s = 300$ kW (1) $Q_s = 400$ kVAR
b.	the real and reactive powers taken by the the pump.	$P_m = 7.46$ kW 74.6 $Q_m = 9.95$ kVAR 99.5
c.	the total real and reactive powers supplied by the source after installing the pump.	$P_s = 307.46$ kW (2) $Q_s = 390.05$ kVAR (2)
d.	the overall (combined) system power factor, $PF_{overall}$.	$PF_{overall} = 0.6184$ lead lag

$$P_s = 1.51 \cdot 10^3 \text{ kW} = 300 \text{ kW}$$

$$Q_s = 1.51 \cdot \sin(\cos^{-1} 0.6) = 400 \text{ kVAR}$$

$$P_m = P_{in} = P_{out} = 7.46 \text{ kW} \quad 74.6 \text{ kW}$$

$$Q_m = \frac{P}{PF} \cdot \sin(\cos^{-1} 0.6) = 9.95 \text{ kVAR} \quad 99.5 \text{ kVAR}$$

$|S| = 500 \text{ kVA}$
 Load 0.6 lag.

(SM) 0.6 lead.

$$P_{in} = P_{out} = 100 \times 746 = 7.46 \text{ kW}$$


$$P_s = 300 \text{ K} + 7.46 \text{ K} = 307.46 \text{ kW}$$

$$Q_s = 400 \text{ K} - 9.95 \text{ K} = 390.05 \text{ kVAR}$$

$$S_s = 496.66 \angle 51.8^\circ \text{ kVA}$$

$$\Rightarrow Pf = \cos(51.8^\circ)$$

$$= 0.6184$$

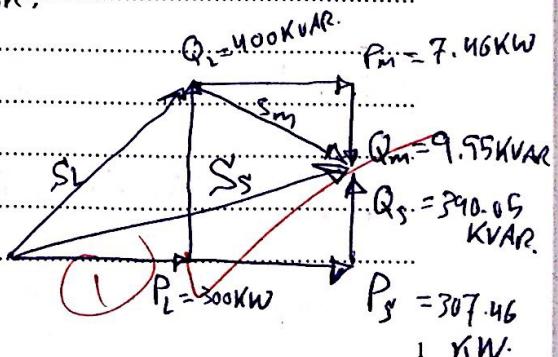

Question # 2 (6 marks)

SHOW YOUR CALCULATIONS

A 3-phase, 2400 V, 60 Hz, four pole, Y-connected synchronous motor has a per phase synchronous reactance X_s of 16 Ω and negligible armature resistance. The excitation is adjusted so that the induced voltage is 2400 V. The motor drives a load connected to its shaft, and the stator current is 80 A. Draw the phasor diagram and calculate

a.	the developed torque at the above load condition	$T_d = 1564.43$	Nm
b.	the motor's power factor	$PF = 0.8868$	lead lag
c.	the new motor's speed, if the load is doubled.	$N_s = 900$	rpm
d.	the maximum torque the machine can develop	$T_{dmax} = 1909.81$	Nm

$$I_a = \frac{V_t - E_a}{jX_s}$$

$$|I_a|^2 = \frac{|V_t|^2 + |E_a|^2 - 2|V_t||E_a|\cos\delta}{(X_s)^2}$$

$$(16)^2 \cdot (80)^2 = \frac{2400^2}{3} + \frac{2400^2}{3} - 2 \cdot \frac{(2400)^2}{3} \cos\delta$$

$$\cos\delta = 0.5733 \Rightarrow \boxed{\delta \approx 55^\circ}$$

$$P_d = \frac{3V_t E_a \sin\delta}{X_s} = \frac{(2400)^2}{16} \sin 55^\circ$$

$$P_d = 294394.7 \text{ W} \Rightarrow n_s = \frac{120}{4}(60) = 1800 \text{ rpm}$$

$$\tau_d = \frac{P_d}{\omega_s} = 1564.4 \text{ N.m.} \quad \text{or} \omega_s = \frac{2\pi}{60}(1800) = 188.5 \text{ rad/s.}$$

$$P_d = \sqrt{3} V_t I_a \text{ PF} \quad \theta_I = -27.5^\circ$$

$$P_d = 294394.7 = \sqrt{3} (2400)(80) \text{ PF} \Rightarrow \boxed{PF = 0.8868 \text{ lagging.}}$$

$\tau \propto \frac{1}{N_s} \Rightarrow$ reduced to half

$$P_{max} = \frac{3V_t E_a}{X_s} = \frac{(2400)^2}{16} = 36000 \text{ W}$$

$$\tau_{max} = \frac{36000}{188.5} = 1909.81 \text{ N.m}$$

Question # 3 (7 marks)

SHOW YOUR CALCULATIONS

Consider a three phase, 100 hp, 400 V, Y-connected, 4 pole, 60 Hz induction motor. The equivalent circuit parameters are:


$$R_1 = 0.06 \Omega, R'_1 = 0.08 \Omega, X_1 = 0.3 \Omega, X'_1 = 0.3 \Omega, X_m = 5 \Omega$$

The motor drives its load at a slip $S = 0.02$. Calculate

a.	the magnitude of the motor's armature current	$ I_a =$	70.65	A
b.	the motor's power factor	$PF =$	0.712	lead lag
c.	the magnitude of the rotor's current	$ I_2 =$	53.16	A
d.	the developed torque at the above load condition	$T_d =$	179.9	Nm
e.	the maximum developed torque	$T_{dmax} =$	640.13	Nm

using IEEE model:
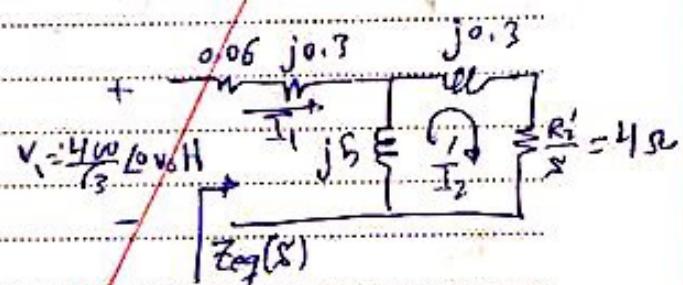
$$Z_{eq}(s) = (0.06 + j0.8) + (j5) // (4 + j0.3)$$



$$Z_{eq} = 2.33 + j2.29 \Omega$$

$$= 3.27 \angle 44.6^\circ \Omega$$

$$\frac{I_a}{V_1} = \frac{I_1}{Z_{eq}} \Rightarrow I_a = \frac{400 / \sqrt{3}}{3.27 \angle 44.6^\circ} = 70.6 \angle -44.6^\circ A$$

$$PF = \cos 44.6^\circ = 0.712$$

$$I_2' = I_1 \times \frac{j5}{j6 + 4 + j0.3} = 53.16 \angle -7.6^\circ A$$

$$P_d = 3 |I_2'|^2 \cdot \frac{(1-s) R'_2}{s} = 3 (53.16)^2 \cdot \frac{1-0.02}{0.02} \cdot 0.08 = 33.23 kW$$

$$T_d = \frac{P_d}{\omega_m} = \frac{33.233 \text{ W}}{2\pi (1764)} = 179.9 \text{ N.m}$$

$$n_m = (1-s) n_s = (1-0.02) \times \frac{120}{4} (60) = 1764$$

$$T_{dmax} = \frac{3 |V_1|^2}{2 \omega_s} \cdot \frac{1}{R_1 + \sqrt{R_1^2 + X_{eq}^2}} = \frac{3 (400)^2}{2 \omega_s \cdot 0.06 + \sqrt{0.06^2 + 0.6^2}} \approx 188.5$$

$$T_{dmax} = 640.13 \text{ N.m}$$

Question # 4 (4 marks)

SHOW YOUR CALCULATIONS

A three-phase, 400 V, 50 Hz, 6-pole wound-rotor induction motor drives a constant torque load at a speed of 950 rpm when the rotor terminals are short-circuited. It is required to reduce the speed of the motor to 850 rpm by inserting external resistances R'_{ext} in the rotor circuit. The rotor winding resistance $R'_2 = 0.2 \Omega$ per phase and the rotational losses are negligible. Draw the speed-torque characteristics before and after adding the external resistance, and determine approximately

a.	the value of the external resistance.	$R'_{ext} =$	4.8 Ω
b.	the motor's developed torque	$T_d =$	1145.92 Nm

$$n_m = 950 \text{ rpm} \quad n_{m2} = 850 \text{ rpm} \Rightarrow R'_{ext} = ?$$

$$\omega_s = 1000 \text{ rad/s}$$

$$S_1 = \frac{n_m - n_m}{n_m} = 0.05$$

$$R'_2 = 0.2 \Omega$$

$$S_2 = \frac{n_s - n_{m2}}{n_s} = 0.15$$

$$P_g = 3$$

$$P_{out} = P_d$$

$$P_d = (1 - S) P_g$$

$$P_{out2} = S P_g$$

$$T = \frac{400^2}{2\pi \cdot 1000} \cdot \frac{0.05}{0.2} = 381.97 \text{ N.m}$$

$$T_d = \frac{3 |V|_s^2}{\omega_s} \cdot \frac{R'_2 + R_{ext}}{(R'_2 + R_{ext})^2 + X_q^2} = ?$$

$$T_d = \frac{3 |V|_s^2}{\omega_s} \cdot \frac{0.15}{(0.15 + 0.2)^2 + 0.05^2} = 1145.92 \text{ N.m}$$

$$P_d = \omega_m T_d = 2\pi \frac{850}{60} (1145.92) = 10.2 \text{ kW} = P_{out}$$

$$P_g = \frac{P_d}{1 - S} =$$

$$R'_2 + R_{ext} = \frac{(1145.92) \cdot \omega_s}{3 |V|_s^2 S}$$


$$R'_2 + R_{ext} = \frac{1145.92 \cdot 1000}{3 \cdot 400^2 \cdot 0.15} = 4.8 \Omega$$

Question # 5 (3 marks)**SHOW YOUR CALCULATIONS**

A pair of synchronous machines (SM) on the same shaft, may be used to generate power at 60 Hz from a given power source at 50 Hz as shown below. SM1 has P_1 number of poles while SM2 has P_2 number of poles. Determine for this type of operation,

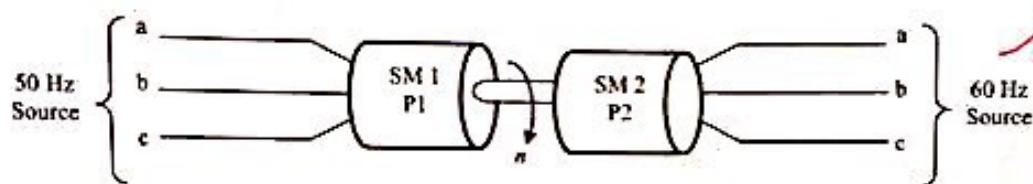- a. the mode operation of SM1 and SM2 (Generator/Motor).
- b. the minimum number of poles P_1 and P_2 .
- c. the shaft-speed in rpm, n .

SM1: Motor.
SM2: Generator.
$P_1 = 10$ poles.
$P_2 = 12$ poles.
$n = 600$ rpm.



SM1 \rightarrow will have an electrical input
so it will give an output mechanical
so it is Motor.

SM2 \Rightarrow will have an mechanical input
& give an output electrical
so it is Generator.

$$n_s = \frac{120 f}{P}$$

	n_s (RPM)	
P	50	60
2	3000	3600
4	1500	1800
6	1000	1200
8	750	900
10	600	720
12	500	600

SM1: @ $50\text{Hz} \rightarrow 10$ poles.

SM2: @ $60\text{Hz} \rightarrow 12$ poles.

$$n_s = 600 \text{ rpm}$$

Q1

$$P_s = 181 \text{ Pf} = 300 \text{ kW}$$

$$Q_s = 181 \sin(\cos^{-1} 0.6) = 400 \text{ kVAR}$$


$$P_m = P_{in} = P_{out} = 74.6 \text{ kW}$$

$$Q_m = \frac{P}{\text{Pf}} \sin(\cos^{-1} 0.6) = -99.5 \text{ kVAR}$$

$$P_s = 300 \text{ k} + 74.6 \text{ k} = 374.6 \text{ kW}$$

$$Q_s = 400 \text{ k} - 99.5 \text{ k} = 300.5 \text{ kVAR}$$
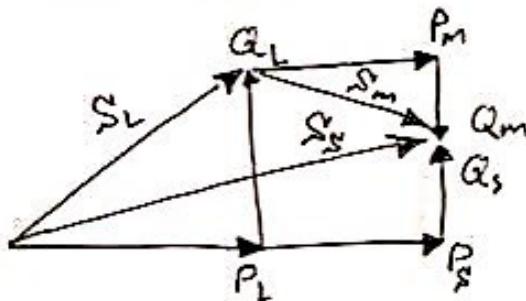
$$S_s = 480 \cdot 2 \angle 38.7^\circ \Rightarrow \text{Pf} = \cos(38.7) = 0.78 \text{ lagging.}$$



*

*

*

*

Q4

$$n_{m_1} = 950 \text{ rpm.} \quad \Rightarrow \quad S_1 = 0.05$$

$$n_s = 1000 \text{ rpm.} \quad S_2 = 0.15$$

$$n_{m_2} = 850 \text{ rpm.}$$

$$\tau_d = \frac{3|V|^2}{\omega_s} \cdot \frac{S}{R'_2} = \frac{400^2}{2\pi \cdot \frac{1000}{60}} * \frac{0.05}{0.2} = 381.97 \text{ N.m.}$$

$$\tau_{d_1} = \tau_{d_2} \Rightarrow \frac{3|V_2|^2}{\omega_s} \cdot \frac{S_1}{R'_2 + R_{ext}} = \frac{3|V_1|^2}{\omega_s} \cdot \frac{S_1}{R'_2}$$

$$\frac{0.15}{0.2 + R_{ext}} = \frac{0.05}{0.2} \Rightarrow R_{ext} = 0.4 \Omega$$