



Machines2


Summer017



Dr. **E**yad **A**bu^alⁱlat



By: **S**ara **A**udeh

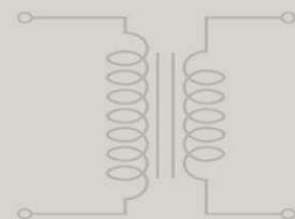

Powerunit-ju.com

Machines :-

No. Monday 24-7


* Synchronous Generators :-


$$e = -N \frac{d\phi}{dt}$$

$$E_{rms} = 4.44 f N \phi_m$$

$$E_{rms} \propto \phi_m \rightarrow \phi \propto I_f \quad \text{so } E_{rms} \propto I_f$$

$$n = \text{constant}$$

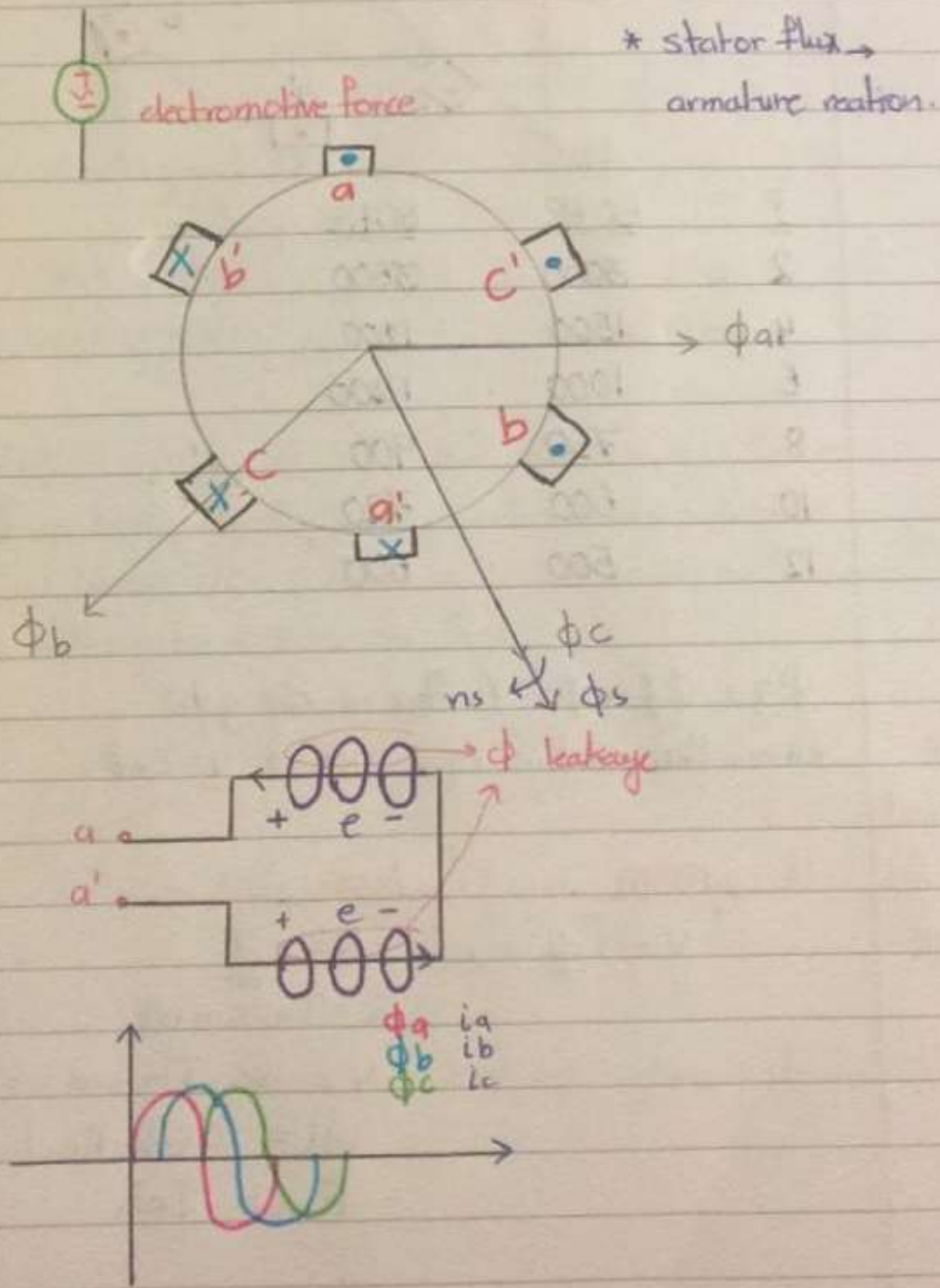


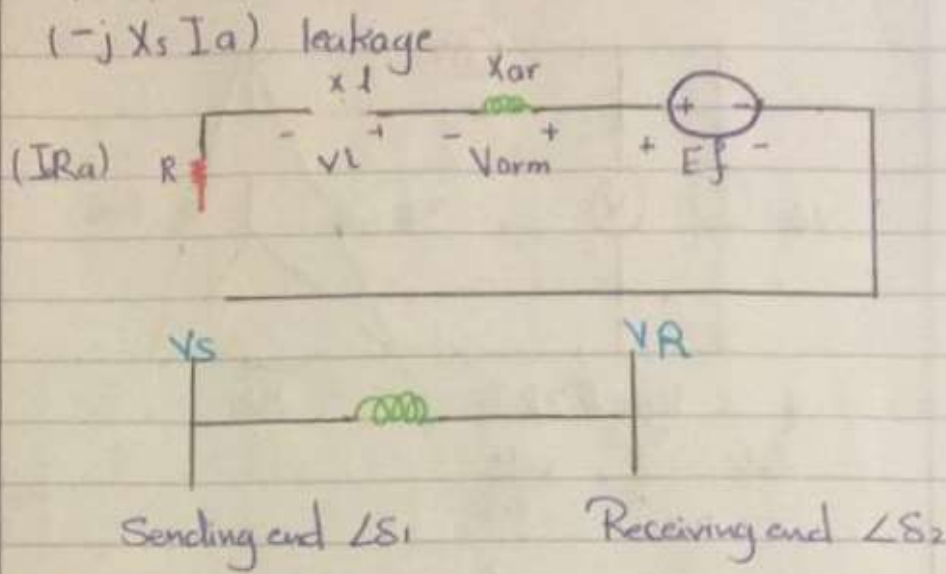

$$|V_s| > |V_r| \rightarrow Q \quad \delta_1 > \delta_2 \rightarrow P$$

$$|V_s| < |V_r| \leftarrow Q \quad \delta_1 < \delta_2 \leftarrow P$$

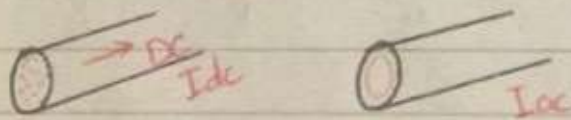$\angle E_f > \nu$ $P \rightarrow$ the generator gives Real power
 * If we have short circuit \rightarrow the current become $= \frac{E_f}{Z}$
 * Coil under DC \rightarrow Resistance = 0 $\omega = 0$ no Reactance Impedance
 $L \rightarrow$ voltage to oppose the flux




$$R \nearrow = \frac{\rho l}{A} \text{ (machine supply ac current)}$$

\rightarrow ρ is resistivity
 \rightarrow A is cross-sectional area

$$R_{ac} = (1.1 - 1.5) R_{dc}$$

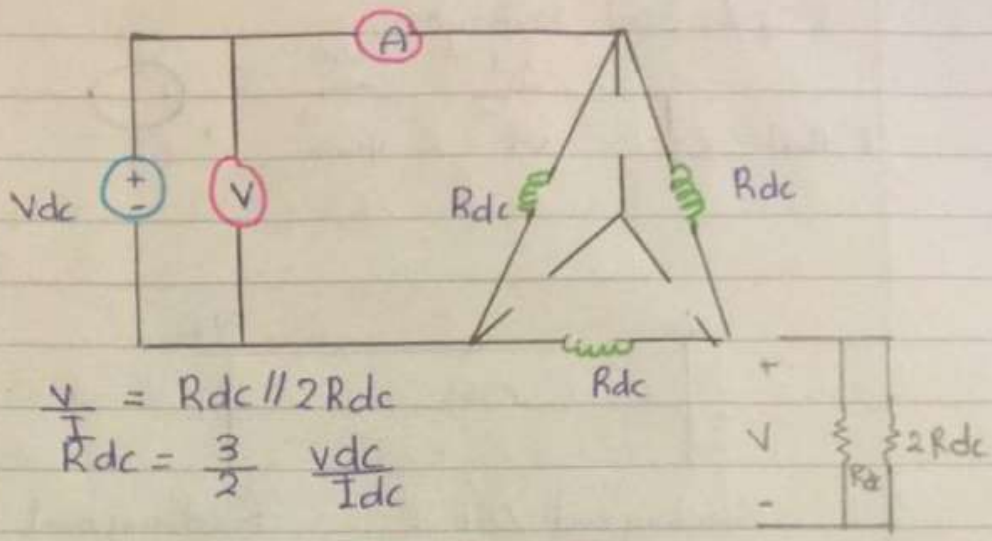* for high frequency we don't use cylindrical we use sheets



$$\frac{V}{I} = R_{dc} // 2R_{dc}$$



$$\frac{V}{R_{dc}} = \frac{3}{2} \frac{V_{dc}}{I_{dc}}$$

Tuesday 25-7

$$E_{rms} = 4.44 f N \phi$$

$$E_{rms} \propto \phi$$


$$E_{rms} \propto I_f$$

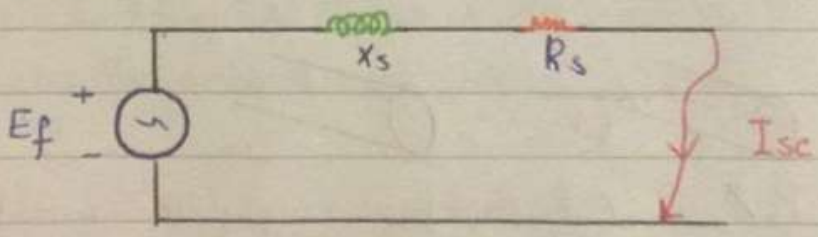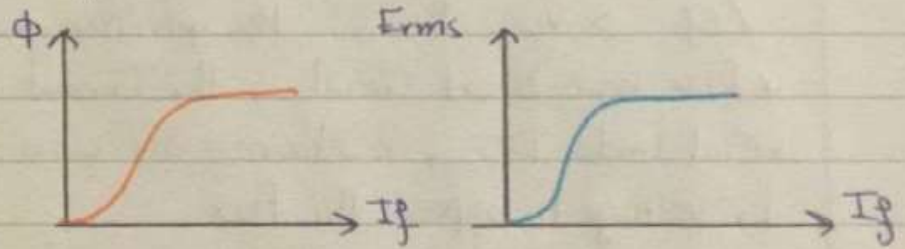


$$|I_{sc}| = \frac{|E_f|}{|Z_s|} = \frac{|E_{sph}|}{\sqrt{R_s^2 + X_s^2}}$$

$$I_{sc} \propto |E_{ph}|$$

$$|E_{ph}| \propto I_f$$

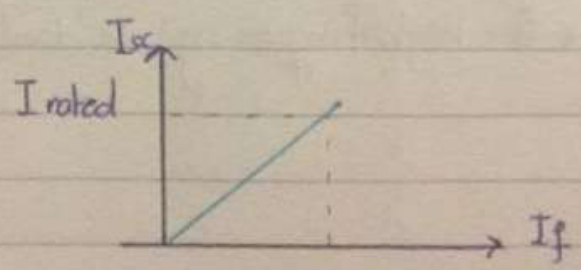

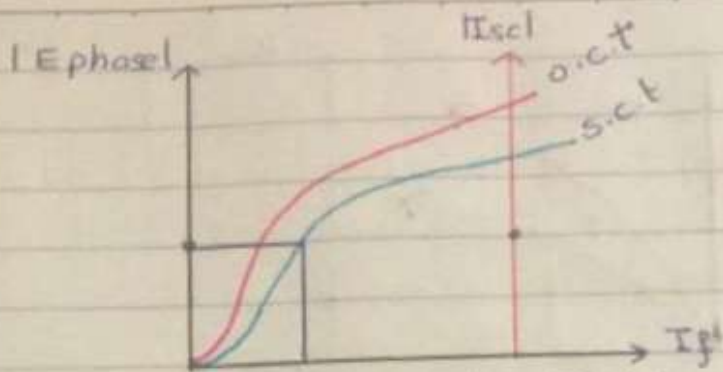


$X_s = \sqrt{Z_s^2 - R_s^2} \rightarrow X_s = \frac{|E_{\text{phase}}|}{I_{sc}}$, $R_s = 0.0$
 $R_s \ll X_s$

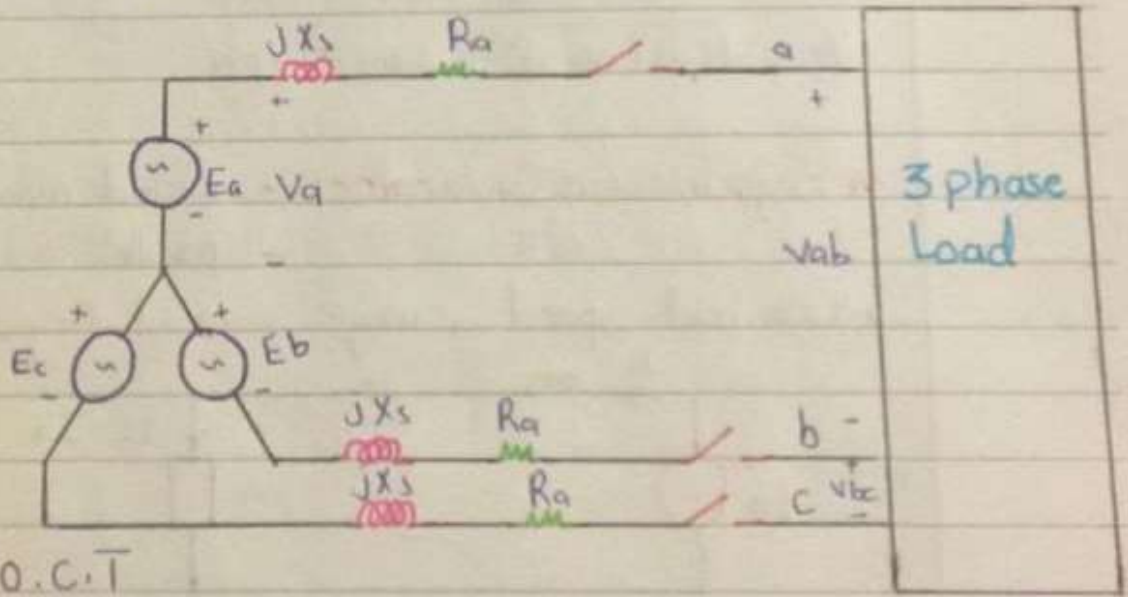***Example ① :-**

$I_{\text{rated}} = I_{FL}$

$I_L = \frac{S_{FL}}{\sqrt{3} V_L} \rightarrow \frac{S_{FL}}{3 V_{ph}} = I_{ph}$



O.C.T


$V_{L-L} = 540 \text{ V}, I_f = 5 \text{ A}$

s.c.T

$I_{sc} = 300 \text{ A}, I_f = 5 \text{ A}$

DC.T

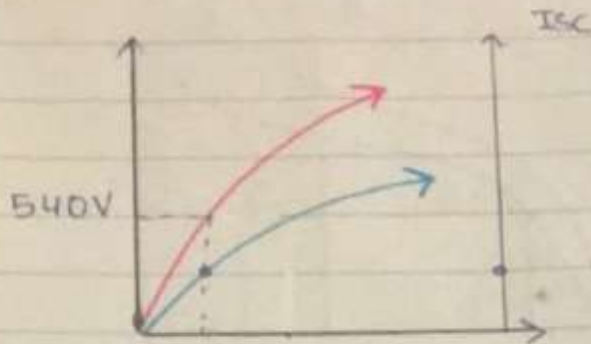$V_{dc} = 10 \text{ V} \quad I_{dc} = 25 \text{ A}$



$$Z_s = \frac{540}{\sqrt{3}}$$

In γ -Connection

$$V_{ph} = \frac{V_{LL}}{\sqrt{3}} \quad I_{ph} = I_L$$

In Δ -Connection


$$V_{ph} = V_{LL} \quad I_{ph} = I_L / \sqrt{3}$$

$$R_{dc} = \frac{1}{2} \frac{V_{dc}}{I_{dc}} = \frac{1}{2} \times \frac{10}{25} = 0.2 \Omega$$


$$X_s = \sqrt{(1.04)^2 - (0.2)^2} \approx 1.04 \Omega / ph$$


- * Synchronous Generator: - stand alone (off grid)
- parallel (on grid)

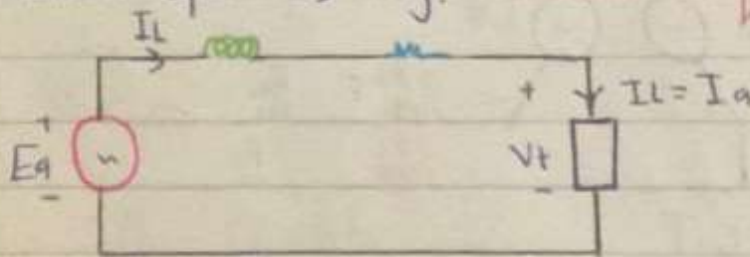* Constant speed \rightarrow why? constant frequency *for class*



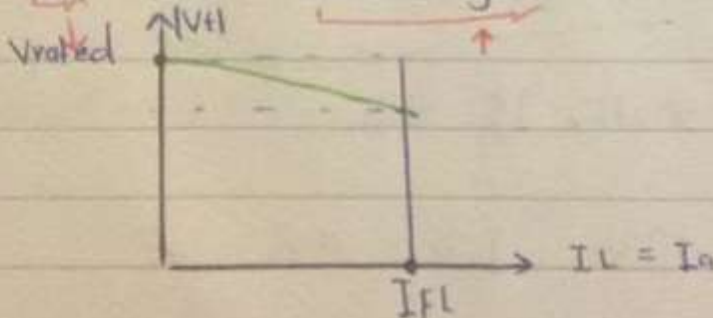
$$\vec{V}_t = \vec{E}_g - \vec{I}_a (R_a + jX_s)$$



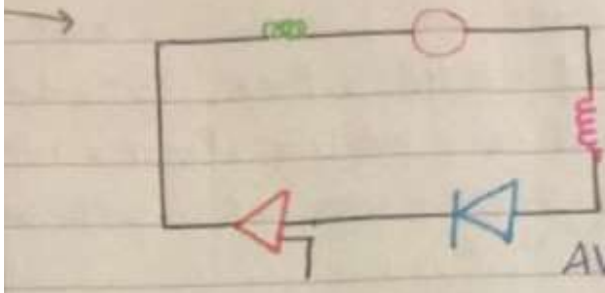

AVR: automatic voltage regulator

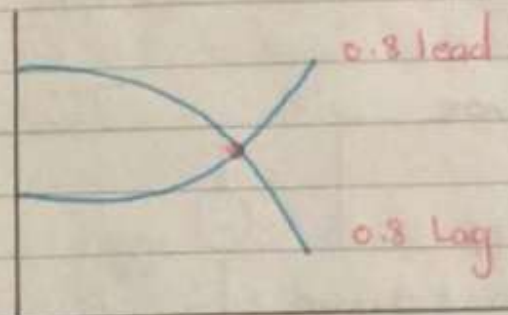


* half Full Load → half the Current


$$E_{g_{F.L}} = \vec{V}_t + \vec{I}_{a_{F.L}} (R_a + jX_s)$$

$$E_a = \sqrt{(V_t \cos \theta + I_a R_a)^2 + (V_t \sin \theta + I_s X_s)^2}$$

$$\%VR = \frac{|E_g| - V_{FL}}{V_{FL}} * 100\%$$

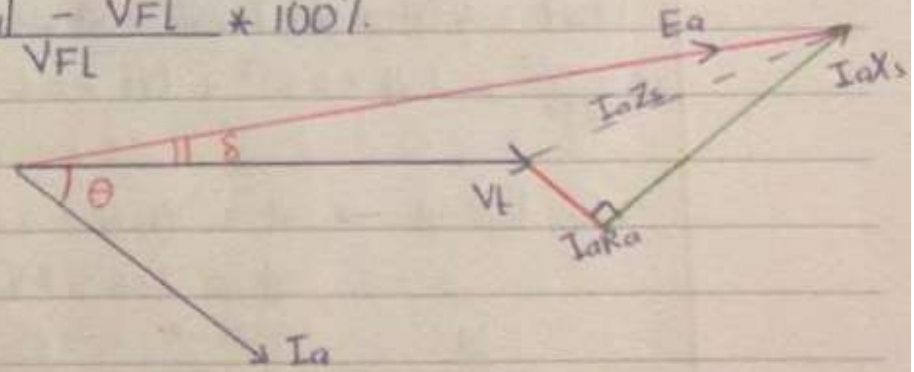

I_a is the Reference

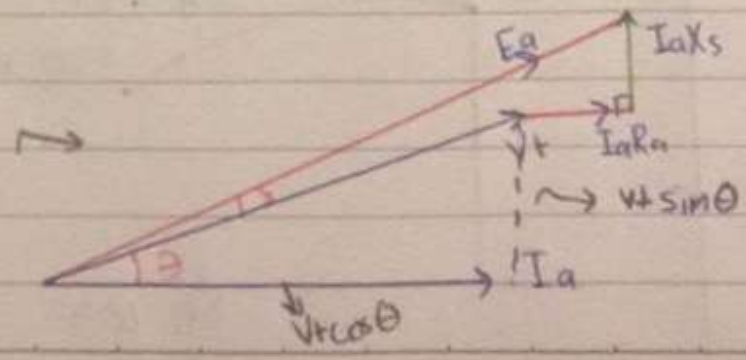


No. Wednesday 26-7

* Example:

$V_{LL} = 480\text{ V}$, $f = 60\text{ Hz}$, $P = 6$, $X_s = 0.1\ \Omega/\text{ph}$
 $I_{FL} = 60\text{ A}$, $\text{PF}_{FL} = 0.8\ \text{Lag}$, $P = 1.5\text{ kW}$,
 $P_{\text{core}} = 1\text{ kW}$, $V_{NL} = 480 \rightarrow E$, Y-connected

Find: n_s


a) $n_s = \frac{120f}{P} = \frac{120 \times 60}{6} = 1200\text{ rpm}$

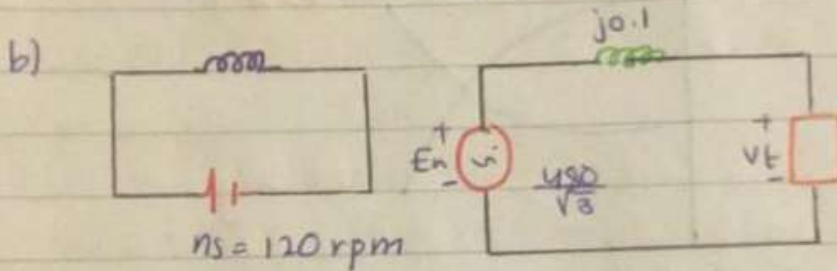

Case 1:-

$E_a = V_t + I_a(R_a + jX_s)$


$\frac{480}{\sqrt{3}} \angle 8$

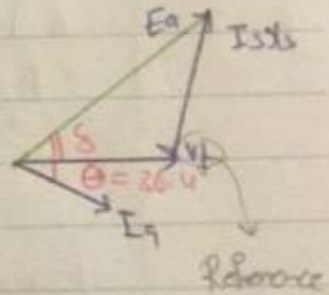

$|E_n| = \sqrt{(V_t \cos \theta + I_a R_a)^2 + (V_t \sin \theta + I_a X_s)^2}$
 $(\frac{480}{\sqrt{3}})^2 = (V_t + 0.8)^2 + (V_t * 0.6 + 60 * 1)^2$


Solve for $V_t \rightarrow V_t = V_{L-N} = 236.8$

$V_t = 236.8 * \sqrt{3} = 410\text{ V}_{LL}$

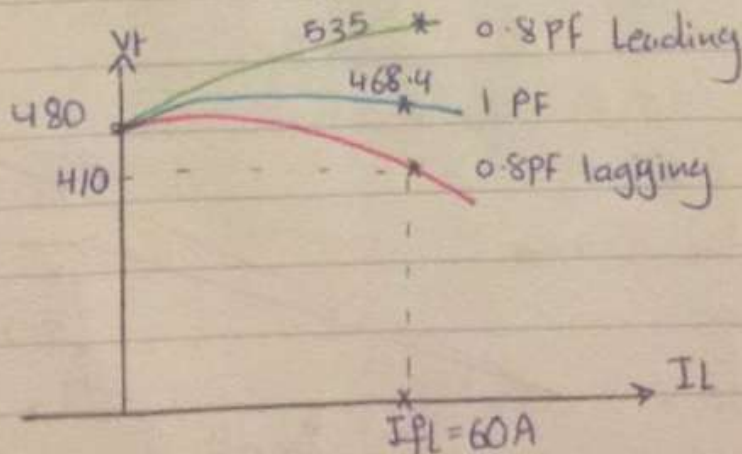

Case 2: Unity Power Factor $\theta = 0$
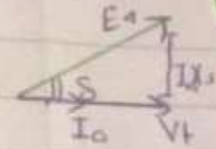
$$\left(\frac{480}{\sqrt{3}}\right)^2 = (V_t \times 1)^2 + (V_t \times 0 + 60 \times 1)^2$$



$$\begin{aligned} \text{Solve for } V_t &\rightarrow V_t = 270.4 \text{ VL-N} \rightarrow V_t = \sqrt{3} \times 270.4 \\ &= 468.4 \text{ VLL} \end{aligned}$$

Case 3: 0.8 PF leading

$$\left(\frac{480}{\sqrt{3}}\right)^2 = (V_t \times 0.8)^2 + V_t \times 0.6 \times (60 \times 1)^2$$

$$\begin{aligned} \rightarrow \text{Solve for } V_t &= 308.8 \text{ VL-N} \\ &= \sqrt{3} \times 308.8 = 535 \text{ VLL} \end{aligned}$$


$$\rightarrow E_a = 4.44 f N \phi$$

$$\textcircled{1} \text{ VR} = \frac{480 - 410}{480} \times 100\% = 17.1\% \quad \text{inductive} \quad \text{التأخرية}$$

$$\textcircled{2} \text{ VR} = \frac{480 - 468.4}{468.4} \times 100\% = 2.6\%$$

$$\textcircled{3} \text{ VR} = \frac{480 - 535}{535} \times 100\% = -10.3\% \quad \text{Capacitive} \quad \text{التأخرية}$$

Q: From HV to LV

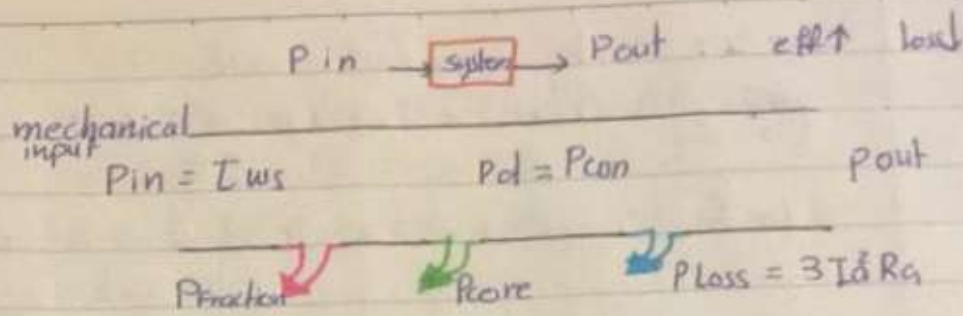

$$P_{out} = \sqrt{3} V_L I_L \cos \theta = 3 V_t I_a \cos \theta$$

$$P_{\text{converted}} = 3 E_a I_a \cos \delta \rightarrow \text{between } E_n \text{ and } I_n$$

$$\textcircled{1} P_{out} = \sqrt{3} * 410 * 60 * 0.8 = 34.1 \text{ kW}$$

$$Q_{out} = \sqrt{3} * 410 * 60 * 0.6 =$$

$$P_{in} = (34.1 + 1.5 + 1) \text{ k} = 36.6 \text{ kW} = P_{out} + \sum \text{losses}$$

$$\eta = \frac{34.1}{36.6} * 100\% = 43.2\%$$

or we can find P_{out} from Power triangle.

$$Q_{out} = P_{out} \cdot \tan \theta = 34.1 \text{ k} * \frac{3}{4} = 25.6 \text{ kVAR}$$

$$\text{apparent} = S_{out} = \sqrt{3} V_L I_L = 3 V_{ph} * I_{ph}$$

$$= \sqrt{(P_{out})^2 + (Q_{out})^2}$$

$$\text{or } S_{out} = \frac{34.1}{0.8} = 42.6 \text{ kVA}$$

$$\omega_s = \frac{2\pi n_s}{60}$$

$$f_s = \frac{1200}{60} = 20 \text{ Hz}$$

$$\omega_s = 2\pi f_s$$

$$\omega_e = \frac{P}{2} \omega_s$$

$$\omega_e = 388 \text{ rad/s}$$

$$T_{in} = \frac{P_{in}}{\omega_s} = \frac{36.6}{125.7} = 291.8 \text{ N.m}$$

$$f_e = 60 \text{ Hz}, \quad \omega_e = 2\pi \cdot 60 = 388 \text{ rad/s}$$

↳ electrical

$$f_e = \frac{P}{2} \cdot f_m$$


$$\omega_s = 2\pi \cdot 20 = 125.7 \text{ rad/s}$$

*Grid: infinite bus = the voltage on this bus bar is fixed and $f = 60 \text{ Hz}$ (frequency for supplying)

→ in generator mode there is a motor action

Synchronous run always on constant speed

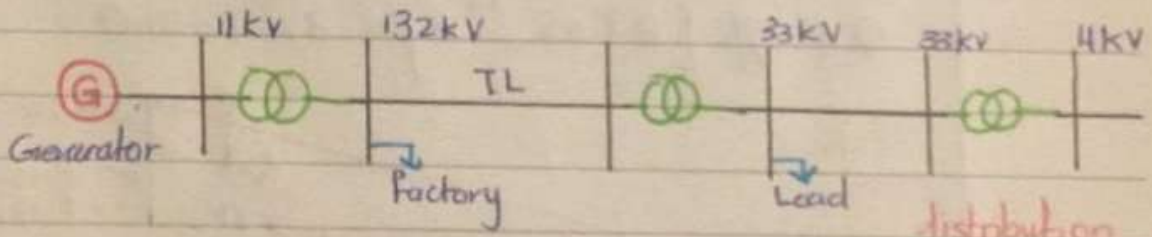$I_a X_s$ → the drop voltage, we can take V_t reference because E_f → over excited



distribution medium voltage

*Power Equation

$$E_a \sin \delta = I_a X_s \cos \theta$$

$$\frac{E_a \sin \delta}{X_s} = I_a \cos \theta$$

$$P_{\text{developed}} = \frac{3V_t E_a \sin \delta}{X_s} = 3V_t I_a \cos \theta$$

$$P_d = P_{\text{out}} \quad (R \approx 0.0)$$

$$\frac{3V_t E_a \sin \delta}{X_s} = 3V_t I_a \cos \theta = I_d \cdot \omega_s$$


$$E_a \cos \delta = I_a X_s \sin \theta + V_t$$

$$\frac{E_a \cos \delta}{X_s} = I_a \sin \theta + \frac{V_t}{X_s}$$

$$\frac{3V_t E_a \cos \delta}{X_s} = 3V_t I_a \sin \theta + \frac{3V_t^2}{X_s}$$

$$I_a \frac{3V_t \sin \theta}{X_s} = \frac{3V_t E_a \cos \delta}{X_s} - \frac{V_t^2}{X_s}$$
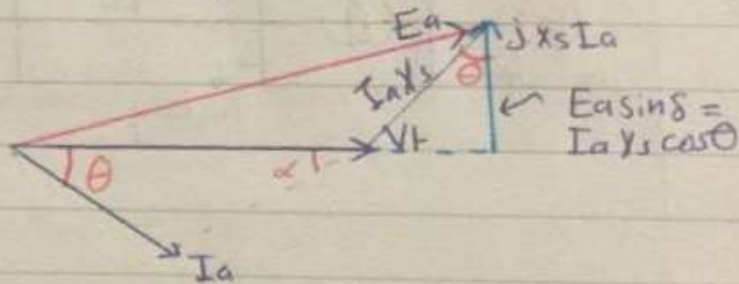
$$Q = \frac{3V_t}{X_s} [E_a \cos \delta - V_t] = 3V_t I_a \sin \theta$$




$$3V_t I_a \sin \theta = \frac{3V_t E_a \cos \delta}{X_s} - \frac{V_t^2}{X_s}$$

$E_a \cos \delta > V_t \rightarrow$ over excited Generator

$Q > 0 \rightarrow$ supply VAR

$E_a \cos \delta < V_t \rightarrow$ under excited

$Q < 0 \rightarrow$ absorb VAR

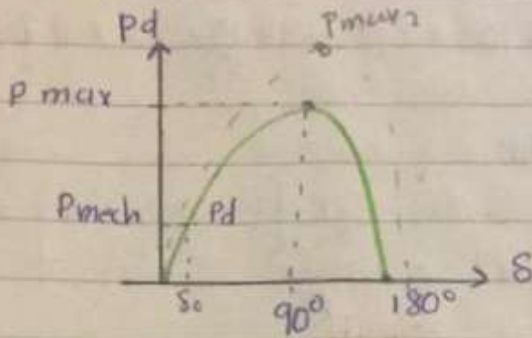


$$P_{max} = \frac{3VtE_a}{X_s}$$

$$P_{d1} = P_{d2}$$

$$E_1 \sin \delta_1 = E_2 \sin \delta_2$$
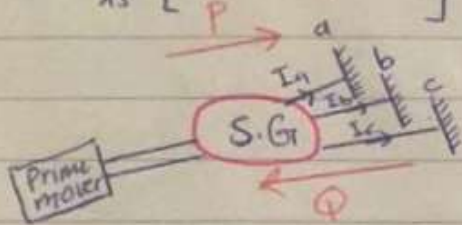
$$Q = \frac{3Vt}{X_s} [E_a \cos \delta - Vt] \quad \text{نقله توريه لاس - توريه في}$$





$$n = \text{constant} = n_s$$

$$T_{net} = T_{mech} - T_s = 0$$

$$P_{mech} = P_{in} - P = P_d$$

* Example ④: $P_{max} = \frac{3VtE_a}{X_s} = \frac{3 * 230 * 203.8k}{\sqrt{3} * 11.5} = 54.13 \text{ MW}$
 (3φh * Vph) / Xs

* Example ③: $n_s = 180 \text{ rpm}$

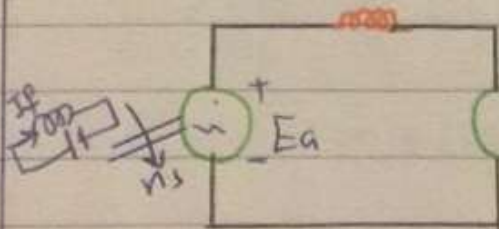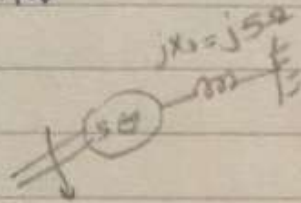

$$I_a = 1000 \text{ A}$$

$$V_{\infty} = \frac{15}{\sqrt{3}} \angle 0, \theta = \cos^{-1} 0.9 = 25.8^\circ$$

$$E_a = V_{\infty} = jI_a X_s = \frac{15}{\sqrt{3}} \times 10^3 \angle 0 + 1000 \angle -25.8^\circ * 5 \angle 90^\circ$$

$$E_a = 11.74 \angle 22.5^\circ \text{ kV} \rightarrow |E_{LL}| = \sqrt{3} * 11.74 = 20.3 \text{ kV}$$


$$P_{out} = P_d = 3Vt I_a \cos \theta = \frac{3Vt E_a \sin \delta}{X_s}$$


$$= 3 \times \frac{15 \times 10^3}{\sqrt{3}} \times 100 \times 0.9 = 3 \times \frac{15 \times 10^3}{\sqrt{3}} \times 11.74 \times 10^3 \sin 22.5^\circ$$

$$P_{out} = 23.38 \text{ MW}$$

$$Q_{out} = 3 V_t I_a \sin \theta = \frac{3 V_t}{X_s} [E_a \cos \delta - V_t] = 11.32 \text{ MVAR}$$
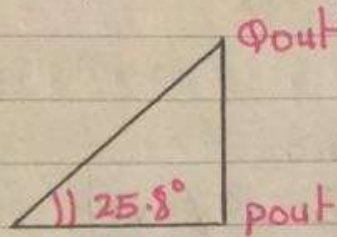
$$n_s \text{ (mech speed)} = 120 \frac{f_e}{p} \rightarrow \text{electrical}$$



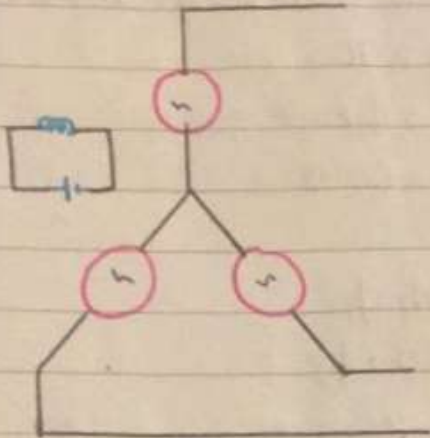

$$V_{LLOC} = 360 = E_{ALL}$$

$$I_P = 3.6 \text{ A}$$

$$60 \text{ Hz}$$

$$I_{P2} = 2.4 \text{ A}, P_2 = 40 \text{ Hz}$$

$$E_1 = 360 \text{ V}, I_{P1} = 3.6 \text{ A}, P_1 = 60 \text{ Hz}$$


$$E_2 = ? \quad I_{P2} = 2.4 \text{ A}, P_2 = 40 \text{ Hz}$$

$$E_{rms} = 4.44 f N \phi$$

$$\rightarrow E_{rms} \propto f \cdot I \phi$$

$$\frac{E_2}{E_1} = \frac{I_2 f_2}{I_1 f_1}$$
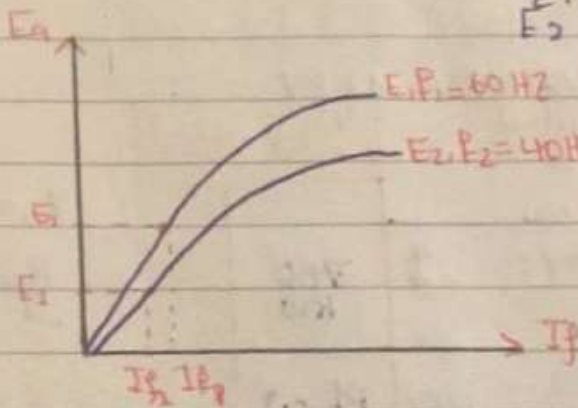
$$E_2 = 360 \times \frac{2.4}{3.6} \times \frac{40}{60} = 160 \text{ Hz}$$



b. $V_{NL} = E_{NL} = 620 \text{ V}, f = 60 \text{ Hz} \rightarrow \text{ms} = \frac{120}{P}$

$$\Phi_2 = 0.85 \Phi_1$$

$$f_2 = 1.1 f_1 \rightarrow f_2 = 1.1 \times 60 = 66 \text{ Hz}$$

$$\frac{E_2}{E_1} = \frac{f_2 \cdot \Phi_2}{f_1 \cdot \Phi_1}$$

$$E_2 = 1.1 \times 0.85 \times 620 = 580 \text{ V}$$

Q2: $P=8$, $n_s=900$ rpm (60Hz) Y-connection


$N_p = 120$ turns $k_u = 0.90$

$E_{LL} = V_{mL} = 2400$ V $\rightarrow \phi_p = ?$


$f = \frac{n_s \times P}{120} = \frac{900 \times 8}{120} = 60$ Hz

$E_{rms} = 4.44 k_w f N_{ph} \phi_p$
 $\frac{2400}{\sqrt{2}} = 4.44 \times 0.9 \times 60 \times \phi_p$
 $\phi_p = \text{wb}$

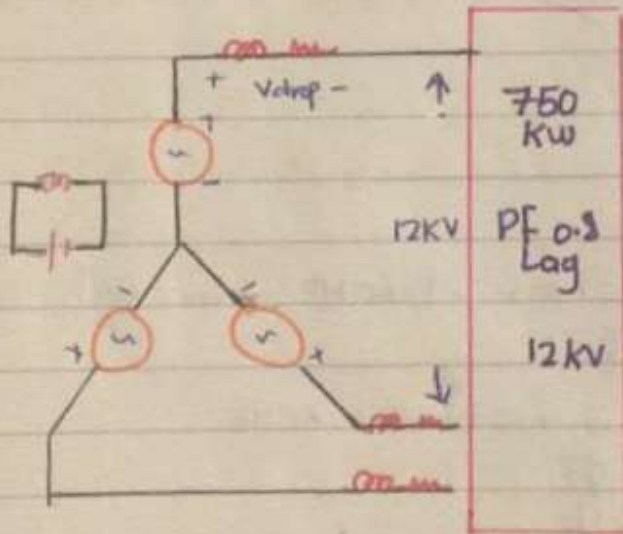Q3: 3-ph, 1000 kVA, 12 kV
rated V_{L-L} *rated*



$X_s = 30 \Omega$
 $R_a = 0.0$

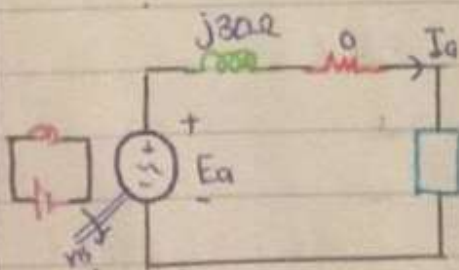

$I_a = 45.1 \angle -36.9^\circ$ A



$E = V_t + jI_a X_s$

$PF = 0.8 \rightarrow \cos^{-1} 0.8 = 36.9^\circ$

$$V_f = \frac{1200}{\sqrt{3}} \angle 0^\circ$$

For Y connection $|I_a| = |I_l| = \frac{P_{3\phi} / PF}{\sqrt{3} V_{LL}} = \frac{750 \times 10^3 / 0.8}{\sqrt{3} \times 12 \times 10^3}$

$$|I_a| = 45.1 \text{ A}$$

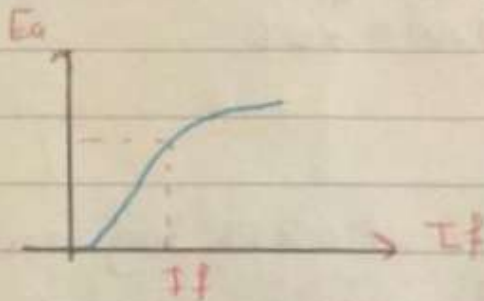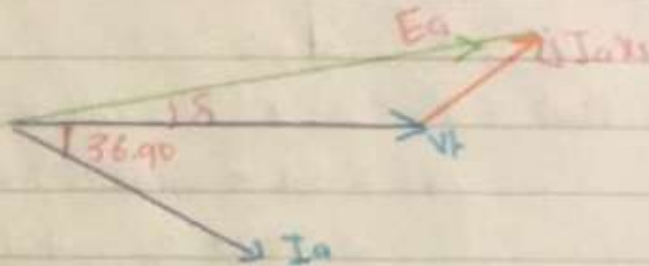

$$E_a = \frac{1200}{\sqrt{3}} \angle 0^\circ + 45.1 \angle -36.9^\circ \times 30 \angle 90^\circ$$

$$= \frac{1}{\sqrt{3}} 7816 \angle 7.9^\circ \text{ V}$$

$$|E_{aLL}| = \sqrt{3} \times 7816 = 13.5 \text{ kV}$$

$|E_a| > |V_t| \Rightarrow$ Generator is overexcited, Generator supplies VAR


$$\%VR = \frac{|V_{nl}| - |V_l|}{|V_l|} \times 100\%$$

$$= \frac{|E_a| - |V_t|}{|V_t|} \times 100\% = \frac{13.5 - 12}{12} \times 100\% = 12.5\%$$

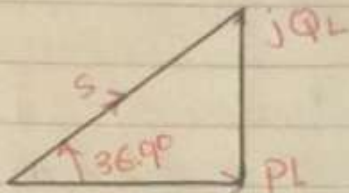Q.5: 1200 KVA (1.2 MVA), 6.6 kV, 3ph Y-Connection

$R_a = 0.4 \Omega / \text{ph}$, $X_s = 6 \Omega / \text{ph}$, $P = 2$, $f = 50 \text{ Hz}$

$P_{out} = P_{FL}$ $S_{out} = S_{FL} = 1200 \text{ KVA}$



$$P_{out} = P_L = S_L \times \text{PF} = 1200 \text{ K} \times 0.8 = \quad \text{KW}$$


$$Q_L = S_L \times \sin(36.9^\circ) = P_L \times \tan(36.9^\circ)$$

$$= 960 \times \frac{3}{4} = 720 \text{ KVAR}$$


$$= 1200 \text{ K} \times 0.6$$

$$n_s = 3000 \text{ rpm}$$

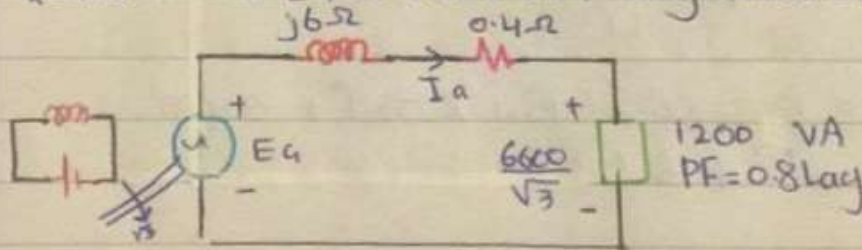* Find:- a) E_a FL at 0.8 PF Lag and rated voltage.



b) V_t for leading PF

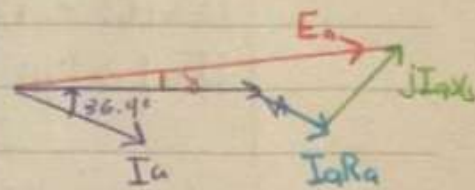

$$\boxed{a} \quad \vec{E}_a = \vec{V}_t + \vec{I}_a (R_a + jX_s)$$

$$\boxed{b} \quad \vec{V}_t = \frac{6600}{\sqrt{3}} \angle 0^\circ$$

$$|I_{\text{mph}}| = |I_L| = \frac{S_{3\phi}}{\sqrt{3} V_L} = \frac{1200 \times 10^3}{\sqrt{3} \times 6600} = |I_{aFL}| = 105 \text{ A}$$


$$|I_{aFL}| = 105 \angle 36.9^\circ \text{ A}$$

$$E_a = 66W \angle 0 + 105 \angle -36.9^\circ (0.4 + j6)$$

$$\vec{E}_a = \frac{\sqrt{3}}{1} \times 4249.4 \angle 6.6^\circ V$$

$$|\vec{E}_{aLL}| = \sqrt{3} \times 4249.4 = 7360V$$

Underexcited supply VAR

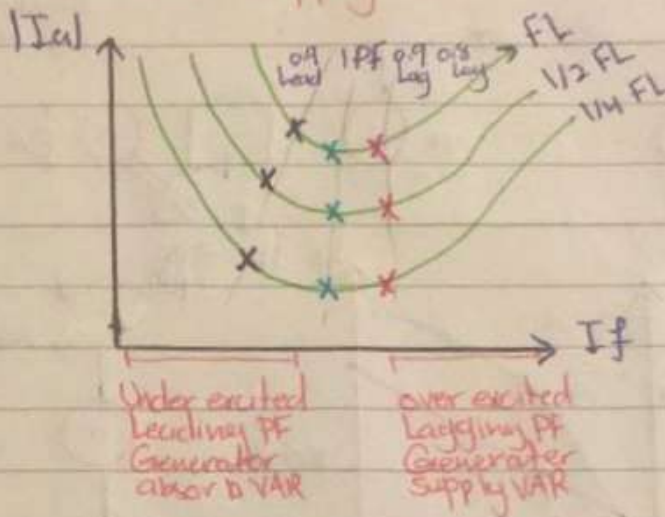


$$E_a \angle \delta_2 = \vec{V}_t \angle \theta + \vec{I}_a (R_a + jX_s)$$

$$|\vec{E}_a| = \sqrt{(V_t \cos \theta + I_a R_a)^2 + (V_t \sin \theta - I_a X_s)^2}$$

$$4249.4 = \sqrt{(V_t \times 0.8 + 105 \times 0.4)^2 + (V_t \times 0.6 - 105 \times 6)^2}$$


Solve $V_t \rightarrow V_t = 4837.2V$
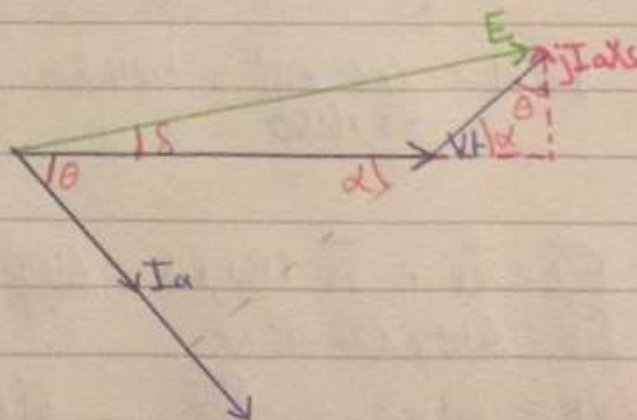
$$V_{tLL} = \sqrt{3} \times 4831.1 = 8367.9V$$



$$|E_a - V_t|$$

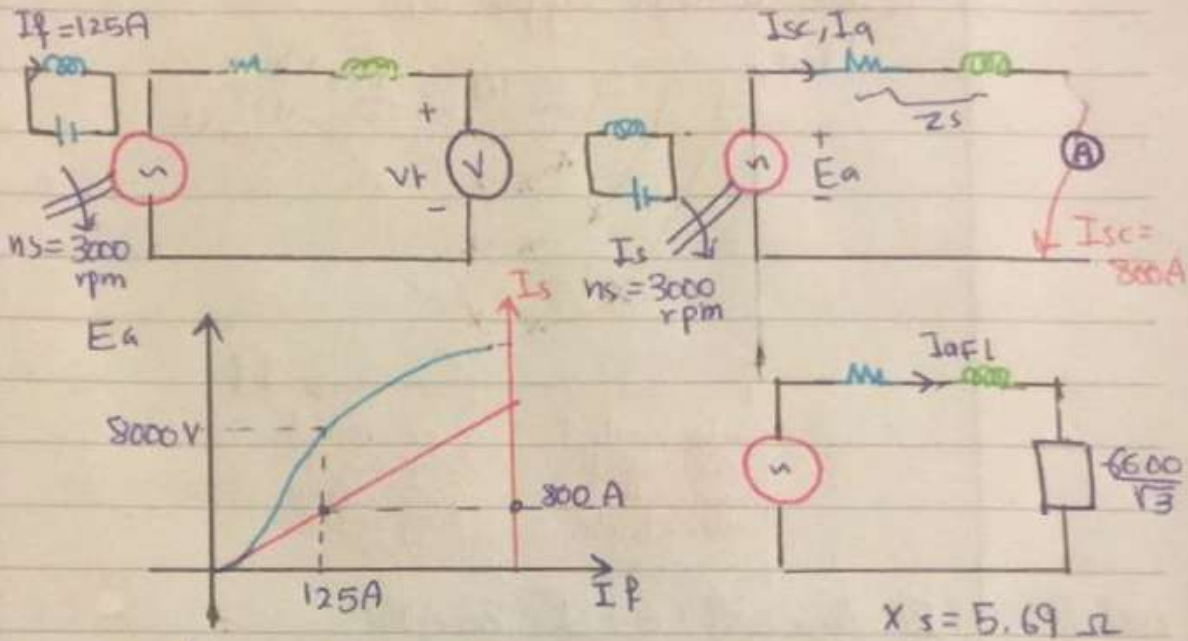Q.6:- 3-ph 6000 KVA, 6.6 KV, Y-connected, 2-pole
 $f = 50\text{ Hz}$ $I_f = 125\text{ A} \rightarrow V_{oc} = 8000\text{ V}$ at $n = n_s = 3000\text{ rpm}$
 $I_f = \quad \text{A} \rightarrow I_{sc} = 800\text{ A}$ at $n = n_s = 3000\text{ rpm}$



$$|Z_s| = \frac{E}{I_{sc}} = \frac{8000/\sqrt{3}}{800} = 5.7 \Omega$$

$$|Z_s| = \sqrt{R_a^2 + X_s^2} \Rightarrow X_s = \sqrt{Z_s^2 - R_a^2} = \sqrt{5.7^2 - 0.22^2}$$

$$I_a \text{ FL} \times R_a = 0.03 \times \frac{6600}{\sqrt{3}} \rightarrow R =$$

$$I_a \text{ FL} = \frac{6000 \times 10^3}{\sqrt{3} \times 6600} = 524.8\text{ A} \rightarrow R_a = 0.22 \Omega$$

$$\vec{E}_L = \vec{V}_t + \vec{I}_L (R_a + jX_s) = \frac{6600}{\sqrt{3}} + 524.8 \angle 36.9^\circ (0.22 + j5.7)$$


$$\vec{E}_a = 6148 \angle 22.4^\circ \text{ V}$$

$$\%VR = \frac{6148}{6600/\sqrt{3}} = 61\%$$

Tutorial #2:-

Synchronous Motor

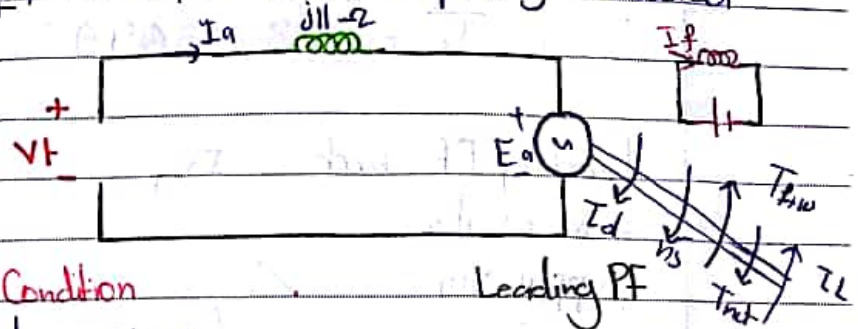Q.1: \rightarrow mech. power
 3000hp, 6600V, 60 Hz, 3-ph, Y-connected




\rightarrow Full Load Condition

$V_t = \text{rated} = 6600V$

$P_{out} = 3000hp = \frac{3000 \times 746}{\sqrt{3}}$

$PF = \cos\theta$

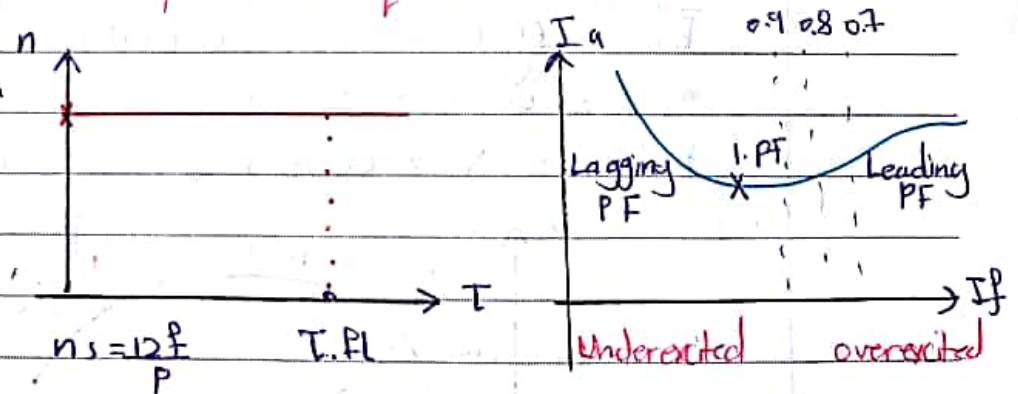* Synchronous motor used to make speed constant because it has constant speed-torque characteristic.



$= 0.746 = \frac{P_{out}}{P_{in}}$

a. $S_{ph} = V_{ph} I_{ph} = \frac{P_{in}}{PF}$

$P_{out} = 3000 \times 746 = 2238KW$

$P_{in} = \frac{2238}{\sqrt{3}} = 3000KW = 3MW$


$S_{\phi} = \frac{3M}{0.8} = 1.25 MVA/ph = 1250 KVA/ph$

$$|I_a| = |I_{ph}| = \frac{S \phi}{\sqrt{\phi}} = \frac{1250 \times 10^3}{\frac{6600}{\sqrt{3}}}$$

$$\rightarrow |I_a| = 328 \text{ A}$$

$$\vec{I}_a = 328 \angle +36.9^\circ \text{ A}$$

Leading PF mode
→ overexcited
Supply Var

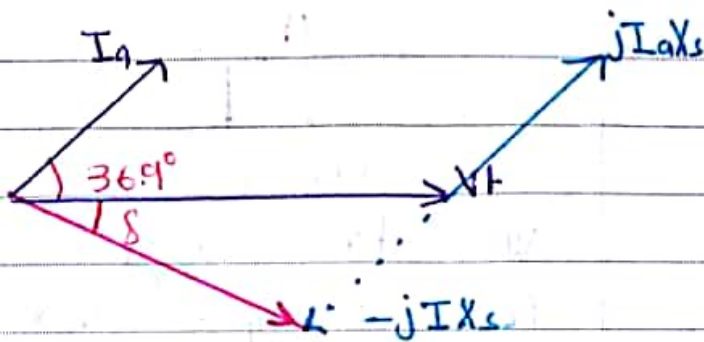


$$\vec{V}_T = \vec{E}_g + \vec{I}_a(R_a + jX_s)$$


$$\vec{E}_g = \vec{V}_T - \vec{I}_a(R_a + jX_s)$$

$$\vec{E}_g = \frac{6600}{\sqrt{3}} - 328 \angle 36.9^\circ (j11)$$
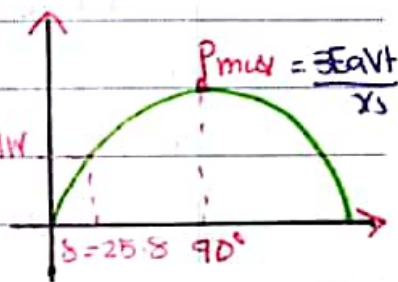
$$= 6636.8 \angle -25.8^\circ \text{ V}$$


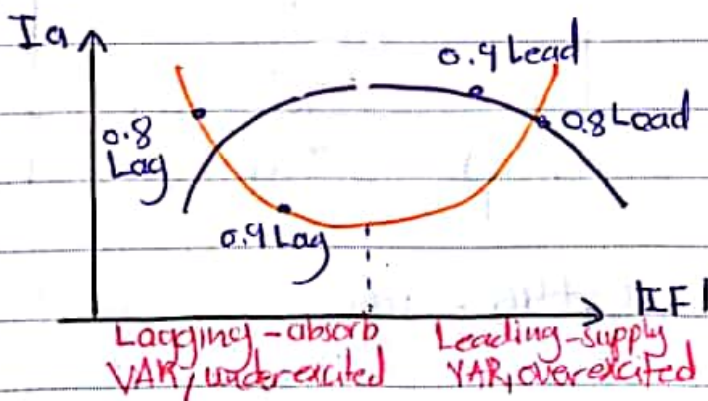
$$E_g \text{ L-L} = \sqrt{3} * 6636.8 \angle -25.8 = 11.494 \text{ kV}$$



$$P_{in} = 3 I_a \cos \theta$$

$$= \sqrt{3} V_L I_L \cos \theta$$

$$P_d = P_{conv} = 3 E_g I_a \cos \theta$$

$$= T \omega_s$$

$$P_{out} = T \omega_s = 2238 \text{ kW}$$

$$P_{co} = 3 I_a^2 R_a$$

$$= \frac{2 \pi n_s}{60}$$


$$= 4 \pi \frac{f}{p}$$

$P_{rot} = P_{core}$
P Friction
and winding

Q.2:- 3ph, P=4, f=60Hz, Y connection, S.M

$V_{tLL} = 3980V \rightarrow |E_a|_{LL} = 3100V \quad I_f = 25A$

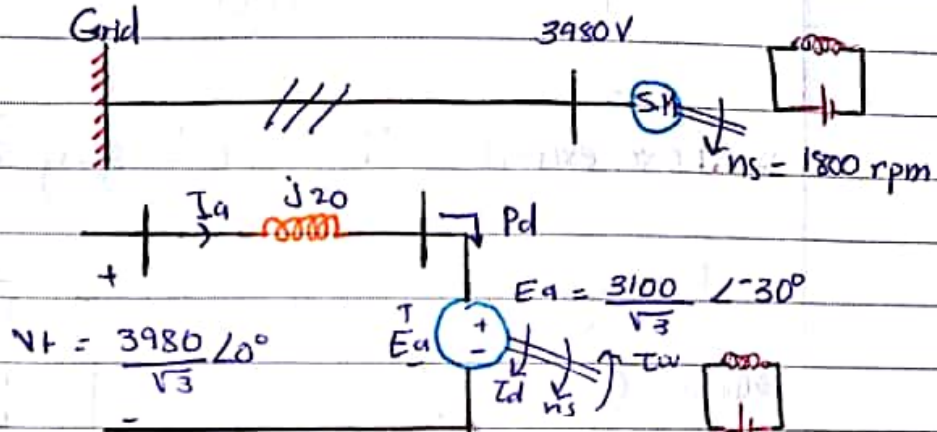$X_s = 22 \Omega \quad \delta = 30^\circ$




$\vec{I}_L = \vec{I}_a = \frac{\vec{V}_t - \vec{E}_a}{jX_s} = \frac{\frac{3980}{\sqrt{3}} \angle 0^\circ - \frac{3100}{\sqrt{3}} \angle -30^\circ}{22 \angle 90^\circ}$

$= 53 \angle -39.9^\circ A$

$PF = \cos \theta = \cos(39.9) = 0.767 \text{ lag.}$

$T_d = \frac{P_d}{\omega_s}, \quad P_d = \frac{3V_t E_a \sin \delta}{X_s} = 3V_t I_a \cos \theta$

$P_d = P_{in} \rightarrow R = 0.0$

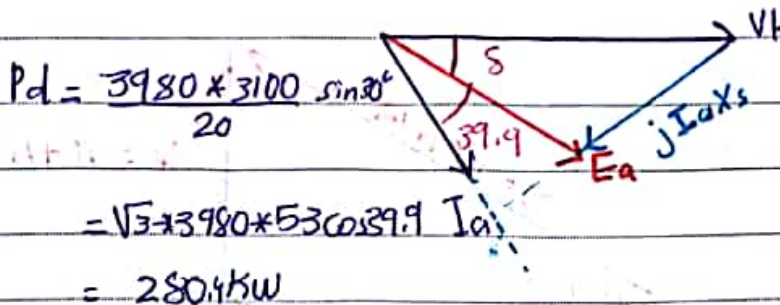

$P_d = \frac{3980 \times 3100 \sin 30^\circ}{20}$

$= \sqrt{3} \times 3980 \times 53 \cos 39.9 \text{ Ia}$
 $= 280.4 \text{ kW}$


$T_d = \frac{280.4 \times 10^3}{188.5} = 1487.4 \text{ N.m}$

No. Sunday 6/8

Q.3: 3 ϕ , Y connected, 400 Volt, $P_{out} = 12 \text{ hp}$, $PF = 0.86 \text{ lag}$
 $\Delta p \text{ Losses} = 1200 \text{ watt}$, $R_u = 0.75$, η ??

$$\eta = \frac{P_{out}}{P_{in}} = \frac{12 \times 746}{12 \times 746 + 1200} \times 100\% = 88\%$$

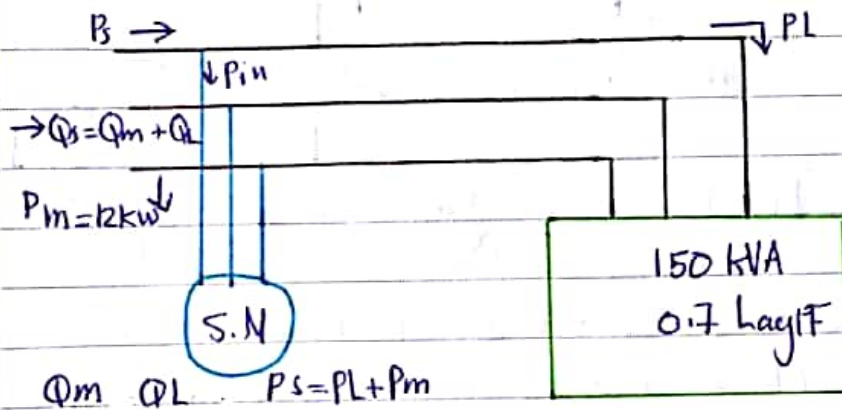
Q.4: overexcited S.M \rightarrow PF Lagging so it's supply VAR



q. $\theta = \cos^{-1} 0.7 = 45.5^\circ$

$$PL = 150 \text{ k} \times 0.7 \rightarrow 105 \text{ kW}$$
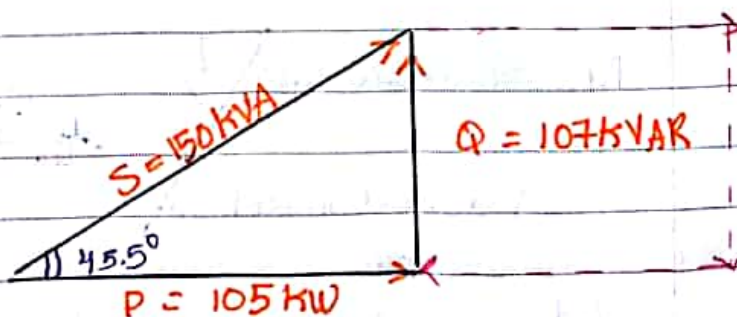
$$Q_L = PL \tan \theta = 107 \text{ kVAR}$$




$$Q_m = 107 \text{ kVAR} \rightarrow S_m \sqrt{Q_m^2 + P_m^2} = \sqrt{12^2 + 107^2} = 107.6 \text{ kVA}$$

$$\theta_m = \tan^{-1} \left(\frac{Q_m}{P_m} \right) = 83.6^\circ$$

$$\vec{S} = 107.7 \angle -83.6^\circ \text{ VA}$$

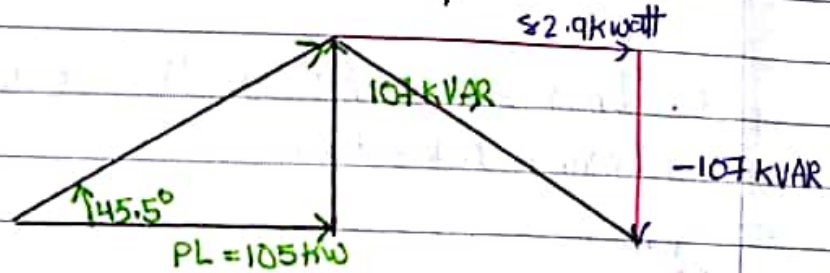b. $P_{out} = 100 \text{ hp} \rightarrow P_{out} = 100 \times 746 \rightarrow 74600 \text{ watt}$
 $P_{in} = 82.9 \text{ kWatt.} \rightarrow \frac{P_{out}}{P_{in}} = \text{eff}$




$$S_m = \sqrt{(82.9)^2 + (107)^2} = 135.3 \text{ kVA}$$

$$\theta_m = \tan^{-1}\left(\frac{Q_m}{P_m}\right) = \tan^{-1}\left(\frac{107}{82.9}\right) = 52.2^\circ$$


$$PF = \cos(52.2) = 0.6 \text{ leading.}$$

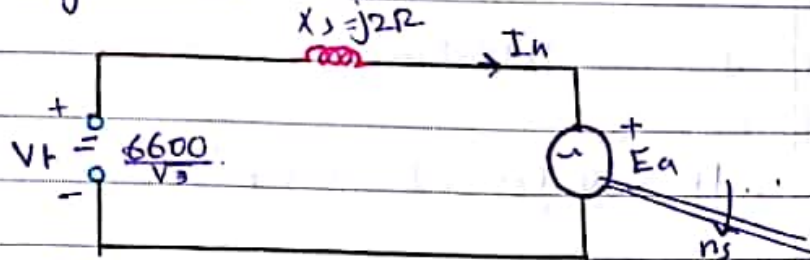Q.5: 6600 Volt, 50 Hz, $p=6$, Y connection SM. $P_{in} = 400 \text{ kWatt}$
 0.8 PFLag. / $R_a = 0 \Omega$



$$P_{in} = \sqrt{3} I_L V_L \cos\theta \Rightarrow I_L = \frac{400 \text{ k}}{\sqrt{3} \times 6600 \times 0.8}$$

$$|I_L| = |I_a| = 43.7 \text{ A} \quad \vec{I}_a = 43.7 \angle -36.9^\circ \text{ A}$$

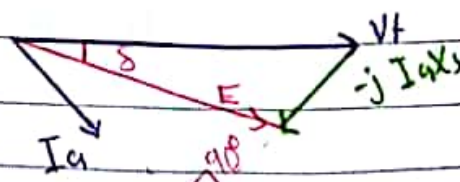

$$b. \vec{E}_a = \frac{6600 \angle 0^\circ}{\sqrt{3}} - j2 (43.7 \angle -36.9^\circ)$$

$$= 3758.6 \angle -1.1^\circ \text{ volt}$$

$$|E_{aL-L}| = 6510 \text{ volt (Under excited, absorbed VAR)}$$

$$c. T_{max} = P_{max} / \omega_s = \frac{V_{tL-L} E_{aL-L}}{X_s \omega_m} = \frac{6600 * 6510}{2 * 2\pi * \frac{50}{3}}$$

$$T_{max} = 204.3 \text{ kN.m}$$

2:

$$a. E_{a2} = 1.25 * E_{a1}$$

$$= 1.25 * 3758.6 = 4698.3 \text{ V}$$

$$\vec{E}_{a2} = 4698.3 \angle -0.86^\circ \text{ volt}$$

$$b. \vec{I}_{a2} = \frac{\vec{V}_t - \vec{E}_{a2}}{jX_s} = \frac{6600/\sqrt{3}}{j2} - \frac{4698.3 \angle -0.86^\circ}{j2}$$

$$= 445.1 \angle 85.5^\circ \text{ A}$$


$$c. \text{PF} = \cos(85.5^\circ) = 0.07 \text{ Leading.}$$

$$d. P_{max} = 1.25 P_{dmax1} = 1.25 * 21.4 \text{ M}$$

$$= 26.75 \text{ M watt}$$

No. Monday 7-8

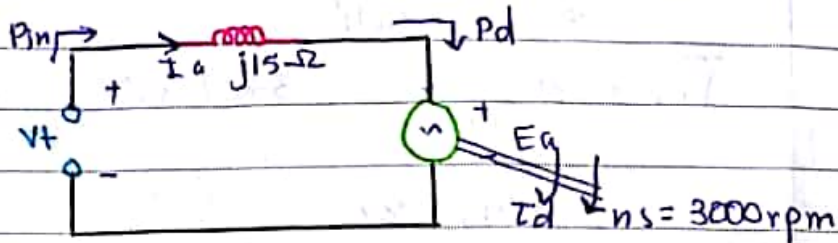Q.6: 3300 volt, 50Hz, P=2 - Y-connected, $Z_s = 15j \Omega$
 $E_{GL-L} = 3300$ volt.



$$a. P_{max} \Big|_{\delta=90^\circ} = \frac{V_{tL-L} E_{GL-L}}{X_s} = \frac{3300 \times 3300}{15} = 726 \text{ kWatt}$$



$$T_{dmax} = \frac{P_{dmax}}{\omega_m} = \frac{726 \text{ K}}{2\pi \times 50} = 2311 \text{ N}\cdot\text{m}$$

$$b. \vec{I}_a = \frac{\vec{V}_t - \vec{E}_g}{jX_s} = \frac{3300/\sqrt{3} - 3300/\sqrt{3} \angle -90^\circ}{j15} = 179.6 \angle -45^\circ \text{ A}$$

$$PF = \cos(45^\circ) = 0.707 \text{ Lagging}$$

$$Q = \sqrt{3} V_{tL-L} I_{aL-L} \sin \theta$$
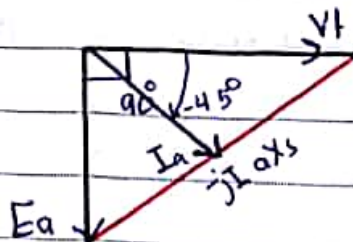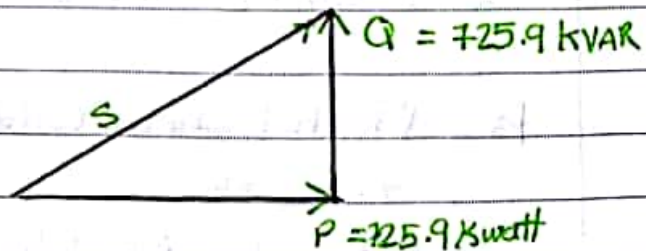
$$= \sqrt{3} \times 3300 \times 179.6 \times \sin(45^\circ) = 725.9 \text{ KVAR} = P_{in} = 725.9 \text{ kWatt}$$



No. _____

$$c. E_{a1} \sin \delta_1 = E_{a2} \sin \delta_2$$

$$E_{a1} \sin \delta_1 = 1.2 E_1 \sin \delta_2$$

$$\delta_2 = 56.4^\circ$$

$$\vec{I}_{a2} = \frac{\vec{V}_t - \vec{E}_{a2}}{jX_s} = \frac{3300/\sqrt{3} \angle 0^\circ - (3300 \times 1.2)/\sqrt{3} \angle -56.4^\circ}{j15}$$


$$= 134 \angle -18.6^\circ$$

$$PF = \cos(-18.6^\circ) = 0.9477 \text{ Lagging.}$$

$$Q = \sqrt{3} \times 3300 \times 134 \times \sin(18.6^\circ)$$

$$= 244.3 \text{ kVAR.}$$

the voltage profile.

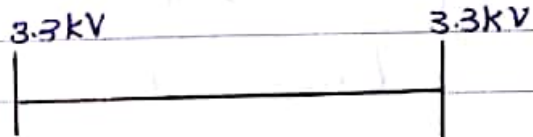

$$d. P_{d3} = 1.1 P_{d2} = P_{d1} \rightarrow \frac{3\sqrt{3} V_t E_{a3} \sin \delta_3}{X_s} = 1.1 \times \frac{3\sqrt{3} V_t E_{a1} \sin \delta_1}{X_s}$$

$$\sin \delta_3 = 1.1 \sin \delta_2 \rightarrow \delta_3 = \sin^{-1}(1.1 \sin \delta_2)$$

$$\delta_3 = 66.6^\circ$$

$$\vec{I}_{a3} = \frac{\vec{V}_t - \vec{E}_{a3}}{jX_s} = \frac{3300/\sqrt{3} - 1.2 \times 3300/\sqrt{3} \angle -66.6^\circ}{j15}$$

$$= 154.9 \angle -25.4^\circ \text{ A}$$


$$P_3 = \sqrt{3} V_L I_L \cos(\theta) = \sqrt{3} \times 3300 \times 154.9 \cos(25.4^\circ)$$

$$= 799.8 \text{ kW}$$

$$= 1.1 \times 726 = 798.6 \text{ kWatt}$$

$$Q_3 = \sqrt{3} V_L I_L \sin \theta = 379.7 \text{ kVAR}$$

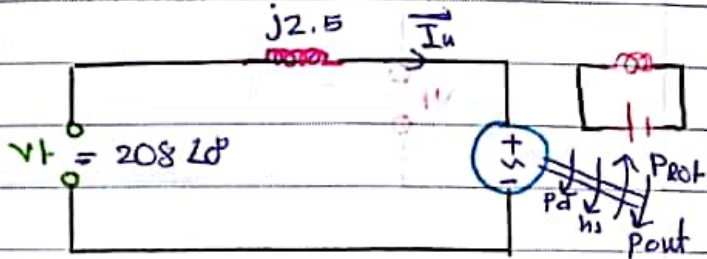Q.7: 208 volt, 45 kVA, 0.8 PF Leading; Δ -connected
60 Hz SM, $X_s = 2.5 \Omega$, $R_a \approx 0$, $P_{rot} = 2.5 \text{ kWatt}$



a. $P_d = P_{rot} + P_{out} = 15 \times 746 + 2500 = 13.69 \text{ kWatt}$
 $= P_{in} (R_a \approx 0)$

$P_{in} = \sqrt{3} V_{tL-L} I_L \cos \theta \Rightarrow |I_L| = 47.5 \text{ A}$

$|I_{\phi}| = 27.4 \text{ A} \rightarrow \vec{I}_a = 27.4 \angle 36.9^\circ \text{ A}$

$E_a = \vec{V}_t - j \vec{I}_a X_s$

$E_a = 208 \angle 0^\circ - 27.4 \times 15 \angle (36.9^\circ + 90^\circ)$

$\vec{E}_a = 255 \angle -14^\circ \text{ Volt}$

$|\vec{E}_{aL-L}| =$


b. $P_d = 30 \times 746 = 3 \times 208 \times 255 \times \sin(\delta_2)$

$\delta_2 = 20.9^\circ, \vec{I}_{a2} = 208 \frac{2.5}{255} \angle -20.6^\circ = 37.9 \angle 18.9^\circ \text{ A}$


$\text{PF} = \cos(18.9^\circ) = 0.94 \text{ leading}$

$P_{in_1} = P_{in_2} = 30 \times 746 \text{ watt}$

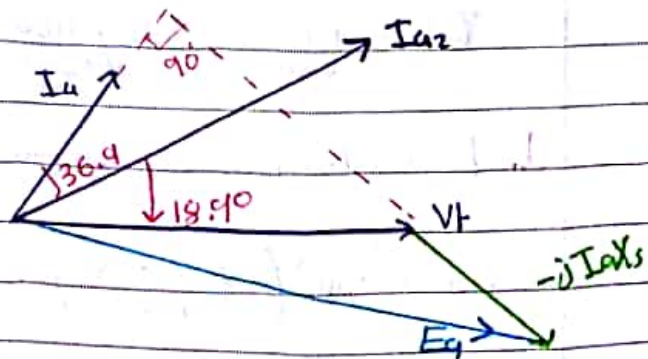$Q_{2in} = \sqrt{3} V_{tL} I_{aL} \sin \theta = 4.4 \text{ kVAR}$



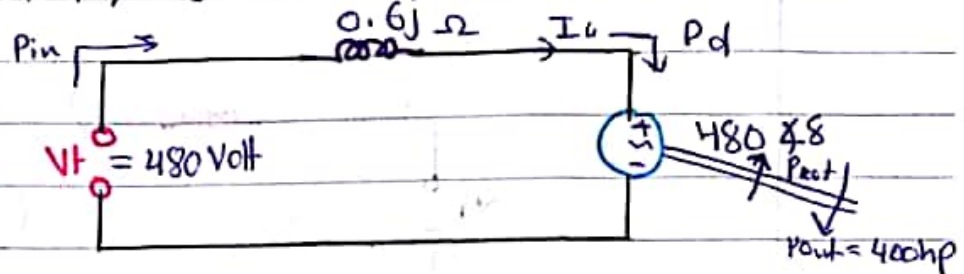Q.8: 480V, 60Hz, 400hp, 0.8 PF leading, $P=8$,
 Δ connected, $X_s = 0.6 \Omega$, $R_a = 0.0 \Omega$



a. $n_s = \frac{120f}{p} = \frac{120 \times 60}{8} = 900 \text{ rpm}$, $\omega_m = 2\pi f_m$

$$\omega_m = 2\pi \times \frac{60}{4} = 30\pi \text{ rad/s}$$

b. $P_{in} = P_d = P_{out} = 400 \times 746 \text{ watt}$

$$400 \times 746 = \sqrt{3} \times 480 \times I_L \times 0.8$$

$$I_L = 448.6 \text{ A}$$

$$\vec{I}_a = 259 \angle -36.9^\circ \text{ A}$$

$$\vec{E}_a = 480 - 0.6 \times 259 \angle 90^\circ - 36.9^\circ = 406.4 \angle -17.8 \text{ volt}$$

c. $T_d \text{ max} = \frac{P_d \text{ max}}{\omega_m} = \frac{3V_t E_a}{X_s \omega_m} = \frac{3 \times 480 \times 406.4}{0.6 \times 2\pi \times \frac{60}{4}}$

$$= 10354.1 \text{ N.m}$$

$$T_d = \frac{P_d}{\omega_m} = \frac{746 \times 400}{2\pi \times \frac{60}{4}} = 3167.7 \text{ N.m}$$

d. $E_{a2} = 1.3 E_{a1} \rightarrow E_{a2} \sin \delta_2 = E_{a1} \sin \delta_1 = 1.3 \sin \delta_2 = \sin \delta_1$



$$\delta_2 = \sin^{-1} \left(\frac{\sin(17.5^\circ)}{1.3} \right) \rightarrow \delta_2 = 13.6^\circ$$

$$\vec{I}_{a2} = \frac{\vec{V}_T - \vec{E}_{a2}}{jX_s} = \frac{480 - 1.3 \times 406.4 \angle -13.6}{j0.6}$$


$$I_{a2} = 214.6 \angle 15.1^\circ \text{ A}$$

$$\text{PF} = \cos(13.1) = 0.965 \text{ Leading.}$$

No. Wednesday 9-8

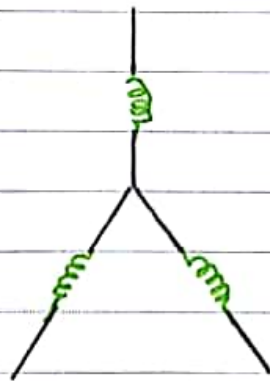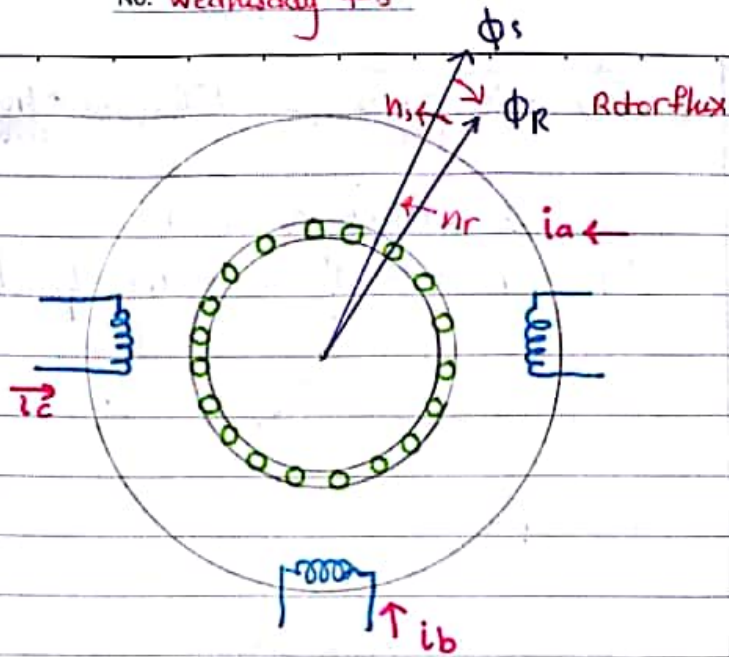

Y-connected

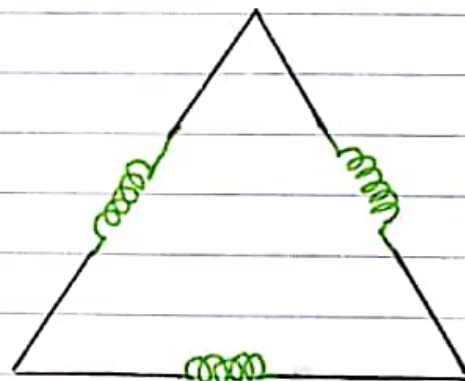

Δ -connected

n_m ; motor speed


$$n_m + n_r = n_s$$




$$n_s - n_m = n_r$$

$$n_m < n_s$$


$$S = n_s - n_m \text{ (rpm)}$$

$$S = \frac{n_s - n_m}{n_s}$$

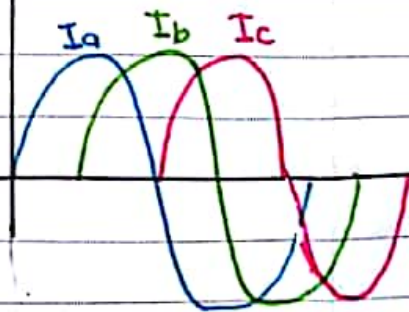

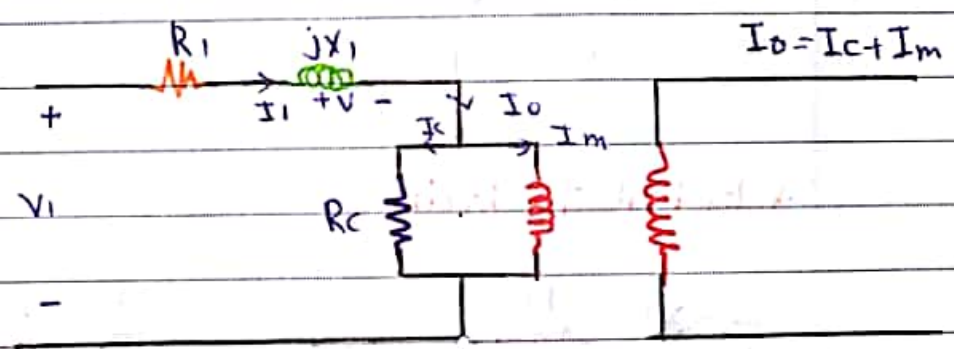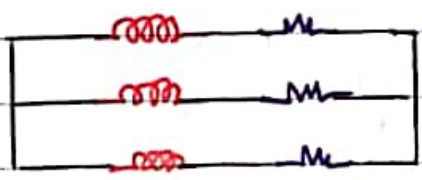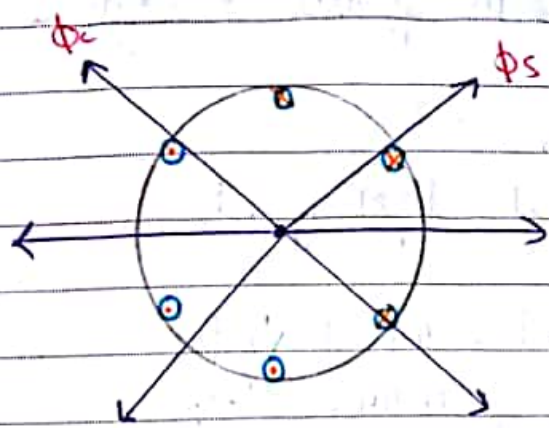

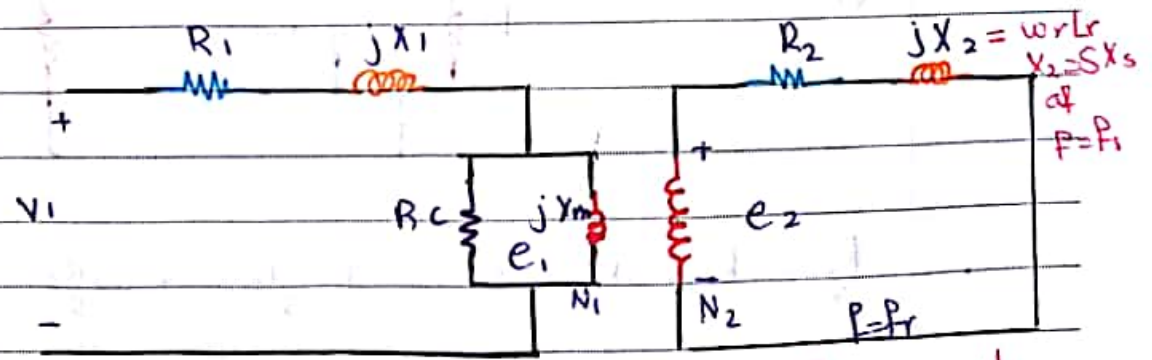* Power dissipated in the core = $I^2 R_c$



armature circuit

rotor circuit

$$n_s = \frac{120 \cdot f_s}{P}$$

$$f_s = \frac{n_s \cdot P}{120}$$

$$P_r = \frac{n_r \cdot P}{120}$$

$$n_r = n_s (1 - s)$$

$$s = \frac{n_s - n_m}{n_s}$$

$$f_r = \frac{(n_s - n_m) \times P}{120} = \frac{P \times n_s}{120} - \frac{n_m P}{120} = f_s - f_2 + S f_s$$

$$f_r = S f_s$$

$$|i_2| = \frac{|e_2|}{|r_2 + jx_2|} = \frac{|e_2|}{\sqrt{R_2^2 + X_2^2}}$$


$$|e_2| = 4.44 f_r N_r \phi$$

$$e_2 = 4.44 f_r N_r \phi$$

$$i_2 = \frac{S E_2}{\sqrt{R_2^2 + (S X_2)^2}} = \frac{E_2}{\sqrt{(R_2/S)^2 + X_2^2}} = I_2 \quad f = f_s$$

$$= S \cdot E_2 \Big|_{f=f_s}$$

* Equivalent Circuit

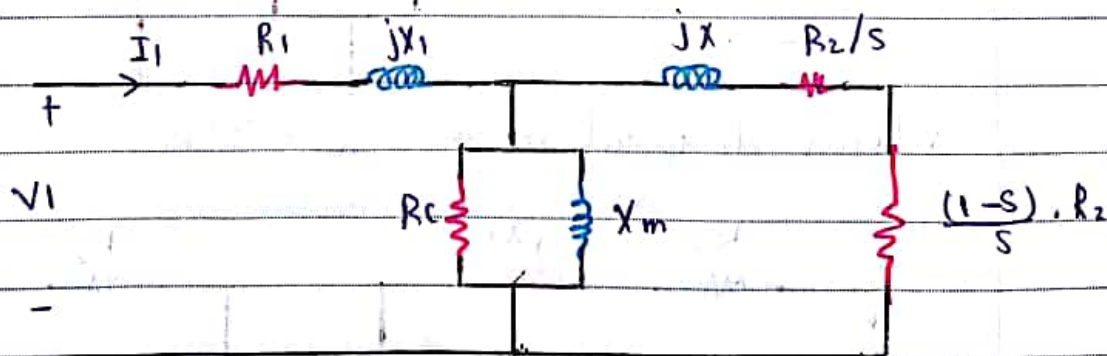

$$\frac{R_2}{s} = R_2 + \frac{S R_2}{s} - S R_2 = \frac{(1-S) R_2}{s} + \frac{S R_2}{s}$$

$$P_d = 3 |I_2|^2 \cdot \left(\frac{(1-S) R_2}{s} \right)$$

$$P_{in} = \sqrt{3} V_L I_L \cos \theta$$

$$= 3 V_L I_L \cos \theta$$

$$P_g = 3 I_a^2 R_c$$

$$P_{cu1} = 3 I_a^2 R_c$$

 P_{conv}

$$P_{cu2} = 3 I_a^2 R_c$$

 P_{frand}

P_g = Air gap power

$$P_g = P_{in} - P_{cu1} - P_{conv}$$

$$= 3 I_a^2 R_c$$

$$P_d = P_g - P_{cu2}$$

$$P_d = 3 I_a^2 (1-s) \cdot R_c$$

$$P_d = T_d \omega_m$$

$$P_d = P_g - s P_g$$

$$P_d = (1-s) P_g$$

$$P_{cu2} = s \cdot P_g$$

$$T_d = \frac{P_d}{\omega_m} = \frac{(1-s) P_g}{(1-s) \omega_s} = \frac{P_g}{\omega_s}$$

$$P_{out} = T_{out} \cdot \omega_m$$


$$\omega_m = \frac{2\pi N_m}{60}$$

$$\omega_s = \frac{2\pi n_s}{60}$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + \sum \text{losses}}$$

at no load \rightarrow Power in R_c

* approximate Circuit :


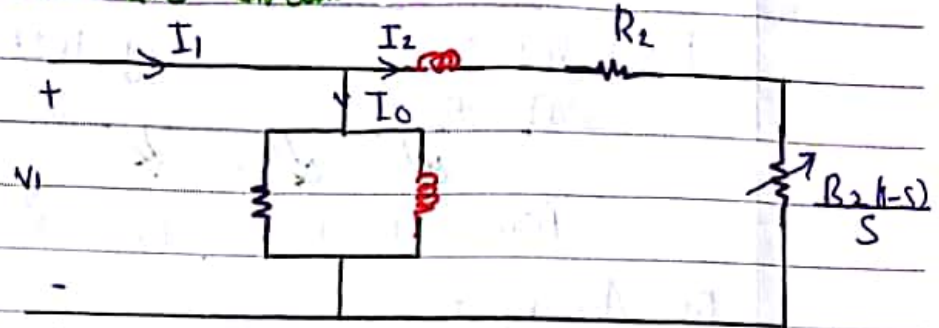


$$I_2 = \frac{|V_1|}{\left| \frac{R_2}{s} + j(X_1 + X_2) \right|}$$


$$|I_2| = \frac{|V_1|}{\sqrt{\left(\frac{R_2}{s}\right)^2 + (X_1 + X_2)^2}}$$

$$\Phi = V_1 I_0 \sin \theta_0$$

$\underbrace{\hspace{2cm}}_{I_m}$

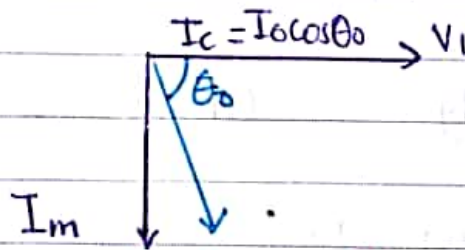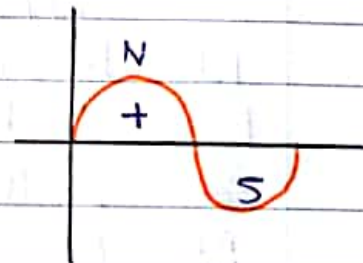


* IEEE Standard model :-

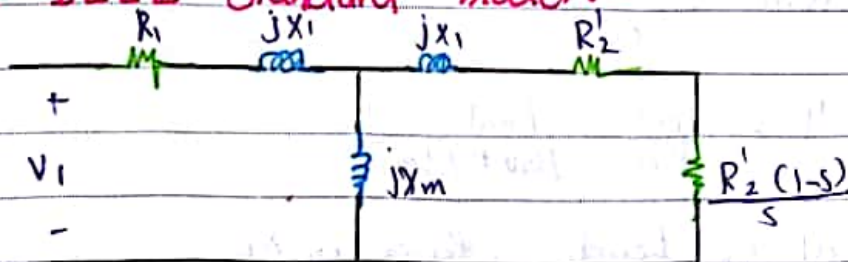


$$Z_{th} = jX_m \parallel (R_1 + jX_1)$$
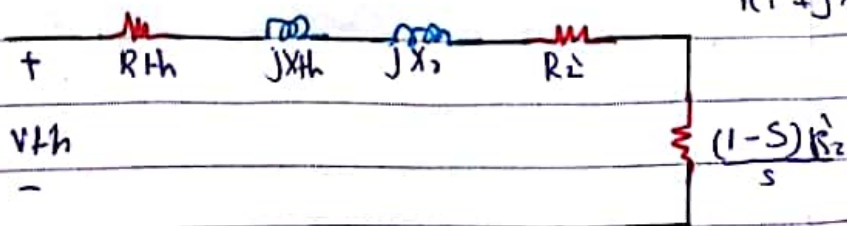
$$V_{th} = V_{oc} = \frac{V_1 + jX_m}{R_1 + jX_m}$$




No. Thursday 10-8

* we derive the exact equivalent Circuit

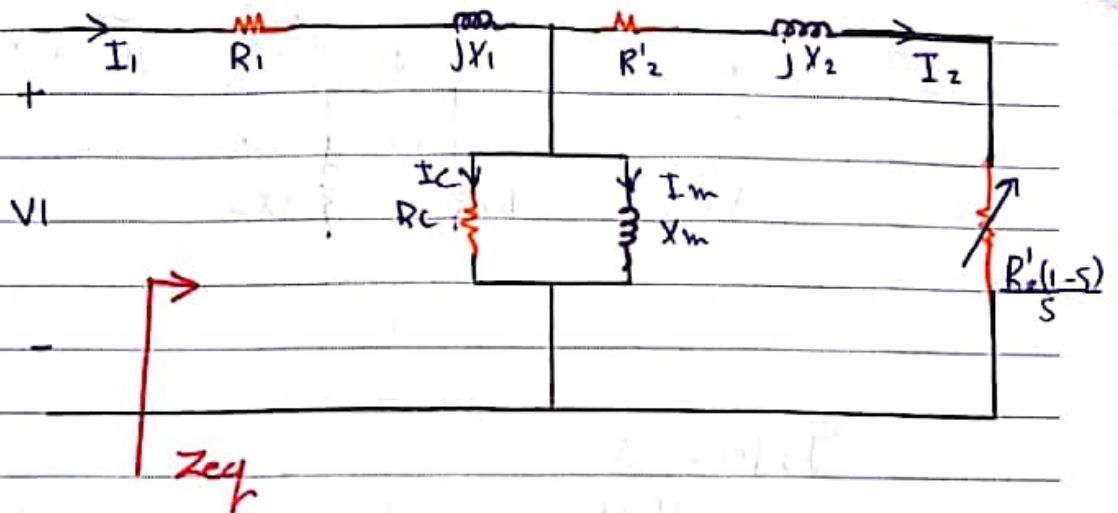
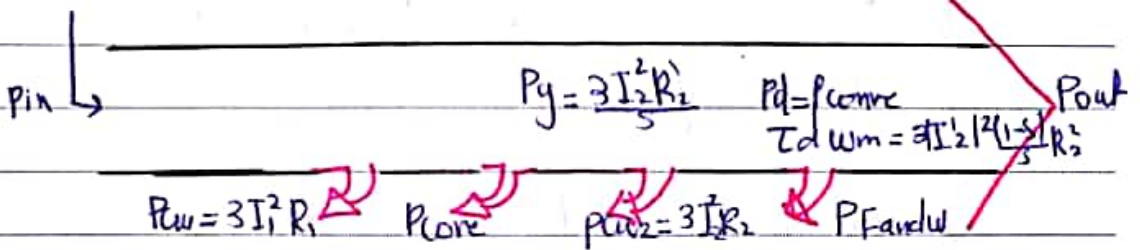
$$P_{in} = 3V_1 I_1 \cos\theta = \sqrt{3} V_L I_L \cos\theta$$




$$Z_{eq}(s) = \left(\frac{R_2'}{s} + jX_2' \right) \parallel (R_c \parallel jX_m) + (R_1 + jX_1)$$

$$P_g = \frac{3I_2^2 R_2'}{s} \rightarrow P_g = \frac{P_{cu2}}{s} \rightarrow P_{cu2} = s P_g$$

$$T_d = \frac{P_d}{\omega_m} = \frac{(1-s) P_g}{(1-s) \omega_s} = \frac{P_g}{\omega_s}$$

② Approximate Model

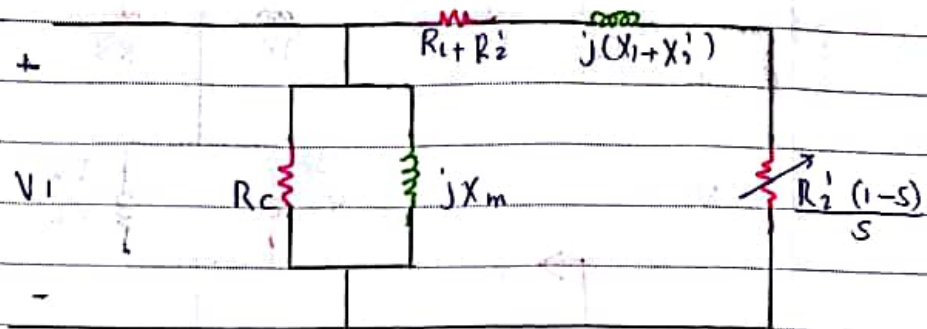


$$\bar{I}_2(s) = \frac{V_1}{(R_1 + \frac{R_2}{s}) + j(X_1 + X_2)} = \frac{V_1}{\sqrt{(R_1 + \frac{R_2}{s})^2 + (X_1 + X_2)^2}}$$

$$P_g = \frac{3|I_2|^2 R_2'}{s} = \frac{3V_1^2 R_2'/s}{(R_1 + \frac{R_2}{s})^2 + (X_1 + X_2)^2}$$

$$\omega_s = \frac{2\pi \cdot 60}{60}$$
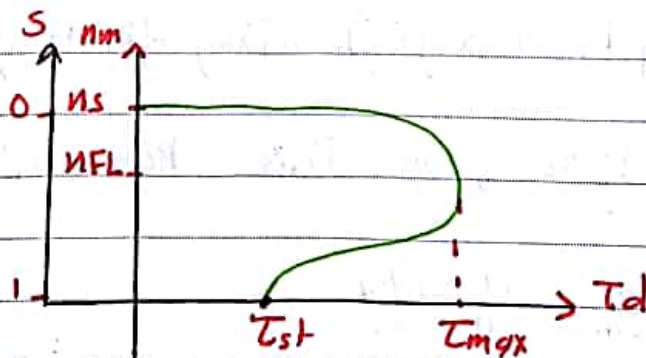
$$T_d(s) = \frac{3V_1^2 R_2'/s}{\omega_s (R_1 + \frac{R_2}{s})^2 + (X_1 + X_2)^2}$$



$$T_d(s) = \frac{3V_1^2 R_2'/s}{\omega_s (R_1 + \frac{R_2}{s})^2 + (X_1 + X_2)^2}$$

① Stand still ($s=1, n_m=0$) (start)

$$T_d(s=1) = \frac{3V_1^2}{\omega_s} \cdot \frac{R_2'}{(R_1+R_2')^2 + (X_1+X_2')^2}$$

② at Full Load (SFL)


$$T_d(sFL) = \frac{3V_1^2}{\omega_s} \cdot \frac{R_2'/SFL}{(R_1 + \frac{R_2'}{SFL})^2 + (X_1 + X_2')^2}$$

*For maximum power at Load (R_2'/s)

$$\frac{R_2'}{s_{max}} = \sqrt{R_1^2 + X_{eq}^2}, \quad s_{max} = \frac{R_2'}{\sqrt{R_1^2 + X_{eq}^2}}$$

$$T_{dmax} \Big|_{s_{max}} = \frac{3V_1^2}{\omega_s} \cdot \frac{R_2'/s_{max}}{(R_1 + \frac{R_2'}{s_{max}})^2 + X_{eq}^2}$$


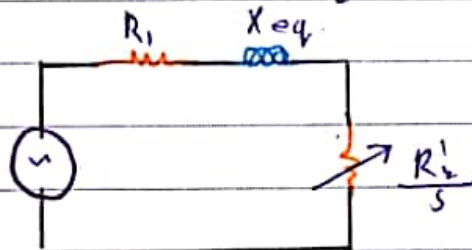
$$T_{dmax} = \frac{3V_1^2}{2\omega_s} \left[\frac{1}{R_1 + \sqrt{R_1^2 + X_{eq}^2}} \right]$$




③ IEEE model

$$R_{th} = (R_1 + jX_1) \parallel jX_m$$
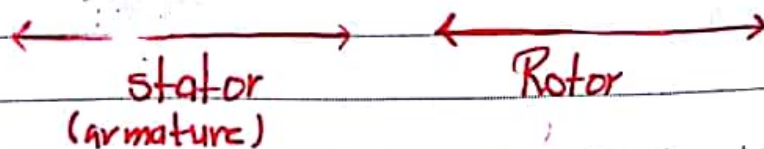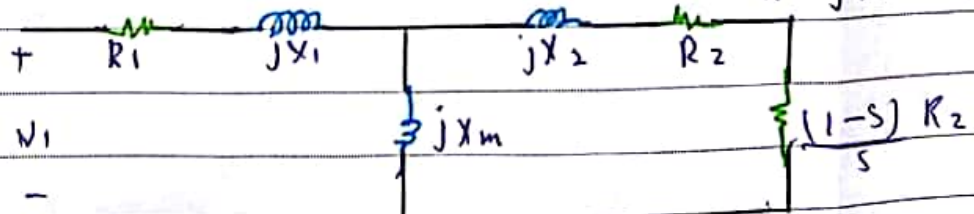
$$V_{th} = \frac{V_1 * jX_m}{R_1 + j(X_1 + X_m)}$$



No. _____

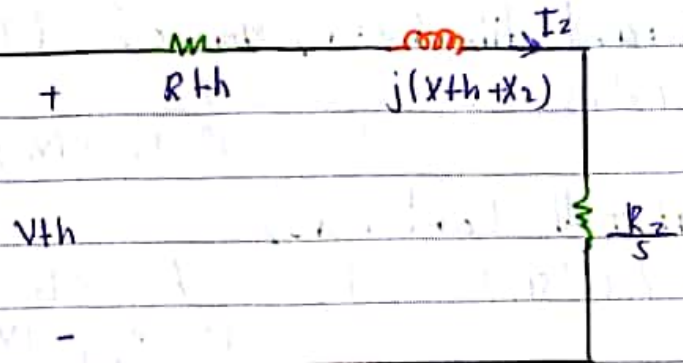

$$|I_2| = \frac{V_{th}}{\left(\frac{R_2}{s} + R_{th}\right)^2 + (x_{th} + x_2)^2}$$

* Tutorial (3): Induction motor

Q1: 100 hp, 60 Hz, 3 ϕ , IM, SFL = 0.03, $P_{Frxw} = 900$ W
 $P_{core} = 4200$ W $P_{cu} = 2700$ W

$$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{cu1} + P_{cu2} + P_{core} + P_{Frxw}}$$

$$P_d = P_{out} + P_{Frxw}$$

$$P_d = 74600 + 900 = 75500 \text{ watt}$$

$$P_{cu2} = S P_g = \frac{S P_d}{1-s} = 2.3 \text{ kWatt}$$

$$\eta = \frac{74600}{74600 + 2300 + 900 + 4200 + 2700} = 88\%$$

Q2: 3 ϕ , 480 V, 60 Hz, 12 pole, IM, $R_1 = 1 \Omega$, $R_2' = 0.5 \Omega$
 $X_{eq} = 10 \Omega$, $X_m = 100 \Omega$, $R_c = 800 \Omega$

$$S_{max} = \frac{R_2'}{\sqrt{R_1^2 + X_{eq}^2}} = \frac{0.5}{\sqrt{100+1}} = 0.05 = 5\%$$

$$n_{m_{max}} = (1 - S_{max}) n_s = 0.95 \times \frac{120 \times 60}{12} = 570 \text{ rpm}$$

$$I_{max} = \frac{V_l}{\sqrt{(R_1 + \frac{R_2'}{s_{max}})^2 + X_{eq}^2}} = 18.64 \text{ A}$$

$$T_{max} = \frac{3V_l^2}{2\omega_s(R_1 + \sqrt{R_1^2 + X_{eq}^2})} = 166.68 \text{ N}\cdot\text{m}$$

No. Sunday 13-8

Q.3: 3-ph: 30hp: 480 V: $p=4$: $f=60$ Hz: IM


$$R_1 = 0.25 \Omega \quad R_2 = 0.2 \Omega \quad X_1 = 1.3 \Omega \quad X_2 = 1.2 \Omega$$

$$X_m = 35 \Omega \quad P_{rot} = P_{F\&W} + P_{core} = 1250 \text{ W} = 1.25 \text{ kW}$$

$$V_{LL} = 440 \text{ V} \quad S = 3.5\% = 0.035$$

* Find: 1. n_m , $|I_1|$, PF

2. P_{in} , T_{out} , η

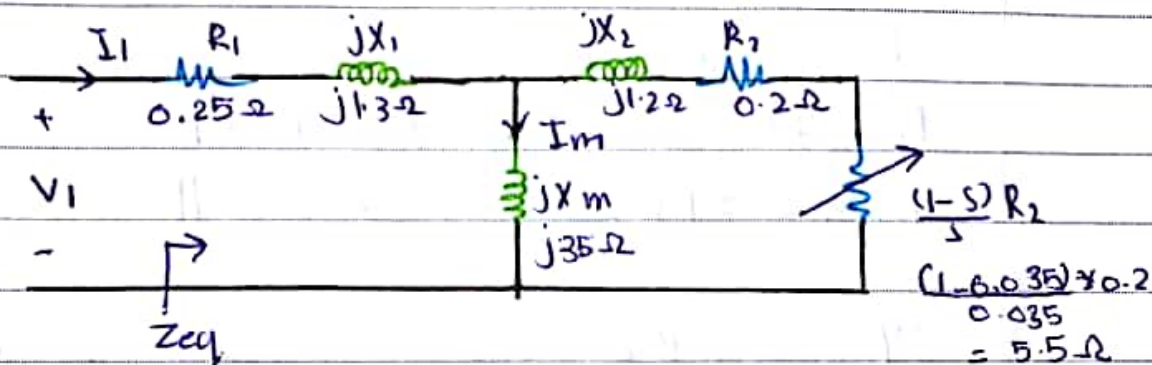


$$n_m = (1-s) * n_s$$

$$n_s = \frac{120f}{p} = \frac{12 * 60}{4} = 1800 \text{ rpm}$$

$$n_m = (1 - 0.035) * 1800 = 1737 \text{ rpm}$$


$$Z_{eq} = [(5.7 + j1.2) // j35] + 0.25 + j1.3$$

$$Z_{eq} \Big|_{s=0.035} = 6.35 \angle 31^\circ \Omega = 5.4 + j3.3 \Omega$$

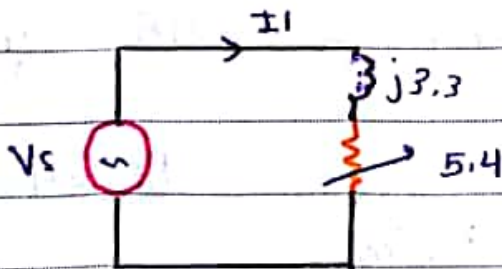

$$\vec{I}_1 = \frac{440 \sqrt{3}}{6.35 \angle 31} = 140 \angle -31^\circ$$
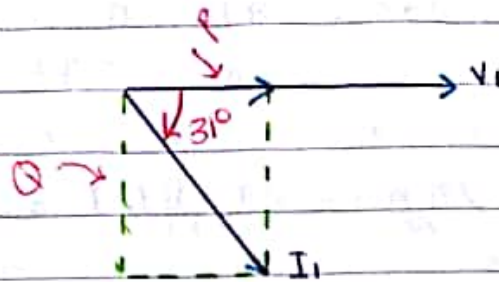
$$PF = \cos(31^\circ) = 0.858 \text{ Lag.}$$



$$P_{in} = \sqrt{3} V_L I_L \times PF = \sqrt{3} \times 440 \times 40 \times 0.858$$

$$= 3 V_L I_L \cos \theta$$

$$P_{in} = 26.1 \text{ kW}$$

$$I_{out} = \frac{P_{out}}{W_m}$$


$$P_{out} = P_{in} - \sum \text{losses}$$

$\begin{matrix} P \\ \swarrow \\ P_{Rct} \\ \searrow \\ P \end{matrix}$

$$P_{cu1} = 3 |I_1|^2 R_1 = 3 (40)^2 0.25 = 1200 \text{ W}$$

$$P_{cu2} = 3 |I_2|^2 R_2$$
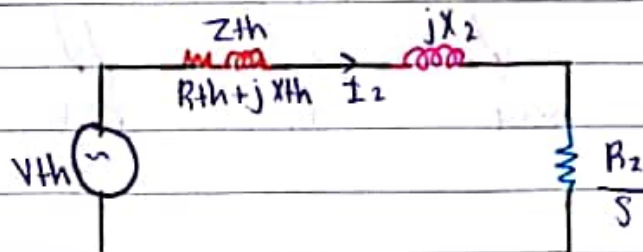
$$I_2 = I_1 \times \frac{jX_m}{R_2 + j(X_1 + X_2)} = 38.2 \angle -22^\circ \text{ A}$$



$$\vec{V}_{th} = \vec{V}_1 \times \frac{jX_m}{R_1 + j(X_1 + X_m)} = \frac{400/\sqrt{3} \times 35 \angle 90^\circ}{0.25 + j36.25} = 245.3 \angle 0.4^\circ \text{ V}$$

$$Z_{th} = jX_m \parallel (R_1 + jX_1) = 35 \angle 90^\circ \times (0.25 + j1.3)$$

$$= 1.7 \angle 46.5^\circ \Omega = 1.17 + j1.23$$

$$\vec{I}_2 = 33.6 \angle -19^\circ \text{ A}$$

$$P_{cu2} = 3(38.2) \times 0.2 = 875.5 \text{ W}$$

$$P_{out} = 26.1 \text{ kW} - 1.2 \text{ kW} - 0.755 \text{ kW} - 1.25 \text{ kW} \\ = 22.8 \text{ kW}$$


$$\omega_m = \frac{2\pi n_m}{60} = \frac{2\pi \times 1.737}{60} = 181.9 \text{ rps}$$

$$T_{out} = \frac{22.8 \times 10^3}{181.9} = 125.4 \text{ N.m}$$

$$T = \frac{P}{\omega} = \frac{P}{\frac{2\pi n}{60}} = \frac{60}{2\pi} \frac{P}{n} = 9.55 \frac{P}{n}$$

$$T = \frac{9.55 \times 22.8 \times 10^3}{1.737} = 125.4 \text{ N.m}$$
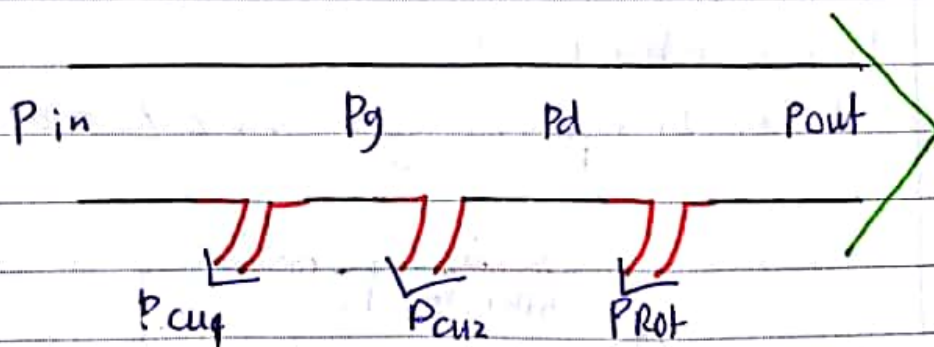
$$\eta = \frac{P_{out}}{P_{in}} = \frac{22.8}{26.1} \times 100\% = 87.3\% \\ s = 0.035$$



Q.4: 3-ph, $P=6$, $f=80$ Hz, $n_s=1200$ rpm

$$n_m = 1152 \text{ rpm}$$

$$P_{in} = 44 \text{ kW}, P_{rot} = 500 \text{ W}, P_{cu1} = 1600 \text{ W}$$

Find: a) slip, P_g , P_{cu2}

b) T_d , P_d (hp), T_{out} , P_{out} (hp)

$$S = \frac{n_s - n_m}{n_s} = \frac{1200 - 1152}{1200} \times 100 = 4\% = 0.04$$

$$a. P_g = P_{in} - P_{cu1} = 44 - 1.6 = 42.4 \text{ kW}$$

$$P_{cu2} = S P_g = 0.04 \times 42.4 = 1.7 \text{ kW}$$

$$b. T_d = \frac{P_g}{\omega_s} = \frac{P_d}{\omega_m} = 9.55 \frac{P}{n_s} = 9.55 \times \frac{42.4 \times 10^3}{1200}$$

$$= 337.4 \text{ N.m}$$

$$P_d = T_d \omega_m = (1 - S) P_g = (1 - 0.04) 42.4 \text{ kW}$$

$$= 40.7 \text{ kW}$$

$$P_d (\text{hp}) = \frac{40.7 \times 10^3}{746} = 54.6 \text{ hp.}$$

$$T_{out} = \frac{P_{out}}{\omega_m} = 9.55 \frac{P_{out}}{n_m}$$

$$P_{out} = P_d - P_{rot} = 40.7 - 0.5 = 40.2 \text{ kW}$$


$$T_{out} = 9.55 \times \frac{40.2}{1152} = 333.3 \text{ N.m}$$

$$P_{out} = \frac{40.2}{746} = 53.9 \text{ hp}$$

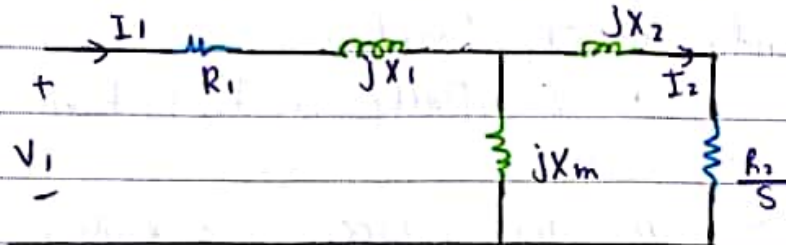
Q.5: 3-ph, 10hp, 230V $p=4$ $f=60\text{Hz}$ Y-connected

IM :- $S_{FL} = 4.5 (0.045)$

$R_1 = 0.35$, $X_1 = 0.5$, $X_2 = 0.5$, $X_m = 15$


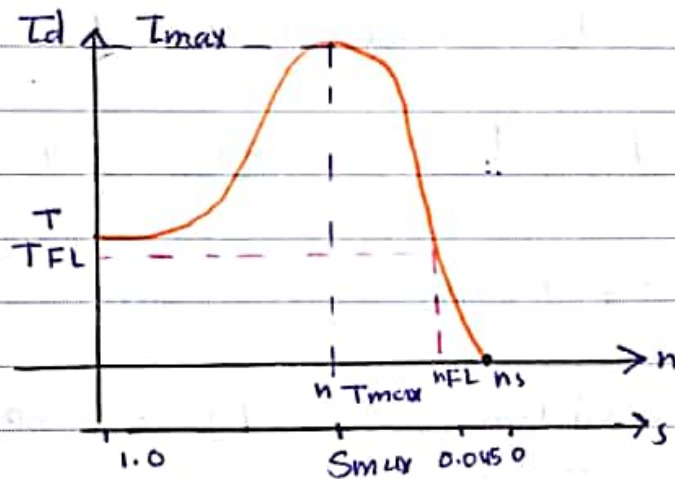
$$P_{rot} = 0 \rightarrow P_{cl} + P_{rot} = P_{out} \rightarrow P_{cl} = P_{out} = 10\text{hp}$$



$$T_{d(FL)} = \frac{3|V_1|^2}{\omega_s} \times \frac{R_2/s_{FL}}{\left(R_1 + \frac{R_2}{s_{FL}}\right)^2 + (X_1 + X_2)^2}$$

$$= \frac{3|V_1|^2}{\omega_s} \times \frac{R_2/s_{FL}}{\left(R_{th} + \frac{R_2}{s}\right)^2 + (X_1 + X_2)^2}$$

$$T_{d FL} = 9.55 \times \frac{P_{d FL}}{n_{FL}}$$

$$n_{FL} = (1 - S_{FL}) \cdot n_s$$

$$= (1 - 0.045) \times 1800$$

$$n_{FL} = 1719 \text{ rpm}$$

$$T_{dFL} = \frac{9.55 \times 10 \times 746}{1719} = 41.4 \text{ N.m.}$$

$$41.4 = \frac{3 \left(\frac{230}{\sqrt{3}}\right)^2}{188.5} \times \frac{R_2}{\left(0.35 + \frac{R_2}{0.045}\right)^2 + 1^2}$$

$$\rightarrow \text{solve for } R_2 \rightarrow R_2 = 0.265 \Omega$$

$$\text{OR } T_d \approx \frac{3|V|^2}{\omega_s} \times \frac{S}{R_2} \Rightarrow R_2 = 0.3 \Omega$$

$$T_{st} \Big|_{s=1} = \frac{3|V|^2}{\omega_s} \times \frac{R_2}{(R_1 + R_2)^2 + X_{eq}^2} = \frac{3 \times \left(\frac{230}{\sqrt{3}}\right)^2}{188.5} \times \frac{0.265}{(0.35 + 0.265)^2 + 1^2}$$

$$T_{st} = 53.9 \text{ N.m}$$

$$T_{max} = \frac{3|V|^2}{2\omega_s} \times \frac{1}{R_1 + \sqrt{R_2^2 + X_{eq}^2}} = \frac{3 \left(\frac{230}{\sqrt{3}}\right)^2}{2 \times 188.5} \times \frac{1}{0.35 + \sqrt{0.265^2 + 1^2}}$$

$$T_{max} = 99.6 \text{ N.m}$$

$$\eta T_{max} = (1 - S_{max}) \eta_s$$

$$S_{max} = \frac{R_2}{\sqrt{R_1^2 + X_{eq}^2}} = \frac{0.265}{\sqrt{0.35^2 + 1^2}} = 0.25 = 25\%$$


$$\eta T_{max} = (1 - 0.25) \times 1800 = 1350 \text{ rpm}$$

No. Monday 14-8

Q.6: 3-ph 20hp 440V $p=6$ $f=60\text{Hz}$ Y-connected
IM $T_{\text{start}} = 98 \text{ N.m}$ $T_{\text{FL}} = 72 \text{ N.m}$

a. $T_{\text{start}} \Big|_{V_{\text{LL}}=300\text{V}}$

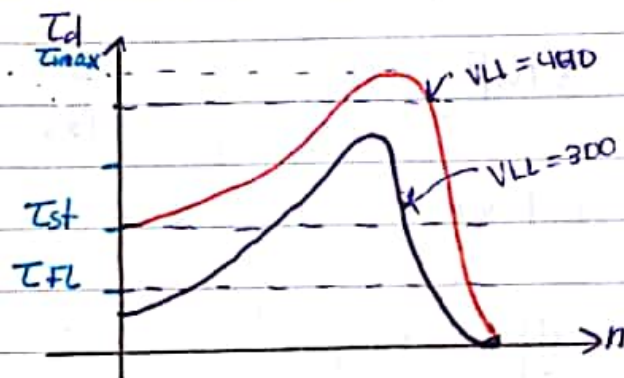b. $V_{\text{LL}} = ? \rightarrow T_{\text{start}} = T_{\text{FL}}$



$$T_d = \frac{3|V_{\text{LL}}|^2}{\omega_s} * \frac{R_2/s}{(R_1 + \frac{R_2}{s})^2 + X_{\text{eq}}^2}$$

at Starting $s=1$

$$T_{d\text{start}} = \frac{3|V_{\text{LL}}|^2}{\omega_s} * \frac{R_2}{(R_1 + R_2)^2 + X_{\text{eq}}^2}$$

at Full Load $s = s_{\text{FL}}$

$$T_{\text{FL}} = \frac{3|V_{\text{LL}}|^2}{\omega_s} * \frac{R_2/s_{\text{FL}}}{(R_1 + \frac{R_2}{s_{\text{FL}}})^2 + X_{\text{eq}}^2}$$

$$\frac{T_{\text{FL}}}{T_{\text{st2}}} = \left(\frac{V_1}{V_2}\right)^2$$

$$T_{\text{st2}} = T_{\text{st1}} * \left(\frac{V_2}{V_1}\right)^2 = 98 * \left(\frac{300}{440}\right)^2 = 45.6 \text{ N.m}$$

$$b. V_2 = \sqrt{\frac{T_{st2}}{T_{st1}}} * V_1$$

$$T_{st2} = T_{FL} = 72$$

$$T_{st1} = 98$$

$$V_2 = \sqrt{\frac{72}{98}} * 440$$

$$V_{2-L-L} = 377.1V$$

Q.7: 3-ph, 440V, 25 hp, 60 Hz, 1750-rpm ($n_s = 1800$ rpm)
 Y connected IM (wound-rotor \rightarrow WRIM) $f = 60$ Hz \downarrow $p = 4$

$$R_1 = 0.2 \Omega \quad R_2 = 0.15 \Omega \quad X_1 = 1 \Omega \quad X_2 = 0.8 \Omega$$


$$X_m = 30 \Omega \quad T_{st} = T_{max}$$

$$X_{eq} = X_1 + X_2$$

$$T_d(s) = \frac{3|V_1|^2}{\omega s} * \frac{R_2/s}{(R_1 + \frac{R_2}{s})^2 + X_{eq}^2}$$

at starting $s=1$

$$T_{st} = \frac{3|V_1|^2}{\omega s} * \frac{R_2'}{(R_1 + R_2 + R_{ext})^2 + X_{eq}^2}$$

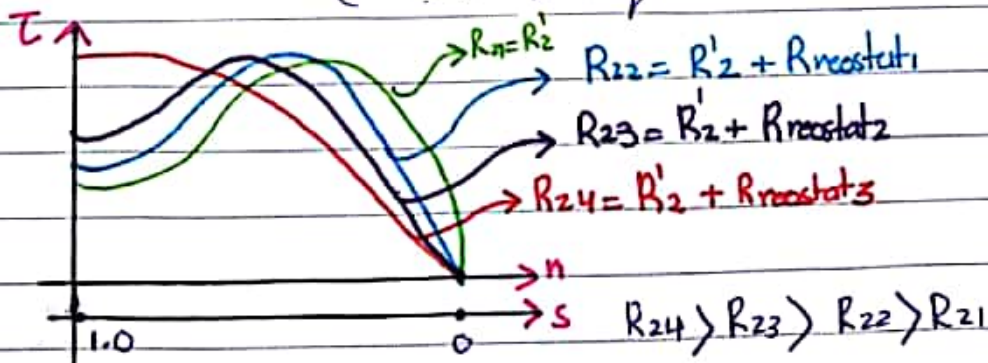

$$T_{max} = \frac{3|V_1|^2}{2\omega s} * \frac{1}{R_1 + \sqrt{R_1^2 + X_{eq}^2}}$$

No. _____


$T_{start} = T_{max}$
at starting $S=1$
at $T_{max} = S_{max}$

$$\frac{R_2 + R_{rostat}}{S_{max}} = \sqrt{R_1^2 + X_{eq}^2}$$


$$\frac{0.15 + R_{rostat}}{1.0} = \sqrt{0.2^2 + 1.8^2}$$

$$R_{rostat} = \sqrt{0.2^2 + 1.8^2} - 0.15 = 1.66 \Omega$$


* Parameter Calculations of I-M

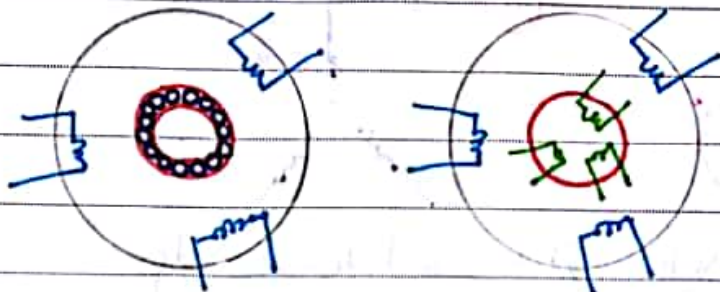


Consider the approximate equivalent ckt

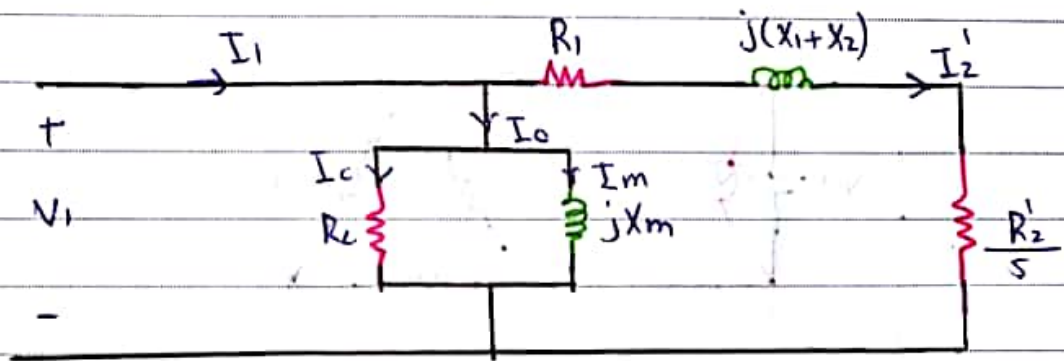



$R_1 =$ Armature winding resistance

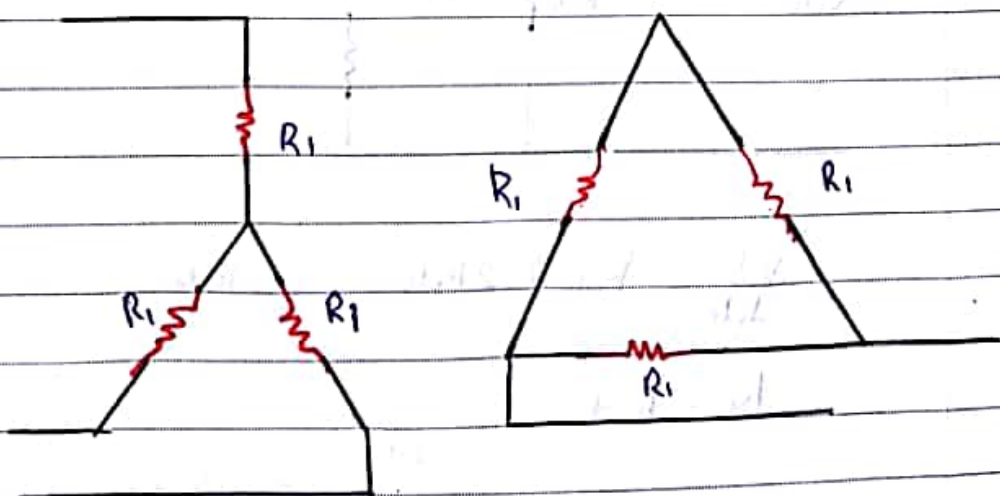

II] DC Resistance test

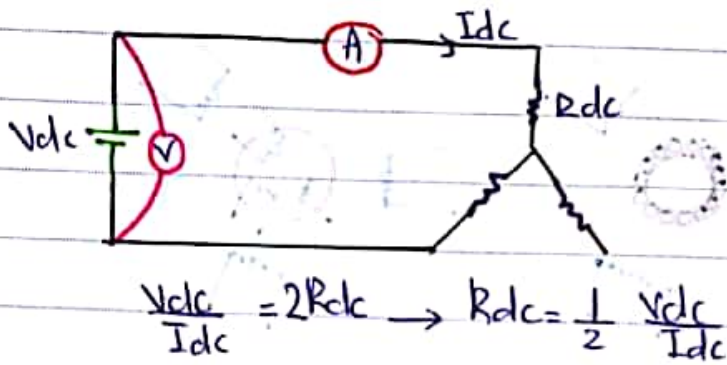


$$R_1 = R_{dc}$$

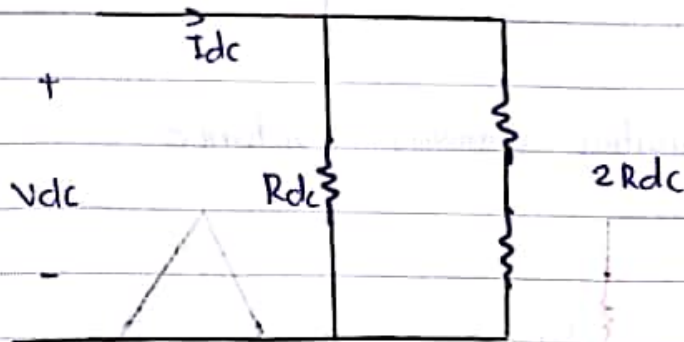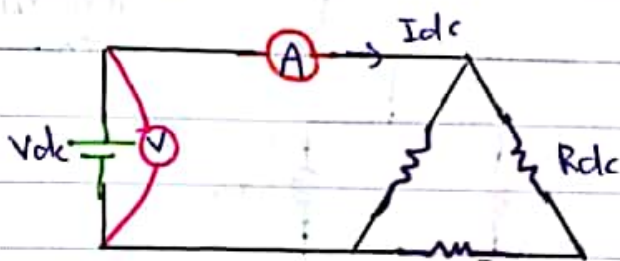

$$\frac{V_{dc}}{I_{dc}} = R_{dc} \parallel 2R_{dc} = \frac{2}{3} R_{dc}$$

$$R_1 = R_{dc} = \frac{3}{2} \frac{V_{dc}}{I_{dc}}$$

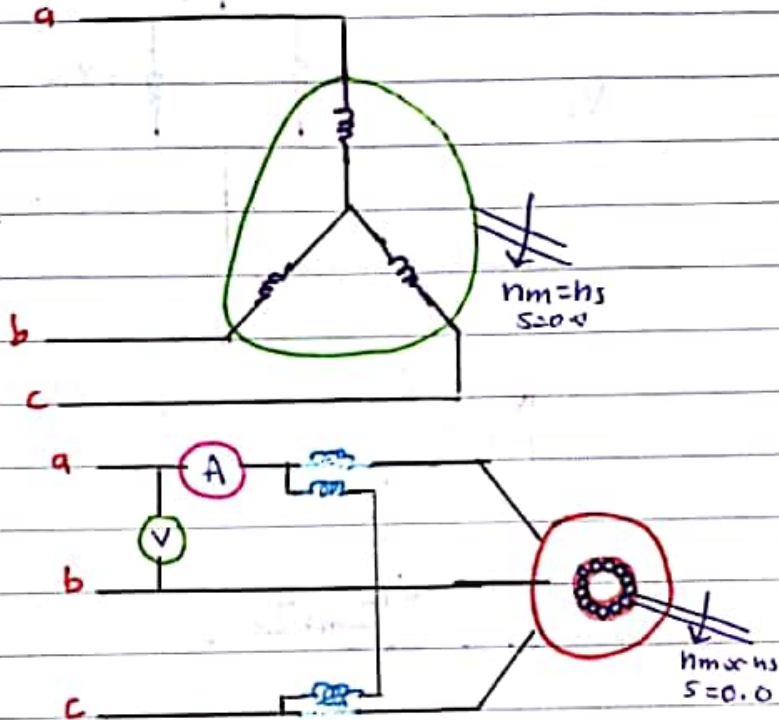② No-Load Test $n_m \times n_s \rightarrow S=0.0$



$$P_{in} = W_1 + W_2$$

$$I = I_m \sin \theta_m$$

$$I_c = I_m \cos \theta_m$$

$$X_m = \frac{V_m / \phi_m}{I_m} = \frac{V_m \phi_m}{I_m \sin \theta_m}$$

$$R_c = \frac{V_m}{I_m \cos \theta_m}$$

$$P_{in} = P_{rot} + P_{core}$$

assume that P_{rot} is known.



$$P_{core} = P_{in} - P_{rot} \rightarrow P_{core} = 3 \frac{V_m^2}{R_c}$$

$$P = 3 V_m I_m \cos \theta_m$$

$$R_c = \frac{3 V_m^2}{P_{core}}$$



$$\cos \theta_m = \frac{P_{in}}{3 V_m I_m} \rightarrow PF_{in}$$

* Equivalent Circuit (no-Load)

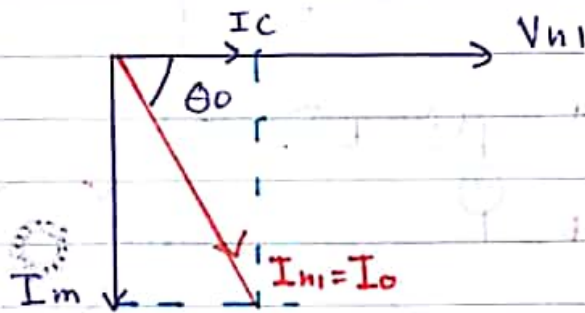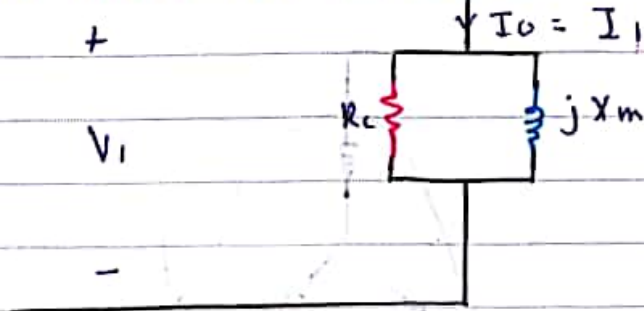

[3] Blocked rotor test

$n_m = 0$ $S = 1$

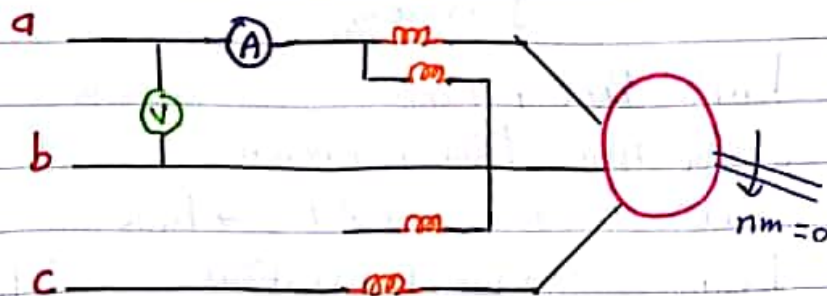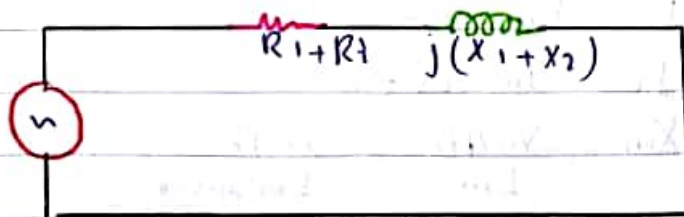


$$Z_{BI} = \sqrt{R_{eq}^2 + X_{eq}^2} = \frac{V_{BI}}{I_{BI}}$$

$$P_{BI} = 3(I_{BI})^2 R_{eq}$$

$$R_{eq} = \frac{P_B}{3(I_{BI})^2} = R_1 + R_2'$$

$$X_{BI} = \sqrt{Z_{BI}^2 - R_{BI}^2} = X_{eq} = X_1 + X_2$$

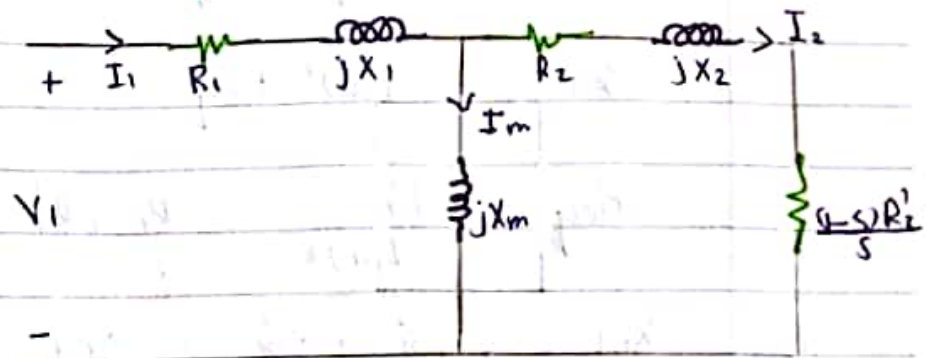* Induction motor parameter calculations of IEEE model:-



① DC Resistance test:

$$R_1 = \frac{1}{2} \frac{V_{dc}}{I_{dc}} \text{ for } \gamma \text{ connected armature}$$



$$R_1 = \frac{3}{2} \frac{V_{dc}}{I_{dc}} \text{ for } \Delta \text{ connected armature}$$

② no-Load test:

$$n_m \approx n_s \rightarrow s = 0.0$$

$$V_{OC} = V_{LL} \text{ rated}$$

$$P_{n1} = w_1 + w_2$$

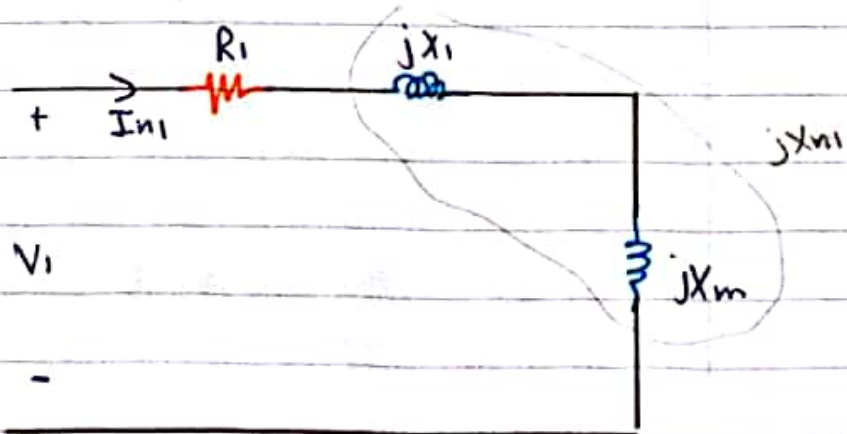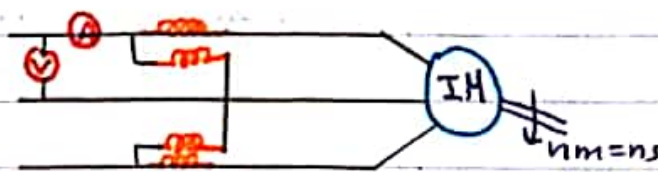

$$P_{in} = 3 |I_{in}|^2 R_1 + P_{rot}$$

$$P_{rot} = P_{in} - 3 |I_{in}|^2 R_1$$



$$|Z_{in}| = \frac{V_{in} \text{ ph}}{I_{in} \text{ ph}} = \sqrt{R_{in}^2 + X_{in}^2}$$

$$R_{in} = \frac{P_{in}}{3 |I_{in}|^2}, \quad X_{in} = X_1 + X_m = \sqrt{Z_{in}^2 - R_{in}^2}$$

③ Blocked Rotor test:

$$n_m = 0.0 \rightarrow s = 1$$

$$|I_B| = I_{rated}$$

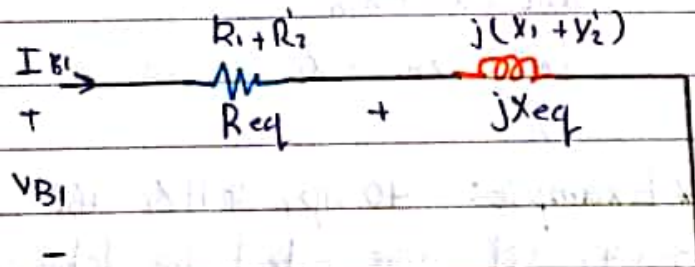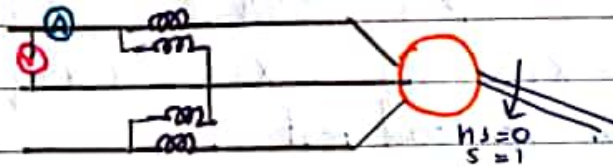

By standard

$$f_{test} = \frac{1}{4} f_{rated}$$

$$X_{eq} \Big|_{f_{test}} = \frac{1}{4} X_{eq} \Big|_{f_{rated}} \rightarrow X_{eq} \Big|_{f_{rated}} = 4 X_{eq} \Big|_{f_{test}}$$

$$P_{B1} = \omega_1 + \omega_2 = 3 |I_{B1}|^2 R_{eq}$$

$$R_{eq} = \frac{P_{B1} \text{ 3ph}}{3 |I_{B1}|^2} = R_1 + R_2' \rightarrow R_2' = R_{eq} - R_1$$

$$|Z_{BL}| = V_{BLph} / I_{BLph} = \sqrt{R_{eq}^2 + X_{eq, test}^2}$$

$$X_{eq, test} = \sqrt{Z_{BL}^2 - R_{eq}^2}$$

$$X_{eq, rated} = \left(\frac{I_{rated}}{I_{test}} \right) X_{eq, test}$$

	A/D	B	C	WRM
X_1	$0.5 X_{eq}$	$0.4 X_{eq}$	$0.3 X_{eq}$	$0.5 X_{eq}$
X_2'	$0.5 X_{eq}$	$0.6 X_{eq}$	$0.7 X_{eq}$	$0.5 X_{eq}$

$$X_1 = X_2 = \frac{X_{eq}}{2} \quad X_1 = 0.4 X_{eq} \quad X_2 = 0.6 X_{eq}$$

→ from no-load test

$$X_{NL} = X_1 + X_m$$

$$X_m = X_{NL} - X_1$$

* Example:- 40 hp, 60 Hz, 460 V, Y-connected, Design B 3-ph, IM was tested to determine its parameter. The DC, no load and Blocked rotor test the results are given below:

The Blocked rotor test was at $f_{test} = 15 \text{ Hz}$ ($\frac{1}{4}$ of rated). Find the parameters R_1 , R_2' , X_1 , X_2' , X_m and P_{rot}

	Blocked rotor test	No load test	DC Test
V_{BI}	36.2 V	V_{NL} 460 V	$V_{DC} = 12 \text{ V}$
I_{BI}	58 A	I_{NL} 32.7 A	$I_{DC} = 59 \text{ A}$
P_{BI}	2573.4 W	P_{NL} 4664.4 W	

*** DC Test**

$$R_1 = \frac{1}{2} \frac{V_{dc}}{I_{dc}} = \frac{1}{2} \times \frac{12}{54} = 0.102 \Omega/\text{ph}$$


*** Blocked Rotor Test**

$$|Z_{B1}| = \frac{V_{B1}}{I_{B1}} = \frac{36.2/\sqrt{3}}{58} = 0.360 \Omega/\text{ph}$$

$$R_{eq} = \frac{P_{B1}}{3 |I_{B1}|^2} = \frac{2573.4}{3 \times 58^2} = 0.255 \Omega/\text{ph}$$

$$R_{eq} = R_1 + R_2' = 0.255 \Omega/\text{ph}$$
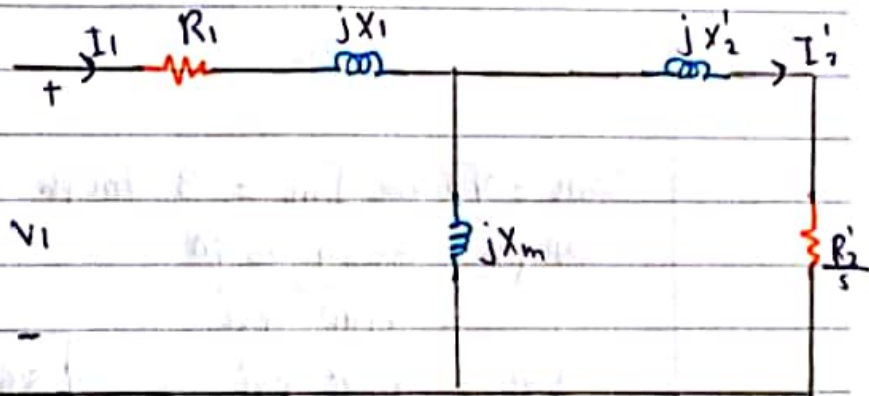
$$R_2' = 0.255 - 0.102 = 0.153 \Omega/\text{ph}$$



$$X_{eq_{\text{test}}} = \sqrt{Z_{eq}^2 - R_{eq}^2} = \sqrt{(0.36)^2 - (0.255)^2} = 0.2545 \Omega/\text{ph}$$


$$X_{eq} \Big|_{f_{\text{rated}}} = \frac{f_{\text{rated}}}{f_{\text{test}}} \times X_{eq_{\text{test}}} = \frac{60}{15} \times 0.2545$$

$$X_{eq} = X_1 + X_2 = 1.018 \Omega/\text{ph}$$


For Class B-III

$$X_1 = 0.4 X_{eq} = 0.4 \times 1.018 = 0.4073 \Omega/\text{ph}$$
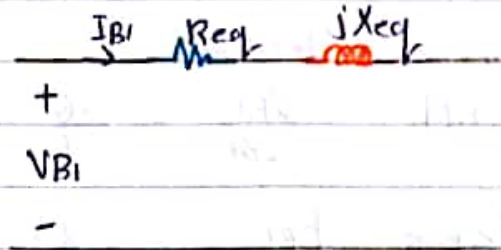
$$X_2 = 0.6 X_{eq} = 0.6 \times 1.018 = 0.6109 \Omega/\text{ph}$$



* NO-load test:

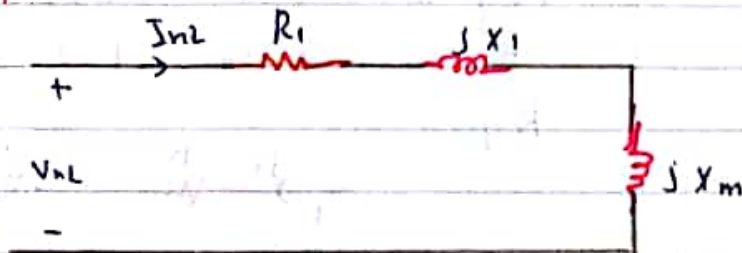

$$S_{NL} = \sqrt{3} V_{NL} I_{NL} = 3 V_{NL\text{ph}} I_{NL\text{ph}} = \sqrt{3} \times 460 \times 32.7$$

$$S_{NL\text{ph}} = 8684.5 \text{ VA}$$

$$= \sqrt{P_{NL}^2 + Q_{NL}^2}$$

$$Q_{NL\text{ph}} = \sqrt{S_{NL}^2 - P_{NL}^2} = \sqrt{8684.5^2 - \left(\frac{4664.4}{3}\right)^2}$$

$$Q_{NL\text{ph}} = 8544.2 \text{ VAR}$$


$$= 3 I_{NL}^2 X_{NL}$$

$$X_{NL} = \frac{8544.2}{3 \times (32.7)^2}$$


$$X_{eq} = X_1 + X_2 = 7.99 \Omega$$

$$X_m = X_{NL} - X_1 = 8 - 0.4073$$

$$X_m = 7.58 \Omega$$

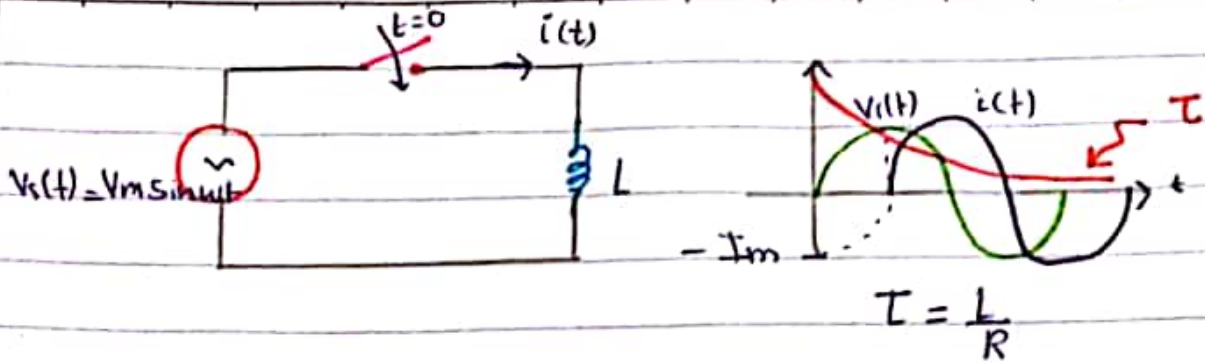

* Starting of IM:

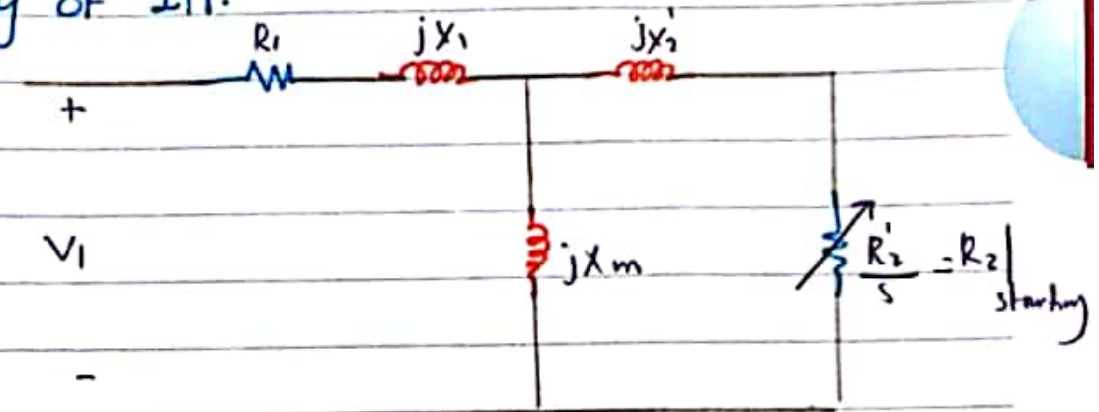

at starting $s=1$



$$Z_{eq}(s=1) = R_1 + jX_1 + jX_m \parallel (R_2 + jX_2') \rightarrow \text{very small}$$

$$I_{s \text{ starting}} = \frac{V_1}{Z_{eq}(s=1)}$$

* Techniques for reducing starting current:-

1. Insert Resistance in Series with the armature or rotor circuit if possible. $I_{s \text{ starting}} = R_{eq} + Z_{eq}$
2. Reduced voltage starting by using autotransformer
By using γ - Δ switch.


No. Thursday 17-8

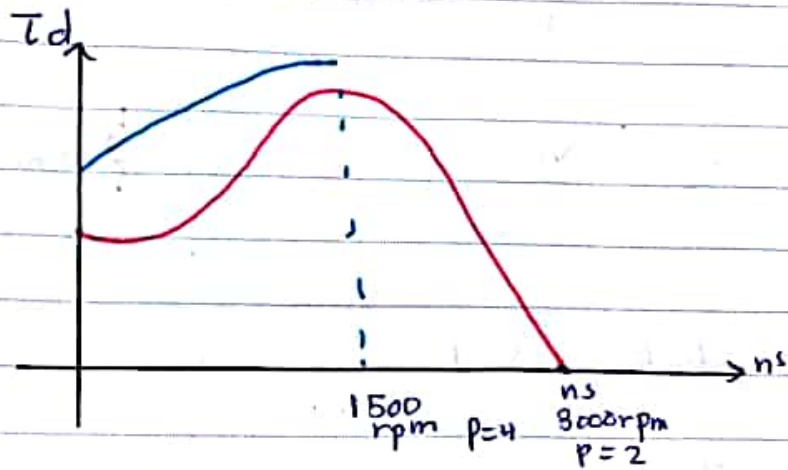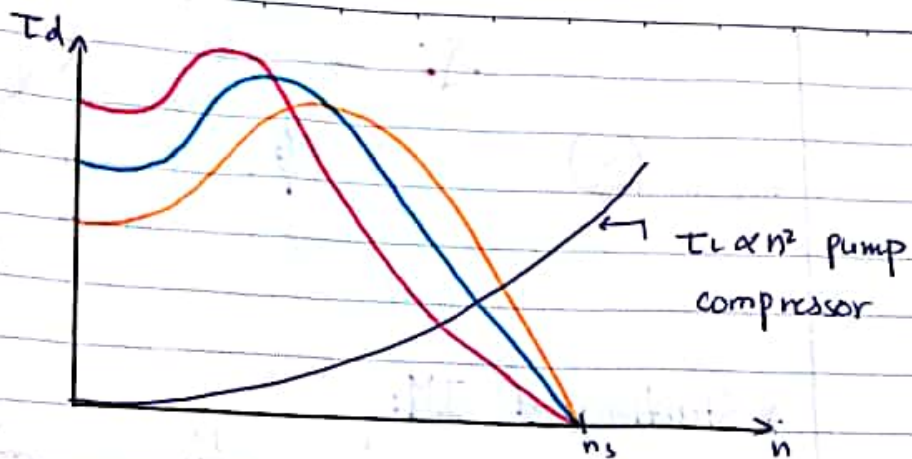

$$\textcircled{1} T_d = \frac{3V_t^2}{\omega_s} \left[\frac{R_2^2/s}{(R_1 + R_2/s)^2 + X_{eq}^2} \right]$$


when p is increased then n_s decreased,
 then $\omega_s = \frac{2\pi n_s}{60}$ is decreased the T_d increased.
 $T_d \propto P$

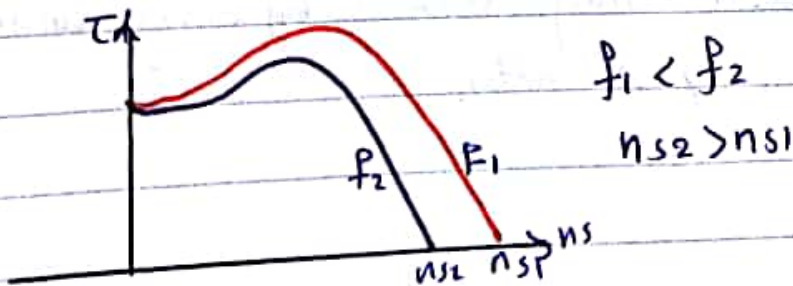$\textcircled{2}$ when we increased f then n_s increased \rightarrow
 $\omega_s = \frac{2\pi n_s}{60}$ increased then $T_d \Rightarrow$ decreased





To keep ϕ constant if f is reduced then V is derated

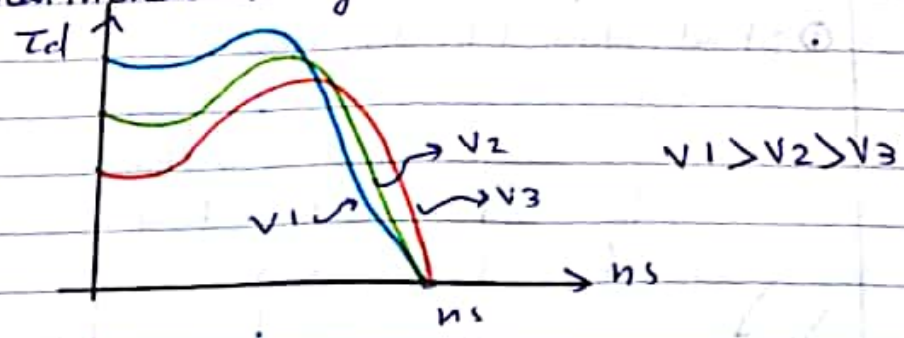③ When increase voltage then T_{ed} increase.



* Induction motor starting:-

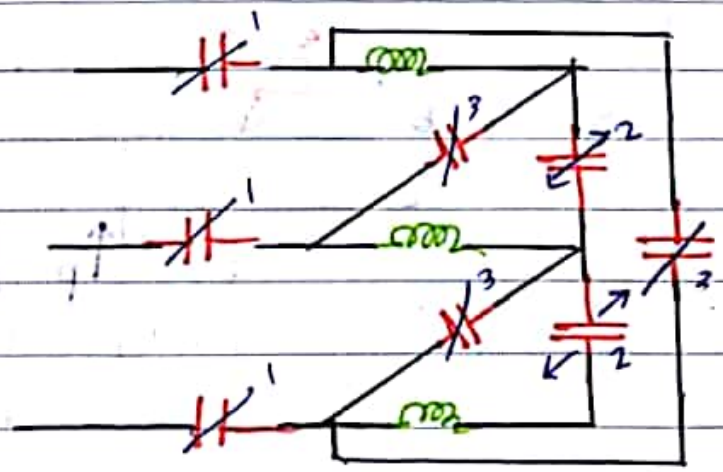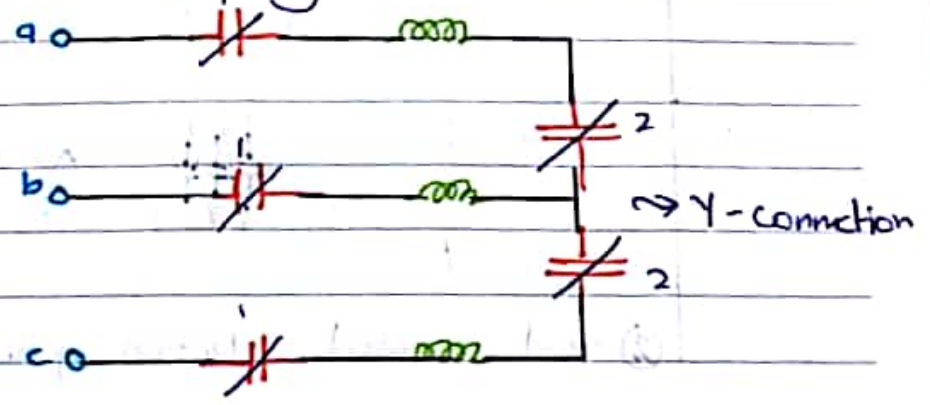


Δ - Connection

No. Sunday 20-8


Induction Generator Induction motor running at a


* Modes of operation:

① Stand alone (Isolated generator)

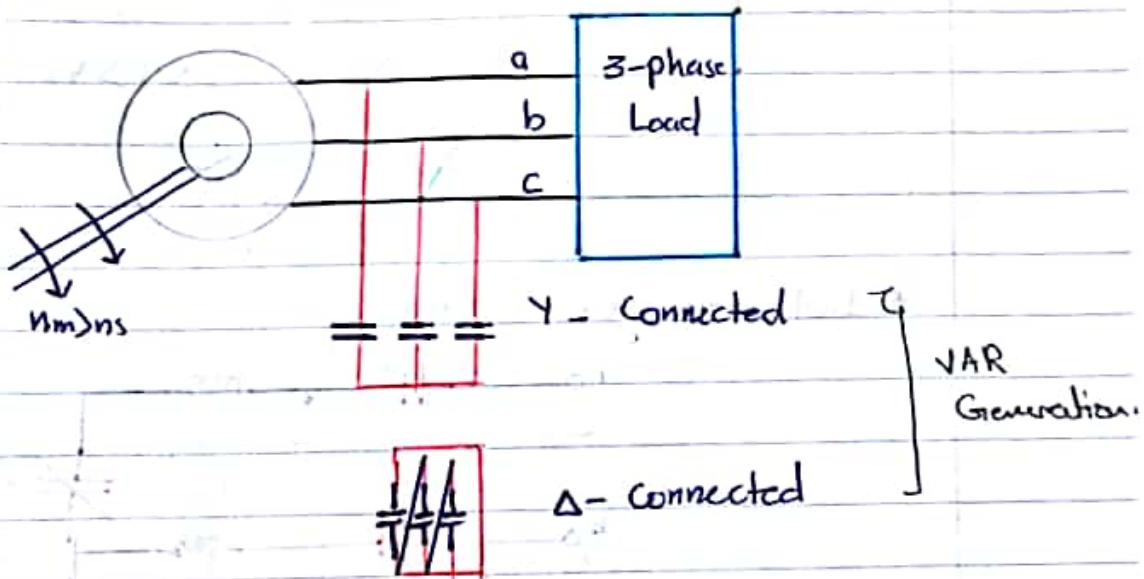

② Grid connected induction generator

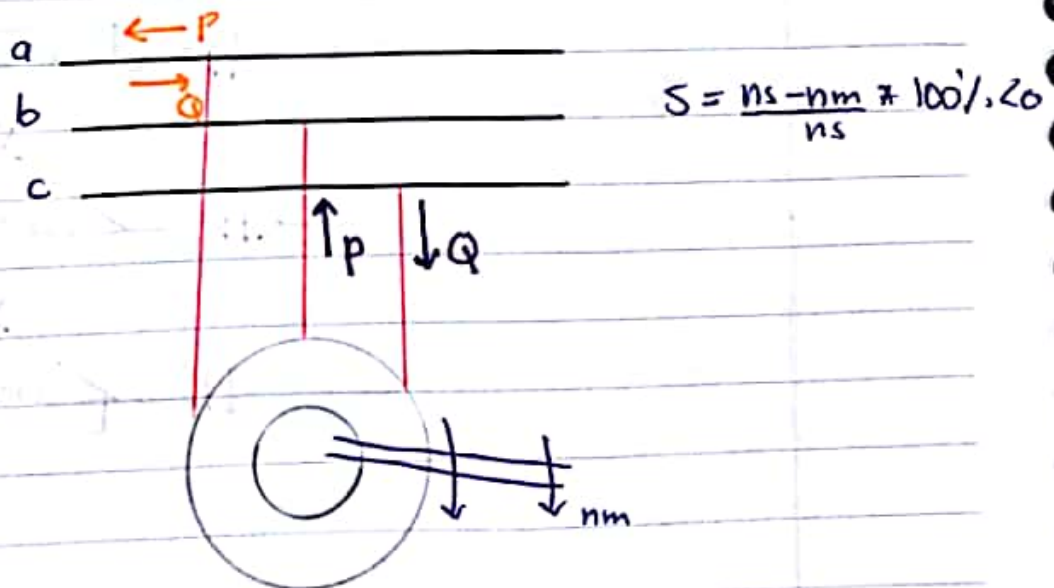

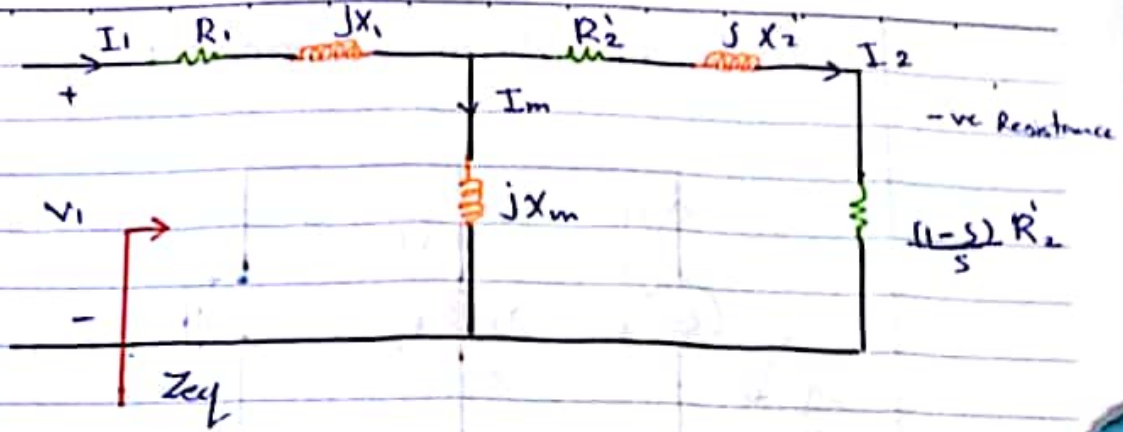

$$Z_{eq}(s) = R_1 + jX_1 + (jX_m \parallel \frac{R_2'}{s} + jX_2')$$

$$\bar{I}_1 = \frac{\bar{V}_1}{Z_{eq}(s)} = |I_1| \angle \theta_1$$

$$P_{in} = 3|V_1||I_1| \cos \theta_1$$

-ve power

$$P_g = 3|I_1|^2 \frac{R_2'}{s}$$

= $T_e \cdot \omega_s$

$$P_d = 3|I_2|^2 R_2' (1-s)$$

= $T_d \cdot \omega_m$

$$P_{out} = T_{out} \cdot \omega_m$$

= $T_{mech} \cdot \omega_m$

$$P_{Cu1} = 3|I_1|^2 R_1$$


$$P_{Cu2} = 3|I_2|^2 R_2$$

$$P_{rot}$$



$$n_m > n_s$$

$$s = \frac{n_s - n_m}{n_s} < 0$$

Recall DC shunt Generator:-

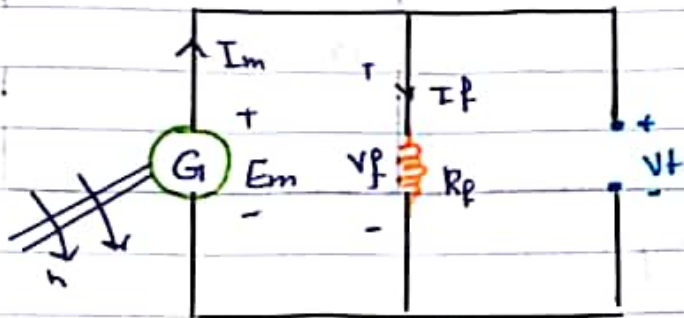



$$E_m = k_a \Phi \cdot \omega$$

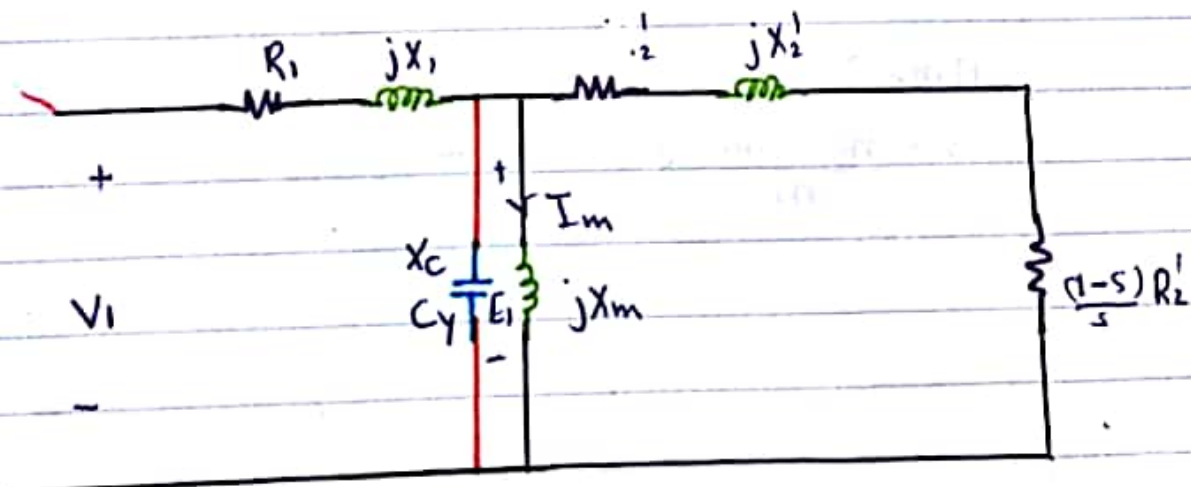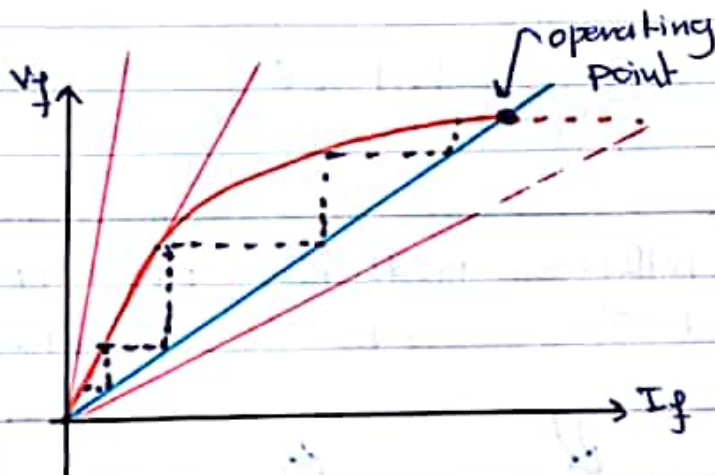

Capacitor bank to produce VAR.

$$\begin{aligned} Q &= \omega C_y V^2 = I_C^2 X_C = \left(\frac{V}{X_C}\right)^2 X_C = \frac{V_C^2}{X_C} = \\ &= \frac{V_C^2}{\frac{1}{\omega C}} = \omega C V_C^2 \end{aligned}$$

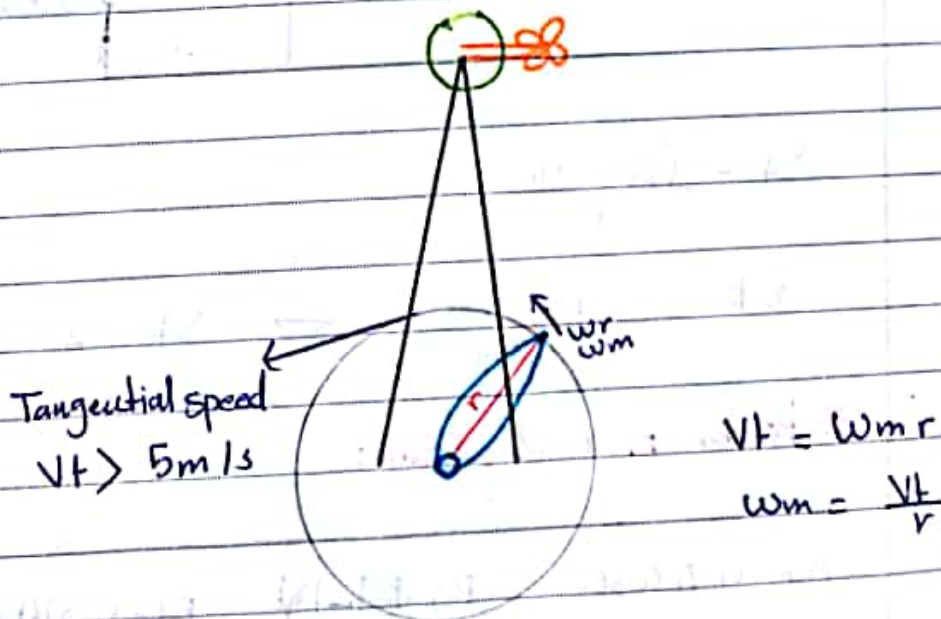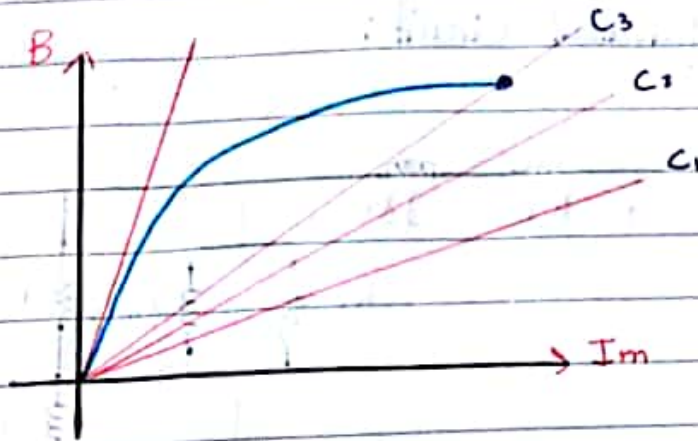
$$Q_{c\text{ sph}} = 3\omega C_y V_{cph}^2$$



No Monday 21-8

- Types of IM →
- ① split-phase
 - ② Capacitor start
 - ③ capacitor
 - ④ Capacitor start-Run

* Equivalent Circuit :-

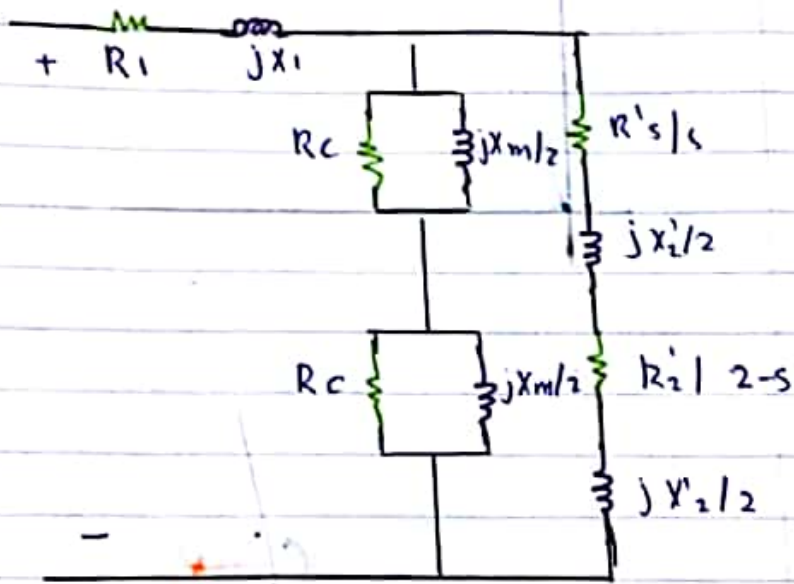

$$SF = \frac{n_s - n_m}{n_s}$$




$$sb = \frac{-n_s - n_m}{-n_s} \rightarrow SF = 2 - sb$$

* Power Flow diagram :-

$$P_{in} = V_1 I_1 \cos \theta \quad P_g = P_g^p - P_{gb} \quad P_d = (1-s)(P_g^p - P_{gb}) \quad P_{out}$$

$$P_{Cu1} = I_1^2 R_1 \quad P_{Cu2} = s P_g^p + (2-s) P_{gb} \quad P_{rot}$$

No. _____

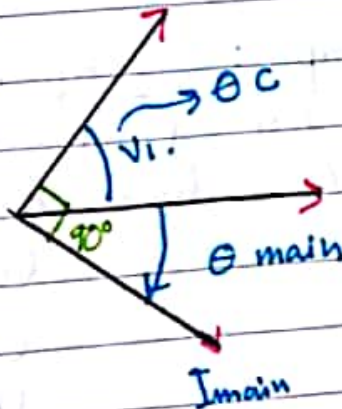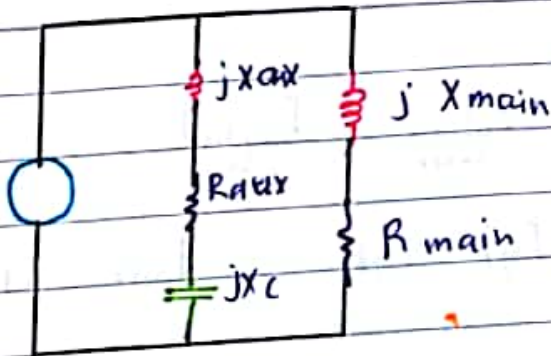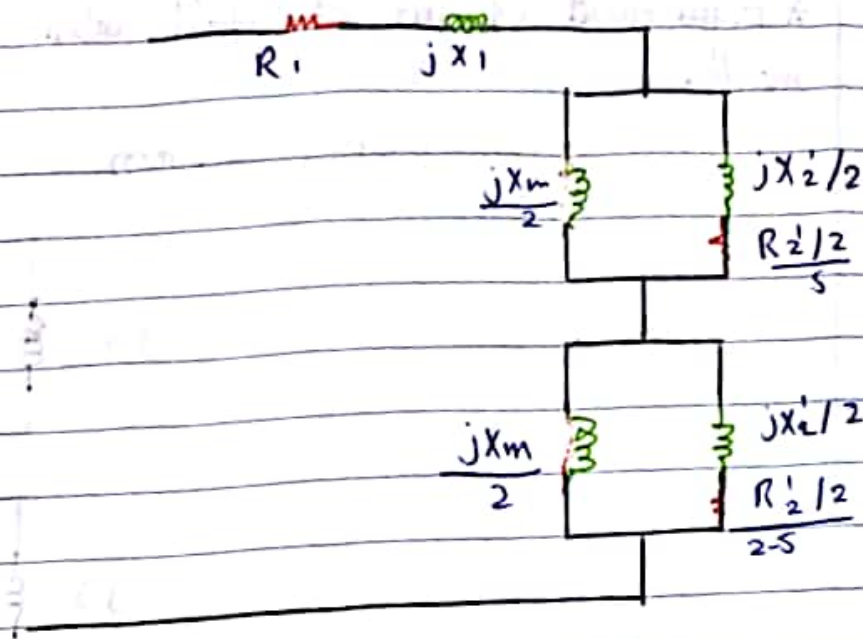


$$\theta_{main} = \tan^{-1}\left(\frac{X}{R}\right)$$

$$\phi_c = 90 - \theta_{main}$$

No Tuesday 22-8

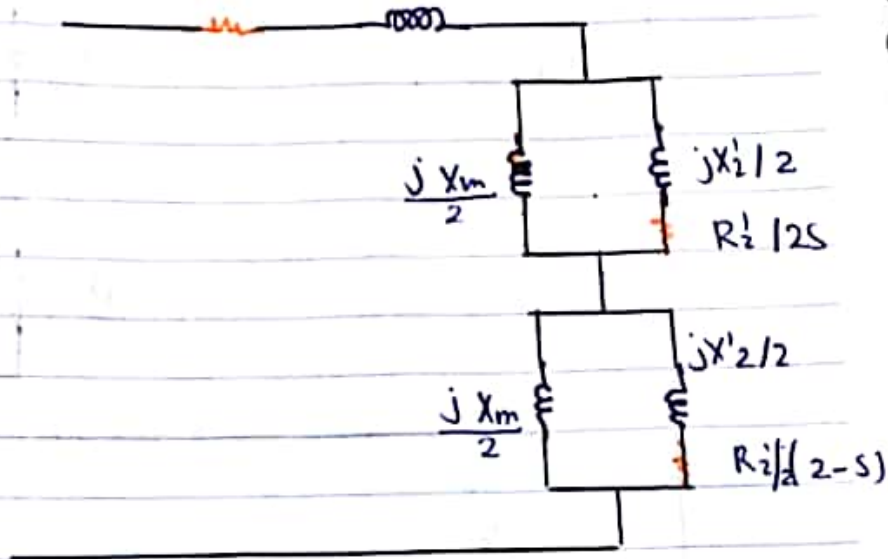* Equivalent Circuit of I.M while the running mode.




$$T_{dnet} = \frac{P_{dnet}}{\omega_m} = \frac{P_{gnet}}{\omega_s}$$

$$P_{gnet} = P_{gf} - P_{gb} \quad P_{cu2} = s P_{gf} + (2-s) P_{gb}$$

$$SF = \frac{n_s - n_m}{n_s} \times 100\% \quad s_b = \frac{n_s - n_m}{-n_s} \times 100\% \quad s_b = 2 - sf$$

* Example:- $\frac{1}{2}$ hp, 110V, 60Hz, P=6, split phase I.M
 $P_{core} = 35$ watt, $P_{Fwx} = 16$ watt
 $s = 5\%$, find:

- | | |
|--------------|---------------|
| (a) n_m | (f) p_d |
| (b) I_1 | (g) T_d |
| (c) PF (Lag) | (h) P_{out} |
| (d) p_{in} | (i) T_{out} |
| (e) p_g | (j) η |

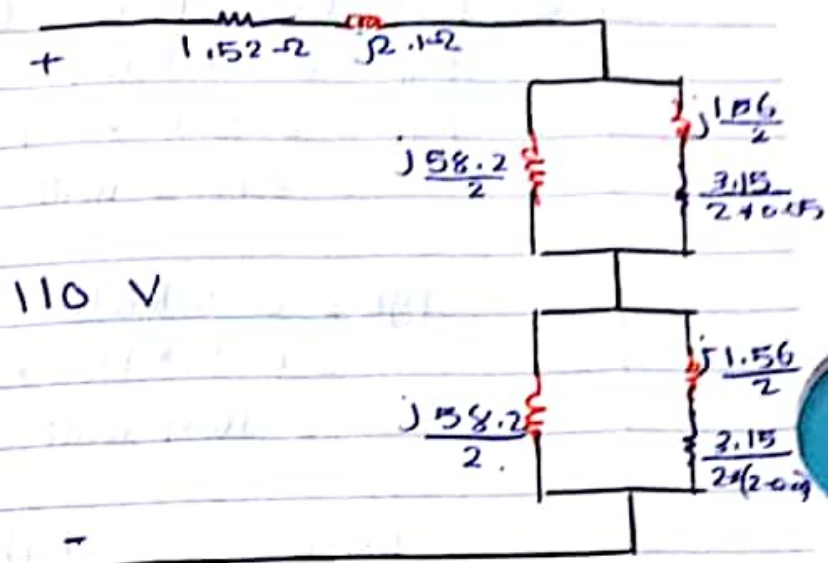

$$\textcircled{a} \quad n_m = (1-s) n_s \rightarrow n_m = (1-0.05) * 1200 = 1140 \text{ rpm}$$

$$\textcircled{b} \quad \vec{I}_1 = \frac{V_1}{R_1 + jX_1 + \frac{Z_f}{2} + \frac{Z_b}{2}} =$$

$$Z_f = jX_m \parallel (R_2' + jX_2')$$

$$Z_b = jX_m \parallel \left(\frac{R_1'}{2-s} + jX_2' \right)$$

$$Z_f = 25.4 + j30.7 = R_f + jX_f$$

$$Z_b = 1.51 + j1.56 = R_b + jX_b$$

$$\vec{I}_1 = \frac{110 \angle 0}{1.52 + j2.1 + \frac{Z_f}{2} + \frac{Z_b}{2}} = \frac{110 \angle 0}{23.6 \angle 50.6^\circ}$$

$$= 4.66 \angle -50.6^\circ \text{ A}$$

$$\textcircled{c} \quad \text{pf} = \cos(50.6^\circ) = 0.635 \text{ Lag.}$$

$$\textcircled{d} \quad P_{in} = V I_1 \cos \theta = 110 * 4.66 * 0.635 = 325 \text{ watt.}$$

No. _____

$$\textcircled{e} P_{in} - P_{cu1} - P_{core} = P_g$$

$$P_{gf} = 0.5 R_f |I_1|^2$$

$$P_{gf} = 0.5 \times 25.4 \times 4.66^2 \\ = 275.8 \text{ watt}$$

$$P_{gb} = 0.5 R_b |I_1|^2$$

$$= 0.5 \times 1.51 \times (4.66)^2$$

$$= 16.4 \text{ watt}$$

$$P_{g \text{ net}} = P_{gf} - P_{gb} = 259.4 \text{ watt}$$

$$\textcircled{f} P_d = (1-s) P_{g \text{ net}} \rightarrow 246 \text{ watt}$$

$$\textcircled{g} T_d = \frac{246}{2\pi \times \frac{1140}{60}} = 2.06 \text{ N.m}$$

$$\textcircled{h} P_{out} = P_d - P_{rot}$$


$$= 246 - 35 - 16 = 195 \text{ watt}$$

$$\textcircled{i} T_{out} = \frac{P_{out}}{\omega_m} = \frac{195}{2\pi \times \frac{1140}{60}} = 1.63 \text{ N.m}$$

$$\textcircled{j} \eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{195}{325} \times 100\% = 60\%$$

* Parameter Calculations of Single Phase Induction Motor :-

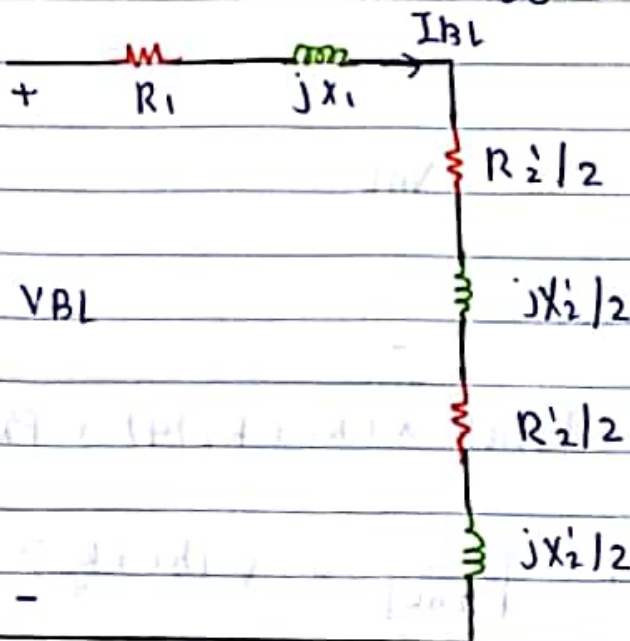II Blocked Rotor test: $n_m = 0$ $s_f = 1$
 $s_b = 2 - s_f = 1$



$$|Z_{BL}| = \left| \frac{V_{BL}}{I_{BL}} \right| = \sqrt{(R_1 + R'_2)^2 + (X_1 + X'_2)^2}$$

$$P_{BL} = |I_{BL}|^2 \times (R_1 + R'_2)$$


$$X_1 = X'_2 = \frac{X_{BL}}{2} \rightarrow X_{BL} = \sqrt{Z_{BL}^2 - (R_1 + R'_2)^2}$$

R_1 is known with DC Resistance test

$$R'_2 = \frac{P_{BL}}{I_{BL}} - R_1$$

No.

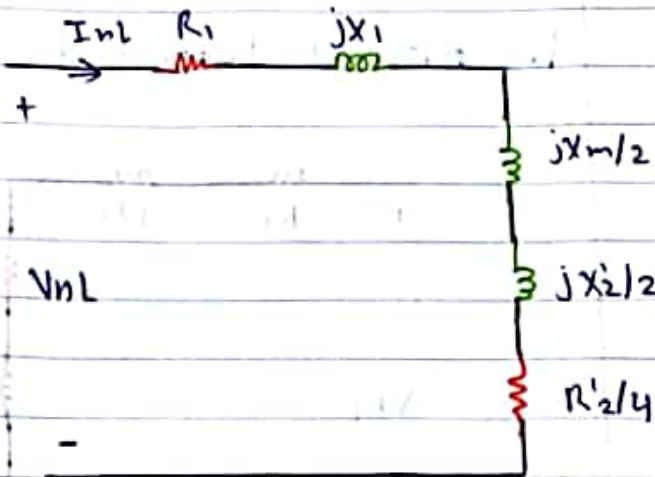2] no-load test $n_m \approx n_s$
 $sf = 0 \rightarrow sb = 2$



$$P_{nL} = |I_{nL}|^2 * (R_1 + R'_2/4) + P_{rot}$$

$$|Z_{nL}| = \frac{|V_{nL}|}{|I_{nL}|} = \sqrt{(R_1 + \frac{R'_2}{4})^2 + (X + \frac{X'_2}{2} + \frac{X_m}{2})^2}$$


* Solve for X_m .

* Example:- 0.5hp, 110V, 950rpm, 50Hz
6 poles, tested for parameter calculation:-
given $R_1 = 18 \Omega$, blocked Rotor \rightarrow

$V_{BL} = 36 \text{ volt}$, $I_{BL} = 5 \text{ A}$, $P_{BL} = 100 \text{ watt}$

No-load $\rightarrow V_{nL} = 110 \text{ V}$, $I_{nL} = 4 \text{ A}$, $P_{nL} = 90 \text{ w}$.

① Blocked Rotor

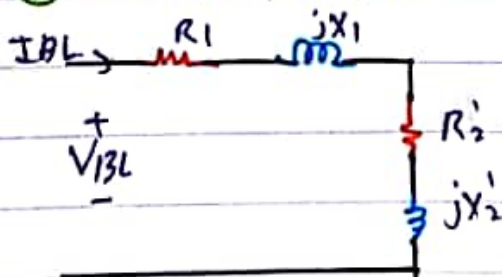

$$|Z_{BL}| = \frac{|V_{BL}|}{|I_{BL}|} = \frac{36}{5} = \sqrt{(R_1 + R_2')^2 + (X_1 + X_2)^2}$$


$$R_1 + R_2' = \frac{P_{BL}}{|I_{BL}|^2} = 1.8 + R_2' = \frac{100}{25}$$

$$R_2 = 2.2 \Omega \quad (X_1 + X_2)^2 = ??$$

$$7.2 = \sqrt{16 + (X_1 + X_2)^2}$$

$$X_1 + X_2 = 6 \Omega \rightarrow X_1 = 3 \Omega = X_2'$$

② no-load test

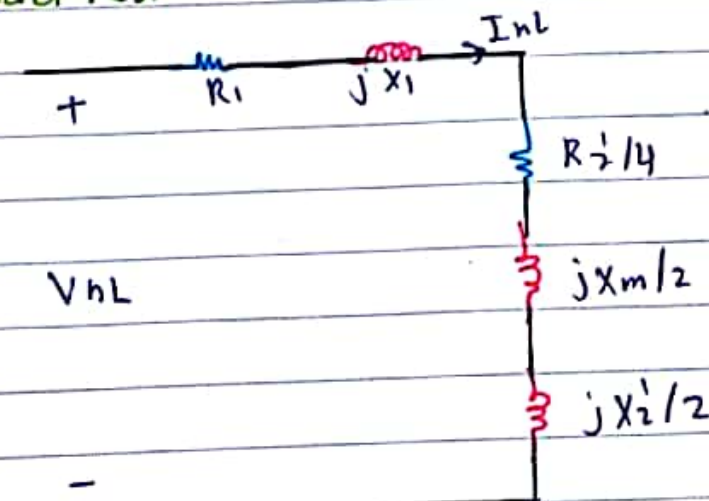

$$|Z_{nl}| = \frac{|V_{nl}|}{|I_{nl}|} = \frac{110}{4} = \sqrt{(R_1 + \frac{R_2'}{4})^2 + (X_1 + \frac{X_m}{2} + \frac{X_2'}{2})^2}$$

$$X_m = ??$$