
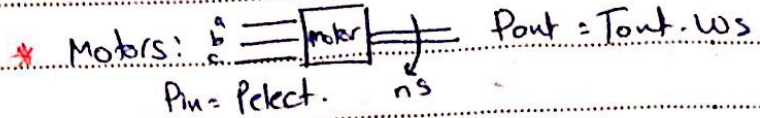
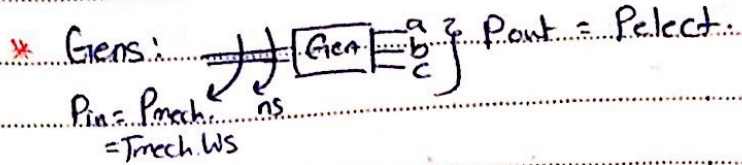


Thursday
13/19/2018

Subject: Machines 2...

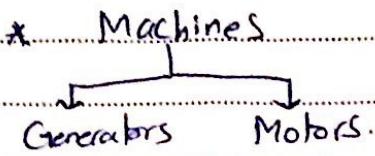

* In synchronous machines:

$$n_s = \frac{120 f_e}{P}$$

$$f_e = \frac{n_s \times P}{120}$$

n_s : synchronous speed in rpm.
 f_e : electric frequency.

$$f_{mech} = \frac{n_s}{60} \text{ : rps (revolutions per second) [\# of cycles / sec]}$$

$$f_{mech} = \frac{120 f_e / P}{60} = \frac{2 f_e}{60 \times P} \rightarrow P_{mech} = \frac{f_e}{P/2} \text{ , } P: \# \text{ of poles. } P/2: \text{ pole pairs} = \frac{P}{2}$$

$$f_e = \frac{P}{2} \cdot f_{mech} \quad (*)$$

* for a 2 pole machine (m/c):

$$f_e = f_m$$

$$* \omega = 2\pi f$$


$$W_{mech} = 2\pi f_m \text{ , } W_{elect} = \frac{P}{2} W_{mech}$$

$$W_{elect} = 2\pi f_e$$


P	n_s (rpm)	
	$f = 120 \text{ Hz}$	$f = 60 \text{ Hz}$
2	3000 rpm	3600
4	1500 rpm	1800
6	1000 rpm	1200
8	750 rpm	900
10	600 rpm	720

Subject:

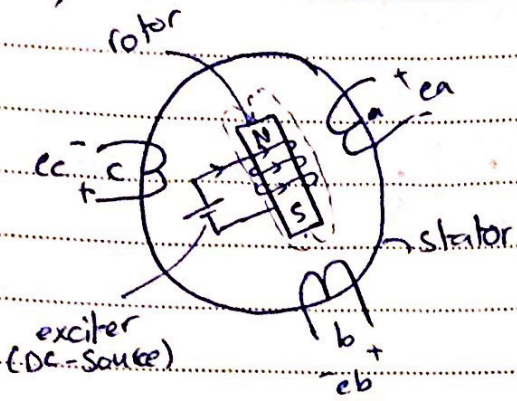* 3 ϕ synchronous machines' construction:



a, b, c! Armature windings.

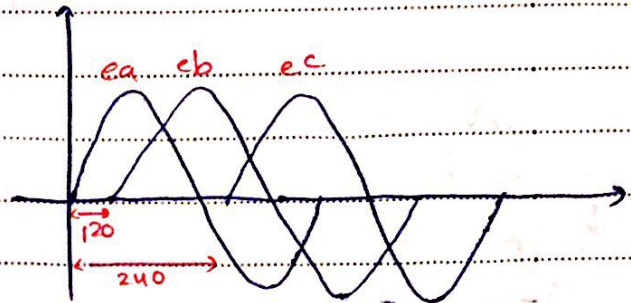

$$\phi_a = \phi_{max} \sin \omega t$$

$$e_a = N \phi \frac{d\phi}{dt} = \omega \phi_{max} N \cos \omega t$$


, $N\phi$: N phase.

$$e_a = E_{max} \cos \omega t$$




$$E_{max} = 2\pi f N \phi_{max}$$


$$E_{rms} = \frac{E_{max}}{\sqrt{2}} = 4.44 f N \phi_{max}$$

ϕ_m d I f
 E_a d I f

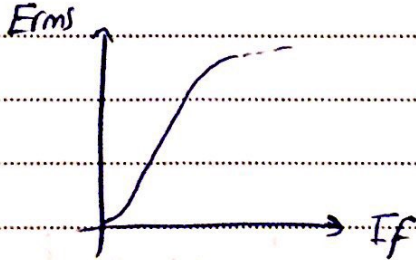

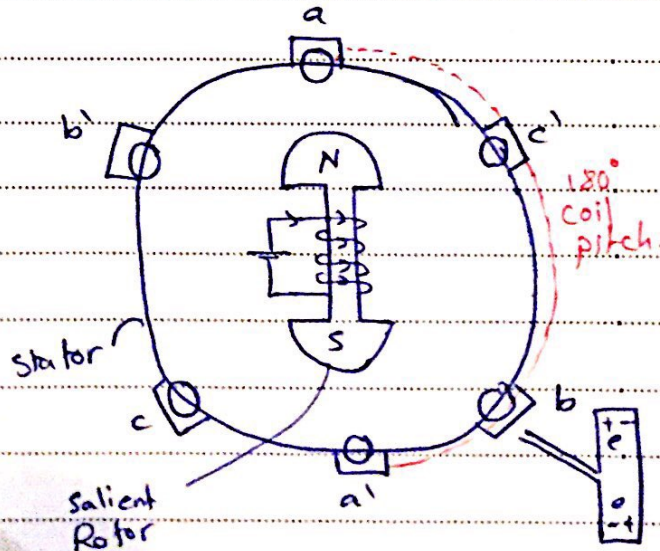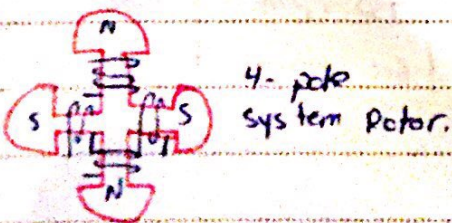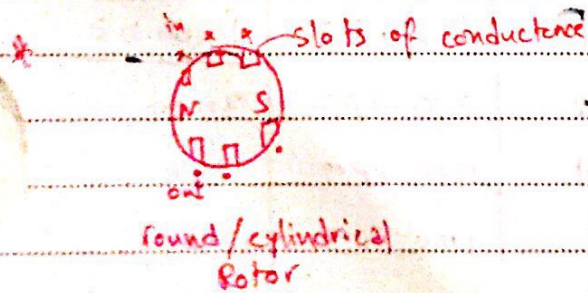* in big AC machines, field is rotor (can be moved) & the armature is the steady circuit.



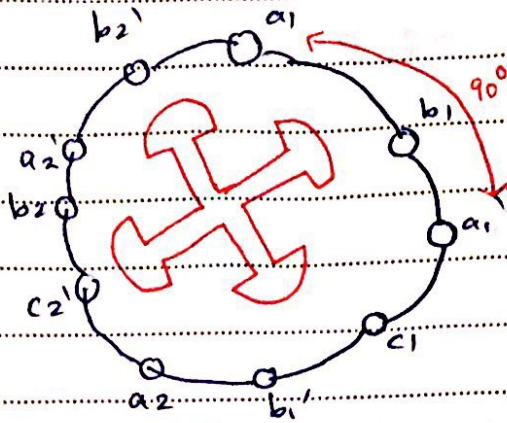


* $\frac{1}{2}$ mechanical cycle \rightarrow 1 electrical cycle

$$f_e = \frac{P}{2} \cdot f_{mech} \quad \text{* very important}$$

Sunday 16/9/2018

* synchronous generator:

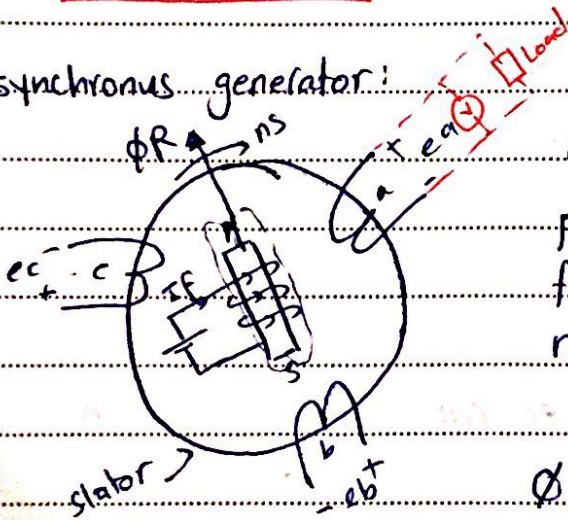

$$n_s = 120 f_e$$

$p = 2$ poles, 2 poles



$f_e = 50 \text{ Hz}, 60 \text{ Hz}$

$n_s = 3000 \text{ rpm} / 3600 \text{ rpm}$

$\phi_R \propto I_f$!

$$\phi_{elect} = \frac{P}{2} \phi_{mech}$$

$$f_e = \frac{P}{2} f_{mech}$$

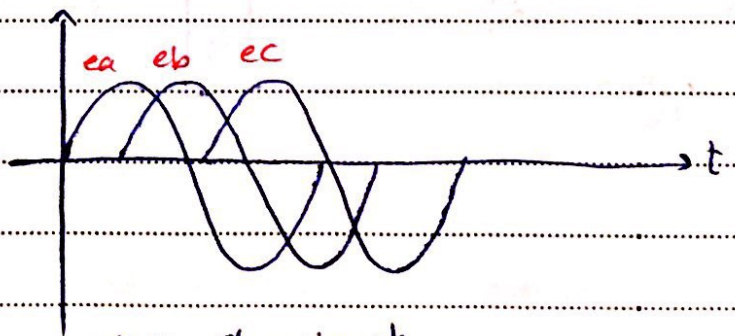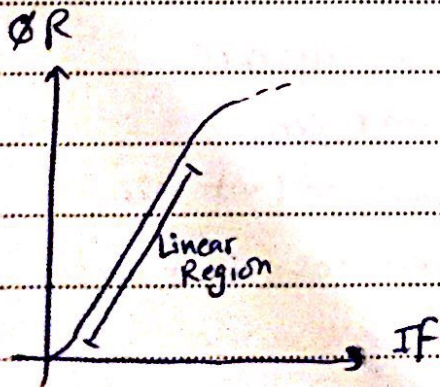

$$\phi(t) = \phi_m \sin \omega t$$

$$e_a = N \frac{d\phi}{dt} = \omega \phi_m N \cos \omega t = e_{max} \cos \omega t$$


* there's 90° shift between the induced voltage (e) & the flux $\phi(t)$.

Subject:


$$* E_{rms} = \frac{E_{max}}{\sqrt{2}} = \frac{2\pi f \cdot N\phi \cdot \phi_{max}}{\sqrt{2}}$$

$$E_{rms} = 4.441 N\phi \cdot f_c \cdot \phi_{max}$$

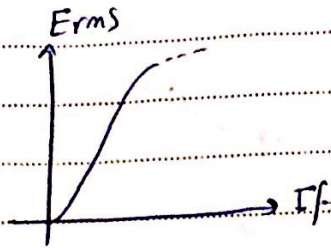
$E_{rms} \propto \phi_{max}$
 $\phi_{max} \propto I_f$
 $E_{rms} \propto I_f$



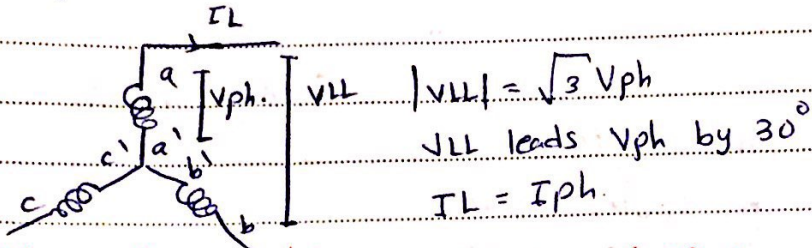* Equivalent circuit of synchronous generator: [Y-connection of Armature]



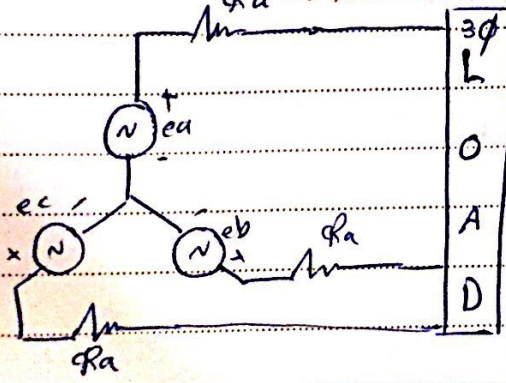Y-connected Armature
 $R_a \rightarrow$ Armature Resistance (effective Resistance).



$$e_a = e_{an}, e_b = e_{bn}, e_c = e_{cn}$$

phase voltages
 instantaneous values \rightarrow lower case letters.

abc +ve sequence.

$$e_a = E_{max} \cos \omega t$$



$$e_b = E_{max} \cos(\omega t - 120^\circ)$$

$$e_c = E_{max} \cos(\omega t + 120^\circ)$$

* DC current flows through the whole cross-section but AC-current flows only on the shell because of skin effect.

Subject:

/ /

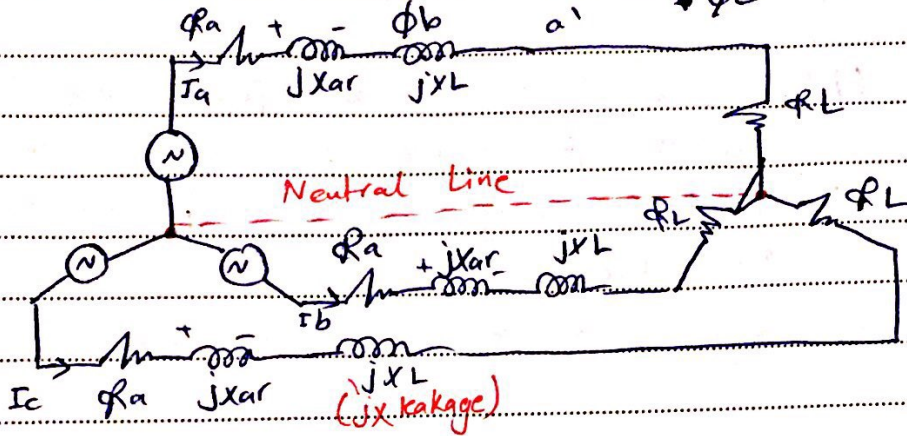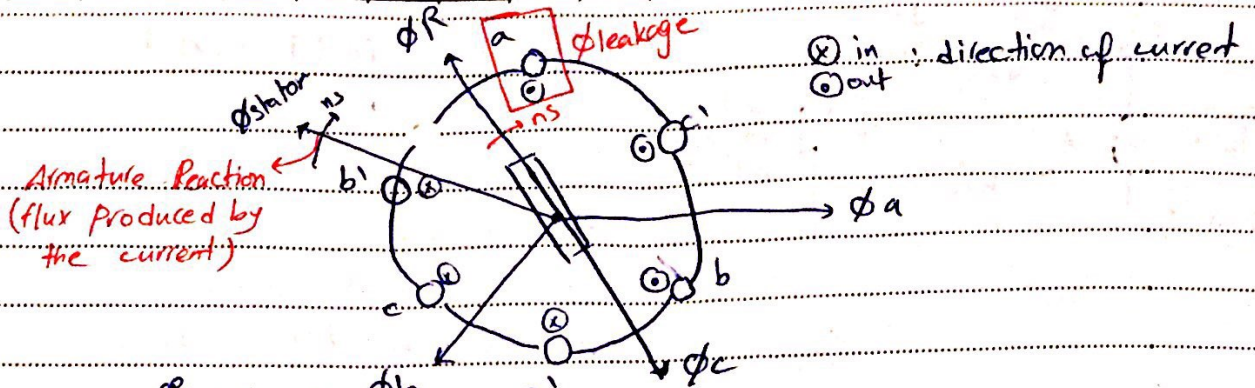

$I_a = I_m \cos(\omega t + \theta)$



$I_b = I_m \cos(\omega t - \theta - 120^\circ)$

$I_c = I_m \cos(\omega t - \theta + 120^\circ)$

$\phi_a = \phi_{max} \sin \omega t$

$\phi_b = \phi_{max} \sin(\omega t - 120^\circ)$

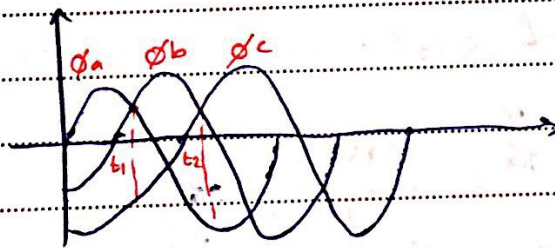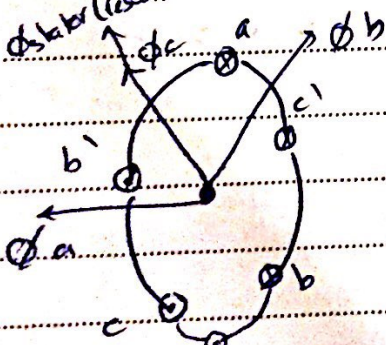
$\phi_c = \phi_{max} \sin(\omega t + 120^\circ)$



$\phi_{stator} = 1.5 \phi_a$

$e = N \frac{d\phi}{dt} = \frac{L}{\omega} \frac{d\omega}{dt}$

* $e = L \frac{di}{dt}$

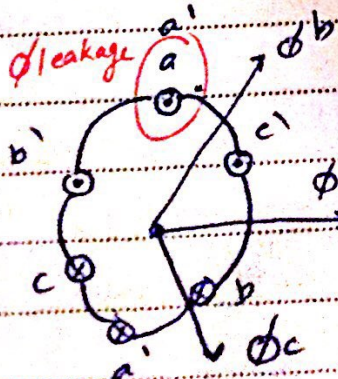

* between Rotor & stator is a gap that we call $\phi_{leakage}$.


$n_s = \frac{120f}{P}$

* flux & current are related by inductance.

* jX_s (synch. reactance)
 $jX_{ar} + jX_L$

Subject:

1 1

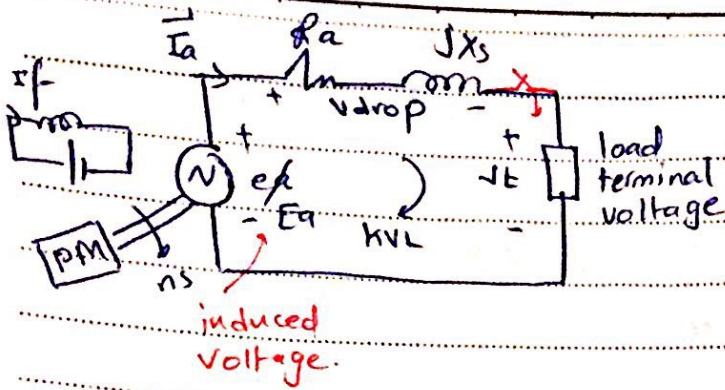


$$\vec{V}_t = \vec{E}_a - \vec{I}_a (R_a + jX_s)$$

[Rated voltage & Rated power are usually given at the terminal]

E_a : rms values (upper case)

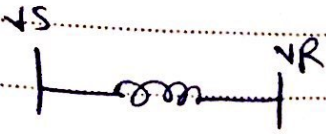e_a : sinusoidal instantaneous values (lower case).



(P): V_s must lead V_R so that power can flow through regardless of the magnitude.
 (Q): $|V_s|$ must be greater than $|V_R|$ so that Φ can flow.

* we take the power from the substational (sub) not from the generator.


* floor is super-conductor.

* for voltage not to be super high, we should make E_a constant [to regulate the voltage at the generator (E_a) by the excitation circuit].

Tuesday 18/9/2018

* Equivalent circuit of S.G (synchronous generator):

Y-connected armature:

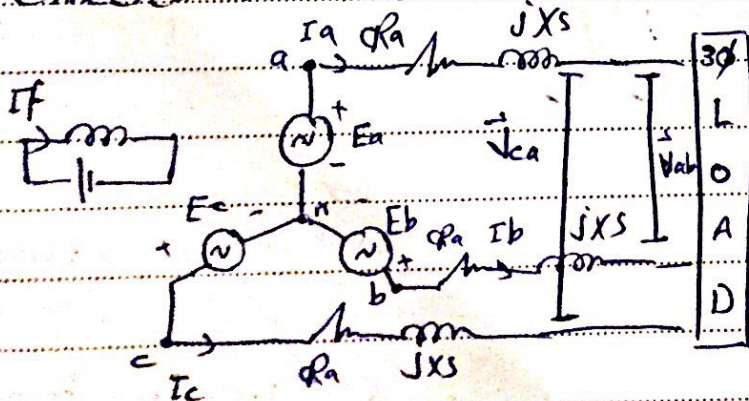

Notes:


lagging PF \rightarrow Inductive load (over-excited)

$E_a > V_t$ to make Φ (VAR) move from left \rightarrow right.

leading PF \rightarrow capacitive load (under-excited)

$E_a < V_t$ to make Φ move from right \rightarrow left.

Subject:


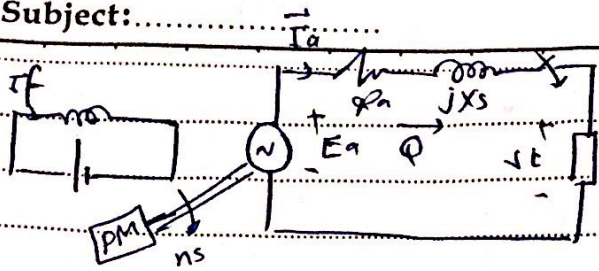


$$|V_{ph}| = |V_L| \sqrt{3}$$

$$|I_{ph}| = I_L$$

V_L leads I_{ph} by 30°

Δ -connected Armature:

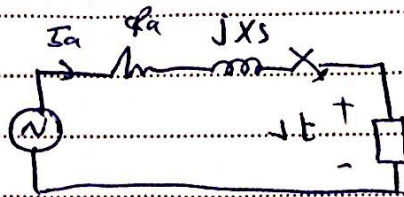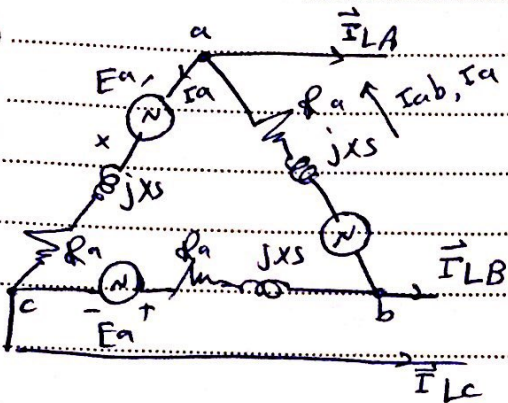


$$|V_{ph}| = |V_{LL}|$$

$$|I_{ph}| = |I_L| / \sqrt{3}$$




I_L lags I_{ph} by 30°

* Modes of operation of synchronous generator:

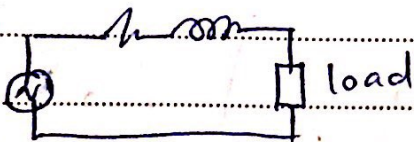1 stand-alone (off grid) machine connected to a load.




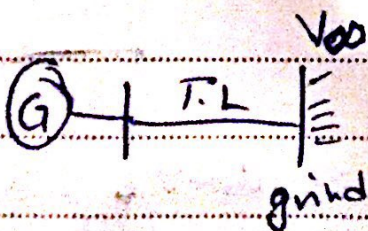
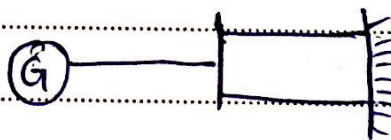
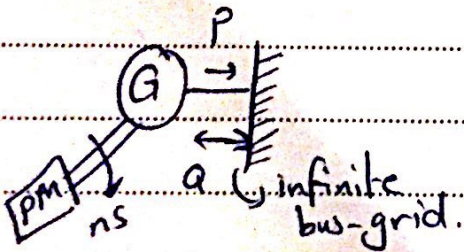
2 on grid (machine connected to an infinite load):




Subject:

* $v(t) = V_{max} \cos(\omega t)$ } Inductive load
 $i(t) = I_{max} \cos(\omega t - \theta)$ }

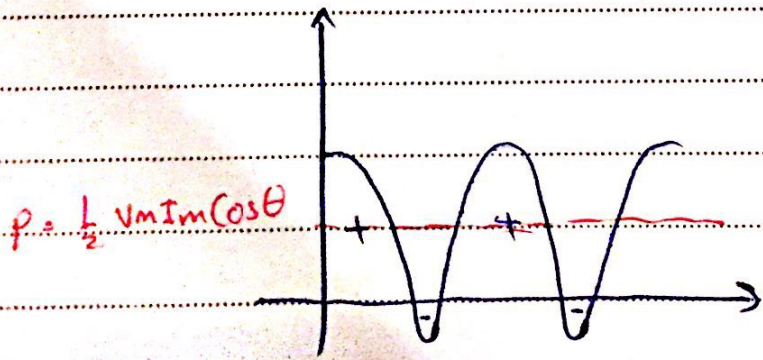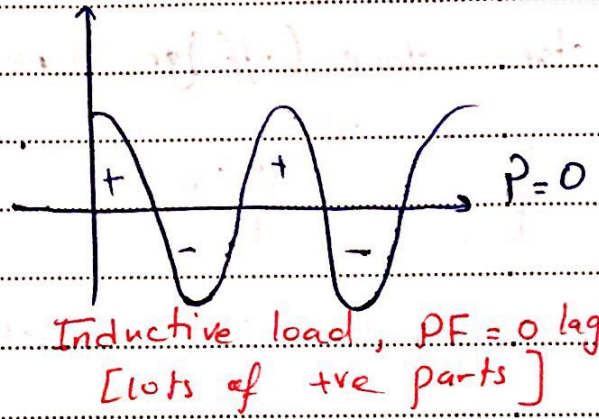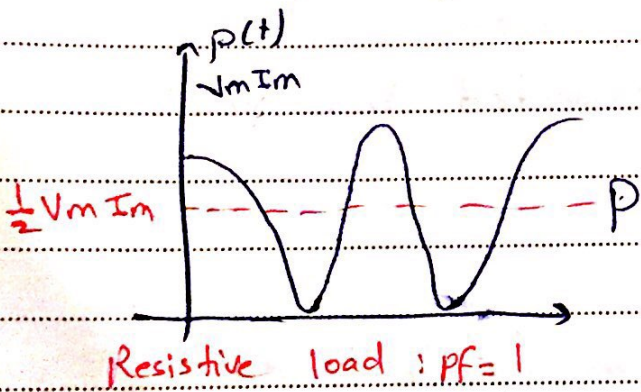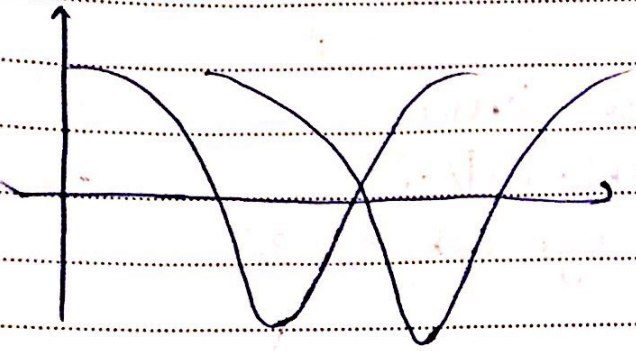$p(t) = v(t) \cdot i(t)$ instantaneous power.
 $= V_{max} \cos(\omega t) \cdot I_m \cos(\omega t - \theta)$
 $= \frac{1}{2} V_m I_m [\cos \theta + \cos(2\omega t - \theta)]$
 $= \frac{1}{2} V_m I_m \cos \theta + \frac{1}{2} V_m I_m \cos(2\omega t - \theta)$
Avg. power (DC-term) Instantaneous power



Inductive load $0 < PF < 1$ (little -ve)

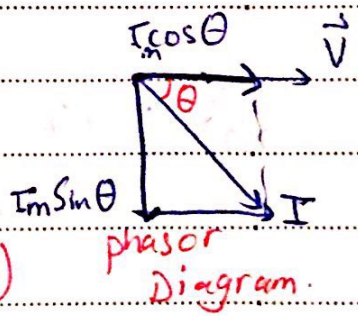


Subject:

/ /


$$p(t) = \frac{1}{2} V_m I_m \cos \theta + \frac{1}{2} V_m I_m [\cos 2\omega t \cos \theta + \sin 2\omega t \sin \theta]$$
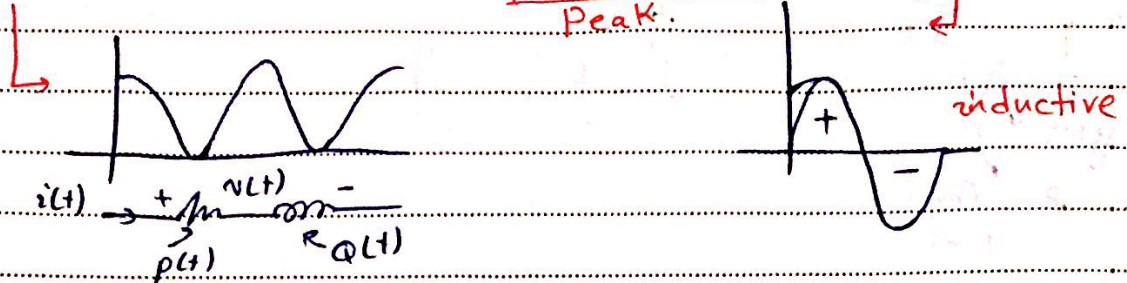
$$= \frac{1}{2} V_m I_m \cos \theta [1 + \cos 2\omega t] + \frac{1}{2} V_m I_m \sin \theta [\sin 2\omega t]$$




* Real power is the average of the instantaneous power.

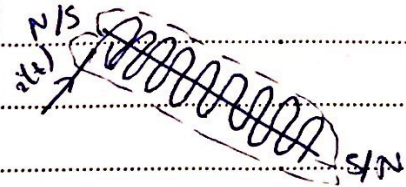* VAR is the peak of the instantaneous power absorbed by the capacitor or inductive load.



Mode [1]: Generator connected to a load.

1) Inductive load.

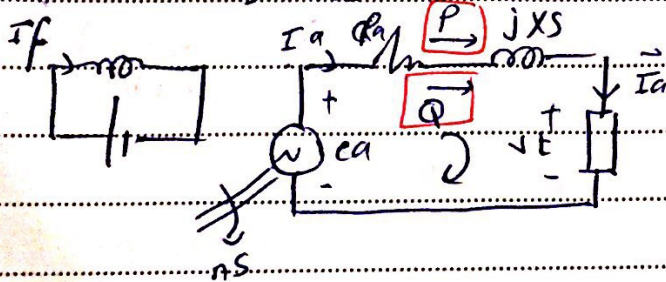


* \vec{I}_a lags \vec{v}_t by θ

* current lags V by θ

$$\vec{E}_a = \vec{v}_t + \vec{I}_a (R_a + jX_s)$$

let \vec{v}_t be the reference.

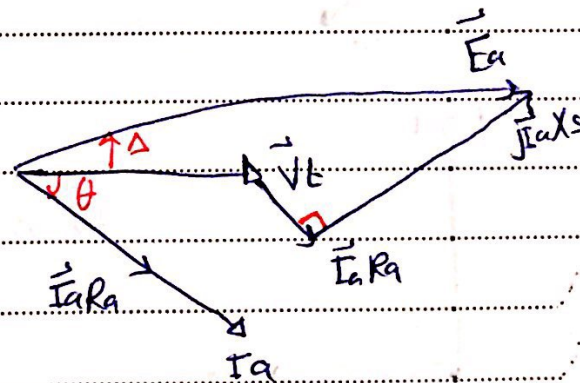

$|\vec{E}_a| > |\vec{v}_t|$ (over-excited)

supplies VAR.

\vec{E}_a leads \vec{v}_t


(P) power is generated.

Thursday
20 / 9 / 2018

Subject:

* Modes of operation of synchronous generators:

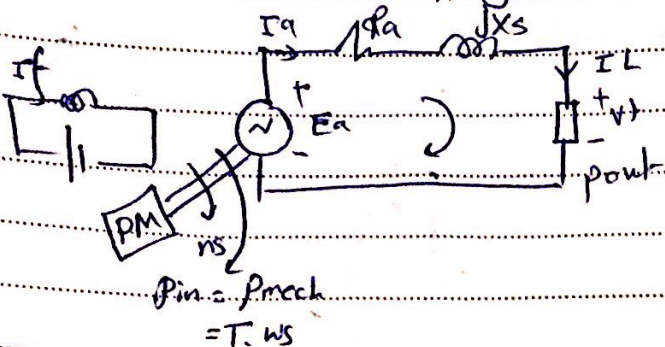1) Isolated Mode (off-grid), (stand-alone operation):-




load
unity PF leading PF lagging PF

$$\vec{E}_a = \vec{V}_t + \vec{I}_a (R_a + jX_s) \quad [\text{per phase equivalent ckt}]$$

phase voltage
phase current

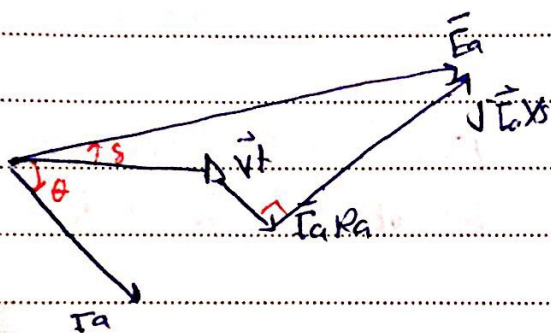* lagging PF operation: (Inductive load):




a. $|E_a| > |V_t|$: lag PF

Gen. supplies ϕ
(over excited).

b. \vec{E}_a leads V_t

↳ can supply Real power (P)

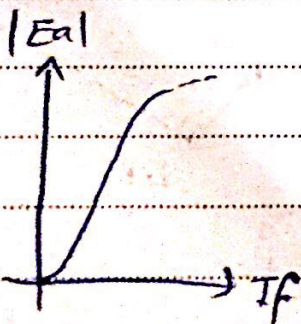


E_a is related to the excitation.

No load characteristic.

Subject:

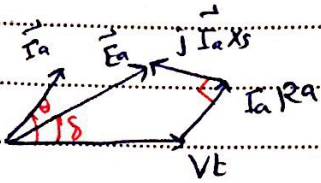
* leading PF operation: (capacitive load) :-




a. $|E_a| < |V_t| \rightarrow$ under-excited (Gen. absorbs P)

b. \vec{E}_a leads $\vec{V}_t \rightarrow$ (Gen supplies P)

* unity PF operation:

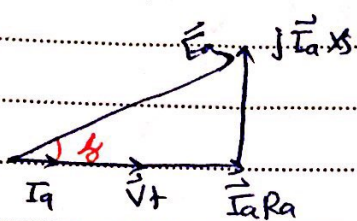

$|\vec{E}_a| > |\vec{V}_t|$ slightly.

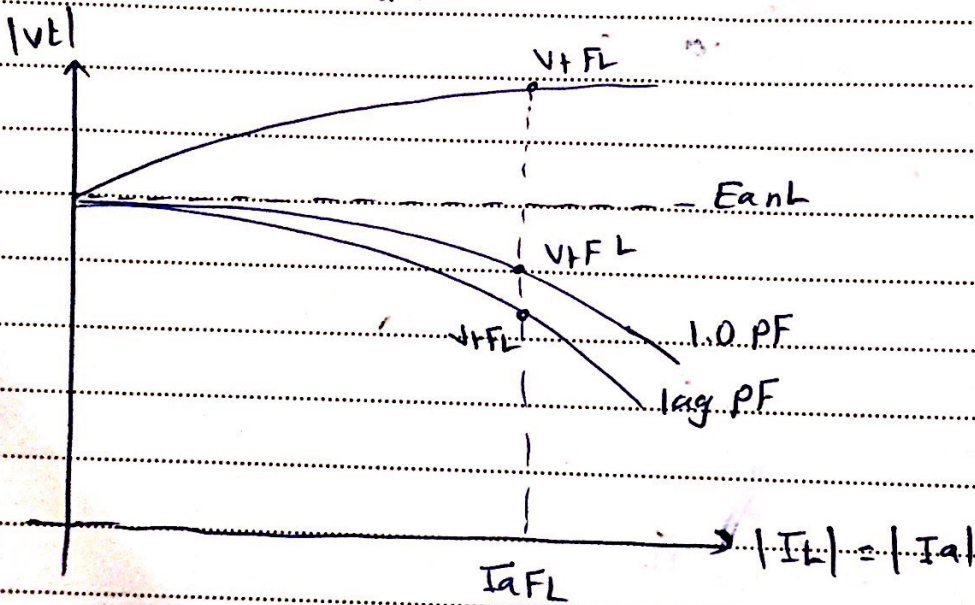


* E_{aNL} ! NO-load



load characteristic.

$$\begin{aligned} \% \text{ Voltage Regulation} &= \frac{|V_{NL}| - |V_{FL}|}{|V_{FL}|} \times 100\% \\ &= \frac{|E_a| - |V_{FL}|}{|V_{FL}|} \times 100\% \end{aligned}$$

Subject:

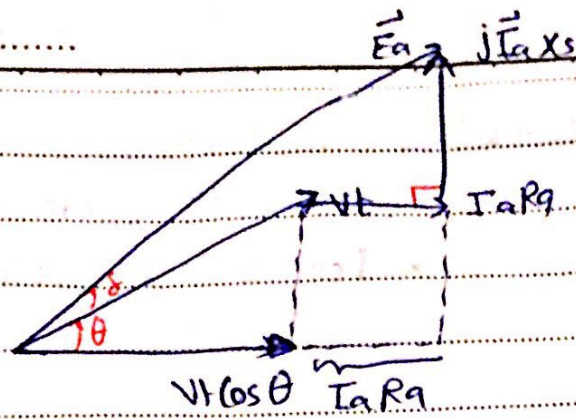

$$|E_a| = \sqrt{(V_t \cos \theta + I_a R_a)^2 + (V_t \sin \theta + I_a X_s)^2} \quad (*)$$

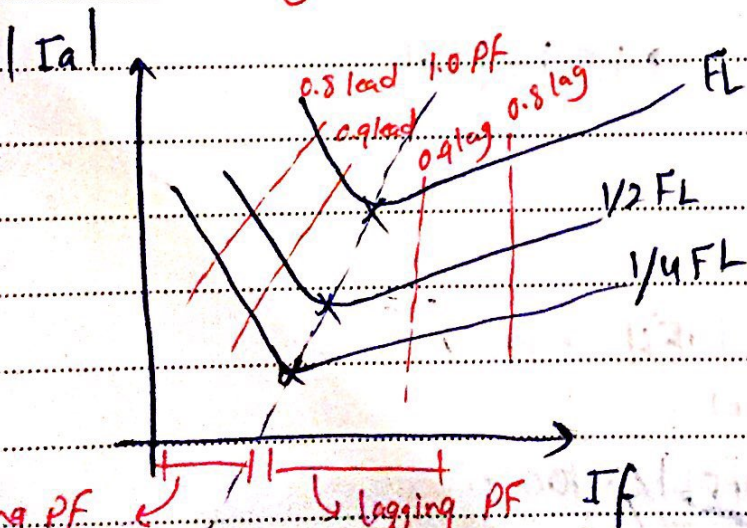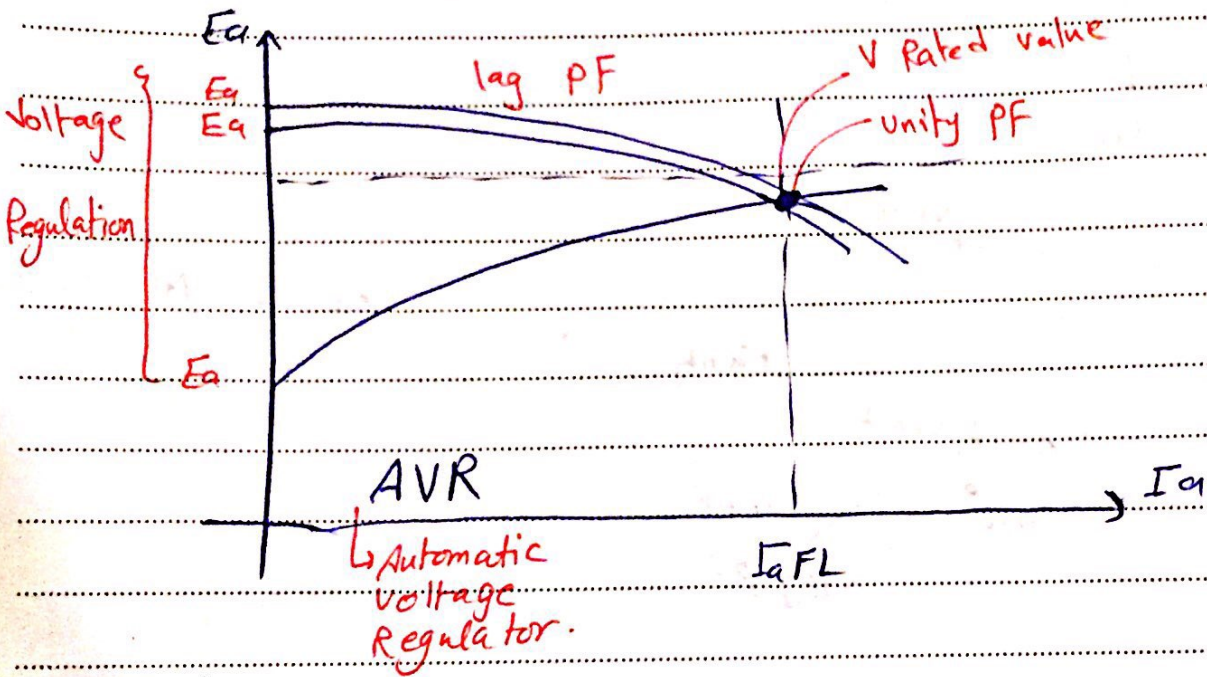

leading PF operation.
(absorbs VAR) under-excited.

lagging PF operation.
(supplies VAR) over-excited.

Subject:


x power flow diagram:-

$$P_{in} = T_{in} \cdot WS$$

$$P_{converted} = P_{developed}$$

$$T_{d} \cdot WS = \sqrt{3} E_a I_L \cos(\delta + \theta)$$

P_{out}

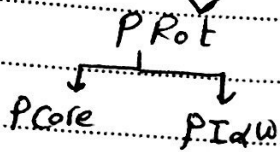

$$P_{out} = 3 V I_a \cos \theta$$

$$= \sqrt{3} V_L I_L \cos \theta$$


$$3 I_a^2 R_a \quad y = \frac{P_{out}}{P_{in}}$$

$$PF = \frac{P_{out}}{P_{in}}$$

$$= \frac{3 V I_a \cos \theta}{3 V I_a \cos \theta + P_{Cu} + P_{Rot}}$$

$$= \frac{P_{out}}{P_{out} + \text{Losses}}$$

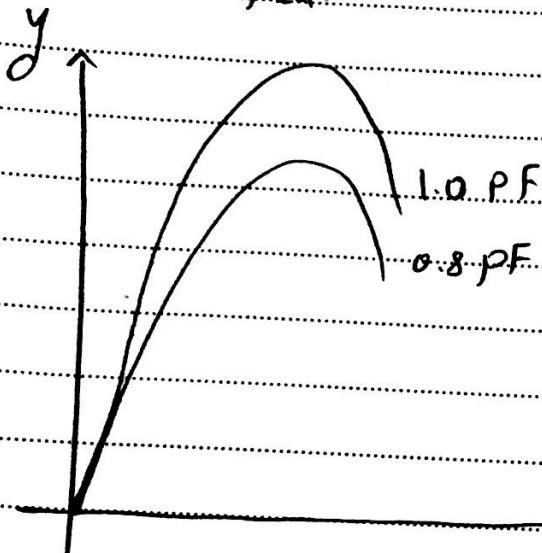
$$= \frac{P_{in} - \text{Losses}}{P_{in}}$$



Subject:

Tuesday - 25/9/2018

* parameter calculation of synch. m/c

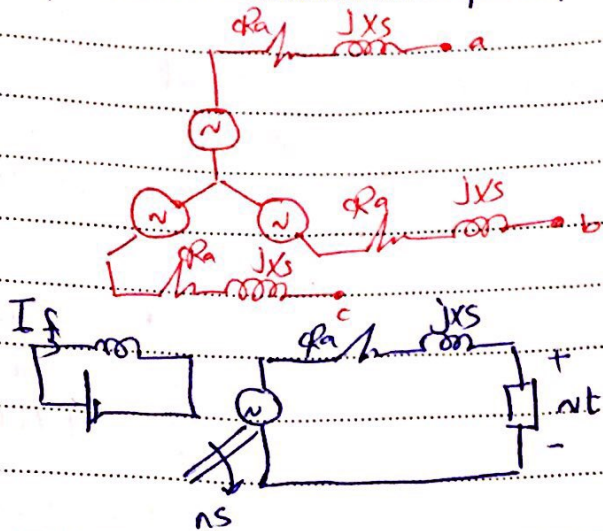


single phase equivalent circuit.

* to find the parameters R_a , X_s , these tests are applied:

- 1] DC-resistance test
- 2] open circuit test (o.c.t)
- 3] short circuit test (s.c.t)

1] DC-Resistance test:

while the m/c is at stand still ($n=0$)

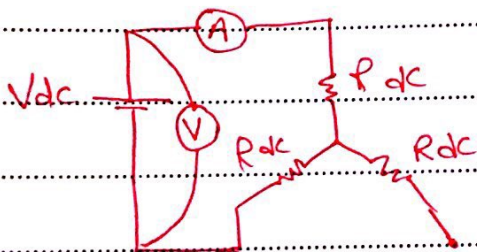

V_{dc}	I_{dc}
X	X
	↳ R_{dc}


$$\frac{V_{dc}}{I_{dc}} = 2R_{dc} \rightarrow R_{dc} = \frac{1}{2} \frac{V_{dc}}{I_{dc}}$$

* for γ -connected armature

subject:


1 / 1

for Δ -connected armatures

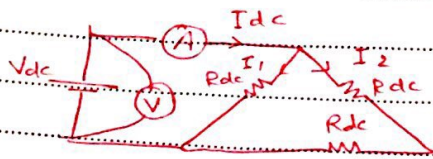


$$\frac{V_{dc}}{I_{dc}} = R_{dc} // 2 R_{dc} = \frac{2}{3} R_{dc}$$

$$R_{dc} = 1.5 \frac{V_{dc}}{I_{dc}}$$

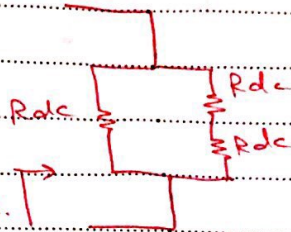

* under AC current, there's skin effect:

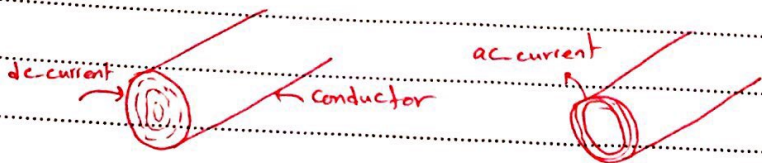


$$R_{dc} = \frac{\rho L}{A} = \frac{L}{6A}$$

$$R_{ac} > R_{dc}$$

for synch. m/c!

$$R_{ac} = (1.1 - 1.5) \times R_{dc}$$

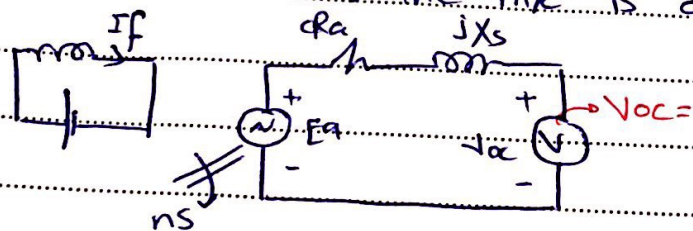③ No load test, the m/c is open circuit ($n = n_s$)




$$|E_a| = 4.44 k \phi f N_{ph} \phi$$

$$E_a \propto \phi$$


$$\phi \propto I_f$$

$$E_a \propto I_f$$

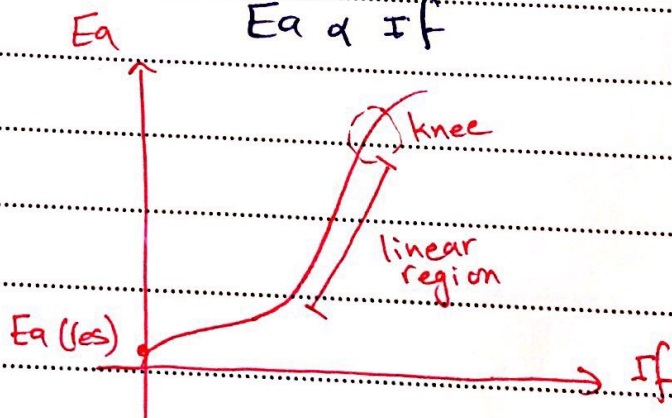


Subject:

3 Short circuit test:

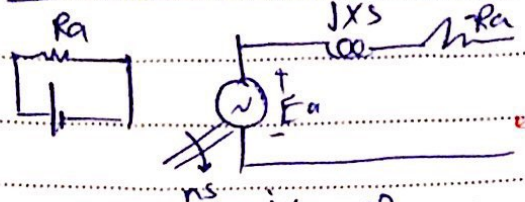




$I_{sc} \ 3\phi$

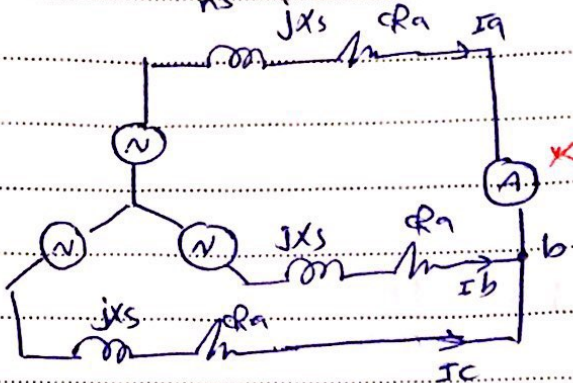

equivalent to s.c
 3ϕ balanced fault
 $|I_a| = |I_b| = |I_c|$
 $= I_{sc} \ 3\phi$

$$|I_{sc}| = \frac{|E_a|}{|Z_s|} = \frac{|E_a|}{\sqrt{R_a^2 + X_s^2}} \rightarrow Z_s = \frac{|E_{a\text{ph}}|}{I_{sc\text{ph}}} = \sqrt{R_a^2 + X_s^2}$$

$$X_s = \sqrt{Z_s^2 - R_a^2}$$

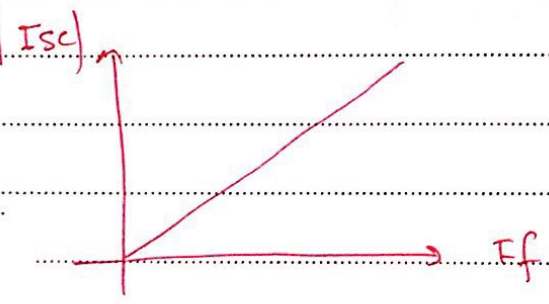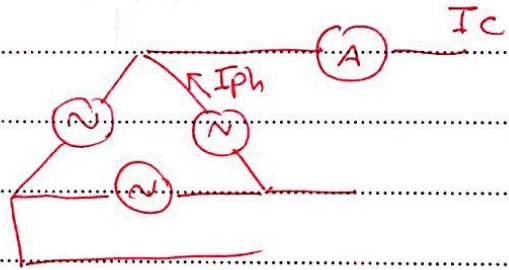
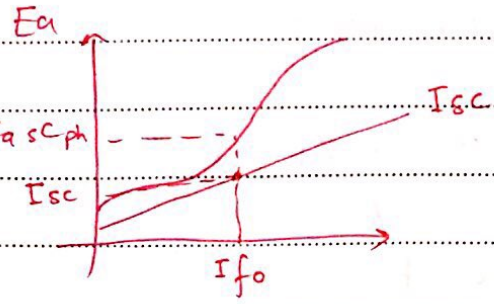


Subject:

* synchronous generator connected to a bus (Grid):-



$R_a \ll X_s$ (R_a isn't negligible)

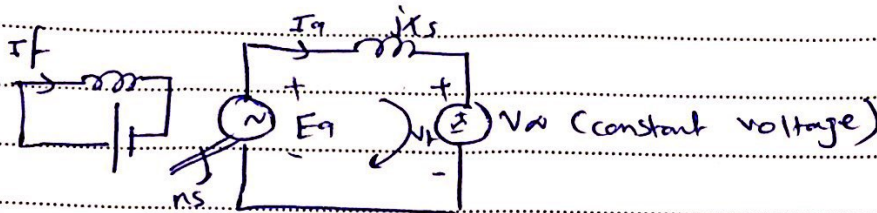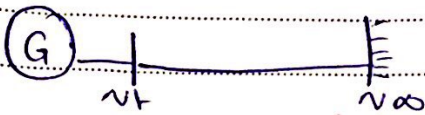


$$E_a = V_t + j I_a X_s$$

consider lagging PF operation, $PF = \cos \theta$

leading PF, capacitive I_a \searrow V_t

δ = power (torque) angle


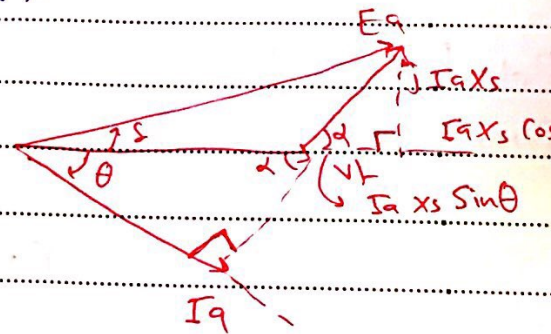


$$E_a \sin \delta = I_a X_s \cos \theta$$

$$\frac{E_a}{X_s} \sin \delta = I_a \cos \theta$$

$$P = \frac{3 V_t E_a \sin \delta}{X_s} = 3 V_t I_a \cos \theta = P_{3\phi} = P_{out} \quad (\text{Imp})$$





↳ developed power

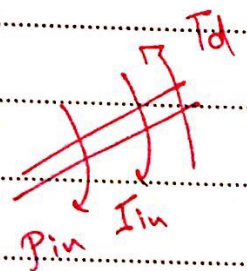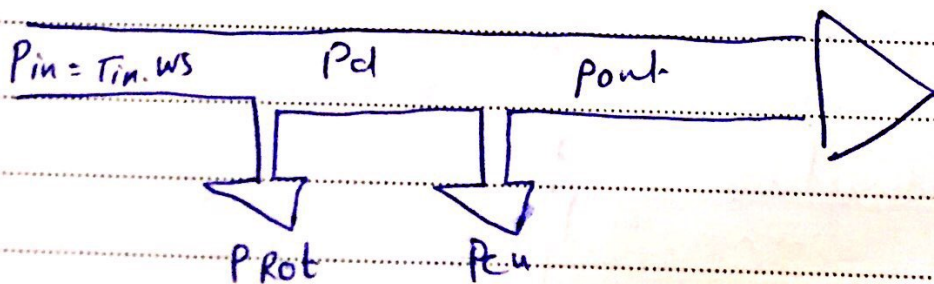

Subject:


$$P_{developed} = P_{out} = \frac{3V_t E_f \sin \delta}{X_s} = 3V_t I_a \cos \theta$$

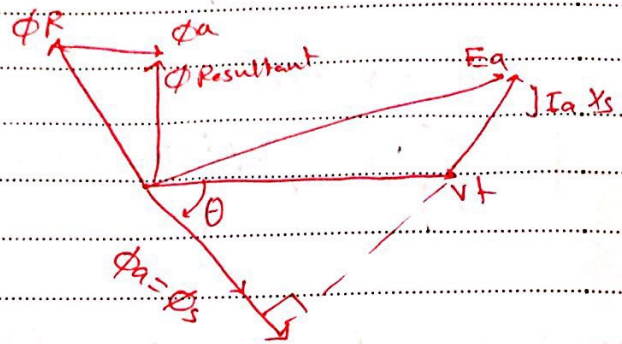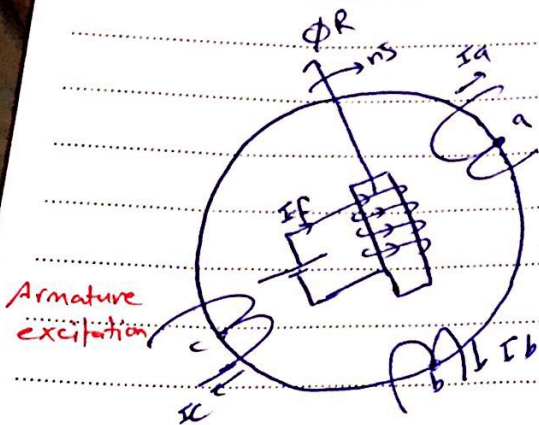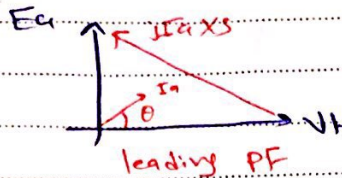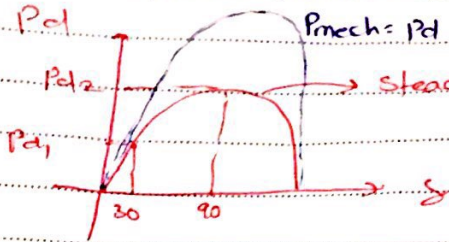$P_{mech} = P_d \xrightarrow{X_s}$ to solve this instability we increase E_f



$$P_d = P_{max} \sin \delta$$

$$P_{max} = \frac{3V_t E_f}{X_s}$$

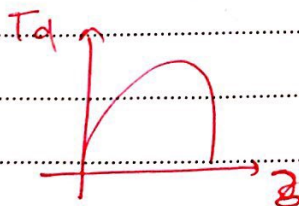


$$P_d = T_d \cdot \omega_s$$

$$E_f \cos \delta = V_t + I_a X_s \sin \theta$$

$$E_f \cos \delta - V_t = I_a X_s \sin \theta$$

$$\frac{1}{X_s} [E_f \cos \delta - V_t] = I_a \sin \theta$$
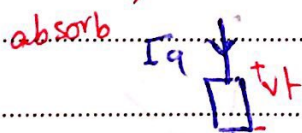
$$\frac{3V_t}{X_s} [E_f \cos \delta - V_t] = 3V_t I_a \sin \theta = Q \quad \leftarrow \text{+ absorb}$$



$P = |V_t| |I_a| \cos \theta$
 $p > 0$ absorb
 $p < 0$ generate



① $E_f \cos \delta > V_t$
 (over-excited, supplies VAR)

② $E_f \cos \delta < V_t$
 (under-excited, absorbs VAR)






$P = |V_t| |I_a| \cos \theta$
 $p > 0$ generate
 $p < 0$ absorb

• 3rd harmonic is 0 sequence.

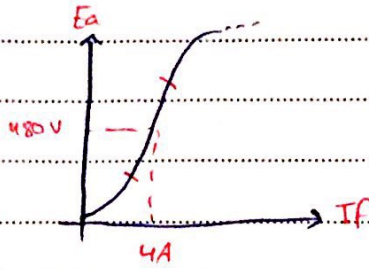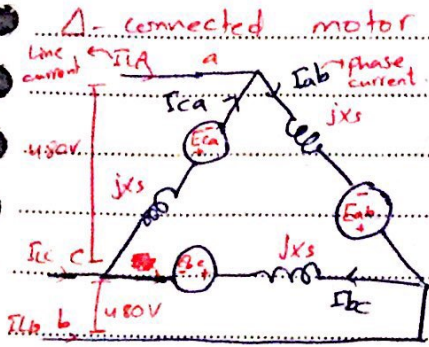

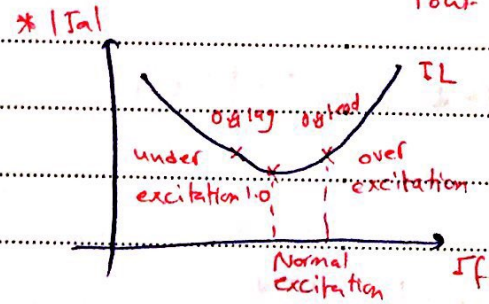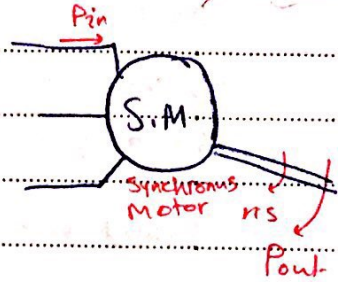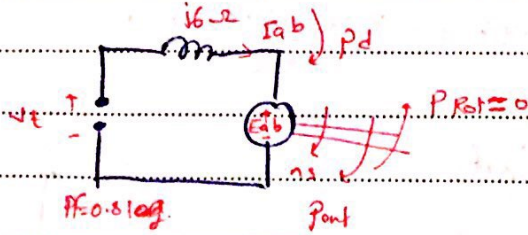- $f = 60 \text{ Hz}$, $p = 8$
- $V_L = 480 \text{ V}$
- $X_s = 6 \Omega$
- $R_a = 0$
- $P_{core} + P_{friction} = P_{rot} \approx 0$
- 400 hp
- Rated $\text{app. PF} = 0.8$
- leading.



$P_d = P_{out} = P_{in}$

Sol: $P_{out} = 400 \text{ hp}$

$$= \frac{400 \times 746}{1000} = 298.3 \text{ kW}$$

$$P_d = P_{out} = P_{in} = 298.3 \text{ kW}$$

$$P_{in} = 3 V_L |I_{ph}| \cos \theta = \sqrt{3} V_L I_L \cos \theta$$

$$= 3 \times 480 \times I_{ph} \times 0.8 = \sqrt{3} \times 480 \times I_L \times 0.8$$

$$I_L = \frac{298.3 \times 10^3}{\sqrt{3} \times 480 \times 0.8} = \sqrt{3} \times I_{ph}$$

$$I_L = 448.5 \text{ A}, \quad I_{ph} = 258.9 \text{ A}$$


Subject:

$$\bar{E}_a = \bar{V}_t - j\bar{I}_a X_s$$

$$= 480 \angle 0^\circ - 258.9 \angle -36.9^\circ \times 6 \angle 90^\circ$$

$$= 406.2 \angle -17.8^\circ \text{ V}$$

$$|E_{ab2}| = |E_{ab1}| \times$$

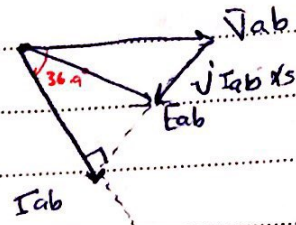

$$T_d = \frac{3 V_t E_{ab} \sin \delta}{X_s \omega_s}$$


$$= \frac{3 \times 480 \times 406.2 \sin(17.8^\circ)}{6 \times 94.2} = \frac{9.55 \times 298.3 \times 10^3}{900}$$

$$T_d = 3166 \text{ N.m} = T_{out} = T_{shaft}$$

$$|E_{ab2}| = 1.3 \times |E_{ab1}|$$

$$= 1.3 \times 406.2$$

$$= 528 \text{ V}$$

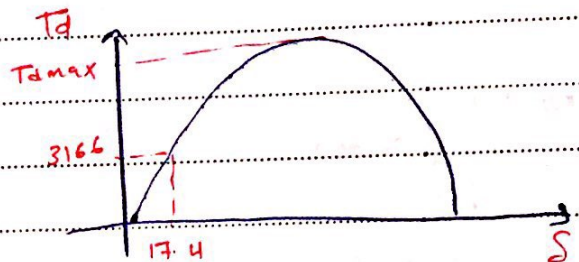

$$|E_{ll}| = 480 \text{ V}$$

$$I_f = 4 \text{ A}$$

$$T_{dmax} = \frac{3 \times 480 \times 406.2}{6 \times 94.2}$$

$$\delta = 90^\circ$$

$$= 10356 \text{ N.m}$$

$$n_s = \frac{120 f_e}{P} = \frac{120 \times 60}{8} = 900 \text{ rpm}$$

$$\frac{T_{max}}{T_d} = \frac{10356}{3166} \approx 3$$

$$P_{d1} = P_{d2}$$

$$E_{ab} \sin \delta_1 = E_{ab2} \sin \delta_2$$

$$\delta_2 = 13.6^\circ$$

$$\bar{E}_{ab2} = 528 \angle -13.6^\circ \text{ V}$$

$$\bar{I}_{ab2} = \frac{\bar{V}_t - \bar{E}_{ab2}}{jX_s} = \frac{480 \angle 0^\circ - 528 \angle -13.6^\circ}{6 \angle 90^\circ}$$


$$= 21.4 \angle 15^\circ \text{ A}$$

Done for synchronous motor.

* Power factor correction (slide 34)

lag $\rightarrow Q$ -ve
lead $\rightarrow Q$ -ve

(Question in the exam about this topic)

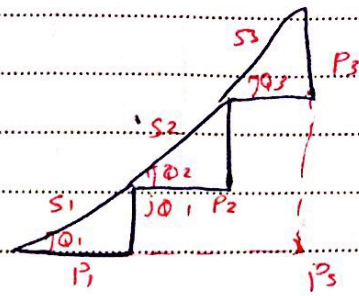


$$Q_s = Q_1 + Q_2 + Q_3$$

$$P_s = P_1 + P_2 + P_3$$

End of exam (bst) material.


Sunday 21/10/2018

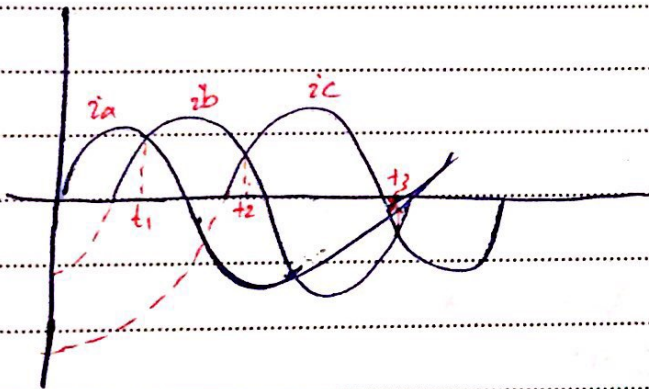Topic 2-a: Three phase Induction (Asynchronous motor).




$$\frac{3000}{P/2} \quad \frac{3600}{P/2} \quad 50 \text{ Hz}$$

$$n = \frac{120 f_e}{P}$$

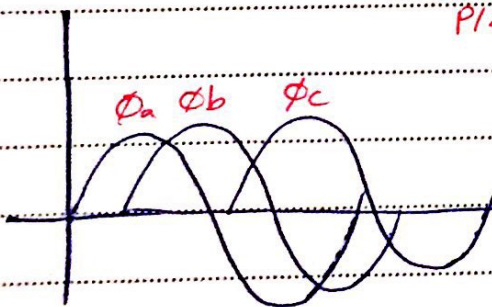


* Torque slows down \rightarrow relative speed is induced again.



Tuesday 23/10/2018

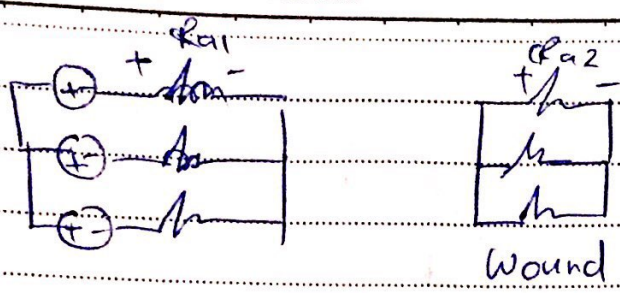

Wound

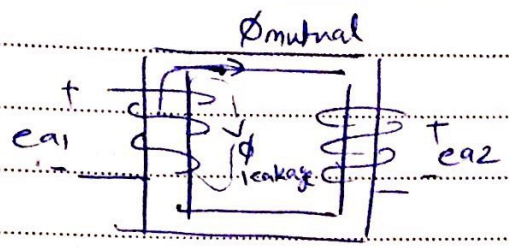
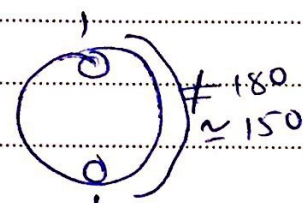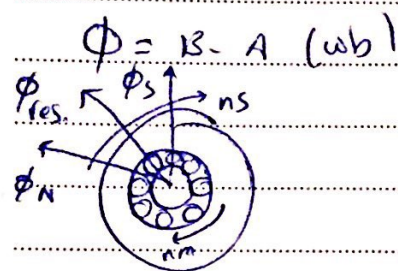
$$e_1 = N_1 \frac{d\phi}{dt}, \quad \frac{e_1}{e_2} = \frac{N_1}{N_2}$$



to cancel 6th harmonic
 $k_w \approx 0.9 \rightarrow 0.95$

$$i \rightarrow \frac{e}{L}$$

$$e = N \frac{d\phi}{dt} = L \frac{di}{dt}$$

EM theory CKT theory