

Spring017



Dr.Sahban Alnaser

BY:

Mohammed Abuhashieh


Powerunit-ju.com

Measurements

second
semester
(2017)

Dr. Sahban .


Mohammad
Abu Hashia.

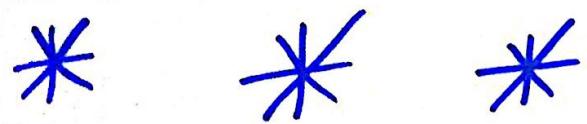


* Instrument:

- Device Collect Data.
- Display.
- Optional (Analysis)

* Instruments

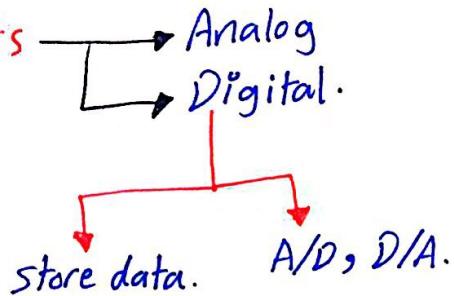

Ammeter.

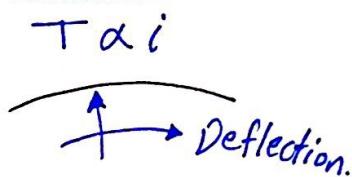

EN50160 standard
Distribution code

1 week
10-min \Rightarrow 95% within voltage limit.
 $-6\% \leq \Delta V \leq 10\%$

* Does this instrument provide true value?

true value \triangleq theoretical value based on models.

* Characteristics of measurement instruments:

① Accuracy: How close is the reading from the true value.

Ex. Voltmeter:


$$\begin{aligned} \text{measured value} &= 10 \text{ V.} \\ \text{accuracy} &= 10\% \text{ (close to the true value)} \\ \text{Range } 0-15 \text{ V} & \quad \text{True value} = 10 \pm (10\% * 15) \\ &= 8.5 \rightarrow 11.5 \text{ volt.} \end{aligned}$$

find true value?

* Accuracy (expressed)
(inaccuracy)

② Precision: \Rightarrow Reproducibility.

Ex.

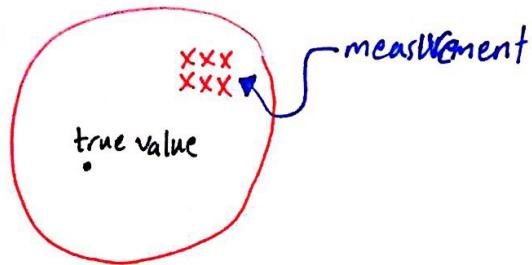

for Ex:

- * High precise.
- * Low accuracy.

③ Sensitivity: it is the ability to respond to the changes in the measured quantity. (inputs).

$$S = \frac{\Delta \text{ output}}{\Delta \text{ input}}$$

④ Threshold: minimum input that could be measured.

⑤ Resolution: -

Precision:

metric.

σ \triangleq standard deviation.

$$\sigma^2 = E[(x - \bar{x})^2]$$

Mean.


Expectation.

$$\sigma = \sqrt{\frac{\sum_{i=1}^N (x_i - \bar{x})^2}{N}}$$

mean "average"

Sample Size

Reading.

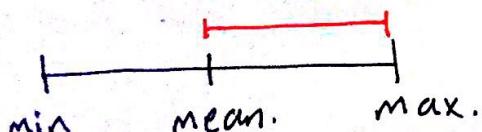

$|max - mean| \rightarrow$ precision.

we use it to compare between two devices to know which one has better precision.

\Rightarrow the smallest value $|max - mean|$ is higher precision.

Ex. A voltmeter is used to read voltage of 5V. "DC Load" (3)

A: " 5.03, 4.97, 5, 5.02, 4.99, 4.98, 5.03, 5.02, 5.01, 4.97"

B: " 5.2, 5.2, 5.2, 5.2

⇒ Compare accuracy, precision?

Accuracy:


A true = 5V.
mean = 5V.

B true = 5V.
average = 5.2V.

A is more accurate than B.

Precision:

the precision in B is higher than in A.

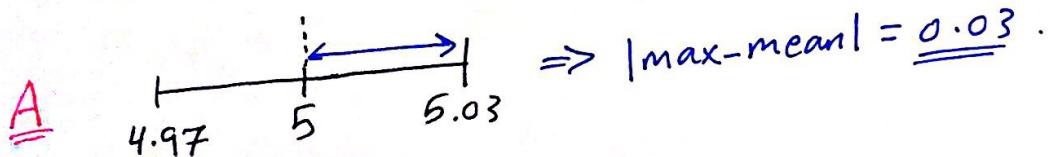

Note:

reading	10	8	20
freq.	100	20	80

$$\bar{X} = E[X] \\ = 10 * \left(\frac{100}{200}\right) + 8 * \left(\frac{20}{200}\right) \\ + 20 * \left(\frac{80}{200}\right) \\ = \underline{\underline{13.8}}$$

mean average.

Ex. (Resolution) A digital system (A/D) uses a specific # of bits
12 bits How much is the resolution? (Full scale = 5V).


$$12 \text{ bits} \Rightarrow \# \text{ of levels} = 2^{12}$$

$$\text{Resolution} \equiv \frac{\text{step size}}{\text{size}} = \frac{5}{2^{12}} = \underline{\underline{1.221 * 10^{-3}}}$$

Ex. (Sensitivity)

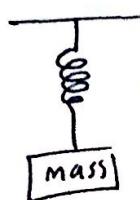(4)

measuring system aims to measure the mass




\Rightarrow mass \propto Displacement.

always like these
table it must
have operating
condition.

input (kg)	0	50	100
O/P (cm)	0	10	20

Displacement.

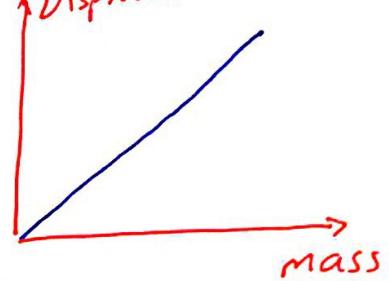
$$\text{sensitivity} \triangleq \text{slope} = \frac{10}{50} \text{ cm/Kg.}$$



\checkmark we can't
do this.


\Rightarrow power-system
single line
diagram.

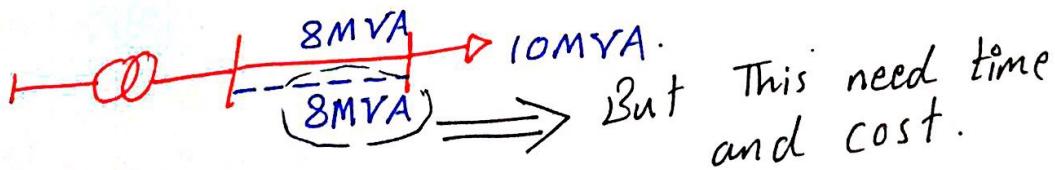\Rightarrow Solution ①: install new line.



But This need time
and cost.

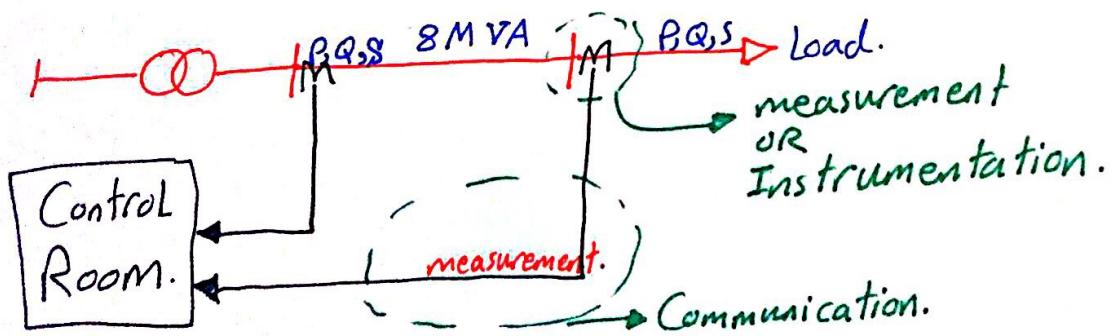\Rightarrow Solution ②: Control Load \Rightarrow "Active Network Management".




Example:

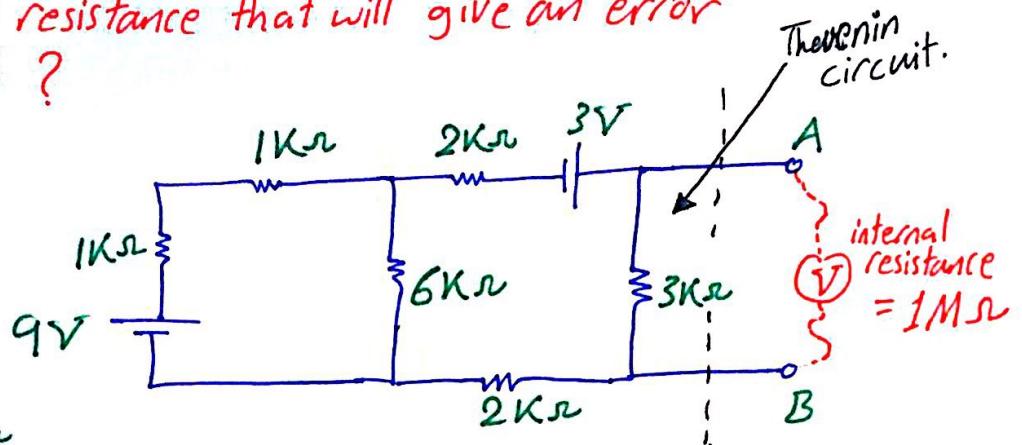
(5)

For the shown circuit:

- ① Find the error in the measurement?
- ② Find the internal resistance that will give an error smaller than 1%?


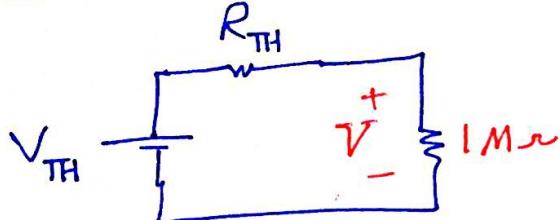
$$\textcircled{1} \quad R_{TH} = 2\text{ k}\Omega$$



$$V_{real} = V_{th} \quad (\text{when } R_V \rightarrow \infty)$$

$$V_{measured} = \frac{1\text{ M}}{1\text{ M} + 2\text{ k}} V_{th} \\ = 0.998 V_{th}.$$

$$\text{Error} = \frac{V_{real} - V_{measured}}{V_{real}} * 100\% \\ = \frac{V_{th} - 0.998 V_{th}}{V_{th}} * 100\% =$$

$$= 0.2\%$$

② Final Answer:


$$R_V \geq 198\text{ k}\Omega \quad \text{To achieve error smaller than 1\%}$$

$$\Rightarrow \left[1 - \frac{R_V}{R_V + 2\text{ k}} \right] * 100 \leq 1 \Rightarrow 0.01 R_V \geq 1980$$

so $\underline{\underline{R_V \geq 198\text{ k}\Omega}}$

(6)

* Transfer Function:

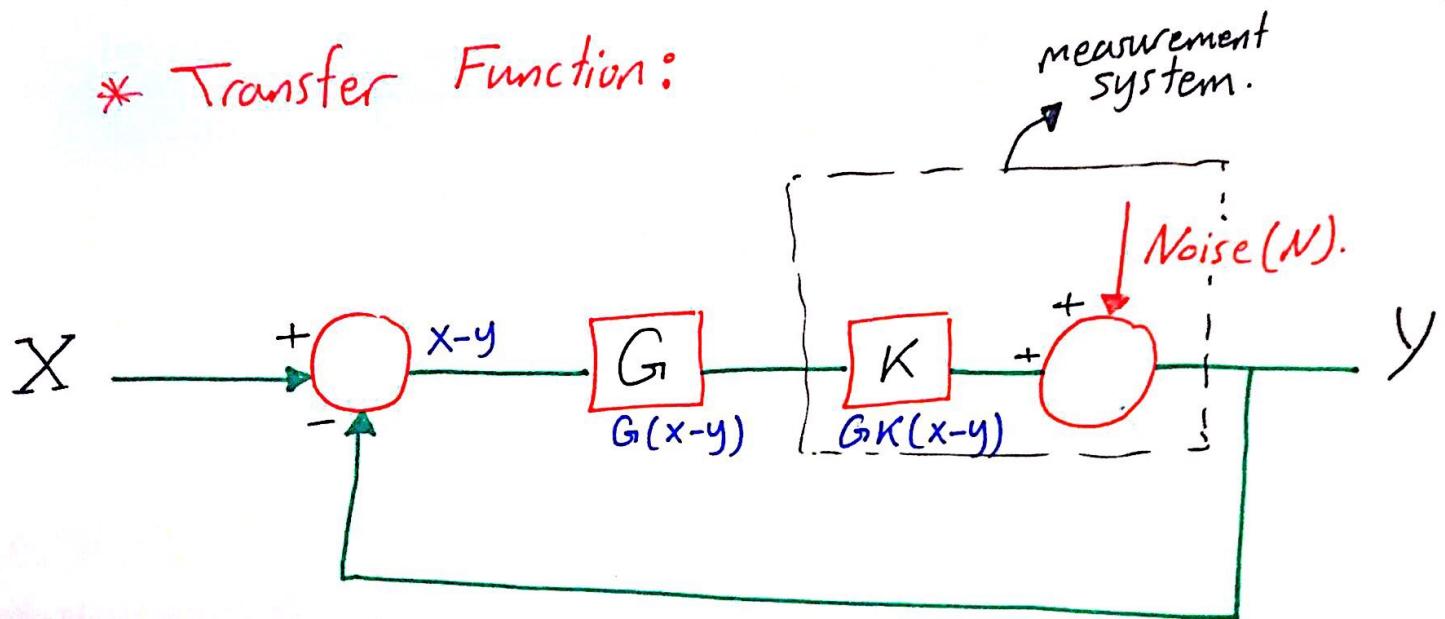

$$\Rightarrow y = (x - y)GK + N$$

$$\Rightarrow y = \frac{xGK}{1+GK} + \frac{N}{1+GK}$$

if G is very large:

\Rightarrow Eliminate the noise

$$y = x$$

Note:

with No
feedback


$$y = xGK + N$$

"open loop"
system


Note:

There is a Time Constant for the measurement.

* State Estimation:

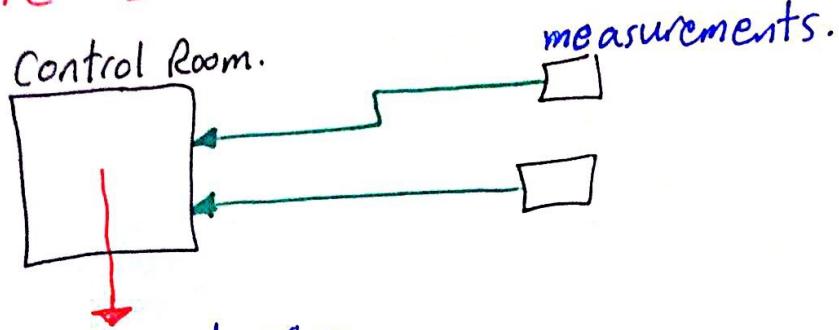

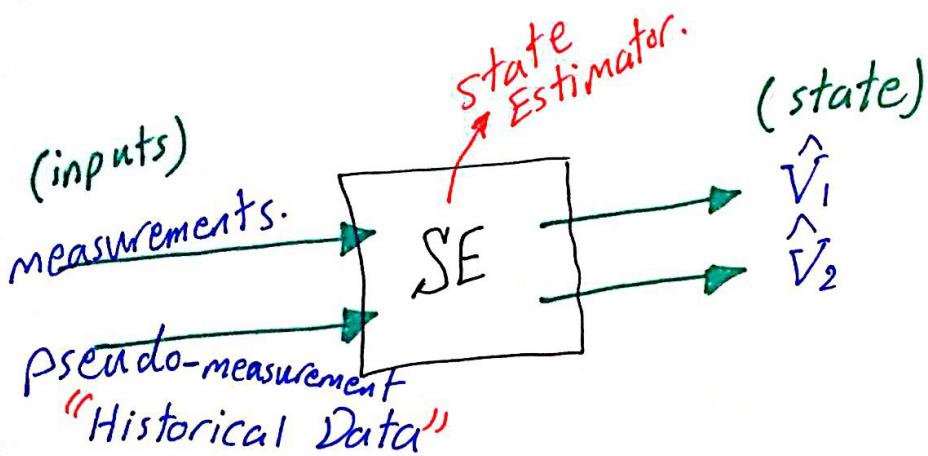- 1) Monitoring.
- 2) Decision-making algorithm.




$$\sigma^2 = \frac{1}{n} \sum_{\text{sample}} (x - \bar{x})^2$$

mean.


$\sigma \triangleq$ standard deviation.

Variance. measurement
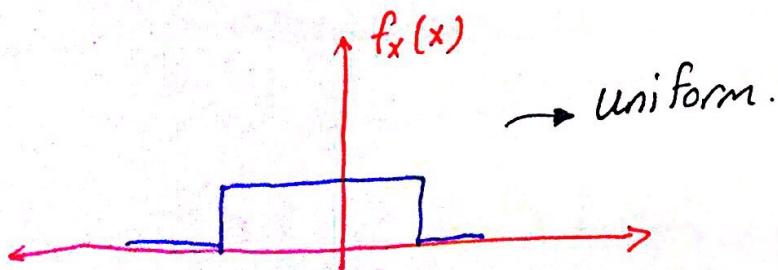
$$\left. \begin{array}{l} \text{mean} = \frac{1}{n} \sum x \\ \text{mean} = \sum x_i \Pr(x_i) \end{array} \right\}$$



Ex:

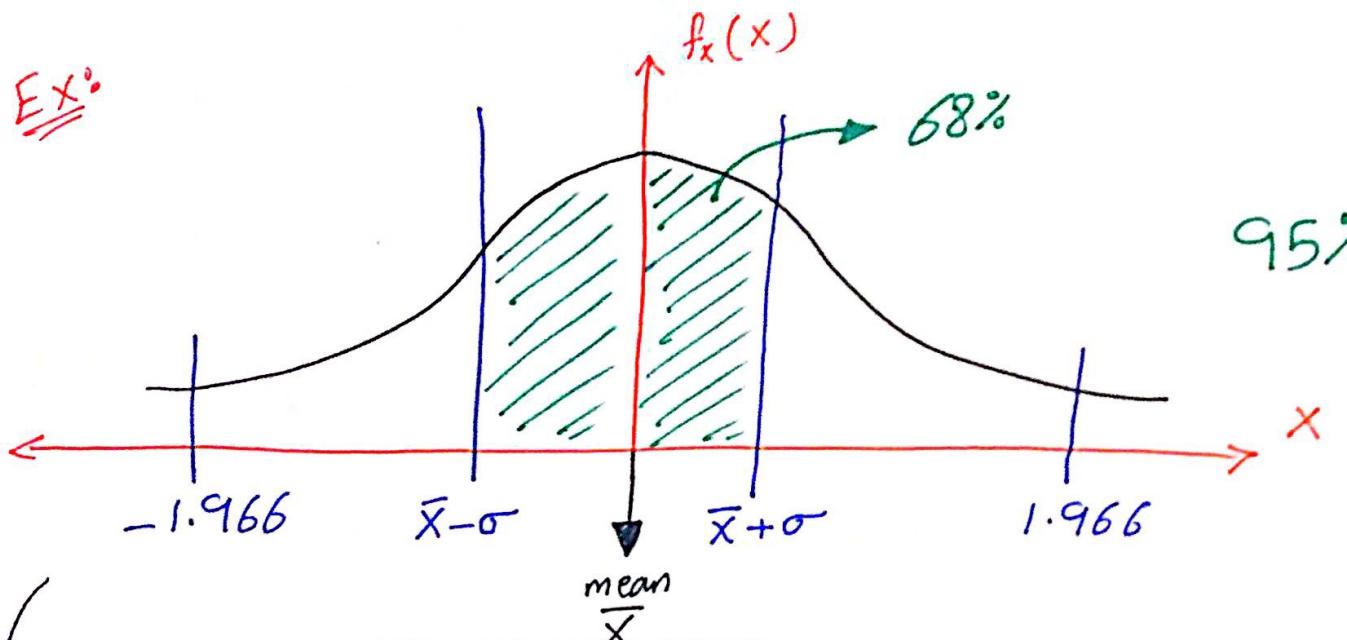

$$f_x(x) = \frac{1}{\sqrt{2\pi\sigma^2}} e^{-\frac{(x-\bar{x})^2}{2\sigma^2}}$$

$\Pr(\bar{x} - 1.966 \leq x \leq \bar{x} + 1.966) = 95\%$

$\Pr(\bar{x} - 6 \leq x \leq \bar{x} + 6) = 68\%$

* Pdf: "probability density function".

symbol → $f_x(x)$.

$$\Rightarrow \Pr(x_1 \leq x \leq x_2) = \int_{x_1}^{x_2} f_x(x) dx.$$

* cdf: "cumulative distribution function".

$$\Rightarrow F_x(x_0) = \Pr(x \leq x_0)$$

(→ it is called non decreasing).

$$\Rightarrow \int_{-\infty}^{x_0} f_x(x) dx.$$


(9)

$$F_X(x_0) = \Pr(X \leq x_0)$$

$$z_0 = \frac{x_0 - \text{mean}}{\sigma}$$

from table.

* How to find Z_0 from table:

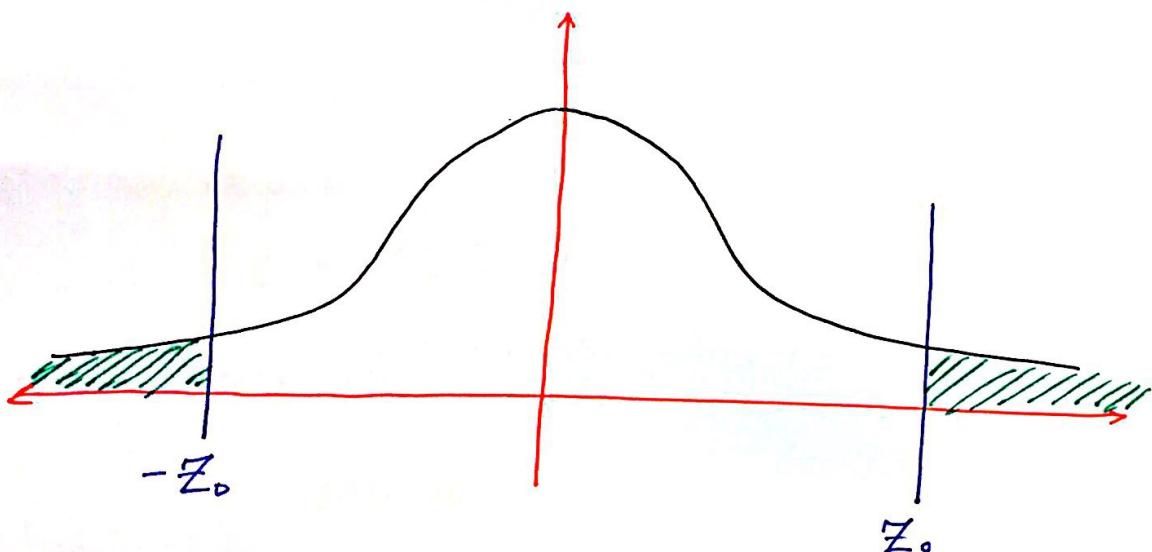


if we want to find $f(-z_0)$:

$$f(-z_0) = 1 - F(z_0)$$

Example: Slide 21

$$0.05\bar{x} = 23.5 = \sigma$$

part(1):

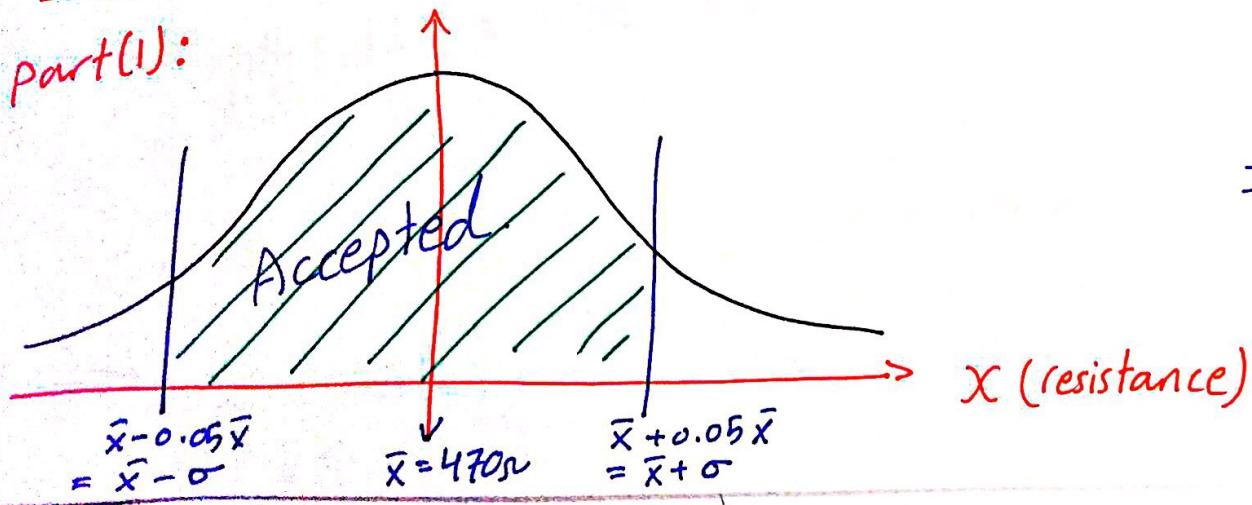

\Rightarrow accepted:

$$[\bar{x} - \sigma \leq x \leq \bar{x} + \sigma] = \underline{\underline{68\%}}$$

But assume we don't know that is $= 68\%$!!

$$\begin{aligned}\Rightarrow \Pr(\bar{x} - 0.05\bar{x} \leq x \leq \bar{x} + 0.05\bar{x}) \\ &= \Pr(x \leq \bar{x} + 0.05\bar{x}) - \Pr(x \leq \bar{x} - 0.05\bar{x}) \\ &= F_x(\bar{x} + 0.05\bar{x}) - F_x(\bar{x} - 0.05\bar{x})\end{aligned}$$

\Rightarrow Now from table:

$$Z = \frac{x - \text{mean}}{\sigma}$$

$$\Rightarrow F_Z\left(\frac{\bar{x} + 0.05\bar{x} - \bar{x}}{\sigma}\right) - F_Z\left(\frac{\bar{x} - 0.05\bar{x} - \bar{x}}{\sigma}\right)$$

substitute $\bar{x} = 470$, $\sigma = 23.5$

$$\text{so } \Rightarrow F_Z(1) - F_Z(-1) = 68\% \quad \text{Acceptance value.}$$

* For rejection:

$$\Pr(\text{rejection}) = 1 - 68\% = \underline{\underline{32\%}}$$

$$\Rightarrow 32\% * 10,000 = \boxed{3174} \quad \text{resistors will be rejected.}$$


Part(2):

$$\begin{aligned}\bar{x} &= 475 \text{ m} \\ \sigma^2 &= \frac{1}{N} \sum (x - \bar{x})^2\end{aligned}$$

cancel each other.
so standard deviation
doesn't change.

* Standard Error of the mean:

(11)

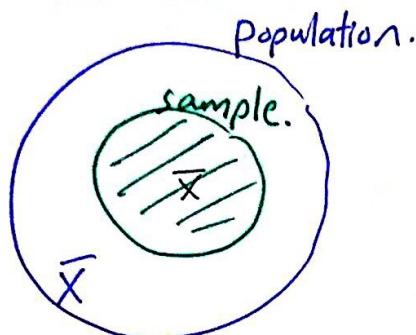


⇒ Confidence level.

2. 2	3. 25	68%
2. 5	3. 5	95%
2. 25	3. 75	99%

α = standard error of the mean.

$$\alpha = \frac{\sigma}{\sqrt{n}}$$

$x|_{\text{population}} = \alpha \pm x_{\text{mean}}$ under condition
confidence level 68%

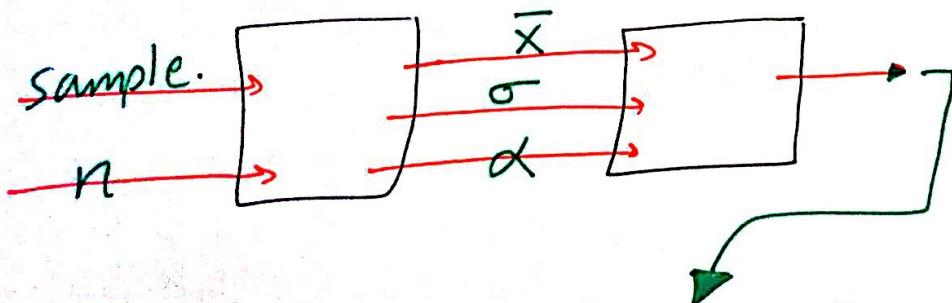

$$\bar{x} \pm \alpha \text{ (confidence level 68%)}$$

$$\bar{x} \pm 2\alpha \text{ (confidence level 95.4%)}$$

$$\bar{x} \pm 1.96\alpha \text{ (confidence level 95%)}$$

Example: slide (26)

$$\text{Sample : } \bar{x} = \frac{\sum x_i}{N} = \boxed{35.93}$$

$$\sigma_{n-1} = \sqrt{\frac{1}{N-1} \left[\sum_{i=1}^N (x_i - \bar{x})^2 \right]} \\ = \boxed{0.365}$$

$$\Rightarrow \alpha = \frac{\sigma}{\sqrt{n}} = \frac{0.365}{\sqrt{10}} = \boxed{0.115}$$

confidence level 95.4%

↳ we have $\bar{x} \pm 2\alpha$

so mean true value is:

$$\underline{\overline{35.93 \pm 2(0.115)}}$$

* Aggregation of Errors:

* Addition:

Assume two measurements with sum = u :

$$u = \underline{\overline{v}} + \underline{\overline{w}} \rightarrow \text{tolerance} \pm n\%$$

tolerance
 $\pm m\%$

Ex.

(13)

$$\text{Ex. } V = 10 \text{ volt.}$$

$$\omega = 5 \text{ volt.}$$

$$\Rightarrow u = v + \omega = 15 \text{ volt. (No error).}$$

with error :

$$\text{Given: } v = 10 \pm 10\% \quad \& \quad \omega = 5 \pm 10\%$$

for U_{\max} :

$$U_{\max} = 10 * 1.1 + 5 * 1.1 = 11 + 5.5 = \boxed{16.5} \text{ volt.}$$

for U_{\min} :

$$U_{\min} = 10 * 0.9 + 5 * 0.9 = \boxed{13.5} \text{ volt.}$$

* Multiplication:

$$u = v \cdot \omega (1 \pm (m+n))$$

Example : slide (32)

$$F = \underbrace{(E) \frac{Ad}{l}}_{\text{constant.}}$$


$$F = \Delta A \frac{\partial F}{\partial A} + \Delta d \frac{\partial F}{\partial d} + \Delta l \frac{\partial F}{\partial l}$$

$$\left| \frac{\Delta F}{F} \right|_{\min} = \frac{\Delta A}{A} + \frac{\Delta l}{l} + \frac{\Delta d}{d}$$

$$\left| \frac{\Delta F}{F} \right|_{\max} = - \frac{\Delta A}{A} - \frac{\Delta l}{l} - \frac{\Delta d}{d}$$

Example: slide (36)

(14)

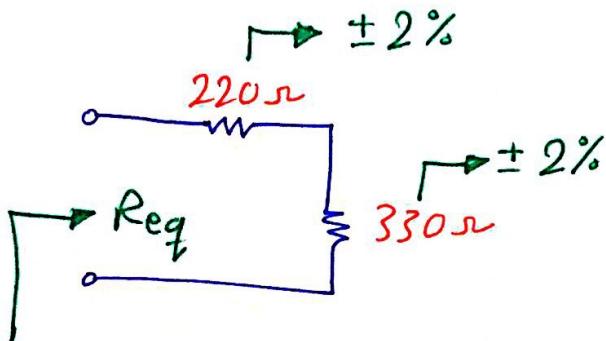


* using Limiting error:

$$\frac{220 * 0.02}{220} + \frac{330 * 0.02}{330}$$

$$220(1+2\%) + 330(1+2\%) \\ = \underline{\underline{561\ \Omega}}$$

* Using Probable error:

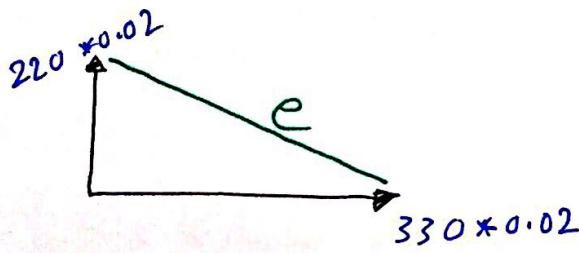

probable error:

$$e = \sqrt{(220 * 0.02)^2 + (330 * 0.02)^2} \\ = \underline{\underline{7.93\ \Omega}}$$

$$\text{for } R_{\text{series}} = 220 + 330 = 550\ \Omega$$

as a relative error:


$$\text{Tolerance} = \frac{7.93}{550} * 100\% = \underline{\underline{1.44\%}}$$

$$\text{so } R = 550 \pm (1.44\% * 550) = \underline{\underline{557.92\ \Omega}}$$

** The value in Probable error best than in Limiting error:
since Limiting error always take the worst case that both measurements had errors in same time.


※ State Estimation:

(15)

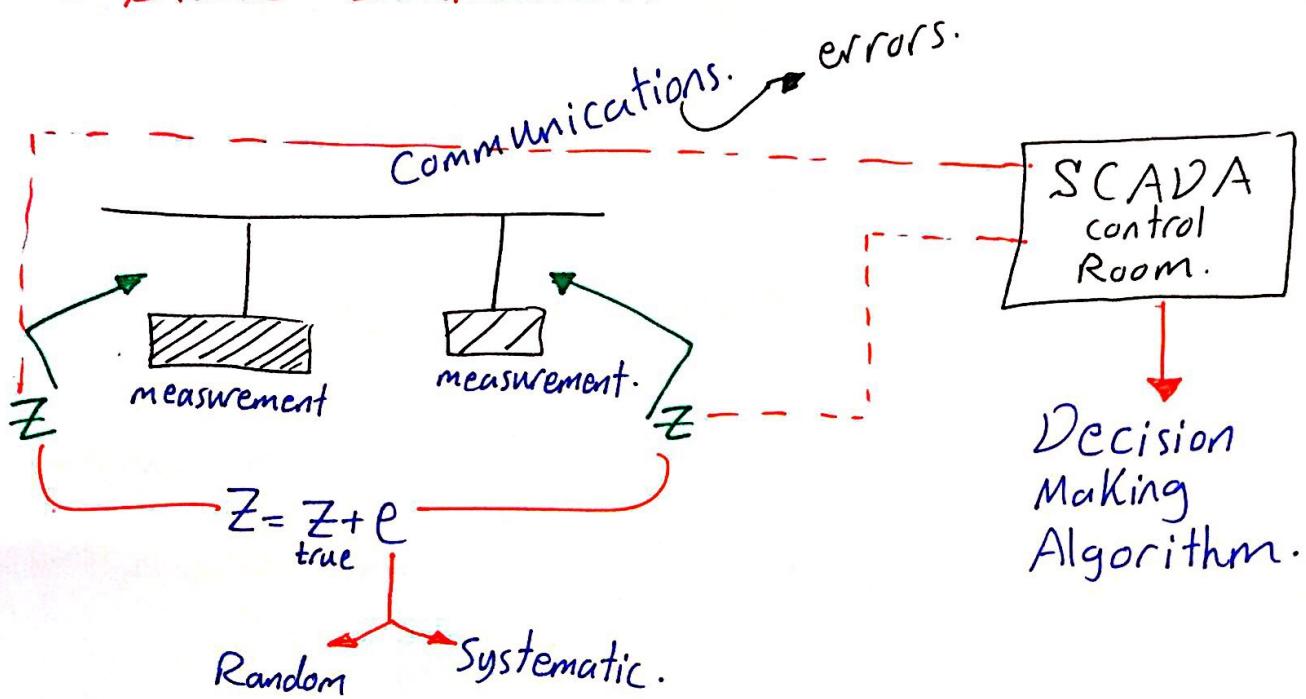

\Rightarrow Know values of system states
(voltages & angles at each node)

↳ from them you find current P, Q .

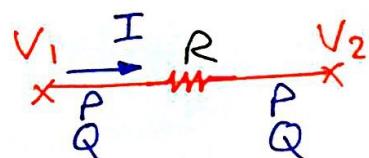

① ** errors in measurements
in measurements/comms/SCADA.

② ** Not enough real measurements.

$$Z_i = h_i(\bar{x}) + c$$

states [Unknown.]

measurements [Known.]

mathematical model.

error [Unknown.]

(16)

* Random errors (assumptions)

- Gaussian.
- measurements are independent.

* Weighted Least square error: (WLSE)

\Rightarrow minimization:

$$\min \sum_{i=1}^m \frac{[z_i - h(x)]^2}{\sigma_i^2}$$

→ emphasis trusted measurements.


\Rightarrow we solve it by Numerical Analysis

"Newton-Raphson - Method"

* Pseudo measurements \Rightarrow Historical Data.

* Linear Least Squares estimation:

Example:

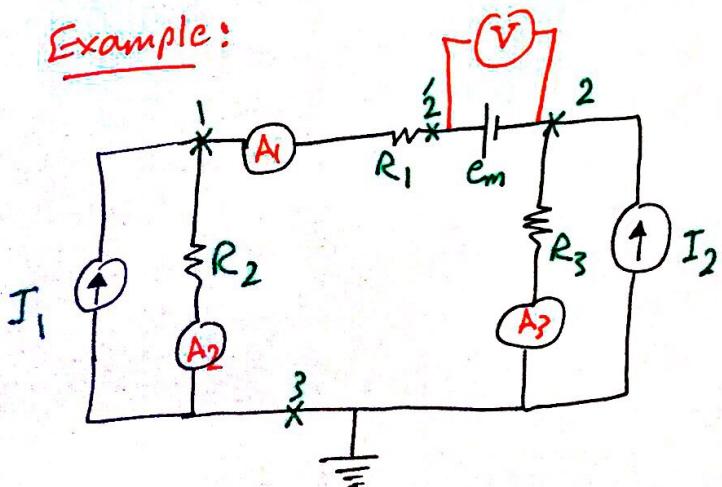

I_1, I_2, e are all unknown
Given $R_1 = R_2 = R_3 = 1 \Omega$

Measurements:

- $A_1: i_{12} = 1 \text{ A}$.
- $A_2: i_{31} = -3.2 \text{ A}$.
- $A_3: v_{23} = 0.8 \text{ V}$.
- $V: e = 1.1 \text{ Volt}$.



states $\begin{bmatrix} V_1 \\ V_2 \\ e_m \end{bmatrix}$??

$$Z_i = h(x) \rightarrow \begin{bmatrix} V_1 \\ V_2 \\ e \end{bmatrix}$$

* $i_{12} = \frac{V_1 - V_2'}{R_1} \Rightarrow V_2' = e_m + V_2$

$$\Rightarrow i_{12} = \frac{V_1 - e_m - V_2}{1} \Rightarrow i_{12} = V_1 - e_m - V_2 = 1 \quad \boxed{1}$$

* $i_{31} = \frac{V_3 - V_1}{1} = -3 \cdot 2 = 0 - V_1 \Rightarrow -V_1 = -3 \cdot 2 \quad \boxed{2}$

* $i_{23} = \frac{V_2 - V_3}{1} \Rightarrow \frac{V_2 - 0}{1} = 0 \cdot 8 \Rightarrow V_2 = 0 \cdot 8 \quad \boxed{3}$

* $e = 1.1 \text{ V} \quad \boxed{4}$

As a matrix:

$$\begin{bmatrix} 1 & -1 & -1 \\ -1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ e \end{bmatrix} = \begin{bmatrix} 1 \\ -3 \cdot 2 \\ 0 \cdot 8 \\ 1.1 \end{bmatrix}$$

$$A \cdot \underline{\underline{X}} = Z$$

$\hookrightarrow ??$
since 4 equations & 3 variables.
 \Rightarrow "Best Solution"

$$\text{Error} = Z - AX$$

↳ minimize WLSE.

$$A \underset{\overline{X}}{X} = b$$

measurements.

→ Best estimate.

⇒ minimize error between measurements & values resulting from the model.

$$A_1 = IA + C$$

$$\Rightarrow e = IA - (h(x))$$

model.

$$[\text{Error}] = \begin{bmatrix} 1 \\ -3.2 \\ 0.8 \\ 1.1 \end{bmatrix} - \left\{ \begin{bmatrix} 1 & -1 & 1 \\ -1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ e_m \end{bmatrix} \right\} = \begin{bmatrix} 1 - V_1 + V_2 + e_m \\ -3.2 + V_1 \\ 0.8 - V_2 \\ 1.1 - e_m \end{bmatrix}$$

WLSE

$$\Rightarrow \text{Min } (1 - V_1 - V_2 + e_m)^2 + (-3.2 + V_1)^2 + (0.8 - V_2)^2 + (1.1 - e_m)^2$$

$$V_1, V_2, e_m$$

or use the following relation:

$$X = G^{-1} A^T b$$

Gain Matrix. $G = A^T \cdot A$.


$$\Rightarrow X = \begin{bmatrix} 3.125 \\ 0.875 \\ 1.175 \end{bmatrix} \begin{matrix} V_1 \\ V_2 \\ e_m \end{matrix}$$

$$\times \text{ residual: } r = b - AX = \begin{bmatrix} 1 \\ -3.2 \\ 0.8 \\ 1.1 \end{bmatrix} - \begin{bmatrix} 1 & -1 & 1 \\ -1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 3.125 \\ 0.875 \\ 1.175 \end{bmatrix}$$

$$= \begin{bmatrix} -0.075 \\ -0.075 \\ -0.075 \end{bmatrix}$$

meters:

* Basic DC ammeter:

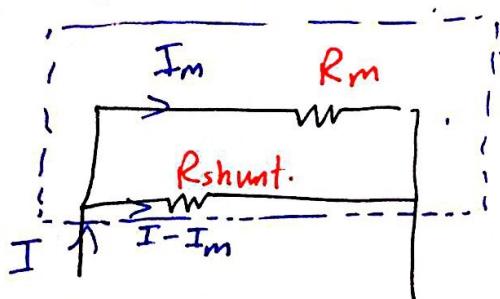

$$I_m R_m = R_{\text{shunt}} (I - I_m)$$

$$R_{\text{shunt}} = \frac{I_m R_m}{I - I_m} = \frac{R_m}{\frac{I}{I_m} - 1}$$

$$\Rightarrow R_{\text{shunt}} = \frac{R_m}{n - 1}$$

Example: slide() :


$$R_m = 100 \Omega$$

$$I_m = 1 \text{ mA}$$

$$I = 0 - 10 \text{ mA.}$$

$$\Rightarrow R_{\text{shunt}} = \frac{100}{\frac{10 \text{ mA}}{1 \text{ mA}} - 1} = \underline{\underline{11.11 \Omega}}$$

* Multiple Range Ammeter:

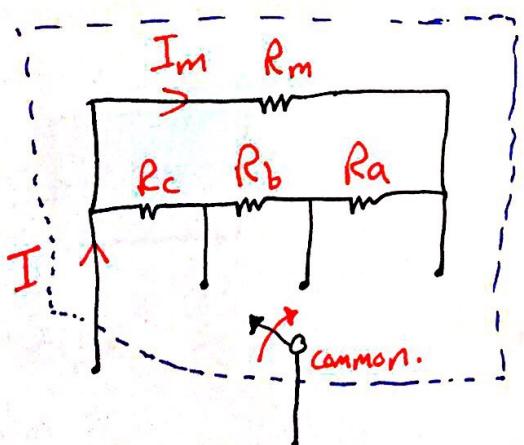


Example: slide() :

$$I_m = 50 \text{ mA.}$$

$$R_m = 2400 \Omega$$

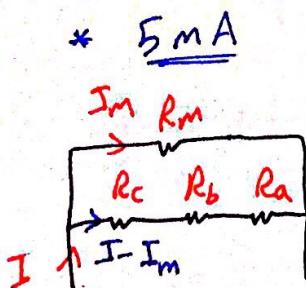3 ranges \rightarrow 5mA
 \rightarrow 50mA
 \rightarrow 500mA




$$R_a + R_b + R_c = \frac{I_m R_m}{I - I_m} = \frac{50 \text{ mA} \times 2400 \Omega}{50 \text{ mA} - 5 \text{ mA}} = \boxed{1}$$




(20)

* 50mA.

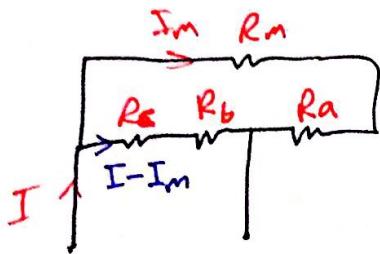

$$\Rightarrow \frac{I_m (R_m + R_a)}{I - I_m} = R_c + R_b \quad \boxed{2}$$

* 500 mA.



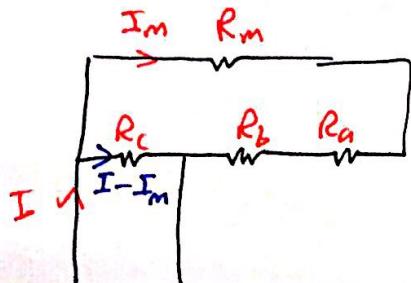


$$\Rightarrow \frac{I_m (R_m + R_a + R_b)}{I - I_m} = R_c \quad \boxed{3}$$

solving 3 equations:

$$\begin{aligned} R_a &= 21.81 \Omega \\ R_b &= 0.94 \Omega \\ R_b &= 2.18 \Omega \end{aligned}$$

* Ammeter Loading Effect:

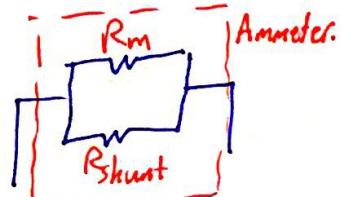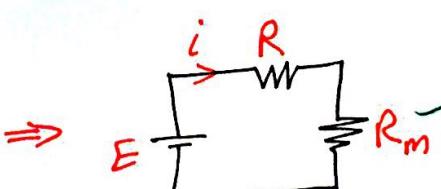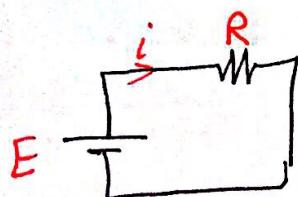

$$i_{\text{expected}} = \frac{E}{R}$$


$$i_{\text{measured}} = \frac{E}{R + R_m}$$

Ammeter
Resistance.


$$\text{Insertion Error} = \frac{i_{\text{expected}} - i_{\text{measured}}}{i_{\text{expected}}} * 100\%$$

Example: slide ():

(21)

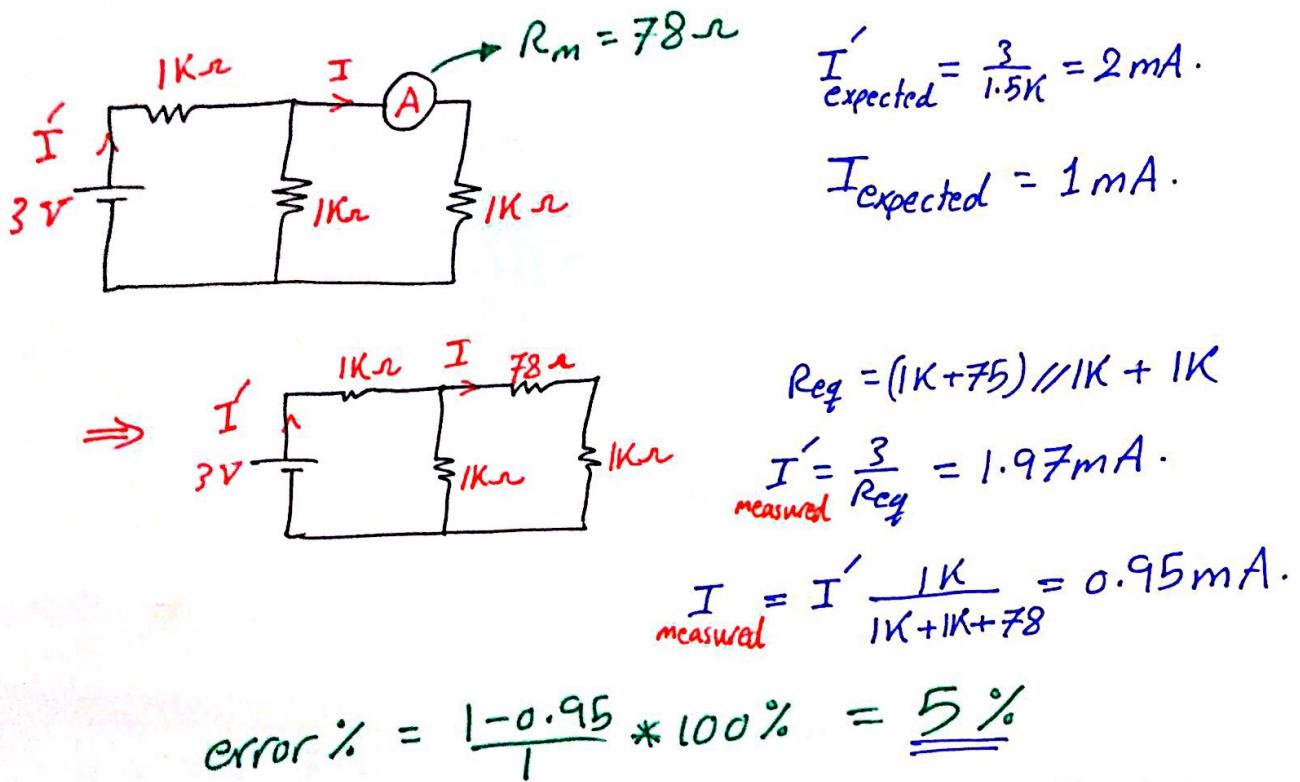

*Basic DC voltmeters

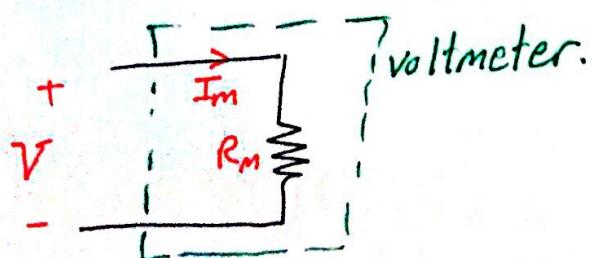


$$V_{\text{full scale deflection}} = I_m R_m$$

↳ maximum that voltmeter can handle.


* To extend the $V_{\text{full scale deflection}}$ we have to add R_s series with R_m .

Example.
→

Example: slide():

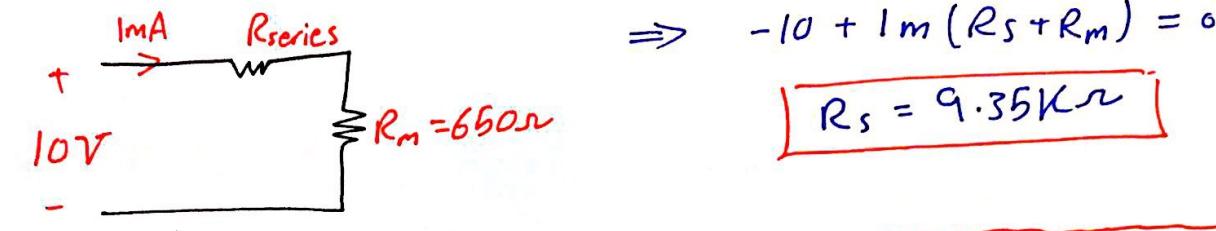

Example: slide():

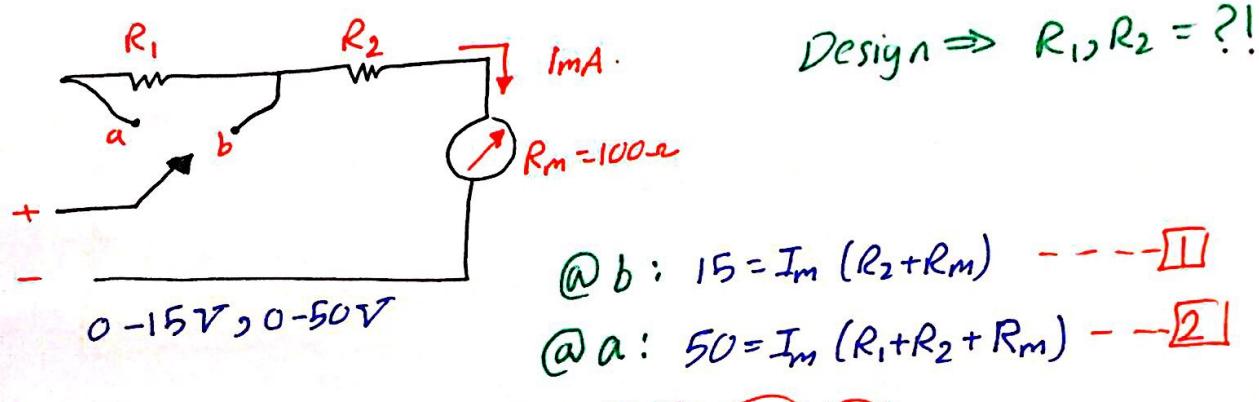

solving:

$$R_1 = 35\text{ k}\Omega$$

$$R_2 = 14.9\text{ k}\Omega$$

* Sensetivity:

$$\text{Sensitivity} = \frac{1}{I_{\text{fullscale deflection}}} \left(\frac{\text{V}}{\text{V}} \right) \Rightarrow S = \frac{1}{I_m}$$

* for the last example what is the sensitivity?

$$S = \frac{1}{I_m} = \frac{1}{I_m} = \boxed{1000 \text{ }\Omega/\text{V.}}$$


$$\begin{aligned} \text{Total series resistance} &= 15 * 1000 = 15\text{k}\Omega \quad | 15\text{ V} \\ " " " &= 50 * 1000 = 50\text{k}\Omega \quad | 50\text{ V} \end{aligned}$$

$$15\text{ k} = R_2 + R_m$$

$$50\text{ k} = R_1 + R_2 + R_m$$

solving, it will give same results.

Example: slide (58):

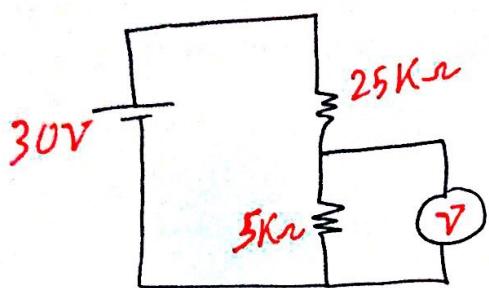


meter A:

$$R_{voltmeter} = 10 * \frac{1k\Omega}{V}$$

$$= 10k\Omega$$

represent R_{series} & R_m

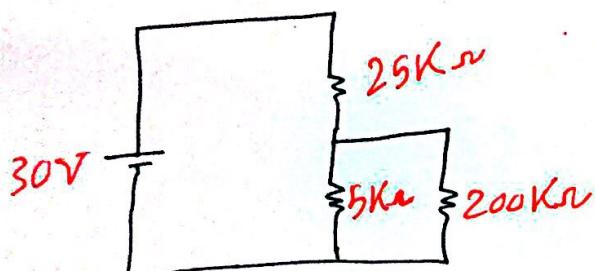
$$\begin{array}{c} R_{series} \\ \parallel \\ R_m \end{array}$$



meter B:

$$R_V = 10 * \frac{20k\Omega}{V} = 200k\Omega$$


find voltage by voltage division.

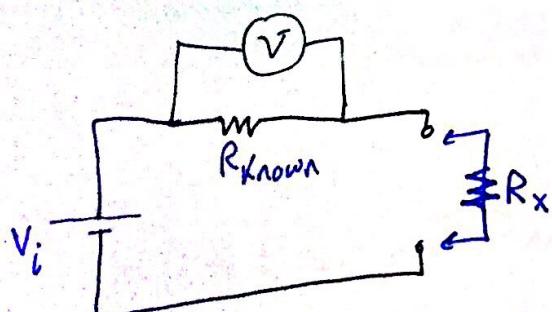

when $R_x = 0$

voltmeter will read maximum voltage. (full scale).

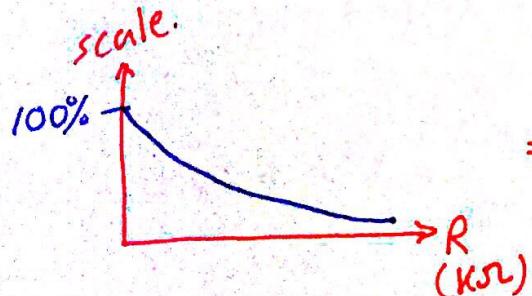
as long as R_x increasing voltmeter reading decrease.



\Rightarrow This type called:

Reversed - Non linear scale.

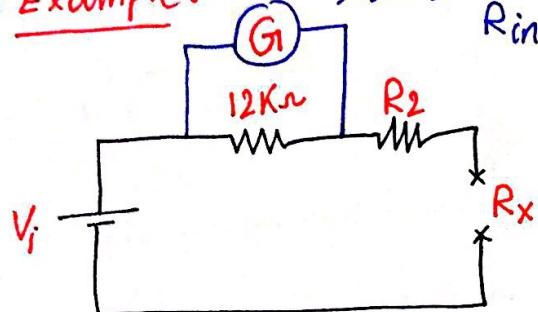* Example: $50\mu A$, Full scale deflection
 $R_{in} = 2400 \Omega$




Find V_i, R_2 ?

under these conditions:
→ Full scale deflection, $R_x = 0$
→ 20% Full scale deflection
 $R_x = 200 \text{ k}\Omega$.

$$\Rightarrow \frac{50\mu A}{2400 \Omega} \quad \text{full scale deflection voltage} = 50\mu A * 2400 = \underline{\underline{120mV}}$$
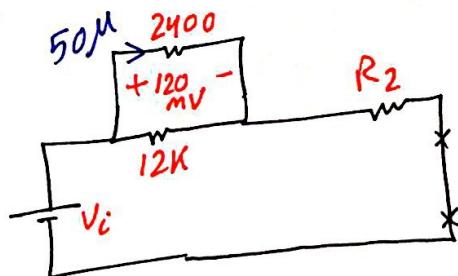
$$120mV = V_i * \frac{12K // 2400}{(12K // 2400) + R_2}$$




$$\Rightarrow 240 + 0.12R_2 = 2000V_i \quad \boxed{1}$$

Now:

20% full scale deflection :
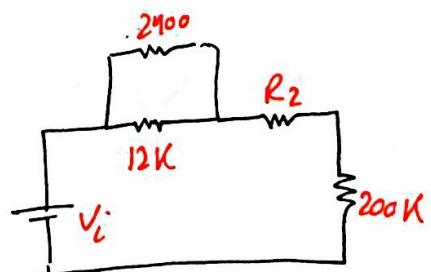
$$20\% (2400 * 50\mu A) = \underline{\underline{0.024}} \text{ volt.}$$



$$\Rightarrow 0.024 = V_i \cdot \frac{(12K // 2400)}{(12K // 2400) + R_2 + 200K}$$

$$\Rightarrow 484.8 + 0.024R_2 = 2000V_i \quad \boxed{2}$$


Solving $\boxed{1}$ & $\boxed{2}$:

$R_2 = 48K\Omega$, $V_i = ? \text{ volt.}$

continue.

Now find the deflection when $\{ R_x = 450 \text{ k}\Omega :$
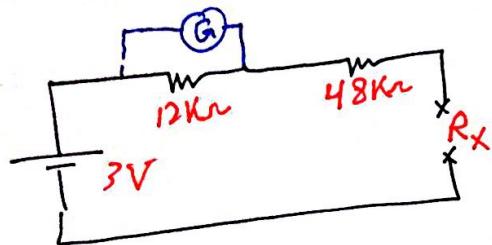
$$\begin{cases} R_x = 450 \text{ k}\Omega \\ R_x = 75 \text{ k}\Omega \\ R_x = 50 \text{ k}\Omega \end{cases}$$





full scale deflection = 120 mV.

$$\frac{\% d}{\% d} * 120m = \frac{3 * (2400//12K)}{(2400//12K) + 48K + \underline{\underline{450K}}} \\ \underline{\underline{75K}} \\ \underline{\underline{50K}}$$


Answers: $450 \text{ k}\Omega \rightarrow 10\%$
 $75 \text{ k}\Omega \rightarrow 40\%$
 $50 \text{ k}\Omega \rightarrow 50\%$ \Rightarrow Test for the slope to know if it is linear or Not.

* AC voltmeter:

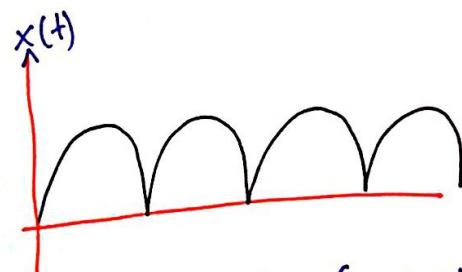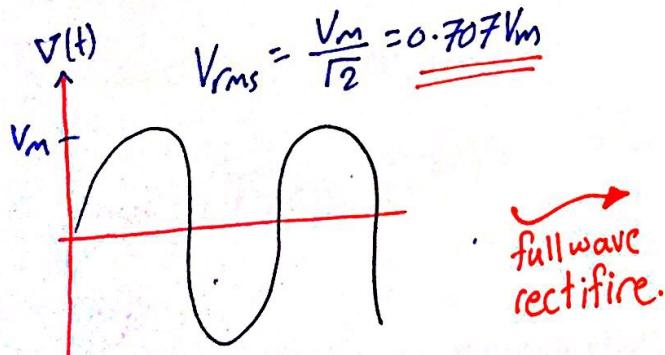

$$\text{average} = \frac{1}{T} \int x(t) dt \\ = \underline{\underline{0.636 V_m}}$$

Example:

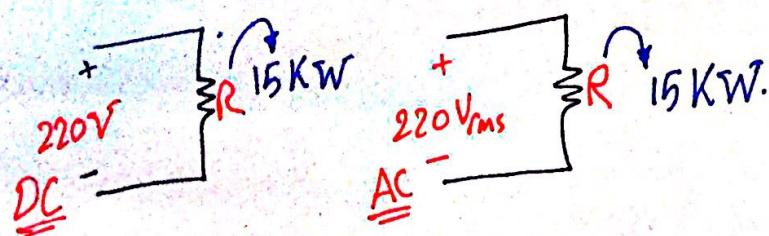

\Rightarrow same rated power in DC & AC.

* AC signal: $V_{rms} = 0.707 V_m$

* Half-wave-Rectifier: $V_{av.} = 0.5 V_m$


* Full-wave-Rectifier: $V_{av} = 0.636 V_m$

* Average for any signal: $\frac{1}{T} \int x(t) dt$

* Safe Factor (SF) = $\frac{V_{rms}}{V_{avg}}$

↳ for pure sinusoidal: $SF = \frac{0.707 V_m}{0.636 V_m}$

$$\Rightarrow SF = 1.1$$

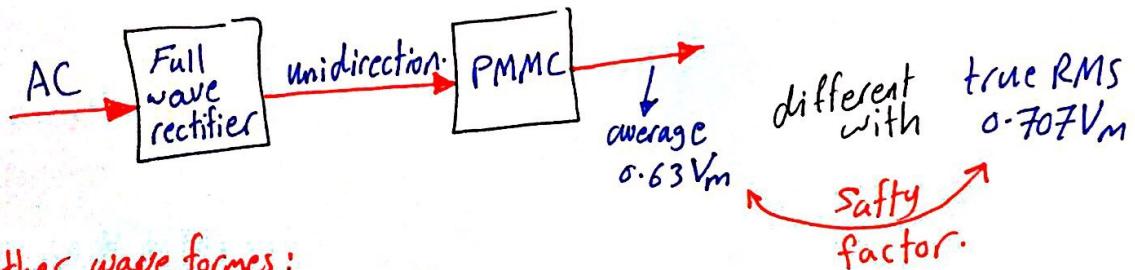

* for other waveforms:

$$\text{Correction Factor (CF)} = \frac{SF_{\text{waveform}}}{SF_{\text{sinusoidal}}}$$

* if we have: Accuracy = 3% Full scale.

$$\text{Full scale} = 10 V$$

$$\Rightarrow \text{Accuracy} = 10 * 0.03 \\ = 0.3 \text{ Volt.}$$


$\Rightarrow \text{reading} = 9 V \Rightarrow 9 \pm 0.3 V$ better than
 $\text{reading} = 1 V \Rightarrow 1 \pm 0.3 V$

the best is to choose the full scale close to the expected readings.

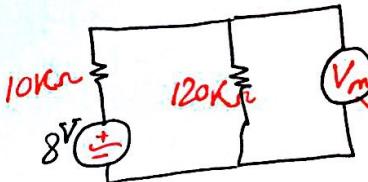Example: slide (73) : Find V_{measured} % ?

→ $V_m \text{ o/c.}$

$$V_{\text{true voltage}} (\text{ideal}) = 8 * \frac{120K}{120K + 10K} = 7.38 \text{ Volt.}$$



Analogue (0-10V)
sensitivity = $10 \frac{\text{K}\Omega}{\text{V}}$

calibrated
to read V_{rms}
for sinusoidal.

* measured value:

$$V_{\text{rms}} = 8 \text{ } \boxed{= 8} \quad \text{parallel branches: } \frac{10K\Omega}{V} \times 10V = 100K\Omega$$

$$\Rightarrow V_{\text{measured}} = \frac{8 * (120K // 100K)}{10K + (120K // 100K)} = 6.76 \text{ volt.}$$


$$\% \text{ error} = \frac{6.76 - 7.38}{7.38} * 100\% = -8.4\%$$

Example: slide (73) :

1) find V_{rms} ?

2) $V' \rightarrow$ $V_{\text{measured}} = ?!$
calibrated to measure sinusoidal signal.

3) error in the RMS reading ?

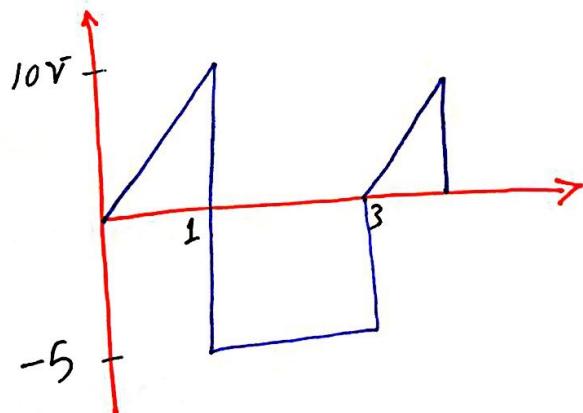

solution.



Solution:

$$1) V_{rms} = \sqrt{\frac{1}{3} \left[\int_0^1 (10t)^2 dt + \int_1^3 (-5)^2 dt \right]} = 5.27 \text{ volt.}$$

$$2) \begin{array}{c} \text{Graph of } V(t) \\ \text{Time } t \text{ axis} \\ \text{Voltage } V \text{ axis} \\ \text{At } t=1, V=10 \\ \text{At } t=3, V=5 \end{array} \Rightarrow V_{average} = \frac{1}{3} \left[\int_0^1 10t dt + \int_1^3 5 dt \right] = 5 \text{ volt.}$$

$$\Rightarrow V_{measured} = 5 * SF = 5 * 1.11 = 5.55 \text{ volt.}$$

we multiply by SF since the voltmeter calibrated to measure sinusoidal signal.

$$3) \% \text{ error} = \frac{5.55 - 5.27}{5.27} * 100\% = 5.31\%$$

Example :

Need the correction factor given that

$$V_{rms} = 28.87 V, V_{average} = 25 V, \text{ correction factor} = ?$$

(rectified)
signal

$$28.87 = 25 * 1.11 * \text{correction factor}$$

$$\Rightarrow CF = 1.04$$


also we could use $CF = \frac{SF_{\text{waveform}}}{SF_{\text{sinusoidal}}} \rightarrow \frac{V_{rms}}{V_{avg}}$

*Digital multimeter:

(29)

the type could be $4\frac{1}{2}$ digit.

↳ This means:

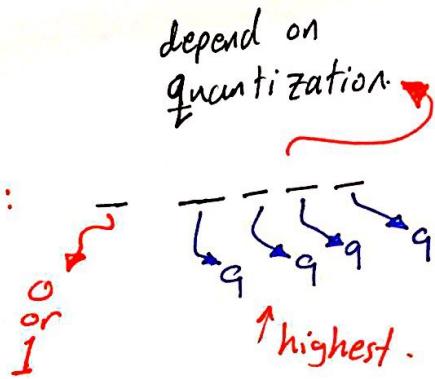

$$\text{Accuracy} = \pm 0.1\% \pm \frac{1}{L}$$

* LSD.

↳ Least significant digit.

*For the resolution:

as long as we increase the range \Rightarrow it will cause the resolution to be worse.

** 4½ digit

count 1.9999 (decimal point)

if max voltage < 2 :

$$\Rightarrow 1.9999 \left(\begin{smallmatrix} \text{max} \\ \text{display} \end{smallmatrix} \right)$$

↳ resolution:

$$\Rightarrow 0.0001 = \underline{\underline{100}} \mu\text{V}$$

if we want to display 2:

$$02.000 \Rightarrow \text{resolution} = 0.001 = \underline{\underline{1}} \text{ mV}$$

so increasing in range cause a decreasing in resolution.

3½ digit reads 20 Volt:

$$\begin{array}{ccccccc} 0 & 2 & 0. & \underline{\underline{=}} \\ \text{0,1} & \text{w} & \text{0} \rightarrow 9 \end{array} \quad \text{resolution} = 0.1 \text{ volt.}$$

Example : slide(81) :

(30)

4 1/2 digit.



reading: 1.8000

Accuracy: $(\pm 0.05\% + 1)$

$$\begin{aligned} * \text{Range: } & \max = 1.8000 * \frac{1.05}{100} = \underline{\underline{1.8009V}} \\ & \min = 1.8000 * \frac{0.95}{100} = \underline{\underline{1.7991V}} \end{aligned}$$

$$\begin{array}{c} \pm 0.05\% + 1 \\ \hline 1 \Rightarrow \text{LSD.} \\ \hline 1.8000 \end{array}$$

LSD = 0.0001

we add it to the max.
we subtract it from the min.

* expected readings:

$$1.8009 + 0.0001 = \underline{\underline{1.8010V}}$$

$$1.7991 - 0.0001 = \underline{\underline{1.7990V}}$$

Example : slide(83) :

4 digit:



reading: 1.8 V.

Accuracy: $\pm 0.1\% + 5$

Range: 1000 V.

need it:
 $\underline{\underline{< 1000V}}$

max display: 999.9

resolution = 0.1

0.1% * 1.8 almost zero.

$$\Rightarrow 0.1 * 5 = \underline{\underline{0.5V}}$$

$$\begin{aligned} \text{range: } & 1.8 + 0.5 = 2.3 \\ & 1.8 - 0.5 = 1.3 \end{aligned}$$

$$\underline{\underline{1.3 \rightarrow 2.3V}}$$

* End of first Material. *

Summary "First"

* Accuracy:

$$\text{accuracy} = A\%$$

$$\text{True} = \text{measured} \pm A\% * \text{range}$$

$$*\text{resolution: } = \frac{\text{full scale}}{\# \text{of bits}}$$

* Gaussian Curve:

$$f_x(x) = \frac{e^{-\frac{(x-\bar{x})^2}{2\sigma^2}}}{\sqrt{2\pi\sigma^2}}$$

* standard error of mean:

$$\alpha = \frac{\sigma}{\sqrt{n}} \left\{ \begin{array}{l} \bar{x} \pm \alpha \text{ (68%)} \\ \bar{x} \pm 1.96\alpha \text{ (95%)} \\ \bar{x} \pm 2\alpha \text{ (95.4%)} \\ \bar{x} \pm 3\alpha \text{ (99.7%)} \end{array} \right\}$$

* limiting error:

$$\begin{aligned} \text{Addition: } u &= \overbrace{v}^{n} + \overbrace{w}^{m} \\ \Rightarrow u &= v*(1 \pm n) + w(1 \pm m) \end{aligned}$$

Subtraction:

$$u = v*(1 \pm n) - w(1 \pm m)$$

multiplication & division:

$$u = v; w \cdot (1 \pm (m+n))$$

* precision:

$$\boxed{1} \quad \sigma^2 = \frac{\sum (x - \bar{x})^2}{N \text{ or } (N-1)}$$

$$\boxed{2} \quad |\max - \text{mean}|$$

$$*\text{Error} = \frac{\text{real-measured}}{\text{real}} * 100\%$$

$$*\text{pdf: } \Pr(x_1 \leq x \leq x_2) = \int_{x_1}^{x_2} f_x(x) dx.$$

$$*\text{cdf: } \Pr(x \leq x_0) = \int_{-\infty}^{x_0} f_x(x) dx.$$

$$\hookrightarrow Z_0 = \frac{x_0 - \text{mean}}{\sigma}$$

* Probable error:

Addition:

$$u = v + w \pm \sqrt{(nv)^2 + (mw)^2}$$

Subtraction:

$$u = v - w \pm \sqrt{(nv)^2 + (mw)^2}$$

Division & multiplication:

$$u = v; w * \left(1 \pm \sqrt{m^2 + n^2}\right)$$

WLSE:

$$Z_i = h_i(x) + e$$

$$\min \sum_{i=1}^m \frac{[Z_i - h_i(x)]^2}{\sigma_i^2}$$

⇒ How to find X !?

$$X = G^{-1} A^T b$$

$$G^{-1} = A^T \cdot A$$

* Residual: $r = b - A \cdot X$

* DC ammeter:

$$R_{shunt} = \frac{R_m}{\frac{I}{I_m} - 1}$$


* Ammeter loading effect:

$$\text{insertion error} = \frac{I_{\text{expected}} - I_{\text{measured}}}{I_{\text{expected}}} * 100\%$$

* sensitivity:

$$S = \frac{1}{I_m}$$

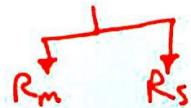Total Series Resistance = sensitivity * full voltage Range.



* full-rectified signal:

m

$$V_{avg} = 0.636 V_m$$

for sinusoidal:

$$V_{rms} = 0.707 V_m$$

* Half-rect:

$$V_{avg} = 0.3 V_m$$

form factor

* Safe. factor:

$$SF = V_{rms}/V_{avg}$$

for sinusoidal $SF = 1.11$

* Correction Factor:

$$CF = \frac{SF_{\text{waveform}}}{SF_{\text{sinusoidal}}}$$

* error: $= \frac{1 - CF}{CF}$

* Error:

$$e = \frac{V_{avg} - V_{rms}}{V_{rms}} * 100\%$$

$$\boxed{\begin{aligned} V_{ind} &= SF * V_{meas.} \\ V_{ind} * CF &= V_{rms} \end{aligned}}$$


* Triangular: full-rec:

$$V_{avg} = 0.5 V_m, SF = 1.155$$

$$V_{rms} = 0.577 V_m$$

*Analogue & Digital:

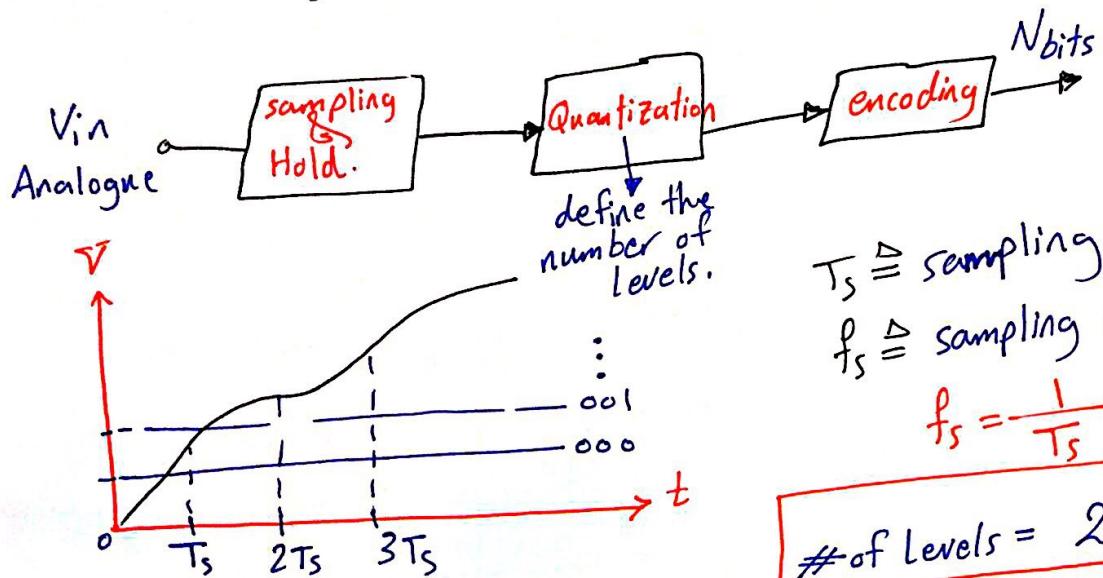Basic for digital \Rightarrow (ADC) analogue to digital converter.



$T_s \triangleq$ sampling Time.
 $f_s \triangleq$ sampling frequency.


$$f_s = \frac{1}{T_s} \text{ Hz.}$$

#of Levels = 2^N

step size = $\frac{V_{max} - V_{min}}{\text{#of levels}}$
 "Resolution"

Quantization Error = $\frac{\Delta}{2}$
 $V_{in} = \frac{V_{ref}}{2^N} * R$ digital code.


Example:

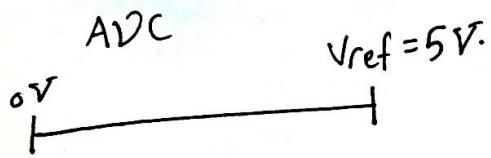

3 bits \Rightarrow 8 Levels.

#of bits = 3.

$$V_{in} = ?$$

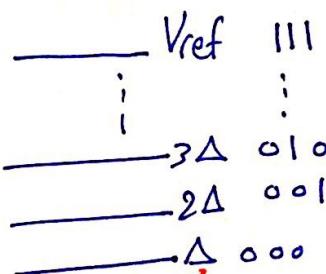

$\Delta = \text{step size} = \frac{V_{ref}}{2^N}$
 resolution.

Max Quantization error = $\frac{\Delta}{2}$

Quantization error % = $\frac{\Delta/2}{V_{full\ scale}} * 100\% = \frac{\left(\frac{V_{full\ scale}}{2^N}\right)/2}{V_{full\ scale}} * 100\%$

Quantization error % = $\frac{1}{2^{N+1}} * 100\%$

Example: slide (89):

(32)

$$800 \text{ mV} \rightarrow 150 \text{ mV}$$

\downarrow ADC code


80 150

$\Delta = ??$

$800 \text{ mV} = 80 \Delta$
 $\Delta = 10 \text{ mV}$

* Ramp-Type Digital Voltmeter:

"Voltage to Time Conversion".

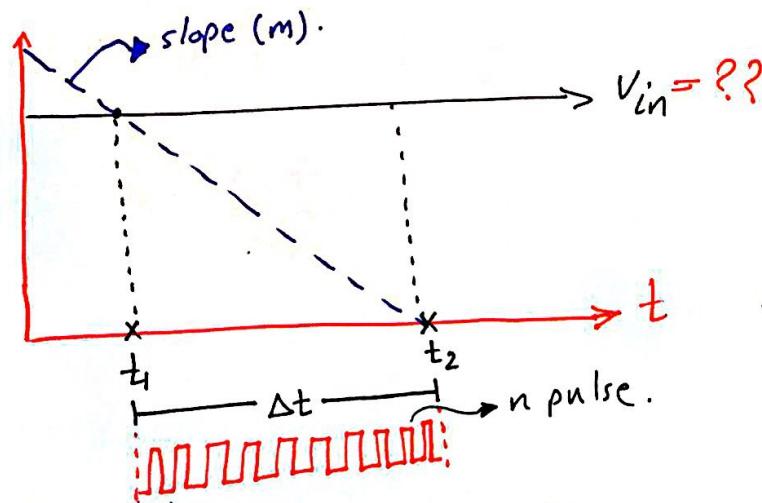

$$V(t) = V_o - mt$$

@ t_1 :

$$V_{in} = V_o - mt_1 \dots \text{I}$$

@ t_2 :

$$V_{in} = V_o - mt_2 = 0 \dots \text{II}$$


from I & II:

$$\underline{V_{in} = m(t_2 - t_1)}$$

* $\Delta t = \frac{V_{in}}{m}$ $\rightarrow V_{in} = m n T_s$

$$\Delta t = n T_s$$

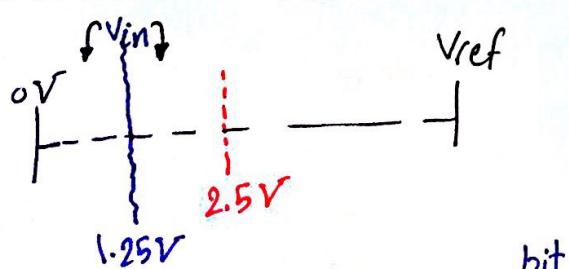* Successive Approximation Digital Voltmeter:




let $V_{ref} = 5 \text{ V}$ & # of bits = 3

suppose V_{in} is between 0 & 2.5 V.

- * Compare with $2.5 \text{ V} \Rightarrow 0$
- * Compare with $1.25 \text{ V} \Rightarrow 1$
- * Compare with $\underline{\quad}$ $\Rightarrow 0$

MSB
 $\underline{010}$

* Dual-Slope Digital Voltmeter:

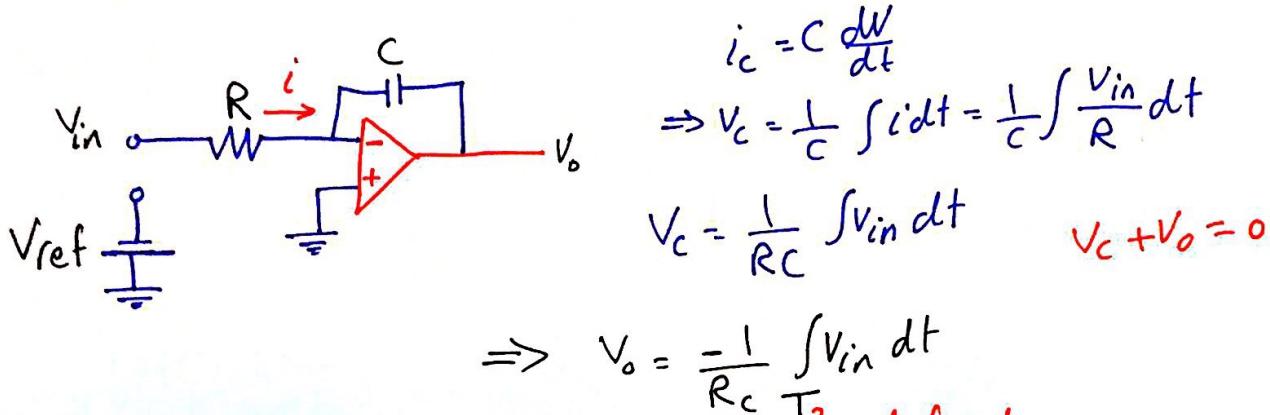

when we connect it to V_{ref} :

$$V_o = -\frac{1}{RC} \int -V_{ref} dt + V_{initial} = 0$$

$$0 = \frac{V_{ref}}{RC} T_x - \frac{V_{in}}{RC} T$$

$$\Rightarrow T_x = \frac{V_{in} T}{V_{ref}}$$

$$\Rightarrow V_{in} = \frac{T_x V_{ref}}{T}$$

advantage: doesn't depend on R & C .
disadvantage: slow.

Example: slide (102) :

$$V_{ref} = 10V$$


$$T = 10ms$$

$$\Rightarrow T_x = \frac{V_{in} T}{V_{ref}} = \frac{6.8 * 10m}{10} = 6.8 \underline{\underline{msec.}}$$


if he asked about $T_{conversion}$:

$$T_{conversion} = T + T_x = 10m + 6.8m = 16.8 \underline{\underline{msec.}}$$


* Bridges:

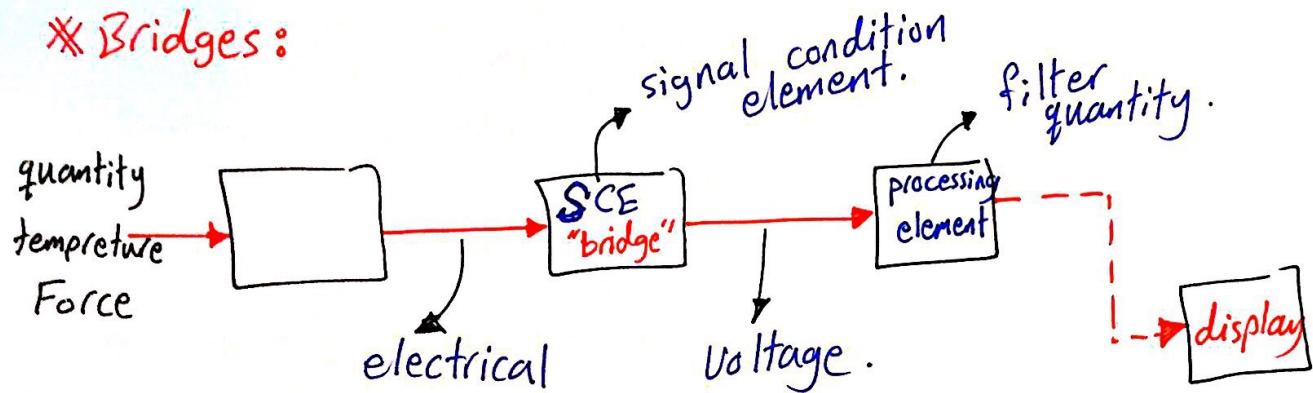

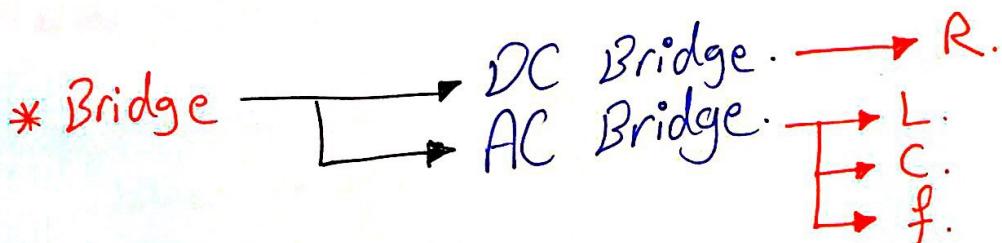- Resistance.
- Inductor.
- Capacitor.
- frequency.
- phase.



* Wheatstone Bridge:

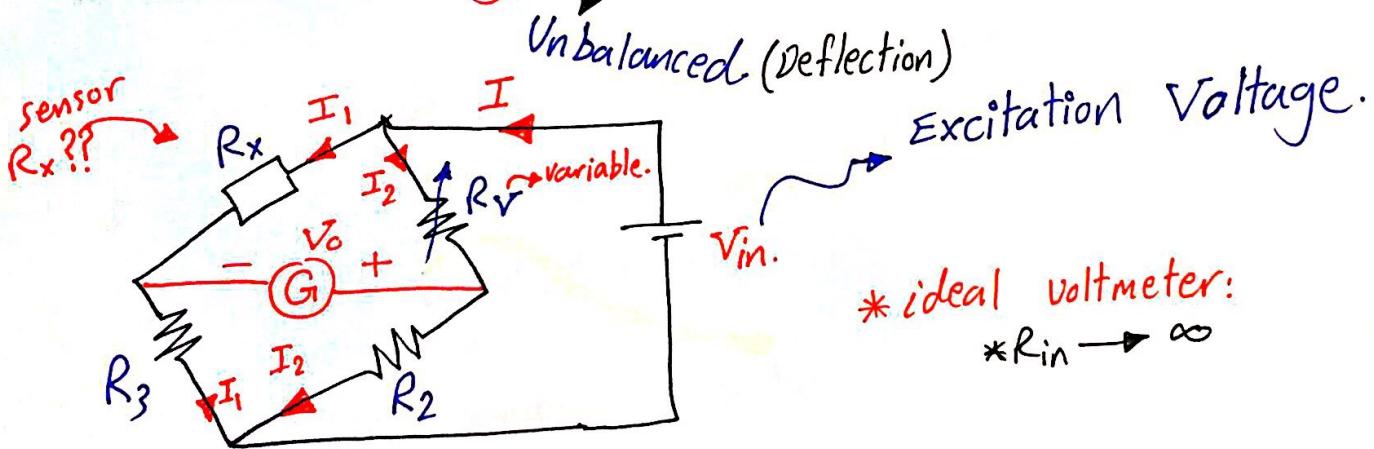

By using voltage division:

$$V_o = V_{in} \left(\frac{R_x}{R_x + R_3} \right) - V_{in} \left(\frac{R_v}{R_v + R_2} \right)$$

* Null method: $R_v \Rightarrow V_o = 0$ so $V_{in} \left(\frac{R_x}{R_x + R_3} - \frac{R_v}{R_v + R_2} \right) = 0$

$$\Rightarrow \frac{R_x}{R_x + R_3} = \frac{R_v}{R_v + R_2} \Rightarrow R_x R_v + R_x R_2 = R_v R_x + R_v R_3$$


$$R_x R_2 = R_v R_3$$

$R_x = \frac{R_v R_3}{R_2}$

"balanced"

* if the internal resistance of the voltmeter considered
Obtaining the thevenin circuit would be a solution

(35)

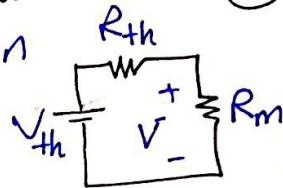

* Deflection method:

R_V replaced $\rightarrow R_1$ (Nominal R_x)

$$V_o = V_{in} \left(\frac{R_x}{R_x + R_3} - \frac{R_1}{R_1 + R_2} \right)$$

↳ one of the problem of
this method:

that is the relation isn't
a linear between V_o & R_x .

$$\checkmark \Delta R_x$$

\Rightarrow Case: $R_2 = R_3$
 $R_x = R_1$ (Nominal) $\Rightarrow V_o = 0$
 $R_x = R_1 \pm \Delta R_x$ $\rightarrow V_o^{+ve}$ $\rightarrow V_o^{-ve}$

$$V_o = f(R_x)$$

Examples: pressure sensor measures pressure (0-10 bar)

$$R = 120 + \frac{338 \text{ m}\Omega}{\text{bar}} \rightarrow R_{\text{Voltmeter}} \rightarrow \infty$$

max current sensor $\leq 30 \text{ mA}$

" R_x "
Find V_o when pressure is 10 bar & max V_{in} is used?


$$\text{given } R_1 = R_2 = R_3 = 120 \Omega$$

$$I_i \leq 30 \text{ mA}$$

$$\frac{V_{in}}{R_x + R_3} \leq 30 \text{ mA} \Rightarrow \frac{V_{in}}{120 + 120} \leq 30 \text{ mA} \Rightarrow V_{in} \leq 7.2 \text{ volt.}$$

$$@ 10 \text{ bar: } R_x = 120 + 0.338 * 10 = 123.38 \Omega$$
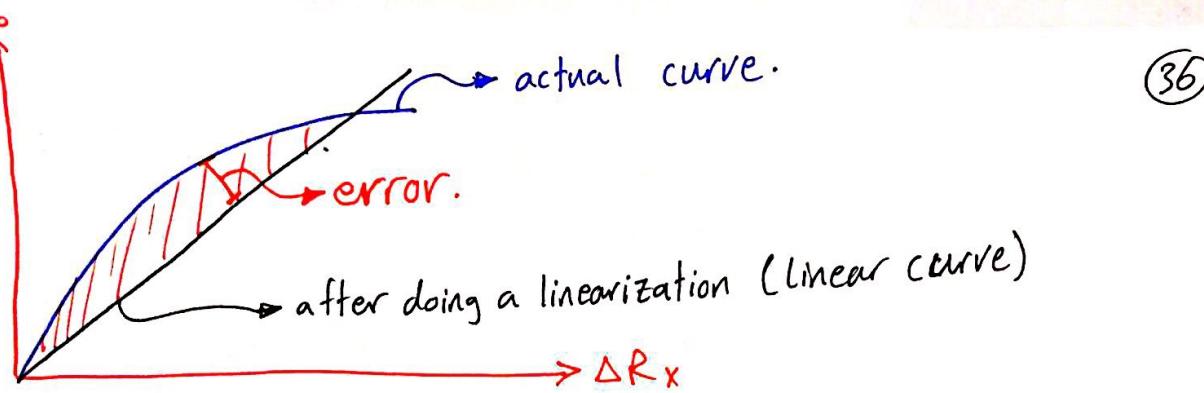
$$V_o = V_{in} \left(\frac{R_x}{R_x + R_3} - \frac{R_1}{R_1 + R_2} \right) \Rightarrow V_o = 50 \text{ m volt.}$$



* An illustration case: ΔR_x is small compared to nominal.

$$V_o = V_{in} \left(\frac{R_x}{R_x + R_3} - \frac{R_1}{R_1 + R_2} \right) \Rightarrow V_o = V_{in} \left(\frac{R_x + \Delta R_x}{R_x + \Delta R_x + R_3} - \frac{R_1}{R_1 + R_2} \right)$$

$$\underline{\delta V_o = f(\Delta R_x)}$$
□
□

subtracting □ from □ & approximate:

$$\rightarrow R_x + \underline{\Delta R_x} \xrightarrow[\text{small}]{\text{just for the Dominator.}} \simeq R_x$$

$$\delta V_o = V_o - V_o$$

$$\Rightarrow \underline{\delta V_o = V_{in} \frac{\Delta R_x}{R_x + R_3}}$$

* Sensitivity Bridge:

$$\underline{\underline{\frac{\delta V_o}{\Delta R_x} = \frac{V_{in}}{R_x + R_3}}}$$

Example:

A resistance thermometer ($0^\circ\text{C} \rightarrow 50^\circ\text{C}$), $R_{\text{nominal}} = 500 \Omega @ 0^\circ\text{C}$

& $\Delta R = \frac{4 \Omega}{1^\circ\text{C}}$, $R_1 = R_2 = R_3 = 500 \Omega$ & $V_{in} = 10 \text{ volt.}$

$$\Rightarrow R_x = 400 + 4T$$

$$V_o = V_{in} \left(\frac{R_x}{R_x + R_3} - \frac{R_1}{R_1 + R_2} \right)$$

$$V_o = 10 \left(\frac{125 + T}{250 + T} - 0.5 \right)$$

$$\Rightarrow @ T=0 \Rightarrow V_o = 0$$


$$@ T=2 \Rightarrow V_o = 0.455 \text{ volt.}$$

$$@ T=50 \Rightarrow V_o = 0.833 \text{ volt.}$$

=====
continue.

doing a linearization:

(37)

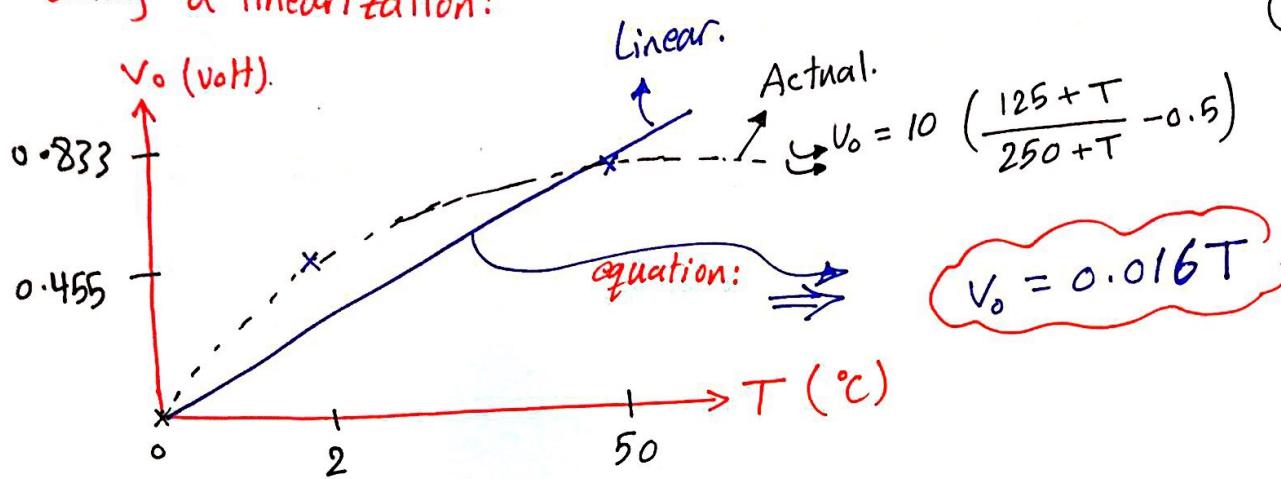

* Measurement errors:

Balanced:

$$R_2 R_3 = R_x R_1 \quad \text{Tolerance.}$$
$$\Rightarrow R_x = \frac{R_2 R_3}{R_1}$$

$$R_2 = R_2 \pm \Delta R_2$$

$$R_3 = R_3 \pm \Delta R_3$$


$$R_1 = R_1 \pm \Delta R_1$$

L * limiting error:

$$R_x = \frac{(R_2 \pm \Delta R_2)(R_3 \pm \Delta R_3)}{(R_1 \pm \Delta R_1)}$$

$$\text{Do an approximation: } R_x = \frac{R_2 R_3}{R_1} \left(1 \pm \frac{\Delta R_1}{R_1} \pm \frac{\Delta R_2}{R_2} \pm \frac{\Delta R_3}{R_3} \right)$$

* Sensitivity of Galvanometer:

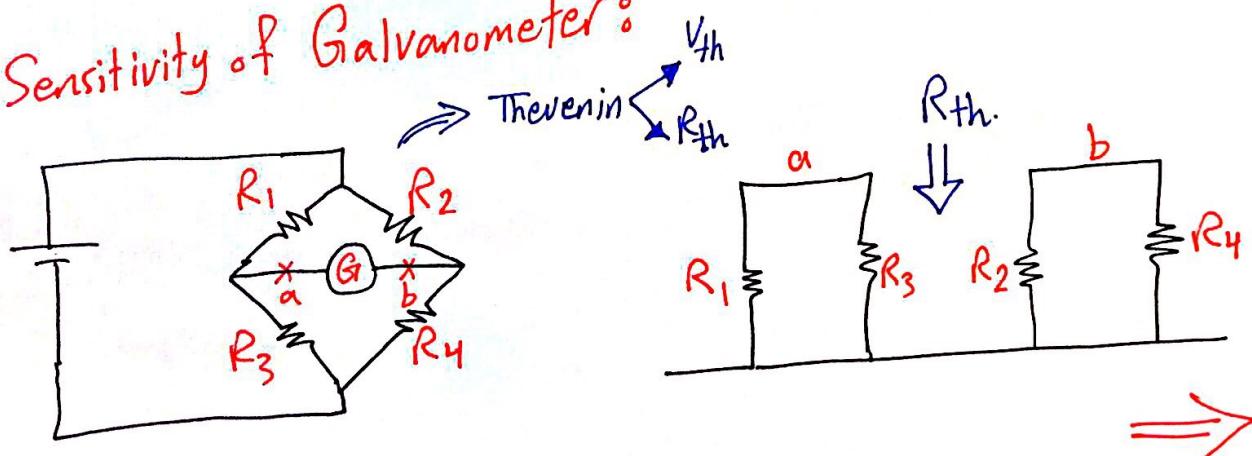


(38)

$$\Rightarrow R_{th} = (R_1 \parallel R_3) + (R_2 \parallel R_4)$$


$$V_{th} = V_1 \left(\frac{R_1}{R_1+R_3} - \frac{R_2}{R_2+R_4} \right)$$

Example: slide (121):

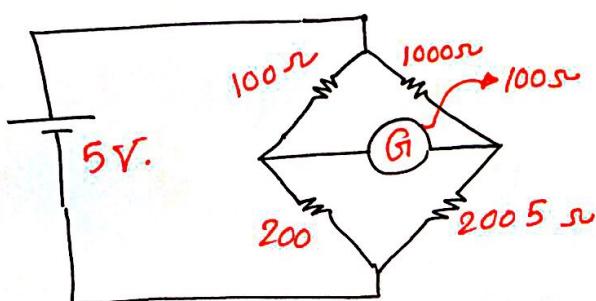

$$\text{sensitivity} = \frac{10 \text{ mm}}{1 \mu\text{A}}$$

* Deflection by the Galvanometer:

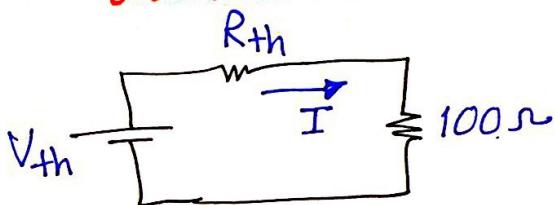

$$R_{th} = 734 \Omega$$

$$V_{th} = 2.77 \text{ mV}$$

$$I = 3.32 \mu\text{A}$$


$$\Rightarrow \text{deflection} = I * \text{sensitivity} = 3.32 \mu\text{A} * \frac{10 \text{ mm}}{1 \mu\text{A}} \\ = 33.2 \text{ mm.}$$

* Capacitor:


* any capacitor has:

$$\underline{\underline{E, \sigma}}$$

parallel.

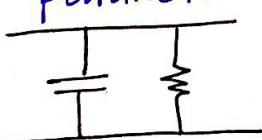


or

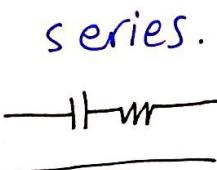

series.

* Quality Factor = $\frac{\text{Energy stored}}{\text{Average Energy Dissipated.}}$

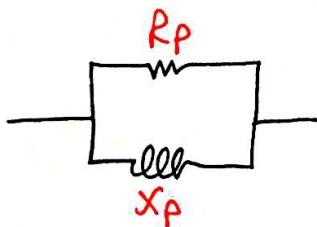* Dissipation factor = $\frac{\text{Energy Lost}}{\text{Energy stored}}$



→ Need it in series:

$$Z_{eq} = \frac{R_p // X_p}{R_p^2 + X_p^2} + j \frac{R_p^2 X_p}{R_p^2 + X_p^2}$$

$$Z_{eq} = R_s + j \frac{X_s}{R_s}$$

* Quality factor of inductance:

in series:

$$Q = \frac{|I|^2 * X_L}{|I|^2 * R} = \frac{\omega L}{R}$$

in Parallel:



$$Q = \frac{V^2/X_L}{V^2/R} = \frac{R}{\omega L}$$

* AC Bridge (Balanced Condition):

Balanced:

$$Z_1 Z_4 = Z_2 Z_3$$

↳ magnitude balance. $Z_1 Z_4 = Z_2 Z_3$

↳ phase. balance. $\underline{X}^{\theta_1} + \underline{X}^{\theta_4} = \underline{X}^{\theta_2} + \underline{X}^{\theta_3}$

*Oscilloscope Fundamentals:

(40)

10:1 voltage divider Probe.

↳ it is reduce the input signal if it was 10 volt signal, make it 1 volt.

*Why the internal resistance of oscilloscope very high (in Mn)?

→ To Reduce the high loading effect.

* Oscilloscope consists R & C, at low frequency C become open circuit.


* for a $1\mu\text{s}/\text{Div}$ & $1\text{V}/\text{Div}$:

→ max V_{pp} is 8 volt.

→ max period is $10\mu\text{sec}$.

* Trigger: we use it to have the signal stable on the oscilloscope screen.

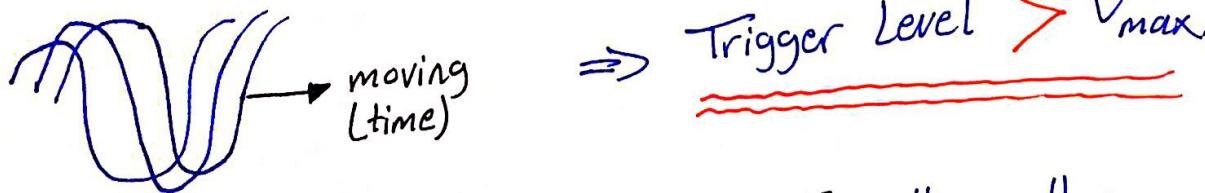
* if the trigger was above the peak voltage
Then the picture will be unsynchronized.




** If the oscilloscope was ANALOGUE, then the picture will be shown starting from the trigger point.

* Trigger Level in a DIGITAL oscilloscope:

(41)

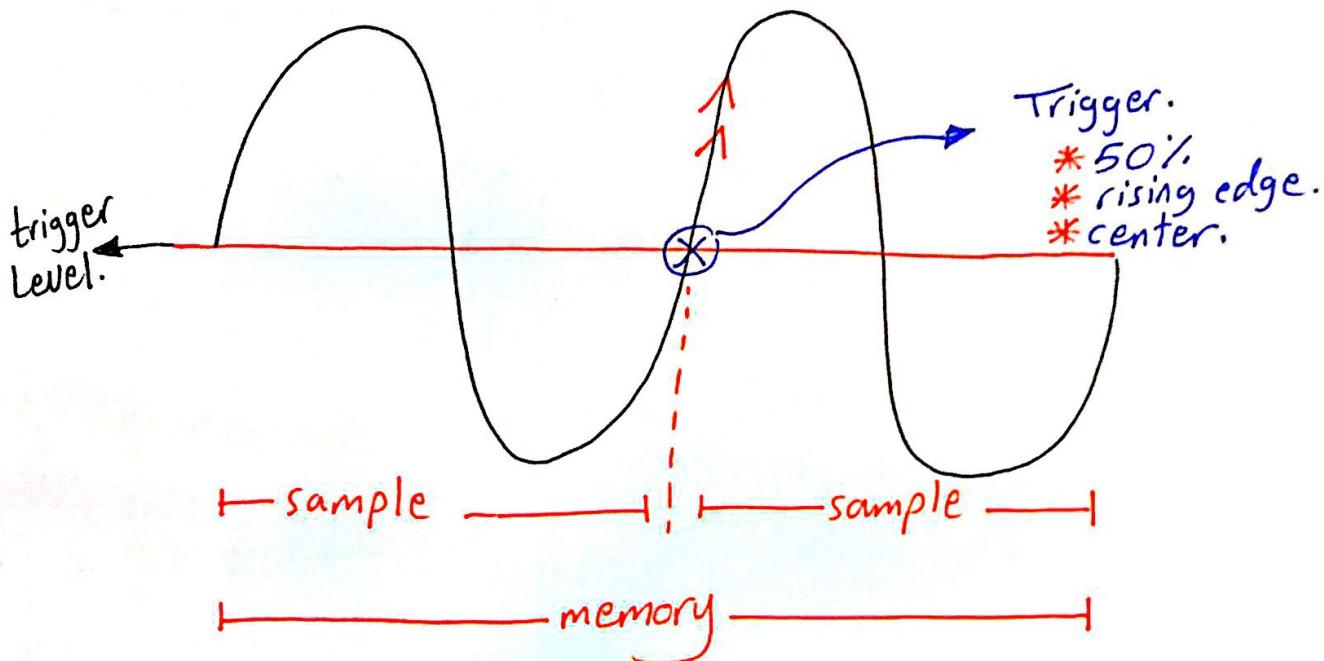

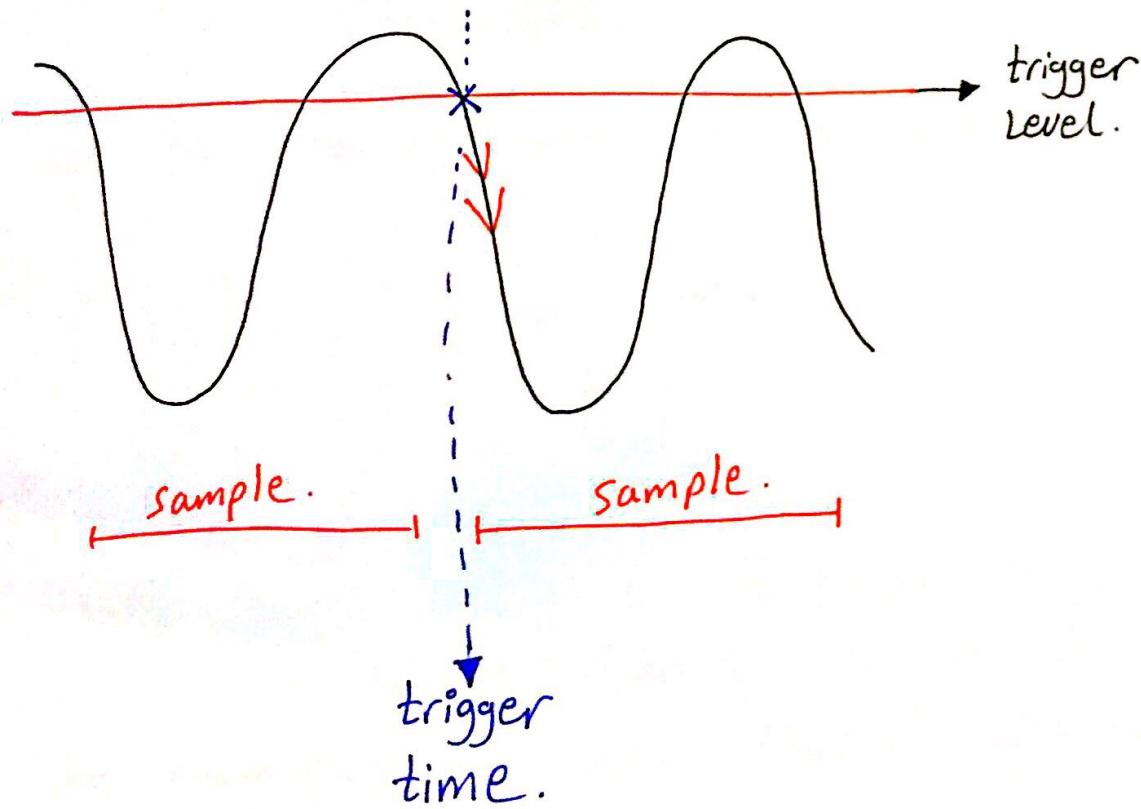* in the following we have falling edge :




* Always when determine trigger point

we need the following:


- 1] Determine Trigger Level.
- 2] Centre of the screen.
- 3] Determine if it is falling edge or Rising edge.

* Oscilloscope Performance Specifications:

* for a Low pass frequency response:

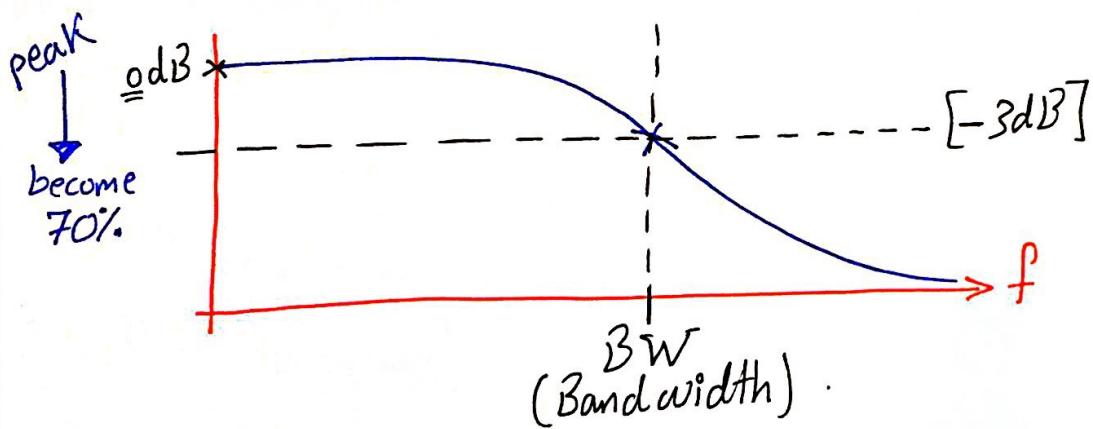

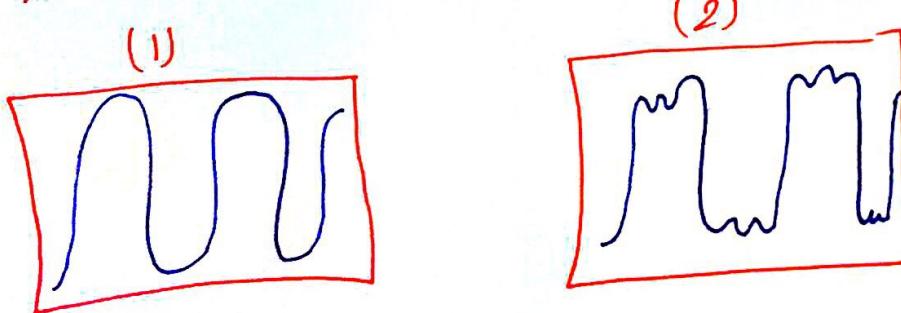* for the two following signals on oscilloscope:




(2) is better than (1) since it is with higher BW.

and (2) is more accurate than (1) since you will


see the harmonics in the signal so that it is distorted.

* Oscilloscope (x-y mode):

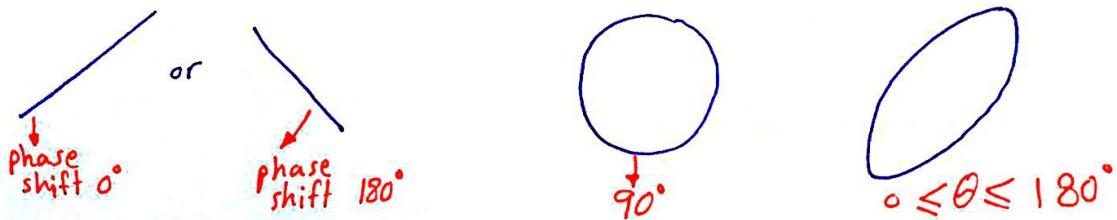if we insert a sinusoidal signal, $\underline{?}$ possible cases in the x-y mode:



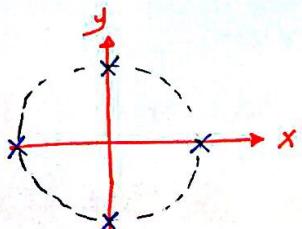Ex. $x = \sin \omega t$, $y = \cos \omega t$



* Zero crossing ($x=0$)

$$x = \sin \omega t = 0 \Rightarrow \omega t = 0, \pi$$

$$y(\omega t = 0) = 1 \quad \& \quad y(\omega t = \pi) = -1$$

$$\Downarrow \quad \quad \quad \Downarrow$$

$$(0, 1) \quad \quad \quad (0, -1)$$

* ($y=0$)

$$\cos \omega t = 0 \Rightarrow \omega t = \frac{\pi}{2}, \frac{3\pi}{2}$$

$$x\left(\frac{\pi}{2}\right) = 1 \quad \& \quad x\left(\frac{3\pi}{2}\right) = -1$$

$$\Downarrow \quad \quad \quad \Downarrow$$

$$(1, 0) \quad \quad \quad (-1, 0)$$

* Max x :

$$\max \sin \omega t \Rightarrow \omega t = \frac{\pi}{2}$$

$$x\left(\frac{\pi}{2}\right) = 1 \quad y\left(\frac{\pi}{2}\right) = 0 \Rightarrow (1, 0)$$

* Max y : $\max \cos(\omega t) \Rightarrow \omega t = 0$ $x(0) = 0 \Rightarrow (0, 1)$

$$y(0) = 1$$

* Min x :

$$\min \sin \omega t \Rightarrow \omega t = \frac{3\pi}{2}$$

$$y\left(\frac{3\pi}{2}\right) = 0 \quad (-1, 0)$$

$$x\left(\frac{3\pi}{2}\right) = -1$$

* Min y :

$$\min \cos \omega t \Rightarrow \omega t = \pi$$

$$x(\pi) = 0 \quad (0, -1)$$


$$y(\pi) = -1$$



(44)

⇒ so we have:

$$(0,1), (1,0), (0,-1), (-1,0)$$

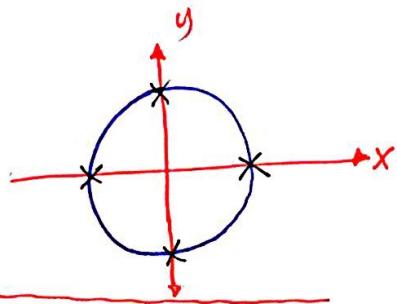

Ex. $x = \cos(\omega t)$
 $y = \cos(\omega t - 45^\circ)$

Do the same steps
as the previous example.


$d_1 \equiv$ Zero crossing.

$d_2 \equiv$ peak-to-peak.

from d_1 & d_2 we evaluate
the phase shift:


$$\theta = \sin^{-1}\left(\frac{d_1}{d_2}\right)$$

⇒ The final figure would be:

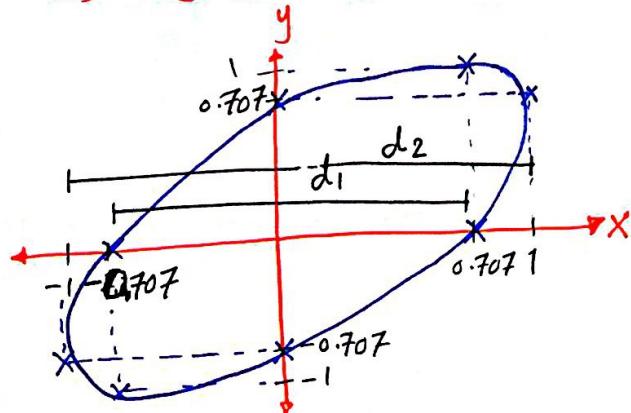

Note: also we could use the y-axis to find the phase-shift with the same way.

XX Earthing:

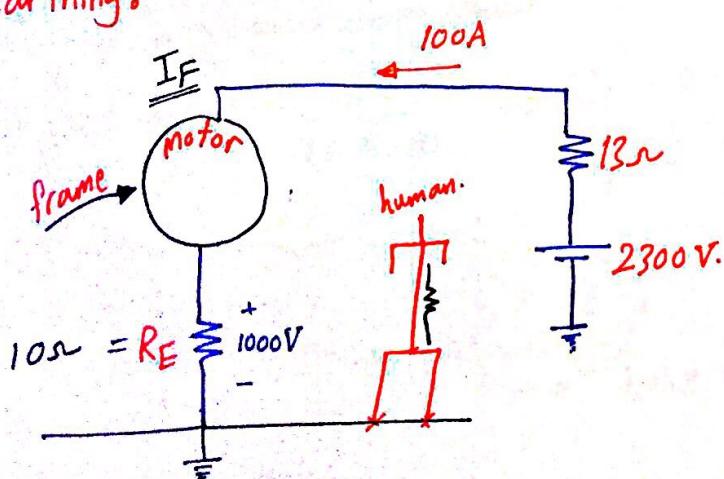

if the human touch the
motor after a fault happen
we protect him :

- by wearing a safty
shoes.
- by using Tire to
clear fault.
- by reducing R_E .

* The conductor between motor & the earth
⇒ must be able to carry the fault current.

$0 \rightarrow 10 \text{ mA}$ (NO Impact)

(45)

$150 \text{ mA} \rightarrow 200 \text{ mA}$ (Dead).

* Current relation that related to human to has No impact from the current:

$$I = \frac{116 \text{ mA}}{\sqrt{t}}$$

Max Safe Current.

Time to clear fault.


* Electrical Shock:

Difference in the voltage & will create a path of the current.

* The worst path for the current passing through the human, that between human hands (since it will pass through the heart).


Ex.

3-phase transformer

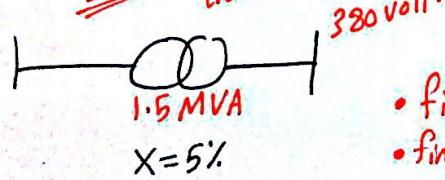

- find I_f ?!
- find cross section ?!
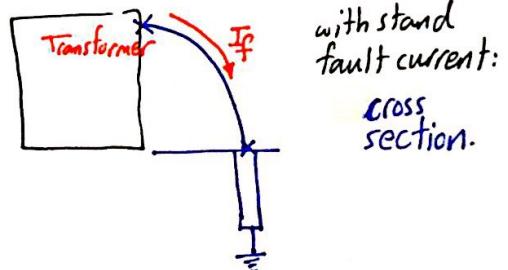
$$I_f = \frac{1}{X\%} * \text{Full Load current.}$$



$$\text{full load current} = \frac{1.5 \text{ M}}{\sqrt{3} * 380} \Rightarrow I_f = 20 * \text{full load}$$

$$I_f \approx 45 \text{ kA}$$

$$\text{cross section (mm}^2\text{)} = 9 * \sqrt{t} * I_f$$

time to clear fault.

assume $t = 0.5 \text{ sec.}$



$$\text{cross section} = 9 * \sqrt{0.5} * 45 \text{ k} = 286 \text{ mm}^2$$

* Grounding:

→ Connect a network point to the ground through an impedance.

(46)

Enclosure.

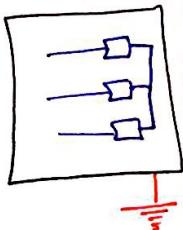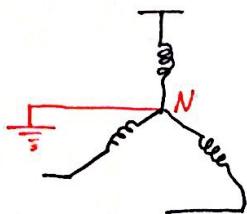


Grounding
Safty
[Unenergized element.]


performance
of the network.

* How to do the earthing?

By using Rod or a mesh of Rods.

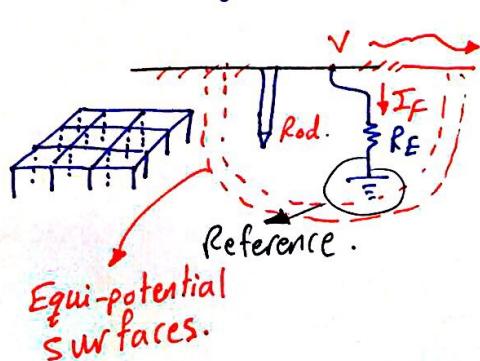

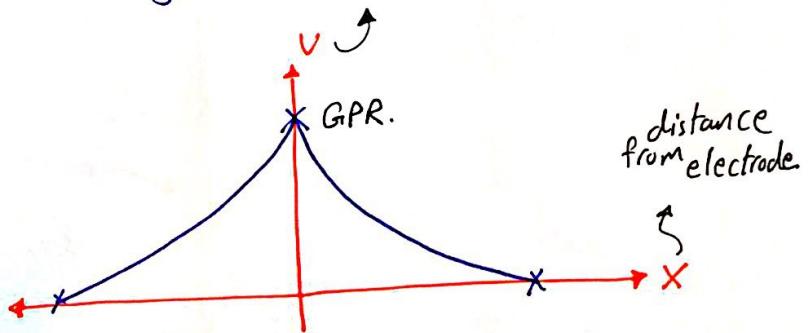
This voltage called:
ground potential rise. (GPR)



* Safety:

- Insolation (Gloves, boots).
- Grounding → Reduce GPR.
- Equi-potential rise → Reduce voltage difference in the site.

* Hemispherical electrode.


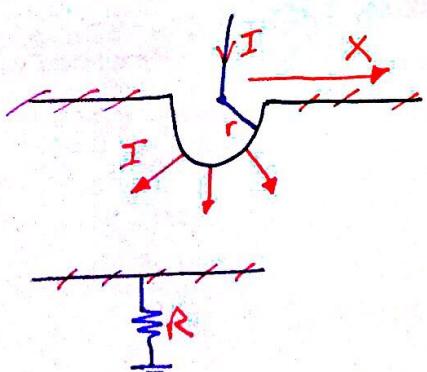


where R :


$$R = \frac{\rho}{2\pi r}$$

soil Resistivity.

⇒

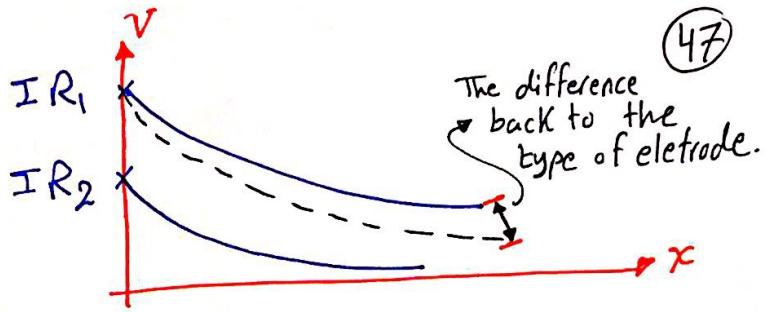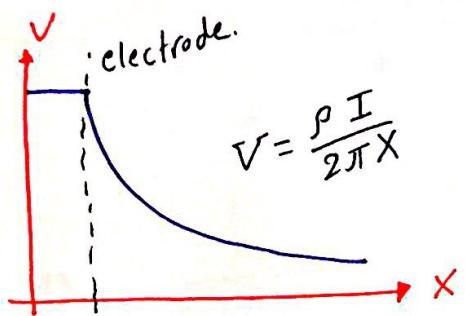


* Using 2-electrode:

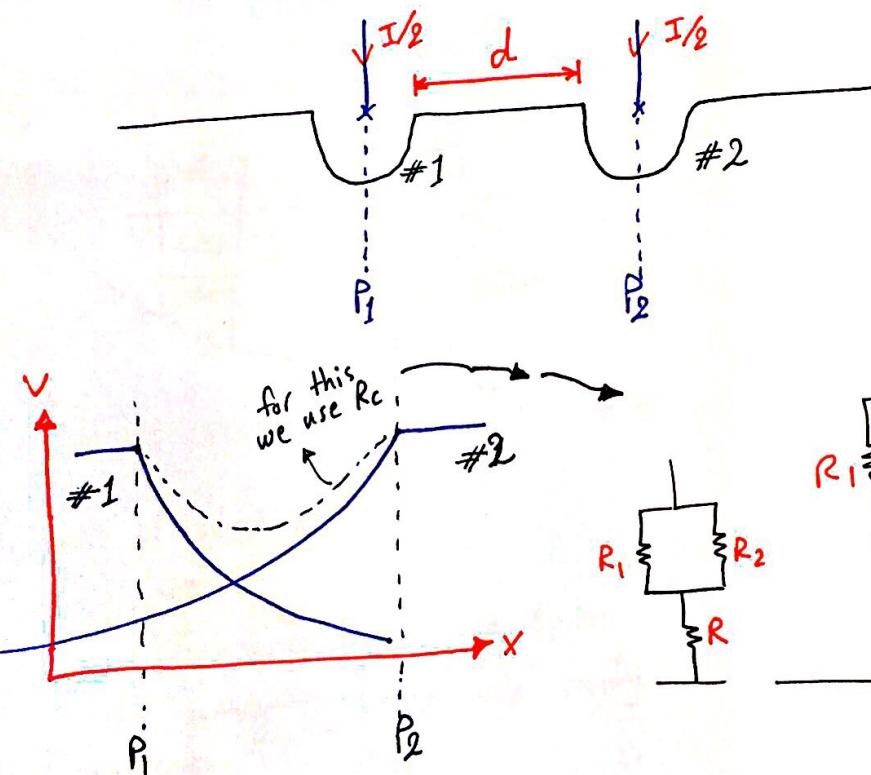

$$R_{eq} = \frac{R}{N \times m}$$


depend on space

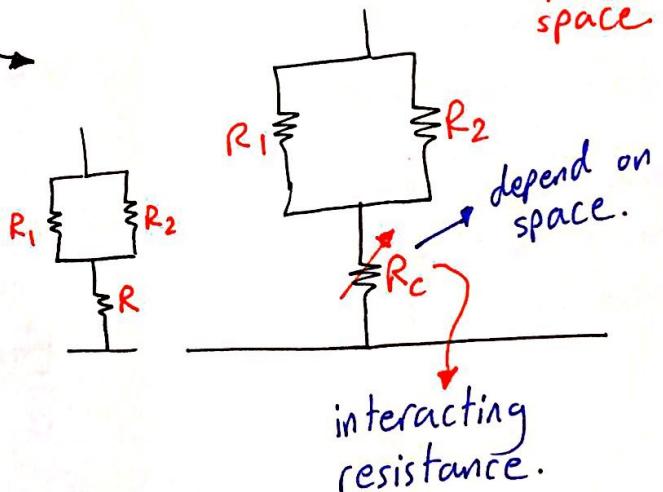


interacting resistance.

* Touch & Step voltage:

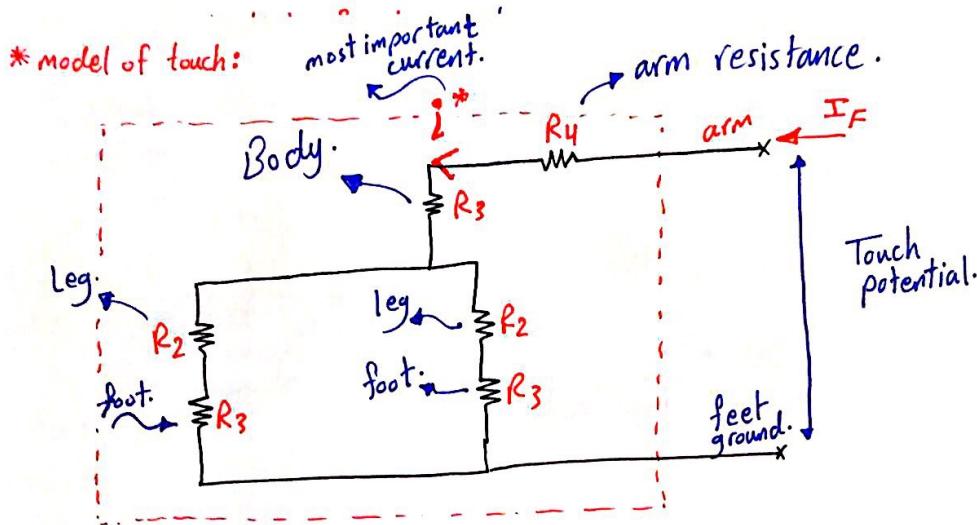
- Touch: Voltage difference between your hands & your feet.
- Step voltage: Voltage difference between your feet.



(48)


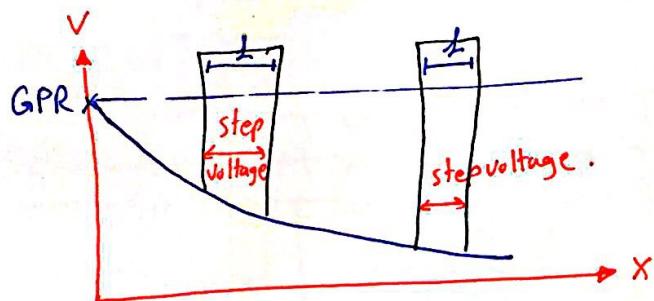


* Model of step voltage:


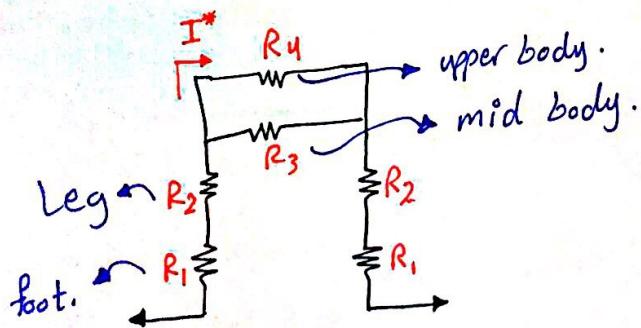


* IEEE	
< 1mA	No sensation.
1-8mA	sensation of shock.
8-15mA	painful shock
15-20mA	loss of muscle control.
20-50mA	muscles failure
50-200mA	heart failure
> 200mA	death & burns.



* Grounding & Bonding:

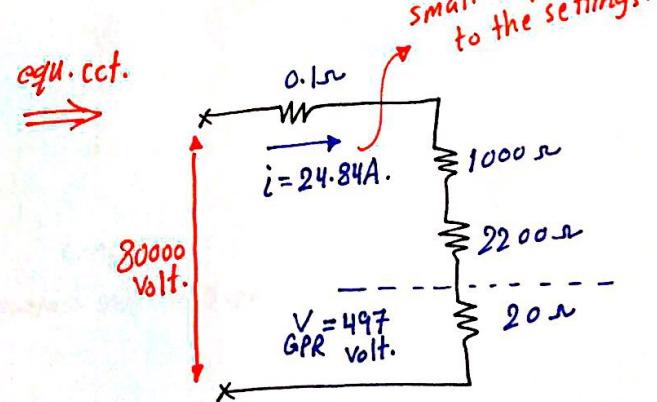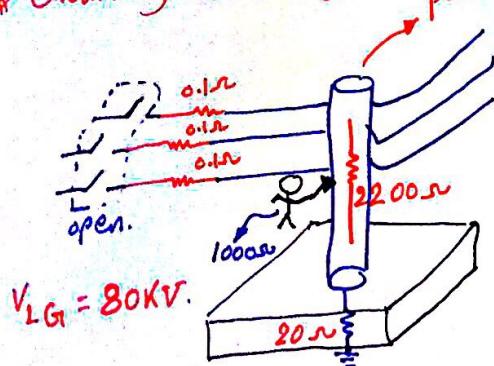


equipotential bonding.

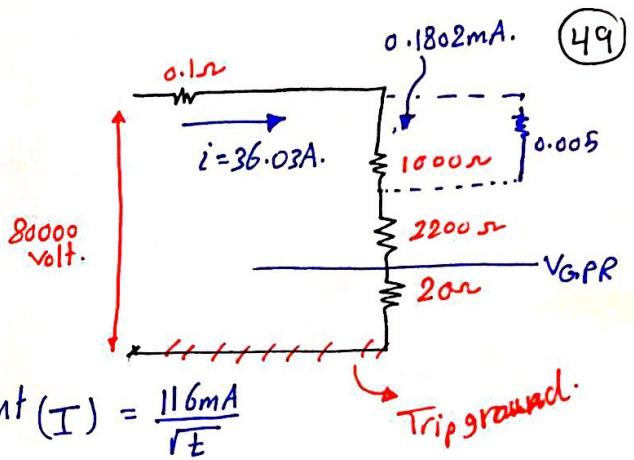
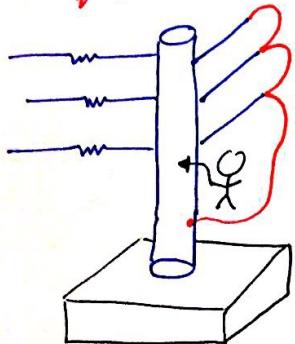


brackets grounding.

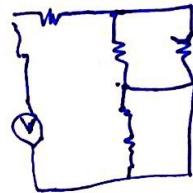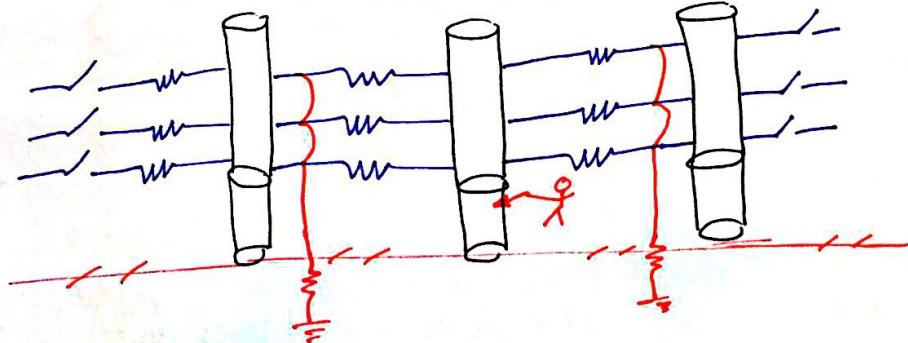

* Types of earthing systems:

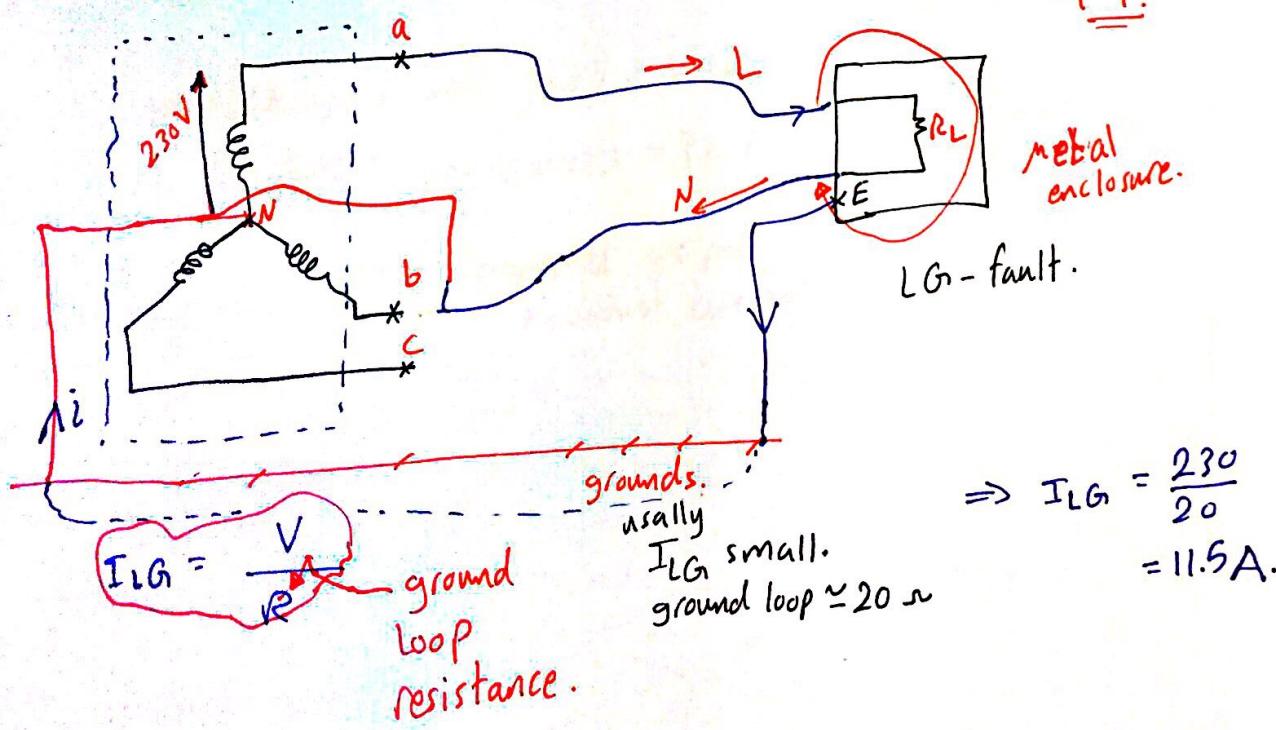

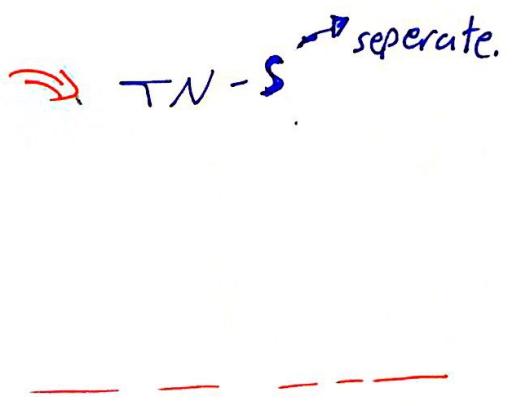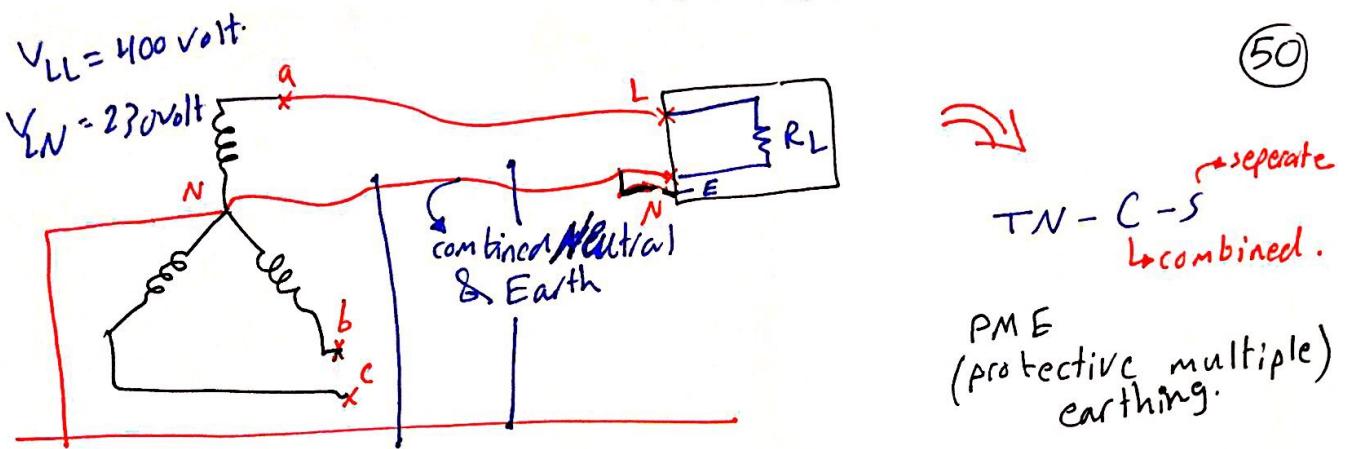


* ground loop:

$$\begin{aligned}
 TNS &\approx 0.8 \Omega \Rightarrow I_{LG} = 230 / 0.8 = 287 \text{ A.} \\
 TN - C - S &\approx 0.35 \Omega \Rightarrow I_{LG} = 657 \text{ A.} \\
 TT &= 21 \Omega \text{ or } 100 \Omega \Rightarrow I_{LG} = 11 \text{ A.} \\
 &\quad I_{LG} = 2.3 \text{ A.}
 \end{aligned}$$

MCB 32A type B $\Rightarrow 32 * 5 = 160 \text{ A.}$

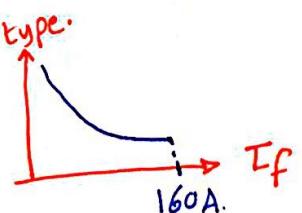MCB 32A type C $\Rightarrow 10 * 32 \text{ A} = 320 \text{ A.}$




\Rightarrow To be connected we put RCD
Residual current Device.



* Ground Testing:

(51)

Fall of potential - Testing:

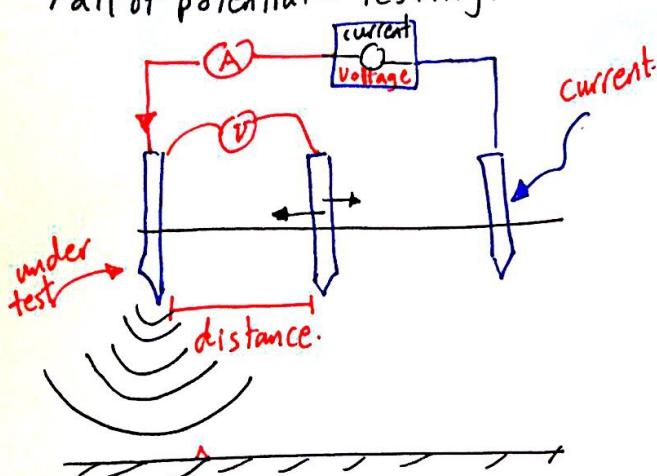


$$R_E = \frac{V}{I}$$

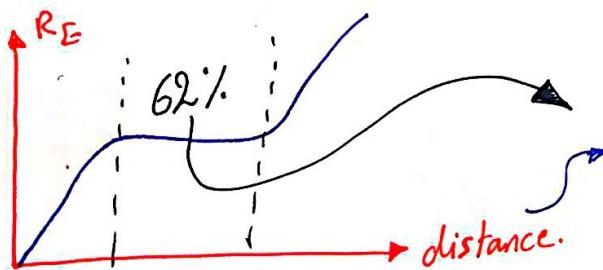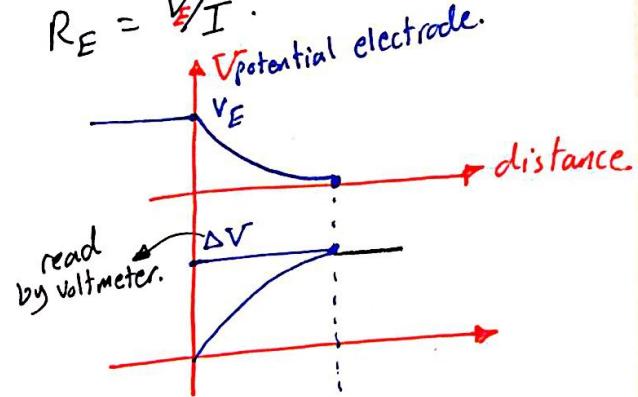

it is the distance between Electrode under Test & potential electrode.



* Transducer:

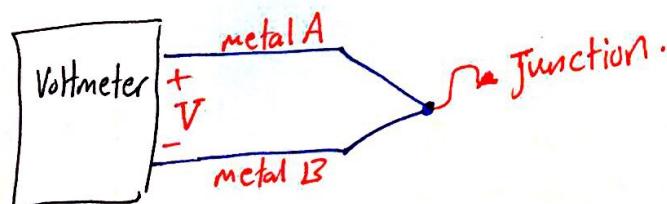* Thermo couple: \Rightarrow Temperature $\xrightarrow{\text{convert to}}$ Voltage.



$$V = \alpha T$$

\Rightarrow emf.

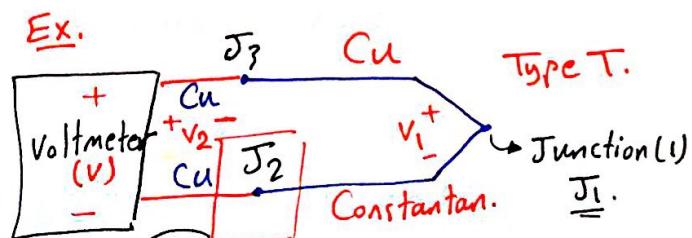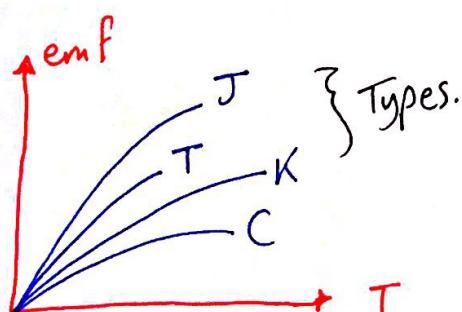

Ex. $J_3 \Rightarrow \text{Cu with Cu (No emf).} \xrightarrow{\text{By KVL}}$

$J_2 \Rightarrow \text{Cu with C (emf).} \Rightarrow V = V_1 - V_2$

ice $\left\{ \text{ref} \Rightarrow T = 0^\circ \right. \} \quad V_2 = 0$

Continue.


(52)

* Reference Junction:

$$J_2 \Rightarrow \text{reference (ice)} \Rightarrow 0^\circ\text{C} \Rightarrow V_2 = 0$$

since $V_2 = \alpha T$


$$V = V_1 = \alpha T_{J_1}$$

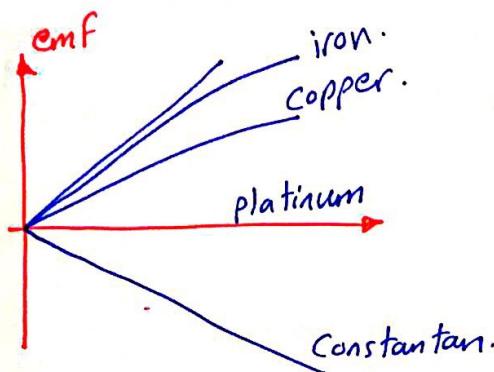

\Rightarrow depend on the junction between the two material.

Example:

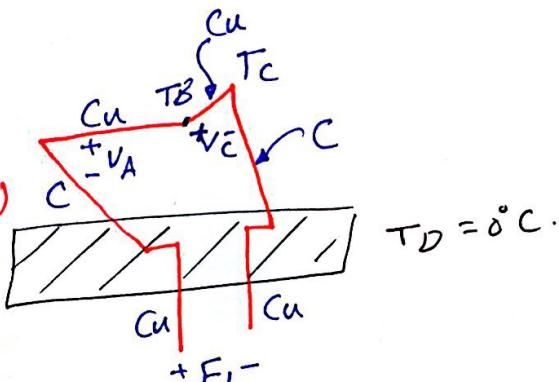- (1) find $\text{Emf}(B, C)$
- (2) find T_A, T_C .



Solution:

(1)

$V_{B,C} = 0$ (Cu-Cu Junction).

for C : KVL: $-E_t - V_A + V_C = 0$

$$\text{so } V_C = E_t + V_A \Rightarrow V_C = 3.567 \text{ mV}$$

given : $T_B = 121.1^\circ\text{C}$


$V_A = +1.517 \text{ mV}$

$E_t = 2.05 \text{ mV}$

curve $Cu-Cu$ is given.

(2)

$T_A \Rightarrow$ from Curve.

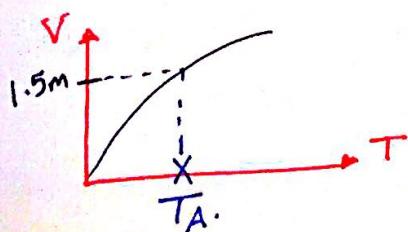


if a table is given for V & T
& we didn't find the needed point.
 \Rightarrow we do a linearization and find
that point.

* Signal Analysers:

Time domain $\xrightarrow{\text{Fourier Series}}$ Frequency Domain.

$$\Rightarrow x(t) = a_0 + \sum_{n=1}^N (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$

ω_0 \equiv Fundamental Frequency.

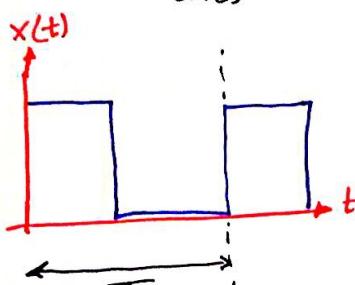

$$f_0 = \frac{1}{T} \text{ Hz.}$$

f_0
2f₀
3f₀
4f₀
⋮

Harmonics.

$a_0 \equiv$ DC signal Average.

$$a_0 = \frac{1}{T} \int x(t) dt.$$

for a_n & b_n :

$$a_n = \frac{2}{T} \int x(t) \cos n\omega_0 t dt.$$

$$b_n = \frac{2}{T} \int x(t) \sin n\omega_0 t dt.$$

* Power Quality Analysers:

This device can read:
Voltage, current, power, Accumulated Energy, magnitude, frequency,
, THD "Total Harmonics Distortion".
It also has a memory.

$$\begin{aligned} dB &= 20 \log \frac{V_2}{V_1} \\ &= 10 \log \frac{P_2}{P_1} \end{aligned}$$

dB_m \leftrightarrow mW.



End of Material

