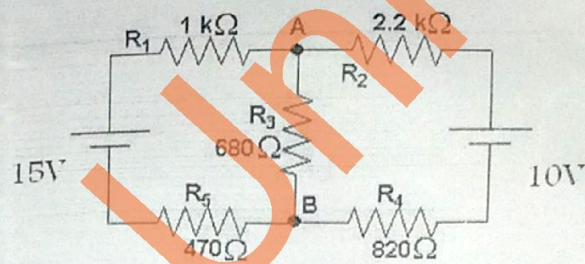


University of Jordan  
Faculty of Engineering and Technology  
Electrical Engineering Department  
Electrical Circuits Lab (EE 219) / mid term exam

Student Name: \_\_\_\_\_ student # \_\_\_\_\_

- 1) It's required to measure the current through  $R_3$  using Thevenin theorem show all your work in steps (3marks).



2. Connect a series RLC circuit, with the following values:

$$R=820\Omega \quad L=100\text{mH} \quad C=0.1\mu\text{F}$$

Draw your connection (showing the connections for Ammeter to measure the source current , Voltmeter to measure the source voltage ( 2marks ) .

3. (DON'T use the oscilloscope to determine the resonance frequency ) Set the power supply to  $1 V_{RMS}$  , calibrate all devices as you need (be ready to take the first reading), then raise your hand so your circuit will be checked by the instructor. (8marks)

Then fill the following table (8 marks) :

f(Hz)	$ I _{rms}$	$ V_R _{peak}$ <i>rms</i>	$V_C$ rms
1000			
$F_r =$			

GOOD LUCK ☺