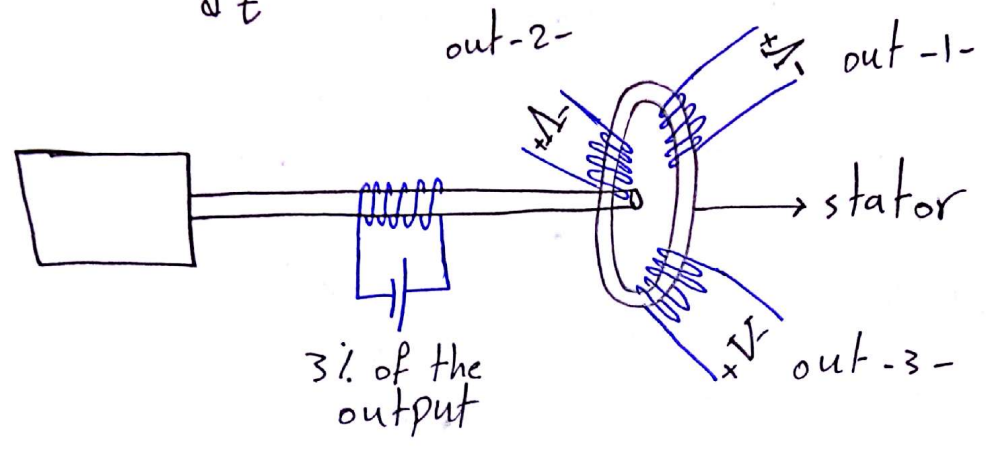


Chp -12- : three - phase circuits.



How electricity is being generated?



$$V = -N \frac{d\phi}{dt} \rightarrow \text{Flux}$$



Amper's law :
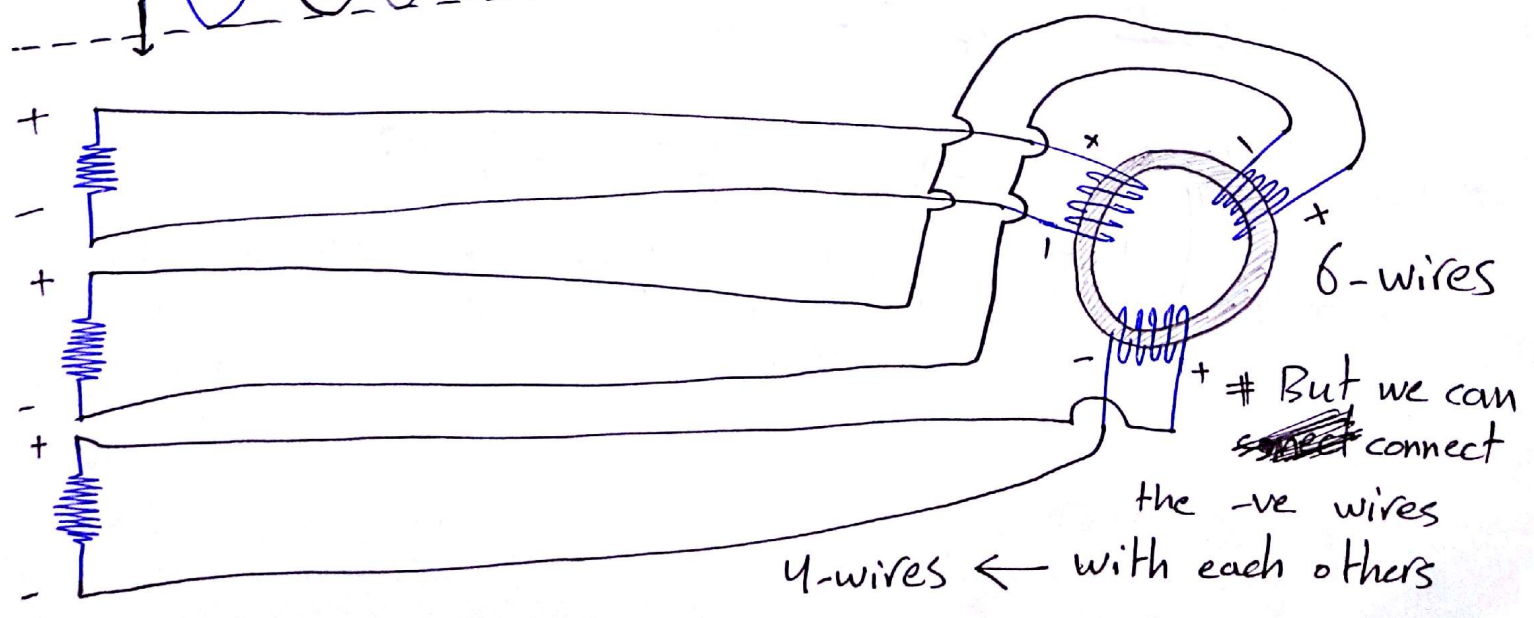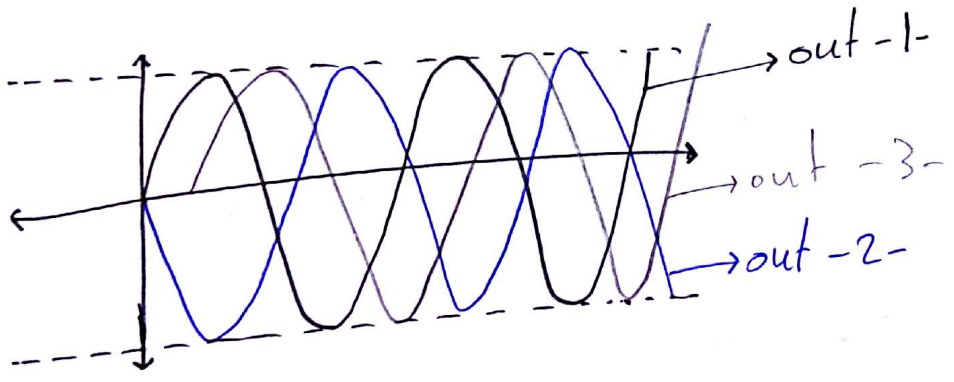
$$I = \oint H \cdot dl \rightarrow \left. \begin{array}{l} \text{ای سلاک جبر فیہ تیار یوں} \\ \text{حوالہ مجال مغناطیسی} \end{array} \right\}$$



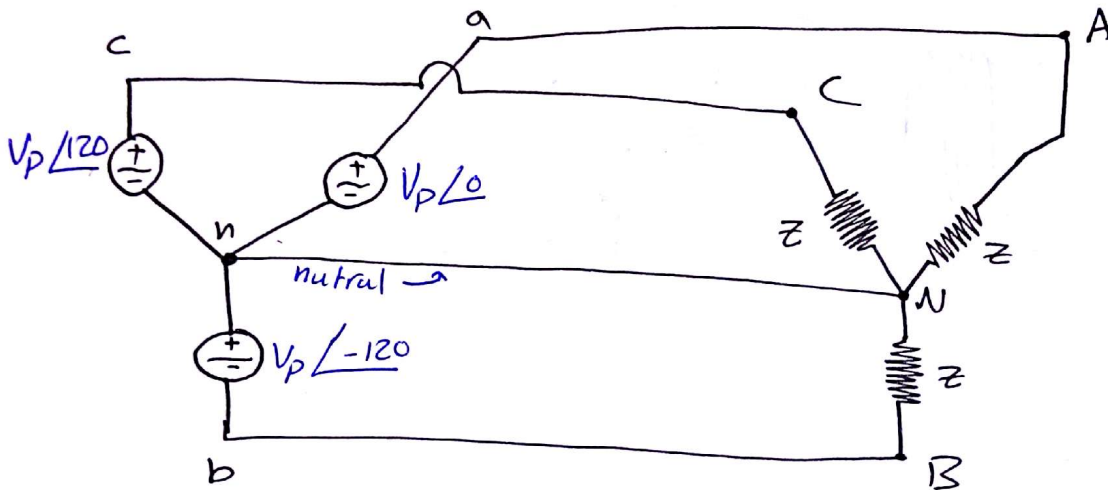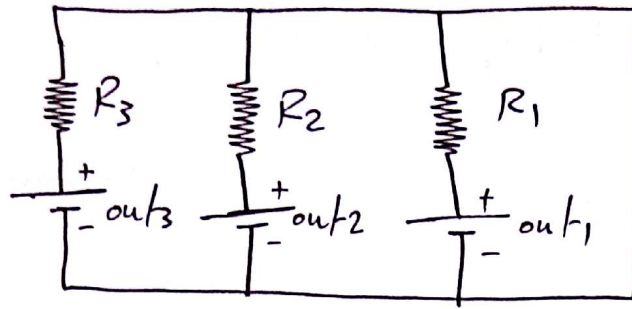

$Y - Y$ 3 phase-system

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$

$$\left\{ |V_{an}| = |V_{bn}| = |V_{cn}| \right\}$$


$$* V_{an} + V_{bn} + V_{cn} = V_p \angle 0 + V_p \angle -120 + V_p \angle 120$$

$$= V_p + V_p \cos(-120) + j V_p \sin(-120) + V_p \cos(120) + j V_p \sin(120)$$

$$\cancel{1} + \cancel{\frac{-1}{2}} + \cancel{\frac{-\sqrt{3}}{2}} + \cancel{\frac{-1}{2}} + \cancel{\frac{\sqrt{3}}{2}}$$

$$= \text{Zero}$$

إذا أخذنا (load) بين (A, B) -

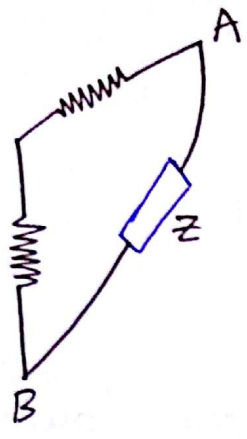

$$V_{ab} = V_{AB} = V_{an} - V_{bn}$$

$$= V_p \angle 0^\circ - V_p \angle -120^\circ$$

$$V_{ab} = V_p - V_p \cos(-120^\circ) - j V_p \sin(-120^\circ)$$

$$V_{ab} = V_p - (-\frac{1}{2} V_p) - j V_p (-\frac{\sqrt{3}}{2})$$

$$V_{ab} = \frac{3}{2} V_p + j V_p \frac{\sqrt{3}}{2}$$

$$V_{ab} = \sqrt{3} \left(\frac{\sqrt{3}}{2} V_p + j V_p \frac{1}{2} \right)$$

$$V_{ab} = \sqrt{3} V_p \angle 30^\circ$$

- and so on -

$$V_{ca} = V_p \angle 150^\circ, \quad V_{bc} = \sqrt{3} V_p \angle -90^\circ$$

* $I_a = I_{aA}$ (From (a) to (A))

$I_b = I_{bB}$

$I_c = I_{cC}$

$I_n = I_{nN} \quad ?? \rightarrow$ (التيارة)

$V_{an} = V_p \angle 0^\circ$

$V_{bn} = V_p \angle -120^\circ = |V_{an}| \angle -120^\circ$

$V_{cn} = V_p \angle 120^\circ = |V_{an}| \angle 120^\circ$

$\rightarrow I_a \rightarrow kV \rightarrow -V_{an} + I_a Z = 0 \rightarrow I_a = \frac{V_{an}}{Z} = \frac{V_p \angle 0^\circ}{Z} = I_p \angle 0^\circ$

$\rightarrow I_b \rightarrow kV \rightarrow -V_{bn} + I_b Z = 0 \rightarrow I_b = \frac{V_{bn}}{Z} = \frac{V_p \angle -120^\circ}{Z} = I_p \angle -120^\circ$

$\rightarrow I_c \rightarrow kV \rightarrow -V_{cn} + I_c Z = 0 \rightarrow I_c = \frac{V_{cn}}{Z} = \frac{V_p \angle 120^\circ}{Z} = I_p \angle 120^\circ$



⇒ So we can grounded n and N

- but we must to transfere the wire that the loads are not equal (un Balanced)


- but at the (Balanced system) → we can ground it.

I_a, I_b, I_c → line current (خارج موصل)

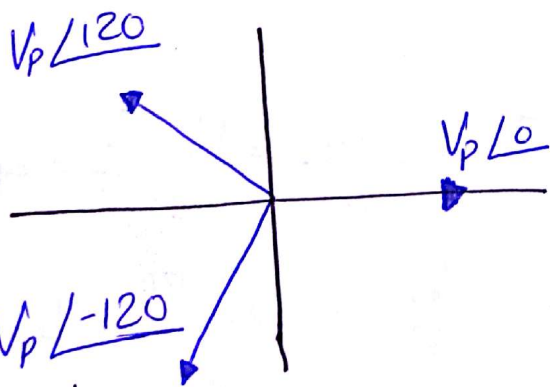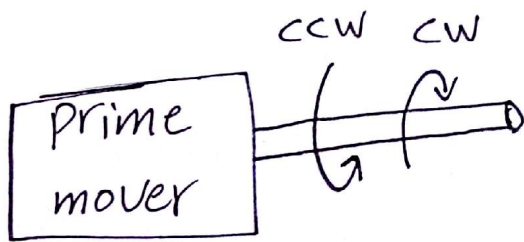I_A, I_B, I_C → phase current (داخل موصل)



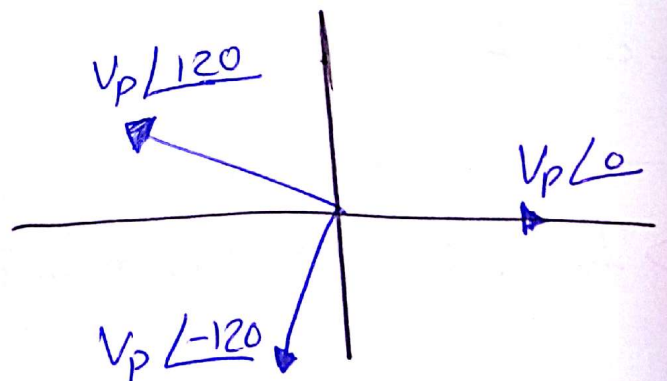- ccw.
- Negative sequence.
- california.



- cw
- positive sequence
- the rest of world.

$I_n(Y)$ connection :-

(5)

$$I_{\text{line}} = I_{\text{phase}}$$

$$\# V_{ab} = V_{AB} = \sqrt{3} V_p \angle +30$$

$$\# V_{bc} = V_{BC} = \sqrt{3} V_p \angle -90$$

$$\# V_{ca} = V_{CA} = \sqrt{3} V_p \angle +150$$

line to line voltage
(voltage line).

$V_p \rightarrow \begin{cases} V_{an} \\ V_{bn} \\ V_{cn} \end{cases} \rightarrow \begin{matrix} \text{phasor} \\ \text{to} \\ \text{neutral} \\ \text{voltage} \end{matrix} \rightarrow \text{phasor voltage} \rightarrow \text{phase to neutral}$

proof

$$\Rightarrow V_{ca} = V_{CA} = V_{cn} - V_{an}$$

$$= V_p \angle 120^\circ - V_p \angle 0^\circ$$

$$= V_p (\cos(120) + j \sin(120)) - V_p$$

$$= \frac{-1}{2} V_p + j \frac{\sqrt{3}}{2} V_p - V_p$$

$$= -\frac{3}{2} V_p + j \frac{\sqrt{3}}{2} V_p$$

$$= \sqrt{3} \left(\frac{-\sqrt{3}}{2} V_p + j \frac{1}{2} V_p \right)$$


$$= \sqrt{3} V_p \angle 150^\circ$$

$$\# V_{ab} = \sqrt{3} V_p \angle 30^\circ$$

$$\# V_{bc} = \sqrt{3} V_p \angle -90^\circ$$

$$\# V_{ca} = \sqrt{3} V_p \angle 150^\circ$$

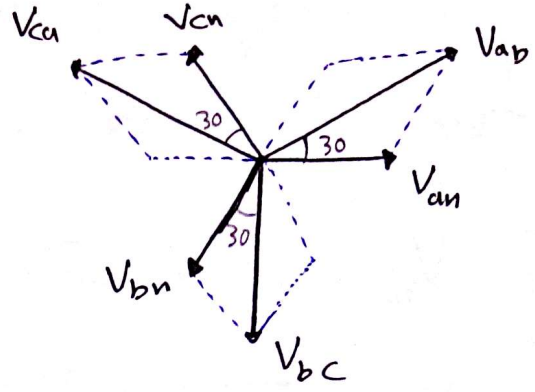(phase) (line) کے لیے -
 الے کوئی ہا بہتار (30°)



- in general :-

In Y-connection loads :-

$$V_{LL} = \sqrt{3} V_p \angle +30^\circ$$


$$\# V_{ab} = \sqrt{3} V_{an} \angle +30^\circ$$

$$\# V_{bc} = \sqrt{3} V_{bn} \angle +30^\circ$$

$$\# V_{ca} = \sqrt{3} V_{cn} \angle +30^\circ$$

(ex) for the Balanced ckt shown, find (line phase voltage) and (line & phase current), then find the (total power absorbed By the load).
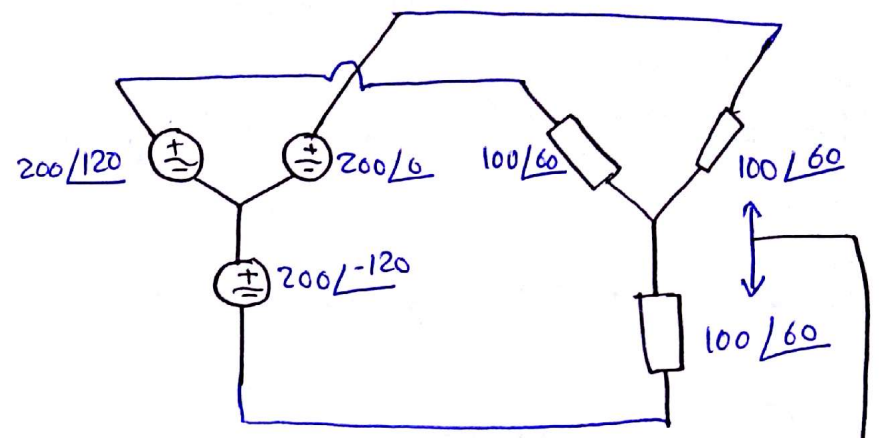
$$\left. \begin{aligned} V_{an} &= 200 \angle 0^\circ \\ V_{bn} &= 200 \angle -120^\circ \\ V_{cn} &= 200 \angle 120^\circ \end{aligned} \right\} \text{phase voltage}$$



load متوازن (balanced)

$$\begin{aligned} \# V_{ab} &= \sqrt{3} V_{an} \angle +30^\circ \text{ V} \\ &= \sqrt{3} * 200 \angle 0^\circ * \angle +30^\circ \\ &= 346.4 \angle +30^\circ \text{ V} \end{aligned}$$

$$\# V_{bc} = 346.4 \angle -90^\circ \text{ V}$$


$$\# V_{ca} = 346.4 \angle 150^\circ \text{ V}$$

$$\# I_a = \frac{V_{an}}{Z} = \frac{200 \angle 0^\circ}{100 \angle 60^\circ} = 2 \angle -60^\circ$$

$$\# I_b = \frac{V_{bn}}{Z} = \frac{200 \angle -120^\circ}{100 \angle 60^\circ} = 2 \angle -180^\circ$$

$$\# I_c = \frac{V_{cn}}{Z} = \frac{200 \angle 120^\circ}{100 \angle 60^\circ} = 2 \angle 60^\circ$$
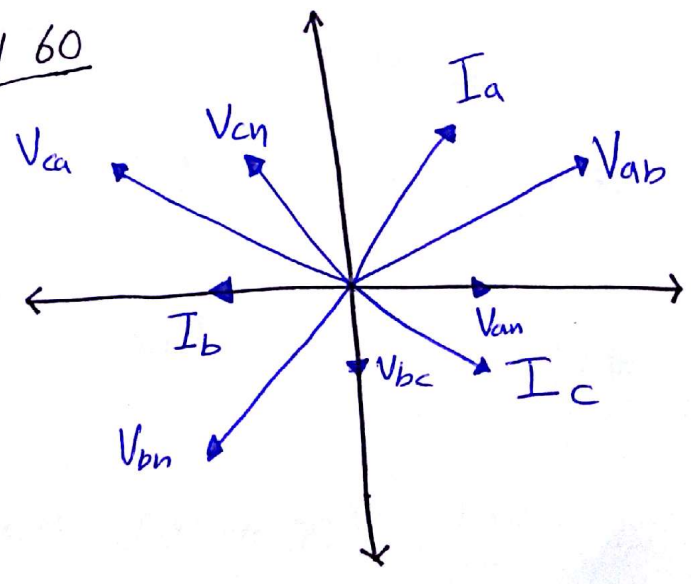
$$\left. \begin{aligned} \# I_{\text{line a}} &= I_a \\ \# I_{\text{line b}} &= I_b \\ \# I_{\text{line c}} &= I_c \end{aligned} \right\} \begin{aligned} &Y-Y \\ &I_{\text{line}} = I_{\text{phase}} \end{aligned}$$



Power

$$P_A = |V_{an}| |I_a| \cos(\theta_v - \theta_i) \\ = 200 * 2 * \cos(0 - -60) = 200 \text{ W}$$

$$P_B = 200 \text{ W} \rightarrow \cos(\theta_v - \theta_i) = \cos(-120 - -180)$$

$$P_C = 200 \text{ W} \rightarrow \cos(120 - 60).$$

$$P_{\text{total}} = 600 \text{ W} \rightarrow (\text{مجموع}) \text{ (avg. power)}.$$

For Balanced system $\rightarrow P_{3\phi} = 3 P_{1\phi}$

inst. power :-

$$V_{an} = 200 \angle 0 \rightarrow V_{an}(t) = 200\sqrt{2} \cos(\omega t).$$

$$I_a = 2 \angle -60 \rightarrow I_a(t) = 2\sqrt{2} \cos(\omega t - 60).$$

$$p(t) = V_{an}(t) * I_a(t) \\ = 400 \cos(\omega t - 60) \cos(\omega t)$$

$$\# P_a(t) = 200 + 400 \cos(2\omega t - 60)$$

$$\# P_b(t) = 200 + 400 \cos(2\omega t + 60)$$

$$\# P_c(t) = 200 + 400 \cos(2\omega t - 180)$$

} instantaneous
power

But

$$P(t)_{total} = P_a(t) + P_b(t) + P_c(t).$$

$$= 600 + 400 \cos(2\omega t - 60) + 400 \cos(2\omega t + 60) + 400 \cos(2\omega t - 180) \Bigg] \text{Zero.}$$

$$= 600 \text{ W}$$

$$\rightarrow P_{inst} = P_{avg} \text{ in } 3\phi$$

$$P = \omega T \rightarrow P \rightarrow \text{constant. } \{ \omega, T \rightarrow \text{constant} \}$$

↳ less vibration and stress on the mechanical system.


(ex) a Balanced 3ϕ system with $V_{LL} = 300\text{ V}$
and supplying a balanced Y -connected load

\rightarrow By default

with (1200 W) @ a leading power factor = .8

• Find the line current and the per phase load impedance?

(ex) Sol

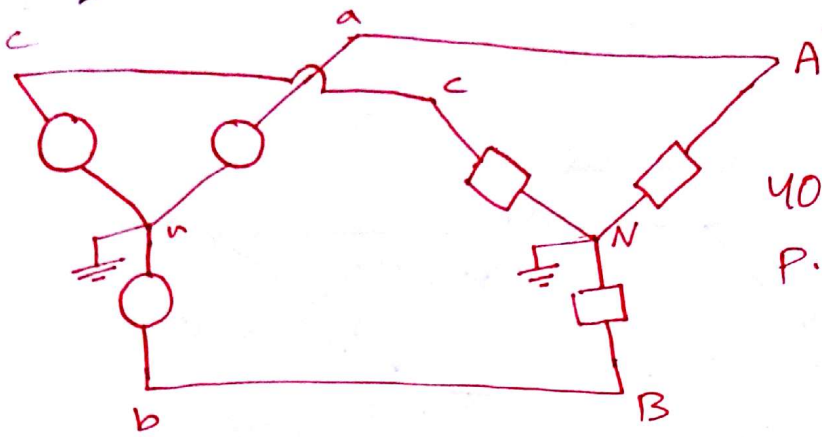


400 W
P.F. = .8 leading

$$V_{ab} = 300 / \sqrt{3}$$

↓

single phase equ ckt:-

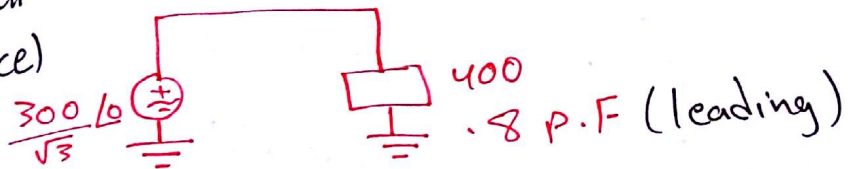
$$V_{an} = \frac{300}{\sqrt{3}} \angle 0^\circ \rightarrow \text{By default (reference)}$$



$I_{a \text{ line}} = I_{\text{phase}}$

$P = V_{an} I_a \text{ P.F.}$
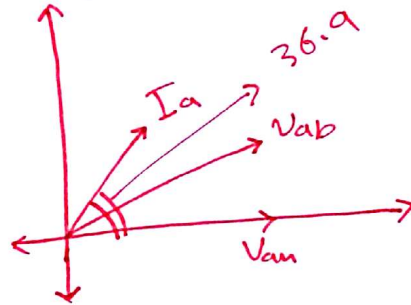
$$400 = \frac{300}{\sqrt{3}} * I_a * .8$$




$$|I_a| = 2.89 \text{ A} \rightarrow \cos^{-1}(.8)$$

$$I_a = 2.89 \angle +36.9^\circ$$


* Find the per phase impedance?

$$Z = \frac{V_{an}}{I_a} = \frac{\frac{300}{\sqrt{3}} \angle 0^\circ}{2.89 \angle 36.9^\circ} = 60 \angle -36.9^\circ \Omega$$

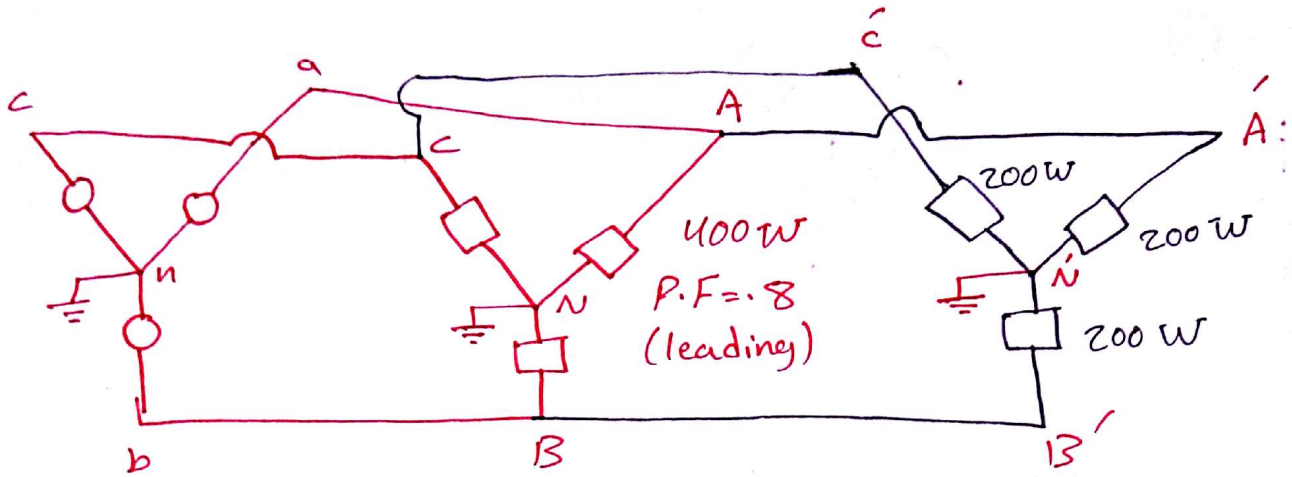(ex) Find the line current if a 600 W load is added in parallel with the previous load? 10



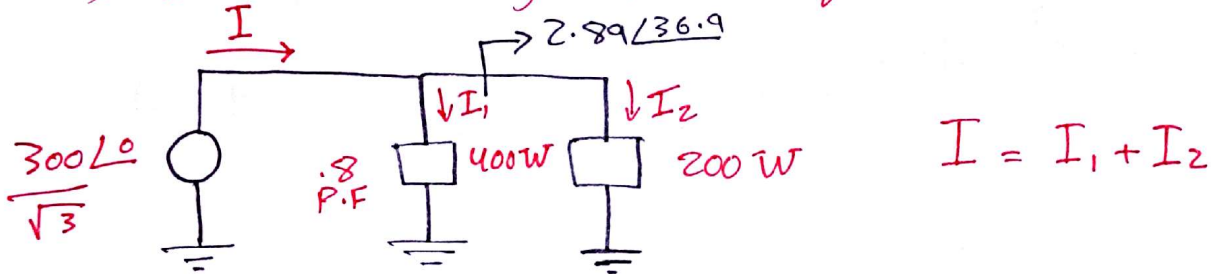⇒ Draw the single phase equivalent ckt :-



Find I_2 :-

$$P = V_{\text{cm}} I_2 \text{ P.F.}$$

$$200 = \frac{300}{\sqrt{3}} * I_2 * 1$$

$$I_2 = 1.155 \angle 0$$


$$I_{\text{total}} = I_1 + I_2$$

$$= 2.89 \angle 36.9 + 1.155 \angle 0$$

$$= 3.87 \angle 26.6$$

$$P = \frac{300}{\sqrt{3}} * 3.87 * \cos(0 - 26.6) = 600 \text{ W } \{ 1\phi \}$$
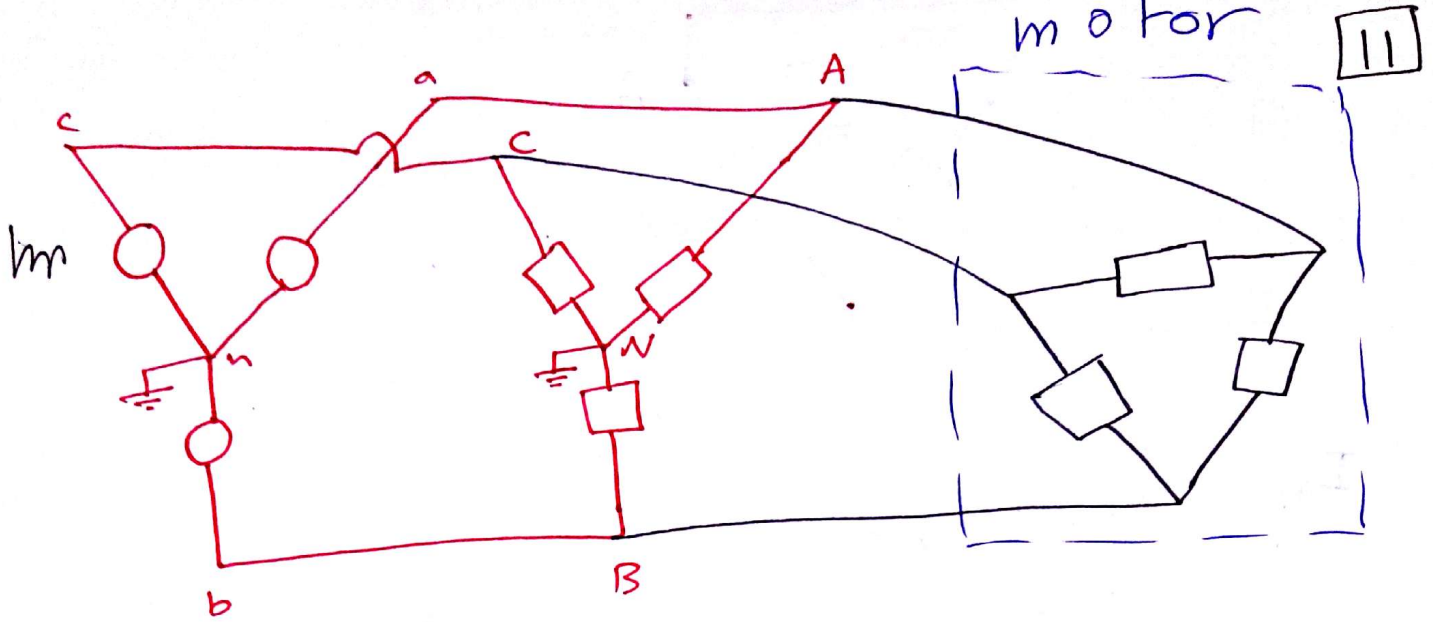
$$P_{3\phi \text{ source}} = 600 * 3 = 1800 \text{ W}$$




Delta connection \rightarrow (useful)

- increase the voltage.
- No neutral.

Y source \triangle load:

\Rightarrow the neutral point is not always accessible

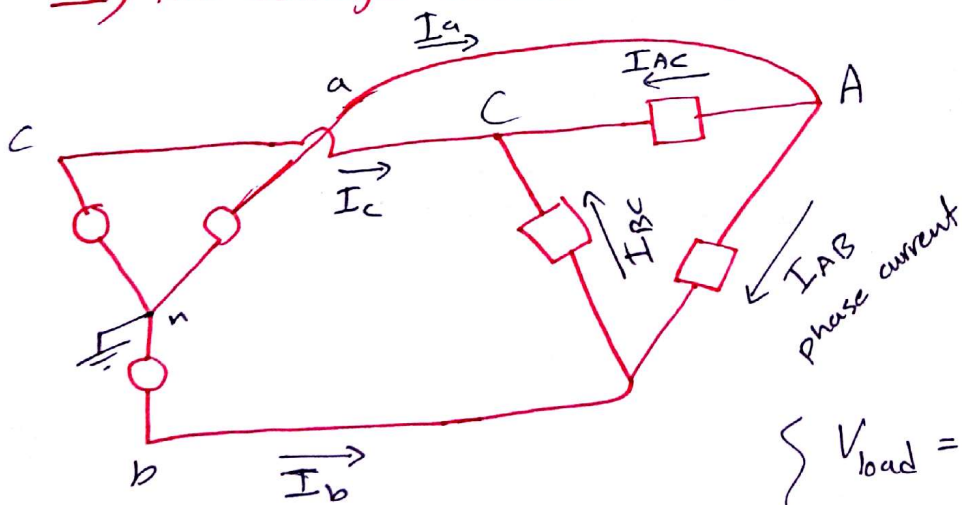\Rightarrow the voltage across the phase is V_{LL}



$$I_a \neq I_{AB}$$


the voltage across any load is line-to-line voltage.

$$V_{load} = V_{LL} = |V_{AB}| = |V_{BC}| = |V_{CA}|$$

$$V_{AB} = \sqrt{3} V_p \angle +30^\circ$$

$$V_{BC} = \sqrt{3} V_p \angle -90^\circ$$
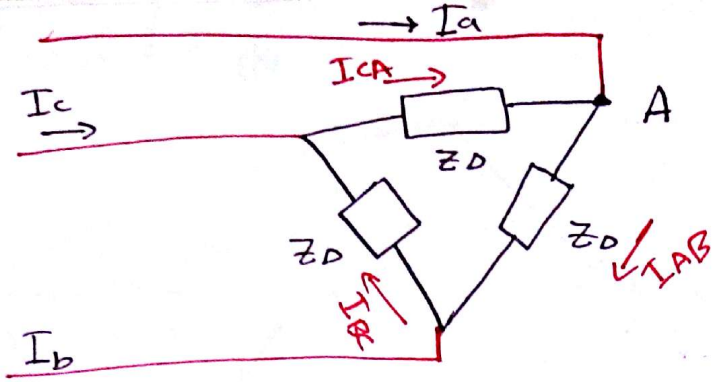
$$V_{CA} = \sqrt{3} V_p \angle 150^\circ$$



$$I_{AB} = \frac{V_{AB}}{Z_D} = I_p \angle 0$$

$$I_a \neq I_{AB}$$

$$I_{BC} = \frac{V_{BC}}{Z_D} = I_p \angle -120$$

$$I_{CA} = \frac{V_{CA}}{Z_D} = I_p \angle 120$$

- apply KCL at (A):-

$$I_a + I_{CA} = I_{AB} \rightarrow I_a = I_{AB} - I_{CA}$$

$$I_a = I_p \angle 0 - I_p \angle 120$$

$$I_a = I_p - I_p \underbrace{\cos(120)}_{-\frac{1}{2}} - j I_p \underbrace{\sin(120)}_{\frac{\sqrt{3}}{2}}$$

$$I_a = \frac{3}{2} I_p - j \frac{\sqrt{3}}{2} I_p = \sqrt{3} I_p \left(\frac{\sqrt{3}}{2} - \frac{1}{2} j \right)$$

$$\rightarrow * I_a = \sqrt{3} I_p \angle -30^\circ$$

$$\rightarrow * I_b = \sqrt{3} I_p \angle -150^\circ$$


$$\rightarrow * I_c = \sqrt{3} I_p \angle 90^\circ$$

ex) what is the line current in a (3 ϕ) system with line voltage of (300)V and supplies (1200)W to a (Δ -connected) load at a lagging P.F of (0.8) - then find the per phase impedance?



sol

① draw \rightarrow

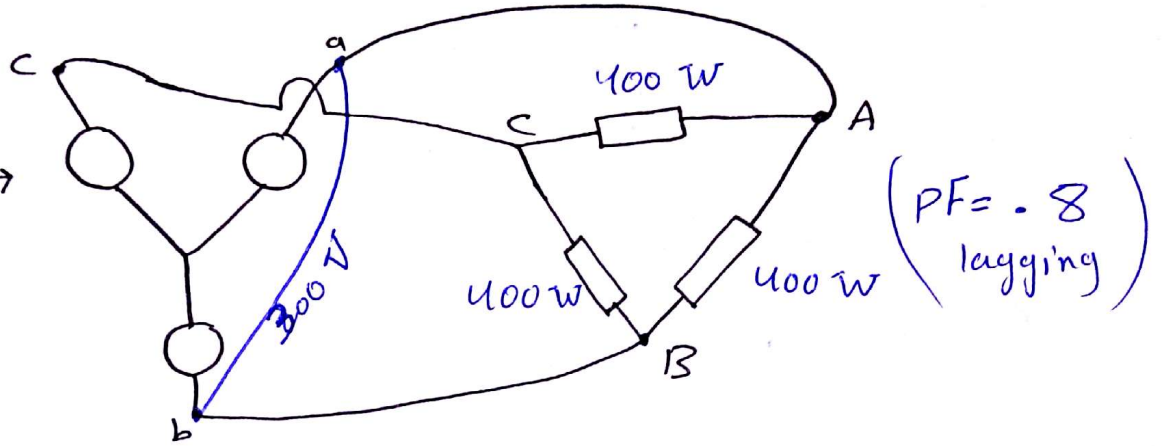

$$\boxed{2} \quad I_{\text{phase}} = \frac{V_{AB}}{Z_D} = I_{AB}$$

$$I_{AB} = \frac{300}{Z_D} \rightarrow P = V_{AB} I_{AB} \cos(\theta)$$

$$400 = 300 * I_{AB} * 0.8$$

$$I_{AB} = \frac{400}{300 * 0.8} = 1.6667 \text{ A}$$

- take V_{AB} as reference:

$$V_{AB} = 300 \angle 0^\circ \rightarrow I_{AB} = 1.6667 \angle \cos^{-1}(0.8) = 1.6667 \angle -36.9^\circ \text{ (lagging)}$$

$$I_a = \sqrt{3} I_{AB} \angle -30^\circ = \sqrt{3} * 1.6667 \angle -36.9^\circ \angle -30^\circ = 2.89 \angle -66.9^\circ \text{ A}$$

$$I_b = 2.89 \angle -66.9^\circ - 120^\circ \text{ A}$$

$$I_c = 2.89 \angle -66.9^\circ + 120^\circ \text{ A}$$



$$* Z_D = \frac{V_{AB}}{I_{AB}} = \frac{300 \angle 0^\circ}{1.667 \angle -36.9} = 180 \angle 36.9 \Omega$$


→ what if the load is (Y) connected?


$$I_a = ??$$

$$P = V_{an} I_a * \cos \theta$$

$$400 = \frac{300}{\sqrt{3}} * I_a * .8$$

$$I_a = 2.84 \text{ A}$$

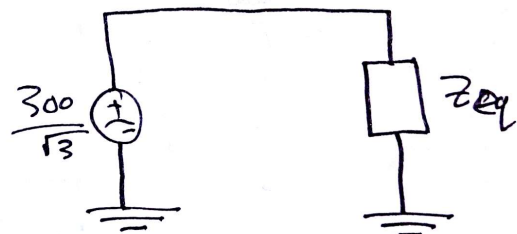


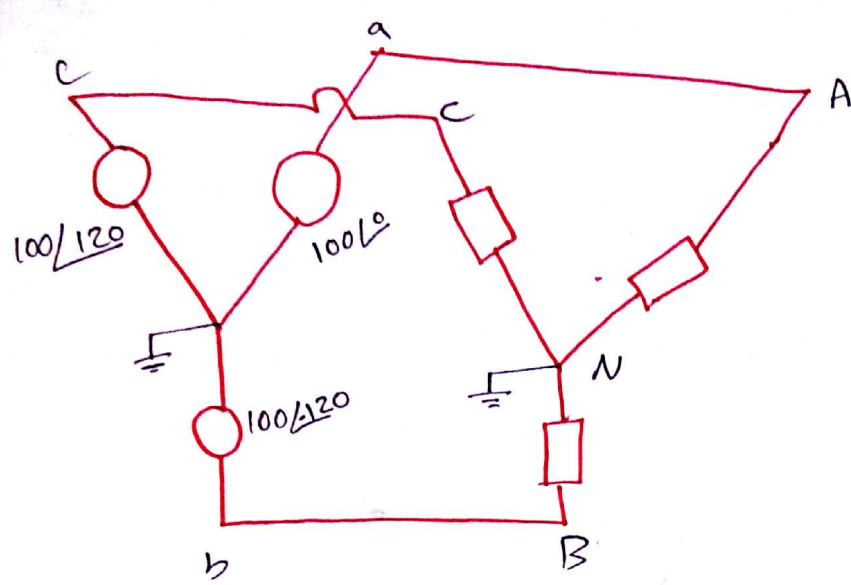

- the voltage across any load phase voltage = 100
 V_{an}, V_{bn}, V_{cn}
 - $I_{\text{phase}} = I_{\text{line}} = \frac{V_{\text{an}}}{Z_Y}$

let $V_p = 100 \text{ V}$
 (Y source \rightarrow Y load)

(Y source \rightarrow Δ load)

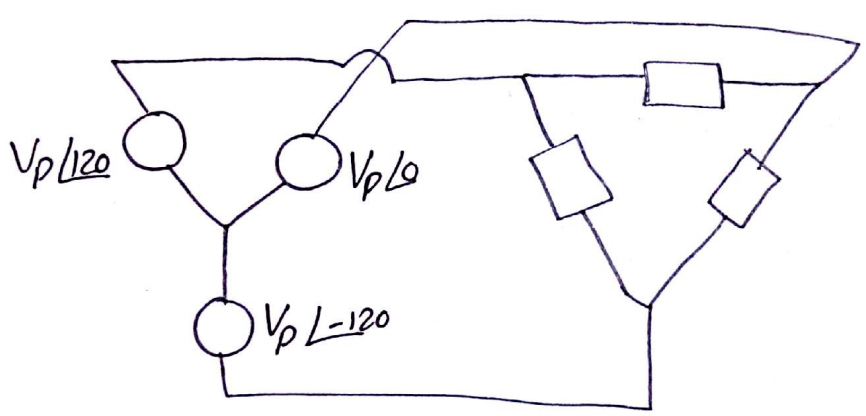

* let $V_p = 100 \text{ V}$
 - the voltage across the load is:
 line voltage = $\sqrt{3} * 100 \angle 0^\circ + 30^\circ$
 $= 173.1 \angle 30^\circ + 0^\circ$

- $I_{\text{line}} \neq I_{\text{phase}}$

- $I_{\text{line}} = \sqrt{3} * I_{\text{phase}} \angle -30^\circ$

- $I_{\text{phase}} = \frac{V_{AB}}{Z_D}$

POWER

(Real) $P_{3\phi} = 3 V_p I_p \cos(\theta_v - \theta_i)$
 $= \sqrt{3} V_L I_L \cos(\theta_v - \theta_i)$

in (Y) connected loads :-

$$I_L = I_p$$

$$V_L = \sqrt{3} V_p$$

in (Δ) connected loads


$$V_L = V_p$$

$$I_L = \sqrt{3} I_p$$

$Q_{3\phi} = \sqrt{3} V_L I_L \sin(\theta_v - \theta_i)$

$\rightarrow S = \sqrt{3} V_L I_L^*$

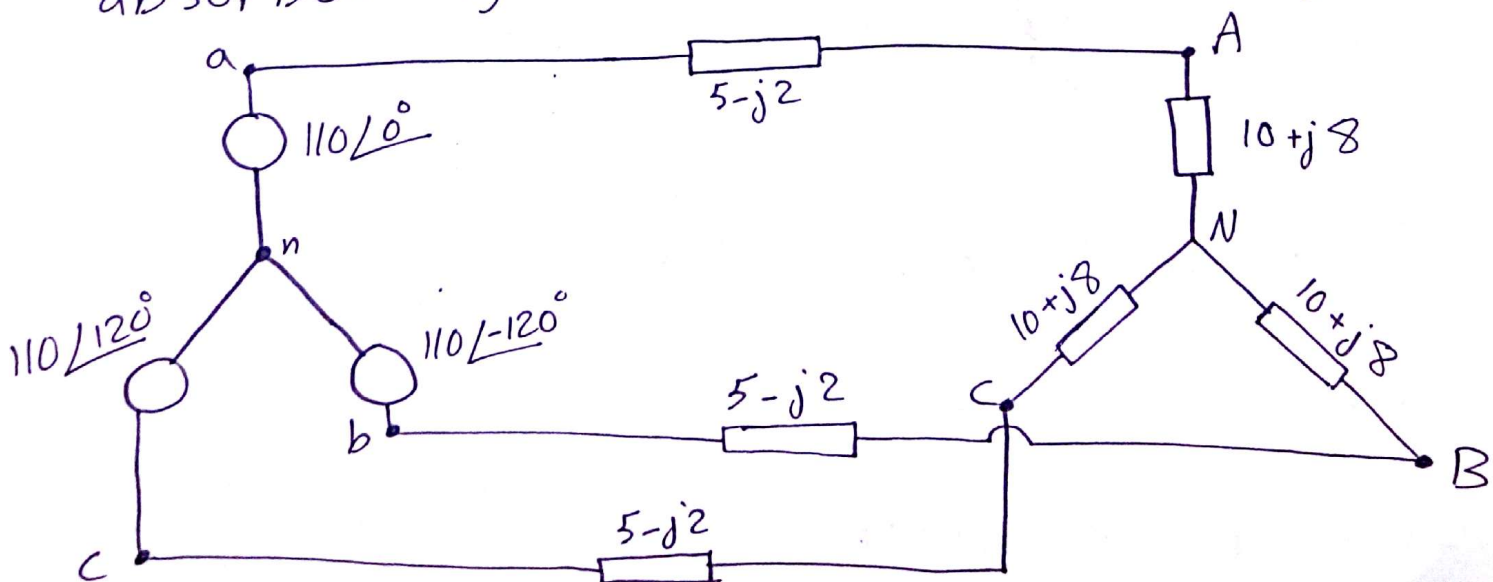ex) Find the complex, Real and Reactive power absorbed by the load for the shown system :-



Sol : since there is an impedance in the transmission lines \rightarrow there is a voltage drop. [16]

$$\rightarrow V_{an} \neq V_{AN}$$

$$\rightarrow V_{bn} \neq V_{BN}$$

$$\rightarrow V_{cn} \neq V_{CN}$$

Reactive power :-

$$Q_A = (V_P I_P \sin \theta)_A$$

$$Q_B = (V_P I_P \sin \theta)_B$$

$$Q_C = (V_P I_P \sin \theta)_C$$

$$\# S_A = (V_P I_P^*)_A = P_A + j Q_A$$

$$S_B = (V_P I_P^*)_B = P_B + j Q_B$$

$$S_C = (V_P I_P^*)_C = P_C + j Q_C$$

$$\rightarrow S_{\text{total (3}\phi)} = 3 V_P I_P^* = 3 S_{(1\phi)}$$


$$\rightarrow |S| = |V_P| |I_P|$$

$$\rightarrow |S_{3\phi}| = 3 |V_P| |I_P|$$

\rightarrow حل السؤال
في صفحة [17]

→ Draw the single phase equivalent crkt 8 -

17

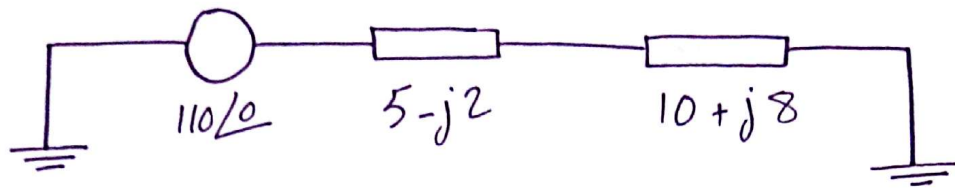

- For phase A :-

$$I_p = I_{line} = \frac{110 \angle 0^\circ}{5 - j2 + 10 + j8} = 6.8 \angle -21.8^\circ \text{ A}$$

(source)

$$\begin{aligned} \rightarrow \int_{3\phi} &= 3 V_p I_p^* = 3 * 110 \angle 0^\circ * 6.8 \angle 21.8^\circ \\ &\downarrow \text{supplied by the voltage source} \quad \downarrow \text{source voltage} \\ &= 2247 \angle 21.8 \text{ VA} \\ &= \underbrace{2084}_{P_{3\phi}} + j \underbrace{834.4}_{Q_{3\phi}} \text{ VA} \end{aligned}$$

(source)

$$\begin{aligned} \rightarrow P_{3\phi} &= 3 |V_p| |I_p| \cos(\theta) = 3 * 110 * 6.8 * \cos(21.8) \\ &= 2084 \text{ W} \end{aligned}$$

(source)

$$\begin{aligned} \rightarrow Q_{3\phi} &= 3 |V_p| |I_p| \sin\theta = 3 * 110 * 6.8 * \sin(21.8) \\ &= 834.4 \text{ VAR} \end{aligned}$$

same as previous.

(load)

$$\rightarrow \sum_{3\phi} = 3 \underbrace{V_p}_{\substack{\downarrow \\ \text{load voltage}}} I_p^*$$

18

$$\begin{aligned} * V_p \text{ load} &= V_{p(\text{source})} * \frac{10 + j8}{10 + j8 + 5 - j2} = 110 \angle 0^\circ * \frac{10 + j8}{15 + j6} \\ &= 87.3 \angle 16.8^\circ \end{aligned}$$

$$\rightarrow \sum_{3\phi} = 3 * 87.3 \angle 16.8^\circ * 6.8 \angle 21.8^\circ$$

$$\sum_{3\phi} = \underbrace{1392}_{P_{3\phi}} + j \underbrace{1113}_{Q_{3\phi}} \text{ VA}$$

#OR

$$\begin{aligned} \sum_{3\phi} &= 3 V_p I_p^* & , V_p \text{ load} &= I_p \text{ load} * Z_{p \text{ load}} \\ &= 3 * (I_p * Z_p) * I_p^* \\ &= 3 * |I_p|^2 * Z_p = 3 * |6.8|^2 * 10 + 8j \\ &= \underbrace{1392}_{P_{3\phi}} + j \underbrace{1113}_{Q_{3\phi}} = 1782 \angle 36.6^\circ \quad \# \end{aligned}$$

load

$$\begin{aligned} \rightarrow P_{3\phi} &= 3 V_p I_p \cos \theta = 3 * 110 \angle 0^\circ * \left(\frac{10 + 8j}{15 + j6} \right) * 6.8 \cos(\theta) \\ &= 3 * 87.3 * 6.8 * \cos(16.8 + 21.8) \\ &= 1392 \text{ W} \end{aligned}$$

load

$$\begin{aligned} \rightarrow Q_{3\phi} &= 3 V_p I_p \sin \theta = 3 * 87.3 * 6.8 * \sin(16.8 + 21.8) \\ &= 1113 \text{ VAR} \end{aligned}$$

→ lost power :-

19

$$* P_{\text{loss}} = 3 |I|^2 \underline{R} \rightarrow \left(\text{resistance of } \frac{5-j2}{x} \right)$$

$$= 3 * (6.8)^2 * 5 = 693.6$$

$$* P_{\text{loss}} + P_{\text{load}} = P_{\text{source}}$$

$$693 + 1392 \stackrel{?}{=} 2087$$

$$2087 = 2087 \checkmark$$

$$* Q_{\text{loss}} = 3 |I|^2 X_c$$

$$= (3) * (6.8)^2 * (-2) = \therefore 278 \text{ VAR}$$

↳ because it's a capacitance load.

(# (Y-Δ) → include in first exam.)