

Spring017



Dr. Mohammed Alhajj

BY:

Omar Abuserrieh

Powerunit-ju.com


# \* Revision :-

(ex) Calculate & sketch  $i_c(t)$  when  $v_c(t) = 5(1 - e^{-t/10^{-6}})$   
 \*  $C = 0.1 \mu F$


Sol:  $i_c(t) = C \cdot \frac{dV}{dt}$

$i_c(t) = (0.1 \mu) * (5 \cdot \frac{1}{\mu} \cdot e^{-t/10^{-6}})$

$i_c(t) = .5 e^{-t/10^{-6}} A$

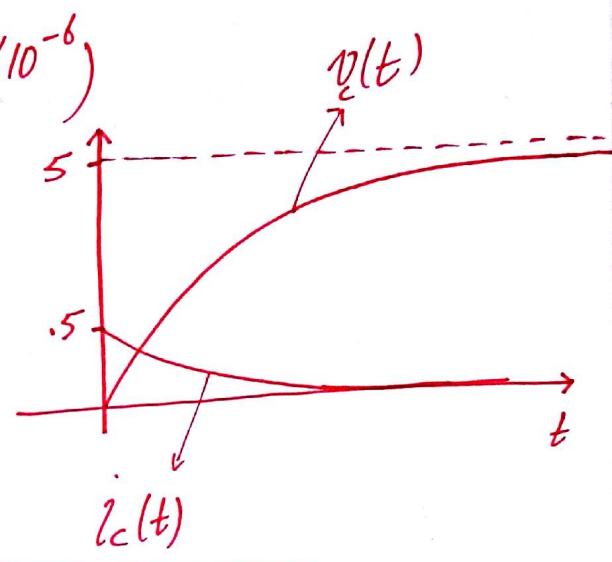


## # Impedance & phasor Domain :-

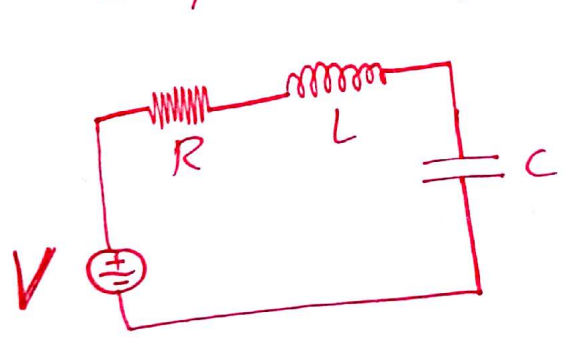

\*  $v(t) = i(t) * R + L \frac{di(t)}{dt} + \frac{1}{C} \int_{-\infty}^t i_c(t) dt$

- changing to phasor Domain :-

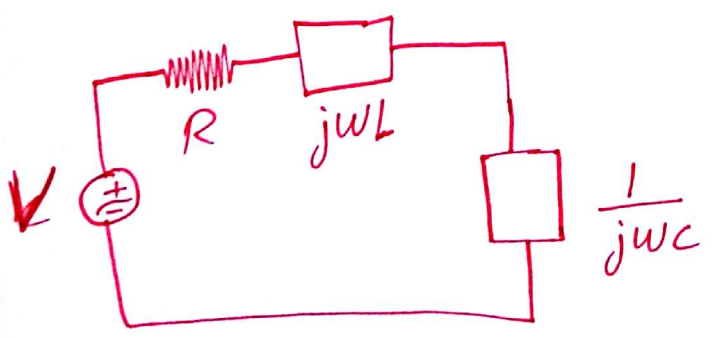

\*  $V = I (R + j\omega L + \frac{1}{j\omega C})$

# to change From time Domain to phasor Domain

① Function in time domain must be periodic source.

② must be in the form of  $\begin{cases} V_m \cos(\omega t + \theta_v) \\ I_m \cos(\omega t + \theta_i) \end{cases}$

③ the phasor domain is in the form -

$$- V_m \angle \theta_v$$

$$- I_m \angle \theta_i$$

(ex) calculate and sketch  $v_L(t)$  when  $i_L(t) = 20te^{-2t}$  A and  $L = 0.1$  H



$$v_L = j\omega L I_L$$

$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$= 0.1 * [-40te^{-2t} + 20e^{-2t}]$$

$$= 2e^{-2t} [1 - 2t]$$

$$I_L = 20te^{-2t}$$

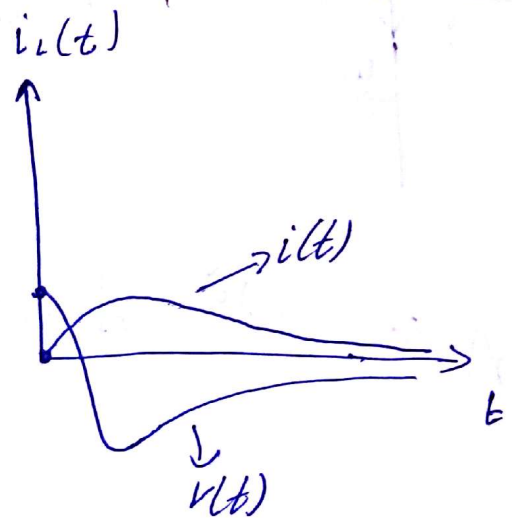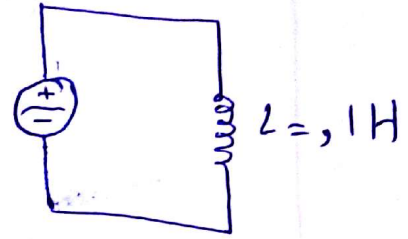


$i(t) = C \frac{dv}{dt} \Rightarrow$  the capacitor ~~current~~

voltage can not be changed instantaneously


(ex)

$$\omega = 1000$$

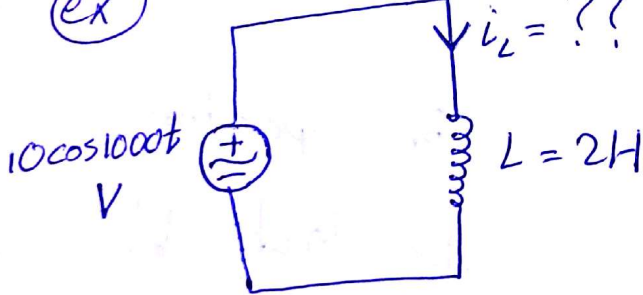

$i_L(0) = 0 \Rightarrow$  For inductor  $v$  leads  $I$  by  $\frac{\pi}{2}$

(time domain)

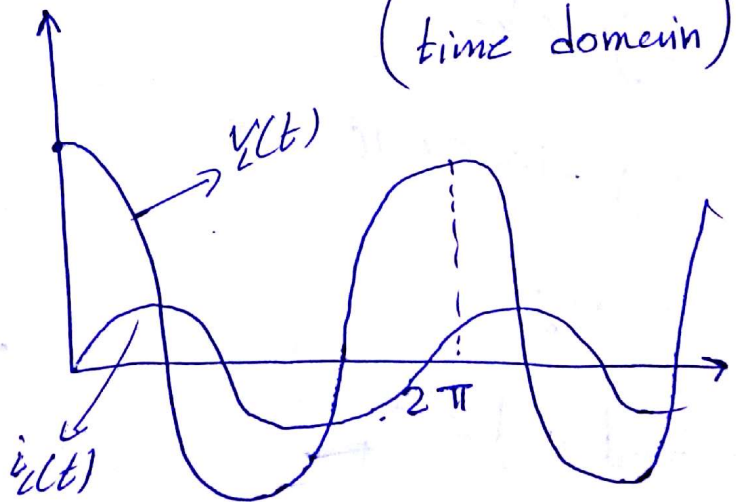

$$v_L(t) = L \frac{di_L(t)}{dt}$$


$$i_L(t) = \frac{1}{L} \int_0^t v_L(t) dt$$

$$= 0.5 * \frac{10}{1000} \sin 1000t = 0.05 \sin 1000t \text{ A}$$

(1)



(Phasor domain)

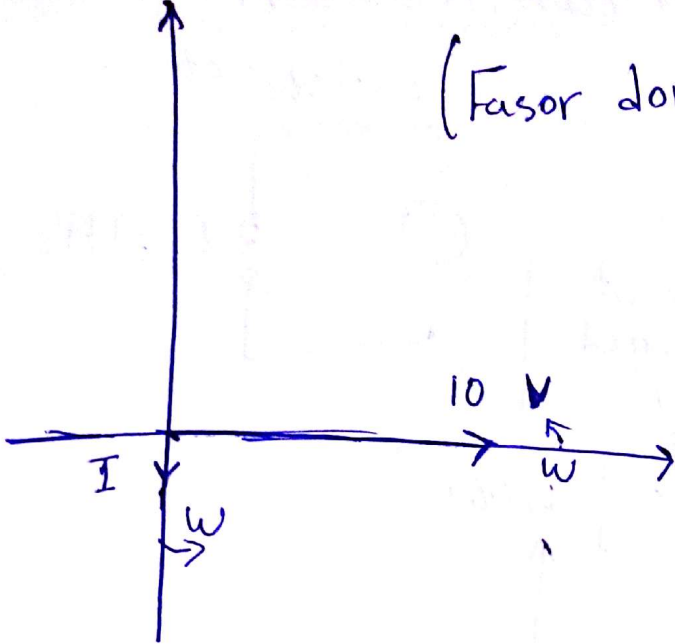

$$V = 10 \angle 0$$


$$I = 0.05 \angle -\frac{\pi}{2}$$

$$A \angle \theta = A e^{j\theta} = A \cos \theta + j A \sin \theta$$

$$j = 1 \angle \frac{\pi}{2}$$

$$-j = 1 \angle -\frac{\pi}{2}$$

ex

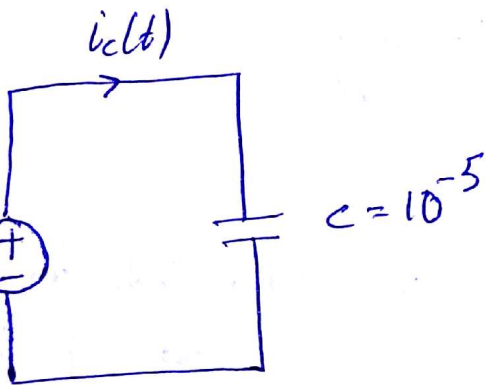

$$V_c(t) = 10 \cos 1000t$$

$$V_c = 10 \angle 0$$

$$= 10$$

$$I_c = j\omega C V_c$$


$$= j * 1000 * 10^{-5} * 10$$

$$= 0.1j$$

$$= 0.1 * 1 \angle \frac{\pi}{2}$$

For capacitors

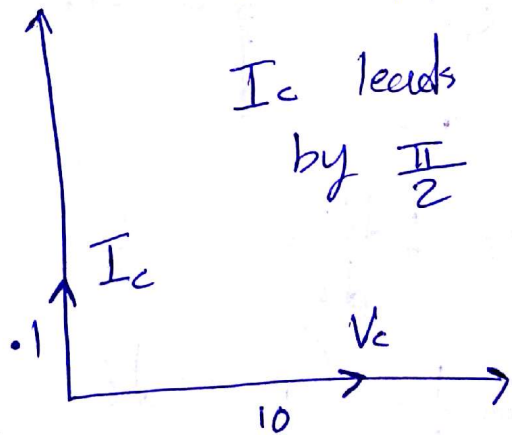$I_c$  leads  $V_c$   
by  $\frac{\pi}{2}$




↳ time domain

$$i_c(t) = 0.1 \cos(1000t + \frac{\pi}{2}) = 0.1 \sin(\omega t)$$

②

(ex)

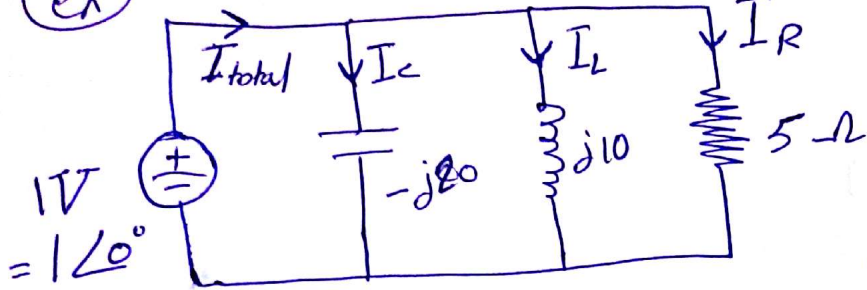

Find the current every where?

$$I_{total} = I_R + I_L + I_c$$

$$I_R = \frac{1\angle 0^\circ}{5} = .2\angle 0^\circ$$

$$I_L = \frac{1\angle 0^\circ}{10j} = -j \cdot .1 = .1\angle -\frac{\pi}{2}$$


$$I_c = \frac{1\angle 0^\circ}{-j20} = j \cdot .05 = 0.05\angle \frac{\pi}{2}$$

$$I_{total} = .2 + \cancel{.1\angle -\frac{\pi}{2}} + .1j + .05j = .2 - j0.05$$

in polar form


$$A = \sqrt{(Re)^2 + (Im)^2} = \sqrt{(.2)^2 + (.05)^2}$$
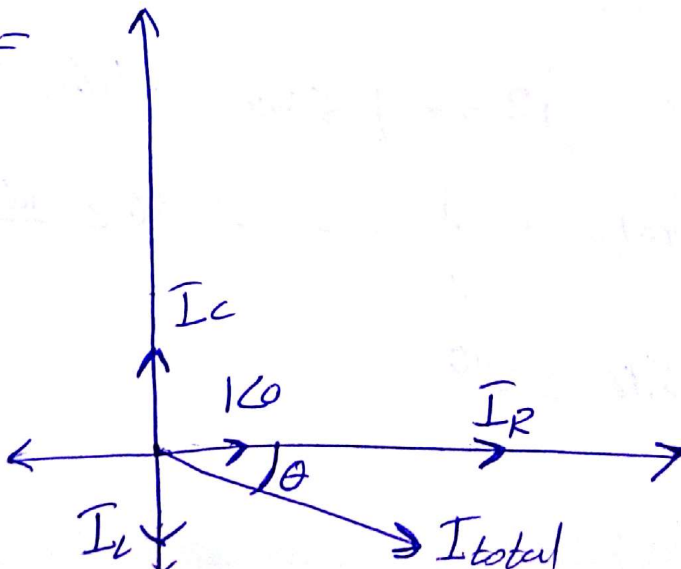
$$\theta = \tan^{-1}\left(\frac{-.05}{.2}\right) =$$



(3)

ex) Draw all phasors:-

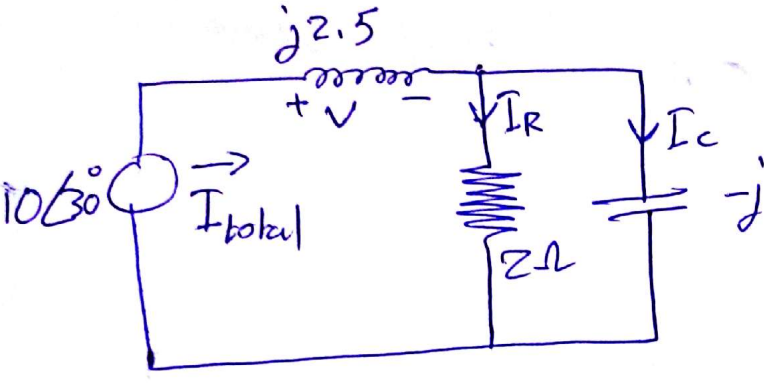


$$I_{total} = \frac{10 \angle 30^\circ}{j2.5 + 2 \parallel -j}$$

$$2 \parallel -j = \frac{-j^2}{2-j}$$

$$I_{total} = \frac{10 \angle 30^\circ}{(2-j)j2.5 + \frac{-j^2}{2-j}}$$
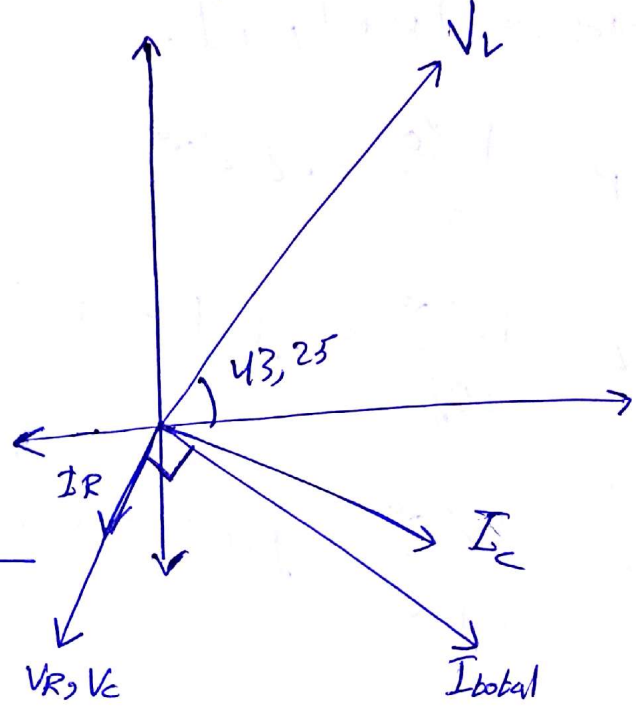
$$= \frac{10 \angle 30^\circ (2-j)}{j5 - 2.5 - j^2} = \frac{10 \angle 30^\circ (2-j)}{2.5 + j3}$$



$$I_{total} = 3.92 - j4.14 = 5.72 \angle -46.75^\circ$$

$$V_L = j2.5 * [5.72 \angle -46.75^\circ] = 14.3 \angle 43.25^\circ$$

$$I_R = I_{total} \frac{-j}{2-j} = 2.56 \angle -110^\circ$$

$$V_R = 5.12 \angle -110^\circ$$

$$V_C = V_R$$

$$I_C = \frac{V_C}{Z_C} = \frac{5.12 \angle -110^\circ}{-j1}$$

$$= 5.12 \angle -20^\circ$$


Find  $V_1 + V_2$  in time domain

$$V_1(t) = 15 \cos(377t + \frac{\pi}{4}) = 15 \angle \frac{\pi}{4}$$

$$V_2(t) = 15 \cos(377t + \frac{\pi}{6}) = 15 \angle \frac{\pi}{6}$$


$$V_1 + V_2 = 15 \cos \frac{\pi}{4} + j 15 \sin \frac{\pi}{4} + 15 \cos \frac{\pi}{6} + j 15 \sin \frac{\pi}{6}$$

Rectangular

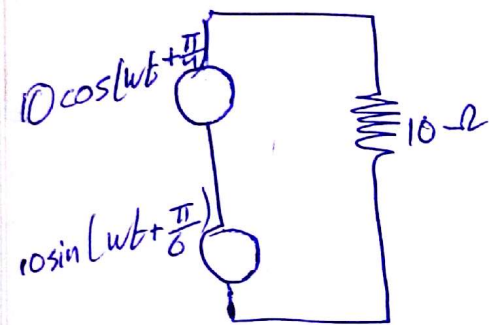

$$V_1 = 10 \angle \frac{\pi}{4}$$

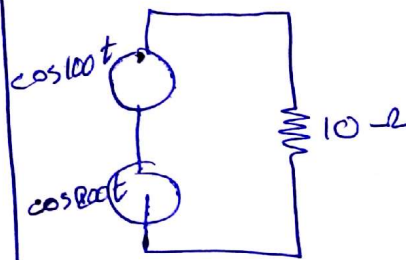
$$V_2 = 10 \angle \frac{\pi}{6} - \frac{\pi}{2}$$



No phasor  
Domain



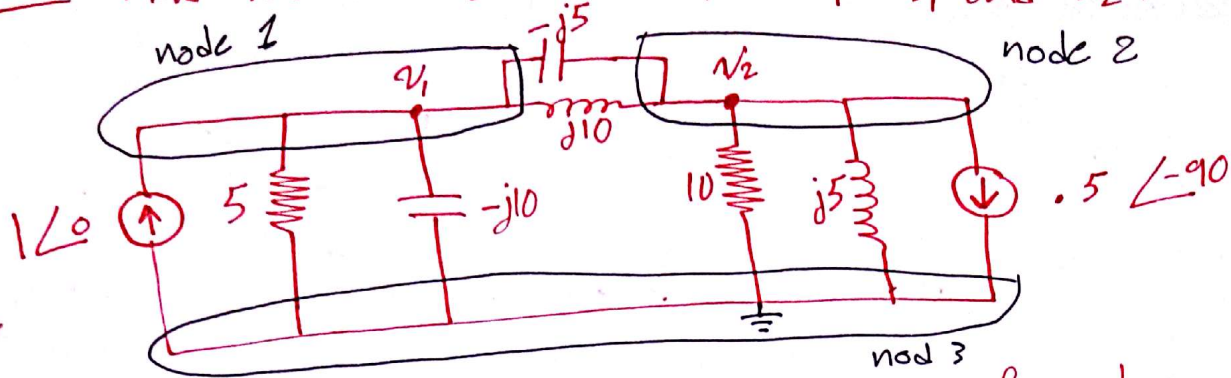ex Find the time domain value of  $v_1$  and  $v_2$  :-



# of equations for mesh analysis: # of meshes - # of current sources

# of equations for nodal analysis: # of nodes - # of voltage sources - 1

\* independent sources

Reference node ←

@ node 1 :-

$$1\angle 0 + \frac{0 - v_1}{5} + \frac{0 - v_1}{-j10} + \frac{v_2 - v_1}{j10} + \frac{v_2 - v_1}{-j5} = 0$$

at node ② :-

$$-.5\angle -90 + \frac{0 - v_2}{j5} + \frac{-v_2}{10} + \frac{v_1 - v_2}{j10} + \frac{v_1 - v_2}{-j5} = 0$$

solve 2 eq :-

$$v_1 = 1 - j2 = 2.24 \angle -63.4 = 2.24 \cos(\omega t - 63.4) \text{ V}$$

$$v_2 = -2 + j4 = 4.47 \angle 116.6 = 4.47 \cos(\omega t + 116.6) \text{ V}$$

$v_1$  leads  $v_2$  by  $180^\circ$


$v_2$  leads  $v_1$  by  $180^\circ$

180° phase difference  
is phasor

lead




Q Find thevenin eq seen by " $-j10$ "

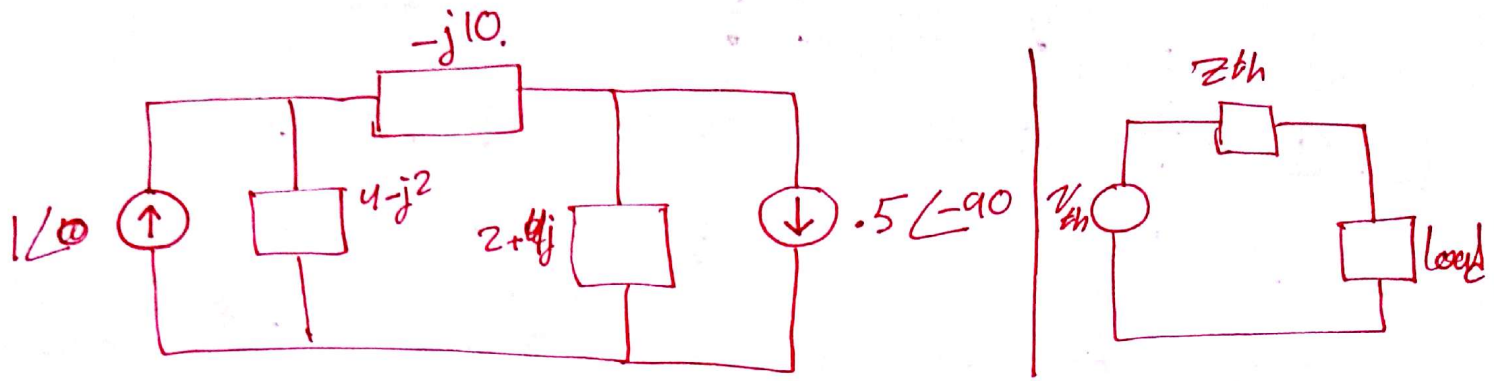

\*  $Z_{Th}$ : ① Kill all sources   
 $Z_{Norton}$    
 voltage → ~~short~~ circuit   
 current → ~~short~~ circuit open   
 and find  $Z_{equiv}$

②  $\frac{V_{o.c}}{I_{s.c}}$

sol

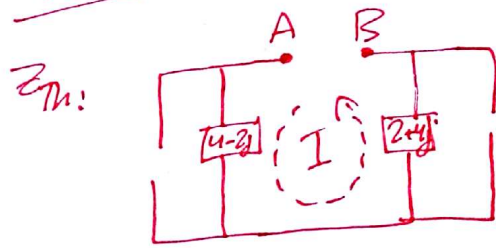


$Z_{Th} = 4-j2 + 2+j4 = (6+j2) \Omega$

\*  $V_{Th}$ :  $V_{o.c}$

\*  $I_{Norton}$ :  $I_{s.c}$


$V_{Th}$

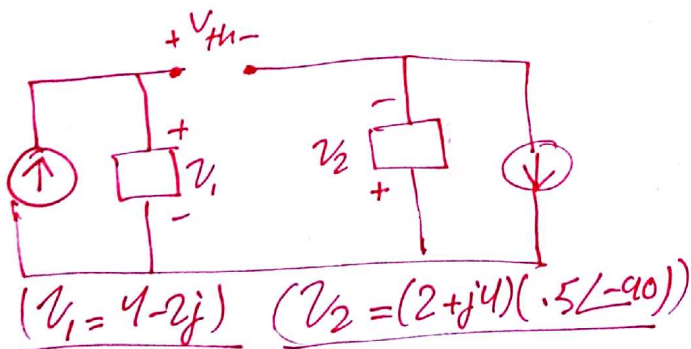


KVL

$-V_1 + V_{Th} - V_2 = 0$



$V_{Th} = V_1 + V_2 = 6-j3$

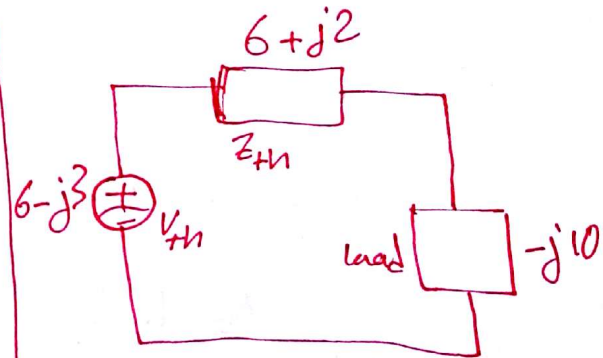

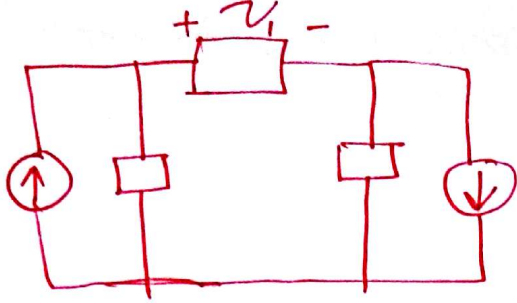



By superposition

$$v_1 = v_1' + v_1''$$

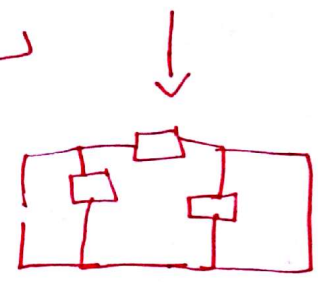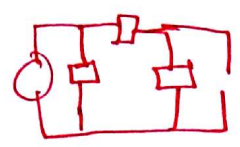

CHP -11- : power analysis :-

Review :-

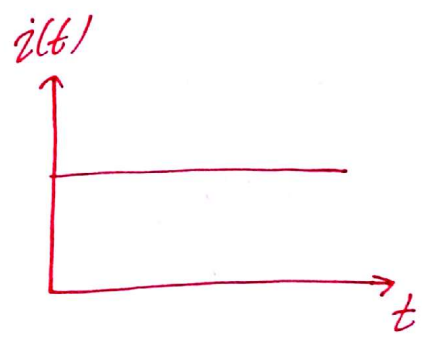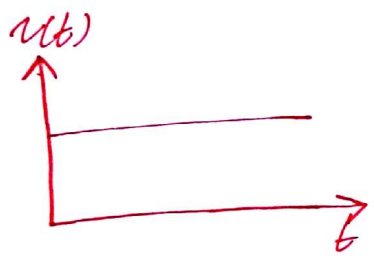

DC

$$P(t) = v(t) * i(t)$$

$$P = v i = V I$$


Instantaneous power :

R  $\rightarrow P(t_0) = v(t) i(t)$

L  $\rightarrow P(t_0) = v(t) i(t) = L \frac{di(t_0)}{dt_0} * i(t_0)$

C  $\rightarrow P(t_0) = v(t) i(t) = v(t) * C \frac{dv(t_0)}{dt_0}$

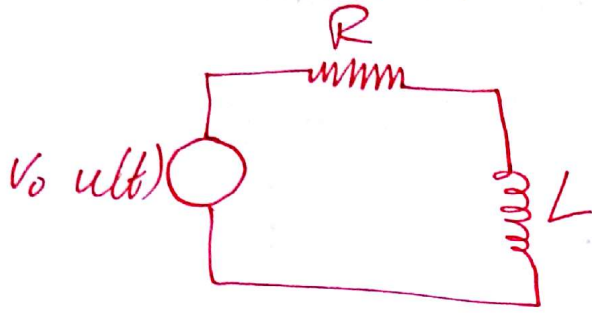ex) Find the inst power across the inductor



$$i(t) = \frac{V_0}{R} \left(1 - e^{-\frac{Rt}{L}}\right) u(t)$$
$$= \frac{V_0}{R} u(t) - \frac{V_0}{R} e^{-\frac{Rt}{L}} u(t)$$

source Ins. power:

$$P(t) = v(t) i(t) = \frac{V_0^2}{R} \left(1 - e^{-\frac{Rt}{L}}\right) u(t)$$

ins. power across  $R$  :-

$$P_R(t) = v(t) i(t) = R i^2(t) = \frac{v(t)^2}{R}$$
$$= R \left[ \left(\frac{V_0}{R}\right)^2 \left(1 - e^{-\frac{Rt}{L}}\right)^2 u(t) \right] = \frac{V_0^2}{R} \left(1 - e^{-\frac{Rt}{L}}\right)^2 u(t)$$

Inst. power across  $L$  :-


$$P(t) = L \frac{di(t)}{dt} * i(t) = L * \frac{-R}{L} * e^{-\frac{Rt}{L}} * \frac{V_0}{R} * \frac{V_0}{R} \left(1 - e^{-\frac{Rt}{L}}\right) u(t)$$

$$P(t) = \frac{V_0^2}{R} \left(e^{-\frac{Rt}{L}}\right) \left(1 - e^{-\frac{Rt}{L}}\right) u(t)$$

(a)



EX

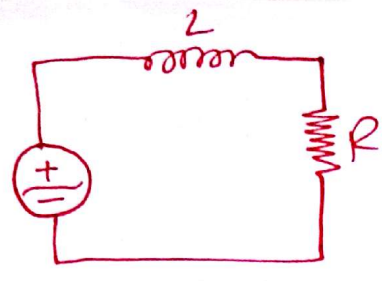

\* source inst. power

$$p(t) = v(t) i(t)$$

$$p(t) = V_m \cos \omega t * I_m \cos(\omega t + \phi)$$

$$\# \cos x * \cos y = \frac{\cos(x+y) + \cos(x-y)}{2}$$


$$p(t) = \frac{V_m I_m}{2} [\cos(2\omega t + \phi) + \cos \phi]$$

$$v(t) = V_m \cos \omega t$$

$$i(t) = I_m \cos(\omega t + \phi)$$

$$I_m = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}}$$
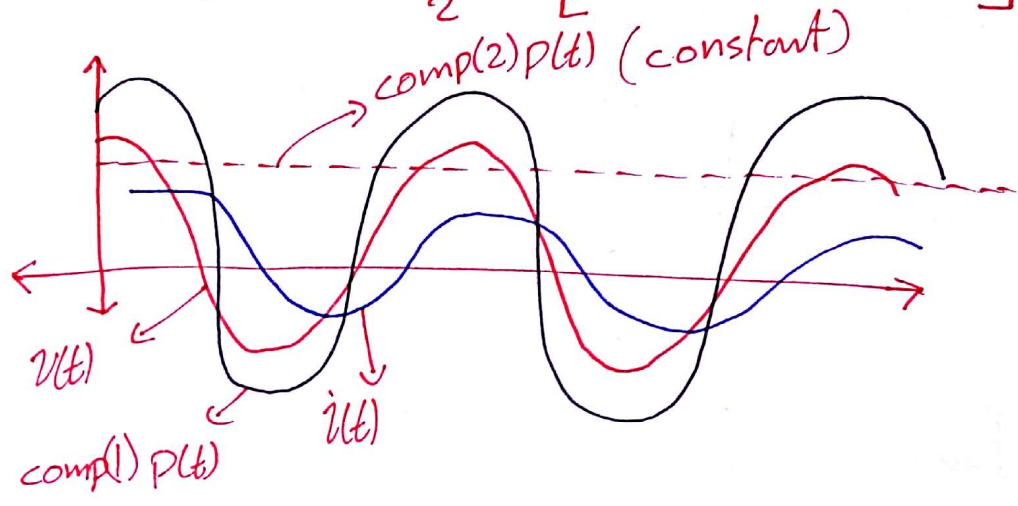
$$\phi = \tan^{-1} \left( \frac{\omega L}{R} \right)$$




# Average power: more accurate & efficient

$$P_{avg} = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} p(t) dt$$



- for a periodic signal
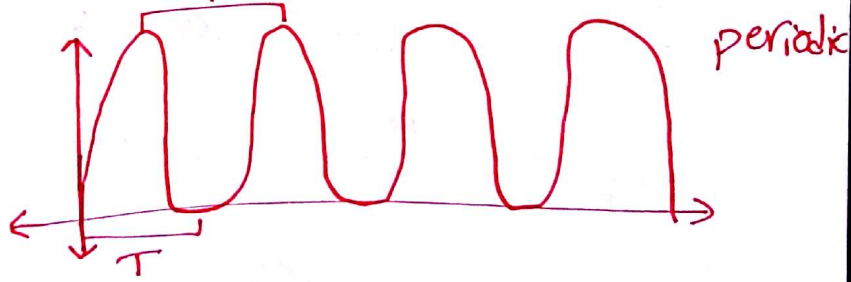
$$P_{avg} = \frac{1}{T} \int_0^T p(t) dt$$



\* let's ~~assume~~ assume:-

$$v(t) = V_m \cos(\omega t + \theta)$$

$$i(t) = I_m \cos(\omega t + \phi)$$

} for any element

- Find the average power

$$p(t) = v(t) * i(t) = V_m \cos(\omega t + \theta) * I_m \cos(\omega t + \phi)$$

$$p(t) = \frac{V_m I_m}{2} [\cos(2\omega t + \theta + \phi) + \cos(\theta - \phi)]$$

$$P_{avg} = \frac{1}{T} \int_0^T p(t) dt$$

$$P_{avg} = \frac{1}{T} \left[ \int_0^T \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi) dt + \int_0^T \frac{V_m I_m}{2} \cos(\theta - \phi) dt \right]$$

$$P_{avg} = \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(\theta - \phi) dt$$

\* the integration for any sinusoidal function for any period equal zero

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

# For a resistive load :-

$$P_{avg} = \frac{V_m I_m}{2} \rightarrow (\theta - \phi) = 0^\circ = \frac{I_m^2 R}{2} = \frac{V_m^2}{2R}$$

# For an inductor :-

$$P_{avg} = 0 \rightarrow (\theta - \phi) = 90^\circ$$


# For a capacitor :-

$$P_{avg} = 0 \rightarrow (\theta - \phi) = -90^\circ$$



(ex)
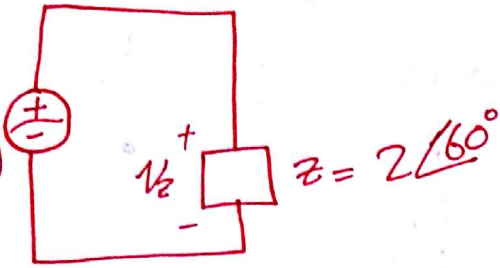
$$v(t) = 4 \cos\left(\frac{\pi}{6}t\right)$$



\*find  $P(t)$ ,  $P_{avg}$  for the element

sol)  $v(t) = 4 \cos\left(\frac{\pi}{6}t\right) = 4 \angle 0^\circ$

$$\omega = \frac{\pi}{6}$$

$$I = \frac{V}{Z} = \frac{4 \angle 0^\circ}{2 \angle 60^\circ} = 2 \angle -60^\circ = 2 \cos\left(\frac{\pi}{6}t - 60^\circ\right)$$

$$P(t) = v(t) i(t) = 4 \cos\left(\frac{\pi}{6}t\right) * 2 \cos\left(\frac{\pi}{6}t - 60^\circ\right)$$

$$= 4 \left[ \cos\left(\frac{\pi}{3}(t - 60^\circ)\right) + \cos(60^\circ) \right]$$

$$= \left[ 2 + 4 \cos\left(\frac{\pi}{3}t - 60^\circ\right) \right] W$$



$$P_{avg} = 2 W$$

(ex) Find the average power delivered to the Impedance :-

$$I = 3 + j4 = \sqrt{4 + 16} \angle \tan^{-1}\left(\frac{4}{3}\right)$$


$$P_{avg} = \frac{V_m I_m}{2} = \frac{I_m^2 R}{2}$$

$$= \frac{(5)^2 * 8}{2} = 100 W$$

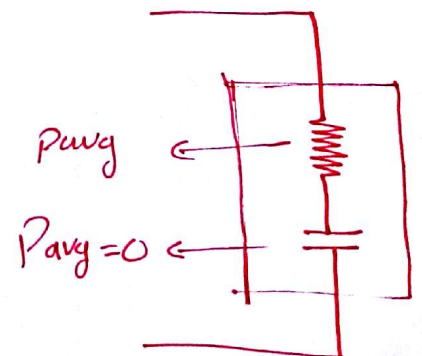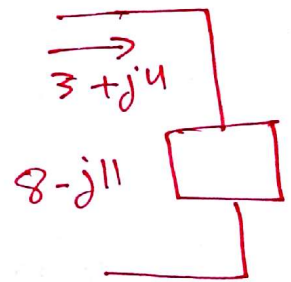

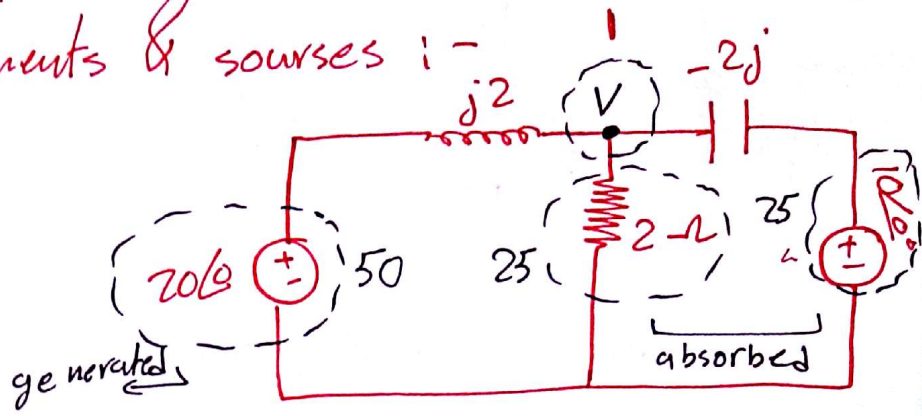(12)

(ex) Find the average power absorbed or generated by elements & sources :-



$$P_{avg}(j2) = 0$$

$$P_{avg}(-j2) = 0$$

at node -1-

$$\frac{20\angle 0 - V}{j2} + \frac{0 - V}{2} + \frac{10\angle 0 - V}{-j2} = 0$$

$$V = 10\angle -90 = -j10$$

$$P_{avg}(R) = \frac{V_m^2}{2R} = \boxed{25 \text{ W}}$$

$$I_1 = \frac{20\angle 0 - 10\angle -90}{j2} = 5 - j10 = 11.18\angle -63.43$$

$$P_{avg}(\text{source}) = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

$$= \frac{20 * 11.18}{2} \cos(0 + 63 + 43) = \boxed{50 \text{ W}}$$


$$I_2 = \frac{10\angle 0 - 10\angle -90}{-j2} = 5 - j5 = 7.07\angle -45$$

$$P_{avg}(10\angle 0) = \frac{10 * 7.07}{2} \cos(0 + 45) = \boxed{25 \text{ W}}$$
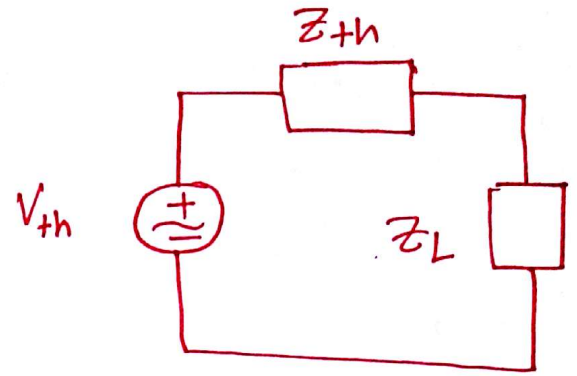
# # Maximum power transfer:-

$$I_L = \frac{V_{th}}{Z_{th} + Z_L}$$

$$I_L = \frac{V_{th}}{R_{th} + jX_{th} + R_L + jX_L}$$



$$V_L = V_{th} * \frac{Z_L}{Z_{th} + Z_L} = \frac{R_L + jX_L}{R_{th} + jX_{th} + R_L + jX_L} * V_{th}$$

$$|V_L| = |V_{th}| * \frac{\sqrt{(R_L)^2 + (X_L)^2}}{\sqrt{(R_L + R_{th})^2 + (X_L + X_{th})^2}}$$

$$\angle V_L = \angle V_{th} + \tan^{-1}\left(\frac{X_L}{R_L}\right) - \tan^{-1}\left(\frac{X_L + X_{th}}{R_L + R_{th}}\right)$$

$$|I_L| = \frac{|V_{th}|}{\sqrt{(R_L + R_{th})^2 + (X_L + X_{th})^2}}$$

$$\angle I_L = \angle V_{th} - \tan^{-1}\left(\frac{X_L + X_{th}}{R_L + R_{th}}\right)$$

$$P_{avg}(Z_L) = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

$$= \frac{|V_L| |I_L|}{2} \cos(\angle V_L - \angle I_L)$$

$$\frac{dP_{avg}}{dR_L} = 0 \rightarrow R_L = R_{th}$$

$$\frac{dP_{avg}}{dX_L} = 0 \rightarrow X_L = -X_{th}$$

For maximum power transfer

$$Z_L = Z_{th}^*$$




To maximize the power transfer :-

(ex) Find  $Z_L$  that maximize the power transfer?


Sol

$$Z_L = 500 - j3$$

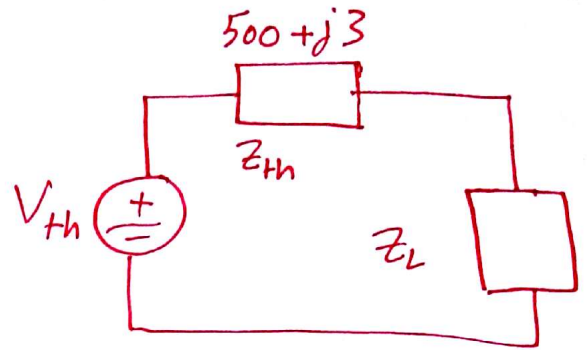

(ex) if  $i(t) = \sin t + \sin \pi t$ ,  $R=1$ , find the average power absorbed by the load :-
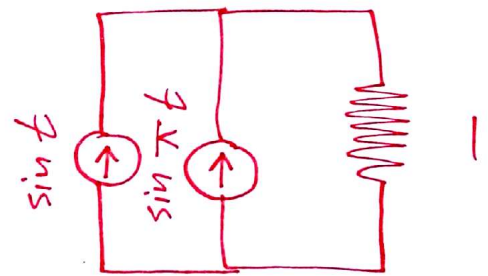
$$\begin{aligned} P(t) &= v(t) * i(t) \\ &= i^2(t) * R \\ &= (\sin t + \sin \pi t)^2 * R \end{aligned}$$



$$\begin{aligned} P_{avg} &= \frac{1}{T} \int_0^T P(t) dt \\ &= \frac{1}{T} \int_0^T (\sin t + \sin \pi t)^2 R dt \\ &= \frac{R}{T} \int_0^T (\sin^2 t + 2 \sin t \sin \pi t + \sin^2 \pi t) dt \\ &= \frac{R}{T} \int_0^T \left( \frac{1}{2} - \frac{1}{2} \cos 2t \right) + \left( \frac{1}{2} \cos(t + \pi t) + \frac{1}{2} \cos(t - \pi t) \right) + \frac{1}{2} - \frac{1}{2} \cos \pi t dt \\ &= \frac{R}{T} * \left[ \frac{1}{2} T + \frac{1}{2} T \right] = 1 W \end{aligned}$$

- For a multiple frequency source: the Avg power across a resistor:

$$P_{avg} = \frac{1}{2} (I_{m1}^2 R + I_{m2}^2 R + I_{m3}^2 R + \dots)$$

$$P_{avg} = P_{avg1} + P_{avg2} + P_{avg3} + \dots$$

$$\# P(t) = P_1(t) + P_2(t) \Rightarrow X$$

$$\begin{array}{cc} \downarrow & \downarrow \\ i_1(t)^2 R & i_2(t)^2 R \end{array}$$

$$P(t) = i(t)^2 * R = (i_1(t) + i_2(t))^2 * R$$

$$= i_1(t)^2 * R + i_2(t)^2 * R + 2 i_1(t) i_2(t) * R \neq P_1(t) + P_2(t)$$

ex)  $i(t) = 2 \cos(10t) - 3 \sin(20t)$ ,  $R = 4 \Omega$

Find the Avg power?

- Different frequency

$$P_{avg} = \frac{1}{2} I_{m1}^2 * R + \frac{1}{2} I_{m2}^2 * R$$

phasor  $\parallel$   $\Delta$ -  
frequency  $\parallel$   $\Delta$

$$= \frac{1}{2} (2)^2 * 4 + \frac{1}{2} (-3)^2 * 4$$

Avg power  $\parallel$   $\Delta$

$$= 8 + 18 = 26 W$$

(16)



$$\textcircled{\text{ex}} \quad i(t) = 2 \cos(10t) - 3 \cos(10t), \quad R = 4$$

Find Avg power? # same frequency

sol

$$i(t) = -\cos(10t)$$

$$P_{\text{avg}} = \frac{I_m^2}{2} * R = \frac{(-1)^2}{2} * 4 = 2 \text{ W}$$

---

$$\textcircled{\text{ex}} \quad i(t) = 2 \cos(\omega t) + 3 \cos(\omega t + \frac{\pi}{6}), \quad R = 4$$

sol Find Avg power?

$$I_1 = 2 \angle 0^\circ = 2$$



$$I_2 = 3 \angle -\frac{\pi}{6} = 3 \cos(-\frac{\pi}{6}) + j 3 \sin(-\frac{\pi}{6})$$

$$I = 2 + \frac{3\sqrt{3}}{2} - j * 3 * \frac{1}{2}$$


$$I_m = \sqrt{\left(2 + \frac{3\sqrt{3}}{2}\right)^2 + \left(\frac{3}{2}\right)^2} = \square$$

$$P_{\text{avg}} = \frac{1}{2} I_m * R = \frac{1}{2} * \downarrow * 4$$


# # Effective values (RMS) :-

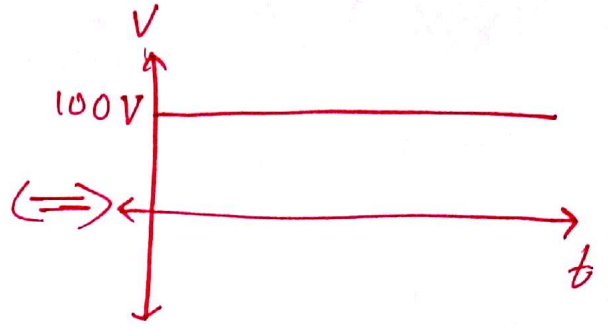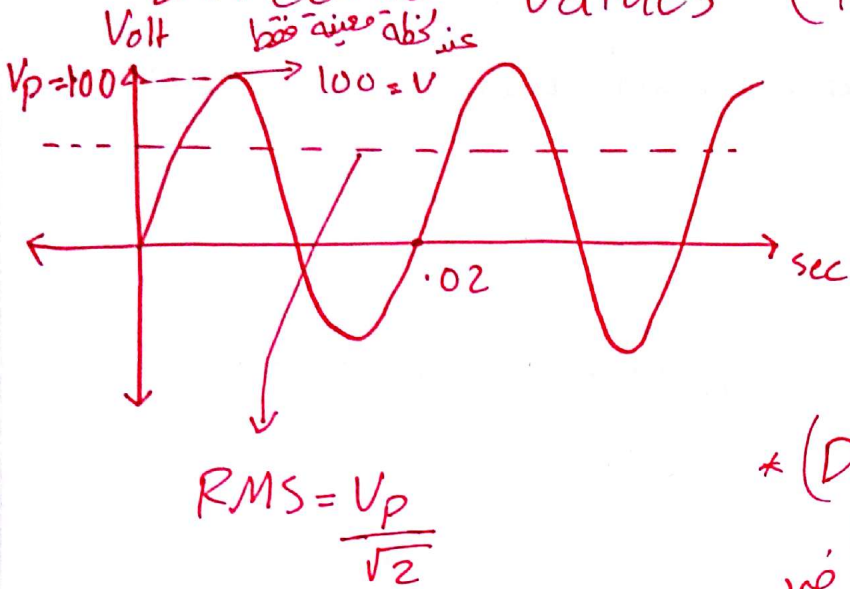

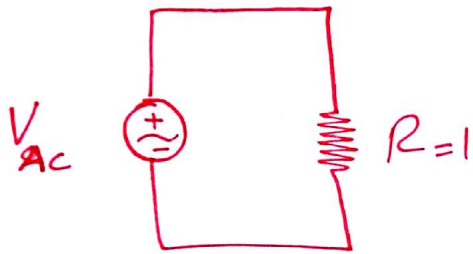\* (DC) أكثر ضرر ← أكثر ضرر  
 (AC) أقل ضرر ← أقل ضرر


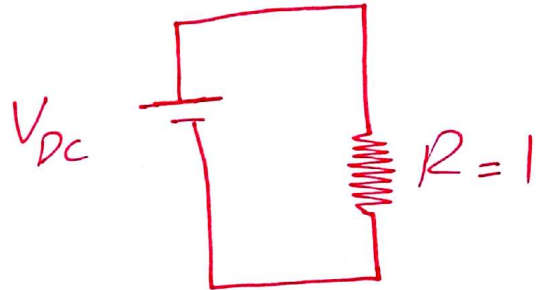
$$P_{avg} = \frac{1}{2} * \frac{V_{ac}^2}{R}$$



$$P_{avg} = \frac{V_{DC}^2}{R}$$

$$P_{avg} = P_{avg}$$

$$\frac{1}{2} \frac{V_{ac}^2}{R} = \frac{V_{DC}^2}{R}$$

$$V_{ac} = \sqrt{2} * V_{DC}$$

- إذا وجد مصدر للطاقة (DC) فإن المصدر المكافئ له بالطاقة  
 في (AC) =  $(\sqrt{2} * V_{DC})$

ex) if there is a (DC) source with 100 V, what is (RMS) of an (AC) source that will produce the same amount of power?

$$V_{ac} = \sqrt{2} * V_{DC} = \sqrt{2} * 100 = 141.2 \text{ V}$$

# if there general (AC) source (not necessarily sin/cos)

$$P_{avg(AC)} = \frac{1}{T} \int_0^T \frac{V_{AC}^2}{R} \cdot dt \quad , \quad P_{avg(DC)} = \frac{V_{DC}^2}{R}$$

$$P_{avg(AC)} = P_{avg(DC)}$$
$$\frac{1}{T} \int_0^T \frac{V_{AC}^2}{R} \cdot dt = \frac{V_{DC}^2}{R}$$


$$V_{DC} = V_{eff} = \sqrt{\frac{1}{T} \int_0^T V_{AC}(t)^2 \cdot dt}$$

Root Mean  
Square Value  
RMS

ex) Find the (RMS) value in the shown signal

$$V_{eff} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$
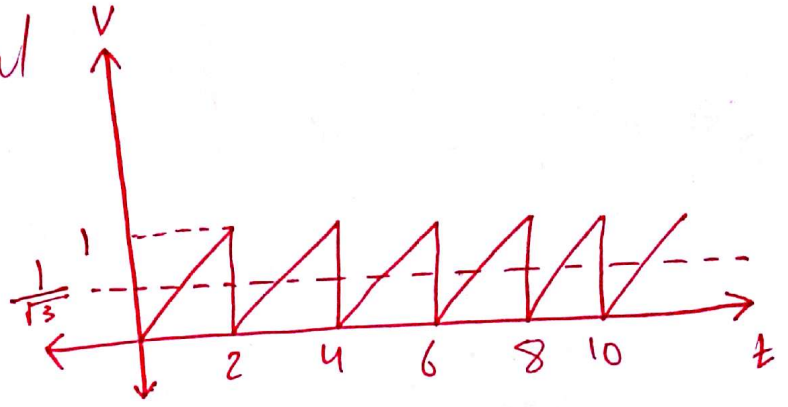
$$T=2 \rightarrow \begin{cases} v(t) = \frac{1}{2}t \\ 0 < t < 2 \end{cases}$$



$$V_{eff} = \sqrt{\frac{1}{2} \int_0^2 \frac{1}{4} t^2 dt} = \sqrt{\frac{1}{2} * \frac{1}{12} t^3 \Big|_0^2} = \sqrt{\frac{1}{2} * \frac{8}{12}} = \frac{1}{\sqrt{3}} V$$

ex) Find (RMS) value at an (AC) signal :-

$$i(t) = I_m \cos(\omega t + \phi) ?$$


$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i(t)^2 dt}$$

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2(\omega t + \phi) dt} \quad * \cos^2(\theta) = \frac{1}{2} + \frac{1}{2} \cos(2\theta)$$

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T \frac{1}{2} I_m^2 dt + \int_0^T \frac{1}{2} I_m^2 \cos(2\omega t + 2\phi) dt}$$

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T \frac{1}{2} I_m^2 dt} \quad I_m$$

$$I_{eff} = \frac{I_m}{\sqrt{2}}$$

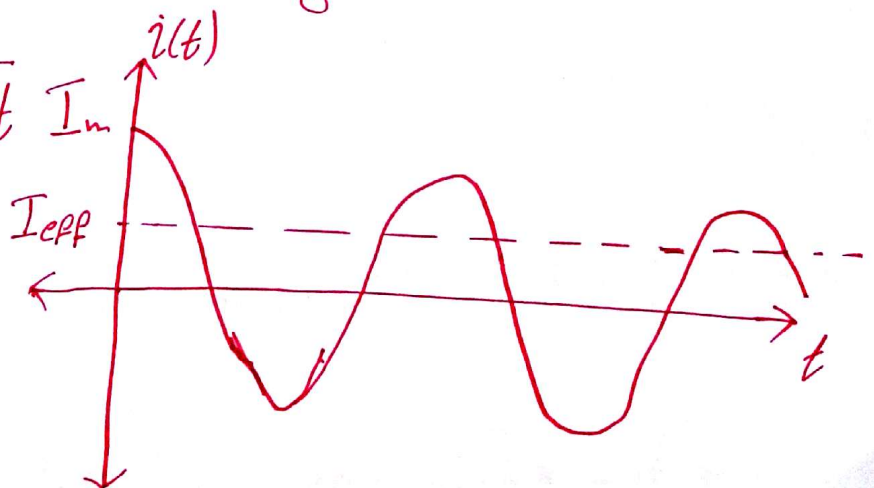


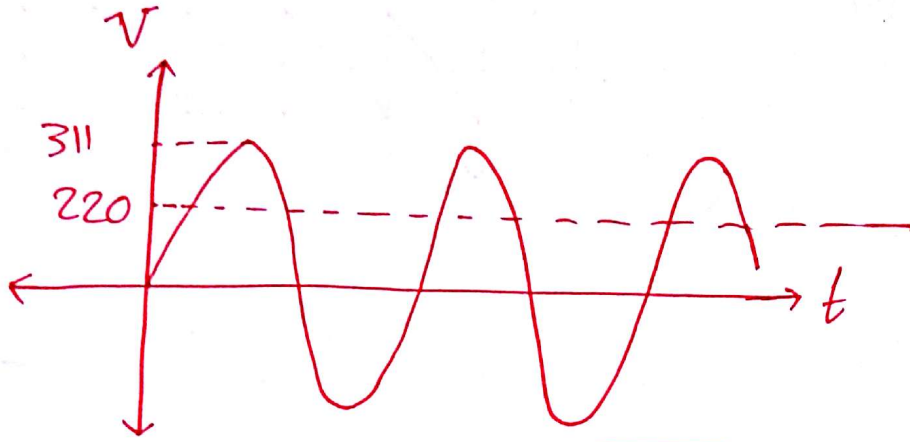(20)



- in jordan  $\rightarrow 220\text{ V}$  (RMS) value

So  $V_p = 220 * \sqrt{2} = 311\text{ V}$



- For a resistive load with a sinusoidal source:-

$$P_{\text{avg}} = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R = \frac{V_m^2}{2R}$$

$$\left. \begin{aligned} - V_m &= \sqrt{2} V_{\text{eff}} = \sqrt{2} V_{\text{RMS}} \\ - I_m &= \sqrt{2} I_{\text{eff}} = \sqrt{2} I_{\text{RMS}} \end{aligned} \right\} \begin{array}{l} \text{(RMS)} \\ \text{(I و V)} \end{array}$$

$$P_{\text{avg}} = V_{\text{RMS}} I_{\text{RMS}} = I_{\text{RMS}}^2 R = \frac{V_{\text{RMS}}^2}{R}$$

\* In general

$$P_{\text{avg}} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

↑ voltage                      → current

$$= V_{\text{RMS}} * I_{\text{RMS}} \cos(\theta_v - \theta_i)$$



$$\textcircled{\text{ex}} \left. \begin{aligned} -i(t) &= 5 \cos(\omega t) \rightarrow I_{\text{eff}} = \frac{5}{\sqrt{2}} \\ -v(t) &= 3 \sin(\omega t) \rightarrow V_{\text{eff}} = \frac{3}{\sqrt{2}} \end{aligned} \right\} \begin{array}{l} \text{any sinusoidal} \\ \text{signal} \\ X_{\text{eff}} = \frac{X_m}{\sqrt{2}} \end{array}$$

$$\textcircled{\text{ex}} -v(t) = 10 \cos(\omega t - \frac{\pi}{3}) \rightarrow V_{\text{eff}} = \frac{10}{\sqrt{2}}$$

$$-i(t) = 4 \sin(\omega t) + 3 \cos(\omega t) \rightarrow I_{\text{eff}} = \frac{5}{\sqrt{2}}$$

$$* A \cos(x) + B \sin(x) = \sqrt{A^2 + B^2} \cos(x - \tan^{-1}(\frac{B}{A}))$$

$$\text{or: } I = 4 \angle -\frac{\pi}{2} + 3 \angle 0^\circ = 3 - j4$$

$$-i(t) = 5 \cos(\omega t) + 3 \sin(2\omega t)$$


\* for a signal with multiple frequency :-

$$\# I_{\text{eff}} = \sqrt{I_{\text{eff}1}^2 + I_{\text{eff}2}^2 + I_{\text{eff}3}^2 + \dots}$$

$$I_{\text{eff}} = \sqrt{\left(\frac{5}{\sqrt{2}}\right)^2 + \left(\frac{3}{\sqrt{2}}\right)^2} = \sqrt{\frac{34}{2}}$$

$$\# P_{\text{avg}} = I_{\text{eff}1}^2 * R + I_{\text{eff}2}^2 * R + I_{\text{eff}3}^2 * R + \dots$$

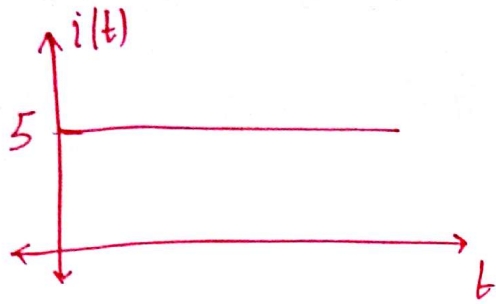(ex)  $i(t) = 5 \rightarrow I_{RMS} = ? \quad \frac{5}{\sqrt{2}} \times$



$$I_{RMS} = \sqrt{\frac{1}{T} \int_0^T (5)^2 dt}$$


$$= \sqrt{\frac{1}{T} 25t \Big|_0^T} = 5$$

$i(t) = 5 \cos(\omega t) \rightarrow I_{RMS} = \frac{5}{\sqrt{2}} \checkmark$


(ex)  $i(t) = 5 + 3 \cos(\omega t - \frac{\pi}{2})$

$I_{RMS} = 5 + \frac{3}{\sqrt{2}} \times$

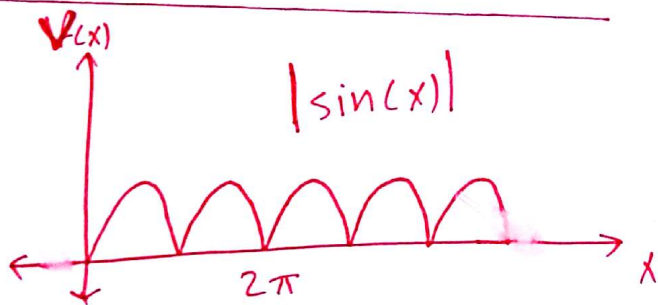$I_{RMS} = \sqrt{(5)^2 + (\frac{3}{\sqrt{2}})^2} = \sqrt{25 + \frac{9}{2}}$



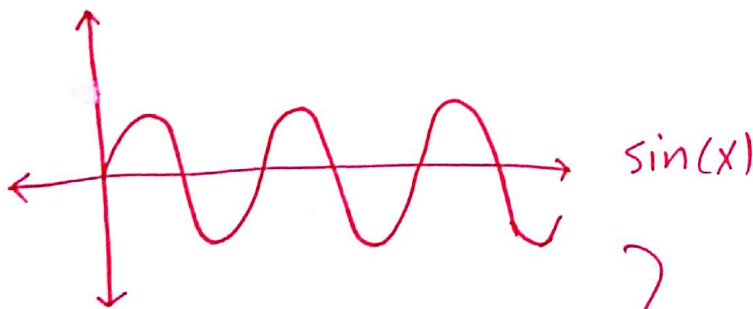
$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$



$\sin(x)$

$\therefore V_{RMS} = \frac{5}{\sqrt{2}}$


} مواضع  
موجبة

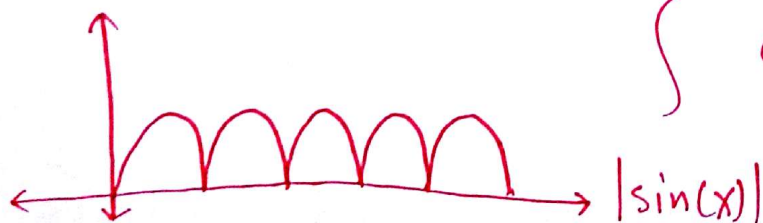



$|\sin(x)|$

$\therefore V_{RMS} = \frac{5}{\sqrt{2}}$


ابن

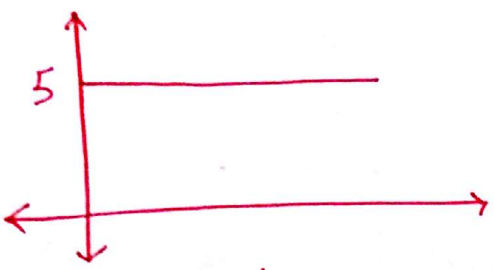

↓  
ع.س.ر

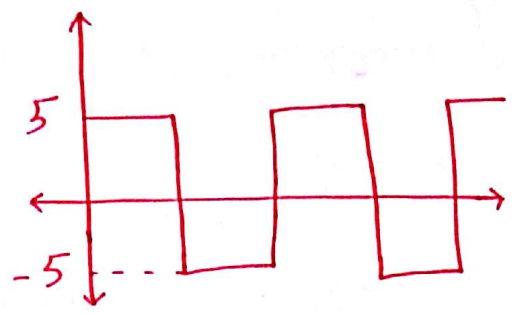
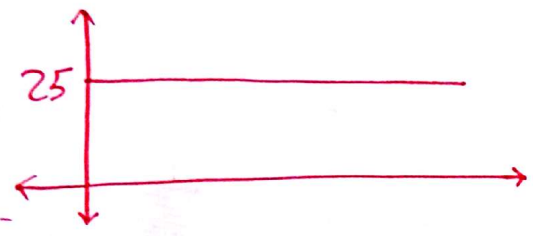


↓  
ع.س.ر

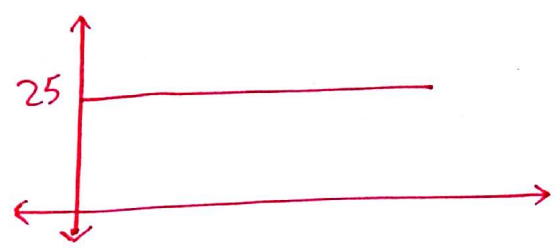

$V_{RMS}$  for Both are 5
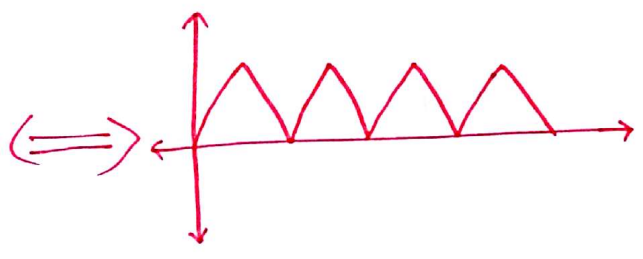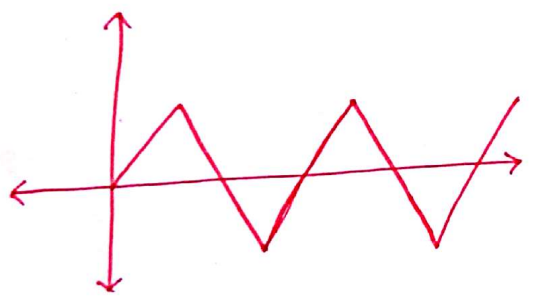
$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^{\frac{1}{2}T} (5)^2 dt + \int_{\frac{1}{2}T}^T (-5)^2 dt} = 5$$



$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt = 0$$

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt} \neq 0$$




# # power factor


$$I = 20 \angle 0^\circ$$

$$P_{avg} = 1000 \text{ W (apparent)}$$

→ resistor

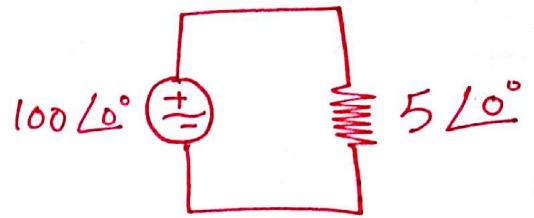
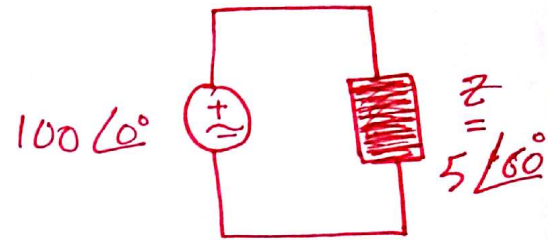
$$I = \frac{100 \angle 0^\circ}{5 \angle 60^\circ} = 20 \angle -60^\circ$$



$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$= \frac{100 * 20}{2} * \cos(60^\circ) = \underline{500 \text{ W (Real)}}$$

There is a lot of power

$$P_{avg} = \frac{V_m I_m}{2} \cos(90) = 0 ??$$

power factor (just for a sinusoidal system)

$$= \frac{\text{Real power}}{\text{apparent power}} = \frac{V_{RMS} I_{RMS} \cos(\theta_v - \theta_i)}{V_{RMS} I_{RMS}}$$

$$P.F = \cos(\theta_v - \theta_i) \quad , \quad (\theta_v - \theta_i) \Rightarrow P.F \text{ angle}$$

- for (R) load  $\rightarrow \theta_v - \theta_i = 0 \rightarrow P.F = 1$

- for (L/C) load  $\rightarrow \theta_v - \theta_i = \pm 90 \rightarrow P.F = 0$

(25)

- For  $R \times$  load  $\rightarrow -\frac{\pi}{2} < \theta_v - \theta_i < \frac{\pi}{2} \rightarrow P.F. \rightarrow 0 < P.F. < 1$

$\swarrow \searrow$   
C L

(ex) let  $V = 5 \angle 30$  } P.F. =  $\cos(30 - -30) = .5$  (lagging RL)  
 $I = 3 \angle -30$  } I lags V

(ex) let  $V = 5 \angle -30$  } P.F. =  $\cos(-30 - 30) = .5$  (leading RC)  
 $I = 3 \angle 30$  } I leads V

(ex) Find the source power factor?

sol - find  $\theta_i \rightarrow$  find I


$$I_{RMS} = \frac{V_{RMS}}{Z_{eq}}$$

$$= \frac{60 \angle 0}{(2-j) + (1+j5)} = 12 \angle -53.13$$

$$P.F. = \cos(\theta_v - \theta_i)$$

$$= \cos(0 - -53.13) = .6$$

(lagging)

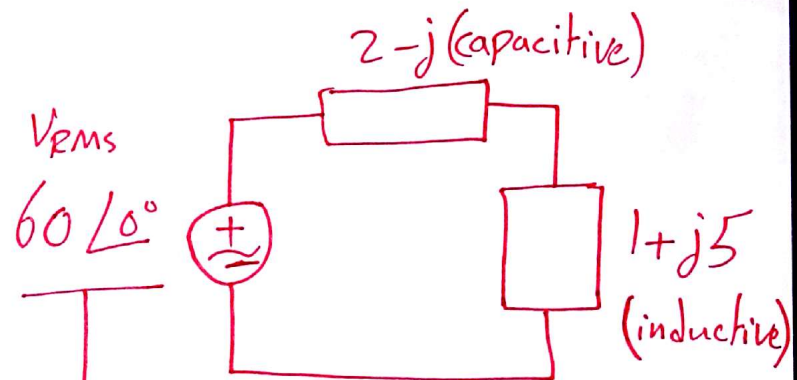

إذا لم يذكر السؤال

نوع ال source نعتبرها RMS

$$-v(t) = \underline{5} \cos(\omega t)$$

peak value

$\rightarrow$  follow

$$-P_{\text{avg}}(2-j) = \frac{1}{2} I_m^2 R = I_{\text{RMS}}^2 R$$

power of imaginary  
= 0

$$= (12)^2 * 2 = 288 \text{ W}$$

$$-P_{\text{avg}}(1+j5) = (12)^2 * 1 = 144 \text{ W}$$

- power (apparent) produced By the source :-

$$= V_{\text{RMS}} * I_{\text{RMS}} = 60 * 12 = 720 \text{            unit ??}$$

$$442 \neq 720 \text{ ?}$$





take :-

$$V = |V_{\text{eff}}| \angle \theta_v \quad \& \quad I = |I_{\text{eff}}| \angle \theta_i$$

$$P = |V_{\text{eff}}| |I_{\text{eff}}| \cos(\theta_v - \theta_i)$$

$$= |V_{\text{eff}}| |I_{\text{eff}}| \operatorname{Re} \left\{ e^{j(\theta_v - \theta_i)} \right\}$$

$$e^{j(\theta_v - \theta_i)} = \cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)$$

$$\operatorname{Re} \left\{ e^{j(\theta_v - \theta_i)} \right\} = \cos(\theta_v - \theta_i)$$

$$\operatorname{Im} \left\{ e^{j(\theta_v - \theta_i)} \right\} = j \sin(\theta_v - \theta_i)$$

$$\Rightarrow P = \operatorname{Re} \left\{ |V_{\text{eff}}| e^{j\theta_v} * |I_{\text{eff}}| e^{-j\theta_i} \right\}$$

$$\text{(real power)} \quad P = \operatorname{Re} \left\{ V I^* \right\}$$

$$Q = \operatorname{Im} \left\{ V I^* \right\} \text{ (reactive power)}$$

$$S = V I^* \text{ (complex power)}$$

$$S = VI^* = P + jQ$$

(complex power)	(Real power)	(Reactive power)	
(unit)	(unit)	(unit)	(L/C)
V.A	W	VAR	
	(R)	↳ (volt Ampere reactive)	

$$- S = VI^* = |V_{eff}| |I_{eff}| e^{j(\theta_v - \theta_i)}$$


$$S = |V_{eff}| |I_{eff}| [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)]$$

$$S = \underbrace{|V_{eff}| |I_{eff}| \cos(\theta_v - \theta_i)}_P + j \underbrace{|V_{eff}| |I_{eff}| \sin(\theta_v - \theta_i)}_Q$$

$$\# P = |V_{eff}| |I_{eff}| \cos(\theta_v - \theta_i)$$

$$P = V_{RMS} I_{RMS} \cos(\theta_v - \theta_i)$$

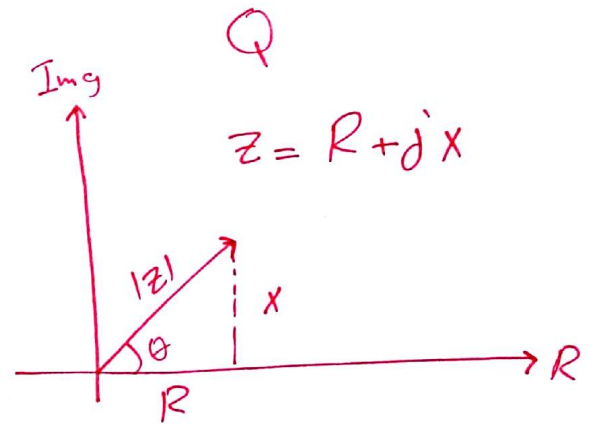
$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$



$$\# Q = |V_{eff}| |I_{eff}| \sin(\theta_v - \theta_i)$$

$$Q = V_{RMS} I_{RMS} \sin(\theta_v - \theta_i)$$
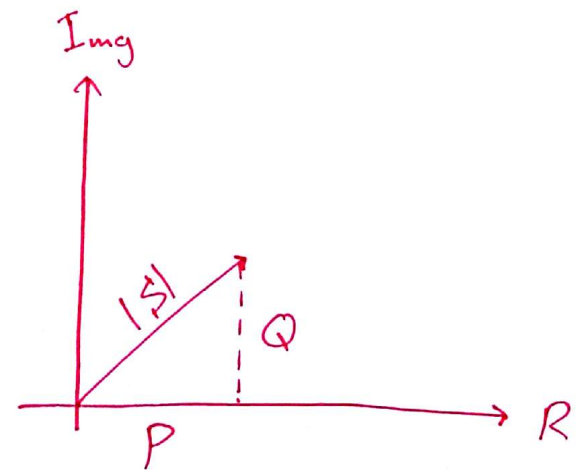
$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$



$$S = P + jQ$$



$$* \mathcal{S} = P + jQ$$

↓            ↓            ↓  
complex    Real        Reactive  
VA        W        VAR

$$* P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$= V_{RMS} I_{RMS} \cos(\theta_v - \theta_i)$$

$$* Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

$$= V_{RMS} I_{RMS} \sin(\theta_v - \theta_i)$$

$$* |\mathcal{S}| = \sqrt{P^2 + Q^2}$$


↓  
apparent  
VA

$$* 0 \leq PF = \frac{P}{|\mathcal{S}|} \leq 1$$

(ex) Find the complex power (absorbed/produced) by each element?

sol
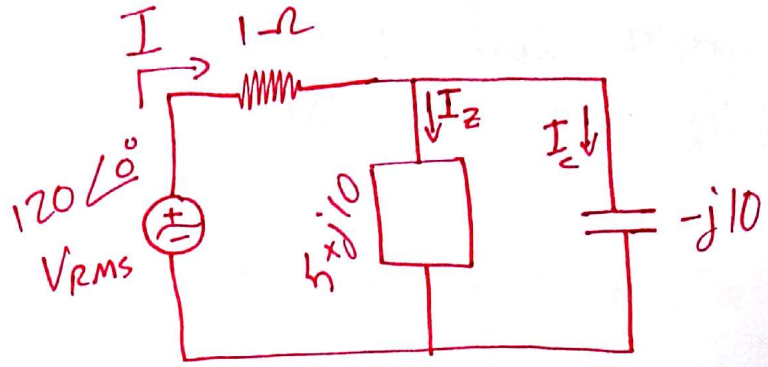
$$I = \frac{120 \angle 0^\circ}{1 + \frac{(5+j10)(-j10)}{5}}$$



$$I = 5.16 \angle 25.46^\circ \text{ A}$$

$$\# \sum_{\text{source}} = V I^* = (120 \angle 0^\circ) (5.16 \angle -25.46^\circ) = 558.98 - j 266.14 \text{ VA}$$

\* For sources: +ve sign means power generated, -ve sign means power absorbed.

\* For elements: the opposite of sources

$$\# \sum_{(1-\Omega)} = V I^* = (I R) I^* \quad * P_{(1-\Omega)} = 26.6 \text{ W}$$

$$= (5.16 \angle -25.46^\circ) * (5.16 \angle 25.46^\circ * 1) = 26.6 + j0 \text{ VA}$$

$$\# \sum_{(-j10)} = V I_c^* = (I_c * (-j10)) * I_c^*$$

$$I_c = I * \frac{(5+j10)}{5} = 11.53 \angle 88.89^\circ \text{ A}$$

\* the capacitor works as a generator at reactive power

$$\sum_{(-j10)} = ((11.53 \angle 88.89^\circ) * (-j10)) * (11.53 \angle -88.89^\circ)$$

$$= -j 1331 \text{ VA} \quad , \quad Q = 1331 \text{ VAR}$$

$$\# \sum_{(5+j10)} = V I_z^* = (I_z * (5+j10)) * I_z^*$$

$$I_z = I - I_c = 10.31 \angle -64.53$$


$$\sum_{(5+j10)} = ((10.31 \angle -64.53) * (5+j10)) * (10.31 \angle 64.53)$$

$$= 531.48 + j1062.96 \text{ VA}$$

⊗ Find (PF) and (complex power) For both source and load?

$$v_L(t) = 60 \cos(\omega t - 10) \text{ V}$$
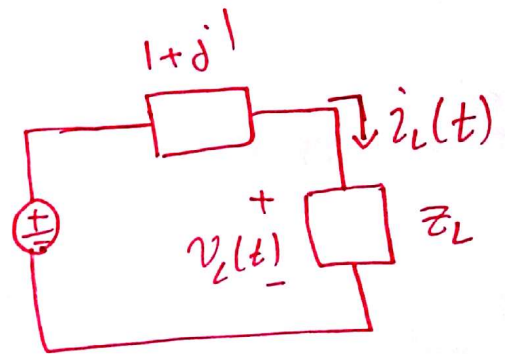
$$i_L(t) = 1.5 \cos(\omega t + 50) \text{ A}$$



$$PF_{(load)} = \cos(\theta_{v_L} - \theta_{i_L})$$

$$= \cos(-10 - 50) = .5 \text{ leading}$$

$$V_{RMSL} = \frac{60}{\sqrt{2}} \angle -10 \text{ V} \quad , \quad I_{RMSL} = \frac{1.5}{\sqrt{2}} \angle 50 \text{ A}$$

$$S_{Load} = V_L I_L^* = \left( \frac{60}{\sqrt{2}} \angle -10 \right) * \left( \frac{1.5}{\sqrt{2}} \angle -50 \right) = 45 \angle -60 \text{ VA}$$

$$= \underbrace{22.5}_P - j \underbrace{38.97}_Q$$

$$|S| = \sqrt{(22.5)^2 + (38.97)^2} = 45$$

$$\left\{ \begin{array}{l} P = |S| \cos(\theta) \\ \text{PF angle} = \theta_v - \theta_i \\ Q = |S| \sin(\theta) \end{array} \right.$$



$$\begin{aligned}
 V_{RMS(\text{source})} &= V_{L(RMS)} + I_{L(RMS)} * (1+j1) \\
 &= \frac{60}{\sqrt{2}} \angle -10 + \frac{1.5}{\sqrt{2}} \angle 50 (1+j1) \\
 &= 41.65 + j5 = 42 \angle -8 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 PF_{(\text{source})} &= \cos(\theta_v - \theta_i) \\
 &= \cos(-8 - 50) = 0.53 \text{ leading}
 \end{aligned}$$

$$\begin{aligned}
 S_{(\text{source})} &= V * I^* = (42 \angle -8) * \left( \frac{1.5}{\sqrt{2}} \angle -50 \right) \\
 &= 44.54 \angle -58 = 23.6 - j 37.7 \text{ VA}
 \end{aligned}$$

$$- P_{\text{loss T.L}} = 23.6 - 22.5 = 1.1 \text{ W}$$



$$- Q_{\text{loss T.L}} = 38.97 - 37.7 = 1.27 \text{ VAR}$$

$$- S_{\text{T.L}} = 1.1 + j 1.27 \text{ VA}$$
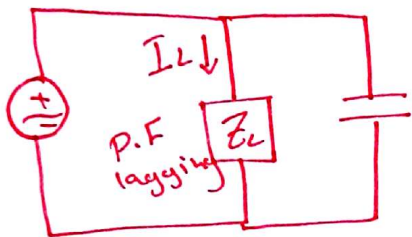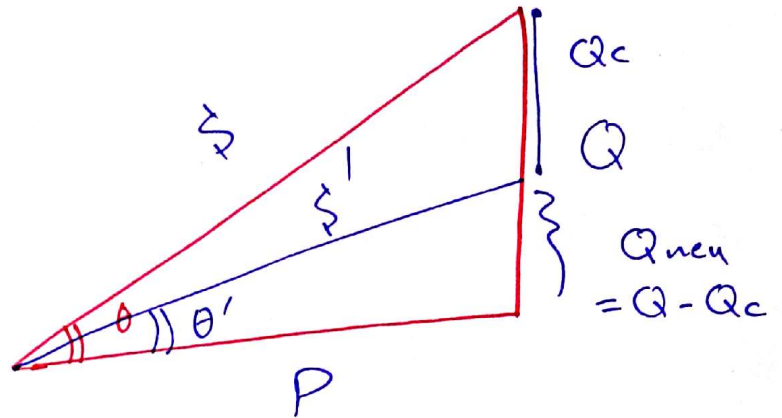
# \* Pf correction :-

- increasing the pf of the load without changing its current or voltage

- it could be done by adding a capacitor in parallel with the load.





$$I_L = \frac{V}{Z_L}$$

$$I'_L = \frac{V}{Z_L}$$

$$I'_S \neq I_S$$

ex) A 50 kw, 0.8 lagging PF motor is operated a 230 V, it is required to increase the pf to 0.95 lagging.

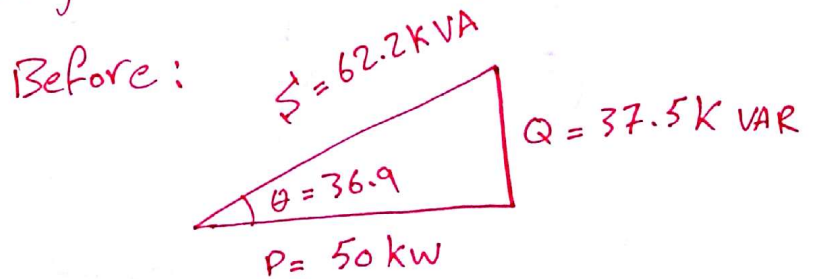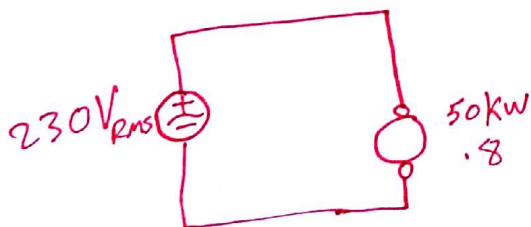sol: - draw the power triangle before adding the capacitor.




$$PF = \cos \theta = .8$$


$$S = \frac{P}{.8} = 62.5$$

$$\tan \theta = \frac{Q}{P}$$

→ follow (35)

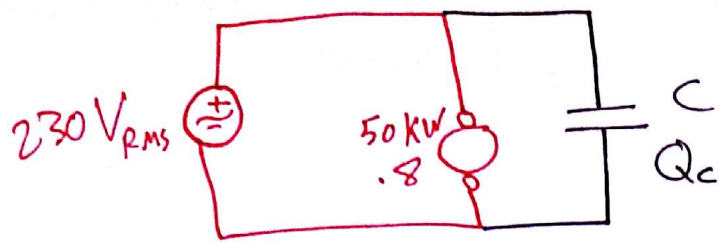

After

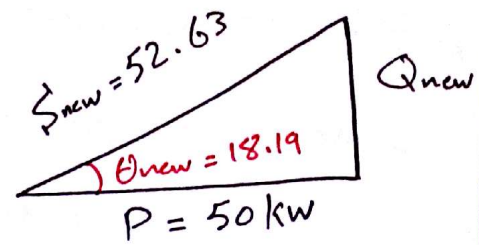

$$Q_c = Q_{\text{new}} - Q_{\text{old}}$$

$$|Q_c| = (16.43 - 37.5) \text{ kVAR}$$


$$= -21.07 \text{ kVAR}$$

$$\theta_{\text{new}} = \cos^{-1}(0.95) = 18.19^\circ$$


$$S_{\text{new}} = \frac{P}{0.95} = 52.63$$

$$\tan(\theta_{\text{new}}) = \frac{Q_{\text{new}}}{P}$$

$$Q_{\text{new}} = 16.43 \text{ kVAR}$$

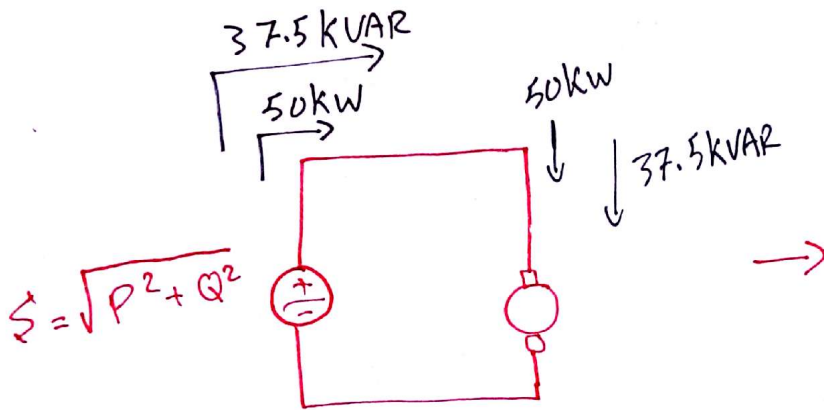
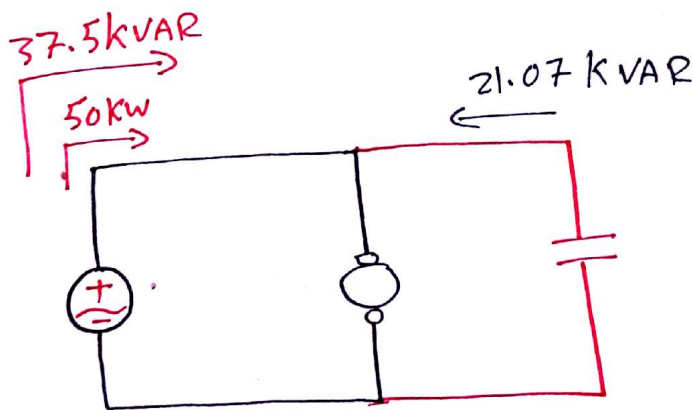
$$PF = \frac{P}{S} = \frac{50}{62.5} = 0.8$$



$$PF = \frac{P}{S} = \frac{50}{\sqrt{(50)^2 + (16.43)^2}} = 0.95$$

$$Q_c = V_{RMS} I_{RMS} \sin(\theta_v - \theta_i)$$

$$Q_c = V_{RMS} I_{RMS} = V_{RMS} * \frac{V_{RMS}}{X_c} \rightarrow \frac{1}{\omega C}$$

$$Q_c = (V_{RMS})^2 * \omega C$$

$$C = \frac{Q_c}{(V_{RMS})^2 * \omega}$$


# In the previous ex :-

$$C = \frac{21070}{(230)^2 * 2\pi * f} \rightarrow$$

تكونه  
بالذال



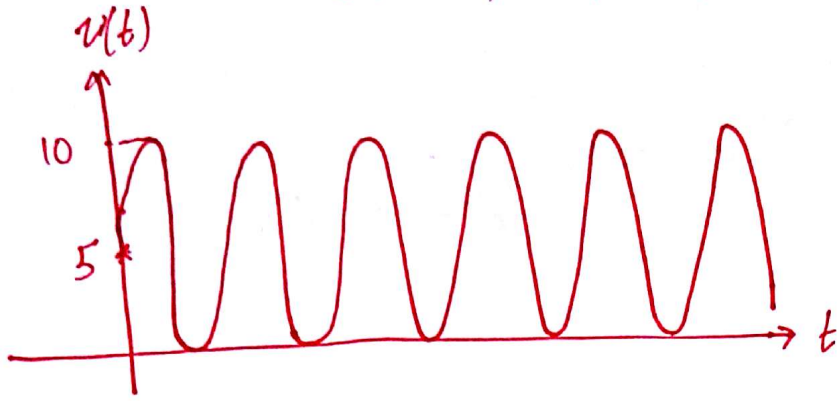(ex) Find the (RMS) value for the shown voltage waveform




$$v(t) = 5 \sin(\omega t) + 5 \text{ V}$$

$$V_{\text{eff}} = \sqrt{\left(\frac{5}{\sqrt{2}}\right)^2 + (5)^2} = 6.123 \text{ V}$$

(ex) (a) Find the (RMS) value :-


$$T = 4$$
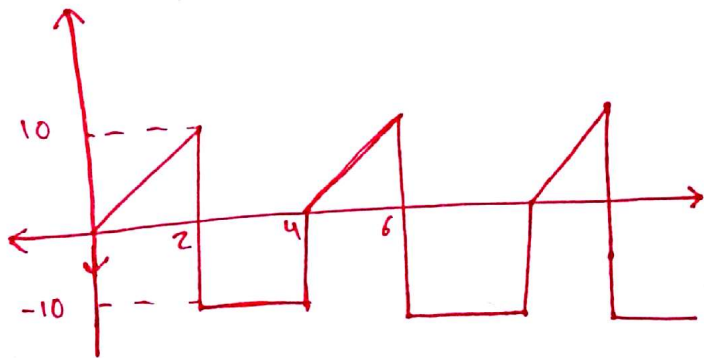
$$v(t) = \begin{cases} 5t, & 0 \leq t < 2 \\ -10, & 2 \leq t < 4 \end{cases}$$



$$V_{\text{RMS}} = \sqrt{\frac{1}{4} \left[ \int_0^2 25t^2 dt + \int_2^4 (-10)^2 dt \right]} = 8.165 \text{ V}$$

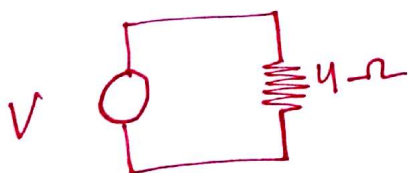(b) what is the absorbed power by a (4 Ω) resistor connected to this voltage source.




$$P = \frac{(V_{\text{RMS}})^2}{R} = \frac{(8.165)^2}{4}$$

(ex) Find the (RMS) value for  $v(t)$ ?

$$T = 4$$


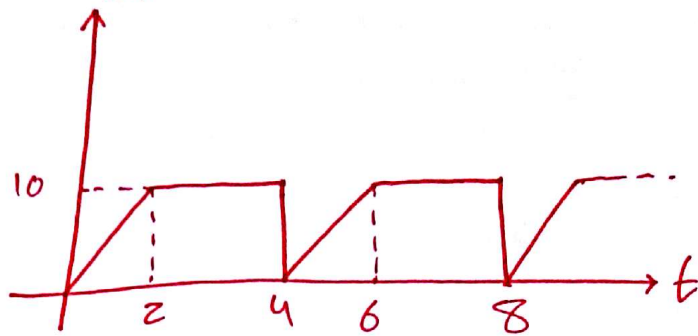
$$v(t) = \begin{cases} 5t, & 0 \leq t < 2 \\ 10, & 2 \leq t < 4 \end{cases}$$



$$V_{RMS} = \sqrt{\frac{1}{4} \left[ \int_0^2 25t^2 dt + \int_2^4 (10)^2 dt \right]} = 8.165 \text{ V}$$

$$V_{avg} = \frac{1}{4} \left[ \int_0^2 5t dt + \int_2^4 (10) dt \right] = \frac{30}{4} = 7.5 \text{ V}$$

(ex) Find (RMS) value

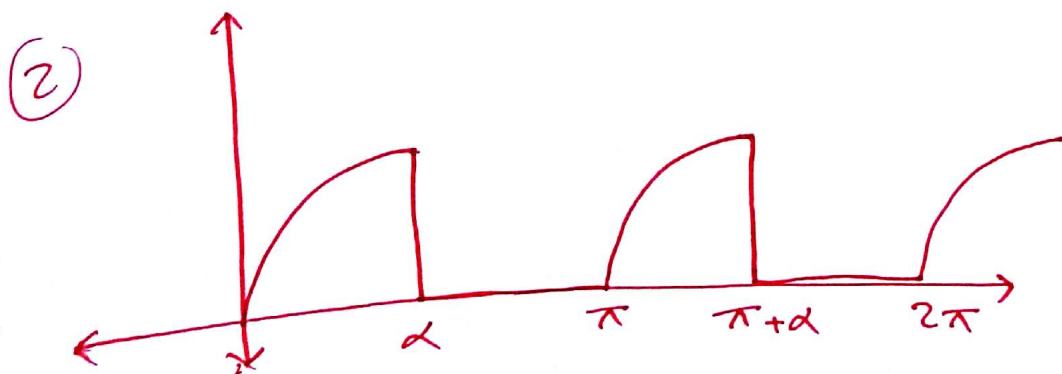
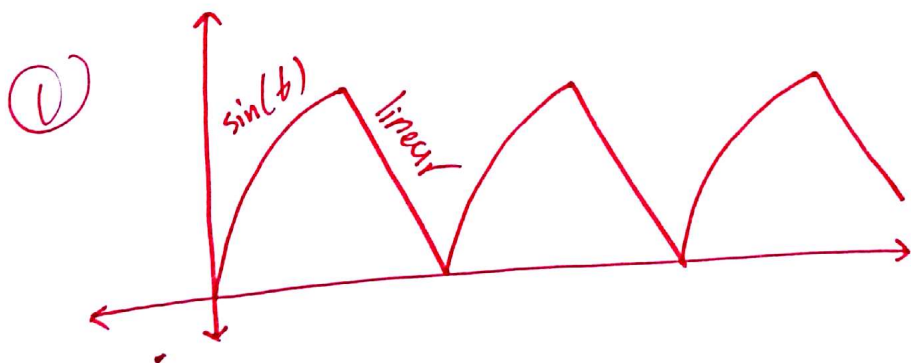


Q8) Determine the load impedance ( $Z_L$ ) that maximize the power drawn from the ckt & find this power?

Sol:


$$Z_L = Z_{th}^*$$

- Find  $Z_{th}$  :-

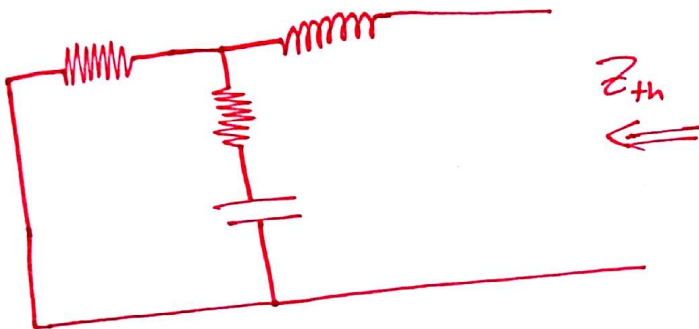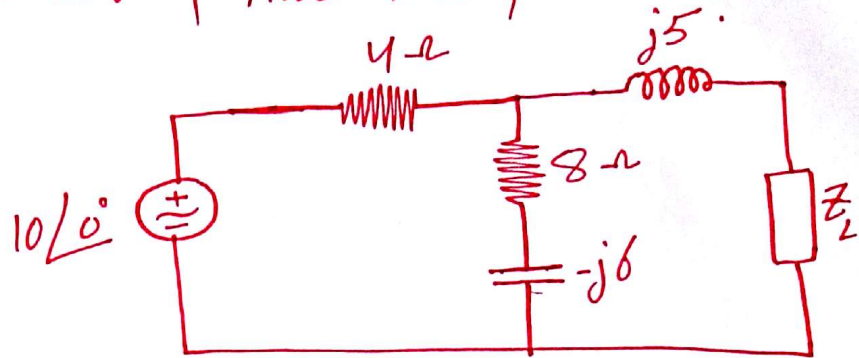


$$Z_{th} = j5 + \frac{4 * (8 - j6)}{12 - j6} = (2.933 + j4.467) \Omega$$
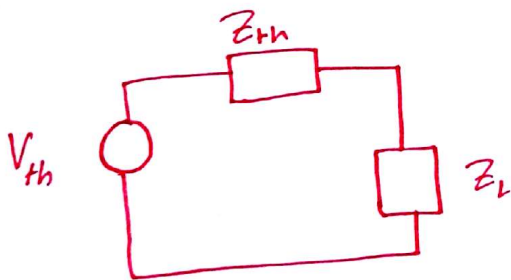
$$Z_L = Z_{th}^* = (2.933 - j4.467) \Omega$$



$$V_{th} = V_{oc}$$

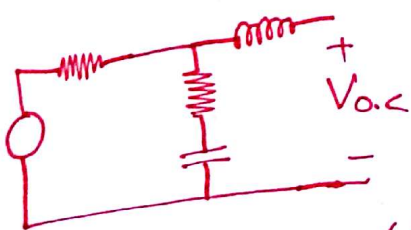

$$V_{oc} = 10 \angle 0^\circ * \frac{(8 - j6)}{(8 + 4 - j6)}$$

$$V_{oc} = 7.45 \angle -10.3^\circ \text{ V}$$

$$P_{max} = V_{RMS(L)} I_{RMS(L)} = \frac{1}{2} V_L I_L$$

$$P_{max} = I_{RMS}^2 * R$$


$$I_{RMS} = \frac{V_{th(RMS)}}{Z_{th} + Z_L} = \frac{V_{th(RMS)}}{2R}$$

$$= \frac{7.45 \angle -10.3^\circ}{2 * 2.933}$$

$$P = I_{RMS}^2 * R = \frac{V_{th(RMS)}^2}{4R^2} * R$$

$$= \frac{V_{thRMS}^2}{4R} = \frac{V_m^2}{8R}$$

- what if  $Z_L = R_L$  :- ?

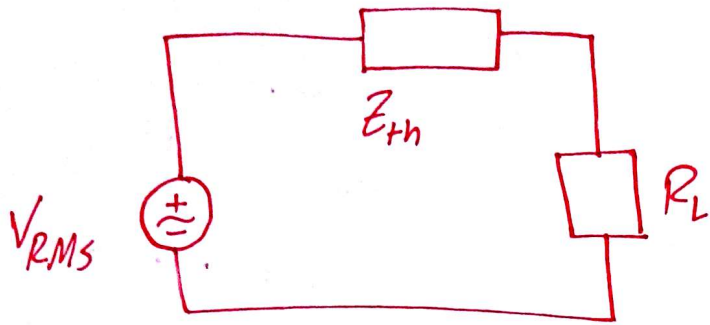

$$R_L = |Z_{th}| = \sqrt{(R_{th})^2 + (X_{th})^2}$$