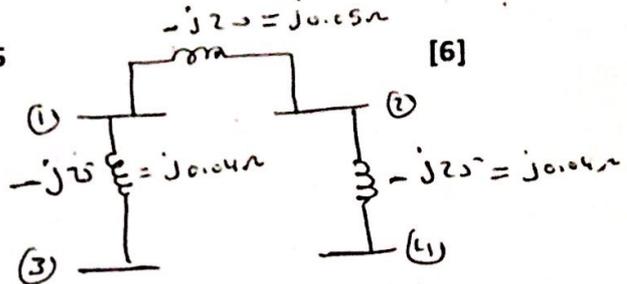


Q1)a- If the 1<sup>st</sup> and 2<sup>nd</sup> rows of a given Bus Admittance Matrix are as follows, draw the corresponding Reactance Diagram.

1<sup>st</sup> Row: -j45 j20 j25 0

2<sup>nd</sup> Row: j20 -j45 0 j25

The system has 4 busbars



b-The power system showing Fig. 1 has the following data:

G: 300 MVA, 20 kV, X=20%

T<sub>1</sub>: 350 MVA, (20 Δ/220 Y) kV, X=10%

T<sub>2</sub>: 300 MVA, (220 Y/13.2 Δ) kV, X=10%

By using the PU system and selected Base values at the generator as 18 kV and 300 MVA, evaluate the followings when the generator is supplying its ratings at 0.8 PF lagging:

i) The voltage at point I.

[12]

ii) The total current supplied to the motors M<sub>1</sub> and M<sub>2</sub>.

[4]

i)  $X_G = j0.2 \times \left(\frac{20}{18}\right)^2 \times \left(\frac{300}{300}\right) = j0.247$

$E = \frac{20}{18} = 1.11 \angle 0^\circ$

$X_{T1} = j0.1 \times \left(\frac{22}{18}\right)^2 \times \frac{300}{350} = j0.105$



Fig. 1


i) The motor currents are on the LV side and assuming +ve ph. sequence

$I_G = \frac{300 \times 10^3}{\sqrt{3} \times 20 \times 10^3} \angle 36.87^\circ = 8660.3 \text{ A}$

$I_b = \frac{300 \times 10^3}{\sqrt{3} \times 18 \times 10^3} = 9622.5 \text{ A}$

$I_G = 8660.3 / 9622.5 \angle 36.87^\circ = 0.9 \angle 56.87^\circ$

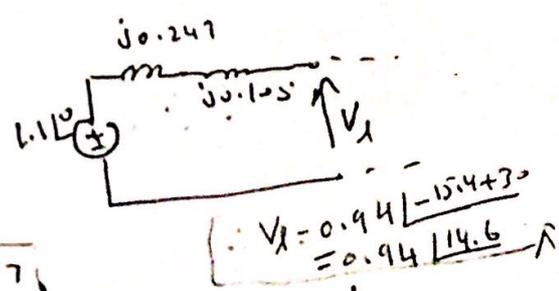$V_I = 1.11 \angle 0^\circ - 0.9 \angle 56.87^\circ \times j0.352 = 1.11 \angle 0^\circ - 0.317 \angle 53.13^\circ = 0.91 \angle -15.4^\circ$   
 Assuming no-phase shift



Q2) A 150 km, 50 Hz transmission line has the following parameters:

$A=0.936 \angle 0.98^\circ$        $B=142 \angle 76.4^\circ \Omega$

i) Evaluate the capacitance of this line. [12]

ii) If a reactive compensation is to be installed at the receiving end of the line with a series compensation factor of 0.8, evaluate the 1<sup>st</sup> row of the matrix of the equivalent [A,B,C,D] parameters after compensation. [20]

i) This is a medium line with:

$A = 1 + Z \frac{Y}{2}$  ,  $B = Z$

$\therefore \frac{Y}{2} = \frac{(A-1)}{Z} = \frac{(0.936 \angle 0.98^\circ - 1)}{142 \angle 76.4^\circ} = \frac{(-0.064 + j0.016)}{142 \angle 76.4^\circ}$   
 $= 0.066 \angle 165.9^\circ / 142 \angle 76.4^\circ = 4.65 \times 10^{-4} \angle 89.55^\circ$

$\therefore Y = 9.36 \times 10^{-4} \angle 90^\circ$

$\therefore |Y| = \omega C = 9.36 \times 10^{-4}$

$\therefore C = \frac{9.36 \times 10^{-4}}{\omega} = \frac{9.36 \times 10^{-4}}{2\pi \times 50} = 0.029 \times 10^{-4} = \boxed{2.9} \mu F$

ii) The matrix of the line is  $M_1 = \begin{bmatrix} 0.936 \angle 0.98^\circ & 142 \angle 76.4^\circ \\ C & D \end{bmatrix}$

The matrix of the compensation is  $M_2 = \begin{bmatrix} 1 & X_c \\ 0 & 1 \end{bmatrix}$

$|X_c| / |X_L| = 0.8$  ,  $\therefore X_c = 0.8 X_L$

Now  $Z = B = 142 \angle 76.4^\circ$

$\therefore |X_L| = 142 \sin 76.4^\circ = 138.02 \Omega$

$\therefore |X_c| = 0.8 \times 138.02 = \boxed{110.42} \Omega$

$\therefore X_c = -j110.42$

$\therefore$  The equivalent matrix  $\begin{bmatrix} 0.936 \angle 0.98^\circ & 142 \angle 76.4^\circ \\ C & D \end{bmatrix} \begin{bmatrix} 1 & -j110.42 \\ 0 & 1 \end{bmatrix}$

$\therefore$  1<sup>st</sup> row =  $\begin{bmatrix} 0.936 \angle 0.98^\circ & 0.936 \angle 0.98^\circ \times 110.42 \angle -90^\circ + 142 \angle 76.4^\circ \end{bmatrix}$

$= \begin{bmatrix} 0.936 \angle 0.98^\circ & 103.35 \angle -89.02^\circ + 142 \angle 76.4^\circ \end{bmatrix}$

$= \begin{bmatrix} 0.936 \angle 0.98^\circ & 48.16 \angle 46.07^\circ \end{bmatrix}$

Q3) A 320 km transmission line has the following data at 60 Hz:

$$z = (0.13 + j0.49) \Omega/\text{km}$$

$$y = j3.39 \times 10^{-6} \text{ S/km}$$

If the line is open-circuited at the receiving end and the receiving end

Phase voltage is 57.4 kV, evaluate:

i) The incident and reflected voltages. [15]

ii) The SIL. [9]

$$i) V_s = \frac{V_R + I_R Z_L}{2} e^{\gamma l} + \frac{V_R - I_R Z_L}{2} e^{-\gamma l}$$

o/c at receiving end, means  $I_R = 0$

$$\therefore \text{Incident voltage, } V_{in} = \frac{1}{2} V_R e^{\gamma l}$$

$$\text{Reflected voltage, } V_{ref} = \frac{1}{2} V_R e^{-\gamma l}$$

$$V_R = 57.4 \text{ kV}$$

$$S \therefore \gamma l = \sqrt{Z_L Y} l = \sqrt{Z Y} l = \sqrt{(0.13 + j0.49) \times 3.39 \times 10^{-6}} \times 320 \approx 320$$

$$= \sqrt{0.51 \angle 75.14^\circ \times 3.39 \times 10^{-6} \angle 90^\circ} \times 320 = 1.31 \times 10^{-3} \angle 82.57^\circ \approx 320$$

$$= \frac{0.42 \angle 82.57^\circ}{0.05 \angle 10.42^\circ} = 0.05 + j0.42$$

$$2 \therefore e^{\gamma l} = e^{0.05 + j0.42} = 1.05 \angle 24.08^\circ$$

$$2 \therefore e^{-\gamma l} = \frac{1}{1.05 \angle 24.08^\circ} = 0.95 \angle -24.08^\circ$$

$$3 \therefore V_{in} = \frac{57.4 \angle 0^\circ \times 1.05 \angle 24.08^\circ}{2} = 60.27 \angle 24.08^\circ \text{ kV} = 30.135 \angle 24.08^\circ \text{ kV}$$

$$3 \therefore V_{ref} = \frac{57.4 \angle 0^\circ \times 0.95 \angle -24.08^\circ}{2} = 54.53 \angle -24.08^\circ \text{ kV} = 27.265 \angle -24.08^\circ \text{ kV}$$

$$ii) \text{SIL} = \frac{|V_L|^2}{|Z_L|}$$

$$Z_L = 0.49 \angle 90^\circ$$

$$Y = \frac{3.39 \times 10^{-6}}{\omega}$$

$$S \text{ SIL} = \frac{|V_L|^2}{\sqrt{\frac{0.49}{3.39 \times 10^{-6}}}} = \frac{(\sqrt{3} \times 57.4 \times 10^3)^2}{0.38 \times 10^3} = 26.01 \text{ MW}$$

Q4) A 400 km, 50 Hz transmission line has the following data:

$$\text{Cosh}\gamma l = 0.9 \angle 1.3^\circ, \quad \text{Sinh}\gamma l = 0.5 \angle 85^\circ, \quad Z_c = 406 \angle -6^\circ \Omega$$

If the load on the line is 125 MVA at 215 kV and unity pf, evaluate the Radius of the power circle diagram. [12]

$$\text{Radius} = \frac{|V_s| |V_R|}{|B|}$$

$$2. \quad |V_R| = \frac{215 \text{ kV}}{\sqrt{3}} \Rightarrow$$

$$3. \quad B = Z_c \text{Sinh}\gamma l = 406 \angle -6^\circ \times 0.5 \angle 85^\circ = 203 \angle 79^\circ$$

$$\therefore |B| = |Z_c| |\text{Sinh}\gamma l| = 203$$

$$A = \text{Cosh}\gamma l$$

$$4. \quad V_s = A V_R + B I_R$$

$$I_R = \frac{125 \times 10^6}{\sqrt{3} \times 215 \times 10^3} \text{ A} = 335.7 \text{ A}$$

$$\therefore V_s = 0.9 \angle 1.3^\circ \times \frac{215}{\sqrt{3}} \times 10^3 \text{ V} + 203 \angle 79^\circ \times 335.7 \text{ A}$$

$$= 111.7 \times 10^3 \angle 1.3^\circ + 68.15 \times 10^3 \angle 79^\circ$$

$$= (124.67 + j 69.43) \times 10^3$$

$$\therefore |V_s| = 142.7 \text{ kV}$$

$$3. \quad \therefore \text{Radius} = 142.7 \times 10^3 \times \frac{215}{\sqrt{3}} \times 10^3 \times \frac{1}{203} = 87.26 \text{ MVA}$$