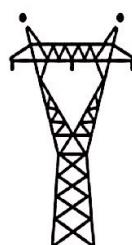





Power1

Fall017



Dr. Deefallah Dalabeeh 

 By: M hmd A buhashya

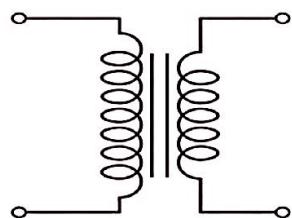

Powerunit-ju.com

Power System Analysis (I)


Dr. Daifallah Dalabeih

dalabeih@ju.edu.jo

Fall 2017-2018


Notebook.

By. Mohammad
Abu Hashya

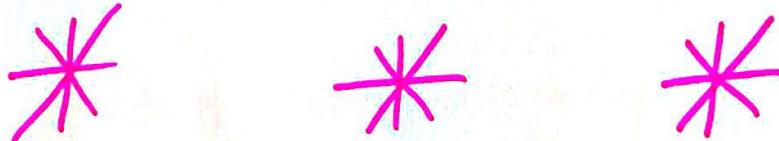

* Power System Components:

→ It consists of 3-subsystems:

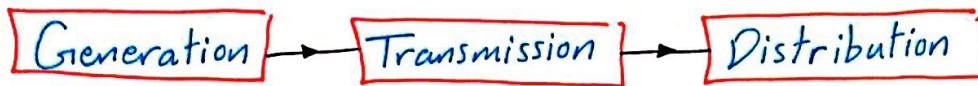

* Generation:

Electrical energy is generated at power stations or plants:

① Conventional power plants:

- a) Thermal: Example: steam turbine, Gas turbine, Combined cycle.
- b) Hydro.
- c) Renewable: Example: solar, wind, Tidal.


⇒ This symbol for generator.

• Bonus Question:

What are the types of power stations in Jordan?

1) Fossil fuel power stations

* Some of these P.S are still proposed.

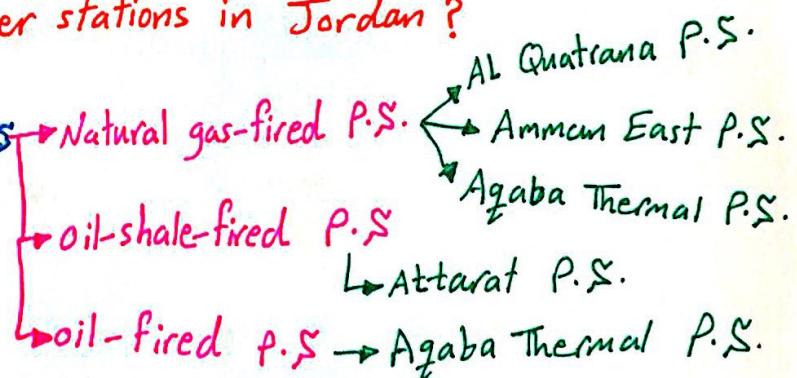

2) Renewable Energy Power stations



* Usually at conventional P.S voltage are generated in the range of (11-25) KV.

→ To transmit electrical energy this voltage is step-up by means of "3-ph transformers".

* In Jordan there are 2-levels of Transmission:
(132 and 400) KV.

[2]

⇒ This voltage is then step-down at transmission substation to various levels.

Example: in Jordan, such voltages are (33 and 11) KV.


* After that, this voltage is stepped-down for various consumers.
e.g. (6.6 KV, 3 KV and 380 V).

Q. How many Distribution Levels in Jordan? [Search in google].

* Power System Representation:


→ There are two approaches: 1) Graphical. 2) Mathematical.

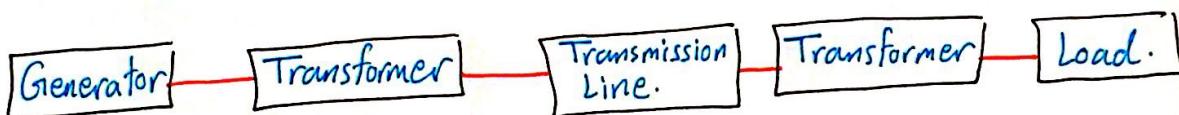* Graphical: This can be introduced by the following ^{block} system:



⇒ Since the system is balanced then one may use per-phase cct.

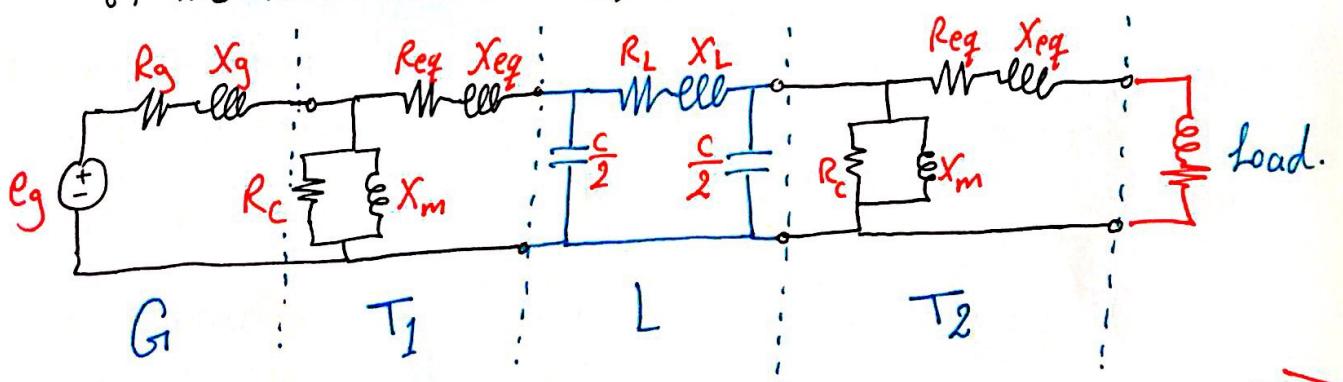
→ Here one make connections between the equivalent ccts of the various elements as follows:



This is "the exact equivalent per-phase cct."



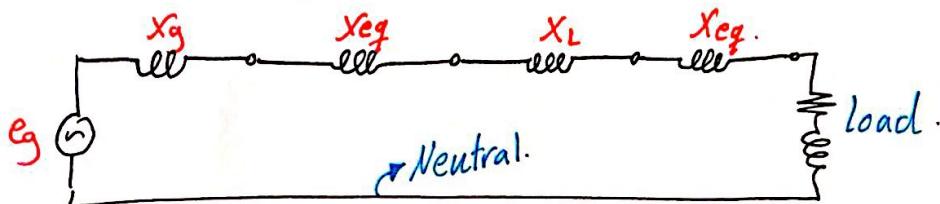- For more simplification one may neglect parallel Branches:
- Also one may neglect resistance of variance elements:



⇒ This Diagram is Called : "Reactance Diagram".

- Which can be used in the analysis of:
a given Power system.

* Single/one Line Diagram:


- since the Neutral is common to all elements, and if one is interested only in the connection between the various elements.
- Then each element or component is represented by a standard Symbol.

<u>Component</u>	<u>Symbol</u>	
Rotating machinery.	○	could be generator/Motor G
2-winding Transformer.	○○ or	
Busbar (i.e node)	or —	
Transmission Line	—○—	
Circuit Breaker.	* or	
Current Transformer	—○—	
Potential Transformer		
Isolator		
Wye Connection.	Y	
Delta Connection.	Δ	

* The amount of components to be displayed depends on the Required application.

- For e.g:
in Load flow analysis PT, CT and C.B are not shown.

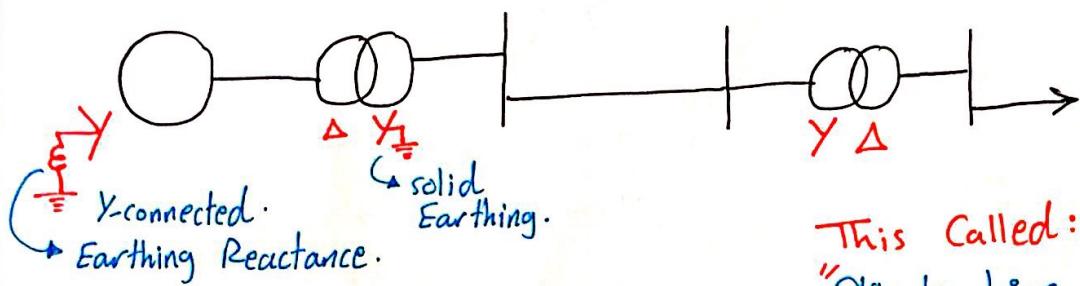* To Illustrate Consider the previous system:



This Called:
"Single Line Diagram".

* See the given paper (Directed Power Flow Diagram)

↳ This SLD shows the power flow for a given load condition.

* See the given paper (Power Supply System & Key Diagram for)
11/0.4 KV substation.

↳ Why we used the Capacitor Bank?

To Improve the pf. (pf Correction).

- C.B : It can make & Break.

- Isolator: It can't Break but It can make.

* Mathematical: \Rightarrow using Node Equations:


→ This is Illustrated as follows:

Example in the Book Fig 1.23.

* Equate the currents leaving a busbar through admittances

To currents entering busbar through sources.

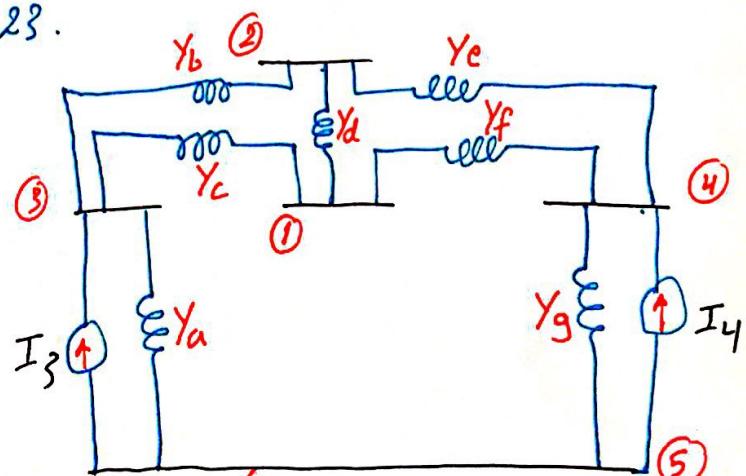$y_a, y_b, \dots =$ Admittance of the line.
 $(1) \rightarrow (5)$ Busbars.



↳ Reference Busbar.

→ Continue ...

$$(V_1 - V_3) Y_C + (V_1 - V_4) Y_F + (V_1 - V_2) Y_D = 0$$

$$\Rightarrow V_1 (Y_C + Y_F + Y_D) - V_2 Y_D - V_3 Y_C - V_4 Y_F = 0 \quad \dots \textcircled{1}$$

$$(V_2 - V_1) Y_D + (V_2 - V_3) Y_B + (V_2 - V_4) Y_E = 0$$

$$\Rightarrow V_2 (Y_D + Y_B + Y_E) - V_1 Y_D - V_3 Y_B - V_4 Y_E = 0 \quad \dots \textcircled{2}$$

$$(V_3 - V_1) Y_C + (V_3 - V_2) Y_B + (V_3 - V_4) Y_A = I_3$$

$$\Rightarrow -V_1 Y_C - V_2 Y_B + (Y_C + Y_B + Y_A) V_3 = I_3 \quad \dots \textcircled{3}$$

$$(V_4 - V_1) Y_F + (V_4 - V_2) Y_E + V_4 Y_G = I_4$$

$$\Rightarrow -Y_F V_1 - Y_E V_2 + (Y_F + Y_E + Y_G) V_4 = I_4 \quad \dots \textcircled{4}$$

• Now Re-write the Equations in a Matrix Form.

$$\begin{bmatrix} Y_C + Y_F + Y_D & -Y_D & -Y_C & -Y_F \\ -Y_D & Y_D + Y_B + Y_E & -Y_B & -Y_E \\ -Y_C & -Y_B & Y_C + Y_B + Y_A & 0 \\ -Y_F & -Y_E & 0 & Y_F + Y_E + Y_G \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ I_3 \\ I_4 \end{bmatrix} \Rightarrow [Y] [V] = [I]$$


Symmetrical Matrix.

$[Y] \Rightarrow$ Bus Admittance Matrix.

* You Can Note the following :

element $y_{ii} = \sum$ of admittance Connected directly to i^{th} busbar.

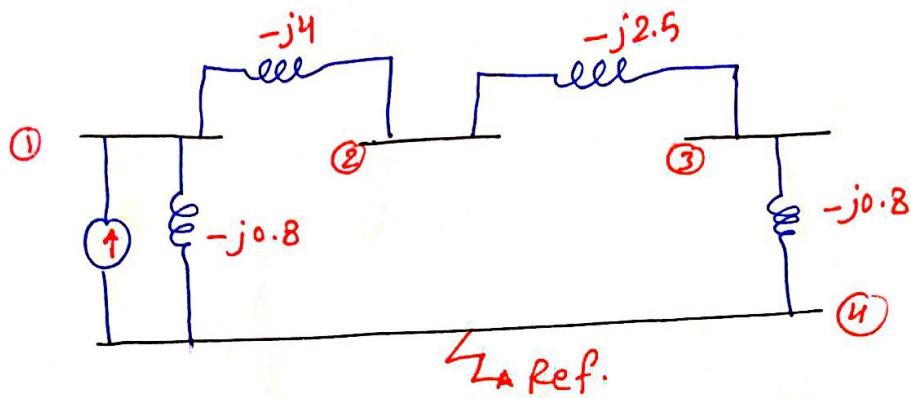element $y_{ij} = -1 * \text{Admittance between the } i^{\text{th}} \& j^{\text{th}} \text{ busbars.}$



example: For the given system, evaluate $[Y]$ bus matrix where the given data represent PV admittance?

solution:

$$Y = \begin{bmatrix} -j4.8 & j4 & 0 \\ j4 & -j6.5 & j2.5 \\ 0 & j2.5 & -j3.3 \end{bmatrix}$$

** Comment:
Bus Impedance $[Z]_{\text{bus}} \triangleq [Y]_{\text{bus}}^{-1}$

** Comment: 1) $[Y]$ is used in the load flow analysis.
2) $[Z]$ is used in the fault analysis.



** Revision of equivalent ccts of Transformers & 3-ph synchronous generator:

• Transformer:

⇒ In 1-ph or 3-ph Transformers, Per-phase equ. cct. is used as follows:

(Neglect the parallel branches).


$N_1:N_2 \equiv$ Turns Ratio.

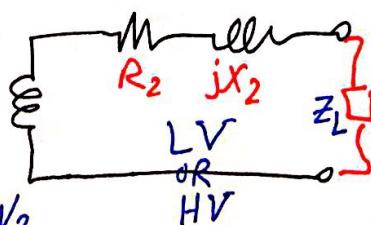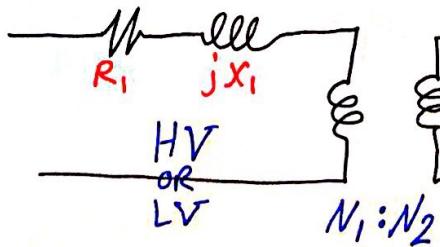

$$1 : \frac{N_2}{N_1} = a_1 \quad \text{or} \quad \frac{N_1}{N_2} = a_2 : 1 \rightarrow$$

⇒ By using the concept of Reflection:

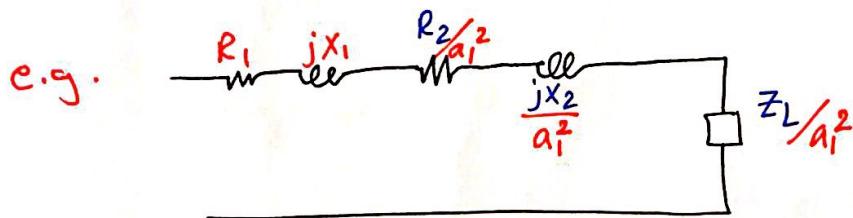- To reflect to (a) side multiply impedance by α_1^2 .
- To Reflect to (l) side divide impedance by α_1^2 .



$$R_{eq_1} = R_1 + R_2/\alpha_1^2, \quad X_{eq_1} = x_1 + x_2/\alpha_1^2$$

In using α units for resistance & Reactance

Then $R_{eq_1} \neq R_{eq_2}$ & $X_{eq_1} \neq X_{eq_2}$

However, By using the PV concept.

Then R_{eq} & X_{eq} are the same irrespective of the side being reflected to.

* Review the advantages of PV system.

1) Simplifies the process of solving system with many transformers.
2) The parameters of generators & transformers have the same range of values.

3) It simplifies the solution of 3-ph system, where $\sqrt{3}$ does not appear.

* For 3-ph Transformers, turns Ratio:

for Y-Y $\Rightarrow N_1 : N_2$

for Δ -Y $\Rightarrow N_1/\sqrt{3} : N_2$

for Δ - Δ $\Rightarrow N_1 : N_2$

for Y- Δ $\Rightarrow N_1 : N_2/\sqrt{3}$


Effective Turns Ratio $\equiv \alpha_{eff.}$



* It can be shown that: $a_{eff} = \text{line Voltage Ratio}$
 \Rightarrow Irrespective of the type of connection.

[8]

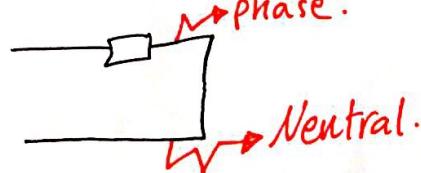- Note: In our solution procedure, we use per-phase^{cct} concept.




- Note: For a given power system, which contain many transformers

Then :

- 1) This system has one base value for Apparent Power.
- 2) However, each section has a base value for the voltage, this base value changes according to Transformer Ratio.

Illustration:

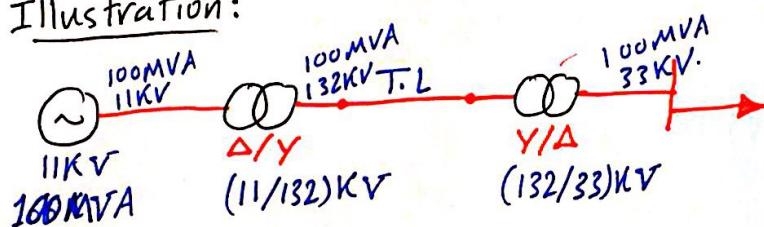

$$\text{Let } S_b = 100 \text{ MVA.} \\ V_b = 11 \text{ KV.}$$


$$X = 8\%.$$

$$X_{\text{new}} = X_{\text{old}} * \left(\frac{S_{\text{new}}}{S_{\text{old}}} \right) * \left(\frac{V_{\text{old}}}{V_{\text{new}}} \right)^2$$

assume we take
a base value $V_b = 22 \text{ KV}$
the base value in the
next transformer found
as follows:

$$\frac{22}{V_b} = \frac{11}{132} \text{ K}$$

Example:

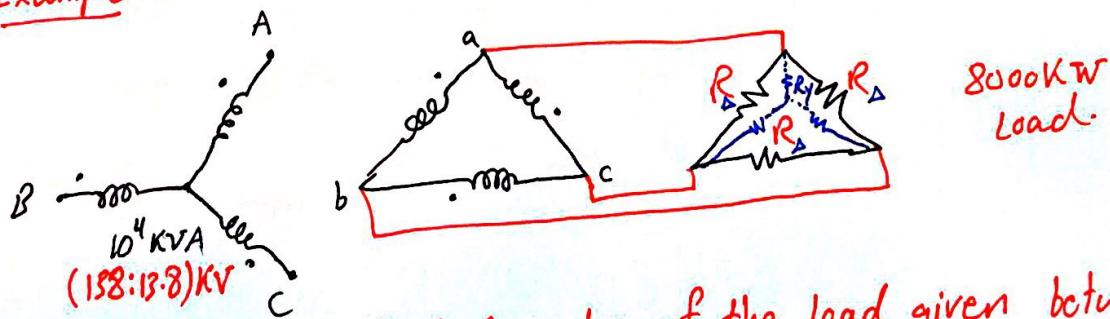

For the given system, find the value of the load given between phase and Neutral on the HV side?



Solution:

$$\text{since } P \triangleq \frac{V^2}{R} \Rightarrow R_{\Delta} = \frac{V^2}{P} = \frac{(13.8 * 10^3)^2}{8000 * 10^3 / 3} \Rightarrow R_{\Delta} = 71.45 \Omega$$

$$R_Y = \frac{R_{\Delta}}{3} \Rightarrow R_Y = 23.805 \Omega$$


$$R_{Y_{HV}} = \alpha_{eff}^2 R_Y = \left(\frac{138}{13.8}\right)^2 * 23.805 = 2380.5 \Omega$$

$$\Rightarrow Z_b = \frac{V_b^2}{S_b} = \frac{(138 * 10^3 / \sqrt{3})^2}{10^4 * 10^3 / 3} = 1904.4 \Omega$$

$$Z_b = \frac{V_{bLL}^2}{S_{b\text{total}}}$$

$$\text{so } R_{Y_{HV}}^{(PU)} = \frac{2380.5}{1904.4} = 1.25 \text{ PU.}$$

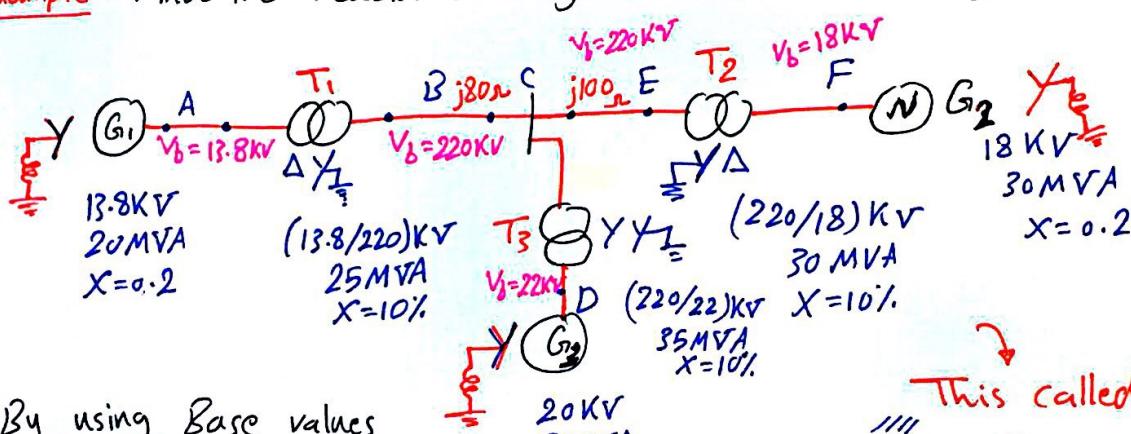Example: Find the Reactance diagram in PU for the following system:



By using Base values
of 50 MVA, 13.8 KV.

→ This called:
" +ve Sequence ccf."

Note: the specified PU Reactance of each component is Based on the Ratings of that component.

→ These considered as old values.

50 MVA, 13.8 KV ⇒ New values.

$$\text{Solution: } X_{\text{new}} = X_{\text{old}} \left(\frac{S_{\text{new}}}{S_{\text{old}}} \right) \left(\frac{V_{\text{old}}}{V_{\text{new}}} \right)^2$$


- for G_1 : $G_1 = 0.2 \left(\frac{13.8}{13.8} \right)^2 \left(\frac{50}{20} \right) = 0.5$

- for T_1 : $T_1 = 0.1 \left(\frac{13.8}{13.8} \right)^2 \left(\frac{50}{25} \right) = 0.2$

• Line BC : $Z_b = \frac{V_b^2}{S_b} = \frac{(220)^2}{50} = \boxed{968}$ (10)


$$\therefore Z_{\text{line (PV)}} = \frac{j80}{968} = \boxed{j0.083} \text{ PV.}$$

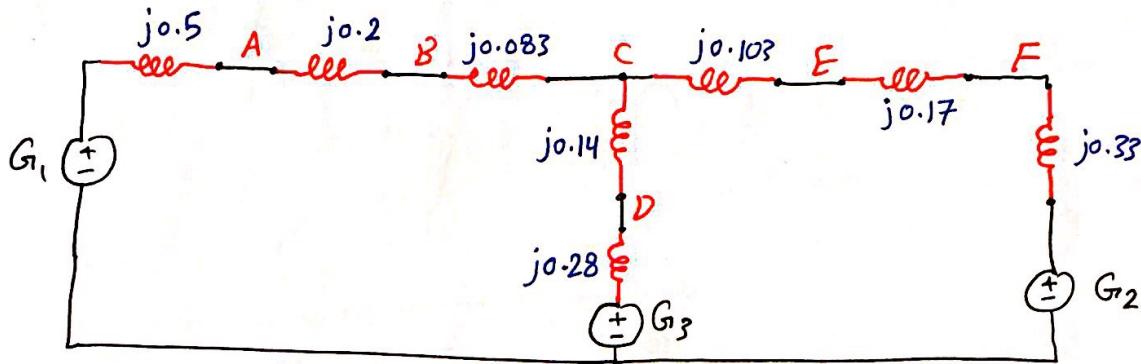• G_3 : $X_{\text{new}} = 0.2 \left(\frac{20}{22} \right)^2 \left(\frac{50}{30} \right) = \boxed{0.28}$




* Equivalent cct. of 3-ph synch. Gen. :

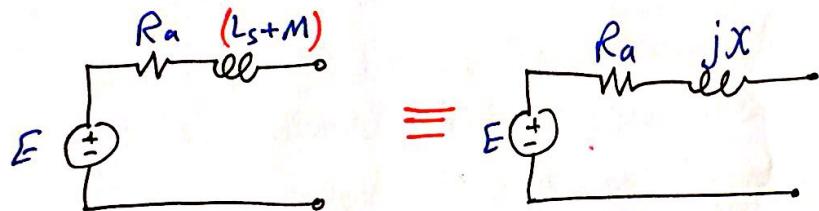- Armature ~~on~~ stator & field on Rotor.




* Equivalent cct. of 3-ph Gen. under S/C conditions:

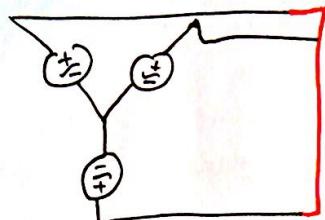- Objective: Find the Equivalent cct. under such condition.



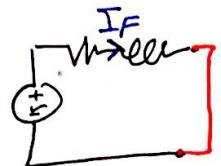⇒ Under this condition, a very high current is going to flow
 → This current generates an opposing flux to the main field flux (i.e. Armature Reaction) causing the generated voltage To Decrease and Consequantly the fault current will decrease.





This looks like the case of RL cct where an AC source is applied.

11

I_F ≡ Fault Current in the Armature Winding.

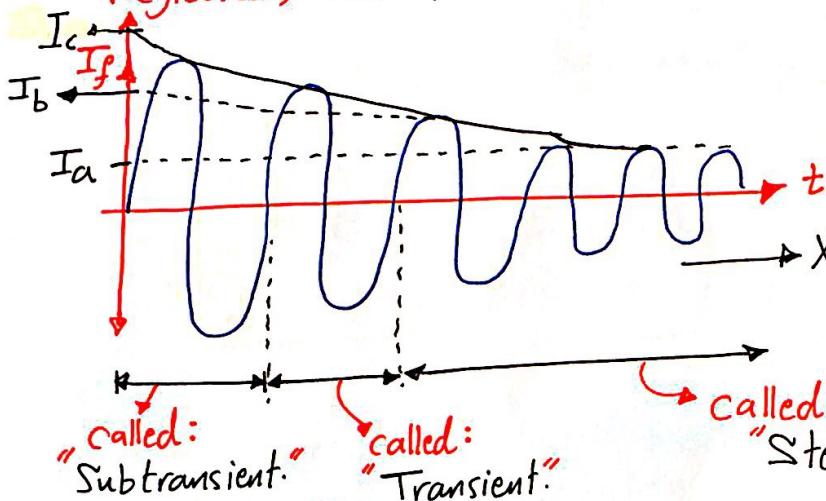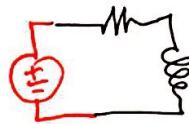- If the DC component in the response is neglected, Then I_F will look like the following:



"figure (1)"

I_a = peak current @ steady state.

* Since it is assumed that No load emf of the generator doesn't change, Then To account for current decrease, it is assumed that the gen. Reactance changes.

The so called "Subtransient Reactance X", "Transient Reactance X", and "Steady State Reactance X".

- I_F can be expressed as :

$$I_F = |E| \frac{1}{x} + |E| \left(\frac{1}{x'} - \frac{1}{x} \right) e^{-t/\tau'} + |E| \left(\frac{1}{x''} - \frac{1}{x'} \right) e^{-t/\tau''}$$

$|E|$ ≡ RMS value of the No-load phase voltage.

τ', τ'' ≡ Time Constants of Transient and Subtransient Conditions.

* If figure(1) is given, Then it can be used to find experimentally x, x', x'' as follows :



$$\frac{I_a}{\sqrt{2}} = \frac{|E|}{X} \dots \textcircled{1}$$

$$\frac{I_b}{\sqrt{2}} = \frac{|E|}{X'} \dots \textcircled{2}$$


$$\frac{I_c}{\sqrt{2}} = \frac{|E|}{X''} \dots \textcircled{3}$$

Comment:

1] If the graph of the fault current is given, Then $\textcircled{1}$, $\textcircled{2}$, & $\textcircled{3}$ can be used to evaluate X , X' , X'' .

2] If X , X' , X'' are known, Then the equivalent cct. can be found and consequently fault current I_f'' , I_f' , I_f can be evaluated.

Equ. cct.:

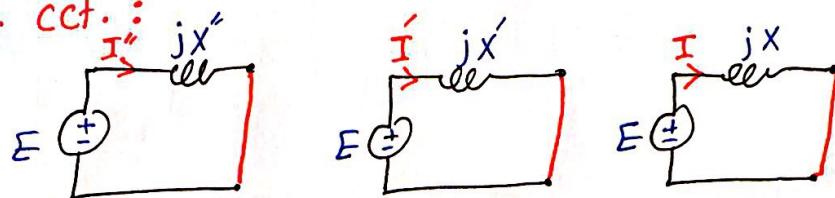

* Subtransient used in circuit breaker.

* Transient used in stability.

* Steady state used in steady state applications.

Example: A 300MVA, 13.8KV, 3-ph Y-connected 60Hz generator.

is adjusted to give rated voltage at O/C.

a 3-ph fault is applied to its O/C terminals, the obtained fault current was as follows:

$$i = 10^4 \left[1 + e^{-t/\tau_1} + 6 e^{-t/\tau_2} \right], \text{ where } \tau_1 = 200 \text{ ms}, \tau_2 = 15 \text{ ms}$$

Evaluate: X , X' , X'' in Ω & in PU.

Solution: $\tau_1 = 200 \text{ ms}$ (Transient) & $\tau_2 = 15 \text{ ms}$ (Subtransient)

By Comparing it with the given general expression

and knowing that $|E| = \frac{13.8}{\sqrt{3}} \text{ KV} \Rightarrow$ $X = 0.797 \Omega$
 $X' = 0.398 \Omega$
 $X'' = 0.0996 \Omega$

$$Z_b = \frac{V_{LL}^2}{S_{3\phi}} = \frac{(13.8K)^2}{300M} = 0.635 \Omega$$

Per unit values:

$X = 1.26 \text{ PU}$
$X' = 0.627 \text{ PU}$
$X'' = 0.157 \text{ PU}$

• Note: In the eqn. cct. of 3-ph Transformer


[13]

in the case of Y-Y or Δ-Δ There is 0°-phase shift.

in the case of Δ-Y or Y-Δ There is a 30° -phase shift.

⇒ In the Convention, in the +ve phase sequence the HV Leads LV by 30° , in the -ve phase sequence the HV Lags LV by 30° .

• +ve phase sequence, in PU:

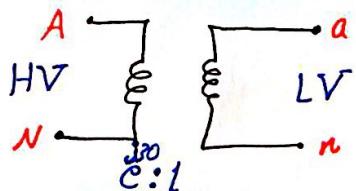

* Illustration:

Assume +ve phase sequence.

If the Line voltage & Line current at the gen. terminals are 11.9KV & 20A respectively, & the pf seen by the gen. is 0.8 lagging. Find the Line Current & voltage at LV side


By using PU concept & using base values of $12\text{KV}, 600\text{kVA}$. ?

Solution:

$$I_b = \frac{600 \times 10^3}{\sqrt{3} \times 12 \times 10^3} \Rightarrow I_b = 28.87\text{A}$$

$$|I_A|_{(PU)} = \frac{20}{28.87} \Rightarrow |I_A| = 0.69 \text{ PU}$$

$$|V_{AN}| = \frac{11.9/\sqrt{3}}{12/\sqrt{3}} \Rightarrow |V_{AN}| = 0.99 \text{ PU}$$

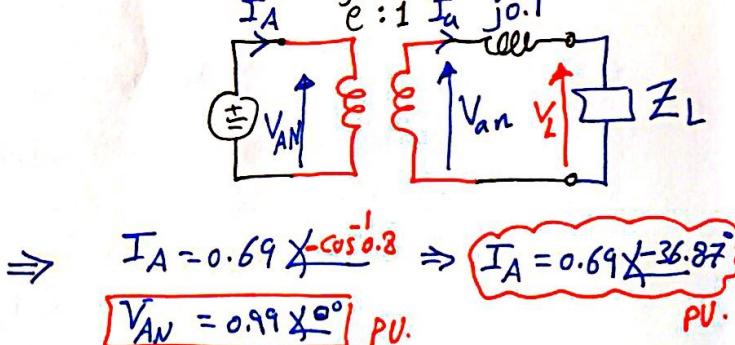

$$\Rightarrow I_A = 0.69 \times \underline{\cos 0.8} \Rightarrow I_A = 0.69 \times 0.87 \text{ PU}$$

$$V_{AN} = 0.99 \times \underline{0^\circ} \text{ PU}$$

Now the values seen from LV: $V_{an} = 0.99 \times \underline{-30^\circ}$ & $I_a = 0.69 \times \underline{-66.87^\circ}$

$$V_L = V_{an} - j0.1 * I_a \Rightarrow V_L = 0.95 \times \underline{-33.4^\circ}$$

$$Z_L = V_L / I_a \Rightarrow Z_L = 1.38 \times \underline{33.5^\circ}$$

*

*

*


Transmission Line:

114


- Objective: To find voltage, Current and Power Relationships.
- Procedure: Find the equivalent cct. of T.L.
- Parameters of Transmission Line:
 - 1) Resistance. 2) Inductance. 3) Capacitance. 4) Conductance.

V_s = Sending End Voltage.

V_R = Receiving End Voltage.

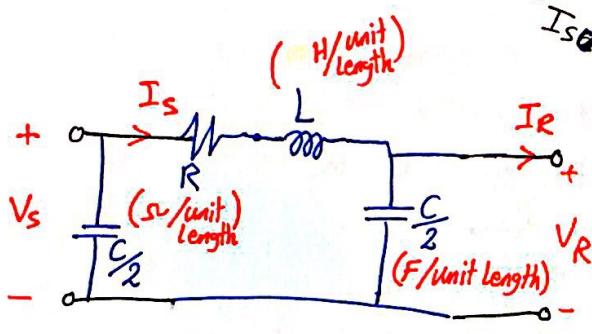

$$R_{dc} = \frac{\rho L}{A}$$

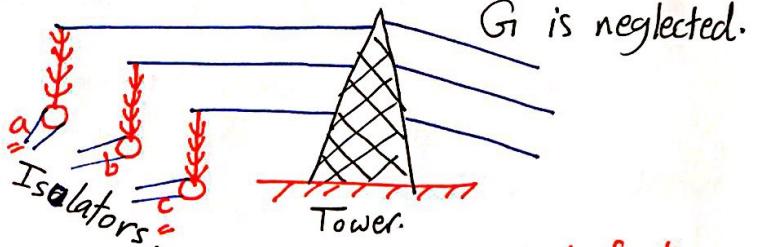

Type classifications.

- * Since the line is made from a Conducting material (e.g AAC, ACSR)
 - Conductor: Aluminum
 - All
- Then it has a Resistance, R.

However, one use R_{ac} . ($R_{ac} > R_{dc}$), which can be found from standard Tables.

- * Since the line carry ac current \rightarrow generate ϕ \rightarrow ϕ will induce a voltage in the Conductor. This is represented by L.

C = Used To Represent The Capacitance Effect Between phase & ground or Neutral.

- * Conductance, which represent the Leakage current along the ~~line~~ insulators of the line due to Pollution, it is very small and variable.

- * The inductance & Capacitance of lines depend on the configuration of the lines.




For e.g.: for Equilateral Lines L & C can be found as follows:

15

$$L = 2 * 10^{-7} \ln\left(\frac{D}{D_s}\right) \text{ H/m.}$$

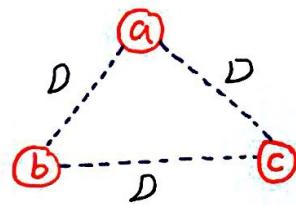D_s \equiv Called Geometrical Radius (G.M.D)
and can be found from standard tables.



D \equiv Distance Between Lines & Conductors.

$$C_n = \frac{2\pi\epsilon}{\ln(D/r)} \text{ F/m}$$

C_n \equiv Capacitance Between Phase & Neutral.
 r \equiv Radius of the Conductor.

Example: A 18 Km, 60 Hz, single-cct. 3-ph line composed of porridge conductors equally spaced with 1.6 m. between centers. Assume wire temperature of 50°C. Find the series impedance of the line? (i.e. $\underline{\underline{R+jX}}$)

Solution: from the given standard tables @ 50°C $R_{af} = 0.3792 \Omega/\text{mi}$

$$\text{for this line: } R = 0.3792 * \frac{18}{1.609} \Rightarrow R = 4.24 \Omega.$$

$$L = 2 * 10^{-7} \ln\left(\frac{D}{D_s}\right) ; D = 1.6 \text{ m, from standard tables } D_s = 0.0217 \text{ ft.}$$

$$\Rightarrow L = 2 * 10^{-7} \ln\left(\frac{1.6}{0.0217 * 0.3048}\right) \Rightarrow L = 10.98 * 10^{-7} \text{ H/m.}$$

Note:

$$\begin{aligned} 1 \text{ mile} &= 1.609 \text{ Km.} \\ 1 \text{ ft} &= 30.48 \text{ cm} = 0.3048 \text{ m} \end{aligned}$$

$$\therefore \text{For this T-Line: } L = 10.98 * 10^{-7} * 18000$$

$$\Rightarrow L = 0.0197 \text{ H.}$$

$$\therefore X = \omega L = 2\pi * 60 * 0.0197 = 7.43 \Omega$$

$$\therefore Z = R + jX$$

$$\Rightarrow Z = 4.24 + j7.43$$

#

*Analysis:

• Lines Can be Classified into:


- 1) Short Line up to 80 Km.
- 2) Medium Line ($80 < L < 240$) Km.
- 3) Long Line ($L > 240$) Km.

Note: There is 2 classifications for T.L : Types & Lengths.

• Short Line:

Hence the capacitance effect is neglected.

∴ Equivalent cct:

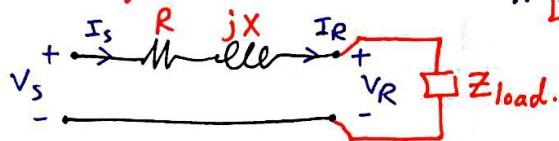

$$\therefore I_s = I_R, \quad V_s = I_s(R + jX) + V_R$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

Called:


* Voltage Regulation: $V_R\% = \frac{|V_{R,NL}| - |V_{R,FL}|}{|V_{R,FL}|} * 100\%$

ABCD parameters
of short T. Line.


⇒ The Line will be analyzed under Inductive, Capacitive and Resistive loading conditions. By using the concept of 'phasor diagram'!

• Here it will be assumed that $|V_R|$ & $|I_R|$ fixed and the pf is varied.


* Inductive load:

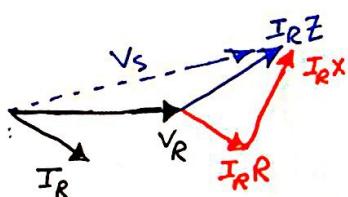

* Capacitive Load:

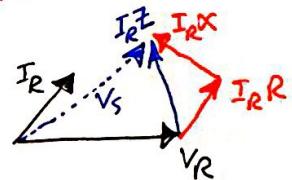


* Resistive Load:

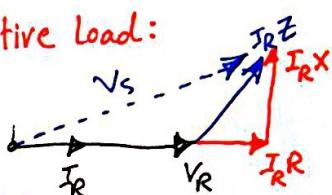

$$V_s(\text{ind}) > V_s(\text{Res}) > V_s(\text{cap})$$

* Ferranti-Effect: It is the increase in voltage occurring at the receiving end of a long T.L above the voltage at the sending end and it is more pronounced as how much the longer the line & the higher the voltage applied, also more pronounced in underground cables.

• Medium Line:

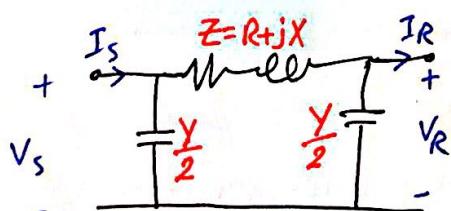

KCL: $I_s = V_s \frac{Y}{2} + (I_R + V_R \frac{Y}{2})$

$Z \equiv$ Total series impedance of the line.

$Y \equiv$ Total shunt admittance of the line = jwC .

KVL: $V_s = Z(I_R + V_R \frac{Y}{2}) + V_R$

$$\Rightarrow V_s = V_R \left(1 + \frac{ZY}{2} \right) + Z I_R$$



⇒ Substitute ① in ②:

$$\begin{aligned} I_s &= \frac{Y}{2} \left[V_R \left(1 + \frac{ZY}{2} \right) + Z I_R \right] + I_R + V_R \frac{Y}{2} \\ &= V_R \left[\frac{Y}{2} \left(1 + \frac{ZY}{2} \right) + \frac{Y}{2} \right] + I_R \left(1 + \frac{ZY}{2} \right) = \boxed{V_R \left(Y + \frac{ZY^2}{4} \right) + I_R \left(1 + \frac{ZY}{2} \right)} \dots ③ \end{aligned}$$

⇒ Re-write ① & ③ in Matrix Form:

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix} \quad \text{As required } D=A \text{. } \# .$$

$$\therefore V_s = A V_R + B I_R \dots ④$$

$$I_s = C V_R + D I_R \dots ⑤$$

$$VR\% = \frac{|V_{R,NL}| - |V_{R,FL}|}{|V_{R,FL}|} * 100\% \Rightarrow V_{R,NL} \text{ means } I_R = 0$$

$$\therefore ④ \Rightarrow V_{R,NL} = \frac{V_s}{A}$$

so, we could write:

$$VR\% = \frac{|V_s/A| - |V_{R,FL}|}{|V_{R,FL}|} * 100\%$$

• Long Transmission Line:


In this case the line is represented by:
a distributed Parameters as follows:

$Z \equiv$ Series Impedance per unit length (Ω/mile)

$y \equiv$ Shunt Admittance per unit length (S/mile)

*Objective: To derive the equations for $V(x)$ & $I(x)$.

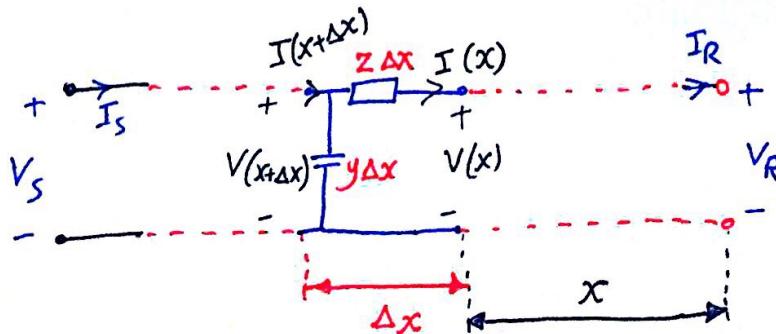*Procedure: Consider a small segment of the line of the length Δx where x is measured from Receiving End.



By KVL: $V(x+Δx) = I(x) Z \Delta x + V(x)$

$$\therefore Z I(x) = \frac{V(x+Δx) - V(x)}{Δx} \Rightarrow \boxed{\frac{dV}{dx} = Z I(x)} \dots \square$$



By KCL: $I(x+\Delta x) = V(x+\Delta x) y \Delta x + I(x)$

$$\therefore \frac{I(x+\Delta x) - I(x)}{\Delta x} = y V(x+\Delta x) \Rightarrow \frac{dI}{dx} = y V(x) \dots [2]$$

* Diff. ② & ① with respect to x :

$$\frac{d^2V}{dx^2} = \gamma \frac{dI}{dx} = \gamma y V(x)$$

$$\frac{d^2I}{dx^2} = y \frac{dV}{dx} = y \gamma I(x)$$

$$\therefore \frac{d^2V}{dx^2} = \gamma y V(x) \dots [3]$$

$$\frac{d^2I}{dx^2} = \gamma y I(x) \dots [4]$$

* To simplify let $\gamma^2 = \gamma y$:

$\therefore \gamma = \sqrt{\gamma y}$, and it is called = propagation Constant.

$Z_c = \sqrt{\frac{\gamma}{y}}$ = Characteristic Impedance.

$$\Rightarrow \frac{d^2V}{dx^2} = \gamma^2 V, \quad \frac{d^2I}{dx^2} = \gamma^2 I \dots [5]$$

* Solve ⑤ & ⑥ To find $V(x)$ & $I(x)$:

$$\begin{aligned} V(x) &= A_1 e^{\gamma x} + A_2 e^{-\gamma x} \dots [7] \\ I(x) &= B_1 e^{\gamma x} + B_2 e^{-\gamma x} \dots [8] \end{aligned}$$

where A_1, A_2, B_1 & B_2 Constants to be found from initial conditions.

* Finding A_1 & A_2 : $V(0) = V_R = A_1 + A_2 \dots [9]$

$$\frac{dV}{dx} = A_1 \gamma e^{\gamma x} - A_2 \gamma e^{-\gamma x} \Rightarrow Z I(x) = A_1 \gamma e^{\gamma x} - A_2 \gamma e^{-\gamma x}$$

$$\gamma I(0) = A_1 \gamma - A_2 \gamma = \gamma I_R \dots [10]$$

* Solve ⑨ & ⑩ To find A_1 & A_2 :

$$\gamma * [9] + [10]: \quad \gamma V_R + \gamma I_R = 2A_1 \gamma \Rightarrow \therefore A_1 = \frac{1}{2} \left(\frac{\gamma V_R + \gamma I_R}{\gamma} \right) = \frac{1}{2} (V_R + \frac{\gamma}{2} I_R)$$

$$\Rightarrow A_1 = \frac{1}{2} (V_R + \sqrt{\frac{\gamma}{2}} I_R) \Rightarrow A_1 = \frac{1}{2} (V_R + Z_c I_R) \dots [11]$$

* from ⑩: $A_2 = V_R - A_1 \Rightarrow A_2 = V_R - \frac{1}{2} (V_R + Z_c I_R) \Rightarrow A_2 = \frac{1}{2} (V_R - Z_c I_R) \dots [12]$

* Substitute ⑪ & ⑫ into ⑦:

$$\begin{aligned} V(x) &= \frac{1}{2} (V_R + Z_c I_R) e^{\gamma x} + \frac{1}{2} (V_R - Z_c I_R) e^{-\gamma x} \\ &= V_R \left(\frac{e^{\gamma x} + e^{-\gamma x}}{2} \right) + I_R Z_c \left(\frac{e^{\gamma x} - e^{-\gamma x}}{2} \right) \Rightarrow V(x) = V_R \cosh \gamma x + Z_c I_R \sinh \gamma x. \end{aligned} \dots [13]$$

* By Similar procedures one can find B_1 & B_2 , By substitution it can be found:

$$I(x) = \frac{V_R}{Z_c} \sinh \gamma x + I_R \cosh \gamma x \dots [14]$$

[19]

$\therefore @ x = L$ (i.e. length of the line)

$$V(L) = V_s = V_R \cosh \gamma L + Z_c I_R \sinh \gamma L$$

$$I(L) = I_s = \frac{V_R}{Z_c} \sinh \gamma L + I_R \cosh \gamma L$$

\therefore Writing V_s & I_s in Matrix Form:

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

where:

$$\boxed{A = D = \cosh \gamma L}$$


$$\boxed{B = Z_c \sinh \gamma L}$$

$$\boxed{C = \frac{1}{Z_c} \sinh \gamma L}$$

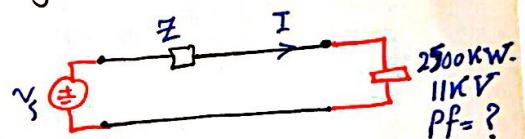Example: For the previous example of the 18Km Line. If this line delivers **2500 KW** of **11KV** to a balance load. Find V_s & voltage Regulation when the pf is 1) 0.8 lagging. 2) unity. 3) 0.9 leading.

Solution: $V_s = V_R + I Z \Rightarrow V_R = \frac{11}{\sqrt{3}} * 10^3 \angle 0^\circ$ volt.

$$Z = 4.24 + j 7.45 = 8.57 \angle 60.35^\circ \Omega$$



$$1) 0.8 \text{ Lag. : } I = \frac{2500 * 10^3}{\sqrt{3} * 11 * 10^3 * 0.8} \angle -\cos^{-1} 0.8 \Rightarrow I = 164.02 \angle -36.87^\circ A$$

$$\text{By substitution: } V_s = 7660.66 \angle 4.19^\circ \text{ volt.}$$

$$VR\% = 20.6\%$$

$$2) \text{ unity : } I = \frac{2500 * 10^3}{\sqrt{3} * 11 * 10^3 * 1} \angle 0^\circ \Rightarrow I = 131.2 \angle 0^\circ A \quad \therefore V_s = 6975.9 \angle 8.05^\circ \text{ volt.}$$

$$VR\% = 9.84\%$$

$$3) 0.9 \text{ Lead: } I = \frac{2500 * 10^3}{\sqrt{3} * 11 * 10^3 * 0.9} \angle \cos^{-1} 0.9 \Rightarrow I = 145.8 \angle 25.8^\circ A \quad \therefore V_s = 6553.6 \angle 10.97^\circ \text{ volt.}$$

$$VR\% = 3.19\%$$

$$* \text{ Voltage Regulation found by: } VR\% = \frac{|V_s| - |V_R|}{|V_R|} * 100\%.$$

Example: A 60HZ, 3-ph Transmission 175 miles Long.

It has a total series impedance of $Z = 35 + j 140 \Omega$, and a total shunt admittance of $Y = 930 * 10^{-6} S$. The line delivers 40MW at 220KV and 0.9 pf lagging.

Find: a) V_s , I_s and the pf @ the sending end.

b) $VR\%$ & γ of the line.

Solution:

$$a) \begin{aligned} V_s &= \cosh \gamma L V_R + (Z_c \sinh \gamma L) I_R \\ I_s &= \left\{ \begin{array}{l} \frac{1}{Z_c} \sinh \gamma L V_R + (\cosh \gamma L) I_R \\ C \end{array} \right. \end{aligned}$$

$$\Rightarrow Z_c = \sqrt{Z/Y} = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{35 + j 140}{930 * 10^{-6}}} \Omega$$

$$Z_c = 393.9 \angle 7^\circ \Omega$$

$$\gamma L = \sqrt{ZY} L = \sqrt{(35 + j 140)(j 930 * 10^{-6})}$$

$$\Rightarrow \gamma L = 0.3663 \angle 83^\circ$$

$$\text{So } \gamma L = 0.3663 \angle 83^\circ = 0.0446 \cdot j 0.3636 \text{ rad.}$$

$$\Rightarrow \underline{C} = 1.0456 \times^{20^\circ}, \quad \underline{\bar{C}} = \frac{1}{e^{\gamma L}} = 0.9563 \times^{-20^\circ}$$

20

$$A = D = \cosh \gamma L = \frac{1}{2} [\underline{C} + \underline{\bar{C}}] \Rightarrow A = D = 0.9407 \times^{1^\circ}$$

$$B = Z_c \sinh \gamma L \Rightarrow B = 135.9 \times^{76^\circ}$$

$$C = \frac{1}{Z_c} \sinh \gamma L = \frac{1}{2Z_c} [\underline{C} - \underline{\bar{C}}] \Rightarrow C = 875 * 10^6 \times^{90^\circ}$$

$$V_R = \frac{220}{\sqrt{3}} \times^0 \text{KV} \Rightarrow I_R = \frac{40 * 10^6}{\sqrt{3} * 220 * 10^3 * 0.9} \times^{-\cos 10.9^\circ} \Rightarrow I_R = 116.6 \times^{-25.8^\circ} \text{A}$$

$$\text{By substitution it can be found: } V_s = 130.4 \times^{6.3^\circ} \text{KV}$$

$$I_s = 119 \times^{33^\circ}$$

$$\text{PF @ sending end} = \cos(6.3 - 33) = 0.8934 \text{ Leading.}$$

$$b) VR\% = \frac{|V_s/A| - |V_R|}{|V_R|} * 100\% = 9.15\%, \quad \eta = \frac{P_{out}}{P_{in}} = \frac{40 * 10^6}{\sqrt{3} V_s I_s \text{ PF}} \Rightarrow \eta = 96.5\%$$

Note: See the report about the losses in NEPCO.

* Comments:


- It was found that: $V_s(x) = \frac{V_R + I_R Z_c}{2} e^{\gamma x} + \frac{V_R - I_R Z_c}{2} e^{-\gamma x}$

$$\text{let } \gamma = \alpha + j\beta$$

where: $\alpha \equiv \text{Attenuation Constant}$. so $\frac{\gamma x}{e^{\gamma x}} = \frac{\alpha x}{e^{\alpha x}} \cdot \frac{j\beta x}{e^{\alpha x}}$
 $\beta \equiv \text{Phase shift.}$ $\frac{-\gamma x}{e^{-\gamma x}} = \frac{-\alpha x}{e^{-\alpha x}} \cdot \frac{-j\beta x}{e^{-\alpha x}}$

$\therefore V_s \text{ & } I_s \text{ consists of Incident & Reflected components.}$

If the line is Terminated by its Characteristic Impedance (i.e Z_c)
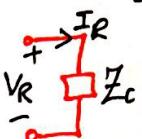
$$\therefore V_R = I_R Z_c$$


\therefore In this case, There is NO Reflected Component in $V_s \text{ & } I_s$.

\Rightarrow In this Case, The line is Called "Flat or ∞ -line."

* Surge Impedance:

↳ it is the characteristic impedance of a Lossless Line ($R=0$) since $Z=R+jX$
 $Z_c = \sqrt{Z/X} = \sqrt{\frac{j\omega L}{j\omega C}} \Rightarrow Z_c = \sqrt{\frac{L}{C}}$


* Surge Impedance Loading (SIL) of a Transmission Line:

21

SIL it is the power supplied by the line to a pure resistive load whose magnitude is equal to surge impedance.

$$|I| = \frac{|V|}{R} \Rightarrow |I| = \frac{|V_p|}{\sqrt{L/C}}$$

phase voltage.

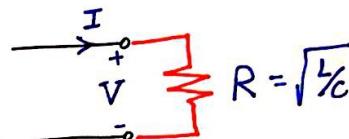

$$P = \sqrt{3} V_I * I = \sqrt{3} V \frac{V}{\sqrt{3}} \frac{1}{\sqrt{L/C}} \Rightarrow P = \frac{V^2}{\sqrt{L/C}}$$


Line voltage

$$|V_L| = \sqrt{3} |V_p|$$

* Equivalent Circuit of a Long Transmission Line:

• objective: To represent by the π -equivalent.

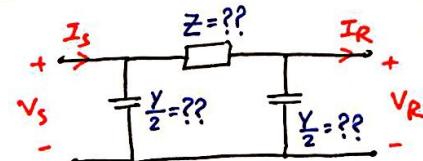• procedure: To find the equivalents of the series & shunt components. (i.e Z' & $\frac{Y}{2}$).



* For this π -cct it was found that:

$$V_s = (1 + \frac{Z Y}{2}) V_R + Z I_R \dots (1)$$

$$* \text{For Long T.L it was found that: } V_s = \cosh \gamma L V_R + Z_c \sinh \gamma L I_R \dots (2)$$

$$\therefore \text{by equating (1) \& (2): } Z = Z_c \sinh \gamma L \dots (3)$$

$$\Rightarrow 1 + \frac{Z Y}{2} = \cosh \gamma L \Rightarrow \frac{Z Y}{2} = \cosh \gamma L - 1 \Rightarrow \frac{Y}{2} = \frac{\cosh \gamma L - 1}{Z} \dots (4)$$

Substitute (3) into (4):

$$\frac{Y}{2} = \frac{\cosh \gamma L - 1}{Z_c \sinh \gamma L} = \frac{\frac{\gamma L}{2} - \frac{\gamma L}{2}}{\frac{e^{\gamma L} - e^{-\gamma L}}{2}} - 1 \cdot \frac{1}{Z_c} = \frac{1}{Z_c} \frac{\left(\frac{\gamma L}{2} - \frac{\gamma L}{2}\right)^2}{\left(\frac{e^{\gamma L/2} - e^{-\gamma L/2}}{2}\right)^2}$$

$$\Rightarrow \frac{Y}{2} = \frac{1}{Z_c} \frac{\frac{\gamma L}{2} - \frac{\gamma L}{2}}{\frac{e^{\gamma L/2} + e^{-\gamma L/2}}{2}} \Rightarrow \frac{Y}{2} = \frac{1}{Z_c} \tanh\left(\frac{\gamma L}{2}\right) \dots (5)$$

$\therefore (3) \& (5)$ Can be used to find Equivalent π -cct.

Example: Find π -Egu. cct of the Long T.L in the previous example?

Solution:

By substitution it can be found that:

$$\boxed{Z' = 135.9 \angle 76^\circ}$$

$$\boxed{Y/2 = 4.64 \times 10^{-4} \angle 90.9^\circ}$$


* Power Flow in a T-Line:

- Although one can calculate power flow at any point along the line by knowing voltage, current & pf. However the objective: is to evaluate such power by using the $[A \ B]$ constants.

• procedure: it was found that:

$$V_s = A V_R + B I_R \quad \therefore I_R = \frac{V_s - A V_R}{B}$$

$$S = V_R I_R^* \quad , \text{Let: } V_s = |V_s| \angle \delta, A = |A| \angle \alpha \\ V_R = |V_R| \angle 0^\circ, B = |B| \angle \beta$$

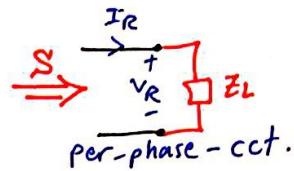

$$\therefore I_R = \frac{|V_s| \angle \delta - |A| |V_R| \angle \alpha}{|B| \angle \beta} = \frac{|V_s| \angle \delta - \beta}{|B|} - \frac{|A| |V_R| \angle \alpha - \beta}{|B|}$$

$$S = V_R I_R^* = \frac{|V_R| |V_s| \angle \beta - \delta}{|B|} - \frac{|A| |V_R|^2 \angle \beta - \alpha}{|B|} \dots \textcircled{1}$$

since $S = P + j Q \dots \textcircled{2}$ * Applying $\textcircled{2}$ to $\textcircled{1}$:

$$\Rightarrow P = \frac{|V_R| |V_s|}{|B|} \cos(\beta - \delta) - \frac{|A| |V_R|^2}{|B|} \cos(\beta - \alpha) \dots \textcircled{3}$$

$$Q = \frac{|V_R| |V_s|}{|B|} \sin(\beta - \delta) - \frac{|A| |V_R|^2}{|B|} \sin(\beta - \alpha) \dots \textcircled{4}$$


Hence by using $\textcircled{3}$ & $\textcircled{4}$ one may calculate P & Q transmitted by a T. Line.

equation $\textcircled{1}$ can be used to express S graphically.

$$S = \left(\frac{|V_R| |V_s| \angle \beta - \delta}{|B|} - \frac{|A| |V_R|^2 \angle \beta - \alpha}{|B|} \right) \textcircled{2}$$

shift the origin from point n to point o .

Let the load changes by keeping $|V_s|$ & $|V_R|$ constants.

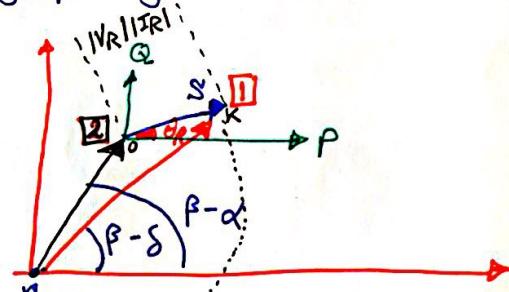

As the load changes by changing α , then the line (nK) is going to move along a circle. Consequently, P & Q are going to change.

P_{max} will occur when $\beta - \delta = 0 \quad \therefore \beta = \delta$



$$P_{max} = \frac{|V_R| |V_s|}{|B|} - \frac{|A| |V_R|^2}{|B|} \cos(\beta - \alpha) \quad \text{max @ leading pf.}$$

* Reactive Compensation:

At heavy load, there will be large voltage drop in the impedance of the line and consequently high value for V_R . Since the major component of the impedance is inductive Reactance (X_L). Then this can be reduced by inserting Capacitance (X_C) in series with the line. This is called "Series Compensation".

Ratio of $\frac{X_C}{X_L}$ is called "Series Compensation Factor".

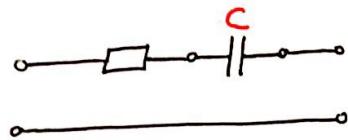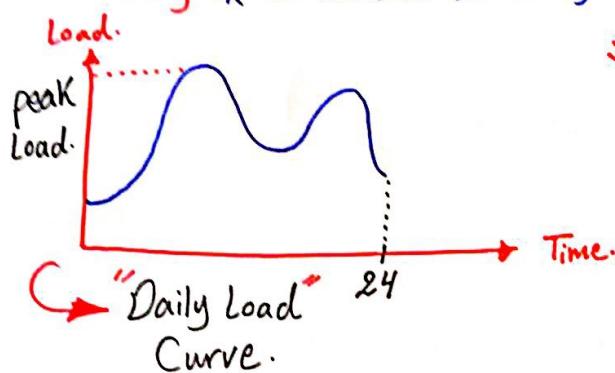* Under No-load or lightly Load Line, the effective Load will be Capacitive. Causing V_R to increase to a high value.



23

* To solve this problem, then an Inductor is placed in Parallel between phase & Neutral. This is called "Shunt Reactive Compensation". Hence, shunt compensation factor $\cong \frac{B_L}{B_C}$

$$\text{where: } B_L = \frac{1}{\omega L} \text{ & } B_C = \omega C$$

* To reduce charging current:


$$I_B = j\omega C V$$

$$\text{Before: } I_A = V \left(j\omega C - \frac{j}{\omega L} \right) = V j\omega C \left(1 - \frac{1}{\omega C} \cdot \frac{1}{\omega L} \right)$$

$$\text{After: } I_A' = V j\omega C \left(1 - \frac{B_L}{B_C} \right)$$

* Parameters of Compensation:

• Series:

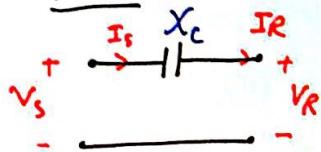

$$V_s = V_R + I_R X_C$$


$$I_s = I_R$$

$$X_C = \frac{-j}{\omega C}$$

$$\therefore \begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & X_C \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$\therefore A=D=1, B=X_C, C=0$$

• Parallel:

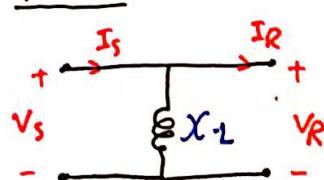

$$X_L = j\omega L$$

$$V_s = V_R$$

$$I_s = I_R + \frac{V_R}{X_L}$$

$$\therefore \begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{1}{X_L} & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$


$$\therefore A=D=1, B=0, C=\frac{1}{X_L}$$


* Application:

Compensation Could be:

1) At one of the terminals of T.L.

2) At a given Location in the line.

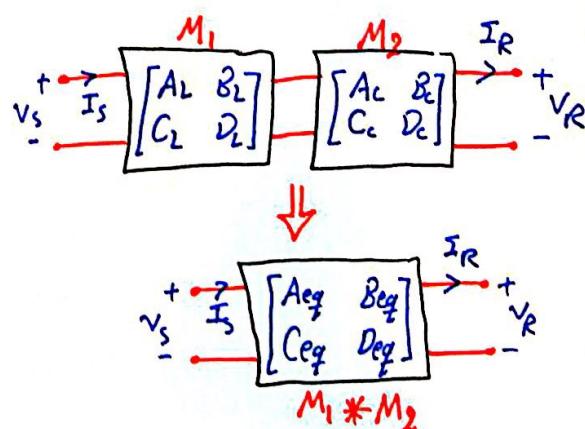

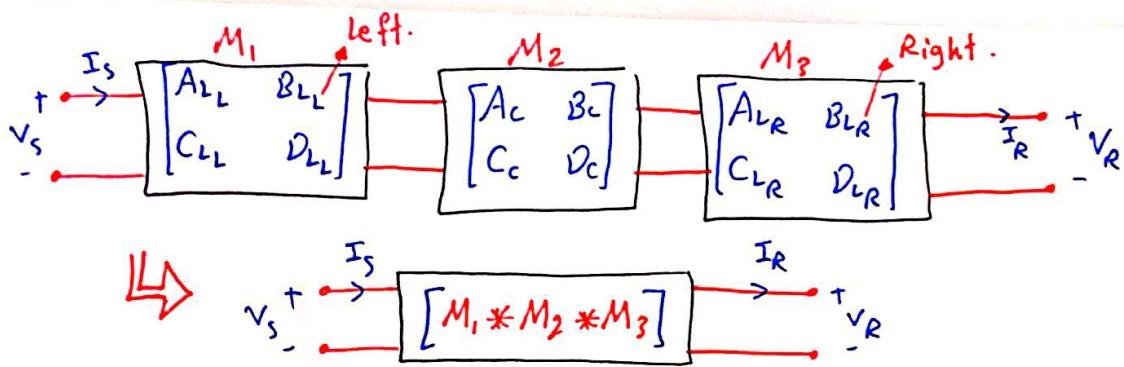

Example: A 3-ph T.L is 300 mile long and serves (supply) a load of 400MVA with 0.8 pf lagging at 345KV, if the line parameters as follows:

$$A=D=0.818 \angle 1.3^\circ, B=172.2 \angle 84.2^\circ, C=0.001933 \angle 90.4^\circ$$

1) Determine \$V_s\$ & \$I_s\$?

$$V_s = A V_R + B I_R \Rightarrow V_R = \frac{345}{13} \angle 0^\circ \text{ KV.}$$

$$I_s = C V_R + D I_R \quad I_R = \frac{400 * 10^6}{13 * 345 * 10^3} \angle \cos^{-1} 0.8$$


∴ By substitution: $I_s = 447.7 \angle 8.5^\circ \text{ A}$

$$V_s = 256.8 \angle 20.1^\circ \text{ KVolt.}$$

$$VR\% = \frac{|V_s| - |V_R|}{|V_R|} * 100\% = 57.6\%$$

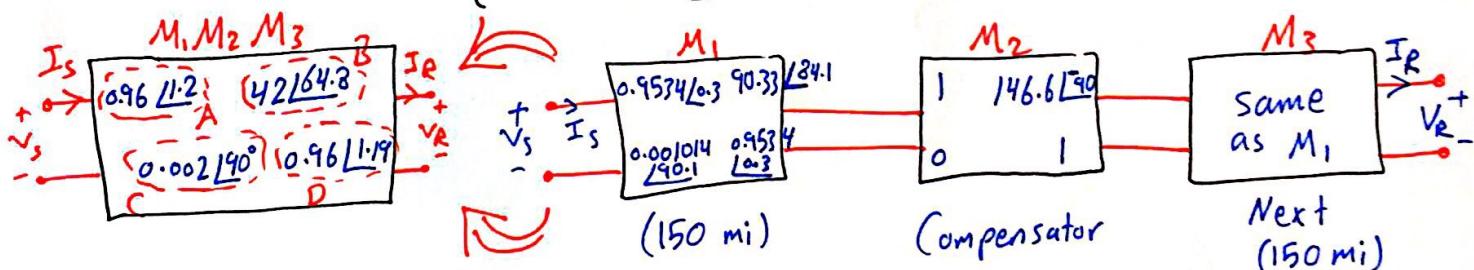2) If a series Capacitor bank have a reactance (146.6) \$\Omega\$ is installed at the mid-point of the Line & the $\begin{bmatrix} A & B \\ C & D \end{bmatrix}$ constant for each 150 mile are $A=D=0.9534 \angle 0.3^\circ, B=90.33 \angle 84.1^\circ, C=0.001014 \angle 90.1^\circ$

for the capacitor $\begin{bmatrix} 1 & 146.6 \angle -90^\circ \\ 0 & 1 \end{bmatrix}$, Find [equation] ?



$$\therefore V_s = A V_R + B I_R = (0.96 \angle 1.2^\circ * 199.2 * 10^3 \angle 0^\circ) + (42 \angle 64.8^\circ * 669.4 \angle -36.87)$$

$$\Rightarrow V_s = 216.7 \angle 4.5^\circ \text{ KVolt.}$$

$$\therefore VR\% = \frac{|V_s| - |V_R|}{|V_R|} * 100\% \Rightarrow VR\% = 13.3\%$$


*Comment:	Parameter	Before Comp.	After Comp.
	$A=D$	$0.818 \angle 1.3^\circ$	$0.96 \angle 1.2^\circ$
	B	$172.2 \angle 84.2^\circ$	$42 \angle 64.8^\circ$
	C	$0.001933 \angle 90.4^\circ$	$0.002 \angle 90.1^\circ$







Power1

Fall017

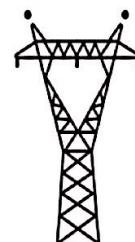

Dr. Deefallah Dalabeeh 

 By: M hmd A buhashya

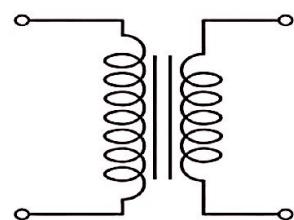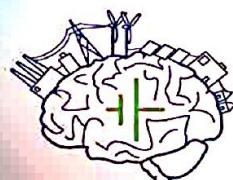

Powerunit-ju.com

→ It can be observed that the change in A, C, D is minimal.
 → However there is a major change in B (i.e. $B \downarrow$).

* Since as seen in the expression of power flow in the line $\propto \frac{1}{B}$
 ∴ Power capability of the line increases.

end of first material

* Fault Analysis:

what!!

- Definition (Fault): It is an abnormal condition which may occur on the power system such as O/C & S/C.

- In this course one is interested in S/C.

why!!

- Objective: Results of fault Analysis can be used in the setting of protection system components: PT + CT, Relays & Circuit Breaker.

How!!

S/C Faults Can be Classified into:


- Balanced or Symmetrical (3-ph fault).
 use per phase analysis. → Symmetrical Components concept is used.
- Unbalanced or Unsymmetrical could be:
 - 1) Single Line to ground Fault.
 - 2) Line to Line Fault.
 - 3) Line to Line to ground Fault.

* Balanced Fault:

To start consider a small system:



* Equivalent cct.:

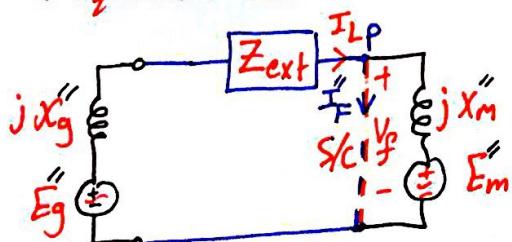

Problem: S/C occurs at the terminal of the fault.

• Objective: To find I_F .

→ a Balanced 3-ph fault occurs @ P.

V_F ≡ Pre-Fault Voltage at point P.


I_L ≡ Load Current.

Before the fault: $E_g'' = I_L(jX_g'' + Z_{ext}) + V_F \dots ①$

 $E_m'' = V_F - I_L j X_m'' \dots ②$

After the fault: $E_g'' = I_g''(jX_g'' + Z_{ext}) \dots ③$

 $E_m'' = I_m'' j X_m'' \dots ④$

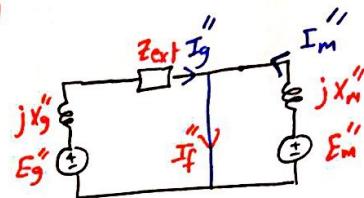

where I_g'' , I_m'' = The Contribution of the gen. & motor to fault current.

* Substitute ① into ③ & ② into ④:

$$I_L(jX_g'' + Z_{ext}) + V_F = I_g''(jX_g'' + Z_{ext}) \therefore I_g'' = I_L + \frac{V_F}{jX_g'' + Z_{ext}} \dots ⑤$$

$$V_F - I_L j X_m'' = I_m'' j X_m'' \therefore I_m'' = \frac{V_F}{jX_m''} - I_L \dots ⑥$$

* Now for I_f'' : $I_f'' = I_m'' + I_g'' \dots ⑦$

* Substitute ⑤ & ⑥ into ⑦: $I_f'' = \frac{V_F}{jX_g'' + Z_{ext}} + \frac{V_F}{jX_m''} \dots ⑧$

Hence, from ⑧ one can calculate the fault current I_f'' .


* By observing ⑧, one can represent by a Thevenin Equivalent as follows:

⑧ could be written as:

$$I_f'' = V_F \frac{jX_m'' + jX_g'' + Z_{ext}}{(jX_m'')(jX_g'' + Z_{ext})}$$

$$\Rightarrow * I_f'' = \frac{V_F}{jX_m'' // (jX_g'' + Z_{ext})} *$$

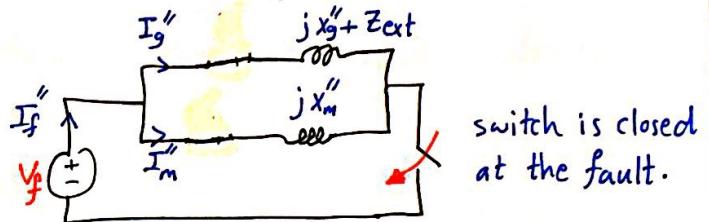• Then one can use ⑧ or ⑨
To evaluate I_f'' .



$$\begin{aligned} V_{th} &= V_F \\ Z_{th} &= (jX_m'') // (jX_g'' + Z_{ext}) \\ I_f'' &= \frac{V_{th}}{Z_{th}} \end{aligned} \dots ⑨$$

Example: A gen. is connected through a transformer to a synch. motor, for the same base values. the PU reactances are as follows: $X_g'' = j0.15$, $X_m'' = j0.35$, $Z_{ext} = j0.1$. A 3-ph fault occur at the terminals of the motor when the terminal voltage of the generator is 0.9 PU & the output current is 1 PU @ 0.8 pf leading

Find I_f'' , I_g'' & I_m'' ?

→
continue.

Solution:

This can be calculated by using Thevenin.

• method(1):

$$E_g'' = I_L j X_g'' + V_t$$

$$= (1 \angle 36.87^\circ) (0.15 \angle 90^\circ) + (0.9 \angle 0^\circ) \Rightarrow E_g'' = 0.82 \angle 8.42^\circ$$

$$E_m'' = V_t - I_L (Z_{ext} + j X_m'') = (0.9 \angle 0^\circ) - (1 \angle 36.87^\circ) (0.45 \angle 90^\circ) \Rightarrow E_m'' = 1.22 \angle -17.1^\circ$$

$$\therefore I_g'' = \frac{E_g''}{j X_g'' + Z_{ext}} \Rightarrow I_g'' = 3.28 \angle -81.58^\circ \quad I_m'' = \frac{E_m''}{j X_m''} \Rightarrow I_m'' = 3.49 \angle -107.1^\circ$$

$$\therefore I_f'' = I_g'' + I_m'' \Rightarrow I_f'' = 6.6 \angle -94.78^\circ \quad \#$$

• method(2):

using Thevenin Equivalent cct. $I_f'' = \frac{V_f}{Z_{th}}$

$$Z_{th} = (j X_g'' + Z_{ext}) \parallel (j X_m'')$$


$$V_f = V_t - I_L Z_{ext} = (0.9 \angle 0^\circ) - (1 \angle 36.87^\circ) (j 0.1) \Rightarrow V_f = 0.963 \angle -4.76^\circ$$

$$\therefore I_f'' = \frac{V_f}{Z_{th}} \Rightarrow I_f'' = 6.6 \angle -94.76^\circ$$

*By current division, it can be found:

$$I_g'' = 3.85 \angle -94.76^\circ$$

$$I_m'' = 2.75 \angle -94.76^\circ$$

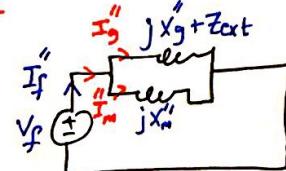

Note in method(2) I_g'' & I_m'' are different in values with method(1) due to the load current $(I_g'' + I_L)$, $(I_m'' - I_L)$

* Fault Calculation Using Z_{bus} Method:


This is used to calculate fault currents & voltages due to a balanced 3-ph fault.

• procedure: Consider the following system:

The shown voltage on the elements give subtransient reactance.

• Objective:

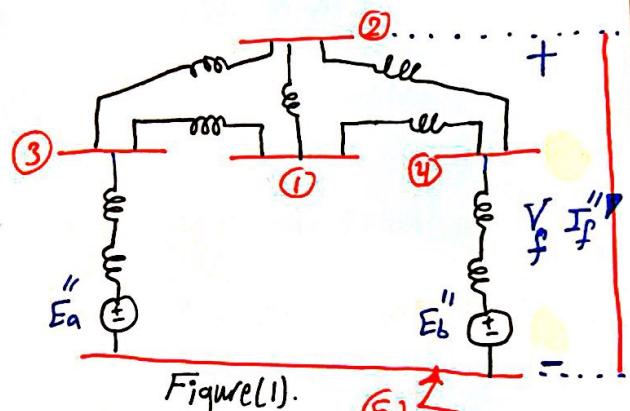if a s/c occurs between a busbar & the ref evaluate I_f'' & the voltage at the busbars.



Figure(1).

* for e.g Let a fault occur between busbar 2 & the Ref.

V_f ≡ Pre-Fault Voltage.



* I_f'' is going to flow from busbar 2 to the Ref. Then go inside the system causing voltage changes @ each busbar.


* S/C between ② & the Ref can be Simulated or represented by 2 voltage sources V_f & $-V_f$ connected in series.

* By Super Position:

Consider:

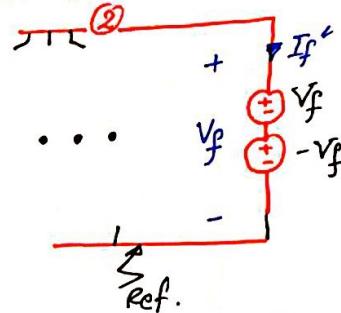i) $-V_f$ on its own. $\Rightarrow V_f, E_a'', E_b''$ together.

if V_f, E_a'', E_b'' are considered, these represent pre-fault condition, Then They DONOT contribute to I_f'' .



Hence the only source which contributes to I_f'' is $-V_f$.
(a S/C will be for E_a'', E_b'' & V_f)

* It was shown before: $[I] = [Y][V]$... ①
 $\hookrightarrow Y_{bus}$ -matrix.

$$\Rightarrow [V] = [Z][I] \dots ② \\ \hookrightarrow Z_{bus}\text{-matrix} = [Y_{bus}]^{-1}$$

* I_f'' is going to cause voltage changes at the busbars:

$$\text{Apply ② to: } \begin{bmatrix} \Delta V_1 \\ \Delta V_2 \\ \Delta V_3 \\ \Delta V_4 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & Z_{13} & Z_{14} \\ Z_{21} & \dots & \dots & Z_{24} \\ Z_{31} & \dots & \dots & Z_{34} \\ Z_{41} & \dots & \dots & Z_{44} \end{bmatrix} \begin{bmatrix} 0 \\ -I_f'' \\ 0 \\ 0 \end{bmatrix}$$

Note that $\Delta V_2 = -V_f$.
matrix 4×1 . matrix 4×4 = matrix 4×1

$$\Rightarrow \begin{bmatrix} \Delta V_1 \\ -V_f \\ \Delta V_3 \\ \Delta V_4 \end{bmatrix} = \begin{bmatrix} Z_{11} & \dots & Z_{14} \\ \vdots & \ddots & \vdots \\ Z_{41} & \dots & Z_{44} \end{bmatrix} \begin{bmatrix} 0 \\ -I_f'' \\ 0 \\ 0 \end{bmatrix} = -I_f'' \begin{bmatrix} Z_{12} \\ Z_{22} \\ Z_{32} \\ Z_{42} \end{bmatrix}$$

$$\therefore -V_f = -I_f'' Z_{22}$$

$$\Rightarrow I_f'' = \frac{V_f}{Z_{22}}$$

- V_f is Known \equiv pre-fault voltage.
- Z_{22} is an element in the Z_{bus} matrix.

\therefore In general, for a Balanced 3-ph fault at the K^{th} bus:

$$I_f'' = \frac{V_f}{Z_{KK}}$$

$$\therefore \begin{aligned} \Delta V_1 &= -I_f'' Z_{12} = -V_f \frac{Z_{12}}{Z_{22}} \\ \Delta V_2 &= -V_f \\ \Delta V_3 &= -I_f'' Z_{32} = -V_f \frac{Z_{32}}{Z_{22}} \\ \Delta V_4 &= -I_f'' Z_{42} = -V_f \frac{Z_{42}}{Z_{22}} \end{aligned} \dots ③$$

\hookrightarrow These are the voltages due to source $-V_f$.

** Reintroduce the 3-sources E_a'', E_b'' & V_f . Since they present pre-fault.

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} V_f \\ V_f \\ V_f \\ V_f \end{bmatrix} \dots ④$$



\Rightarrow Voltages at the busbars = ③ + ④

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} V'_1 \\ V'_2 \\ V'_3 \\ V'_4 \end{bmatrix} + \begin{bmatrix} \Delta V_1 \\ \Delta V_2 \\ \Delta V_3 \\ \Delta V_4 \end{bmatrix} = \begin{bmatrix} V_f \\ V_f \\ V_f \\ V_f \end{bmatrix} + \begin{bmatrix} \Delta V_1 \\ -V_f \\ \Delta V_3 \\ \Delta V_4 \end{bmatrix} = \begin{bmatrix} V'_1 + \Delta V_1 \\ 0 \\ V'_3 + \Delta V_3 \\ V'_4 + \Delta V_4 \end{bmatrix}$$

29

ΔV ≡ Voltage at the busbar due to I_f'' .

* Fault Calculations Using Zbus Egu. cct.:


The previous results can be used to deduce the equ. cct. between any 2 buses of interest by using the elements of the Z-bus Matrix as follows:

• Before the fault: switch S is open

$V_K = V_j = V_f$ (i.e pre-fault voltage)

At the fault switch S is closed

Then I_f'' is going to flow.

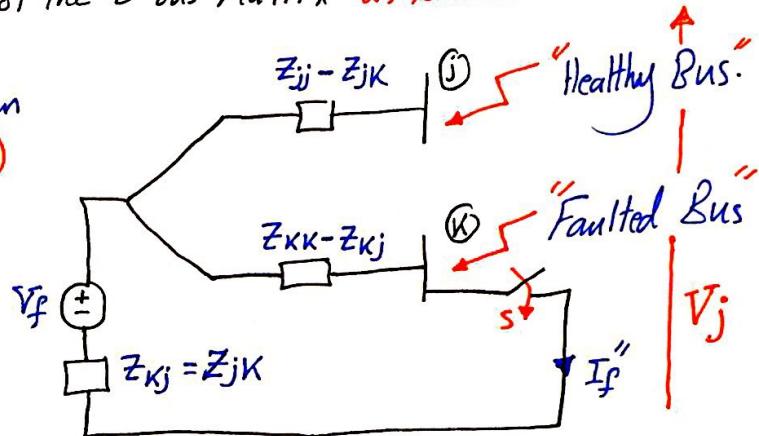

* Apply KVL to Lower Loop:

$$I_f'' Z_{Kj} - V_f + I_f'' (Z_{KK} - Z_{Kj}) = 0$$

$$\therefore V_f = I_f'' Z_{KK} \Rightarrow I_f'' = \frac{V_f}{Z_{KK}}$$

* Apply KVL to upper loop: $-V_j + V_f - I_f'' Z_{Kj} = 0 \Rightarrow V_j = V_f - I_f'' Z_{Kj}$

Example: The Zbus Matrix of a 4-bus system is as follows: (in PV)

$Z_{bus} = j \begin{bmatrix} 0.15 & 0.08 & 0.04 & 0.07 \\ 0.08 & 0.15 & 0.06 & 0.09 \\ 0.04 & 0.06 & 0.13 & 0.05 \\ 0.07 & 0.09 & 0.05 & 0.12 \end{bmatrix}$ having generators @ buses ① & ② and their subtransient reactance are included in the Zbus.

Find i) I_f'' for a 3-ph fault on bus ④?

ii) the current from gen. 2 whose $X'' = j0.2$?

Solution: Solve the problem by using 1) The equations 2) Equ. cct.


$$I_f'' = \frac{V_f}{Z_{44}} = \frac{1 \times 0}{j0.12} = 8.33 \angle -90^\circ \text{ PV}, \quad V_2 = V_f - I_f'' Z_{24} = (1 \times 0) - (8.33 \angle -90^\circ)(j0.09)$$

$$V_2 = 0.251 \angle 0^\circ \text{ PV}$$

$\overline{\text{Eg}_2} \text{ } \overset{\text{G}}{\textcircled{2}} \text{ } j0.2$

$$I_{g_2} = \frac{Eg_2 - V_2}{j0.2} = 3.745 \angle -90^\circ \text{ PV}$$

→ Continue

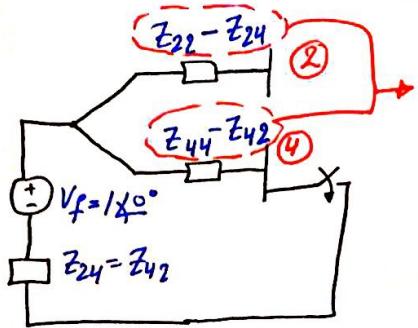

elements obtained from Z_{bus} Matrix.

30

* Comment: Calculating fault current within the system.

Having calculated the voltages at the busbars, then the current flow in any Branch, say between buses $i \& j$ can be found by:

$$I_{ij} = \frac{V_i - V_j}{Z_{ij}}$$

Impedance of the Branch between $i \& j$

* Be careful: it doesn't
be found from Z_{bus} matrix.
(found from Y_{bus} matrix).

Evaluate I_{34} :

$$I_{34} = \frac{V_3 - V_4}{\text{impedance between } 3 \& 4 \text{ branch.}}$$

Balanced 3-ph Fault on T.L:

Transmission Lines are exposed to 3-ph faults more than that on Busbars at substations.



* for the condition where one breaker open & the other fails to open; under this condition, fault current persist.

- Objective: To Evaluate I_f'' Under this Condition.

- Procedure: Introduce a busbar at point P, say Kth bus, and Re-calculate Z_{bus} matrix.

* Here the concept of Z_{th} can be used.

- i) Z_{th} between a bus & the Ref. OR ii) Z_{th} between any 2 buses.

$$Z_{th} = Z_{KK}$$


$\Leftrightarrow Z_{th}$ between Kth bus & the Ref.

$$Z_{th,ij} = Z_{jj} + Z_{ii} - 2Z_{ij}$$

All found from Z_{bus} Matrix.

Z_b = Impedance of the line.

* Eqn. cct will be as follows:

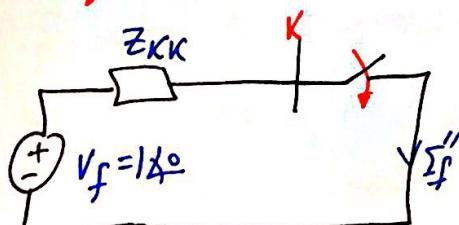

$$I_f'' = \frac{V_f}{Z_{KK}}, \text{ where: } Z_{KK} = Z_{11} + Z_b - \frac{(Z_{11} - Z_{21})^2}{Z_{th,12} - Z_b} \dots (1)$$

$$\Rightarrow Z_{th,12} = Z_{11} + Z_{22} - 2Z_{12} \dots (2)$$

where the elements on the RHS (right hand side) of (1) & (2) can be found from $[Z_{bus}]$ matrix.

* Illustration: By using Z_{th} of the previous example, it can be found:

[31]

$$Z_{th} \text{ for Bus 3} = Z_{33} = j0.13$$

$$Z_{th} \text{ between Buses 2 & 4} = Z_{th,24} = Z_{22} + Z_{44} - 2Z_{24} = j(0.15 + 0.12 - 2 * 0.09)$$

$$= j0.09$$

* Introduction to C.B Selection:

If an industrial consumer or a consumer to be connected to a Network
Then the power distribution Company supply the consumer with $SC MVA$
@ the terminal of connection.

$$SC MVA \equiv \sqrt{3} * |Nominal\ voltage, KV| * |I_{SC}| * 10^3 \dots ①$$


I_{SC} \equiv It is the RMS current in Ampers due to a Balanced 3-ph fault
@ the point of the connection.

* If the Base MVA, $MVA_B = \sqrt{3} * |Base\ voltage, KV| * |I_b| * 10^3 \dots ②$

* If the Base voltage = Nominal Voltage.

$$\Rightarrow \text{Divide } ① \text{ by } ② : SC MVA(PU) = I_{SC}(PU) \dots ③$$

* The Equ. cct @ s/c :

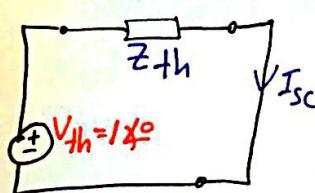

$$\therefore I_{SC} = \frac{1}{Z_{th}} \rightarrow SC MVA(PU) = \frac{1}{Z_{th}}$$

$$\therefore Z_{th} = \frac{1}{SC MVA(PU)}$$

* Among the other Rating of C.B to be selected:

1) The Maximum Instantaneous Current which the C.B must withstand.

* In our Calculations, we have neglected DC component, Then:
of I_f .

$$\text{Total Instantaneous Current} = I_f * \text{factor}$$

* This Factor > 1 & depend on the Nominal voltage & Type of C.B.

* For Example: for 5KV oil C.B \Rightarrow factor = 1.6

2) Current to be interrupted by C.B

3) The Maximum Continuous Current.

↳ This is Related to the Load.





4) Interrupting, MVA or KVA & this is Defined as:

Interrupting KVA = $\sqrt{3} * (KV \text{ of the bus to which the Breaker is connected}) * \left(\begin{array}{l} \text{The current which} \\ \text{Breaker is Capable} \\ \text{to interrupt} \end{array} \right)$

⇒ This interrupting KVA depends on the speed of the breaker.
(i.e. interrupting time), usually measure in cycles (e.g. 2, 4, 6, ... cycles). [32]

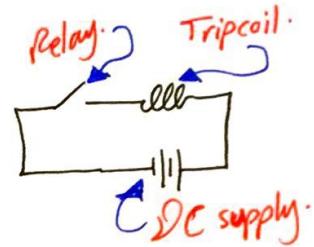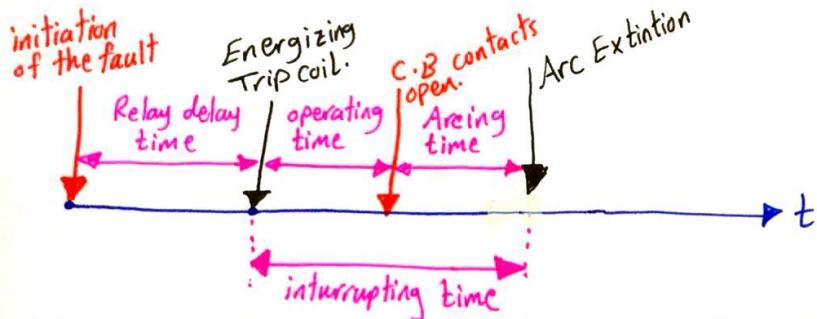* for 50 Hz system $\Rightarrow T = \frac{1}{50} = 20 \text{ msec.}$



- Note: interrupting time = operating time + Arcing time.
- Note: Arc is interrupted by: 1) oil 2) air 3) SF₆ gas 4) vacuum

⑤ Voltage Range Factor (K). $\Rightarrow K = \frac{\text{Max. operating voltage}}{\text{Lower limit of operating voltage.}}$

Example: A C.B having: Nominal Rating of 34.5 KV, Continuous Current of 1500 A., K = 1.65. Rated Max. voltage 38 KV, Rated s/c current 22 KA @ Rated Max voltage.

① Find the lower limit for operating voltage $V_{\min} = 38 / 1.65 = 23.03 \text{ KV.}$

$K = \frac{\text{Max. Voltage}}{\text{Min Voltage}}$ → this is the voltage below which the breaker Tripcoil doesn't work.

K determining the range over which the product (Rated s/c * operating voltage) = constant.


② Find Rated s/c current @ 23.03 KV? $I_{sc} = \frac{38 * 22}{23.03} = 36.3 \text{ KA}$

Example 10.7 page 406:

If a fault occurs @ point P.



Find:

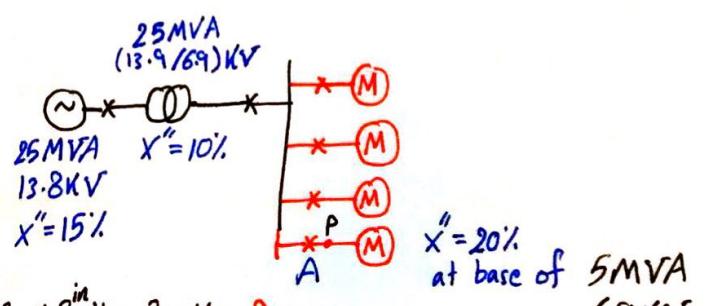- ① The subtransient fault current, I_f'' ?
 - ② Subtransient Current in Breaker A? S.S.
 - ③ The symmetrical s/c interrupting current in the fault & the breaker?
- * Subtransient = immediately after the fault.



Solution: By using Base value of 25000 kVA & 13.8 KV, Then Reactance Diagram will be as follows:

33

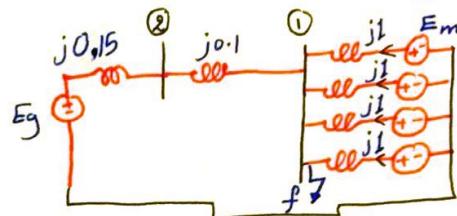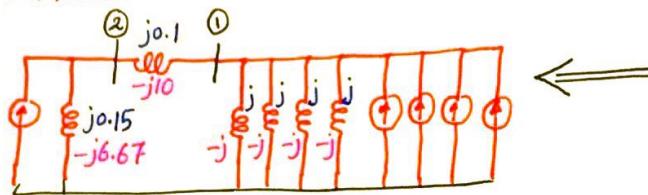

Blue is a Reactance.
Pink is an Admittance.

$$[Y] = \begin{bmatrix} -j14 & j10 \\ j10 & -j16.67 \end{bmatrix} \Rightarrow [Z] = [Y]^{-1} = \begin{bmatrix} j0.125 & j0.075 \\ j0.075 & j0.105 \end{bmatrix}$$

① $I_f'' = \frac{V_f}{Z_{11}} = \frac{1X_0}{j0.125} = -j8$. ② To find Contribution of Gen. & Motor: $V_2 = V_f - \frac{Z_{21}}{Z_{11}} V_f$

$$\Rightarrow V_2 = 1X_0 - \frac{j0.075}{j0.125} 1X_0 \Rightarrow V_2 = 0.4$$


* all in PU *

* Contribution of gen: $= \frac{V_2 - V_1}{j0.1}$ $\rightarrow V_1 = 0$ since at V_1 the fault occurred. $= \frac{0.4 - 0}{j0.1} = -j4$

* Remaining is supplied by the 4 Motors: $= -j8 - (-j4) = -j4$

\Rightarrow so Each Motor Contributes by: $\frac{-j4}{4} = -j$

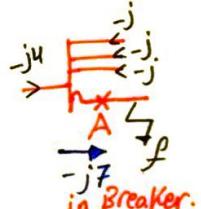\therefore The Current Passing through the Breaker $= -j4 + (3 \times -j) = -j7$



③ Objective: is to select a C.B specification for a Breaker A.

• Among the Methods to do this is the so called E/X method.

\Rightarrow Here Keep the same X'' for the Gen., However for the Motor use X' which is equal to 1.5 X_m''.

\therefore In this Case in the Reactance Diagram $X_m' = 1.5 * j1 = j1.5$

* Re-Calculate [Y] \rightarrow then [Z].

• It can be found: $Z_{11} = j0.15$

$$I_f'' = -j6.67 \text{ PU}, I_b = \frac{25000}{\sqrt{3} * 6.9} = 2090 \text{ A} \quad \therefore I_f'' = 13940 \text{ A}$$

According to the E/X Method, The specification can be specified as follows:

1) Select a C.B in such away that the voltage of the system falls within its operating range.

2) The Calculated Current ≤ 0.8 of the rated s/c current of the Breaker being selected.

* In this e.g.: A 14.4 KV C.B rated @ max voltage of 15.5 KV & K=2.67.

Also @ 15.5 KV rated s/c interrupting current = 8900 A [from DATA sheet]

continue

\Rightarrow * Lower voltage @ this selected C.B = $\frac{15.5}{2.67} = \underline{\underline{5.8}} \text{ KV}$.

\therefore operating Range of the selected C.B ($5.8 \rightarrow 15.5$) KV

Since the voltage of the system is 6.9 KV \therefore the first condition satisfied.

\therefore The S/C interrupting current of 6.9 KV is: $I_{sc} * 6.9 = 15.5 * 8900$

$$\Rightarrow I_{sc} = 19992.7 \Rightarrow I_{sc} \approx 20000 \text{ A} \quad \& \quad I_{\text{calculated}} = 13940 \text{ A.}$$

since $13940 < 0.8 * 20000 \therefore$ Selected C.B satisfy the second condition.

* Unbalanced (Unsymmetrical) Faults:

To analyze such faults, The Mathematical Concept of symmetrical Components used.

* Symmetrical Components: Here any Unbalanced voltage or current can be expressed as the sum of 3 components, the so called Zero seq. \rightarrow +ve seq. & -ve seq.

\Rightarrow where these sequences are represented by superscript of (0), (1), (2) respectively.

* Consider Unbalanced 3-ph voltages, Then: $V_{an} = V_{an}^{(0)} + V_{an}^{(1)} + V_{an}^{(2)}$

$$V_{bn} = V_{bn}^{(0)} + V_{bn}^{(1)} + V_{bn}^{(2)} \quad , \quad V_{cn} = V_{cn}^{(0)} + V_{cn}^{(1)} + V_{cn}^{(2)}$$

"Zero Seq."

$$\begin{array}{c} \rightarrow V_{an}^{(0)} \\ \rightarrow V_{bn}^{(0)} \\ \rightarrow V_{cn}^{(0)} \end{array}$$

"+ve Seq."

$$\begin{array}{c} V_{cn}^{(1)} \\ \searrow \\ V_{an}^{(1)} \\ \nearrow \\ V_{bn}^{(1)} \end{array}$$

"-ve Seq."

$$\begin{array}{c} V_{bn}^{(2)} \\ \searrow \\ V_{an}^{(2)} \\ \nearrow \\ V_{cn}^{(2)} \end{array}$$

* In this Concept, The Complex Operator (a) is introduced & defined as: $a = 1 \times \underline{120^\circ}$

\Rightarrow This is introduced to simplify the process of Calculations as follows:

• V_{bn} & V_{cn} will be expressed in terms of the symmetrical components of phase a.

$$V_{an} = V_{an}^{(0)} + V_{an}^{(1)} + V_{an}^{(2)}$$

$$V_{bn} = V_{an}^{(0)} + a^2 V_{an}^{(1)} + a V_{an}^{(2)}$$

$$V_{cn} = V_{an}^{(0)} + a V_{an}^{(1)} + a^2 V_{an}^{(2)}$$

$$\Rightarrow \begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_{an}^{(0)} \\ V_{an}^{(1)} \\ V_{an}^{(2)} \end{bmatrix}$$

$$\left\{ \begin{array}{l} a = 1 \times \underline{120^\circ} \\ a^2 = 1 \times \underline{240^\circ} \\ a^3 = 1 \times \underline{360^\circ} \end{array} \right.$$

$$\begin{bmatrix} V_{abc} \end{bmatrix} = [A] \begin{bmatrix} V_{012} \end{bmatrix}$$

$$\therefore [V_{012}] = [A]^{-1} [V_{abc}]$$

$$* \text{ It can be shown that: } [A^{-1}] = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} * \frac{1}{3}$$

*Note: The sum definition can be applied to line voltages as follows:

[35]

$$\begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_{ab}^{(0)} \\ V_{ab}^{(1)} \\ V_{ab}^{(2)} \end{bmatrix} \Rightarrow \therefore \begin{bmatrix} V_{ab}^{(0)} \\ V_{ab}^{(1)} \\ V_{ab}^{(2)} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix}$$

$\therefore V_{ab}^{(0)} = (V_{ab} + V_{bc} + V_{ca}) * \frac{1}{3} = \text{Zero by KVL applied to double subscript notation.}$

\therefore in line voltages there is **NO** zero-sequence component.

** Same Definitions apply to currents: $\begin{bmatrix} I_{an} \\ I_{bn} \\ I_{cn} \end{bmatrix} = [A] \begin{bmatrix} I_{an}^{(0)} \\ I_{an}^{(1)} \\ I_{an}^{(2)} \end{bmatrix}$

• Process :

- 1) for each element find $Z^{(0)}, Z^{(1)}, Z^{(2)}$.
- 2) Find the 3-seg. Networks.
- 3) The connection between Networks depend on the type of fault.


Example: When a gen. has terminal a o/c & other 2 terminals suffered s/c to ground the symm. component of phase a, where $I_a^{(1)} = 600 \angle -90^\circ$, $I_a^{(2)} = 250 \angle 90^\circ$ and $I_a^{(0)} = 350 \angle 90^\circ$ A. Find the current between each phase & current to ground?

Solution: $\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix} = \begin{bmatrix} I_a^{(0)} = 350 \angle 90^\circ \\ I_a^{(1)} = 600 \angle -90^\circ \\ I_a^{(2)} = 250 \angle 90^\circ \end{bmatrix}$

Knowing $a = 1 \angle 120^\circ$, $a^2 = 1 \angle 240^\circ$ By multiplication it can be found that:
 $I_a = 0$, $I_b = 904.16 \angle 144.5^\circ$, $I_c = 904.16 \angle 35.5^\circ$

$$\therefore I_f = I_b + I_c$$

$$I_f = 1050.1 \angle 90^\circ$$

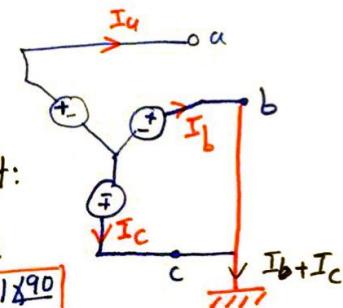


* Symmetrical Components of Δ & Y Loads:

Objective: for a symm. load, and by using the concept of symm. components, find the relationships between: ① Line current & phase current for Δ-load. ② Line voltage & phase voltage for Y-load.

• Δ-load:

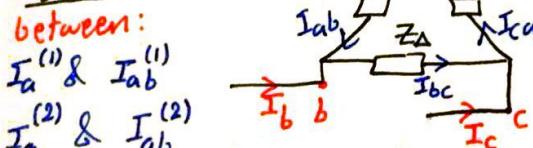objective: find relation between: $I_a^{(1)}$ & $I_{ab}^{(1)}$, $I_a^{(2)}$ & $I_{ab}^{(2)}$



Procedure: By KCL:

$$I_a = I_{ab} - I_{ca} \quad \dots \textcircled{1}$$

$$I_b = I_{bc} - I_{ab} \quad \dots \textcircled{2}$$

$$I_c = I_{ca} - I_{bc} \quad \dots \textcircled{3}$$

⇒ Express ① by using symm. components:

$$(I_a^{(0)} + I_a^{(1)} + I_a^{(2)}) = (I_{ab}^{(0)} + I_{ab}^{(1)} + I_{ab}^{(2)}) - (I_{ca}^{(0)} + I_{ca}^{(1)} + I_{ca}^{(2)}) \quad \dots \textcircled{4}$$

$$\text{since } [I_{abc}] = [A]^{-1} [I_{abc}] \quad \dots \textcircled{5}$$

$$\text{Then using } \textcircled{5} \text{ it can be found: } I_a^{(0)} = \frac{1}{3}(I_a + I_b + I_c) \quad \dots \textcircled{6}$$

$$\text{By substituting } \textcircled{1}, \textcircled{2} \text{ & } \textcircled{3} \text{ into } \textcircled{6}: \boxed{I_a^{(0)} = 0}.$$

$$\therefore \textcircled{4}: I_a^{(1)} + I_a^{(2)} = (\underbrace{I_{ab}^{(0)} - I_{ca}^{(0)}}_{= \text{Zero}}) + (I_{ab}^{(1)} - I_{ca}^{(1)}) + (I_{ab}^{(2)} - I_{ca}^{(2)})$$

$$= \text{Zero} \rightarrow \text{since } I_{ab}^{(0)} = I_{bc}^{(0)} = I_{ca}^{(0)}$$

$$\therefore I_a^{(1)} + I_a^{(2)} = (I_{ab}^{(1)} - I_{ca}^{(1)}) + (I_{ab}^{(2)} - I_{ca}^{(2)}) \quad \dots \textcircled{7}$$



(7) $I_a^{(1)} + I_a^{(2)} = (I_{ab}^{(1)} - a I_{ab}^{(1)}) + (I_{ab}^{(2)} - a^2 I_{ab}^{(2)}) = I_{ab}^{(1)}(1-a) + I_{ab}^{(2)}(1-a^2) \dots (8)$

* By similar approach, it can be found: $I_b^{(1)} + I_b^{(2)} = I_{bc}^{(1)}(1-a) + I_{bc}^{(2)}(1-a^2) \dots (9)$


$\Rightarrow I_b^{(1)} + I_b^{(2)} = a^2 I_a^{(1)} + a I_a^{(2)} = I_{bc}^{(1)}(1-a) + I_{bc}^{(2)}(1-a^2) = a^2 I_{ab}^{(1)}(1-a) + a I_{ab}^{(2)}(1-a^2)$

$\Rightarrow a^2 I_a^{(1)} + a I_a^{(2)} = a^2 I_{ab}^{(1)}(1-a) + a I_{ab}^{(2)}(1-a^2) \dots (10)$

\Rightarrow Solving (8) & (10) To find $I_a^{(1)}$ & $I_a^{(2)}$: $I_a^{(1)} = \sqrt{3} \times -30^\circ I_{ab}^{(1)}$
 $I_a^{(2)} = \sqrt{3} \times +30^\circ I_{ab}^{(2)}$ ***

• Y-load:

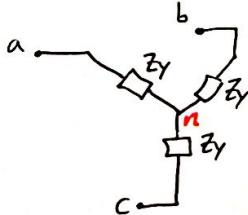- Objective: find relation between: $V_{ab}^{(1)}$ & V_{an} , $V_{ab}^{(2)}$ & V_{an}



- Procedure: by KVL or Double subscription Notation:

$$V_{ab} = V_{an} + V_{nb} = V_{an} - V_{bn} \dots (1)$$

$$V_{bc} = V_{bn} + V_{nc} = V_{bn} - V_{cn} \dots (2)$$

$$V_{ca} = V_{cn} + V_{na} = V_{cn} - V_{an} \dots (3)$$

Express (1) in terms of P symm. components:

$$(V_{ab}^{(1)} + V_{ab}^{(1)} + V_{ab}^{(2)}) = (V_{an}^{(1)} + V_{an}^{(1)} + V_{an}^{(2)}) - (V_{bn}^{(1)} + V_{bn}^{(1)} + V_{bn}^{(2)})$$

* By using $[V_{012}] = [A]^{-1} [V_{abc}] \dots (4)$

$$V_{ab}^{(0)} = \frac{1}{3} (V_{ab} + V_{bc} + V_{ca}) \dots (6)$$

* Sub. (1), (2), (3) into (6) $\Rightarrow V_{ab}^{(0)} = 0$

$\therefore (4): V_{ab}^{(1)} + V_{ab}^{(2)} = (V_{an}^{(1)} - V_{bn}^{(0)}) + (V_{an}^{(1)} - V_{bn}^{(1)}) + (V_{an}^{(2)} - V_{bn}^{(2)})$
 $\downarrow = 0$ since $V_{an}^{(0)} = V_{bn}^{(0)} = V_{cn}^{(0)}$


$$\Rightarrow V_{ab}^{(1)} + V_{ab}^{(2)} = (V_{an}^{(1)} - a^2 V_{an}^{(1)}) + (V_{an}^{(2)} - a V_{an}^{(2)}) = V_{an}^{(1)}(1-a^2) + V_{an}^{(2)}(1-a)$$

* Similarly: $V_{bc}^{(1)} + V_{bc}^{(2)} = V_{bn}^{(1)}(1-a^2) + V_{bn}^{(2)}(1-a)$

It can be shown: $V_{ab}^{(1)} = \sqrt{3} \times -30^\circ V_{an}^{(1)}$

$$V_{ab}^{(2)} = \sqrt{3} \times +30^\circ V_{an}^{(2)}$$

*Relationship between Z_Δ & Z_y :

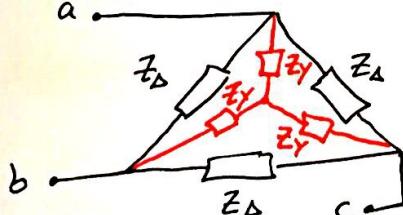

$$\Rightarrow Z_\Delta = \frac{V_{AB}^{(1)}}{I_{AB}^{(1)}} = \frac{\sqrt{3} \times -30^\circ V_{AN}^{(1)}}{\frac{I_{AN}^{(1)}}{\sqrt{3}}} = \frac{3 V_{AN}^{(1)}}{I_{AN}^{(1)}} = 3 Z_y$$

$$Z_\Delta = 3 Z_y$$

OR you can use $Z_\Delta = \frac{V_{AB}^{(2)}}{I_{AB}^{(2)}}$
To do the same proof.

*Power in terms of symmetrical components:

- Objective: if symmetrical components are known then one can calculate power as follows:

$$S = V_{an} I_{an}^* + V_{bn} I_{bn}^* + V_{cn} I_{cn}^* = [V_{an} \ V_{bn} \ V_{cn}] \begin{bmatrix} I_{an} \\ I_{bn} \\ I_{cn} \end{bmatrix}^* = [V_{an} \ V_{bn} \ V_{cn}]^T \begin{bmatrix} I_{an} \\ I_{bn} \\ I_{cn} \end{bmatrix}^*$$

$$= [A] [V_{012}] \cdot [A] [I_{012}]^* \Rightarrow S = [V_{012}]^T [A]^T [A]^* [I_{012}]^* \dots (1)$$

where: $[V_{012}] = \begin{bmatrix} V^{(0)} \\ V^{(1)} \\ V^{(2)} \end{bmatrix}$, $[I_{012}] = \begin{bmatrix} I^{(0)} \\ I^{(1)} \\ I^{(2)} \end{bmatrix}$

37


$$A = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \Rightarrow [A]^T = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}, [A]^* = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix}$$

remember:

$$a^2 = 1 \times 240$$

$$(a^2)^* = 1 \times -240 = 1 \times 120^\circ = a$$

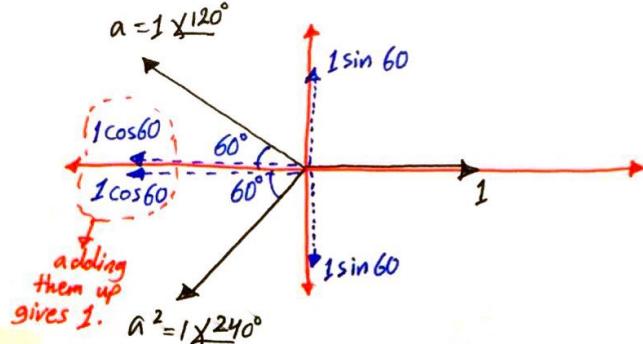Knowing: $1 + a + a^2 = 0$
(you can see that in)
phasor diagram.



$$\therefore [A]^T [A]^* = \begin{bmatrix} 3 & 0 & 0 \\ 0 & 3 & 0 \\ 0 & 0 & 3 \end{bmatrix} = 3 \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \dots \textcircled{2}$$

Substitute $\textcircled{2}$ in $\textcircled{1}$:

$$[V^{(0)} \ V^{(1)} \ V^{(2)}] \cdot 3 \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} I^{(0)*} \\ I^{(1)*} \\ I^{(2)*} \end{bmatrix} = 3 V^{(0)} I^{(0)*} + 3 V^{(1)} I^{(1)*} + 3 V^{(2)} I^{(2)*} \dots \textcircled{3}$$

(in VA)

* if $S_b = 3 S_{1\phi} \dots \textcircled{4}$, Then divide $\textcircled{3}$ by $\textcircled{4}$: $\frac{S}{3 S_{1\phi}} = \frac{V^{(0)} I^{(0)*}}{S_{1\phi}} + \frac{V^{(1)} I^{(1)*}}{S_{1\phi}} + \frac{V^{(2)} I^{(2)*}}{S_{1\phi}}$ (PV)
 \Rightarrow Hence, in PV factor (3) in equation $\textcircled{3}$ disappears.

Example: A Balance Y-resistive Load of 10Ω have the following terminal voltages:


$$V_{ab} = 100 \times 0^\circ \text{ V}, V_{bc} = 80.8 \times -121.44^\circ \text{, and } V_{ca} = 90 \times 130^\circ \text{ V.}$$

Assuming there is NO connection to Neutral Find:

1) The Line Current from the sym. comp. of Line voltages ?

2) The Complex Power supplied by using sym. comp. of voltages & currents ?

Solution:

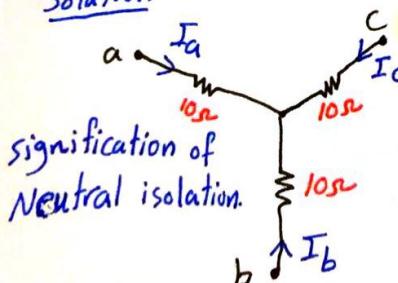

1) By KVL: $I_a + I_b + I_c = 0$, $I^{(0)} \triangleq \frac{1}{3} [I_a + I_b + I_c] = 0$

$$\therefore V_{ab}^{(1)} = \sqrt{3} \times 30^\circ V_{an}^{(1)} \quad \therefore V_{an}^{(1)} = \frac{V_{ab}^{(1)}}{\sqrt{3} \times 30^\circ}$$

$$\begin{bmatrix} V_{ab}^{(0)} \\ V_{ab}^{(1)} \\ V_{ab}^{(2)} \end{bmatrix} = [A^{-1}] \begin{bmatrix} V_{abc} \end{bmatrix} = \begin{bmatrix} 0 \\ 89.9 \times 2.9^\circ \\ 11.16 \times -2.96^\circ \end{bmatrix} \Rightarrow V_{an}^{(1)} = \frac{89.9 \times 2.9}{\sqrt{3} \times 30^\circ}$$

$$\Rightarrow V_{an}^{(1)} = 51.9 \times 27.1^\circ$$

$$\Rightarrow V_{an}^{(2)} = \frac{V_{ab}^{(2)}}{\sqrt{3} \times -30^\circ} = \frac{11.16 \times -23.96}{\sqrt{3} \times -30^\circ} \Rightarrow V_{an}^{(2)} = 6.4 \times 6.04^\circ$$

38

$$\therefore I^{(1)} = \frac{V_{an}^{(1)}}{10} \Rightarrow I^{(1)} = 5.19 \times -27.1^\circ \quad \text{and} \quad I^{(2)} = \frac{V_{an}^{(2)}}{10} \Rightarrow I^{(2)} = 0.64 \times 6.04^\circ$$

\therefore The Line Currents are: $\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = [A] \begin{bmatrix} I^{(0)} \\ I^{(1)} \\ I^{(2)} \end{bmatrix}$ By substitution:

$$I_a = 5.73 \times -23.57^\circ$$


$$I_b = 5.25 \times -14.8^\circ$$

$$I_c = 4.75 \times 87.5^\circ$$

$$2) S = 3 \left[V^{(0)*} I^{(0)*} + V^{(1)*} I^{(1)*} + V^{(2)*} I^{(2)*} \right] \Rightarrow S = 820.371 \text{ VA } \times 0^\circ \text{ since it is a resistive load.}$$

* Sequence Impedances:

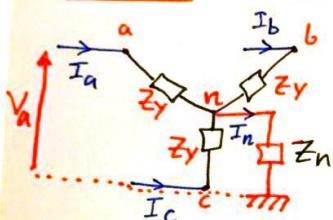- Objective: To find Zero,+ve & -ve seq. impedance of the various component in power system.
- 3-ph Load: Consider Y-connected load.



$$I_n = I_a + I_b + I_c = (I_a^{(0)} + I_a^{(1)} + I_a^{(2)}) + (I_b^{(0)} + I_b^{(1)} + I_b^{(2)}) + (I_c^{(0)} + I_c^{(1)} + I_c^{(2)})$$

$$= [I_a^{(0)} + I_b^{(0)} + I_c^{(0)}] + [I_a^{(1)} + I_b^{(1)} + I_c^{(1)}] + [I_a^{(2)} + I_b^{(2)} + I_c^{(2)}]$$

$$\Rightarrow I_n = 3 I_a^{(0)}$$

since $I_a^{(0)} = I_b^{(0)} = I_c^{(0)}$ \Rightarrow = zero (because they are balanced phasor).

* Let our reference is the ground.

* Let V_a, V_b and V_c = The terminal voltages w.r.t Ref. \therefore By KVL: $V_a = V_{an} + I_n Z_n$

$$\Rightarrow V_a = I_a Z_y + 3 I_a^{(0)} Z_n$$

$$V_b = I_b Z_y + 3 I_a^{(0)} Z_n$$

$$V_c = I_c Z_y + 3 I_a^{(0)} Z_n$$

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix} + 3 I_a^{(0)} Z_n \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix}$$

$$V_b = V_{bn} + I_n Z_n$$

$$V_c = V_{cn} + I_n Z_n$$

* By Using Symm. Components: $[A] \begin{bmatrix} V_a^{(0)} \\ V_a^{(1)} \\ V_a^{(2)} \end{bmatrix} = [A] \begin{bmatrix} V_{an}^{(0)} \\ V_{an}^{(1)} \\ V_{an}^{(2)} \end{bmatrix} + 3 I_a^{(0)} Z_n \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} \Rightarrow$ multiply by $[A]^{-1}$

$$\Rightarrow \begin{bmatrix} V_a^{(0)} \\ V_a^{(1)} \\ V_a^{(2)} \end{bmatrix} = \begin{bmatrix} V_{an}^{(0)} \\ V_{an}^{(1)} \\ V_{an}^{(2)} \end{bmatrix} + 3 I_a^{(0)} Z_n * \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} = \begin{bmatrix} V_{an}^{(0)} \\ V_{an}^{(1)} \\ V_{an}^{(2)} \end{bmatrix} + I_a^{(0)} Z_n \begin{bmatrix} 3 \\ 0 \\ 0 \end{bmatrix} \dots (1)$$

$$\Rightarrow V_a^{(0)} = V_{an}^{(0)} + 3 Z_n I_a^{(0)} = I_a^{(0)} Z_y + 3 Z_n I_a^{(0)} \dots (2)$$

$$V_a^{(1)} = V_{an}^{(1)} + 0$$

$$= I_a^{(1)} Z_y \dots (3)$$


$$V_a^{(2)} = V_{an}^{(2)} + 0$$

$$= I_a^{(2)} Z_y \dots (4)$$


Each Equation in (2), (3) & (4) is an independent equation & Related only to one sequence (i.e. 0, +ve, or -ve)

* Use These Equations To deduce the Eqn. Cct.


from (2):

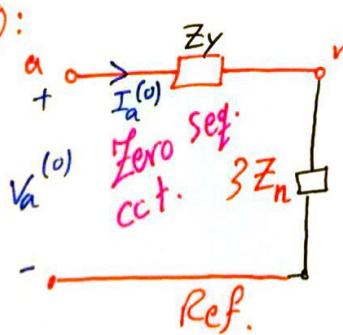


from (3):

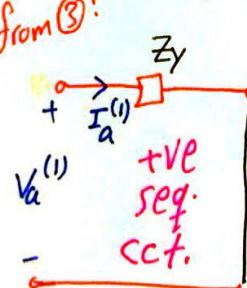

from (4):

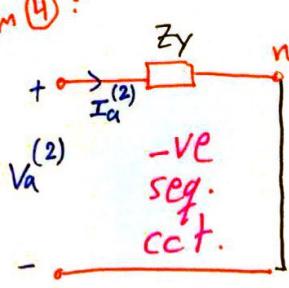

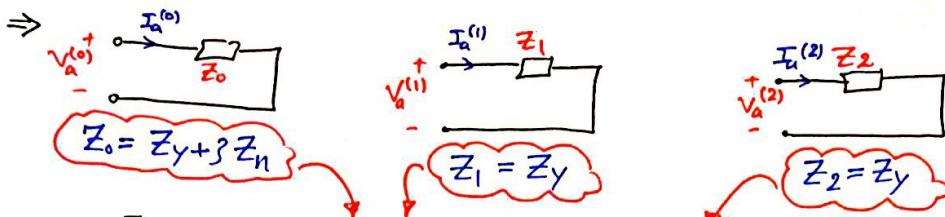

39


$$Z_1 = Z_2$$

$Z_0, Z_1, Z_2 \Rightarrow$ Called Zero +ve & -ve seq. impedance of the Y-connected Load.


** Earthing Impedance Only Effect Zero - Seg-cct.

for e.g: if n is isolated $\therefore Z_n = \infty$, if n is solidly grounded $\therefore Z_n = 0$



- 3-ph load: Consider Δ -connected load.

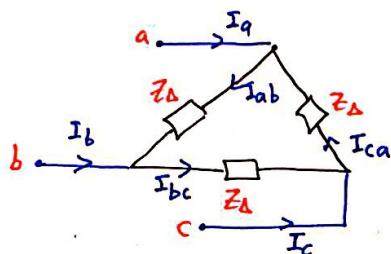

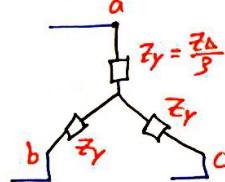* Line currents CANNOT provide a path to Neutral
 \therefore The Equ. Y-load will be:



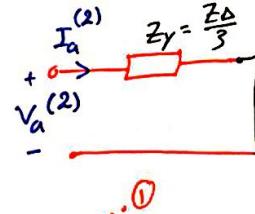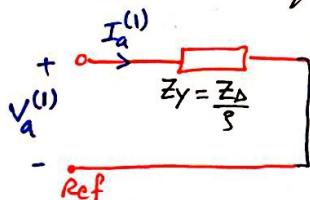* The Equ. Y-connection Can be used to find the +ve & -ve equ. cct:




* For the Zero seq.: $V_{ab} = I_{ab} Z_\Delta$; $V_{bc} = I_{bc} Z_\Delta$; $V_{ca} = I_{ca} Z_\Delta$

$$\textcircled{1} + \textcircled{2} + \textcircled{3}: V_{ab} + V_{bc} + V_{ca} = Z_\Delta (I_{ab} + I_{bc} + I_{ca}) = 0$$

$$\Rightarrow 0 = Z_\Delta (3I_{ab}^{(o)}) = 3V_{ab}^{(o)} \quad \text{as we did in the previous page for } I_a + I_b + I_c$$

$$\therefore \boxed{V_{ab}^{(o)} = 0} \quad \therefore \boxed{I_{ab}^{(o)} = 0} \quad \therefore \boxed{I_{bc}^{(o)} = I_{ca}^{(o)} = 0} \quad \Rightarrow I_a^{(o)} = I_{ab}^{(o)} - I_{ca}^{(o)} \Rightarrow \boxed{I_a^{(o)} = 0}$$


\Rightarrow The Equ. Cct.:

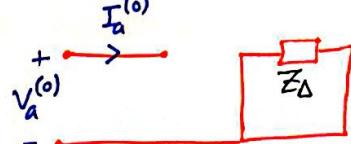

** Sequence ccts of T.L: \Rightarrow All phase conductors has the same impedance $= Z_{aa}$
 \Rightarrow Neutral has impedance $= Z_{nn}$.

* Mutual inductance between phase conductors is represented by an impedance $= Z_{ab}$

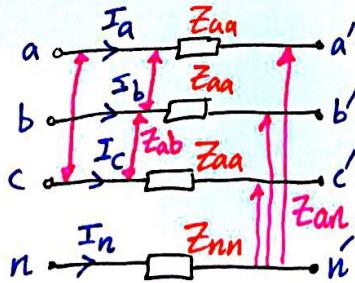* Between Neutral & Conductors is represented by $= Z_{an}$



$$Z_{aa} = R + j\omega L \rightarrow Z_{ab} = j\omega M$$

40

- *Apply KVL: $V_{an} = I_a Z_{aa} + I_b Z_{ab} + I_c Z_{ac} + I_n Z_{an} + V_{a'n'} - (I_n Z_{nn} + I_a Z_{an} + I_b Z_{an} + I_c Z_{an})$
- $\Rightarrow V_{an} - V_{a'n'} = I_n (Z_{aa} - Z_{an}) + I_b (Z_{ab} - Z_{an}) + I_c (Z_{ac} - Z_{an}) + I_n (Z_{an} - Z_{nn})$
- $\therefore V_{an} - V_{a'n'} = I_a (Z_{aa} - Z_{an}) + (Z_{ab} - Z_{an})(I_b + I_c) + I_n (Z_{an} - Z_{nn}) \dots ①$
- $\therefore \text{By KCL: } I_n = -(I_a + I_b + I_c) \dots ②$

Sub. ② into ①:



$$V_{an} - V_{a'n'} = I_a (Z_{aa} - 2Z_{an} + Z_{nn}) + (Z_{ab} - Z_{an} - Z_{an} + Z_{nn})(I_b + I_c)$$

$$\Rightarrow V_{an} - V_{a'n'} = I_a (Z_{aa} - 2Z_{an} + Z_{nn}) + I_b (Z_{ab} - 2Z_{an} + Z_{nn}) + I_c (Z_{ab} - 2Z_{an} + Z_{nn})$$

The same procedure can be repeated for V_{bn} & V_{cn} to find $(V_{bn} - V_{b'n'})$ & $(V_{cn} - V_{c'n'})$: It can be found that: $V_{an} - V_{a'n'} = I_a Z_S + I_b Z_m + I_c Z_m \dots ①$

$$V_{bn} - V_{b'n'} = I_a Z_m + I_b Z_S + I_c Z_m \dots ②$$

$$V_{cn} - V_{c'n'} = I_a Z_m + I_b Z_m + I_c Z_S \dots ③$$

Rewrite ①, ② & ③ in a matrix form:

$$\begin{bmatrix} V_{aa} \\ V_{bb} \\ V_{cc} \end{bmatrix} = \begin{bmatrix} V_{an} - V_{a'n'} \\ V_{bn} - V_{b'n'} \\ V_{cn} - V_{c'n'} \end{bmatrix} = \begin{bmatrix} Z_S & Z_m & Z_m \\ Z_m & Z_S & Z_m \\ Z_m & Z_m & Z_S \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

*Introduce Symmetrical Components:

$$[A] \begin{bmatrix} V_{aa'}^{(0)} \\ V_{aa'}^{(1)} \\ V_{aa'}^{(2)} \end{bmatrix} = \begin{bmatrix} Z_S & Z_m & Z_m \\ Z_m & Z_S & Z_m \\ Z_m & Z_m & Z_S \end{bmatrix} [A] \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix} \xrightarrow{\text{multiply By } A^{-1}}$$

$$\begin{bmatrix} V_{aa'}^{(0)} \\ V_{aa'}^{(1)} \\ V_{aa'}^{(2)} \end{bmatrix} = [A]^{-1} \begin{bmatrix} Z_S & Z_m & Z_m \\ Z_m & Z_S & Z_m \\ Z_m & Z_m & Z_S \end{bmatrix} [A] \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix}$$

By Multiplication, it can be found:

$$\begin{bmatrix} V_{aa'}^{(0)} \\ V_{aa'}^{(1)} \\ V_{aa'}^{(2)} \end{bmatrix} = \begin{bmatrix} Z_S + 2Z_m & 0 & 0 \\ 0 & Z_S - Z_m & 0 \\ 0 & 0 & Z_S - Z_m \end{bmatrix} \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix}$$


: The result is 3-independent Equations:

$$V_{aa'}^{(0)} = (Z_S + 2Z_m) I_a^{(0)} \rightarrow Z_0$$


$$V_{aa'}^{(1)} = (Z_S - Z_m) I_a^{(1)} \rightarrow Z_1$$

$$V_{aa'}^{(2)} = (Z_S - Z_m) I_a^{(2)} \rightarrow Z_2$$

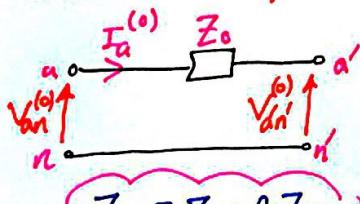
*from these Equations, They can be used To find seq. ccts of T.L:



$$Z_0 = Z_S + 2Z_m$$

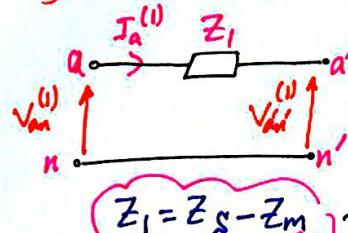

$$Z_1 = Z_S - Z_m$$

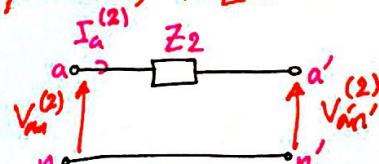

$$\therefore Z_1 = Z_2$$

where:

$$Z_S = Z_{aa} - 2Z_{an} + Z_{nn}$$

$$\Rightarrow Z_1 = Z_2 = Z_{aa} - Z_{ab}$$

: Neutral only effect Z_0 . Since it depend on Z_{nn} .

$$Z_m = Z_{ab} - 2Z_{an} + Z_{nn}$$

* Same General Procedure can be applied to find seq. ccts for 3-ph Gen. + Transformer.

[41]

* Seq. cct. of 3-ph Generator:

By following the same previous procedure it can be found that:


$Z \equiv$ Self impedance of the gen.

$M_s \equiv$ Mutual Inductance between any two phases.

$L_s \equiv$ Self inductance.


$Z_n \equiv$ Earthing Impedance.

- Zero Seq.:

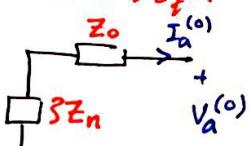


$$Z_0 = R + j\omega(L_s - 2M_s)$$

- +ve Seq.:

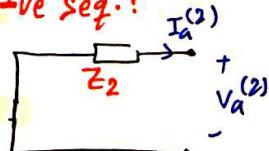


$$Z_1 = Z_2 = R + j\omega(L_s + M_s)$$

- +ve seq.:

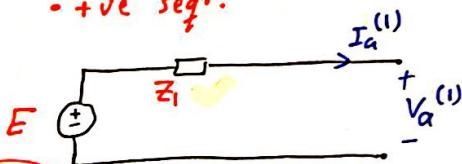

* The only active Network is the +ve seq of the Gen.

* Seq. cct. of 3-ph Transformer:

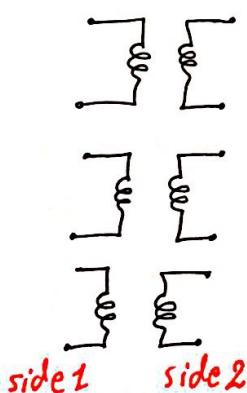


Each side can be connected as Δ or Y .

- +ve seq.:




- ve seq.:

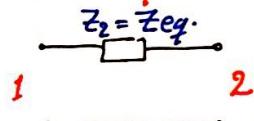

$Z_{eq} \equiv$ Equivalent Series Impedance of the Transformer.

- Zero Seq.:

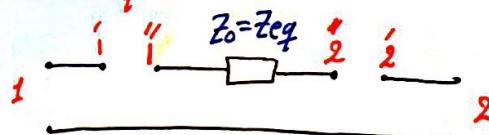

* Connection Between (1'-1'') & (2'-2'') depends on the type of connection (i.e. Δ or Y).

- For Y-type:

the connection is made by an impedance = $3Z_n$, where Z_n is the earthing impedance of Neutral.



- For Δ -type:

S/C 1'' or/and 2'' to the Ref.

* Illustration:



$$\Rightarrow Z_0 = Z_{eq}$$

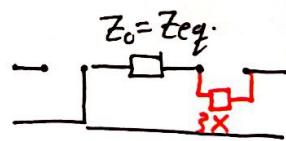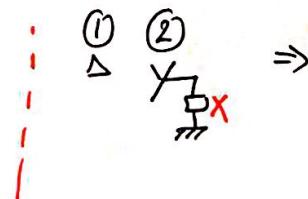


* Seq. Networks:

Having produced seq. ccts of the individual components (i.e gen., Trans., T.L & load) these ccts can be interconnected to produce :

42

+ve seq. Network , -ve seq. Network , Zero seq. Network.

Example:

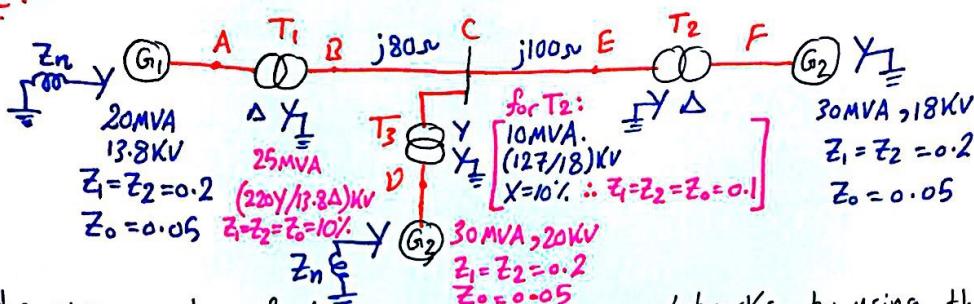

For the given system, find +ve, -ve & zero seq Networks by using the given data & using Base value of 50MVA & 13.8KV @ the gen(1) ?

Given Information:

- * The Reactance (Earthing Reactance) of G_1 & G_2 = 5%
- * The zero-seq. Reactance of T.L is 210Ω for B-C & 250Ω for C-E.

Note: All the passive elements are Pure Reactance.

for T_3 : $85 \text{ MVA}, (220y/22y) \text{ KV}, X=10\% \Rightarrow Z_1 = Z_2 = Z_0 = 0.1$


Note: 1) The given PU values of each component are based on the Ratings of the component.

2) In this e.g. Base voltage doesn't change only S_B change $\therefore Z_{\text{new}} = Z_{\text{old}} * \frac{S_{\text{new}}}{S_{\text{old}}}$

3) +ve & -ve seq. Networks are identical Except that +ve seq. has source.


Solution:

Component	$Z_1 = Z_2$	Z_0	Z_n
G_1	0.5	0.125	0.125
T_1	0.2	0.2	
L_{BC}	0.083	0.217	
L_{CE}	0.103	0.258	
T_2	0.17	0.17	
G_2	0.33	0.083	
G_3	0.28	0.0689	0.0689
T_3	0.14	0.14	

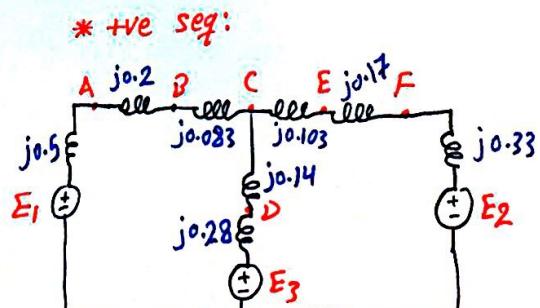

* -ve seq: Same as +ve seq with E_1, E_2, E_3 replaced by S/C .

* Zero seq:

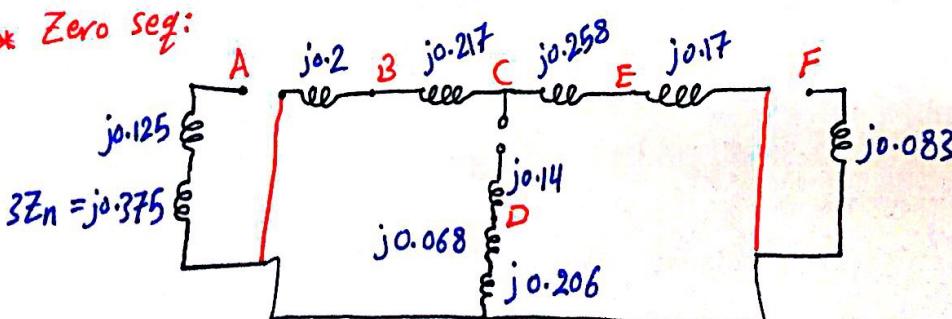

* Comments:

1) The interconnection between seq. Networks will depend on the type of the fault as will be shown later. [43]




2) In the analysis, Each Network will be represented by its Thevenin equivalent according to the location of the fault.

For example: in the given example Assume the fault is on Bus C, Then one has to find Z_{eq} seen between Bus C & Bus Ref.


∴ from the previous Zero-seq cct: $Z_o = (j0.217 + j0.2) // (j0.258 + j0.17)$

∴ The equivalent cct :

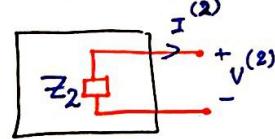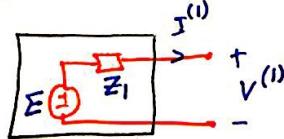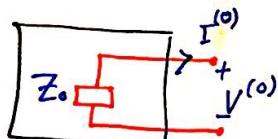* By similar procedure one finds +ve & -ve equivalents:



* Line-ground-fault:

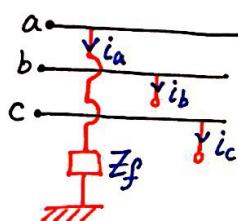

$Z_f \equiv$ fault impedance.

• General Procedure: 1) From schematic diagram, find relationship for phase currents/voltages.

2) Convert to symmetrical components.

3) Deduce the interconnection.

4) Evaluate symm. Components.

5) Evaluate corresponding phase voltages and currents under fault condition.

↳ for this cct: 1) $i_b = i_c = 0 \dots ①$

$$v_a = i_a Z_f \dots ②$$

$$2) \text{ from equation } ①: \frac{i^{(o)} + a^2 i^{(1)} + a i^{(2)}}{I_b} = \frac{i^{(o)} + a i^{(1)} + a^2 i^{(2)}}{I_c} \Rightarrow i^{(1)} (a^2 - a) = i^{(2)} (a^2 - a) \therefore i^{(1)} = i^{(2)}$$

$$\text{also from } ①: i_b = 0 = i^{(o)} + a^2 i^{(1)} + a i^{(2)} = i^{(o)} + i^{(1)} (a^2 + a) \quad \text{remember: } a + a^2 + 1 = 0 \\ \Rightarrow \therefore 0 = i^{(o)} - i^{(1)} \quad \therefore i^{(o)} = i^{(1)} = i^{(2)} \dots ③ \quad \Rightarrow a^2 + a = -1$$

$$\text{from equation } ②: v_a^{(o)} + v_a^{(1)} + v_a^{(2)} = Z_f (i_a^{(o)} + i_a^{(1)} + i_a^{(2)}) \dots ④$$

$$\text{substitute } ③ \text{ into } ④: v_a^{(o)} + v_a^{(1)} + v_a^{(2)} = Z_f * 3 i_a^{(o)} \Rightarrow v_a^{(o)} + v_a^{(1)} + v_a^{(2)} = i_a^{(o)} 3 Z_f \dots ⑤$$

3) ∴ Seq. Networks should be connected in such away to satisfy ④ & ⑤ as follows:

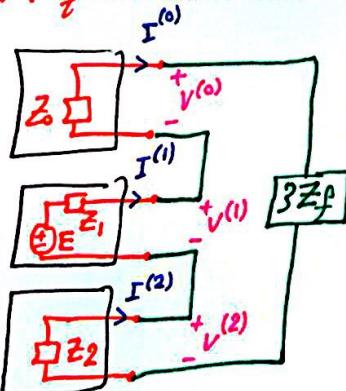


figure (1).

4) Symm. Components:

$$\therefore i^{(o)} = i^{(1)} = i^{(2)} = \frac{E}{Z_o + Z_1 + Z_2 + 3Z_f} \dots ⑥$$

$$v^{(o)} = -i^{(o)} Z_o \dots ⑦$$


$$v^{(1)} = E_1 - i^{(1)} Z_1 \dots ⑧$$

$$v^{(2)} = -i^{(2)} Z_2 \dots ⑨$$


$$5) [V_{abc}] = [A] [V_{o12}]$$

$$[I_{abc}] = [A] [I_{o12}]$$

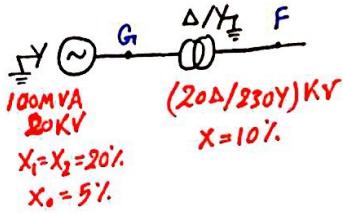Example: For the given system (i.e. gen. connected to transformer at No-load) the terminal voltage of the gen. is **20KV** when a single-line-to-ground fault occurs on the a/c HV side of the transformer (i.e. point F), Given the base values at the generator **20KV & 100MVA**, Find the phase currents @ points G & F?



Solution:

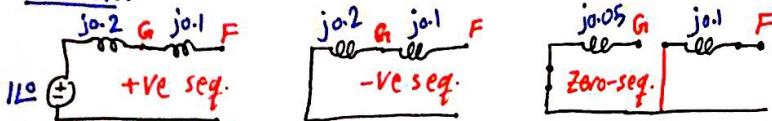

• at the fault Point:


$$I_a^{(0)} = I_a^{(1)} = I_a^{(2)} = \frac{1 \times 0}{j(0.2+0.1)+j(0.2+0.1)+j0.1} = 1.429 \angle -90^\circ$$

$$\therefore \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = [A] \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix} = \begin{bmatrix} -j4.287 \\ 0 \\ 0 \end{bmatrix}$$

$$I_a^{(1)} = 1.429 \angle -90 - 30 = 1.429 \angle -120^\circ$$

$$I_a^{(2)} = 1.429 \angle -90 + 30 = 1.429 \angle -60^\circ$$
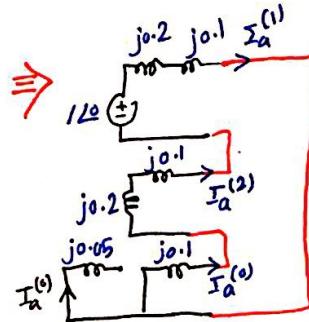
$$I_a^{(0)} = 0 \text{ (From the cct. diagram).}$$




• For the Gen:

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = [A] \begin{bmatrix} 1.429 \angle -120 \\ 1.429 \angle -60 \\ 0 \end{bmatrix} = \begin{bmatrix} 2.475 \angle -90^\circ \\ 2.475 \angle 90^\circ \\ 0 \end{bmatrix}$$

*Comment: Base Current $I_B = \frac{100 M}{\sqrt{3} * 20 K} = 2886.8 A \therefore |I_A| = |I_B| = 2.475 * 2886.8 = 7144.7 A$.

*Comment: Voltage Sag (i.e. voltage drop)

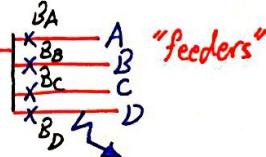for e.g: let a fault occur on feeder D, Then during the period taken for B_D to open, Then a voltage drop (i.e sag) will take place on the healthy feeders A, B & C. which may cause the interruption of sensitive equipment.



* Line-to-line Fault:

$$\begin{aligned} 1) \quad I_a = 0 & \dots ① \quad I_b = -I_c \dots ② \quad V_b = V_c + I_b Z_f \dots ③ \\ 2) \quad \text{Convert to sym. comp. :} \\ ① \Rightarrow I_a^{(0)} &= \frac{1}{3}[I_a + I_b + I_c] = \frac{1}{3}[0 + I_b - I_b] = 0 \quad \therefore I_a^{(0)} = 0 \dots ④.1 \\ ③ \Rightarrow V_b - V_c &= I_b Z_f \Rightarrow (V^{(1)} + a^2 V^{(2)} + a V^{(0)}) - (V^{(0)} + a V^{(1)} + a^2 V^{(2)}) = Z_f (I^{(0)} + a^2 I^{(1)} + a I^{(2)}) \\ &\Rightarrow V^{(1)}(a^2 - a) - V^{(2)}(a^2 - a) = Z_f (a^2 I^{(1)} + a I^{(2)}) \dots ④.2 \end{aligned}$$

$$② \Rightarrow I_b = -I_c \Rightarrow I^{(0)} + a^2 I^{(1)} + a I^{(2)} = -(I^{(0)} + a I^{(1)} + a^2 I^{(2)}) \Rightarrow I^{(1)}(a^2 + a) = I^{(2)}(-a^2 - a) \Rightarrow I^{(1)} = -I^{(2)} \dots ⑤$$

$$V^{(1)}(a^2 - a) - V^{(2)}(a^2 - a) = Z_f (a^2 I^{(1)} - a I^{(2)}) = Z_f I^{(1)}(a^2 - a) \quad \therefore V^{(1)} - V^{(2)} = Z_f I^{(1)} \dots ⑥ \quad ⑤$$

3) interconnection should be made in such away to satisfy ③, ⑤ & ⑥:

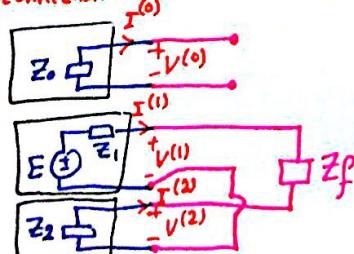


Fig.(1)


$$4) \text{ from Fig.(1): } I^{(0)} = V^{(0)} = 0, \quad I^{(1)} = -I^{(2)} = \frac{E}{Z_1 + Z_2 + Z_f}$$

$$V^{(1)} = E - I^{(1)} Z_1$$

$$V^{(2)} = -I^{(2)} Z_2$$

$$5) \therefore [V_{abc}] = [A] [V_{012}], \quad [I_{abc}] = [A] [I_{012}]$$

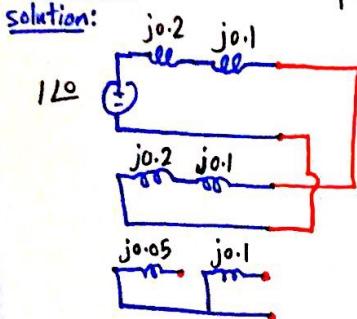Example: Solve the previous example for Line-to-line fault.



@ the fault: $I_a^{(0)} = 0$, $I_a^{(1)} = -I_a^{(2)} = \frac{1 \times 0}{j0.3 + j0.3} = 1.67 \times^{-90^\circ}$

$$\Rightarrow \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = [A] \begin{bmatrix} 0 \\ 1.67 \times^{-90^\circ} \\ 1.67 \times^{90^\circ} \end{bmatrix} = \begin{bmatrix} 0 \\ 2.893 \times^{180^\circ} \\ 2.893 \times^0 \end{bmatrix}$$


@ the Gen.: $I_a^{(0)} = 0$, $I_a^{(1)} = 1.67 \times^{-120^\circ}$, $I_a^{(2)} = 1.67 \times^{120^\circ}$

$$\Rightarrow \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = [A] \begin{bmatrix} 0 \\ 1.67 \times^{-120^\circ} \\ 1.67 \times^{120^\circ} \end{bmatrix} = \begin{bmatrix} 1.67 \times^{180^\circ} \\ 1.67 \times^{180^\circ} \\ 3.34 \times^0 \end{bmatrix}$$

$$|I_a| = |I_b| = 1.67 \times 2886.8 \approx 4821 \text{ A.}$$

$$|I_c| = 3.34 \times 2886.8 \approx 9642 \text{ A}$$

* Line-to-Line-to-ground Fault:

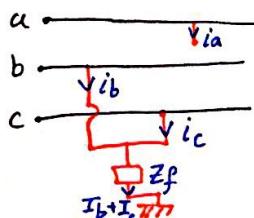

$$1) i_a = 0 \dots ① \quad V_b = V_c \dots ② \quad V_b = Z_f(I_b + I_c) \dots ③$$

$$2) ② \Rightarrow V^{(0)} + a^2 V^{(1)} + a V^{(2)} = V^{(0)} + a V^{(1)} + a^2 V^{(2)} \Rightarrow V^{(1)}(a^2 - a) = V^{(2)}(a^2 - a) \Rightarrow V^{(1)} = V^{(2)} \dots ④$$


$$3) \Rightarrow V^{(0)} + a^2 V^{(1)} + a V^{(2)} = Z_f(I^{(0)} + a^2 I^{(1)} + I^{(2)} + a I^{(1)} + a^2 I^{(2)}) \Rightarrow V^{(1)} = V^{(2)} \dots ④$$

$$\Rightarrow V^{(0)} + V^{(1)}(a^2 + a) = Z_f[2I^{(0)} + I^{(1)}(a^2 + a) + I^{(2)}(a^2 + a)]$$

$$\therefore V^{(0)} - V^{(1)} = Z_f[2I^{(0)} - I^{(1)} - I^{(2)}] \dots ⑤$$

$$① \Rightarrow I^{(0)} + I^{(1)} + I^{(2)} = 0 \Rightarrow I^{(0)} = -(I^{(1)} + I^{(2)}) \dots ⑥ \quad \text{sub } ⑥ \text{ into } ⑤: V^{(0)} - V^{(1)} = Z_f[2I^{(0)} + I^{(0)}]$$
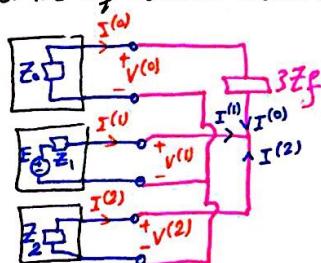
$$3) \text{ Connect the seg. Networks in such away that } ④, ⑥ \& ⑦ \text{ are satisfied: } \therefore V^{(0)} - V^{(1)} = I^{(0)} 3Z_f \dots ⑦$$




$$4) \therefore I^{(1)} = \frac{E}{Z_1 + (Z_0 + 3Z_f) // Z_2} \quad V^{(1)} = V^{(2)} = E - I^{(1)} Z_1$$

$$\text{By current division: } -I^{(0)} = I^{(1)} \frac{Z_2}{Z_0 + Z_2 + 3Z_f}$$

$$V^{(0)} = -I^{(0)} Z_0, \quad I^{(0)} + I^{(1)} + I^{(2)} = 0 \quad \therefore I^{(0)} = -I^{(1)} - I^{(2)}$$

$$5) [V_{abc}] = [A] [V_{012}], \quad [I_{abc}] = [A] [I_{012}]$$

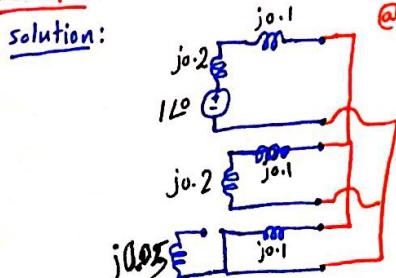Example: Solve the Previous example for L-L-G1 fault.



@F: $I^{(1)} = \frac{I_L0}{j0.3 + (j0.3 // j0.1)} = 2.67 \times^{-90^\circ}$

$$V^{(0)} = V^{(1)} = V^{(2)} = 1.40 - I^{(1)}(j0.3) = 0.2 \quad I^{(0)} = \frac{-V^{(0)}}{j0.1} = 2 \times^{90^\circ}$$

@G: $I^{(0)} = 0$, $I^{(1)} = 2.67 \times^{-120^\circ}$, $I^{(2)} = 0.67 \times^{120^\circ}$

$$@F: \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 0 \\ 4.17 \angle 134^\circ \\ 4.17 \angle 146^\circ \end{bmatrix} \quad @G: \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 2.41 \angle -134^\circ \\ 2.41 \angle 134^\circ \\ 3.34 \angle 0^\circ \end{bmatrix}$$

* Application of Zbus matrix in Unbalanced Fault:


• Objective: is to use this matrix for finding Z_0, Z_1, Z_2 of a given system.

• It was found that: $Z_{bus} = [Y_{bus}]^{-1}$, hence one has to find $[Y_{bus}]$ matrix for each seg. Network. Then find Z_{bus} for each seg Network.



Power1



Fall017

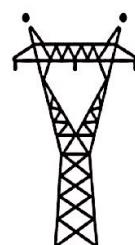

Dr. Deefallah Dalabeeh



By: Mhmd Abuhashya

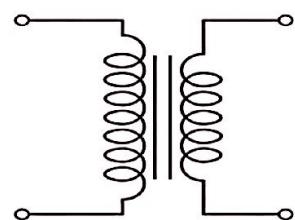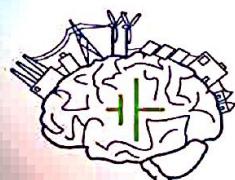


Powerunit-ju.com

• Illustration: Consider the following system:

in Book: Ex 12.1/479 + 12.2/485

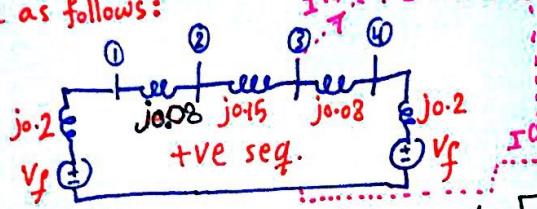
for the given DATA, the seq. Network will be as follows:



-ve seq. same as +ve with sources S/C.

* for +ve seq: $[Y_{bus}^{(1)}] \Rightarrow Z_{bus}^{(1)}$

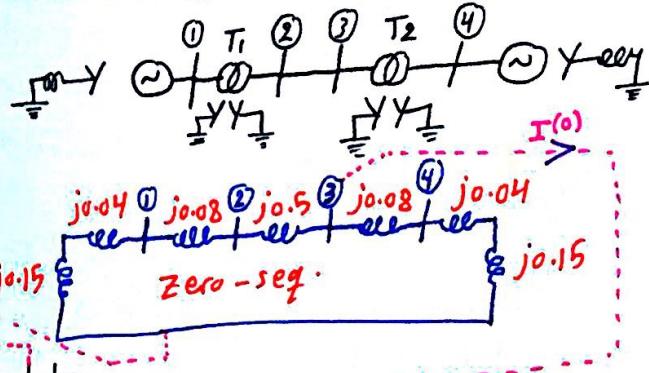* It can be found: $Z_{bus}^{(1)} = Z_{bus}^{(2)} = \left[\begin{array}{cccc} 0.1437 & 0.1211 & 0.0789 & 0.0563 \\ 0.1211 & 0.1696 & 0.1104 & 0.0789 \\ 0.0789 & 0.1104 & 0.1696 & 0.1211 \\ 0.0563 & 0.0789 & 0.1211 & 0.1437 \end{array} \right]$



-ve seq. same as +ve with sources S/C.

* for -ve seq: $[Y_{bus}^{(2)}] \Rightarrow Z_{bus}^{(2)}$

* for 0-seq.: $[Y_{bus}^{(0)}] \Rightarrow Z_{bus}^{(0)}$

* for e.g. Consider a L-G fault @ bus ③: (the connection will be as shown above).

$$I^{(0)} = I^{(1)} = I^{(2)} = \frac{1 \times 0}{Z_0 + Z_1 + Z_2}; \quad Z_0 = [Z_{33} \text{ of } Z_{bus}^{(0)}]; \quad Z_1 = [Z_{33} \text{ of } Z_{bus}^{(1)}] = Z_2$$

* Having Calculated the symm. components of a given fault current, then cct techniques can be used to find the fault current through any element as illustrated by the following e.g (previous system):

[for L-G fault @ bus ③]

\Rightarrow find current supplied by G_1 ?

find $I_{G_1}^{(0)}, I_{G_1}^{(1)}, I_{G_1}^{(2)}$ By using Current Division.


$$I_{G_1}^{(1)} = 0.73 \times -90^\circ, \quad I_{G_1}^{(2)} = I_{G_1}^{(1)} = 0.73 \times -90^\circ$$

$$I_{G_1}^{(0)} = 0.519 \times -90^\circ$$

\therefore for G_1 :

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \sum A \begin{bmatrix} I_{G_1}^{(0)} \\ I_{G_1}^{(1)} \\ I_{G_1}^{(2)} \end{bmatrix} = \begin{bmatrix} 1.99 \times -90^\circ \\ 0.21 \times +90^\circ \\ 0.21 \times 90^\circ \end{bmatrix}$$

* end of second material *

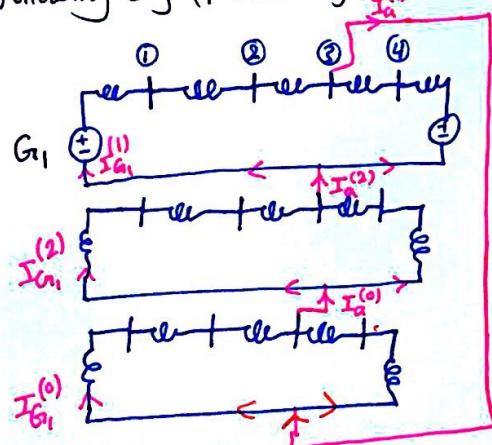

Open-Circuit Fault :

If an O/C occur on one phase or 2-phases (for e.g. due to an accident), then the system becomes Unsymmetrical OR Unbalanced.

Then the objective is to evaluate the voltage across the points p, p' .

• Procedure: The +ve, -ve & Zero seq networks concept can be used.

* This problem can be simulated by: ① Removing the line between m & n .

② Introduce S/C for other phases (e.g. S/C is introduced for phases a & b).


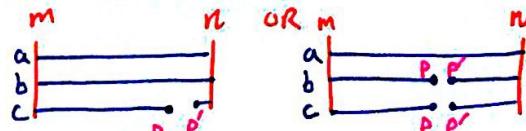



Fig.1

* if Z_1, Z_2 & Z_0 are the seq. impedances of the line between m & n.
 Hence, the removal of the line is simulated by adding: $-Z_1, -Z_2, -Z_0$
 to the Thevenin equivalent between buses m & n, for the +ve, -ve & zero seq.
 And Adding the fraction of the lines as follows:

Consider the +ve Seq. Therv. Eqn. :

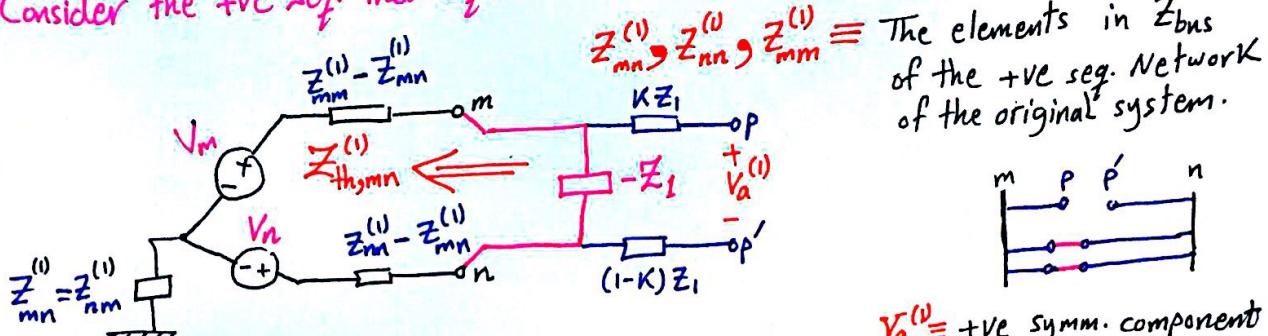

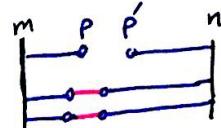$Z_{mn}^{(1)}, Z_{nn}^{(1)}, Z_{mm}^{(1)}$ = The elements in Z_{bus} of the +ve seq. Network of the original system.




$V_a^{(1)}$ = +ve symm. component of phase a for V_{pp} .

* we would like to evaluate: $V_{pp,a} > V_{pp,b} > V_{pp,c}$.

* Note: the -ve seq. Therv. Eqn. is the same, BUT replacing the sources by S/C and superscript (1) by (2).

Zero seq. Therv. Eqn. is the same, BUT replacing the sources by S/C & superscript (1) by (0).

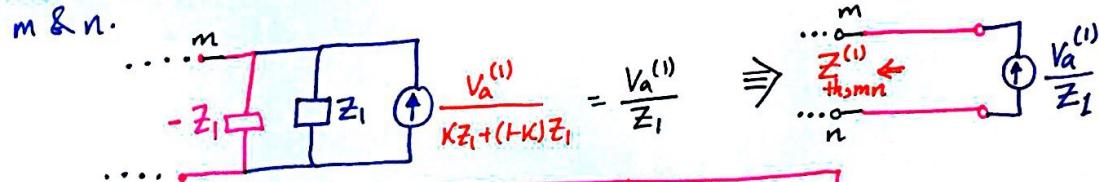* Use source transformation (for the above cct) To find current injections at the busbars m & n.



current injections:		
	+ve seq.	-ve seq.
m	$V_a^{(1)}/Z_1$	$V_a^{(2)}/Z_2$
n	$-V_a^{(1)}/Z_1$	$-V_a^{(2)}/Z_2$
		Zero seq.
		$V_a^{(0)}/Z_0$

∴ By Using Current injections one can find change of voltages at busbar m & n as explained before.

* To find the method of connection between seq. Networks one has to find Thevenin Equivalent for each seq.

* o/c fault was simulated by Current injections at busbars m & n.

* objective: To evaluate voltage changes at busbars due to this fault.

For e.g. at the i th bus, the changes will be as follows:

$$\begin{aligned}\Delta V_i^{(0)} &= (Z_{im}^{(0)} - Z_{in}^{(0)}) V_a^{(0)}/Z_0 \dots ① \\ \Delta V_i^{(1)} &= (Z_{im}^{(1)} - Z_{in}^{(1)}) V_a^{(1)}/Z_1 \dots ② \\ \Delta V_i^{(2)} &= (Z_{im}^{(2)} - Z_{in}^{(2)}) V_a^{(2)}/Z_2 \dots ③\end{aligned}$$

$\underbrace{\text{element of}}_{Z_{bus \ 0,1,2}}$

$Z_1, Z_2, Z_0 \equiv +ve, -ve, zero$
impedances of T-Line.

* ①, ② & ③ can be solved by finding $V_a^{(0)}, V_a^{(1)}$ & $V_a^{(2)}$ as follows:

Finding Th. equ. for the +ve, -ve, zero equivalent networks between buses m & n.

$$\begin{aligned}+ve \ seq. \ Z_{pp'}^{(1)} &= KZ_1 + [(-Z_1)/Z_{th,mn}] + (Z_1 - KZ_1) \Rightarrow Z_{pp'}^{(1)} = -Z_1^2/(Z_{th,mn} - Z_1) \dots ④ \\ \Rightarrow V_{th} = (V_m - V_n) \frac{(-Z_1)}{Z_{th,mn} - Z_1} &\Rightarrow V_{th} = (V_m - V_n) \frac{Z_{pp'}^{(1)}}{Z_1} \dots ⑤\end{aligned}$$

* Before the o/c of the line, the current flowing from m to n is I_{mn} :

$$I_{mn} = \frac{V_m - V_n}{Z_1} \dots ⑥ \quad \therefore \text{substituting } ④ \text{ into } ⑤: \quad V_{th} = I_{mn} Z_{pp'}^{(1)} \dots ⑦$$

$$\begin{aligned}* \text{By similar approach it can be found that: } Z_{pp'}^{(2)} &= -Z_2^2/(Z_{th,mn} - Z_2) \dots ⑧ \\ Z_{pp'}^{(0)} &= -Z_0^2/(Z_{th,mn} - Z_0) \dots ⑨\end{aligned}$$

④ + ⑦ \Rightarrow +ve seq. Network.

⑧ \Rightarrow -ve seq. Network.

⑨ \Rightarrow Zero seq. Network.

* The interconnection between these Networks, depends on the Type of Fault.

\Rightarrow Consider the Case of One Open Conductor.



$$I_a = 0 \dots ⑩$$

$$\therefore I_a^{(0)} + I_a^{(1)} + I_a^{(2)} = 0 \dots ⑪ \quad \text{for phase b \& c: } V_{pp',b} = V_{pp',c} = 0 \dots ⑫$$

* Transpose ⑫ into symm. components:

$$\begin{bmatrix} V_a^{(0)} \\ V_a^{(1)} \\ V_a^{(2)} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_{pp',a} \\ V_{pp',b} = 0 \\ V_{pp',c} = 0 \end{bmatrix} = \frac{1}{3} \begin{bmatrix} V_{pp',a} \\ V_{pp',a} \\ V_{pp',a} \end{bmatrix} \dots ⑬ \quad \therefore V_a^{(0)} = V_a^{(1)} = V_a^{(2)}$$

: Connection between Seq. Networks should satisfy ⑩ & ⑬:

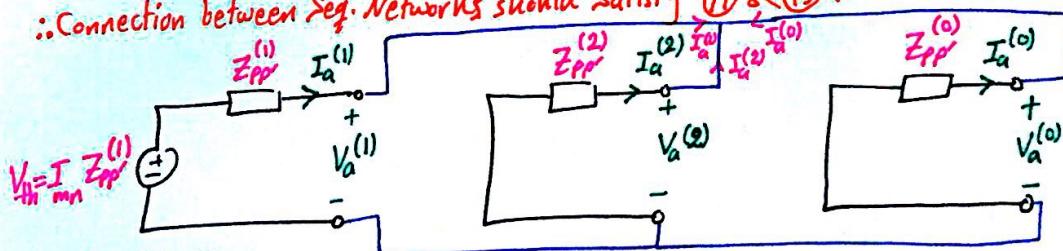


Fig.(1)

$Z_{pp'}^{(1)}, Z_{pp'}^{(2)}, Z_{pp'}^{(0)}$ were evaluated from th. eq. between buses m & n.

\therefore From Fig. (1) :

$$I_a^{(1)} = \frac{V_{Th} = I_{mn} Z_{pp'}^{(1)}}{Z_{pp'}^{(1)} + (Z_{pp'}^{(2)} // Z_{pp'}^{(0)})} \Rightarrow I_a^{(1)} = \frac{I_{mn} Z_{pp'}^{(1)} (Z_{pp'}^{(2)} + Z_{pp'}^{(0)})}{Z_{pp'}^{(1)} Z_{pp'}^{(2)} + Z_{pp'}^{(1)} Z_{pp'}^{(0)} + Z_{pp'}^{(2)} Z_{pp'}^{(0)}}$$

49


Now the symm. Components $V_a^{(0)} = V_a^{(1)} = V_a^{(2)} = I_a^{(1)} \frac{Z_{pp'}^{(2)} Z_{pp'}^{(0)}}{Z_{pp'}^{(2)} + Z_{pp'}^{(0)}}$... (15) (16)


* Substitute (14) into (15) & Re-arrange, it can be found:

* Finally, Substitute ⑯ into ①, ② & ③ To find $\Delta V_i^{(0)}$, $\Delta V_i^{(1)}$, $\Delta V_i^{(2)}$.

Example: for the shown system:

see page 46 for
 $Z^{(1)}, Z^{(2)}, Z^{(0)}$

 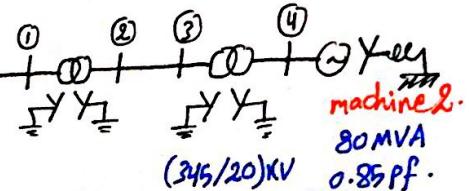$Z_{bus}^{(1)}, Z_{bus}^{(2)}, Z_{bus}^{(0)}$ are given page 482 & 486 in Book.  PV values are according to base values 100MVA, 345KV.



Determine the change in voltages at bus ③, when T.L between Buses ② & ③ undergoes one open-conductor fault?

- choose a base value of 100MVA, 345K volt.
 - Given for the line $X_1 = X_2 = 15\%$ & $X_o = 50\%$.

Solution:

solution: objective is To find ΔV_3 . \Rightarrow load in our case is the motor.

$$I_{mch2} = \frac{80000 * 10^3}{\sqrt{2} * 21 * 10^3} \cancel{\times \cos^{-1}(0.85)} \Rightarrow I_{mch2} = 2309 \cancel{\times -31.8^\circ} A$$

$$I_{23} = 2309 \cancel{\times -31.8^\circ} * \frac{20}{345} \Rightarrow I_{23} = 133.9 \cancel{\times -31.8^\circ} A \quad I_b = \frac{100 * 10}{\sqrt{3} * 345 * 10^3} \Rightarrow I_b = 167.3 A$$


$$Z_{pp}^{(1)} = \frac{-Z_1^2}{Z_{th,23}^{(1)} - Z_1} ; Z_1 = j0.15$$

$$Z_{pp}^{(1)} = j0.712$$

$$Z_{th,23}^{(1)} = Z_{22}^{(1)} + Z_{33}^{(1)} - 2Z_{23}^{(1)} = j0.1184$$

By similar approach it can be found:
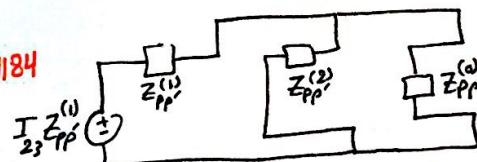
$$Z_{pp'}^{(1)} = Z_{pp'}^{(2)} = j 0.712, \quad Z_{pp'}^{(o)} = j 1.039$$



$$V_a^{(1)} = V_a^{(0)} = V_a^{(2)} = \frac{I_{23}}{\frac{1}{Z_a^{(0)}} + \frac{1}{Z_a^{(1)}} + \frac{1}{Z_a^{(2)}}} \Rightarrow V_a^{(0)} = V_a^{(1)} = V_a^{(2)} = 0.2122 \times 58.2$$

$$\Delta V_3^{(1)} = \Delta V_3^{(2)} = \frac{Z_{32}^{(1)} - Z_{33}^{(1)}}{Z_1} V_a^{(1)} = 0.0837 \cancel{\times -121.8^\circ}, \quad \Delta V_3^{(0)} = \frac{Z_{32}^{(0)} - Z_{33}^{(0)}}{Z_0} V_a^{(0)} = 0.0551 \cancel{\times -121.8^\circ}$$

$$\therefore \Delta V_3 = \Delta V_3^{(0)} + \Delta V_3^{(1)} + \Delta V_3^{(2)} \Rightarrow \Delta V_3 = 0.2225 \times -121.8^\circ \quad \#$$

*in case of 0/c fault: $\begin{bmatrix} \Delta V_1 \\ \Delta V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & \dots & z_{1n} \end{bmatrix} \begin{bmatrix} 0 \\ v_{1/2} \end{bmatrix} \Rightarrow$ in case $m=2$ & $n=3$

$$\begin{bmatrix} \Delta V_1 \\ \Delta V_2 \\ \Delta V_3 \\ \vdots \\ \Delta V_n \end{bmatrix} = \begin{bmatrix} z_{11} & \dots & z_{1n} \\ z_{21} & \dots & z_{2n} \\ z_{31} & \dots & z_{3n} \\ \vdots & & \vdots \\ z_{n1} & \dots & z_{nn} \end{bmatrix} \begin{bmatrix} 0 \\ v_a/z_1 \\ -v_a/z_2 \\ 0 \\ \vdots \end{bmatrix} \Rightarrow \text{in case } m=2 \& n=3 \\ \text{i.e.: O/C fault between } \textcircled{2} \& \textcircled{3}.$$

* Power flow (Load flow) *

What!!

* Power Flow: It is the calculation of voltages at busbars for a given load condition.

* Consequently, the following may calculated:

- i) flow of current in lines.
- ii) flow of power in lines.
- iii) losses in lines.

Why!!

* Power flow analysis is used:

- ① In planning or in expansion.
- ② In operation; to find the optimal solution.

How!!

* Load Flow Formulation Problem:

• Consider the i th bus in a given system.

Current injected into the Network: $I_i = Y_{i1}V_1 + Y_{i2}V_2 + \dots + Y_{iN}V_N$

where $N \equiv$ Number of busbars.

$$\Rightarrow I_i = \sum_{j=1}^N Y_{ij} V_j$$


• Complex Power injected into Network from bus i :

$$S = P + jQ = V_i I_i^* \therefore S = |V_i| |I_i^*| \left(\sum_{j=1}^N Y_{ij} V_j \right)^*$$

$$\Rightarrow S_i = \sum_{j=1}^N |V_i| |V_j| |Y_{ij}| \times \underline{\delta_i - \delta_j - \theta_{ij}} \quad \Rightarrow \text{Power Flow Equation (P&Q).}$$

$$P_i = \sum_{j=1}^N |V_i| |V_j| |Y_{ij}| \cos(\delta_i - \delta_j - \theta_{ij}) \dots \textcircled{1}$$


$$Q_i = \sum_{j=1}^N |V_i| |V_j| |Y_{ij}| \sin(\delta_i - \delta_j - \theta_{ij}) \dots \textcircled{2}$$

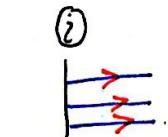

$$[I] = [Y] [V]$$

$$\begin{bmatrix} I_1 \\ \vdots \\ I_N \end{bmatrix} = \begin{bmatrix} Y_{11} & \dots & Y_{1N} \\ \vdots & \ddots & \vdots \\ Y_{N1} & \dots & Y_{NN} \end{bmatrix} \begin{bmatrix} V_1 \\ \vdots \\ V_N \end{bmatrix}$$

$$\begin{aligned} V_i &= |V_i| \times \underline{\delta_i} \\ Y_{ij} &= |Y_{ij}| \times \underline{\theta_{ij}} \\ V_j &= |V_j| \times \underline{\delta_j} \end{aligned}$$

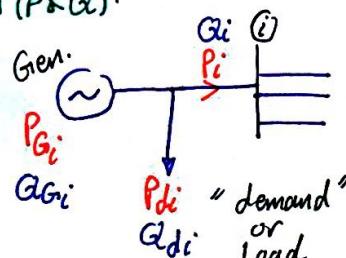


* Equations ① & ② gives the Active & Reactive power injected to the Network from bus i .

* Equations ① & ② can be used to calculate P_i & Q_i .

if $V_i \Rightarrow i=1, N$ are known, then they are called $P_{i,\text{cal}}$ & $Q_{i,\text{cal}}$.

⇒ At any busbar there are 3-parameters:

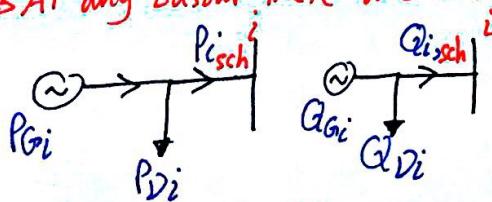

$P_{i,sch}$, $Q_{i,sch}$ are called scheduled generation and load at bus i .

$P_{D,i}$ = Demand OR Load at bus i .

$$\therefore P_{i,sch} = P_{G,i} - P_{D,i} \dots \textcircled{3}$$

$$\therefore Q_{i,sch} = Q_{G,i} - Q_{D,i} \dots \textcircled{4}$$

\therefore In the process of calculations, there will be mismatch between $P_{i,\text{cal}}$ & $P_{i,\text{sch}}$.

$$\therefore \Delta P_i = P_{i,\text{sch}} - P_{i,\text{cal}}$$

$$\Delta Q_i = Q_{i,\text{sch}} - Q_{i,\text{cal}}$$

* Solution will be obtained when Power mismatch = 0 (i.e. $\Delta P_i = \Delta Q_i = 0$).

* By observing ① & ② it can be found that there are 4 unknowns P_{i,G_i} , $|V_j|$ & δ_j . Hence one has to specify 2 parameters and calculate for the other 2 variables.

\Rightarrow This selection depends on the type of busbar, and classify as follows:

① P-Q or Load Bus: This is a Non-generator bus. $\Rightarrow \therefore P_{G_i} = Q_{G_i} = 0$.

• P_{D_i} can be estimated by using (for e.g) "Load for Cast".

• Q_{D_i} can be calculated by assuming a certain Pf.

$$\therefore P_{i,\text{sch}} = P_{G_i} - P_{D_i} \Rightarrow P_{i,\text{sch}} = -P_{D_i} \quad \therefore Q_{i,\text{sch}} = Q_{G_i} - Q_{D_i} \Rightarrow Q_{i,\text{sch}} = -Q_{D_i}$$

here $P_{i,\text{sch}}$ & $Q_{i,\text{sch}}$ are the specified values for P_i & Q_i .

\therefore ① & ② Can be used To calculate $|V_j|$ & δ_j .

② Voltage-Controlled or PV bus:

• This is a generator bus. \Rightarrow here one can specify P_{G_i} & $|V_i|$.

• Q_i can be calculated when ALL the voltages of the busbars are found. Hence, The only unknown is δ_i .

③ Slack or Reference Busbars:

• Since one calculated phasor voltages then one busbar should be selected as a Reference. Usually, This busbar given Number 1 & specified as follows: $V_j = 1 \times 0^\circ \text{ pu}$. Usually, This busbar it is a generator bus.

Why (generator bus) ?!

$$\sum P_i = \sum P_{G_i} - \sum P_{D_i} = P_{\text{Loss}} \quad \text{"Active Losses in Resistive Component"}$$

$$\sum Q_i = \sum Q_{G_i} - \sum Q_{D_i} = Q_{\text{Loss}} \quad \text{"Reactive Losses in Reactive Component"}$$

• Summary:

<u>Bus Type</u>	<u>#of Buses</u>	<u>specified quantities</u>	<u>#of available equations</u>	<u>#of Unknowns state variables</u>
Slack, $i=1$	1	$ V_1 , S_1$	0	0
Voltage Controlled or PV bus. ($i=2, \dots, N_g$)	N_g	$P_i, V_i $	N_g	N_g
Load or PQ bus ($i=N_g+2, \dots, N$)	$N-N_g-1$	P_i, Q_i	$2(N-N_g-1)$	$2(N-N_g-1)$
SUM \Rightarrow	N	$2N$	$2N-N_g-2$	$2N-N_g-2$

* Unknowns: are called dependent or state variables.

- Illustration: If a power system has **9-buses**, at each bus there is a load.
(Example) Generators are connected to buses 1, 2, 5, 7.
- * Identify bus types & unknowns to be evaluated?

Solution: Types:
 • Slack bus \Rightarrow ① • Voltage Controlled or PV bus \Rightarrow ②, ⑤, ⑦
 • Load or PQ bus \Rightarrow ③, ④, ⑥, ⑧, ⑨

Unknowns: Voltage controlled $\Rightarrow S_2, S_5, S_7$ Load $\Rightarrow V_3, V_4, V_6, V_8, V_9$.
 where $V_x = |V_x| \times \delta_x$

$$N=9, N_g=3 \Rightarrow \therefore \# \text{of equations} = 2 * 9 - 3 - 2 = 13 \text{ equations.}$$

* Comment: Since Power flow equations are Non-linear functions of the state variables, Then Iterative Methods are used to solve them

\Rightarrow Here 2-methods will be considered:

1] Gauss-Seidal Method: This uses Power flow equations to Calculate Voltages.


2] Newton-Raphson Method: This uses Power mismatch ($\Delta P, \Delta Q$) to Calculate Voltages.

* Gauss-Seidal Method:

This is introduced as follows:

$$S_i = V_i I_i^* \Rightarrow S_i^* = V_i^* I_i = V_i^* \sum_{n=1}^N Y_{in} V_n$$
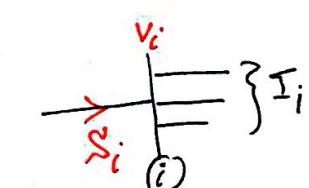
$$\therefore \frac{S_i^*}{V_i^*} = \sum_{n=1}^N Y_{in} V_n = Y_{ii} V_i + \sum_{n \neq i} Y_{in} V_n$$



Y_{in} = element in the $[Y]$ bus matrix..

$$\therefore V_i^{(K)} = \frac{1}{Y_{ii}} \left[\frac{S_i^*}{V_i^*} - \sum_{\substack{n=1 \\ n \neq i}}^N Y_{in} V_n \right] = \frac{1}{Y_{ii}} \left[\frac{S_i^*}{V_i^*} - \sum_{j=1}^{i-1} Y_{ij} V_j - \sum_{j=i+1}^N Y_{ij} V_j \right]$$

53

$K \equiv$ Number of Iterations.

$S_i = P_i + jQ_i$; The complex transmitted power.

$V^{(0)}$ initial. $V_1^{(0)} = 1 \angle 0^\circ$ Let: $V_2^{(0)} = V_3^{(0)} = \dots = V_N^{(0)} = 1 \angle 0^\circ$

$$\Rightarrow V_i^{(K)} = \frac{1}{Y_{ii}} \left[\frac{S_i^*}{V_i^{(K-1)*}} - \sum_{j=1}^{i-1} Y_{ij} V_j^{(K)} - \sum_{j=i+1}^N Y_{ij} V_j^{(K-1)} \right] \dots \quad (1)$$

Equation (1) is used to Calculate New values for voltages as follows:

Procedure:

i) Specify a voltage for the slack bus, $V_1 = 1 \angle 0^\circ$. This value is kept constant during calculations.

ii) Assume initial value for voltage for all other buses. Let $V_j^{(0)} = 1 \angle 0^\circ$ for $j = 2, \dots, N$.

iii) Substitute V_i & V_j in (1) to calculate New values for voltages $V_j^{(1)}, j = 2, \dots, N$.

Note: on the RHS of (1), one always substitute the most recent values.

iv) When all voltages are calculated, then one iteration is completed.

v) At the end of iteration, Check that: $|V_i^{(K)} - V_i^{(K-1)}| < \epsilon$ for all buses.

ϵ = Specified Tolerance e.g. $\epsilon = 10^{-5}$.

After check if Yes, Solution is Obtained.

Not, go to next iteration.

To illustrate the application of equation (1), Consider 4-bus system, with

bus (1) as a slack. (2), (3) & (4) as PQ-buses.
with initial values given as $V_2^{(0)}, V_3^{(0)},$ & $V_4^{(0)}$.

Note: V_1 is fixed $V_1 = 1 \angle 0^\circ$.

$$V_2^{(1)} = \frac{1}{Y_{22}} \left[\frac{P_{2,sch} - jQ_{2,sch}}{V_2^{(0)*}} - (Y_{21} V_1 + Y_{23} V_3^{(0)} + Y_{24} V_4^{(0)}) \right]$$

$$V_3^{(1)} = \frac{1}{Y_{33}} \left[\frac{P_{3,sch} - jQ_{3,sch}}{V_3^{(0)*}} - (Y_{31} V_1 + Y_{32} V_2^{(1)} + Y_{34} V_4^{(0)}) \right]$$

$$V_4^{(1)} = \frac{1}{Y_{44}} \left[\frac{P_{4,sch} - jQ_{4,sch}}{V_4^{(0)*}} - (Y_{41} V_1 + Y_{42} V_2^{(1)} + Y_{43} V_3^{(1)}) \right]$$

1st iteration
is Completed.

Check: $|V_j^{(1)} - V_j^{(0)}| < \epsilon$ for all $j = 2, 3, 4$ if yes solution is obtained.
if NOT go to 2nd iteration.

Example 9.2 page 337:


System has: 4-buses, 2 gen., 4 Lines.
with the following PV data for the line
and buses by using Base value of
100 MVA, 230 KV.

- Objective: Use G.S method to evaluate voltages @ Busbars.

*** Line DATA:**

BUS-Bus	Serie Z	$Y_s = \frac{1}{Z}$	Total charging MVAR	$\frac{Y}{2}$
1 - 2	0.01008	0.05040	3.815629	-19.078144
1 - 3	0.00744	0.03720	5.169561	-25.847809
2 - 4	0.00744	0.03720	5.169561	-25.847809
3 - 4	0.01272	0.06360	3.023705	-15.128528

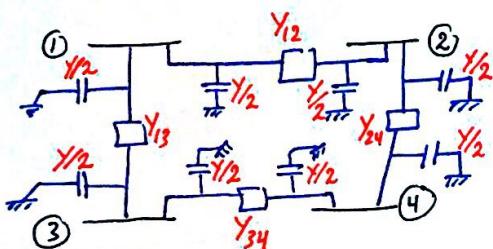
Note: $G, B, Y_{\frac{1}{2}}$ found from the Calculations.



From the given & calculated values for the lines one can evaluate $[Y]_{bus}$.

$$Z = R + jX \Rightarrow Y_s.$$

Line:

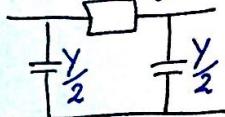

• Calculations:

$$Y_{12} = \frac{1}{Z_{12}} = \frac{1}{0.01008 + j0.0504} \\ \Rightarrow Y_{12} = 3.815629 - j19.078144$$


$$\begin{aligned} \text{Total VAR} &= 3V_\phi I_\phi \\ &= 3V_\phi (Y_s W_C) \\ &= 3V_\phi^2 Y \end{aligned}$$

$$\begin{aligned} Y &= \frac{\text{VAR}}{3V_\phi^2} = \frac{10.25 * 10^6}{3(230)^2 * 10^6} \\ Y_{PV} &= \frac{Y}{Y_b} \rightarrow Y_b = \frac{1}{Z_b} \\ \Rightarrow Z_b &= \frac{(230)^2}{100} \\ \Rightarrow Y_{PV} &= 0.1025 \\ \text{so } \frac{Y}{2} &= 0.05125 \end{aligned}$$

*** Bus DATA:** Bus 1 is slack; P_G & Q_G will be calculated at the end.

Bus	Generation		MV Load		$\frac{Y}{2}$	Calculated from: $Q = P \tan[\cos^{-1} 0.85]$
	P_G	Q_G	P	Q		
slack 1	-	-	50	30.94	$1 \times 0^\circ$	Specified value.
PQ or load 2	0	0	170	105.35	$1 \times 0^\circ$	Initial assumed values for the unknowns.
3	0	0	200	123.94	$1 \times 0^\circ$	
PV 4	318	-	80	49.58	$1.02 \times 0^\circ$	L → voltage control "given"

Procedure as follows:

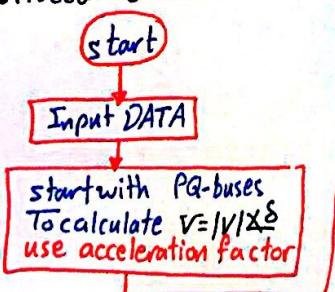

Start with PV buses for each bus: first calculate Q₂
check that: $Q_{min} \leq Q \leq Q_{max}$.
If Yes → Calculate V

If No → Set Q at the violated limit:
e.g. if $Q = Q_{max}$
∴ The busbar is converted (PV) → (PQ).

→ for the Example:

- start with Bus 2:

$$V_2^{(1)} = \frac{1}{Y_{22}} \left[P_{2,sch} - j Q_{2,sch} - (Y_{21}V_1 + Y_{23}V_3^{(0)} + Y_{24}V_4^{(0)}) \right]$$

- from the Line DATA: (There are Two Lines) for Y_{22}

Line 1-2: $Y_{12} = 3.815629 - j 19.078144 \dots ①$

$$\frac{Y}{2} = j 0.05125 \dots ②$$

Line 2-4: $Y_{24} = 5.169561 - j 25.847809 \dots ③$

$$\frac{Y}{2} = j 0.03875 \dots ④$$

$$Y_{22} = ① + ② + ③ + ④ \Rightarrow Y_{22} = 8.98519 - j 44.835953$$

→ See the Table in the Book.

$$P_2 - j Q_2 = (P_{2,sch} - P_{2,l}) - j (Q_{2,sch} - Q_{2,l}) = \frac{(0-170)}{100} - j \frac{(0-105.35)}{100}$$

$$\Rightarrow P_2 - j Q_2 = -1.7 + j 1.0535$$

∴ By Substitution: $\underline{V}_2^{(1)} = 0.983 - j 0.032$

* Acceleration Factor (α): $1 < \alpha < 2$, used in order to reduce the number of iterations, usually they use $\alpha = 1.6$.

* $\underline{V}_{2,acc}^{(1)} = \underline{V}_2^{(0)} + \alpha (\underline{V}_2^{(1)} - \underline{V}_2^{(0)})$

∴ By Substitution: $\underline{V}_{2,acc}^{(1)} = 0.973 - j 0.0517$

** Repeat the same procedure for Bus 3.

it can be found that: $\underline{V}_{3,acc}^{(1)} = 0.953 - j 0.066$

Note: In iteration use V_{acc} .

• Bus 4: (PV bus).

⇒ first Calculate Q_4 .

⇒ In general: $S_i = V_i I_i^* \Rightarrow S_i^* = V_i^* I_i = P_{G,i} - j Q_{G,i} = [V_i^* \sum_{j=1}^n V_j Y_{ij}]$


$Q_i^{(K)} = -\text{Im} \left[V_i^{(K-1)*} \left(\sum_{j=1}^{i-1} Y_{ij} V_j^{(K)} + \sum_{j=i}^N Y_{ij} V_j^{(K-1)} \right) \right]$

imaginary.

⇒ for Bus 4: $Q_4^{(1)} = -\text{Im} \left[V_4^{(0)*} \left[Y_{42} V_{2,acc}^{(1)} + Y_{43} V_{3,acc}^{(1)} + Y_{44} V_4^{(0)} \right] \right]$

∴ By Substitution: $Q_4^{(1)} = 1.654151$

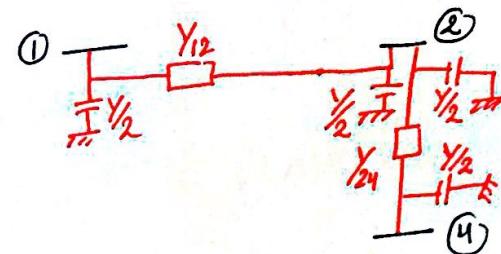in this example: it is assumed that the calculated Q_4 is within the limit
⇒ so calculate $V_4^{(1)}$.



$$V_4^{(1)} = \frac{1}{Y_{44}} \left[P_{4, \text{sch}} - j Q_4^{(1)} - (Y_{42} V_{2, \text{ac}} + Y_{43} V_{3, \text{acc}}) \right] = \underline{\underline{1.017874 - j 0.010604}}$$

$$|V_4^{(1)}| = 1.017929 \quad \therefore V_4^{\text{corr.}} = \frac{1.02}{1.017929} (1.017874 - j 0.010604)$$

Corrected Value.

$$\therefore \underline{\underline{V_4^{(1)} = 1.02 \times S_4^{(1)}}}$$

@ the end of 1st iteration, check for each busbar 2,3,4:

$|V_i^{(1)} - V_i^{(0)}| \leq \epsilon_{\text{specified}}$ is satisfied → if NOT Go to Next iteration.
Tolerance

- Among the input data: ϵ and max. No. of iterations.

*Newton-Raphson Method :

This is based on the Taylor's Expansion for 2 functions with 2 or more variables. It is illustrated as follows:

$h_1(x_1, x_2, u) = b_1 \dots (1)$ $h_1, h_2 \equiv$ 2 functions. $x_1, x_2 \equiv$ Unknown variables.
 $h_2(x_1, x_2, u) = b_2 \dots (2)$ $b_1, b_2 \equiv$ Constants represent specified values of h_1 & h_2 .
 $u \equiv$ Called control variable, and to be taken as constant later on.

*Hence, for initial assumed values for x_1 & x_2 , h_1, h_2 represent Calculated values.

∴ Difference between calculated & specified gives mismatch. Consequently the following 2 functions are introduced:

$$g_1(x_1, x_2, u) = h_1(x_1, x_2, u) - b_1 \dots (3) \quad \therefore \text{one assumes initial solutions:}$$

$$g_2(x_1, x_2, u) = h_2(x_1, x_2, u) - b_2 \dots (4) \quad x_1^{(0)} \& x_2^{(0)}$$

• Objective: is to find the amount of corrections $\Delta x_1^{(0)}$ & $\Delta x_2^{(0)}$ to the assumed solution, in order to obtain the actual or required answers $x_1^* \& x_2^*$.

$$\therefore g_1(x_1^*, x_2^*, u) = g_1(x_1^{(0)} + \Delta x_1^{(0)}, x_2^{(0)} + \Delta x_2^{(0)}, u) = 0 \dots (5)$$

$$g_2(x_1^*, x_2^*, u) = g_2(x_1^{(0)} + \Delta x_1^{(0)}, x_2^{(0)} + \Delta x_2^{(0)}, u) = 0 \dots (6)$$

x_1^* & x_2^* stand for the correct answer.

⇒ Now Taylor's Expansion is applied to (5) & (6) as follows:

$$g_1(x_1^*, x_2^*, u) = g_1(x_1^{(0)}, x_2^{(0)}, u) + \Delta x_1^{(0)} \frac{dg_1^{(0)}}{dx_1} + \Delta x_2^{(0)} \frac{dg_1^{(0)}}{dx_2} + \dots = 0 \dots (7)$$

$$g_2(x_1^*, x_2^*, u) = g_2(x_1^{(0)}, x_2^{(0)}, u) + \Delta x_1^{(0)} \frac{dg_2^{(0)}}{dx_1} + \Delta x_2^{(0)} \frac{dg_2^{(0)}}{dx_2} + \dots = 0 \dots (8)$$

- Partial Derivatives are evaluated at initial values.
- Higher Derivatives are neglected.

$$g_1(x_1, x_2, u) = h_1(x_1, x_2, u) - b_1 \quad \dots @$$

[57]

$$\Rightarrow \frac{dg_1}{dx_1} \Big|^{(0)} \quad \text{Diff. @ w.r.t } x_1. \quad \text{Substitute initial value of } x_1 \& x_2 \text{ to get } \frac{dg_1}{dx_1} \Big|^{(0)}.$$

* Re-write ⑦ & ⑧ in a matrix form:

$$\underbrace{\begin{bmatrix} \frac{dg_1}{dx_1} & \frac{dg_1}{dx_2} \\ \frac{dg_2}{dx_1} & \frac{dg_2}{dx_2} \end{bmatrix}}_{\text{Jacobian Matrix, (J)}} \begin{bmatrix} \Delta x_1^{(0)} \\ \Delta x_2^{(0)} \end{bmatrix} = \begin{bmatrix} -g_1(x_1^{(0)}, x_2^{(0)}, u) = b_1 - h_1(x_1^{(0)}, x_2^{(0)}, u) = \Delta g_1 \\ -g_2(x_1^{(0)}, x_2^{(0)}, u) = b_2 - h_2(x_1^{(0)}, x_2^{(0)}, u) = \Delta g_2 \end{bmatrix} \dots @$$

This matrix Called "Jacobian Matrix, (J)"

$$\text{from } @ : J^{(0)} \begin{bmatrix} \Delta x_1^{(0)} \\ \Delta x_2^{(0)} \end{bmatrix} = \begin{bmatrix} \Delta g_1 \\ \Delta g_2 \end{bmatrix} \quad \therefore \begin{bmatrix} \Delta x_1^{(0)} \\ \Delta x_2^{(0)} \end{bmatrix} = [J^{(0)}]^{-1} \begin{bmatrix} \Delta g_1 \\ \Delta g_2 \end{bmatrix} \dots @$$

• since the RHS of @ is Calculated, then the corrections $\begin{bmatrix} \Delta x_1^{(0)} \\ \Delta x_2^{(0)} \end{bmatrix}$ can be evaluated.

\Rightarrow CHECK: if Corrections $< \epsilon$ (certain specified tolerance, e.g. 10^{-4}).

→ if Yes, solution is obtained. $\boxed{x_1^{(0)} = x_1^{(0)} + \Delta x_1^{(0)}} \\ \boxed{x_2^{(0)} = x_2^{(0)} + \Delta x_2^{(0)}}$

→ if NO, Calculate New Corrections

$$\begin{bmatrix} \Delta x_1^{(1)} \\ \Delta x_2^{(1)} \end{bmatrix} = [J^{(1)}]^{-1} \begin{bmatrix} \Delta g_1 \\ \Delta g_2 \end{bmatrix} \dots @$$

* To Illustrate the application of this procedure:

see example 9.4 (page 344).

Let $g_1(x_1, x_2, u) = 4u x_2 \sin x_1 + 0.6 = 0 \Rightarrow h_1(x_1, x_2, u) = 4u x_2 \sin x_1 \& b_1 = 0.6$
 $g_2(x_1, x_2, u) = 4x_2^2 - 4u x_2 \cos x_1 + 0.3 = 0 \Rightarrow h_2(x_1, x_2, u) = 4x_2^2 - 4u x_2 \cos x_1 \& b_2 = -0.3$

Let in this e.g.: $u=1, x_1^{(0)}=0, x_2^{(0)}=1, \epsilon=10^{-5}$

$$J^{(0)} = \begin{bmatrix} \frac{dg_1}{dx_1} & \frac{dg_1}{dx_2} \\ \frac{dg_2}{dx_1} & \frac{dg_2}{dx_2} \end{bmatrix} = \begin{bmatrix} 4x_2 \cos x_1 & 4 \sin x_1 \\ 4x_2 \sin x_1 & 8x_2 - 4 \cos x_1 \end{bmatrix} \quad \text{substitute } \begin{cases} x_1^{(0)} = 0 \\ x_2^{(0)} = 1 \end{cases}$$

$$\Rightarrow J^{(0)} = \begin{bmatrix} 4 & 0 \\ 0 & 4 \end{bmatrix}$$

$$\therefore \begin{bmatrix} \Delta x_1^{(0)} \\ \Delta x_2^{(0)} \end{bmatrix} = \begin{bmatrix} 4 & 0 \\ 0 & 4 \end{bmatrix}^{-1} \begin{bmatrix} -0.6 \\ -0.3 \end{bmatrix} = \begin{bmatrix} -0.15 \text{ rad} \\ -0.075 \end{bmatrix} \Rightarrow \text{check: Correction } < \epsilon$$

[NO] \Rightarrow so Re-iterate.

* Note: The given equations represent:

The Power flow Equations of the system shown in Fig 9.3. (see the Book).

* solved e.g. represent the load-flow problem of a 2-bus system as follows:
(Fig. 9.3)



$$P_{2,cal} = \sum_{j=1}^2 |V_2| |V_j| |Y_{2j}| \cos(\delta_2 - \delta_j - \theta_{2j}) \dots \textcircled{1}$$

$$= |V_2| |V_1| |Y_{21}| \cos(\delta_2 - \delta_1 - \theta_{21}) + |V_2| |V_2| |Y_{22}| \cos(\delta_2 - \delta_2 - \theta_{22}) \dots \textcircled{2}$$

$$Y_{21} = -\frac{1}{j0.25} = 4 \times 90^\circ \dots \textcircled{2} \quad Y_{22} = \frac{1}{j0.25} = 4 \times -90^\circ \dots \textcircled{3}$$

• By sub. \textcircled{2} & \textcircled{3} into \textcircled{1}: $P_{2,cal} = 4 |V_1| |V_2| \sin \delta_2 \dots \textcircled{4}$

$$\Rightarrow g_1 = P_{2,cal} - P_{2,sch} = P_{2,cal} - (P_g - P_L) = P_{2,cal} - (0 - 0.6) = 4 |V_1| |V_2| \sin \delta_2 + 0.6$$

$$g_1(x_1, x_2, u) = 4 |V_1| |V_2| \sin \delta_2 + 0.6$$

Do the same thing By replacing $P_{2,cal}$ By $Q_{2,cal}$ & cos By sin in equ. \textcircled{1}.




$$\therefore \text{By Substituting: } Q_{2,cal} = 4 |V_2|^2 - 4 |V_2| |V_1| \cos \delta_2$$

$$\therefore g_2 = Q_{2,cal} - Q_{2,sch} = Q_{2,cal} - (0 - 0.3)$$

$$g_2(x_1, x_2, u) = 4 |V_2|^2 - 4 |V_1| |V_2| \cos \delta_2 + 0.3$$

\Rightarrow The Equations of g_1 & g_2 represent the power-flow equations with the unknowns: $x_2 = |V_2|$ & $x_1 = \delta_2$

* N.R Power Flow Solution:

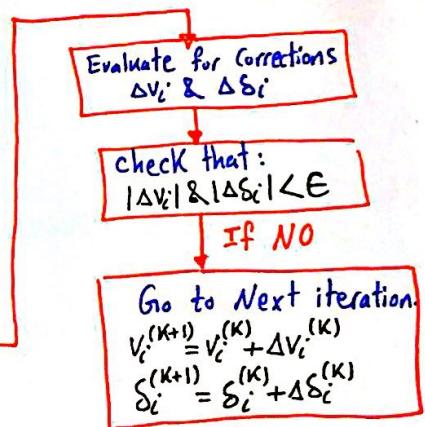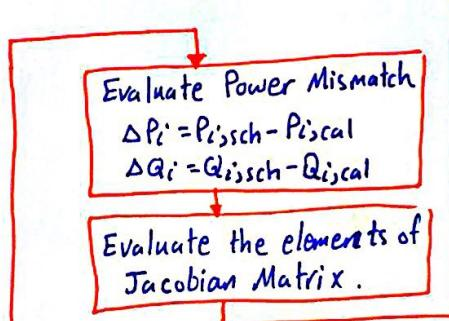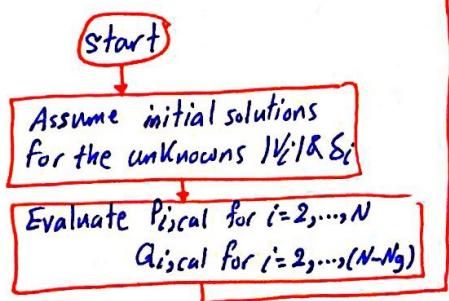

• As found before:

$$P_{i,cal} = \sum_{j=1}^N |V_i| |V_j| |Y_{ij}| \cos(\delta_i - \delta_j - \theta_{ij}) \dots \textcircled{1}$$

$$\Delta P_i = P_{i,sch} - P_{i,cal} \dots \textcircled{3}$$

$$Q_{i,cal} = \sum_{j=1}^N |V_i| |V_j| |Y_{ij}| \sin(\delta_i - \delta_j - \theta_{ij}) \dots \textcircled{2}$$

$$\Delta Q_i = Q_{i,sch} - Q_{i,cal} \dots \textcircled{4}$$

• To Formulate Jacobian Matrix:

Assume that there are 4-Buses where #1 is the "slack" & the other 3 buses are "load buses" or "PQ-buses."

$$\begin{bmatrix} \frac{\partial P_2}{\partial \delta_2} & \frac{\partial P_2}{\partial \delta_3} & \frac{\partial P_2}{\partial \delta_4} & \frac{\partial P_2}{\partial |V_{21}|} & \frac{\partial P_2}{\partial |V_{31}|} & \frac{\partial P_2}{\partial |V_{41}|} \\ \frac{\partial P_3}{\partial \delta_2} & \frac{\partial P_3}{\partial \delta_3} & \frac{\partial P_3}{\partial \delta_4} & \frac{\partial P_3}{\partial |V_{21}|} & \frac{\partial P_3}{\partial |V_{31}|} & \frac{\partial P_3}{\partial |V_{41}|} \\ \frac{\partial P_4}{\partial \delta_2} & \frac{\partial P_4}{\partial \delta_3} & \frac{\partial P_4}{\partial \delta_4} & \frac{\partial P_4}{\partial |V_{21}|} & \frac{\partial P_4}{\partial |V_{31}|} & \frac{\partial P_4}{\partial |V_{41}|} \\ \hline \frac{\partial Q_2}{\partial \delta_2} & \frac{\partial Q_2}{\partial \delta_3} & \frac{\partial Q_2}{\partial \delta_4} & \frac{\partial Q_2}{\partial |V_{21}|} & \frac{\partial Q_2}{\partial |V_{31}|} & \frac{\partial Q_2}{\partial |V_{41}|} \\ \frac{\partial Q_3}{\partial \delta_2} & \frac{\partial Q_3}{\partial \delta_3} & \frac{\partial Q_3}{\partial \delta_4} & \frac{\partial Q_3}{\partial |V_{21}|} & \frac{\partial Q_3}{\partial |V_{31}|} & \frac{\partial Q_3}{\partial |V_{41}|} \\ \frac{\partial Q_4}{\partial \delta_2} & \frac{\partial Q_4}{\partial \delta_3} & \frac{\partial Q_4}{\partial \delta_4} & \frac{\partial Q_4}{\partial |V_{21}|} & \frac{\partial Q_4}{\partial |V_{31}|} & \frac{\partial Q_4}{\partial |V_{41}|} \end{bmatrix} = \begin{bmatrix} \Delta S_2 \\ \Delta S_3 \\ \Delta S_4 \\ \Delta |V_{21}| \\ \Delta |V_{31}| \\ \Delta |V_{41}| \end{bmatrix} = \begin{bmatrix} \Delta P_2 \\ \Delta P_3 \\ \Delta P_4 \\ \Delta Q_2 \\ \Delta Q_3 \\ \Delta Q_4 \end{bmatrix}$$

59

$$\Rightarrow \begin{bmatrix} \Delta S_2 \\ \vdots \\ \Delta |V_{41}| \end{bmatrix} = [\mathbf{J}]^{-1} \begin{bmatrix} \Delta P_2 \\ \vdots \\ \Delta Q_4 \end{bmatrix}$$

Note: Elements of the Jacobian can be found from ① & ② as will be shown later on.

For simplification: each element say $\frac{\partial P_2}{\partial |V_{21}|} * \frac{|V_{21}|}{|V_{21}|}, \frac{\partial P_3}{\partial |V_{31}|} * \frac{|V_{31}|}{|V_{31}|}, \dots$ and so on.

$$v_i^{(k+1)} = v_i^{(k)} + \Delta v_i^{(k)} = v_i^{(k)} \left(1 + \frac{\Delta v_i^{(k)}}{v_i^{(k)}} \right)$$

↳ for J_{21} & J_{22} .

The following can be found:

$$\underline{\underline{J}}_{ii}: \frac{\partial P_i}{\partial \delta_j} = -|V_i| |V_j| |Y_{ij}| \sin(\theta_{ij} + \delta_j - \delta_i) \quad \text{"Non diagonal elements".} \quad \dots (9.52)$$

$$\frac{\partial P_i}{\partial \delta_i} = \sum_{n=1, n \neq i}^N |V_i| |V_n| |Y_{in}| \sin(\theta_{in} + \delta_n - \delta_i) \quad \text{"Diagonal elements".} \quad \dots (9.53)$$

$$\underline{\underline{J}}_{21}: \frac{\partial Q_i}{\partial \delta_j} = -|V_i| |V_j| |Y_{ij}| \cos(\theta_{ij} + \delta_j - \delta_i) \quad \text{"Non diagonal elements".} \quad \dots (9.55)$$

$$\frac{\partial Q_i}{\partial \delta_i} = \sum_{n=1, n \neq i}^N |V_i| |V_n| |Y_{in}| \cos(\theta_{in} + \delta_n - \delta_i) \quad \text{"Diagonal elements".} \quad \dots (9.56)$$

$$\underline{\underline{J}}_{12}: |V_j| \frac{\partial P_i}{\partial |V_{ij}|} = |V_j| |V_i| |Y_{ij}| \cos(\theta_{ij} + \delta_j - \delta_i) \quad \text{"Non diagonal elements".} \quad \dots (9.58)$$

$$|V_i| \frac{\partial P_i}{\partial |V_{ij}|} = P_i + |V_i|^2 G_{ii} \quad \text{"Diagonal elements".} \quad \dots (9.61)$$

where $Y_{ii} = G_{ii} + jB_{ii}$

$$\underline{\underline{J}}_{22}: |V_j| \frac{\partial Q_i}{\partial |V_{ij}|} = -|V_j| |V_i| |Y_{ij}| \sin(\theta_{ij} + \delta_j - \delta_i) \quad \text{"Non diagonal elements".} \quad \dots (9.62)$$

$$|V_i| \frac{\partial Q_i}{\partial |V_{ij}|} = Q_i - |V_i|^2 B_{ii} \quad \text{"Diagonal elements".} \quad \dots (9.63)$$

Note: in the case of PV-Bus, Then: there is NO correction for the voltage magnitude (i.e. $\Delta V=0$) - also G_2 is NOT Known. Hence ΔQ can NOT be calculated.

[60]

→ for example: in the previous system if Bus #1 slack, Bus #2 & 3 load buses, Bus #4 PV.

∴ In this case: $\Delta V_4 = 0$, and ΔQ_4 cannot be calculated.
therefore, in this case Eliminate 6th row & 6th column.

∴ Matrix (6x6) becomes (5x5).

∴ The order of J matrix $2N-N_g-2$

$$\text{in this e.g.: } \frac{2*4-1-2}{=5}$$

Example: Solve the previous system (e.g 9.2) By using N.R Method.

- Find order of J ?
 $2N-N_g-2 = 8-1-2 = 5 \quad \therefore \text{Jacobian} = 5 \times 5.$

- Express the Jacobian Matrix ?

$$\begin{bmatrix} \frac{\partial P_2}{\partial \delta_2} & \dots & \frac{\partial P_2}{\partial \delta_4} & \dots & \frac{\partial P_2}{\partial V_3} |V_3| \\ \vdots & & & & \\ \frac{\partial P_4}{\partial \delta_2} & \dots & \dots & \dots & \frac{\partial P_4}{\partial V_3} |V_3| \\ \vdots & & & & \\ \frac{\partial Q_2}{\partial \delta_2} & \dots & \dots & \dots & \frac{\partial Q_2}{\partial V_3} |V_3| \end{bmatrix} \begin{bmatrix} \Delta \delta_2 \\ \Delta \delta_3 \\ \Delta \delta_4 \\ \frac{\Delta |V_2|}{|V_2|} \\ \frac{\Delta |V_3|}{|V_3|} \end{bmatrix} = \begin{bmatrix} \Delta P_2 \\ \Delta P_3 \\ \Delta P_4 \\ \Delta Q_2 \\ \Delta Q_3 \end{bmatrix}$$

These called Flat start.

$$\text{assumed: } V_2^{(0)} = 1 \angle 0^\circ \\ V_3^{(0)} = 1 \angle 0^\circ$$

- Initial voltages or state variables: specified: $V_1^{(0)} = 1 \angle 0^\circ$
 $V_4^{(0)} = 1.02 \angle 0^\circ$

- Find initial mismatch at Bus 3 ?

$$\Rightarrow \Delta P_3^{(0)} \& \Delta Q_3^{(0)}$$

$$\Rightarrow \Delta P_3 = P_{3,sch} - P_{3,cal} \quad ; \quad P_{3,sch} = P_{3,gen} - P_{3,load} = 0 - 200 = -200 \text{ MW} = -2 \text{ PU.}$$

$$P_{3,cal} = \sum_{j=1}^N |V_3| |V_j| |Y_{3j}| \cos(\delta_3 - \delta_j - \theta_{3j}) \quad \text{By using the given [Ybus] matrix} \Rightarrow \text{find } Y_{31}, Y_{32}, Y_{33}, Y_{34}$$

$$\text{and substituting initial \& specified voltages: } P_{3,cal}^{(0)} = -0.0604731 \text{ PU.}$$

$$\therefore \Delta P_3^{(0)} = -2 + 0.0604731 \Rightarrow \boxed{\Delta P_3^{(0)} = -1.94} ; \text{initial mismatch.}$$

$$\Rightarrow \Delta Q_3 = Q_{3,sch} - Q_{3,cal} ; Q_{3,sch} = Q_{3,gen} - Q_{3,load} = 0 - 123.94 = -1.2394 \text{ PU.}$$

$$Q_{3,cal}^{(0)} = \sum_{j=1}^N |V_3| |V_j| |Y_{3j}| \sin(\delta_3 - \delta_j - \theta_{3j}) \Rightarrow \boxed{Q_{3,cal}^{(0)} = -0.4048696 \text{ PU.}}$$

$$\therefore \boxed{\Delta Q_3^{(0)} = -0.8345304 \\ \simeq -0.835}$$

⇒ By similar approach one can find $\Delta P_4, \Delta P_2 \& \Delta Q_2$.

Continue →

- * Find the element of the Jacobian?
- * for e.g.: Initial value of the element in 2nd row & 3rd column.
 ∵ The required element is: $\frac{\partial P_3}{\partial \delta_4}$ which is Non Diagonal element.
 $\Rightarrow \frac{\partial P_3}{\partial \delta_4} \triangleq -|V_3||V_4| |Y_{34}| \sin(\theta_{34} + \delta_4 - \delta_3)$ By sub. $\boxed{\frac{\partial P_3}{\partial \delta_4} = -15.42}$
- * Initial value of the element in 5th row & 5th column.
 $\therefore \text{element} = |V_3| \frac{\partial G_3}{\partial |V_3|} \triangleq G_{23} - |V_3|^2 B_{33} \Rightarrow \boxed{|V_3| \frac{\partial G_3}{\partial |V_3|} = 40.459}$
 transmitted "calculated" $\hookrightarrow Y_{bus}$ matrix.
- ⇒ The same procedure can be repeated to find all elements of $[J]$.

∴ Now one can proceed to calculate voltages:

⇒ Calculate corrections, repeat iterations

Until ΔP & $\Delta Q < \epsilon$

OR $|V_i^K - V_i^{K-1}| < \epsilon$.

$$\begin{bmatrix} \Delta S_2 \\ \Delta S_3 \\ \Delta S_4 \\ \frac{\Delta V_2}{|V_2|} \\ \frac{\Delta V_3}{|V_3|} \end{bmatrix} = \left[\begin{smallmatrix} \frac{\partial S_2}{\partial J} & \dots \\ \dots & \ddots \\ \dots & \dots \\ \frac{\partial S_3}{\partial J} & \dots \\ \dots & \dots \\ \frac{\partial S_4}{\partial J} & \dots \\ \dots & \dots \end{smallmatrix} \right]^{-1} \begin{bmatrix} \Delta P_2 \\ \Delta P_3 \\ \Delta P_4 \\ \Delta Q_2 \\ \Delta Q_3 \end{bmatrix}$$

Elements of Jacobian Matrix are shown @ the top of Page 355.

The results of this analysis are shown in Figures 9.4 ⇒ Table.

9.5 ⇒ Results on single-line diagram.

Fig. 9.4

Bus No.	$ V $	δ (deg)	Gen		Load	
			P	Q	P	Q
1	1	0	186.81	114.5	50	30.94
2	0.982	-0.976	0	0	170	105.35
3	0.969	-1.872	0	0	200	123.94
4	1.02	1.523	318	181.43	80	49.58

These calculated voltages
can be used to find Any unknowns.

found from
 $Q = P \tan[\cos^{-1} pf]$

also P_G, Q_G, G_{2G_4}
found as shown
in the coming analysis.

• Comment: Having Calculated the voltages at busbars, then one can:

- 1) Find $S_G = P_G + jQ_G$ @ the slack bus.
- 2) Find G_{ij} at PV bus.
- 3) Line flow.
- 4) Any Violated Variable.

1) * Slack Bus: $S_G = S_i + S_D$ → Demand or Load at the busbar.
 power transmitted or calculated
 @ the Busbar.

Continue...

$$S_1 = P_{1, \text{cal}} + j Q_{1, \text{cal}}$$

62

By using $P_i = \sum_{j=1}^N |V_i| |V_j| |Y_{ij}| \cos(\delta_i - \delta_j - \theta_{ij})$, where $i=1$ in case of slack Bus.

By using the results in Fig 9.4 $\Rightarrow V_1 = 1 \angle 0^\circ$, $V_2 = 0.982 \angle -0.976^\circ$, $V_3 = 0.969 \angle -1.872^\circ$, $V_4 = 1.02 \angle 1.523^\circ$ and in Table 9.2 of $[Y_{\text{bus}}]$ matrix.

P_D was given: $P_D = 50 \text{ MW}$.

$$\Rightarrow P_1 = 1.36 \text{ PU} = 136 \text{ MW} \quad \Rightarrow P_G = 136 + 50 = 186 \text{ MW}$$

- Similarly one can calculate Q_1 , it can be found: $Q_1 = 83.51 \text{ MVAR}$.

$$Q_D = 30.99 \text{ MVAR} \quad \therefore Q_{G1} = Q_1 + Q_D = 114.5 \text{ MVAR}$$

2)


* PV Bus #4: By Calculations:

$$Q_{G1} = Q_4 + Q_D \rightarrow Q_D = 49.58 \text{ MVAR} \\ Q_4 = 131.85 \text{ MVAR} \quad \therefore Q_{G1} = 181.43 \text{ MVAR}$$

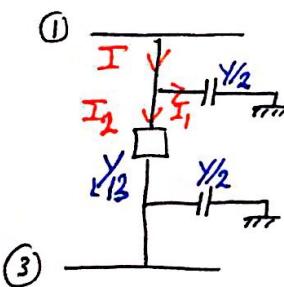
3)

* Line Flow:

Consider for e.g. Line between buses 1 & 3 as shown in Fig 9.5:



use π -equivalent
of the T.L.

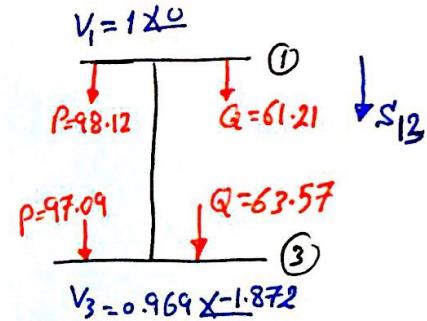

$$\therefore I = I_1 + I_2 = V_1 \frac{Y}{Z} + (V_1 - V_3) Y_{L13} \quad ; \quad Y_2 \text{ and } Y_{L13} \text{ deduced from input DATA of the Line.}$$

Solving: $I = 1.165 \angle -32.1^\circ \text{ PU}$.

$$Y_{L13} = \frac{1}{Z_{L13}}$$

$$\therefore S_{13} = V_1 I^* = 0.987 + j0.619 \text{ PU} \Rightarrow (S_{13} = 98.7 + j61.9) \text{ MVA.}$$

- By similar approach one can find S entering Bus #3.

- Having calculated Power flow in the lines, one can calculate losses in the lines.

For e.g.: for the Line (1-3) $S_{\text{losses}} = [98.12 + j61.21] - [97.09 + j63.57]$

$$\Rightarrow S_{\text{losses}} = 1.03 - j2.36 \text{ MVA.}$$

- By summation over all lines, one can find the losses in the system.

Continue...

4) * Violated Conditions:

- The power flow study under the Normal or forecast Conditions is Called "Base Study".
- Check for any violations, here in the input DATA:
 - i) Specify Tolerance for voltage e.g $\pm 5\%$. $\Rightarrow V_{\text{accepted}} = 1 \pm 0.05 = 0.95 \rightarrow 1.05$
In our 4-bus system; There were No-Voltage Violations.
 - ii) $P_{\min} \leq P_G \leq P_{\max}$, In our example; limits were NOT specified.
 $Q_{\min} \leq Q_G \leq Q_{\max}$
 - iii) Capacity of Lines, for e.g MVA.

* If there is any violation, perform "Sensitivity Analysis".

for example: ① Adding Lines. ② Modifying Loads.


* * * * * * Direct Determination of Z_{bus} Matrix: "see the Book page 301/section 8.4."

1) Number the Busbars & Branches of the given Network.

- A Branch could be between a busbar & the Ref. or between 2 busbars.

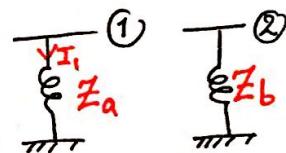2) Start by writing an equation for bus #1 which a branch connected to Ref with impedance $\equiv Z_a$: $\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = [Z_a] \begin{bmatrix} I_1 \end{bmatrix}$

This equation can be considered as 3matrices, each one is of the order (1×1) .



3) Now one may add a new bus connected to first bus or to the Ref.

for e.g: let the second bus connected to Ref. through impedance $\equiv Z_b$


Then one have the following matrix equations: $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_a & 0 \\ 0 & Z_b \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$

This matrix called Original Matrix, To be modified by adding one Branch at a time.

3) One may proceed to modify the original matrix by adding other buses & branches following the procedures. [see 8.4/294]
which may be:

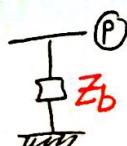3.1 Adding Z_b from a new bus (P) to the ref. Node as follows:

$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_K \\ V_P \end{bmatrix} = \begin{bmatrix} Z_{\text{original}} & Z_a & 0 \\ \dots & \dots & \dots \\ Z_{\text{zeros}} & 0 & Z_b \end{bmatrix} \begin{bmatrix} I_1 \\ I_K \\ \vdots \\ I_P \end{bmatrix} \dots \quad (3.1)$$



Continue...


3.2 Adding Z_b from a new bus (P) to an existing bus (K)

64]

Then the matrix will be as follows:

$$\begin{bmatrix} V_1 \\ \vdots \\ V_K \\ \vdots \\ V_P \end{bmatrix} = \begin{bmatrix} Z_{\text{original}} & \begin{matrix} Z_{1K} \\ Z_{2K} \\ \vdots \\ Z_{KK} \\ \vdots \\ Z_{PK} \end{matrix} \\ \begin{matrix} Z_{1K} \\ Z_{2K} \\ \vdots \\ Z_{KK} \\ \vdots \\ Z_{PK} \end{matrix} & \begin{bmatrix} I_1 \\ \vdots \\ I_K \\ \vdots \\ I_P \end{bmatrix} \end{bmatrix} \quad \dots \quad (3.2)$$

elements of the original matrix.

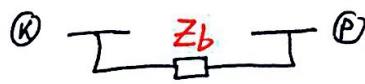

Z_{KK} ≡ Element of the the original Matrix.

3.3 Adding Z_b from existing bus (K) to a Ref. Node:

a) Create a new row & a new column exactly as in (3.2).

b) Eliminate the ($N+1$) row & the ($N+1$) column, To find each element Z_{hi} (new) in the new Matrix as follows:

$$Z_{hi}(\text{new}) = Z_{hi}(\text{old}) - \frac{Z_{h(N+1)} * Z_{(N+1)i}}{Z_{KK} + Z_b} \quad \dots \quad (3.3)$$

($N+1$) is the new row or column.

3.4 Adding Z_b between two existing buses (j) & (K):

• Formulate the following matrix:

$$\begin{bmatrix} V_1 \\ \vdots \\ V_p \end{bmatrix} = \begin{bmatrix} Z_{\text{original}} & \begin{matrix} \text{col. } j - \text{col. } K \\ \text{Row. } j - \text{Row. } K \end{matrix} \\ \begin{matrix} \text{col. } j - \text{col. } K \\ \text{Row. } j - \text{Row. } K \end{matrix} & \begin{bmatrix} I_1 \\ \vdots \\ I_p \end{bmatrix} \end{bmatrix} \quad \text{where: } Z_{bb} = Z_{jj} + Z_{KK} - 2Z_{jk} + Z_b \quad \dots \quad (3.4)$$

found from original matrix.

• Modify the produced matrix by using: $Z_{hi}(\text{new}) = Z_{hi}(\text{old}) - \frac{Z_{h(N+1)} * Z_{(N+1)i}}{Z_{bb}}$... (3.5)

original.

Example: Find Z_{bus} for the given system shown in Fig.1 By using the Building Algorithm?

Note: Subscript is used for Z_{bus} at each step:

1) Starting with Bus 1 $\Rightarrow Z_{bus1} = [j1.25]$.

Note: all elements have j so it will not be written in the following steps.

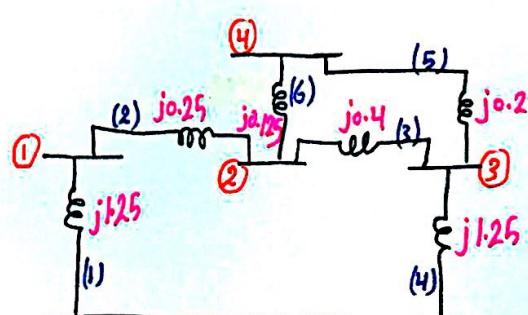


Fig.1.

① ≡ Bus No.

(2) ≡ Branch No.

Continue ...

2) Go to bus ② with its impedance of $j0.25$.

$$\Rightarrow Z_{bus2} = \begin{bmatrix} 1.25 & 1.25 \\ 1.25 & 1.25+0.25 = 1.5 \end{bmatrix}$$

3) Bus ③ with impedance $j0.4$ is connected to Bus ②.

$$\Rightarrow Z_{bus3} = \begin{bmatrix} 1.25 & 1.25 & 1.25 \\ 1.25 & 1.5 & 1.5 \\ 1.25 & 1.5 & 1.5+0.4=1.9 \end{bmatrix} \quad \text{Z}_{\text{original}} \quad 3 \times 3$$

4) If one decide to add impedance $Z_b = j1.25$ from Bus ③ to Ref.

Then one follow equation 3.2 to connect a new bus ④ to obtain the following matrix:

$$\begin{bmatrix} 1.25 & 1.25 & 1.25 & | & 1.25 \\ 1.25 & 1.5 & 1.5 & | & 1.5 \\ 1.25 & 1.5 & 1.9 & | & 1.9 \\ 1.25 & 1.5 & 1.9 & | & 3.15 \end{bmatrix} \rightarrow Z_{33} + Z_b = 1.9 + 1.25 = \underline{\underline{3.15}}$$

The created new column & new row: By using equation 3.3 :

$$Z_{hi}(\text{new}) = Z_{hi}(\text{old}) - \frac{Z_h(N+1) Z_{(N+1)i}}{Z_{KK} + Z_b}$$

$$\text{for e.g.: } Z_{11} \xleftarrow[i=1]{h=1} \Rightarrow N=3, K=3 \quad \therefore Z_{11}(\text{new}) = Z_{11}(\text{old}) - \frac{Z_{14} Z_{41}}{Z_{33} + Z_b}$$

$$\Rightarrow Z_{11}(\text{new}) = 1.25 - \frac{(1.25)*(1.25)}{1.9 + 1.25} \Rightarrow \underline{\underline{Z_{11}(\text{new}) = 0.75397}}$$

* The same procedure can be repeated for the elements $Z_{12}, Z_{13}, Z_{21}, Z_{22}, Z_{23}$, Z_{31}, Z_{32}, Z_{33} .

\Rightarrow To Give:

$$\begin{bmatrix} 0.75397 & \dots & 0.49603 \\ \vdots & & \vdots \\ 0.49603 & \dots & 0.75397 \end{bmatrix} \quad \text{Z}_{\text{original}} \quad 3 \times 3$$

$\underbrace{}_{3 \times 3 \text{ matrix.}}$

5) One may now add impedance $Z_b = j0.2$ from Bus ③ to Bus ④.

$$Z_{bus6} = \begin{bmatrix} \text{Original} & \begin{bmatrix} 0.49603 \\ 0.59524 \\ 0.75397 \end{bmatrix} \\ \hline - & \begin{bmatrix} 0.49603 & 0.59524 & 0.75397 & 0.75397 \end{bmatrix} \end{bmatrix} \rightarrow Z_{33} + Z_b = 0.75397 + 0.2 = \underline{\underline{0.95397}}$$

Continue...

6). Finally one add impedance $Z_b = j0.125$ between ② & ④.

$$Z'_{bus,6} = \begin{bmatrix} Z_{bus,6} \\ \vdots \\ Z_{55} \end{bmatrix} ; \text{ where: } Z_{55} = Z_{22} + Z_{44} - 2Z_{24} + Z_b \\ \text{Col. 2} \\ \text{Col. 4} \\ \text{of} \\ Z_{bus,6} \\ \text{Row 2-Row 4 of} \\ Z_{bus,6} \end{matrix}$$

$$\Rightarrow \underline{\underline{Z_{55} = 0.67421}}$$

* Eliminate the 5th row & 5th column By using equation (3.5):

$$Z_{hi}(\text{new}) = Z_{hi}(\text{old}) - \frac{Z_{h(N+1)} Z_{(N+1)i}}{Z_{bb}} ; Z_{bb} = Z_{55}.$$

for e.g: $Z_{11}(\text{new}) = 0.7166$

⇒ Finally the Z_{bus} will be as follows:

$$Z_{bus} = j \begin{bmatrix} 0.7166 & \dots & 0.5805 \\ \vdots & & \vdots \\ 0.5805 & \dots & 0.7631 \end{bmatrix} \text{ 4x4 Matrix.}$$

* * *
End of Material
* * *

Best Luck.
* * of * *
* * *