

#	Name
1	31 (31)
2	14 (14)
3	5 (11)
4	19 (21)
5	13 (13)
S.M	82 (90)

27
70

University of Jordan

Electrical Eng. Dept

EE 0933481 Power Systems (1)

Time: 75 minutes

الاسم: مهندس احمد رقمان رقم التفاصيل (30) رقم الجامعي 0144235

Second Exam.

29-11-2017

Q1) The Z_{bus} matrix of a given network with values in PU is as follows:

$$Z_{bus} = j \begin{bmatrix} 0.69 & 0.61 & 0.55 & 0.60 \\ 0.61 & 0.73 & 0.63 & 0.69 \\ 0.55 & 0.63 & 0.69 & 0.64 \\ 0.60 & 0.69 & 0.64 & 0.71 \end{bmatrix}$$

a-Evaluate Z_{th} between buses 3 and 4. [6]

$$\begin{aligned} Z_{th}^{34} &= Z_{33} + Z_{44} - 2Z_{34} = j0.69 + j0.71 - 2(j0.64) \\ &\Rightarrow Z_{th}^{34} = j0.12 \end{aligned}$$

b-If a balanced 3-ph fault occur on Bus 1, evaluate the amount of fault current which would flow in the line between buses 2 and 4 if the line admittance is $-j4$ pu.

$$I_{24} = \frac{V_2 - V_4}{Z_b}, \text{ where } Z_b = \text{impedance of the branch} = \frac{1}{-j4} = j0.25 \text{ pu}$$

$$Z_b = j0.25 \quad (2)$$

$$\begin{aligned} V_2 &= V_f \left(1 - \frac{Z_{21}}{Z_{11}}\right) \\ &= 1 \times \left(1 - \frac{j0.61}{j0.69}\right) \Rightarrow V_2 = 0.1159 \text{ pu} \quad (3) \end{aligned}$$


$$\begin{aligned} V_4 &= V_f \left(1 - \frac{Z_{41}}{Z_{11}}\right) \\ &= 1 \times \left(1 - \frac{j0.6}{j0.69}\right) \Rightarrow V_4 = 0.1304 \text{ pu} \quad (4) \end{aligned}$$

Now sub. (2), (3) & (4) into (1) & solving:

$$I_{24} = 0.058 \times 90^\circ \text{ pu} \quad \#$$

c-If an industrial consumer is to be connected to bus 2, what would be the S/C MVA supplied by the power company to the consumer. [5]

$$I_{SC(PU)} = \frac{1}{Z_{th}}, \quad I_{SC(PU)} = S/CMVA(PU) \quad \text{so} \quad S/CMVA = \frac{1}{|Z_{th}|}, \quad Z_{th} = Z_{22} = j0.73 \Rightarrow S/CMVA = -j1.37$$

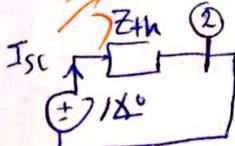

d-If a 25 MVA, 13.8 kV generator is the only source in the network and connected to bus 1 through a circuit breaker and the Z_{bus} includes the generator reactance. The circuit breaker at its maximum voltage of 16 kv has rated s/c interrupting current of 10 kA and K=1.3, is this breaker suitable when a balanced 3-ph fault occur on bus 1. [12]

$$\begin{aligned} \text{Max } V &= 16 \text{ KV} \rightarrow I_{SC} = 10 \text{ KA} \\ K &= 1.3 \end{aligned}$$

Behind
the page.
directly.

Q. 1 (d)

This CB To be selected it must satisfy the followings
① voltage of the system must be within the range of operating voltage of the CB.

$$K = 1.3 = \frac{V_{max}}{V_{min}} \quad \text{so} \quad V_{min} = \frac{16K}{1.3} \Rightarrow V_{min} = 12.31 \text{ Kvolt}$$

so the range as follows: 12.31 Kvolt - 16 Kvolt.

⇒ and we were given that the voltage of the system is 13.8 Kvolt which is within the range.
* Condition ① satisfied

② The calculated fault current ≤ 0.8 rated s/c current @ that voltage (i.e 13.8 Kvolt)

$$I_f = \frac{V_F}{Z_{11}} \quad (\text{since it is on Bus 1})$$

$$\Rightarrow I_f = \frac{13.8}{j0.69} = 1.4493 \times -90^\circ \text{ PU.}$$

$$\text{The base current @ bus 1 given by: } I_B = \frac{25 \times 10^6}{\sqrt{3} \times 13.8 \times 10^3} \Rightarrow I_B \approx 1046 \text{ A.}$$

$$\text{so } |I_f|_{\text{calculated}} = (1.4493)(1046) \Rightarrow I_{\text{cal.}} \approx 1516 \text{ A}$$

Now as the rated s/c current can be found as follows:

$$I_{s/c} * \text{voltage} = \text{Constant}$$

$$\text{so } I_{s/c} * 13.8K = 16K * 10K \Rightarrow I_{s/c} \approx 11594 \text{ A}$$

$$\text{Now } 0.8 * 11594 = 9275.2$$

$$\text{so } I_{\text{cal.}} = 1516 \leq 9275.2$$

so condition ② satisfied.

* This CB is suitable to be used. #

for each Km

$$L_{aa} = \frac{0.002 \text{ mH}}{1000 \text{ m}} \times 1000 = \underline{\underline{2 \text{ mH/Km}}}$$

Q2) A 60 Hz transmission line has the following parameters:

$L_{aa} = 0.002 \text{ mH/m}$, $Z_1 = j 0.524 \Omega/\text{km}$, $Z_0 = j 1.847 \Omega/\text{km}$, $Z_{an} = 0.0$

a-Evaluate the self inductance of the Neutral line. [7]

b-Evaluate the mutual inductance between phase conductors. [7]

a) $Z_0 = Z_S + 2Z_m$; $Z_S = Z_{aa} + 2Z_{an} + Z_{nn}$ & $Z_m = Z_{ab} - 2Z_{an} + Z_{nn}$.

so $Z_0 = Z_{aa} + 2Z_{ab} - 6Z_{an} + 3Z_{nn} = j1.847$.

b) $Z_1 = Z_S - Z_m = Z_{aa} - Z_{ab} = j0.524 = j(120\pi)(2m) - Z_{ab}$.

$\Rightarrow Z_{ab} = j0.23 = j\omega L \Rightarrow L_{ab} = \frac{0.23}{2\pi \times 60} \Rightarrow L_{ab} = 0.61 \text{ mH/Km}$

: mutual between
phase conductors.

Back to part (a):

$$j1.847 = j(120\pi)(2m) + 2(j0.23) + 3Z_{nn}$$

$$\Rightarrow 3Z_{nn} = j0.633 \quad \text{so } j\omega L_{nn} = j\frac{0.633}{3} \Rightarrow L_{nn} = \frac{0.633}{2\pi \times 60} (3)$$

$L_{nn} = 0.56 \text{ mH/Km}$ $\Rightarrow L_{nn} = 1.679 \text{ mH/Km}$

\Rightarrow mutual of Neutral line.

Q3) Derive the expression of Complex Power in terms of Symmetrical Components.

[11]

$S = 3V_a I_a^*$

$+ V_b I_b^*$

$+ V_c I_c^*$

$= V_a = V_a^{(0)} + V_a^{(1)} + V_a^{(2)}$

$I_a^* = I_a^{(0)} + I_a^{(1)} + I_a^{(2)}$

$\Rightarrow S = 3[V_a^{(0)} + V_a^{(1)} + V_a^{(2)}] \cdot [I_a^{(0)} + I_a^{(1)} + I_a^{(2)}]$

S could be written as follows: $S = 3E$

Behind the
Page.
directly.

Q3

The Complex Power in 3ϕ system is given by:

$$\sum_{3\phi} = V_{an} I_{an}^* + V_{bn} I_{bn}^* + V_{cn} I_{cn}^*$$

$$= [V_{an} \ V_{bn} \ V_{cn}] \cdot \begin{bmatrix} I_{an}^* \\ I_{bn}^* \\ I_{cn}^* \end{bmatrix}$$

$$= \begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix}^T \cdot \begin{bmatrix} I_{an} \\ I_{bn} \\ I_{cn} \end{bmatrix}^*$$

Now Converting To Symmetrical Components.

$$= [A]^T \begin{bmatrix} V^{(0)} \\ V^{(1)} \\ V^{(2)} \end{bmatrix}^T \cdot [A]^* \begin{bmatrix} I^{(0)} \\ I^{(1)} \\ I^{(2)} \end{bmatrix}^*$$

Now we can note that: $[A]^T = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}^T = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} = [A]$

also $[A]^* = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}^* = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \Rightarrow [A^{-1}] \times 3$

$\Rightarrow \text{So Now } \sum = [A]^T \begin{bmatrix} V^{(0)} \\ V^{(1)} \\ V^{(2)} \end{bmatrix}^T \cdot [A^{-1}] \begin{bmatrix} I^{(0)} \\ I^{(1)} \\ I^{(2)} \end{bmatrix}^*$

$\Rightarrow [A][A^{-1}] = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} = \begin{bmatrix} 3 & 0 & 0 \\ 0 & 3 & 0 \\ 0 & 0 & 3 \end{bmatrix} = 3 \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = 3 I_n$

so, \sum becomes: $\sum = 3 \begin{bmatrix} V^{(0)} \\ V^{(1)} \\ V^{(2)} \end{bmatrix}^T \begin{bmatrix} I^{(0)} \\ I^{(1)} \\ I^{(2)} \end{bmatrix}^*$

$$\Rightarrow \sum = 3 V^{(0)} I^{(0)*} + 3 V^{(1)} I^{(1)*} + 3 V^{(2)} I^{(2)*} \quad (\text{VA})$$

#

Q4) Fig. 1 shows a pu sequence network for a given power system.

19
21


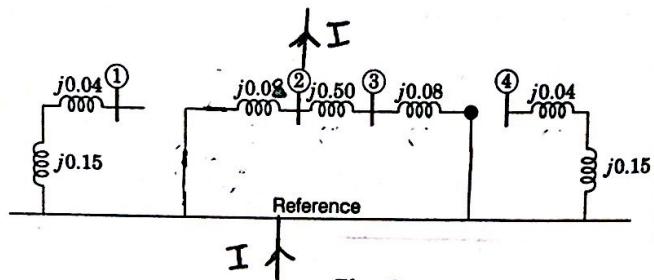


Fig. 1

a-What is the type of this sequence.

~~Zero-seq-Network~~ [since the Neutral impedance is shown] & the connection of Transform tells that.

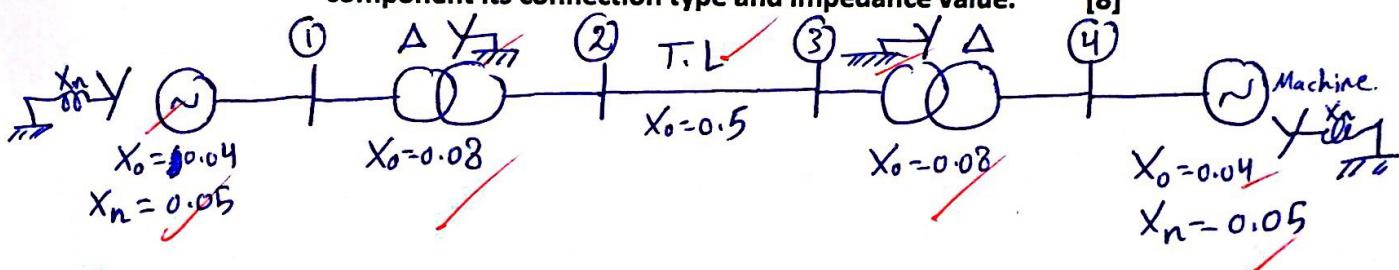b-Draw the corresponding single Line Diagram showing on each component its connection type and impedance value. [8]



c-If $I = -j1.9$ pu, find the value of the corresponding Sequence Voltage.

The fault occur @ busbar ②. [11]

so Z_0 represent the thevenin eqn. seen by bus ② & Ref.

$$\text{as follows: } Z_0 = (j0.08) // (j0.5 + j0.08)$$

$$\Rightarrow Z_0 = j0.0703 \quad \text{--- (1)}$$


$$I = -j1.9 = 3 I^{(0)} \Rightarrow \text{so } I^{(0)} = 0.633 \times -90^\circ \quad \text{--- (2)}$$

The eqn. zero-seq Network for a fault @ busbar ② is given by:

$$\text{so } V^{(0)} = -I^{(0)} Z_0 \quad \text{--- (3)}$$

Now sub. (1) & (2) into (3) gives:
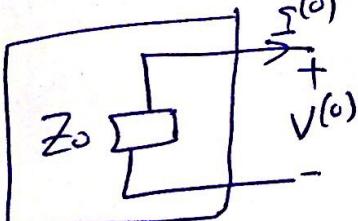
$$V^{(0)} = - (0.633 \times -90^\circ) (j0.0703) \Rightarrow V^{(0)} = -0.0445 \quad \text{pu}$$



1.37
= 1.37
PV.


Q5) Let the Z_{bus} in (Q1) represent $Z_{bus}^{(2)}$ of a given power system. If a line-to-line fault occur at Bus 4 with $Z_f = 0$. By drawing the corresponding connection between sequence networks, evaluate the phase fault currents. [13]

First we have to find Z_0 , Z_1 & Z_2 :

$$13 \quad Z_1 = Z_2 = Z_{44} = j0.71 \text{ PV}$$

Z_0 (we don't care to its value since it would be O/C).

Now the Connection would be as follows:

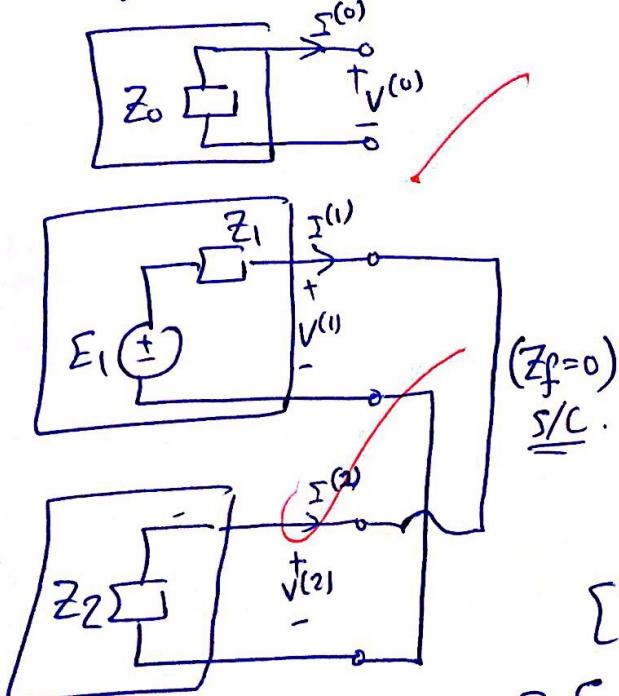

$$I^{(0)} = V^{(0)} = 0$$

$$I^{(1)} = \frac{E_1}{Z_1 + Z_2}$$

$$I^{(1)} = \frac{1 \times 0}{j0.71 + j0.71} \Rightarrow I^{(1)} = 0.7042 \times 90^\circ \text{ A}$$

$$I^{(2)} = -I^{(1)}$$

$$\Rightarrow I^{(2)} = 0.7042 \times 90^\circ \text{ A}$$

$$[I_{abc}] = [A] [I_{12}]$$

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 0.7042 \times 90^\circ \\ 0.7042 \times 90^\circ \end{bmatrix} = \begin{bmatrix} 0 \\ 1.2197 \times 180^\circ \\ 1.2197 \times 0^\circ \end{bmatrix}$$

so

$I_a = 0 \text{ PU}$

$I_b = 1.2197 \times 180^\circ \text{ PU}$

$I_c = 1.2197 \times 0^\circ \text{ PU}$

#