

Power System  
Analysis (I)


Dr. Daifallah Dalabeih

[dalabeih@ju.edu.jo](mailto:dalabeih@ju.edu.jo)

Fall 2017-2018

Notebook.

By. Mohammad  
Abu Hashya.

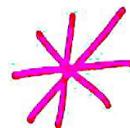

# Power System Analysis (1)

1

## Summary for Laws.

- \* Bus Admittance Matrix: element  $y_{ii} = \sum$  of admittance connected directly to  $i$ th busbar.  
element  $y_{ij} = -1 \times$  Admittance between  $i$ th &  $j$ th busbars.

- \* Bus Impedance Matrix:  $[Z] = [Y]^{-1}$

- \* Reflection  $\rightarrow$  To (a) side ( $\times a^2$ ). for impedances.  
 $\rightarrow$  To (1) side ( $/ a^2$ ).

- $a_{\text{eff}} =$  line Voltage Ratio.
- $X_{\text{new}} = X_{\text{old}} \times \left(\frac{S_{\text{new}}}{S_{\text{old}}}\right) \times \left(\frac{V_{\text{old}}}{V_{\text{new}}}\right)^2$

- Fault Current:  $I_f = |E| \frac{1}{x} + |E| \left(\frac{1}{x'} - \frac{1}{x}\right) e^{-t/\tau'} + |E| \left(\frac{1}{x''} - \frac{1}{x'}\right) e^{-t/\tau''}$

where:  $|E|$  RMS & phase.

$$\frac{I_a}{\sqrt{2}} = \frac{|E|}{x}, \quad \frac{I_b}{\sqrt{2}} = \frac{|E|}{x'}, \quad \frac{I_c}{\sqrt{2}} = \frac{|E|}{x''}$$

- \* for  $\Delta$ -Y connection  $\Rightarrow$  phase shift  $\rightarrow$  +ve seq.: HV leads by  $30^\circ$   
 $\rightarrow$  -ve seq.: LV leads by  $30^\circ$


- \* Transmission Line:  $R_{dc} = \frac{\rho L}{A}$ ,  $R_{ac}$  found from Tables.

- for Equilateral Lines:  $L = 2 \times 10^{-7} \ln\left(\frac{D}{D_s}\right)$ ,  $C = \frac{2\pi\epsilon}{\ln\left(\frac{D}{r}\right)}$   
H/m, F/m

- Voltage Regulation:  $VR\% = \frac{|V_{R,NL}| - |V_{R,FL}|}{|V_{R,FL}|} \times 100\%$


where  $|V_{R,NL}| = \frac{|V_s|}{|A|}$

• Short Line:

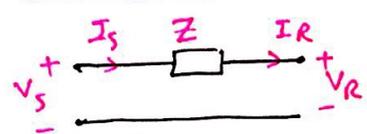


$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

• Medium Line:

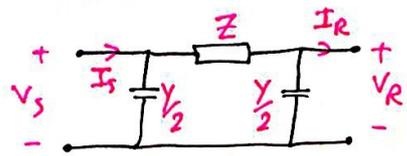

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 + \frac{ZY}{2} & Z \\ Y + \frac{ZY^2}{4} & 1 + \frac{ZY}{2} \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

• Long Line:

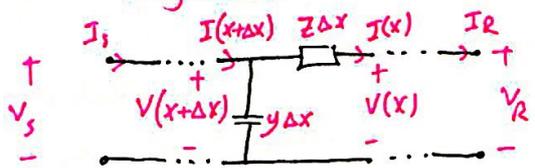


$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} \cosh \gamma L & Z_c \sinh \gamma L \\ \frac{1}{Z_c} \sinh \gamma L & \cosh \gamma L \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

$\gamma = \sqrt{ZY}$  ,  $Z_c = \sqrt{\frac{Z}{Y}}$  ,  $\gamma = \alpha + j\beta$

\* Surge Impedance:  $R=0$  ,  $Z_c = \sqrt{L/C}$

\* Surge Impedance Loading:  $SIL = P = \frac{V^2}{\sqrt{L/C}}$  ,  $R = \sqrt{L/C}$  connected at the load.

\*  $\pi$ -cct for Long T.L:

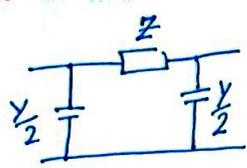

$Z = Z_c \sinh \gamma L$   
 $\frac{Y}{2} = \frac{\cosh \gamma L - 1}{Z} = \frac{1}{Z_c} \tanh\left(\frac{\gamma L}{2}\right)$

\* Power flow in T.L:

$$S = \frac{|V_r||V_s|}{|B|} \angle \beta - \delta - \frac{|A||V_r|^2}{|B|} \angle \beta - \alpha$$

$$P = \frac{|V_r||V_s|}{|B|} \cos(\beta - \delta) - \frac{|A||V_r|^2}{|B|} \cos(\beta - \alpha)$$

$$Q = \frac{|V_r||V_s|}{|B|} \sin(\beta - \delta) - \frac{|A||V_r|^2}{|B|} \sin(\beta - \alpha)$$

$$P_{max} = \frac{|V_r||V_s|}{|B|} - \frac{|A||V_r|^2}{|B|} \cos(\beta - \alpha)$$

→ @  $\delta = \beta$  & Leading Pf.

- series compensation factor  $\equiv \frac{X_c}{X_L}$
- Shunt Compensation factor  $\equiv \frac{B_L}{B_C}$

\* Parameters of Compensation:

• Series: 
$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & X_c \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$


• Parallel: 
$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{1}{X_L} & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$



\* end of first material \*

\* Balanced Fault:

Method (1):

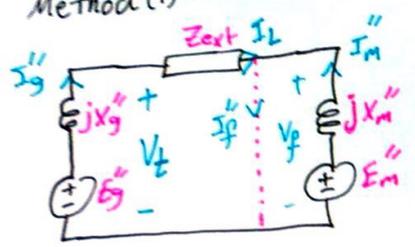

for  $E_g''$  &  $E_m''$  found from:  $E_g'' = V_t + I_L jX_g''$   
 (before fault)  $E_m'' = V_t - I_L (Z_{ext} + jX_m'')$

for  $V_f$ :  $V_f = V_t - I_L Z_{ext}$


for  $I_g''$  &  $I_m''$ :

$$I_g'' = I_L + \frac{V_f}{Z_{ext} + jX_g''} = \frac{E_g''}{Z_{ext} + jX_g''}$$

$$I_m'' = -I_L + \frac{V_f}{jX_m''} = \frac{E_m''}{jX_m''}$$

$I_f'' = I_g'' + I_m''$

Method (2):

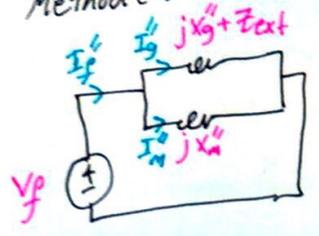

$$V_{th} = V_f$$

$$Z_{th} = (jX_m'') // (jX_g'' + Z_{ext})$$

$$I_f'' = V_{th} / Z_{th}$$

\* Fault Calculations using Zbus Method:

• for 3-ph fault @ bus k:

$$I_f'' = \frac{V_f}{Z_{kk}}$$

where:

$$\begin{bmatrix} V_1' \\ V_2' \\ V_3' \\ V_4' \end{bmatrix} = \begin{bmatrix} V_f \\ V_f \\ V_f \\ V_f \end{bmatrix}$$


• New Voltages are:  
 (assume fault @ bus 2)

$$\begin{bmatrix} V_1' + \Delta V_1 \\ 0 \\ V_3' + \Delta V_3 \\ V_4' + \Delta V_4 \end{bmatrix}$$

and:

$$\begin{bmatrix} \Delta V_1 \\ \Delta V_2 \\ \Delta V_3 \\ \Delta V_4 \end{bmatrix} = \begin{bmatrix} -I_f'' Z_{12} \\ -V_f \\ -I_f'' Z_{32} \\ -I_f'' Z_{42} \end{bmatrix} = \begin{bmatrix} -V_f Z_{12}/Z_{22} \\ -V_f \\ -V_f Z_{32}/Z_{22} \\ -V_f Z_{42}/Z_{22} \end{bmatrix}$$

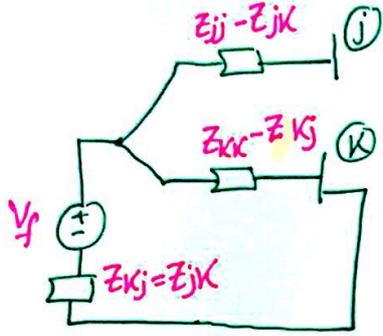
\* Fault Calculations using  $Z_{bus}$  Equ. cct :




- Before fault:  $V_f = V_k = V_j$
- After fault:  $I_f'' = V_f / Z_{kk}$   
 $V_j = V_f - I_f'' Z_{kj}$

• To find any current flowing in any Branch :  
 $I_{ij} = \frac{V_i - V_j}{Z_b}$  → impedance of that Branch.

\* Fault 3-ph Balanced on T.L :

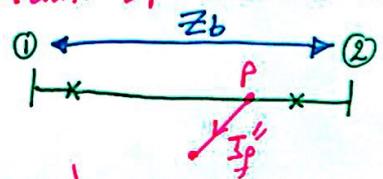

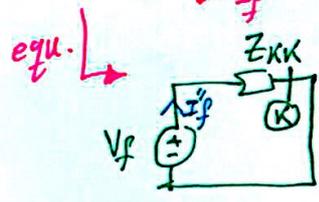• Use  $Z_{th}$  Concept :  
Between bus & Ref  $Z_{th} = Z_{kk}$   
Between 2 buses:  $Z_{th} = Z_{jj} + Z_{ii} - 2Z_{ji}$



$$I_f'' = \frac{V_f}{Z_{kk}}$$


$$Z_{th} = Z_{11} + Z_{22} - 2Z_{12}$$

$$\Rightarrow Z_{kk} = Z_{11} + Z_b - \frac{(Z_{11} - Z_{21})^2}{Z_{12} - Z_b}$$

\* C.B Selection :

$$SCMVA = \sqrt{3} * |Nominal\ Voltage, KV| * |I_{sc}| * 10^{-3}$$

$$SCMVA_{(PU)} = I_{sc(PU)}$$

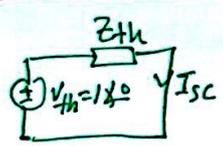

$$Z_{th} = \frac{1}{I_{sc(PU)}} = \frac{1}{SCMVA_{(PU)}}$$

- Total instantaneous current =  $I_f'' * \text{factor}$
- interrupting KVA =  $\sqrt{3} * KV$  of the bus connected to C.B \* Current that C.B capable to interrupt.
- voltage Range factor (K) =  $\frac{\text{Max. voltage}}{\text{Min voltage}}$
- Rated S/C current \* operating Voltage  $\equiv$  Constant.

\* Case when the givens are subtransient & Need transient :

Use E/x Method: keep  $X''$  the same for Gen & Trans. & use  $x'$  for the Motor as:  $X'_m = 1.5 X''_m$

⇒ This Method Must satisfy 2-conditions :

- 1) voltage of the system must be within C.B operating Range.
- 2) Calculated Current ( $I_f''$ )  $\leq 0.8 * \text{Rated S/C current of C.B.}$

**\* Unbalanced Faults:**

$a = 1 \angle 120^\circ$   
 $a^2 = 1 \angle 240^\circ$   
 $a^3 = 1 \angle 360^\circ$

$A_{matrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$


$A^{-1} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix}$

**\* Symm. Components:**


$[V_{abc}] = [A][V_{012}]$   
 $[V_{012}] = [A]^{-1}[V_{abc}]$   
 for line & phase voltages.

$[I_{abc}] = [A][I_{012}]$   
 $[I_{012}] = [A]^{-1}[I_{abc}]$   
 for line & phase currents.

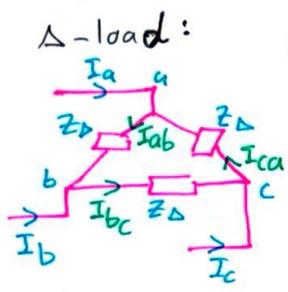**\* Symm. Components of  $\Delta$  & Y loads:**



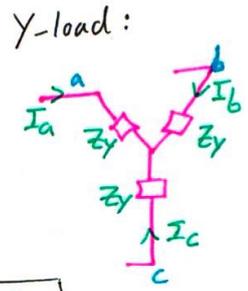$I_a^{(1)} = \sqrt{3} \angle -30^\circ I_{ab}^{(1)}$   
 $I_a^{(2)} = \sqrt{3} \angle +30^\circ I_{ab}^{(2)}$   
 $I_a^{(0)} = 0$



$V_{ab}^{(0)} = 0$   
 $V_{ab}^{(1)} = \sqrt{3} \angle 30^\circ V_{an}^{(1)}$   
 $V_{ab}^{(2)} = \sqrt{3} \angle -30^\circ V_{an}^{(2)}$





$Z_{\Delta} = 3Z_Y$

**\* Power:**

$S_{3\phi} = V_{an} I_{an}^* + V_{bn} I_{bn}^* + V_{cn} I_{cn}^* = 3 V^{(0)} I^{(0)*} + 3 V^{(1)} I^{(1)*} + 3 V^{(2)} I^{(2)*} \rightarrow (VA)$   
 $S_{(PU)} = \frac{S_{3\phi}}{S_b = 3S_{1\phi}} = \frac{V^{(0)} I^{(0)*}}{S_{1\phi}} + \frac{V^{(1)} I^{(1)*}}{S_{1\phi}} + \frac{V^{(2)} I^{(2)*}}{S_{1\phi}} \rightarrow (PU)$





**\* Seq. Impedance: (Earthing only Effect zero Seq.)**

**Y-load:**

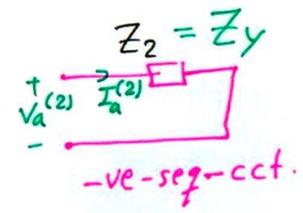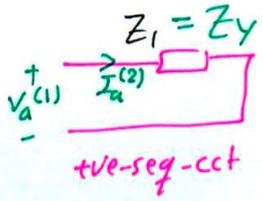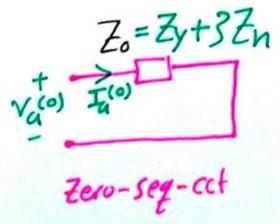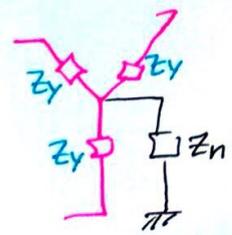


for isolated n:  $Z_n = \infty$  & solidly grounded:  $Z_n = 0$


**$\Delta$ -load: (converted to Y)**

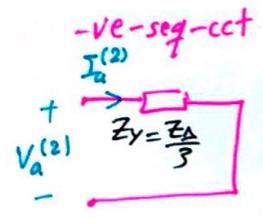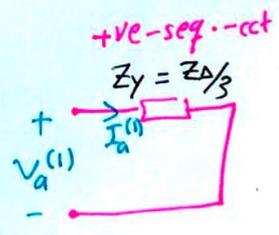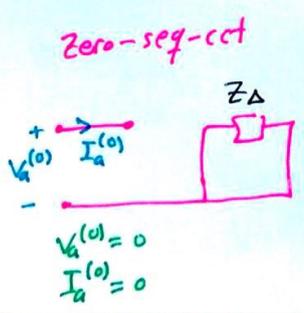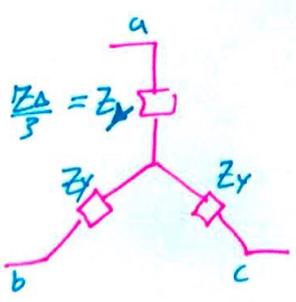


\* Seq. ccts of T.L:

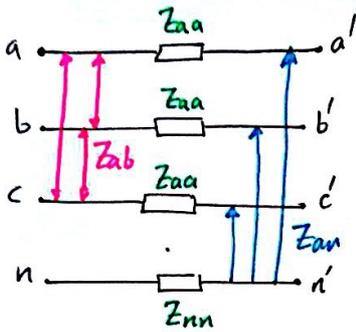


0-seq-cct

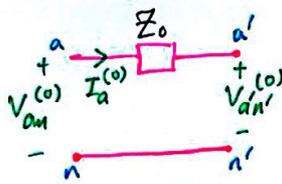

+ve-seq-cct

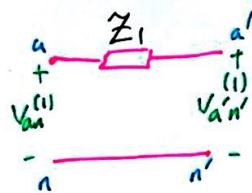

-ve-seq-cct

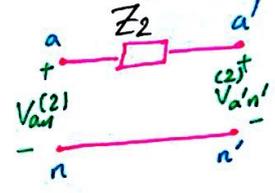


$Z_0 = Z_0 + 3Z_{nn}$

$Z_1 = Z_2 = Z_s - Z_m$

$Z_s = Z_{aa} - 2Z_{an} + Z_{nn}$   
 $Z_m = Z_{ab} - 2Z_{an} + Z_{nn}$

\* Seq. ccts of Gen:

zero-seq-cct

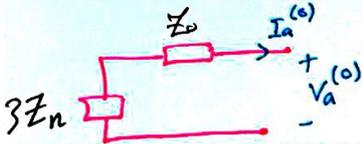


$Z_0 = R + j\omega(L_s - 2M_s)$

+ve-seq-cct




-ve-seq-cct

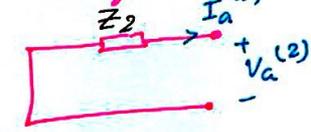

$Z_1 = Z_2 = R + j\omega(L_s + M_s)$

\* Seq. ccts of Trans.:

+ve-seq-cct

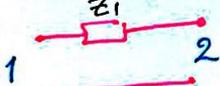


$Z_1 = Z_2 = Z_{eq}$

-ve-seq-cct



zero-seq cct:

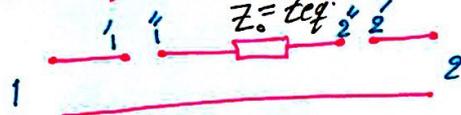


Between (1' & 2'), (2' & 2''):


Y-type  $\rightarrow 3Z_n$

$\Delta$ -type  $\rightarrow s/c$  on 1'' or/and 2''.

\* Line-Ground Fault:

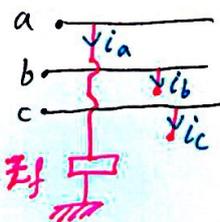

Interconnection:


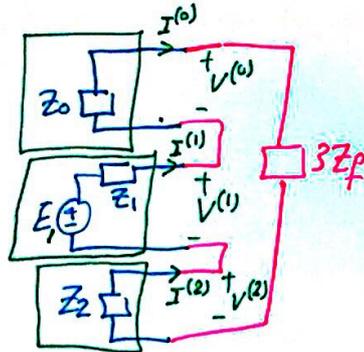


$I^{(0)} = I^{(1)} = I^{(2)} = \frac{E}{Z_0 + Z_1 + Z_2 + 3Z_f}$

$V^{(0)} = -I^{(0)} Z_0$   
 $V^{(1)} = E_1 - I^{(1)} Z_1$   
 $V^{(2)} = -I^{(2)} Z_2$

$I_f = 3 I^{(0)}$

\* Line-Line Fault:

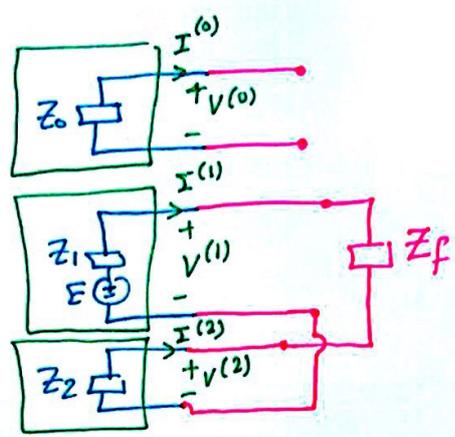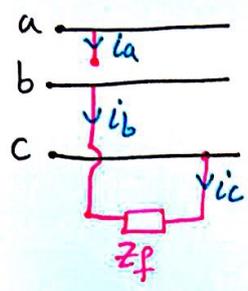



$$I^{(0)} = V^{(0)} = 0$$

$$I^{(1)} = -I^{(2)} = \frac{E}{Z_1 + Z_2 + Z_f}$$

$$V^{(1)} = E - I^{(1)} Z_1$$

$$V^{(2)} = -I^{(2)} Z_2$$

\* Line-Line-Ground Fault:

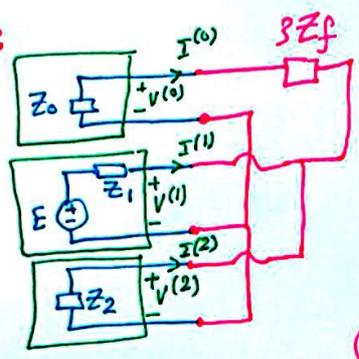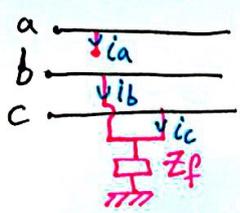

$$I^{(1)} = \frac{E}{Z_1 + [(Z_0 + 3Z_f) // Z_2]}$$

$$I^{(0)} = -I^{(1)} \frac{Z_2}{Z_2 + Z_0 + 3Z_f}$$

$$I^{(2)} = -(I^{(0)} + I^{(1)})$$



$$V^{(0)} = -I^{(0)} Z_0, \quad V^{(1)} = V^{(2)} = E - I^{(1)} Z_1$$

\* Finding Zbus in the Unbalanced Fault:

- Find seq. Network +ve, -ve then find  $V_{bus}^{(0)}, V_{bus}^{(1)}, V_{bus}^{(2)}$  then find  $Z_{bus}^{(0)}, Z_{bus}^{(1)}, Z_{bus}^{(2)}$
- from the relation:  $Z_{bus} = [Y_{bus}]^{-1}$
- Now you can find:  $I^{(0)} = I^{(1)} = I^{(2)} = \frac{1 \times 0}{Z_0 + Z_1 + Z_2}$  if the fault @ bus K:
  - $Z_1 = Z_2 = [Z_{KK} \text{ of } Z_{bus}^{(1)}]$
  - $Z_0 = [Z_{KK} \text{ of } Z_{bus}^{(0)}]$

\* end of second Material\*

\* O/C Fault:

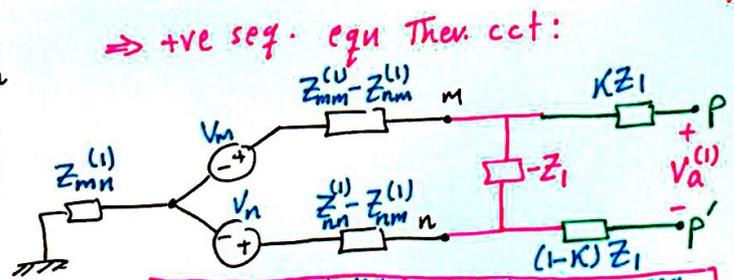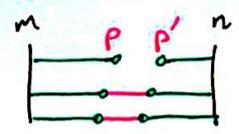


\* -ve & zero seq the same BUT with sources s/c.

current injections:

	+ve seq.	-ve-seq	o-seq.
m	$V_a^{(1)} / Z_1$	$V_a^{(2)} / Z_2$	$V_a^{(0)} / Z_0$
n	$-V_a^{(1)} / Z_1$	$-V_a^{(2)} / Z_2$	$-V_a^{(0)} / Z_0$

After simplify:

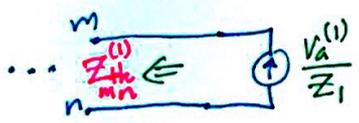

$$Z_{pp'}^{(0)} = \frac{-Z_0^2}{(Z_{th,mn}^{(0)} - Z_0)}$$


$$Z_{pp'}^{(1)} = \frac{-Z_1^2}{(Z_{th,mn}^{(1)} - Z_1)}$$

$$Z_{pp'}^{(2)} = \frac{-Z_2^2}{(Z_{th,mn}^{(2)} - Z_2)}$$

$$I_{mn} = \frac{V_m - V_n}{Z_1}$$

$$V_{th} = (V_m - V_n) \frac{Z_{pp'}^{(1)}}{Z_1} = I_{mn} Z_{pp'}^{(1)}$$

⇒ Interconnection between Networks :

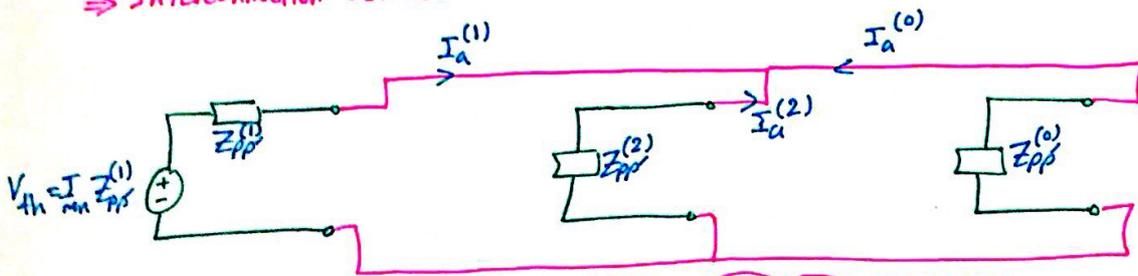

$$I_a^{(1)} = \frac{I_{mn} Z_{PP}^{(1)}}{Z_{PP}^{(1)} + [Z_{PP}^{(2)} // Z_{PP}^{(0)}]} = \frac{I_{mn} Z_{PP}^{(1)} [Z_{PP}^{(0)} + Z_{PP}^{(2)}]}{Z_{PP}^{(1)} Z_{PP}^{(0)} + Z_{PP}^{(1)} Z_{PP}^{(2)} + Z_{PP}^{(0)} Z_{PP}^{(2)}}$$

$$V_a^{(0)} = V_a^{(1)} = V_a^{(2)} = I_a^{(1)} \frac{Z_{PP}^{(0)} Z_{PP}^{(2)}}{Z_{PP}^{(0)} + Z_{PP}^{(2)}} \Rightarrow V_a^{(0)} = V_a^{(1)} = V_a^{(2)} = \frac{I_{mn}}{\frac{1}{Z_{PP}^{(0)}} + \frac{1}{Z_{PP}^{(1)}} + \frac{1}{Z_{PP}^{(2)}}}$$

⇒ change in voltages: @ z<sup>th</sup> bus

$$\Delta V_i^{(0)} = V_a^{(0)} (Z_{im}^{(0)} - Z_{in}^{(0)}) / Z_0$$

$$\Delta V_i^{(1)} = \Delta V_i^{(2)} = V_a^{(1)} (Z_{im}^{(1)} - Z_{in}^{(1)}) / Z_1 \Rightarrow \underline{\underline{\Delta V_i = \Delta V_i^{(0)} + \Delta V_i^{(1)} + \Delta V_i^{(2)}}}$$

\* Power Flow :

⇒ Power flow equations:

$$S_i = \sum_{j=1}^N |V_i| |V_j| |Y_{ij}| \angle \delta_j - \theta_{ij}$$

$$P_i = \sum_{j=1}^N |V_i| |V_j| |Y_{ij}| \cos(\delta_j - \delta_i - \theta_{ij})$$

$$Q_i = \sum_{j=1}^N |V_i| |V_j| |Y_{ij}| \sin(\delta_j - \delta_i - \theta_{ij})$$

• if  $V_i$  for  $(i=1, N)$  are known then  $P_{isch}, Q_{isch}$  obtained.

• Scheduled values:

$$P_{isch} = P_{Gi} - P_{Di}$$

$$Q_{isch} = Q_{Gi} - Q_{Di}$$

• Mismatch values:

$$\Delta P_i = P_{isch} - P_{ical}$$

$$\Delta Q_i = Q_{isch} - Q_{ical}$$

• Classifications:

1] PQ Busbar:  $P_{Gi} = Q_{Gi} = 0$   
 $P_{Di}$  found using load of cost.  
 $Q_{Di}$  found using a certain Pf.

$$\Rightarrow \begin{cases} P_{isch} = -P_{Di} \\ Q_{isch} = -Q_{Di} \end{cases}$$

$P_{isch}$  &  $Q_{isch}$  are specified  
 $\Rightarrow |V_j|$  &  $\delta_j$  unknowns.

2] PV Busbar:  $P_{Gi}$  &  $|V_j|$  are specified,  $\delta_j$  unknown.

3] Slack Busbar:  $V_3 = 1 \angle 0$  ⇒ Reference Busbar is generator Bus.

• Losses:

$$\sum P_i = P_{loss} = \sum P_{Gi} - \sum P_{Di}$$

$$\sum Q_i = Q_{loss} = \sum Q_{Gi} - \sum Q_{Di}$$

**Summary:**

Bus Type	# of Buses	specified quantities	# of available Equations	# of unknowns state variables.
slack $i=1$	1	$ V_i , \delta_i$	0	0
voltage controlled OR PV Bus. ( $i=2, \dots, N_g+1$ )	$N_g$	$P_i,  V_i $	$N_g$	$N_g$
PQ Bus ( $i=N_g+2, \dots, N$ )	$N-N_g-1$	$P_i, Q_i$	$2(N-N_g-1)$	$2(N-N_g-1)$
Summation	$N$	$2N$	$2N-N_g-2$	$2N-N_g-2$


**Gauss Seidal Method:**

$$V_i^{(k)} = \frac{1}{Y_{ii}^*} \left[ \frac{S_i^*}{V_i^{(k-1)*}} - \sum_{j=1}^{i-1} Y_{ji} V_j^{(k)} - \sum_{j=i+1}^N Y_{ji} V_j^{(k-1)} \right]$$

**Steps:**

- i) Specify a voltage for the slack bus ( $V_1 = 1 \angle 0^\circ$ ).
- ii) Assume initial value for other buses ( $V_j^{(0)} = 1 \angle 0^\circ$  for  $j=2, \dots, N$ ).
- iii) Sub.  $V_i$  &  $V_j$  into (1) to find  $V_j^{(1)}$  for  $j=2, \dots, N$ .
- iv) find all voltages, then 1st iteration will be completed.
- v) Check that  $|V_j^{(k)} - V_j^{(k-1)}| < \epsilon$ 
  - if YES solution obtained.
  - if NO Go to 2nd iteration.

**For the Line DATA:**

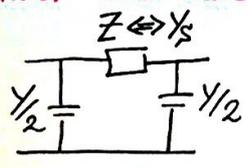

• if  $Z$  given, then one can find  $Y_s$ :  $Y_s = \frac{1}{Z}$   
 • from the given Total MVAR:  $Y_{pu} = \frac{MVAR}{3 V_B^2} \Rightarrow Y_{pu} = \frac{Y_s}{Y_b}$   
 $\Rightarrow$  then find  $Y/2$ .  $Y_b = \frac{1}{Z_b}$

• from the Line DATA  $\Rightarrow$  Obtain  $[Y_{bus}]$  matrix.

**Q of the load:**  $Q = P \tan[\cos^{-1} Pf]$

**Procedure:**

- 1) start "assume the slack bus".
- 2) for PQ-Buses "find  $V = |V| \angle \delta$ "
  - $\Rightarrow$  use acceleration factor ( $\alpha$ ):
  - $1 < \alpha < 2 \Rightarrow$  Typically:  $\alpha = 1.6$
  - Use:  $V_{j,acc}^{(k)} = V_j^{(k-1)} + \alpha (V_j^{(k)} - V_j^{(k-1)})$

- 3) for PV Bus: "find @ first Q"
  - check:  $Q_{min} \leq Q \leq Q_{max}$
  - if Yes: find  $|V| \angle \delta$  using accelerated values.
  - if NO: set Q @ violated limit (e.g  $Q = Q_{max}$ )
  - $\Rightarrow$  convert PV  $\rightarrow$  PQ
  - Then calculate  $|V| \angle \delta$ .

⇒ where  $Q$  found from:  $Q_j^{(k)} = -\text{Im} \left[ V_i^{(k-u)*} \left( \sum_{j=1}^{i-1} Y_{ij} V_j^{(k)} + \sum_{j=i}^N Y_{ij} V_j^{(k-1)} \right) \right]$

\* For the voltage obtained for PV Bus, one can find the corrected value of  $V_j^{(u)}$ :  $V_{j,corr}^{(u)} = \frac{V_j^{(u)}}{|V_j^{(u)}|} * |V_j^{(u)}|$

Newton-Raphson-Method:

$g_1(x_1, x_2, u) = h_1(x_1, x_2, u) - b_1$   
 $g_2(x_1, x_2, u) = h_2(x_1, x_2, u) - b_2$

⇒ Represent power flow equations.  
 $g_1, g_2 \equiv$  Mismatch Values.  
 $h_1, h_2 \equiv$  Calculated values.  
 $b_1, b_2 \equiv$  Specified Values.

These Power flow equ. found by:

$g_1(x_1, x_2, u) = P_{2,cal} - P_{2,sch}$   
 $g_2(x_1, x_2, u) = Q_{2,cal} - Q_{2,sch}$

⇒  $P_{2,sch} = P_{G2} - P_{D2}$   
 $Q_{2,sch} = Q_{G2} - Q_{D2}$

$P_{i,cal} = \sum_{j=1}^N |V_i| |V_j| |Y_{ij}| \cos(\delta_j - \delta_i - \theta_{ij})$   
 $Q_{i,cal} = \sum_{j=1}^N |V_i| |V_j| |Y_{ij}| \sin(\delta_j - \delta_i - \theta_{ij})$

\* Steps:

1) Find the correction values  $\Delta x$  by:

$\begin{bmatrix} \Delta x_1^{(u)} \\ \Delta x_2^{(u)} \end{bmatrix} = [J^{(u)}]^{-1} \begin{bmatrix} \Delta g_1^{(u)} \\ \Delta g_2^{(u)} \end{bmatrix}$

where:  $J^{(u)} = \begin{bmatrix} \frac{dg_1}{dx_1} & \dots & \frac{dg_1}{dx_N} \\ \vdots & & \vdots \\ \frac{dg_N}{dx_1} & \dots & \frac{dg_N}{dx_N} \end{bmatrix}$

$\Delta g = \begin{bmatrix} b_1 - h_1^{(u)}(x_1, x_2, u) \\ b_2 - h_2^{(u)}(x_1, x_2, u) \end{bmatrix}$

2) Find the correct answer by:

$x_1^{(u)} = x_1^{(u)} + \Delta x_1^{(u)}$   
 $x_2^{(u)} = x_2^{(u)} + \Delta x_2^{(u)}$

3) CHECK:  $\{x_1^{(u)} \& x_2^{(u)}\} < \epsilon$

if YES solution is obtained.  
 if NO Re-iterate using  $\begin{bmatrix} \Delta x_1^{(u)} \\ \Delta x_2^{(u)} \end{bmatrix} = [J^{(u)}]^{-1} \begin{bmatrix} \Delta g_1^{(u)} \\ \Delta g_2^{(u)} \end{bmatrix}$

⇒ Procedure:

- 1) start.
- 2) Assume initial solution for the unknowns  $|V|$  &  $\delta_i$ .
- 3) find  $P_{i,cal}$  for  $i=2, \dots, N$   
 $Q_{i,cal}$   $i=2, \dots, N-M_g$

- 4) Evaluate Mismatches:  
 $\Delta P_i = P_{i,sch} - P_{i,cal}$   
 $\Delta Q_i = Q_{i,sch} - Q_{i,cal}$
- 5) Determine Elements of the Jacobian Matrix.

- 6) Evaluate for corrections  $\Delta V_i, \Delta \delta_i$
- 7) CHECK  $|\Delta V_i| \& |\Delta \delta_i| < \epsilon$   
 If NOT: Go Next iteration  
 $V_i^{(k+1)} = V_i^{(k)} + \Delta V_i^{(k)}$   
 $\delta_i^{(k+1)} = \delta_i^{(k)} + \Delta \delta_i^{(k)}$

\* if we have 4-buses ; bus#1 is slack & others PQ buses:

$$\begin{bmatrix} \frac{\partial P_2}{\partial \delta_2} & \dots & \frac{\partial P_2}{\partial |V_2|} |V_2| & \dots & \frac{\partial P_2}{\partial |V_4|} |V_4| \\ \vdots & & & & \vdots \\ \frac{\partial P_4}{\partial \delta_2} & \dots & \frac{\partial P_4}{\partial |V_2|} |V_2| & \dots & \frac{\partial P_4}{\partial |V_4|} |V_4| \\ \vdots & & & & \vdots \\ \frac{\partial Q_4}{\partial \delta_4} & \dots & \frac{\partial Q_4}{\partial |V_2|} |V_2| & \dots & \frac{\partial Q_4}{\partial |V_4|} |V_4| \end{bmatrix} \begin{bmatrix} \Delta \delta_2 \\ \Delta \delta_3 \\ \Delta \delta_4 \\ \Delta |V_2|/|V_2| \\ \Delta |V_3|/|V_3| \\ \Delta |V_4|/|V_4| \end{bmatrix} = \begin{bmatrix} \Delta P_2 \\ \Delta P_3 \\ \Delta P_4 \\ \Delta Q_2 \\ \Delta Q_3 \\ \Delta Q_4 \end{bmatrix}$$

Note: if bus#4 is PV bus ( $\Delta V=0$ ), Q can't be calculated  $\Rightarrow$  you will remove one row & one column.

Order of J matrix =  $2N - N_g - 2$

\* Corrections found from:  $\begin{bmatrix} \Delta \delta_2 \\ \vdots \\ \frac{\Delta |V_4|}{|V_4|} \end{bmatrix} = [J]^{-1} \begin{bmatrix} \Delta P_2 \\ \vdots \\ \Delta Q_4 \end{bmatrix}$

\* Elements of the Jacobian found as follows:

$J_{11}$ : "Non Diagonal"  $\frac{\partial P_i}{\partial \delta_j} = -|V_i||V_j||Y_{ij}| \sin(\theta_{ij} + \delta_j - \delta_i)$

"Diagonal"  $\frac{\partial P_i}{\partial \delta_i} = \sum_{\substack{n=1 \\ n \neq i}}^N |V_i||V_n||Y_{in}| \sin(\theta_{in} + \delta_n - \delta_i)$

$J_{21}$ : "Non Diagonal"  $\frac{\partial P_i}{\partial \delta_j} = -|V_i||V_j||Y_{ij}| \cos(\theta_{ij} + \delta_j - \delta_j)$

"Diagonal"  $\frac{\partial P_i}{\partial \delta_i} = \sum_{\substack{n=1 \\ n \neq i}}^N |V_i||V_n||Y_{in}| \cos(\theta_{in} + \delta_n - \delta_i)$

$J_{12}$ : "Non Diagonal"  $|V_j| \frac{\partial P_i}{\partial |V_j|} = |V_j||V_i||Y_{ij}| \cos(\theta_{ij} + \delta_j - \delta_i)$

"Diagonal"  $|V_i| \frac{\partial P_i}{\partial |V_i|} = P_i + |V_i|^2 G_{ii}$


$J_{22}$ : "Non Diagonal"  $|V_j| \frac{\partial Q_i}{\partial |V_j|} = -|V_j||V_i||Y_{ij}| \sin(\theta_{ij} + \delta_j - \delta_i)$

"Diagonal"  $|V_i| \frac{\partial Q_i}{\partial |V_i|} = Q_i - |V_i|^2 B_{ii}$

$\Rightarrow Y_{ii} = G_{ii} + jB_{ii}$



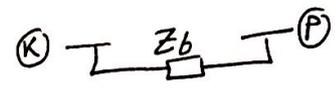4) Add  $Z_b$  from a new bus (P) to an existing Bus (K):



Matrix: 
$$\begin{bmatrix} Z_{org} & \begin{matrix} Z_{1K} \\ Z_{2K} \\ \vdots \\ Z_{KK} \end{matrix} \\ \hline \begin{matrix} Z_{K1} \dots \dots Z_{KK} \end{matrix} & \begin{matrix} Z_{KK} + Z_b \end{matrix} \end{bmatrix}$$

elements in the original matrix.

5) Add  $Z_b$  from existing Bus (K) to a Ref. Node:

- you will create new row & column as previous step.
- eliminate (N+1) row & (N+1) column then find:

$$Z_{ni}(new) = Z_{ni}(old) - \frac{Z_{n(N+1)} * Z_{(N+1)i}}{Z_{KK} + Z_b}$$

6) Add  $Z_b$  between two existing Buses (J) & (K):

Matrix: 
$$\begin{bmatrix} Z_{org} & \begin{matrix} \text{col. } j \\ \text{col. } k \end{matrix} \\ \hline \begin{matrix} \text{row } j - \text{row } k \end{matrix} & Z_{bb} \end{bmatrix}$$

$$Z_{bb} = Z_{jj} + Z_{kk} - 2Z_{jk} + Z_b$$

then find:

$$Z_{ni}(new) = Z_{ni}(old) - \frac{Z_{n(N+1)} * Z_{(N+1)i}}{Z_{bb}}$$

\* \* \*  
End of Material.  
\* \* \*

Best of Luck.  
\* \* \*