

Name(in Arabic) *أحمد عيسى خازن*

Student No. 0114906

Programmable calculators are not allowed.
Derive any formula you use.

1. Answer the following by marking \checkmark for correct answer and X for wrong answer
2marks (each question 0.5 mark)

Power Electronics devices may inject harmonics into the power system which it is part of	T \checkmark
Boost converters are used to step up ac voltage to ac voltage of different frequency	F X
The higher the power capability of power electronics devices, the higher is the frequency possible to use	T \checkmark X
HVDC transmission needs both rectifiers and inverters	F X X

1. Fig 1 shows the diode recovery characteristics of certain diode.

Softness factor = $\frac{t_d}{t_r} = \frac{1.5}{0.5} = 3$ \checkmark

1mark

2. Fig 2 shows the characteristics of two diodes connected in series with a total reverse voltage of 5kV.

2marks

Find the values of the equalizing resistances needed to get equal voltage drop across the two diodes and to have a total reverse current of 10mA.



$$I_{s1} + \frac{V_{D1}}{R_1} = I_{s2} + \frac{V_{D2}}{R_2}$$

$$\frac{7mA}{3m} + \frac{2.5k}{R_1} = \frac{6.5mA}{3.5m} + \frac{2.5k}{R_2}$$

$$I_{R1} = 10mA - 7mA = 3mA$$

$$10 - 3.5 = 6.5$$

$R_1 = 833.3 k\Omega$

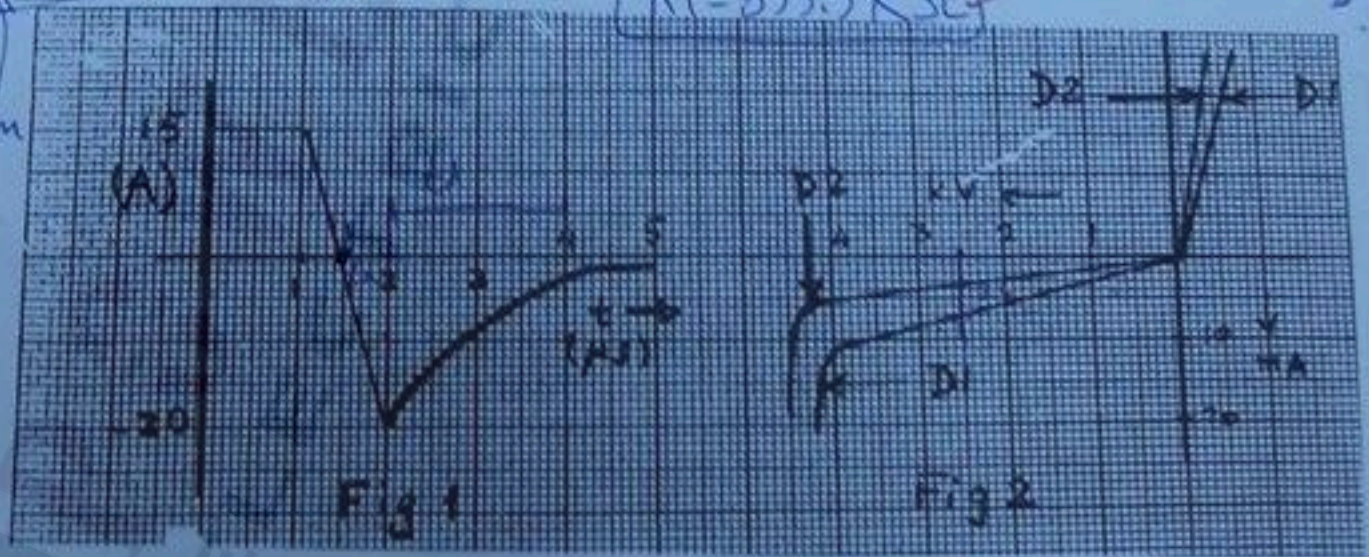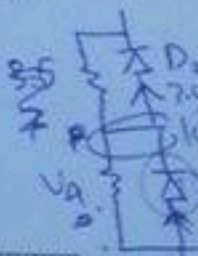

$I_{R2} = 6.5mA \Rightarrow R_2 = 384.62 k\Omega$

2. A voltage of $v(t) = 100 \sin(100\pi t + 30^\circ)$ V, is applied to a certain non-linear load. The flowing current is given by:
 $i(t) = 4 + 10 \cos(100\pi t) + 6 \sin(300\pi t + 30^\circ)$ A

Find:

5marks

- (i) The rms value of the current

$$I_{rms} = \sqrt{4^2 + \left(\frac{10}{\sqrt{2}}\right)^2 + \left(\frac{6}{\sqrt{2}}\right)^2} = 9.165 \text{ A}$$

- (ii) The distortion factor

$$D.F = \frac{I_{1rms}}{I_{rms}} = \frac{\frac{10}{\sqrt{2}}}{9.165} = 0.7715$$

- (iii) The power factor

$$Power = \frac{(100)(10)}{2} \cos(60) = 250 \text{ W}$$

$$\therefore P.F = \frac{250}{V_{rms} I_{rms}} = \frac{250}{\left(\frac{100}{\sqrt{2}}\right)(9.165)} = 0.3858$$

- (iv) The distortion volt ampere

$$Q = \frac{(100)(10)}{2} \sin(60) = 433.012 \text{ VAR}$$

$$P = 250$$

$$S = 648.06 \text{ VA}$$

$$D = \sqrt{S^2 - P^2 - Q^2} = \sqrt{(648.06)^2 - (250)^2 - (433.012)^2}$$

$$D = \sqrt{169982.3715} = 412.29 \text{ VAD}$$

- (v) The total harmonic distortion

$$THD = \sqrt{\frac{I_{2rms}^2 + I_{3rms}^2}{I_{1rms}^2}} = \sqrt{\frac{10^2 + 6^2}{10^2}}$$

$$THD = \sqrt{\frac{1}{DF} - 1} = \sqrt{\frac{1}{(0.7715)^2} - 1} = 0.8825 = 88.25\%$$



$$\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2(\omega t) dt \Rightarrow \frac{V_m^2}{2\pi} \left(\frac{1}{2} \omega t - \frac{1}{4} \cos(2\omega t) \right) \Big|_0^{2\pi}$$

3. A single-phase half wave rectifier supplied from a sinusoidal source and with a pure resistive load of 2Ω . The dc-power consumed by the load = 200W. Find:

(1/2 * π) - (1/2 * π) = 0
 ②
 5marks

(i) The peak value of the transformer secondary voltage

$$P = \frac{V_{rms}^2}{R} \Rightarrow 200 = \frac{V_{rms}^2}{2} \Rightarrow V_{rms}^2 = 400 \Rightarrow V_{rms} = 20V$$

$$V_{dc} = 20V \quad V_{dc} = \frac{V_m}{\pi} \Rightarrow V_m = 62.832V$$

~~$V_{rms} = 20 = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2(\omega t) dt}$~~

~~$20 = \sqrt{\frac{V_m^2}{2\pi} \left(\frac{1}{2} \omega t - \frac{1}{4} \sin(2\omega t) \right) \Big|_0^{2\pi}} \Rightarrow 20 = \sqrt{\frac{V_m^2}{2\pi} \left(\frac{1}{2} \cdot 2\pi \right)}$~~

~~$\Rightarrow 20 = \sqrt{\frac{V_m^2}{4}} \Rightarrow 20 = \frac{V_m}{2} \Rightarrow V_m = 40V$~~

~~$V_{rms} = \frac{V_m}{2}$~~

(ii) The rms value of the transformer secondary current

~~$I_{rms} = \frac{V_{rms}}{R} = \frac{20}{2} = 10A$~~

~~$I_{rms} = \frac{V_{rms}}{R} = \frac{62.832}{2} = 31.416A$~~

$$I_{rms} = \sqrt{\frac{1}{2\pi R} \int_0^{2\pi} (62.832)^2 \sin^2(\omega t) d\omega t}$$

$$= 15.708A$$

(iii) The total power consumed by the load

$$P = I_{rms}^2 R = (15.708)^2 (2) = 493.48W$$


(iv) The ac voltage of the load

$$V_{rms} R = (15.708)(2) = 31.416V$$

$$V_R(t) = 62.832 \sin(\omega t)$$

(v) The volt-ampere of the transformer

$$S = (I_{rms})(V_{rms}) = 493.48VA$$

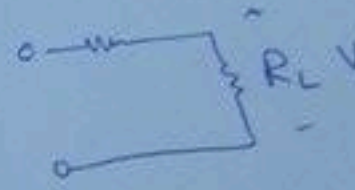

4

ABET Problem for evaluating Students Outcome E:

1. A half wave rectifier with sinusoidal supply voltage with $V_m = 200V$, $50Hz$, a resistance of 4Ω , an inductance of $20mH$ and a dc source of $100V$. 5marks

(i) Calculate the value of the distinction angle β

$$\alpha = \sin^{-1}\left(\frac{V_{dc}}{V_m}\right) = \sin^{-1}\left(\frac{100}{200}\right) = 30^\circ \quad \& \sin(\alpha) = 1/2 \quad \text{0.5}$$

$$\frac{\omega L}{R} = \frac{(2\pi)(50)(20 \times 10^{-3})}{4} = 1.57$$

from graph $\Rightarrow \beta = 185^\circ$

$$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right) = \tan^{-1}(1.57) = 57.52^\circ$$

(ii) Calculate the dc value of the output voltage

~~$V_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin(\omega t) d\omega t$~~

$$V_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin(\omega t) d\omega t = \frac{1}{2\pi} \int_{30^\circ}^{185^\circ} 200 \sin(\omega t) d\omega t$$

$$i(t) = \frac{V_m}{Z} \sin(\omega t) + \frac{V_{dc}}{R}$$

V_{dc}

(iii) Calculate the power supplied to the battery


~~$P = I_{rms} V_{dc}$~~ $P = I_{dc} V_{dc}$

$$\frac{200}{2\pi} \int_{30}^{185} -\cos(\omega t) d\omega t = \dots$$

$$P = (22.78) \times (100) = 2277.61 \text{ W}$$

(iv) Given the waveform of the input voltage, sketch the waveforms of the output voltage, the current and the voltage across the inductance

4.5

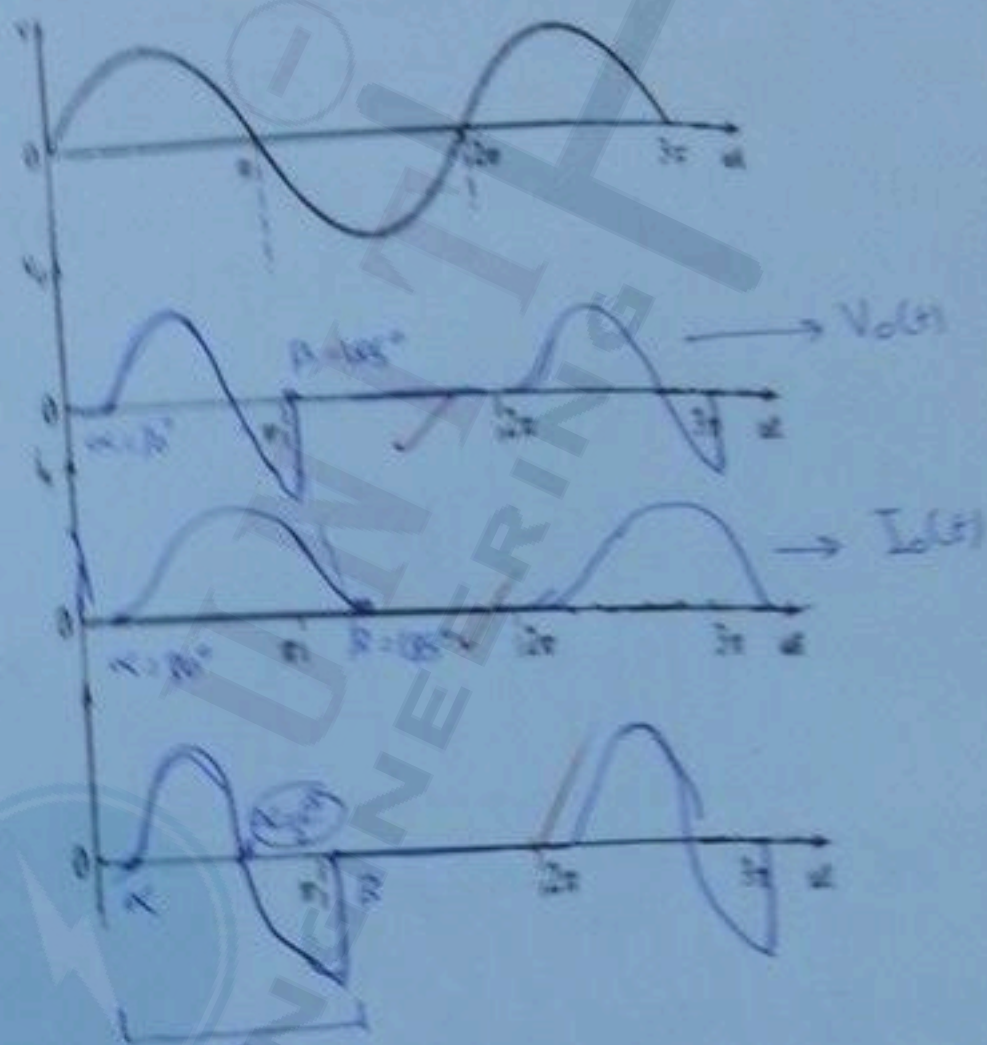

$$i(t) = \frac{V_m}{Z} \sin(\omega t) + \left(\frac{V_{dc}}{R}\right) - \left[\frac{V_m}{Z} \frac{e^{-\alpha t}}{2} \sin(\omega t - \theta) + \frac{V_{dc}}{R} \right] e^{-\alpha t}$$

$$I_{ac} = \frac{V_m}{Z} + \frac{1}{\omega Z} \int \frac{V_m}{Z} \sin(\omega t) dt$$

$$= \frac{V_{dc}}{R} + \frac{V_m}{Z \omega Z} (\cos(\omega t)) \Big|_0^{\pi} \Rightarrow I_{ac}$$

$$\frac{50 \sqrt{2}}{4} + 7.957 \text{ V}$$

$$14.5 \text{ V} + 7.957 = \boxed{22.78 \text{ V}}$$