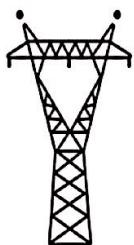





Power Electronics

Fall017



Dr. Sereen Althaher

By: Mhmd Abuhashya

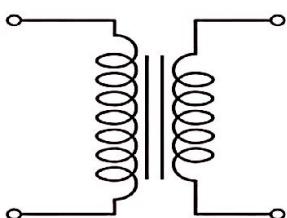

Powerunit-ju.com

Power Electronics

Dr. Sereen Al-thaker.



Sereen.Althaker@ju.edu.jo

Fall 2017-2018

Notebook.


By. Mohammad
Abu Hashya.

*Power Electronics (PE) :

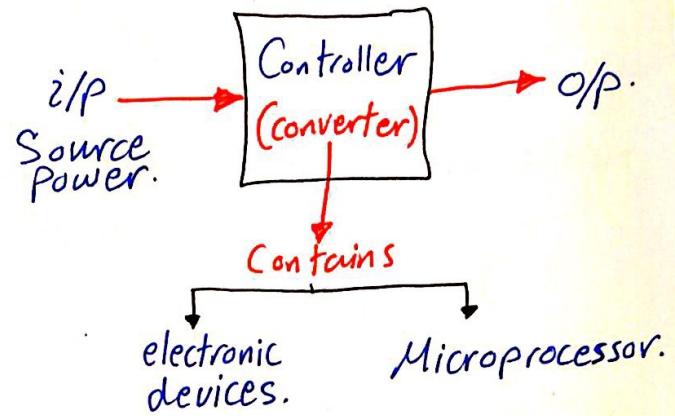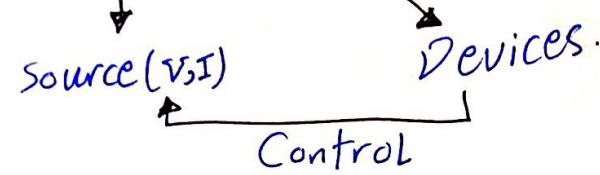


*Application of PE:

1) Charger:

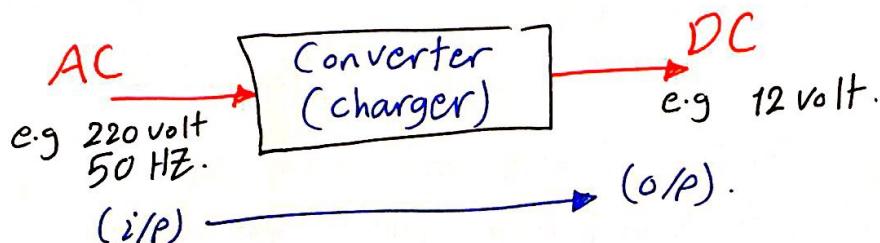

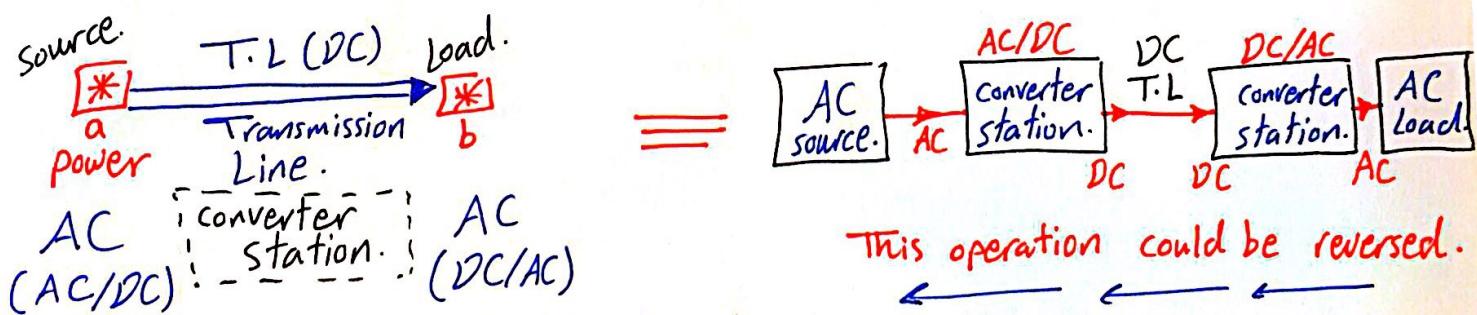
2) High Voltage DC (HVDC):


- Convert power from one city to another. (Egypt & Jordan).



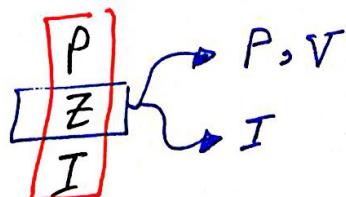3) Energy Efficiency:


- Like the inverters in the Airconditioners & Refrigerators.
- This applied using PIZ model.



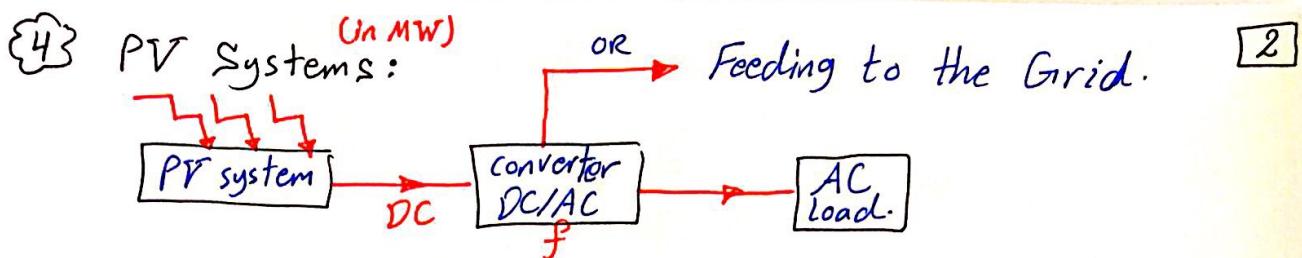


⇒ Here the inverter face a problem with synchronization with the exist frequency.

⑤ Wind Generation Systems :

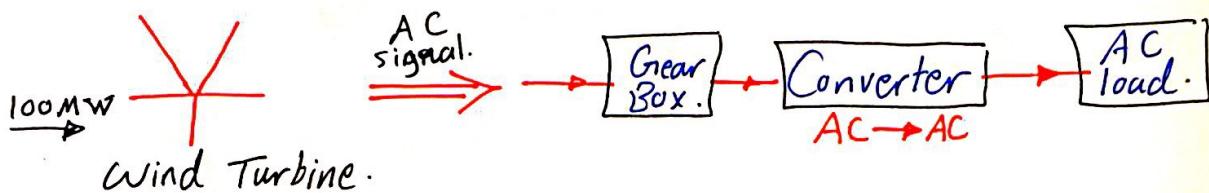

- The input signal has freq. & Amplitude changing because the speed of the wind, and the AC Load need fixed RMS & fixed freq, and this is solved By a converter (AC/AC).

Example:

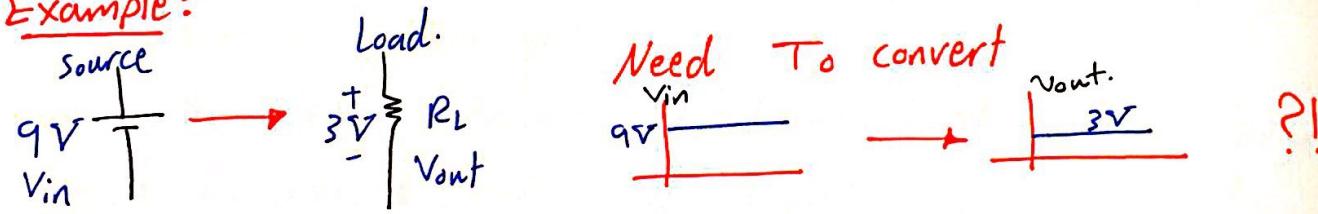

Solutions:

- Simple solution by using Resistance R_x To drop the voltage.

$$R_x = 2R_L$$

$$P_{in} = VI = 9I = \frac{27}{R_L}$$



$$P_{out} = \frac{V^2}{R_L} = \frac{9}{R_L}$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{9/R_L}{27/R_L} = 33\% \text{ (very bad).}$$

$$\frac{18}{R_L} \text{ Watt Lost @ } R_x$$

Continue. →

- Another solution by using a switch.

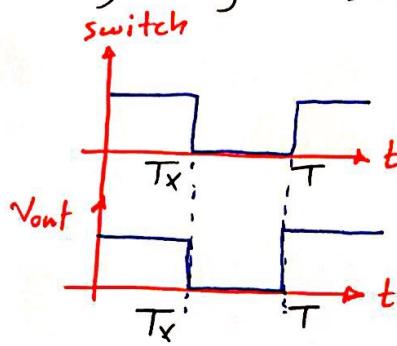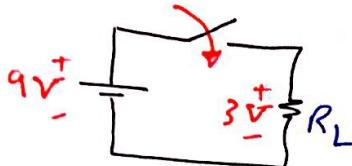

$$DC = \text{Avg.} = \frac{1}{T} \int v(t) dt$$

$$= \frac{1}{T} \int_0^{T_x} 3 dt = 3$$



$$\Rightarrow \frac{q}{T} \frac{T_x}{T} = 3$$

$$\Rightarrow T_x = \frac{T}{3}$$


$\text{close} \Rightarrow S.C \Rightarrow V=0 \text{ so } P=0$

$\text{open} \Rightarrow O.C \Rightarrow I=0 \text{ so } P=0$

$$\eta = 100\%$$

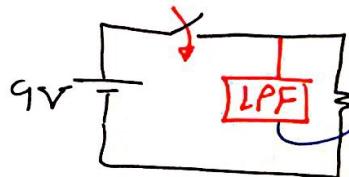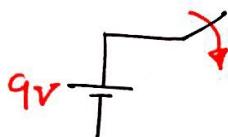

Low-Pass - Filter.

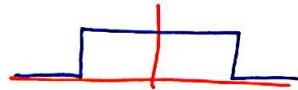

- The converter already include the filter & the switch.

QUESTION

* For an Organization like our university, which is better to use PV system or Wind system?

PV system better, because Wind system Need very large area & makes a very Large Noise.

** Types of Converters :

- ① DC to AC (inverter) → used in PV systems.
- ② AC to DC (Rectifier) → used in HVDC.
- ③ AC to AC ⇒ called AC chopper.
used for:
 - Induction motor.
 - RMS fixed to variable RMS.
 - Variable RMS to fixed RMS.

④ DC to DC \Rightarrow called DC chopper.


[4]

⑤ Cyclo Converter (Not included in our Material).
↳ Control on the frequency.


* Electronic Devices:

- Diode.
- Thyristor.
- Transistor.

1] Diode:

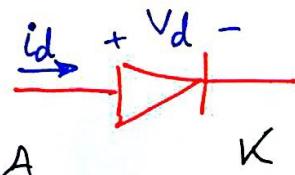

i-v-char. of diode:

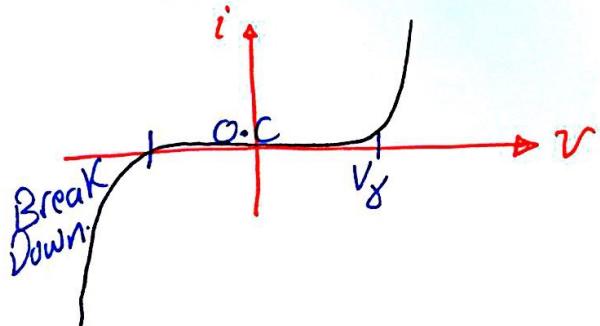

ideal i-v-char:



work almost on any voltage > 0 .
(we will deal with ideal)
diode in this course.

2] Thyristor:

• Controllable device, But Not all types.


Control (on)

Control (on/off) \rightarrow Need two circuits to do on/off.


* Types:

1) • SCR \Rightarrow Silicon Control Rectifier.

uni-direction.

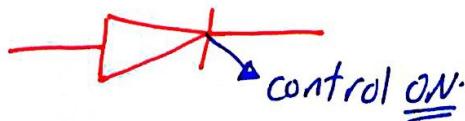


- 2) • GTO \Rightarrow Gate Turn Off.

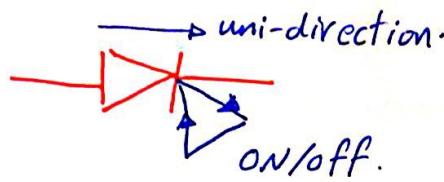

"Comutation Circuit"

5

- 3) • TRIAC


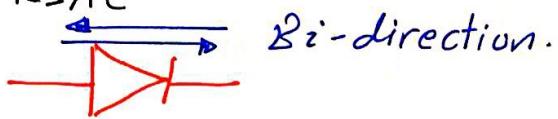


3) Transistor:

- Need just one circuit to do ON/off.
- Types: ① IGBT ② BJT ③ MOSFET

* All previous types will be used as a switch (ON/off) in PE.

* Electrical Vehicles use MOSFET.

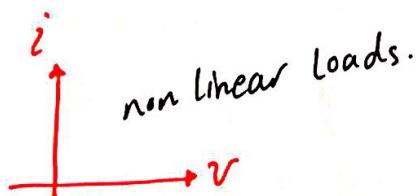
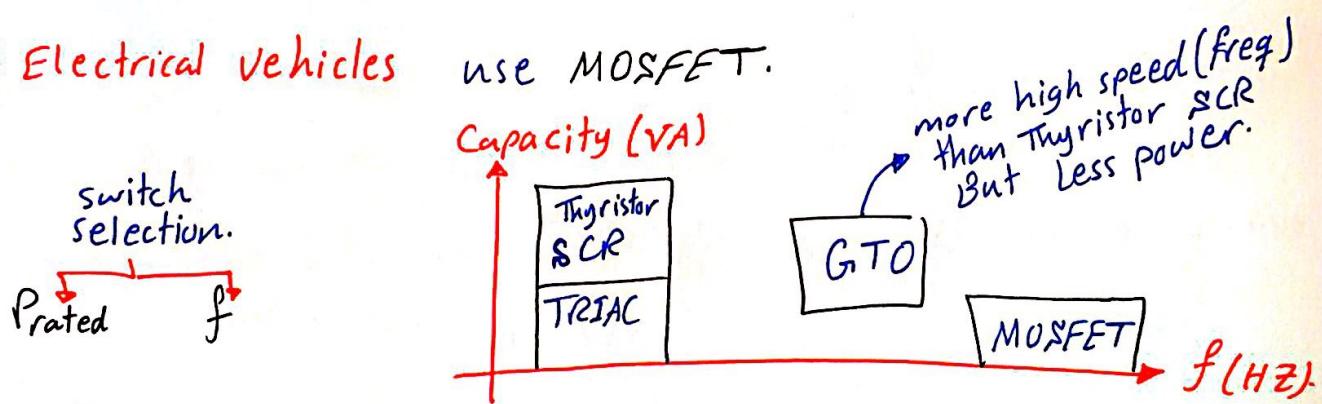


$$V(t) = A \cos \omega t$$

$$i(t) \Rightarrow \text{sinusoidal}$$

$$i(t) \Rightarrow \text{non sinusoidal}$$

$i(t) \Rightarrow$ distortion.

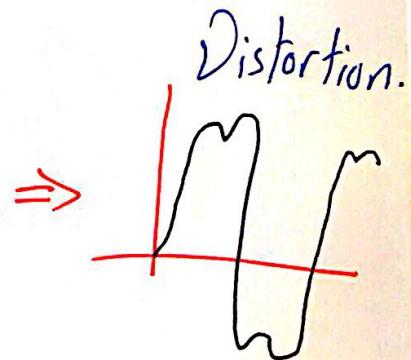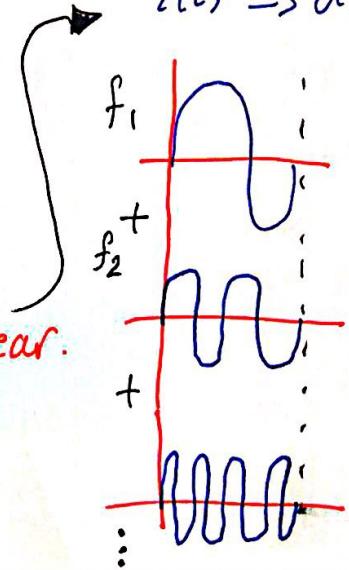


XX Harmonics:

- * Harmonics: are non sinusoidal current, voltage. that are exist in sinusoidal network. [6]

fundamental freq., other freq.

50Hz
100Hz
150Hz
⋮

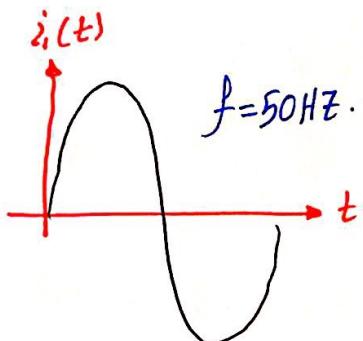

+ other currents multiple freq.

if the current increased ↑:

- 1) Over loaded Network.
 - 2) Over heating transformer.
 - 3) 3rd Harmonics - in neutral losses.
 - 4) Machines (reverse in the Rotation).
 - 5) Cause a decrease in Pf. ↓
- This added extra cost on the network.

*Analysis of Harmonics:

The best way by applying "Fourier Series".

- Fourier Series: for any non sinusoidal periodic signal $f(t)$ could be written as a sum of cosines & sines.

$$f(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos(n\omega t) + b_n \sin(n\omega t))$$

Fundamental Frequency.

a_0 = Avg. value = DC.

$$\Rightarrow a_0 = \frac{1}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} f(t) dt.$$

$$a_n = \frac{2}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} f(t) \cos(n\omega t) dt$$

$$b_n = \frac{2}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} f(t) \sin(n\omega t) dt.$$

* In Compact Form:

$$f(t) = a_0 + \sum_{n=1}^{\infty} C_n \cos(n\omega t + \theta_n)$$

$$C_n = \sqrt{a_n^2 + b_n^2}$$

$$\theta_n = \tan^{-1} \left(\frac{-b_n}{a_n} \right)$$

or we could write it as: $f(t) = a_0 + \sum_{n=1}^{\infty} c_n \sin(nwt + \theta_n)$ [7]

$$\Rightarrow \theta_n = \tan^{-1} \frac{a_n}{b_n}$$

* Evaluating RMS for $f(t)$ & the Average Power:

- RMS: $F_{\text{rms}} = \sqrt{a_0^2 + \sum_{n=1}^{\infty} \left(\frac{c_n}{T/2}\right)^2}$

- Average Power: $v(t) = V_0 + \sum_{n=1}^{\infty} V_n \cos(nwt + \theta_n)$
 $i(t) = I_0 + \sum_{n=1}^{\infty} I_n \cos(nwt + \phi_n)$

$P_{\text{avg}} = \frac{1}{T} \int_T v(t) i(t) dt$


OR $P_{\text{avg}} = V_0 I_0 + \sum_{n=1}^{\infty} V_{\text{rms},n} I_{\text{rms},n} \cos(\theta_n - \phi_n)$

OR $P_{\text{avg}} = V_0 I_0 + \sum_{n=1}^{\infty} \frac{V_{\text{max},n} I_{\text{max},n}}{2} \cos(\theta_n - \phi_n)$

Example: Non-sinusoidal voltage has the following Fourier series form:

$v(t) = 10 + 20 \cos(2\pi \cdot 60 t - 25) + 30 \cos(2(2\pi \cdot 60)t + 20)$

Connected cct as follows:

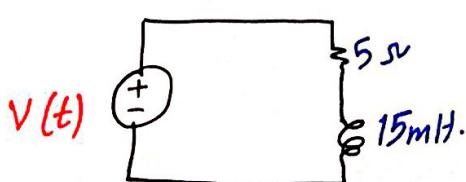



Find power absorbed by the load?

Solution: using $P_{\text{av}} = V_0 I_0 + \sum V_{\text{rms},n} I_{\text{rms},n} \cos(\theta_n - \phi_n)$

$I_0 = \frac{10}{5} = 2 \text{ A.} \quad (\text{remember @ DC, inductor S.C.}) \Rightarrow P_0 = V_0 I_0$

$P_0 = 20 \text{ W}$

$I_1 @ f = 60 \text{ Hz.}$

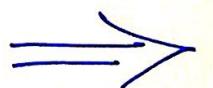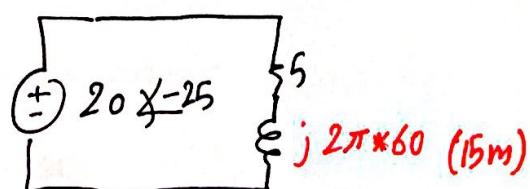

Contine.

$$\Rightarrow I_1 = \frac{20 \angle -25}{5 + j(2\pi * 60 * 0.015)} = 2.65 \angle -73.5^\circ A. \quad [8]$$

$$I_2 @ 120 \text{ Hz}: I_2 = \frac{30 \angle 20}{5 + j(2\pi * 120 * 0.015)} \Rightarrow I_2 = 2.43 \angle 46.2^\circ A.$$

$$\hookrightarrow P_1 = \frac{20}{\sqrt{2}} * \frac{2.65}{\sqrt{2}} \cos(-25 + 73.5) \\ \Rightarrow P_1 = 17.4 W.$$

$$\hookrightarrow P_2 = \frac{30}{\sqrt{2}} * \frac{2.43}{\sqrt{2}} \cos(20 + 46.2) \Rightarrow P_2 = 14.8 W.$$

$$P_{\text{Total}} = 20 + 17.4 + 14.8 \Rightarrow P_T = 52.2 W. \#$$

* Sinusoidal Source + Non linear load:

$$V_s(t) = V_s \cos(\omega t + \theta_s). \Rightarrow P_{\text{avg}} = \frac{1}{T} \int v_s(t) I(t) dt. \\ I(t) = I_0 + \sum_{n=1}^{\infty} I_n \cos(n\omega t + \theta_n) \quad = V_s I_0 + \sum_n V_{n,\text{rms}} I_{n,\text{rms}} \cos(\theta_n - \phi_n).$$

$$\Rightarrow \underline{V_0 = 0} \quad \Rightarrow \quad n=1 \text{ for } v_s(t). \quad P_{\text{avg}} = V_{s,\text{rms}} I_{1,\text{rms}} \cos(\theta_s - \phi_1), \quad Pf = \frac{P}{S}$$

$$\Rightarrow S = V_{s,\text{rms}} I_{\text{rms}} = V_{s,\text{rms}} \left[\sqrt{I_0^2 + \sum_{n=1}^{\infty} \left(\frac{I_n}{\sqrt{2}} \right)^2} \right] \quad \text{Distortion Factor} \equiv DF.$$

$$\Rightarrow Pf = \frac{V_{s,\text{rms}} I_{1,\text{rms}} \cos(\theta_s - \phi_1)}{V_{s,\text{rms}} I_{\text{rms}}} \Rightarrow Pf = \frac{I_{1,\text{rms}}}{I_{\text{rms}}} \cos(\theta_s - \phi_1)$$

Total cause Harmonics. Pf ↓

$$DF = \frac{I_{1,\text{rms}}}{I_{\text{rms}}}$$

* Total Harmonic Distortion: (THD)

$$THD = \frac{I_{\text{rms}}^2 - I_{1,\text{rms}}^2}{I_{1,\text{rms}}^2}$$

OR

$$THD = \sqrt{\sum_{n=1}^{\infty} \frac{I_{n,\text{rms}}^2}{I_{1,\text{rms}}^2}}$$

$I_{\text{rms}} \equiv$ Total which include Harmonics.

$I_{1,\text{rms}} \equiv$ Fundamental RMS current.

$$DF = \sqrt{\frac{1}{1 + (THD)^2}}$$

** for S:

$$S = V_{rms} I_{rms} = V_{rms} \sqrt{I_0^2 + \sum_{n=1}^{\infty} \left(\frac{I_n}{V_2}\right)^2} = \sqrt{P^2 + Q^2}$$

9

$$P = V_{rms} I_{1,rms} \cos(\theta_s - \phi_1)$$

$$Q = V_{rms} S \sum I_{rms} \sin(\theta_s - \phi_n)$$

....

$$S = \sqrt{P^2 + Q^2 + D^2}$$

fund.

fund.

$$\Rightarrow D = V_{1,rms} \sqrt{\sum_{n \neq 1}^{\infty} I_{n,rms}^2}$$

$$D^2 = V_{1,rms}^2 \left(\sqrt{\sum_{n \neq 1}^{\infty} I_{n,rms}^2} \right)^2$$

Example: $v(t) = 100 \cos(377t)$

$$i_L(t) = 8 + 15 \cos(377t + 30^\circ) + 6 \cos(2 \cdot 377t + 45^\circ) + 2 \cos(3 \cdot 377t + 60^\circ)$$

Find the following:

a) Power Absorbed by the load.

b) PF of the load.

c) DF Load current.

d) THD load current.

Solution:

a) $P_{av} = V_{s,rms} I_{1,rms} \cos(\theta_s - \phi_1) = \frac{100}{\sqrt{2}} * \frac{15}{\sqrt{2}} \cos(0 - 30) = 650 \text{ W.}$

b) $\text{PF} = \frac{I_{1,rms}}{I_{rms}} \cos(\theta_s - \phi_1)$

$$I_{1,rms} = \frac{15}{\sqrt{2}} \text{ A}, \quad I_{rms} = \sqrt{(8)^2 + \left(\frac{15}{\sqrt{2}}\right)^2 + \left(\frac{6}{\sqrt{2}}\right)^2 + \left(\frac{2}{\sqrt{2}}\right)^2} = 14 \text{ A.}$$


$$\Rightarrow \text{PF} = 0.66$$

c) $DF = \frac{I_{1,rms}}{I_{rms}} = 0.76$

d) $\text{THD} = 0.86.$

$$\Rightarrow \text{THD} = \sqrt{\frac{14^2 - 225}{225}} = 0.86$$

Example: Find THD:

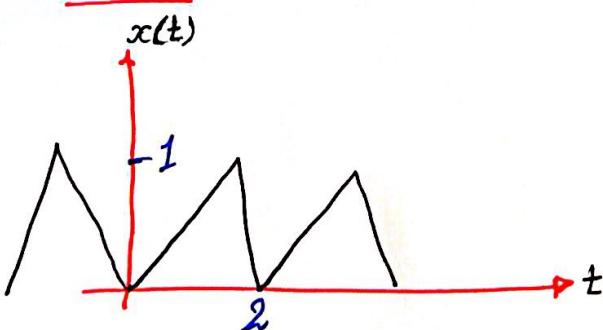

a_0, a_n, b_n

$\Rightarrow \text{RMS} \rightarrow \text{THD} \checkmark$

\Rightarrow
solution.

Solution: Assume we need THD for first 5 Harmonics.

it is even signal so $b_n = 0$

$$a_0 = \frac{1}{T} \int_T x(t) dt = \frac{1}{2} * \text{Area} = \frac{1}{2} (\frac{1}{2} * 2 * 1) \Rightarrow a_0 = \frac{1}{2}$$

$$a_n \Rightarrow x(t) = \begin{cases} t, & t > 0 \\ -t, & t < 0 \end{cases} \quad a_n = \frac{2}{T} \int_{-1}^1 x(t) \cos(n\omega t) dt$$

$$\Rightarrow a_n = 2 \int_0^1 t \cos(n\omega t) dt \quad (\text{By parts})$$

$$= 2 \left[\frac{t}{n\omega} \sin(n\omega t) + \frac{\cos(n\omega t)}{(n\omega)^2} \right]_0^1 \quad \text{Note: } \omega = \frac{2\pi}{T} = \frac{\pi}{1}$$

$$a_n = \frac{-2}{(n\pi)^2} + \frac{2 \cos(n\pi)}{(n\pi)^2} = \frac{-2 + 2(-1)^n}{(n\pi)^2}$$

even $a_n = 0$

n odd $a_n = \frac{-4}{(n\pi)^2}$

$$x(t) = \frac{1}{2} + \sum_{n=1}^{\infty} \frac{-4}{\pi^2 (2n-1)^2} \cos((2n-1)\pi t)$$

$$= \frac{1}{2} + \frac{-4}{\pi^2} \cos(\pi t) + \frac{-4}{9\pi^2} \cos(3\pi t) + \frac{-4}{25\pi^2} \cos(5\pi t)$$

$$\text{THD}^2 = \frac{X_{\text{rms}}^2 - X_{\text{rms},1}^2}{X_{\text{rms},1}^2} \Rightarrow X_{\text{rms}}^2 = \frac{1}{4} + \left(\frac{4/\pi^2}{\sqrt{2}}\right)^2 + \left(\frac{4/9\pi^2}{\sqrt{2}}\right)^2 + \left(\frac{4/25\pi^2}{\sqrt{2}}\right)^2$$

$$= 0.333$$


$$X_{\text{rms},1}^2 = \left(\frac{4/\pi^2}{\sqrt{2}}\right)^2 = 0.082$$

So Now:

$$\text{THD} = \sqrt{\frac{0.333 - 0.082}{0.082}} \Rightarrow \text{THD} = 1.75$$

* DC-DC Converter: (DC chopper).


• Application: 1) DC power source.

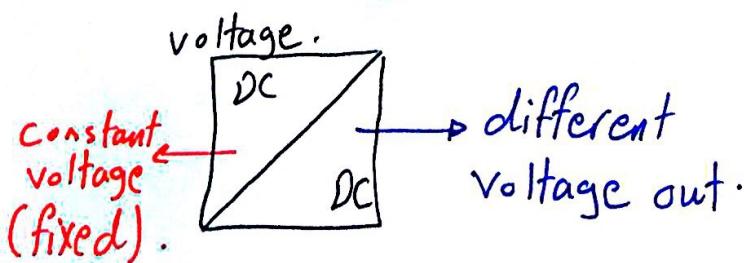

2) Speed DC motors.

↳ Control the speed of the DC motor.


- Idea:

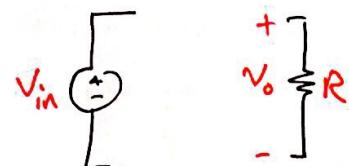


Desired $V_o < V_{in}$.

↳ solution: using ideal switch.
 \downarrow
 $V_{o\ avg} = DC$.

If switch is S/C (closed).

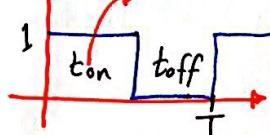

\Rightarrow

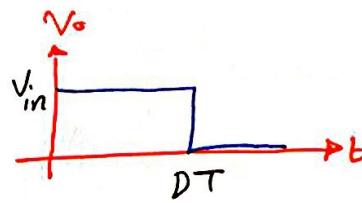

$$V_{o\ avg} = \frac{1}{T} \int_0^T V_{in} dt = DV_{in}$$

$D = \text{Duty Factor.}$

$$\Rightarrow D = \frac{t_{on}}{T} = \frac{t_{on}}{t_{on} + t_{off}}$$

⇒ solution also include using LPF.


$$f_{\text{switching}} = \frac{1}{T}$$

- * Three Types of DC-DC converter:

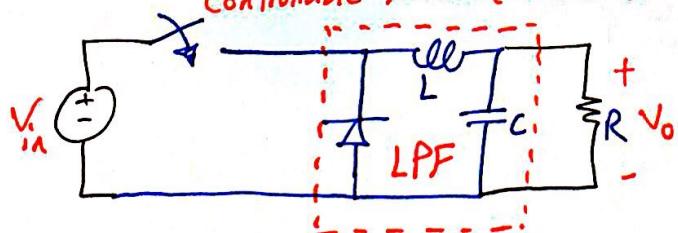- 1) step down (Buck).
- 2) step up (Boost).
- 3) step down/step up (Buck/Boost).

Buck:


⇒ Configuration:
 controllable switch (MOSFET)



* To study this circuit: (Assumptions).


- ① Switch signal: assume ideal switch.

switch

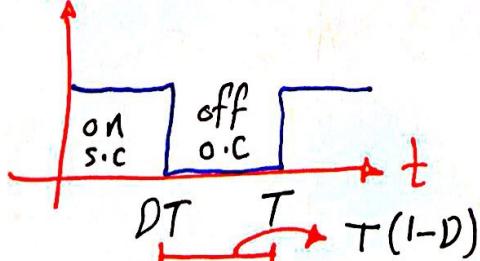


case(1):

** when switch closed:

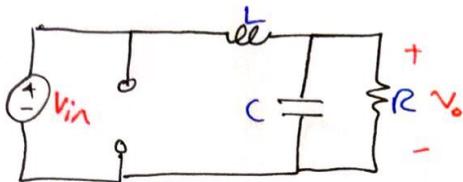 \Rightarrow Diode \rightarrow Reverse (o.c.).

case(2):

** when switch opened:

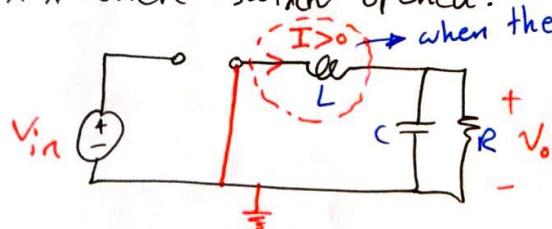


when the inductor in continuous mode.

 \Rightarrow Diode \rightarrow Forward (S.C.).Analysis:

for Case(1): @ steady state. $\begin{cases} I_{av,C} = 0 \text{ (o.c)} \\ V_{avg,L} = 0 \text{ (S.C.)} \end{cases}$


—ee— (C.C.M) continuous Current Mode. $I_L > 0$.
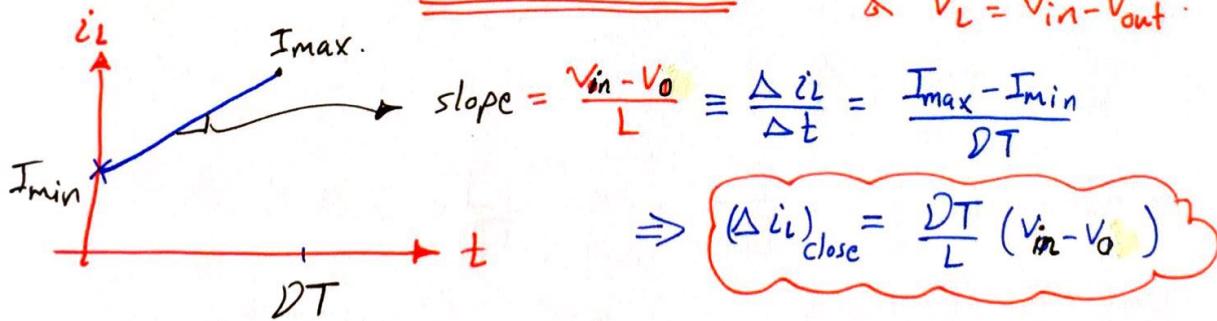
$$L \frac{di_L}{dt} = V_L \Rightarrow \frac{di_L}{dt} = \frac{1}{L} (V_{in} - V_{out}) \rightarrow \text{since } C \text{ is o.c.} \\ \& V_L = V_{in} - V_{out}$$



for Case(2):
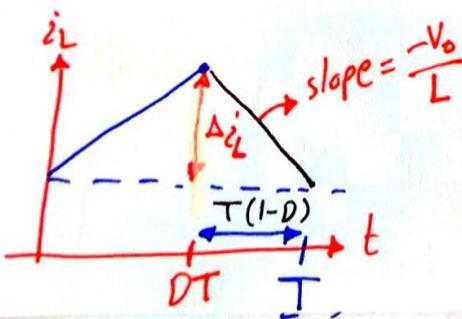
$$L \frac{di_L}{dt} = V_L = 0 - V_o \Rightarrow \frac{di_L}{dt} = -\frac{V_o}{L}$$



for S.S, C.C.M:

$$\frac{(\Delta i)^{open}}{T(1-D)} = -\frac{V_o}{L} \Rightarrow (\Delta i)^{open} = -\frac{V_o}{L} (1-D)T$$

Given S.S, C.C.M:

13


$$(\Delta i)_\text{close} + (\Delta i)_\text{open} = 0 \Rightarrow \frac{DT}{L} (V_\text{in} - V_\text{o}) + \left(\frac{-V_\text{o}}{L}\right) (1-D)T = 0$$

$$\Rightarrow DV_\text{in} - DV_\text{o} = V_\text{o} - DV_\text{o} \Rightarrow V_\text{o} = DV_\text{in}$$

- We want to design Buck converter (LPF), so find C, L .


* To find I_{\min} & I_{\max} C.C.M

$$I_{\min} > 0$$

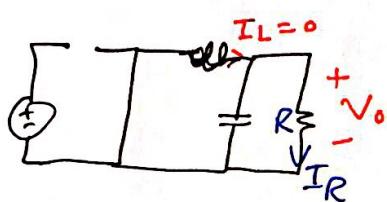

S.S: $I_{\text{av},c} = 0$
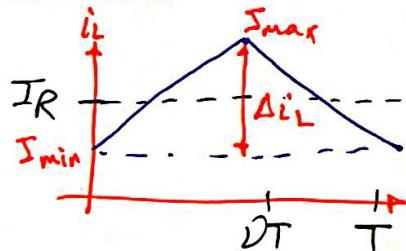
$$I_{L,\text{avg}} = I_R = \frac{V_o}{R}$$



$$I_{\max} = I_R + \frac{\Delta i_L}{2}$$

$$I_{\min} = I_R - \frac{\Delta i_L}{2}$$

for the inductor:

we choose $(\Delta i)_\text{open}$ since we want a relation with just V_o -

$$\Rightarrow I_{\min} = \frac{V_o}{R} - \frac{1}{2} \left| \left(\frac{-V_o}{L} \right) (1-D)T \right| > 0 \quad (\text{C.C.M}) \quad [L_{\min}]$$

$$\frac{V_o}{R} + \frac{1}{2} \left(\frac{V_o}{L} \right) (1-D)T > 0 \Rightarrow \frac{1}{2} \frac{V_o}{L} (1-D)T > -\frac{V_o}{R}$$


$$\Rightarrow (1-D) \frac{T}{2} > -\frac{L}{R} \Rightarrow L > \underline{\underline{\frac{1}{2} RT (1-D)}} \Rightarrow L_{\min}$$

$$L_{\min} = \frac{R}{2} T (1-D) \Rightarrow T = \frac{1}{f} \text{ so } L \propto \frac{1}{f} \quad (\text{To have } L_{\min} \text{ use Higher freq.})$$

for the capacitor:

Need to minimize V_o variation. ($\text{Ripple} = \frac{\Delta V_\text{o}}{V_\text{o}}$).


need it $\ll 1$

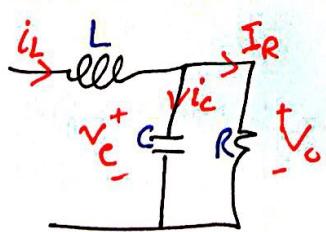

$$C \frac{dV_c}{dt} = i_C \Rightarrow V_c = \frac{1}{C} \left(\int i_C dt \right)$$

$$\frac{\Delta q}{\Delta t} = i \Rightarrow \Delta q = i \Delta t \quad \int \underline{\underline{q}}$$

$$i_c = i_L - I_R$$

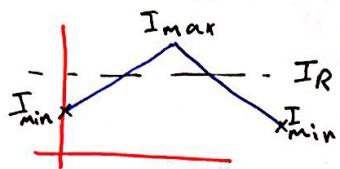

$$I_{\min} = \frac{V_o}{R} - \frac{1}{2} \left(\frac{V_o}{L} \right) (1-D) T$$

$$\bullet I_{C,\min} = I_{\min} - I_R \quad \text{--- } \frac{V_o}{R}$$

$$I_{C,\min} = -\frac{1}{2} \left(\frac{V_o}{L} \right) (1-D) T$$

$$\bullet I_{C,\max} = I_L - \frac{V_o}{R}$$

$$\Rightarrow I_{C,\max} = \frac{T V_o (1-D)}{2L}$$

$$i_c = C \frac{dV_C}{dt}$$

$$i_c = \frac{dq}{dt} = C \frac{dV_C}{dt} \Rightarrow \Delta q = C \Delta V_C$$

same $\underline{\Delta V_o}$

$$I_{\max,2} = V_o \left(\frac{1}{R} + \frac{(1-D)}{2Lf} \right)$$

$$I_{\min,2} = V_o \left(\frac{1}{R} - \frac{(1-D)}{2Lf} \right)$$


$$L = \frac{(V_{in}-V_o)D}{\Delta i_L f}$$

$$L = \frac{(V_o - V_s)D}{\Delta i_L f} \Rightarrow L = \frac{V_o (1-D)}{\Delta i_L f}$$

$$* \text{ Ripple} = \underline{\frac{\Delta V_o}{V_o}} \Rightarrow \underline{i_c = i_L - I_R}$$

Derive I_{\max} :
it will result:
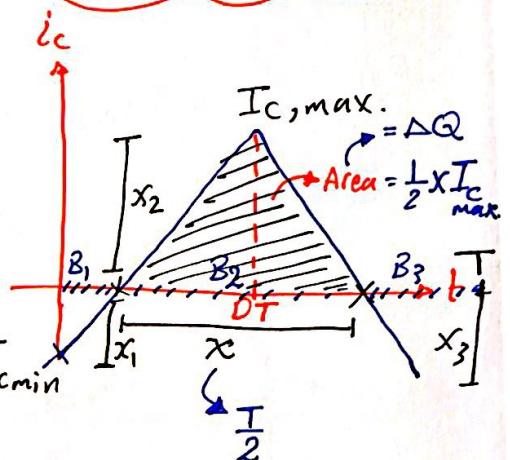
$$I_{\max} = V_o \left(\frac{1}{R} + \frac{T(1-D)}{2L} \right)$$



from $I = \frac{q}{t}$ & $I_{C,\max}$
find C?!

"used when R is"
Unknown.

* Note on the graph of i_c vs. t : Distance $x_1 = x_2 = x_3$

$$\text{also } B_1 + B_3 = B_2 \quad B_1 + B_2 + B_3 = T$$


$$\text{so } B_2 = \frac{T}{2}$$

$$i_c = C \frac{dV_C}{dt}, \Delta Q = C \Delta V$$

$$\Rightarrow i_c = \frac{dq}{dt} \Rightarrow \Delta q = \int i_c dt \quad (i > 0)$$

$$\text{so } \Delta V = \frac{\Delta Q}{C} = \frac{\int i_c dt}{C}$$
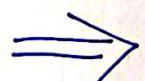
$$\Delta Q = \text{positive area of } I_c = \frac{1}{2} B_2 I_c = \frac{1}{2} \left(\frac{T}{2} \right) \left(\frac{V_o (1-D)}{2Lf} \right)$$




$$\Delta V_o = \frac{\Delta Q}{C} = \frac{V_o(1-D)}{8Lf^2C}$$

$$\Rightarrow \text{Ripple} = \frac{\Delta V_o}{V_o} = \frac{(1-D)}{8Lf^2C}$$


from this equation we find C.

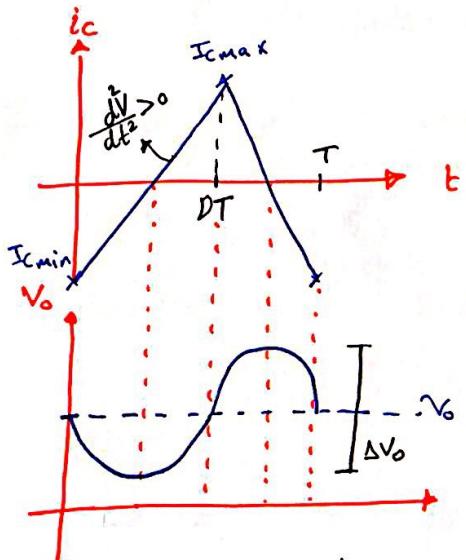*Note: In practice: $L = 1.25 L_{\min}$ $\uparrow f \Rightarrow \text{heat loss} \uparrow$



$$i_C = C \frac{dV}{dt} \\ \Rightarrow V = \frac{1}{C} \int i_C dt.$$

remember:

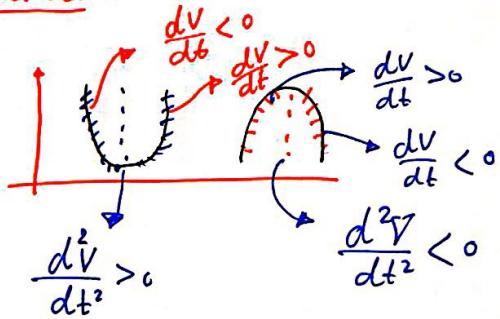

we have min & max of V_o
when $i_C = 0$.

Example: Buck converter has the following:

$$V_s = 50V, D = 0.4, L = 400\mu H, C = 100\mu F, f = 20KHZ, R = 20\Omega$$

Find: a) V_o b) $I_{L,\max}, I_{L,\min}$ c) V_o, Ripple .

Solution:


$$a) V_o = DV_{in} = (0.4)(50) \Rightarrow V_o = 20 \text{ volt.}$$

$$b) I_{L,\max} = V_o \left(\frac{1}{R} + \frac{(1-D)}{2Lf} \right) \Rightarrow I_{L,\max} = 1.75A.$$

$$I_{L,\min} = V_o \left(\frac{1}{R} - \frac{(1-D)}{2Lf} \right) \Rightarrow I_{L,\min} = 0.25A.$$

$$c) \text{Ripple} = \frac{\Delta V_o}{V_o} = \frac{1-D}{8Lf^2C} \Rightarrow \text{Ripple} = 0.47\%$$

*Note: In practice:

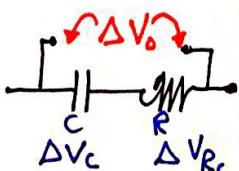

$\Delta V_o = \Delta V_C + \Delta V_{Rc}$ But ΔV_C very small compare to ΔV_{Rc}

$$*\Delta V_o \approx \Delta V_{Rc} = i_C R_C *$$

$$\Delta i_c = I_{C_{\max}} - I_{C_{\min}} = 2 \left(\frac{V_o(1-D)}{2Lf} \right) \Rightarrow \boxed{\Delta i_c = \frac{V_o(1-D)}{Lf}}$$

16

for the example: $\boxed{\Delta i_c = 1.5A}$.


$$\text{given } r_C = 0.1 \Omega \Rightarrow \text{Ripple} = \frac{\Delta V_o}{V_o} = \frac{(0.1)(1.5)}{20} = \underline{0.75\%}$$

Homework: For the example Re-design the Buck ($f_{\text{new}} > f_{\text{new}}$)
To make ripple $< 0.47\%$

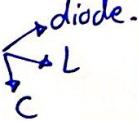Example: Design a buck converter to produce $V_o = 18V$ across $R = 10\Omega$ with switching freq. 40KHZ Given that:

- V_o Ripple $\leq 0.5\%$
- DC supply = $48V$.
- Ideal component, C.C.M, S.S. ($r_C = 0$)

Determine: a) Duty cycle. b) L, C c) Find the peak voltage for each device d) RMS of I_L, I_C .




Solution:

$$a) D = \frac{V_o}{V_{in}} = \frac{18}{48} \Rightarrow \boxed{D = 0.375}$$

$$b) L_{\min} = \frac{(1-D)R}{2f} \Rightarrow \text{in Design: } L_{\min} * 1.25 = L \\ \Rightarrow \boxed{L_{\min} = 78\mu H} \quad \boxed{L = 97.5\mu H}$$

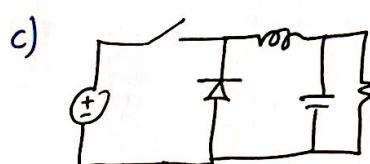
$$c) C = \frac{(1-D)}{8Lf^2 * \text{Ripple}} = \frac{1 - 0.375}{8 * 97.5\mu H (40K)^2 (0.005)} \Rightarrow \boxed{C = 100\mu F}$$



- Diode:
switch closed $\Rightarrow V_D = V_{in} = \underline{48\text{ volt}}$.
switch opened $\Rightarrow V_D = \underline{0}$

$$d) \begin{aligned} \bullet L: & \text{switch closed} \Rightarrow V_L = V_{in} - V_o = 48 - 18 = \underline{30V} \\ & \text{switch opened} \Rightarrow V_L = -V_o = \underline{-18V} \end{aligned}$$
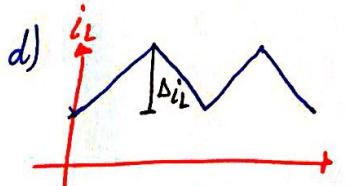
$$\bullet C: \quad V_C = V_o = \underline{18V}$$



For I_C (No DC):

$$I_{C_{rms}} = \frac{\Delta i}{\sqrt{3}} \Rightarrow \boxed{I_{C_{rms}} = 0.83A}$$

if we need $I_{L_{\max}}$:



$$I_{L_{\max}} = \frac{V_o}{R} + \frac{\Delta i}{2}$$

$$I_{L_{\max}} = \sqrt{(DC)^2 + \left(\frac{\Delta i}{\sqrt{3}}\right)^2} \\ \Delta i = DT \left(\frac{V_{in} - V_o}{L} \right) \Rightarrow \boxed{I_{L_{\max}} = 1.98A}$$

*Discontinuous Current Mode (D.C.M.):

Need a relation for:
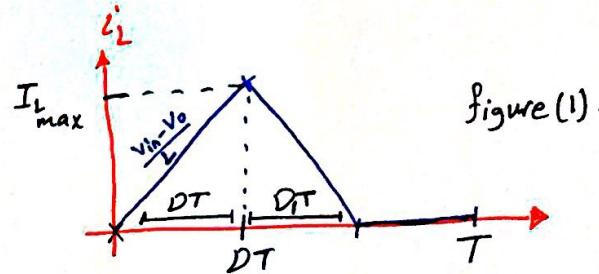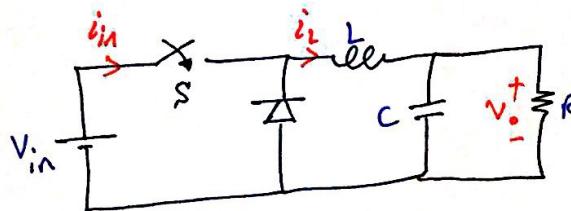
$$V_o, V_{in} \Rightarrow D, D_1, R, L, C$$



figure(1).

$$V_L = L \frac{di}{dt}$$

$$0 \rightarrow DT \Rightarrow V_L = V_{in} - V_o$$


$$> DT \Rightarrow V_L = -V_o$$

*for ideal case:

$$P_{in} = P_{out} \Rightarrow V_{in} i_{in} = \frac{V_o^2}{R}$$

$$P_{avg, L} = 0 = \langle V_L \rangle \langle i_L \rangle \text{ so, } \langle V_L \rangle = 0$$

$$@ S.S: \langle V_C \rangle = 0$$

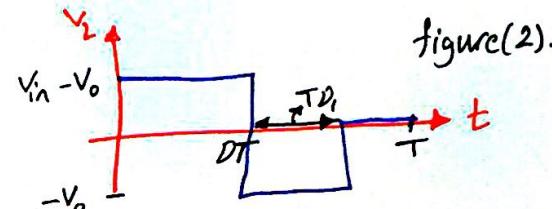

figure(2).

$$\text{For figure(2): } \langle V_L \rangle = 0 \Rightarrow (V_{in} - V_o) DT = V_o D_1 T$$

$$(V_{in} - V_o) D = D_1 V_o$$

$$\Rightarrow D V_{in} - V_o D = V_o D_1 \Rightarrow D V_{in} = V_o (D + D_1) \Rightarrow V_o = V_{in} \frac{D}{D + D_1}$$

from figure(1): slope.

$$V_L = L \frac{di}{dt} = L \left(\frac{I_{max}}{DT} \right) = \frac{V_{in} - V_o}{L} * L \Rightarrow V_{in} - V_o = \frac{L I_{max}}{DT}$$

$$\Rightarrow I_{max} = \frac{DT}{L} (V_{in} - V_o)$$

$$\langle i_L \rangle = \frac{V_o}{R} = \frac{1}{T} \left(\frac{1}{2} (DT + D_1 T) I_{max} \right) = \frac{V_o}{R} \Rightarrow \frac{1}{2} (D + D_1) I_{max} = \frac{V_o}{R}$$

$$\Rightarrow (D_1 + D) DT \frac{(V_{in} - V_o)}{L} = \frac{2V_o}{R} \Rightarrow DT (D + D_1) (V_{in} - V_o) = \frac{2L V_o}{R}$$

$$\Rightarrow D^2 V_{in} - D^2 V_o + DD_1 V_{in} - DD_1 V_o = \frac{2L V_o}{RT} \Rightarrow V_o = V_{in} \left(\frac{D}{D + D_1} \right)$$

$$(DD_1 + D^2) V_{in} - V_o (D^2 + DD_1 + \frac{2L}{RT}) = 0 \Rightarrow DD_1 + D^2 - \frac{V_o}{D + D_1} (D^2 + DD_1 + \frac{2L}{RT}) = 0$$

Divide equation by D then multiply by (D + D_1):

$$\Rightarrow (D_1 + D)(D + D) = D^2 + DD_1 + \frac{2L}{RT} \Rightarrow D_1^2 + 2DD_1 + D^2 = D^2 + DD_1 + \frac{2L}{RT}$$

$$\Rightarrow D_1^2 + DD_1 - \frac{2L}{RT} = 0$$

contine.

solving the equation: $D_1 = \frac{-D \pm \sqrt{D^2 - 4\left(\frac{-2L}{RT}\right)}}{2}$

\Rightarrow So,

$$D_1 = \frac{-D + \sqrt{D^2 + \frac{8L}{RT}}}{2}$$

$$V_o = V_{in} \left(\frac{D}{D+D_1} \right)$$

D.C.M.

$$D_1 < 1-D$$

negative answer
is neglected.

Example: A Buck converter has the following parameters:

$$V_{in} = 24V, L = 200\mu H, R = 20\Omega, f = 10KHZ, D = 0.4$$


a) Is this Buck work in C.C.M or D.C.M?

b) Find V_o ? c) Plot V_o as a function of D ?

Solution:


a) $D_1 = \frac{-0.4 + \sqrt{(0.4)^2 + \frac{8(200\mu)}{20 * \frac{1}{10K}}}}{2} = 0.29$, $1-D = 1-0.4 = 0.6$
since $D_1 < 1-D$
it is **D.C.M**

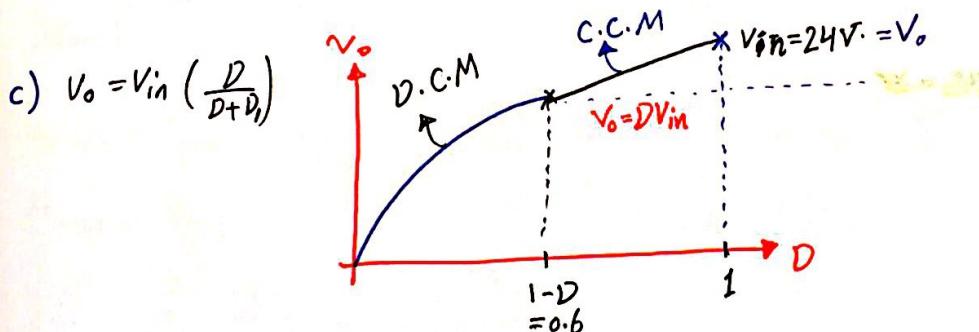b) $V_o = 24 \left(\frac{0.4}{0.29+0.4} \right) \Rightarrow V_o = 13.9V$.



• Boost Converter:

* circuit configuration:

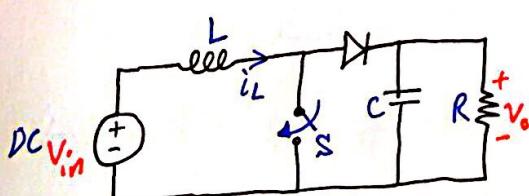

we need relations for:

$$V_o, V_{in}$$

$$I_{L_{avg}}, I_{L_{max}}, I_{L_{min}} \Rightarrow L$$


$$i_c, V_c \Rightarrow \text{Ripple} \Rightarrow C$$

* Assumption:

- ideal component.
- steady state.

- C.C.M ($I_L > 0$).

switch.

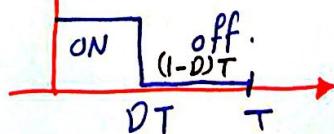

case(1): switch closed. ($t \leq DT$)


- Diode Reverse (o.c.).

$$V_L = V_{in}$$

$$V_L = L \frac{di_L}{dt} = V_{in} \Rightarrow \frac{di_L}{dt} = \frac{V_{in}}{L} = \text{constant.}$$

$$\therefore \frac{V_{in}}{L} = \frac{(\Delta i_L)_{\text{closed}}}{DT}$$
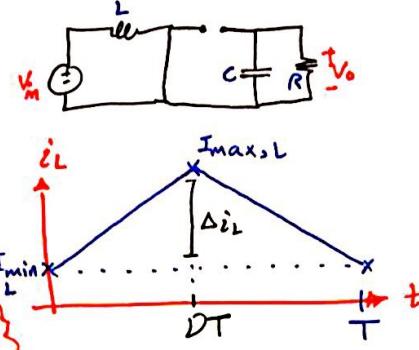
$$\Rightarrow (\Delta i_L)_{\text{closed}} = V_{in} \frac{DT}{L} = \frac{V_{in} D}{L f}$$



case(2): switch off ($t > DT$)

- Diode (S.C.).

$$V_L = V_{in} - V_{out} = L \frac{di_L}{dt}$$

$$\frac{di_L}{dt} = \frac{1}{L} (V_{in} - V_{out}) = \frac{(\Delta i_L)_{\text{open}}}{(1-D)T}$$

$$\Rightarrow (\Delta i_L)_{\text{open}} = \frac{(V_{in} - V_o)(1-D)}{L f}$$



$$\Delta i_L^{\text{open}} + \Delta i_L^{\text{closed}} = \text{Zero} \Rightarrow$$

$$\text{so } V_o = \frac{V_{in}}{1-D} \quad D < 1$$

$$\frac{V_{in} - V_o}{L f} (1-D) + \frac{V_{in} D}{L f} = 0 \Rightarrow V_{in} - D V_{in} - V_o + D V_o + V_{in} D = 0$$

Note that: if $D=1 \Rightarrow V_o = \infty$ (always switch is ON)
if $D=0 \Rightarrow V_o = V_{in}$ (always off)

$$I_{L\max} = I_{L\text{avg}} + \frac{\Delta i_L}{2}$$

$$\text{for } I_{L\text{avg}}: P_{in} = P_{out} \Rightarrow V_{in} I_{L\text{avg}} = \frac{V_o^2}{R}$$

$$I_{L\min} = I_{L\text{avg}} - \frac{\Delta i_L}{2}$$

$$\Rightarrow I_{L\text{avg}} = \frac{V_o^2}{V_{in} R} = \left(\frac{V_{in}}{1-D}\right)^2 \left(\frac{1}{V_{in} R}\right) \Rightarrow I_{L\text{avg}} = \frac{V_{in}}{(1-D)^2 R}$$

$$I_{L\max} = \frac{V_{in}}{R(1-D)^2} + \frac{V_{in} D}{2L f}$$

@ C.C.M: $I_{L\min} > 0$ we find L_{\min} .

$$\frac{V_{in}}{(1-D)^2 R} - \frac{V_{in} D}{2L f} > 0 \Rightarrow L > \frac{D(1-D)^2 R}{2f}$$


$$\text{so } L_{\min} = \frac{D(1-D)^2 R}{2f}$$


* for case(1): $i_C = -\frac{V_o}{R}$ (-ve current)

* for case(2): $i_C = I_L - \frac{V_o}{R}$

$$\Delta i_C = \Delta i_L - \frac{V_o}{R}$$
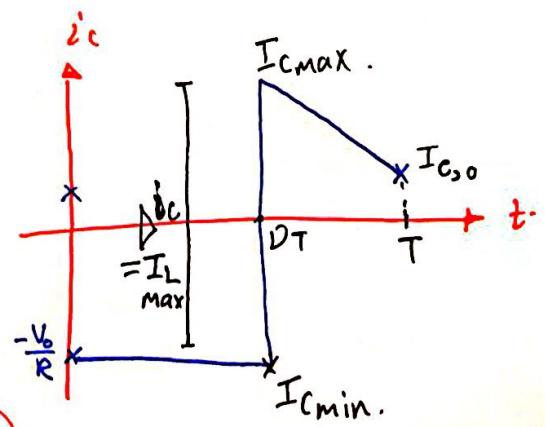
$$= I_{L\max} - \frac{V_o}{R} - \left(-\frac{V_o}{R}\right) \text{ so } \Delta i_C = I_{L\max}$$



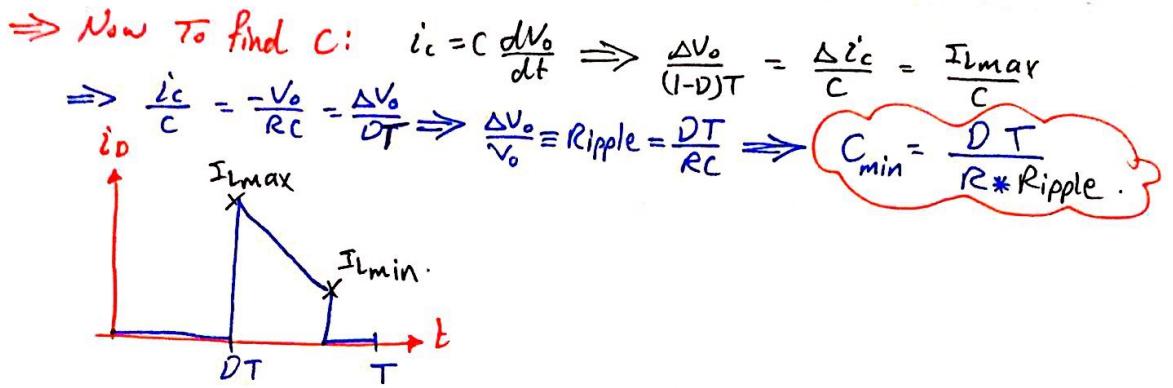

Example: Design a Boost Converter that will have $V_o = 30V$, $V_s = 12V$, Ripple Voltage $\leq 1\%$.
 $R_L = 50\Omega$, $f_s = 25\text{KHZ}$. Given C.C.M.

Find: $\rightarrow D$, L_{\min} , C , $I_{L\max}$ & $I_{L\min}$?

Solution:

$$V_o = \frac{V_{in}}{1-D}$$

$$30 = \frac{12}{1-D} \Rightarrow D = 0.6$$

$$C = \frac{D}{R_f * \text{Ripple}} \Rightarrow C = 48\mu F$$

$$L = DT \frac{(1-D)^2 R_L}{2} = 96\mu H$$

$$\Rightarrow L = 120\mu H$$

In Design:

$$L = L_{\min} * 1.25$$

$$\text{Now for } I_L: I_{L\max} = I_{L\avg} + \frac{\Delta i_L}{2}$$

$$I_{L\avg} = \frac{V_{in}}{(1-D)^2 R} = 1.5A$$

$$\Delta i_L = DT \frac{V_{in}}{L} = 2.4A$$

substitute:

$$I_{L\max} = 2.7A$$

$$I_{L\min} = 0.3A$$

Note $I_{L\min} > 0$
 $\therefore C.C.M.$

Example: A Boost Converter has the following Requirements:

1) $V_o = 8V$, Load current = 1A.

2) $2.7 \leq V_{in} \leq 4.2$

3) Duty cycle is controlled to keep V_o constant, $f = 200\text{KHZ}$.

Determine: ① L s.t. the variation in the inductor current $\leq 40\% I_{L\avg}$.

② C s.t. Ripple Voltage $\leq 2\%$. ③ Max R_C s.t. Ripple voltage $\leq 2\%$.

Solution:

for $V_{in} = 2.7V$

$$\text{for } D \Rightarrow V_o = \frac{V_{in}}{1-D} \Rightarrow 8 = \frac{2.7}{1-D}$$

$$D = 0.663$$

$$L = \frac{DT V_{in}}{\Delta i_L}; \Delta i_L \leq 0.4 I_{L\avg}$$

$$\Rightarrow I_{L\avg} = \frac{V_{in}}{(1-D)^2 R} \Rightarrow I_{L\avg} = 2.96A$$

$$\Delta i_L \leq 2.96 * 0.4 = 1.19A. \quad \text{so } L = 7.5\mu H$$

$$\text{for } V_{in} = 4.2 \text{ volt.} \Rightarrow I_{L\avg} = 1.9A$$

$$L = 13.1\mu H$$

\Rightarrow we select this L since it is larger.

* for this design:

choose $D = 0.475$ & $L = 13.1\mu H$.
 $\text{@ } 4.2V$


$$C = \frac{D}{R_f * \text{ripple.}} = \frac{0.663}{8 * 200K * 0.02} = 20.7 \mu F \quad \text{choosing the higher } C.$$

$$I_{L\max} = I_{L\text{avg}} + \frac{\Delta i_L}{2} \quad \Delta i_L = \frac{DT}{L} V_s$$

$$I_{L\max} @ 2.7V = 2.96 + \frac{\Delta i_L}{2} = 3.6A. \quad I_{L\max} @ 4.2V = I_{L\text{avg}} + \frac{\Delta i_L}{2} = 2.28$$

$$\frac{\Delta V_o}{V_o} = 0.02 \Rightarrow \Delta V_o = 0.02 V_o \Rightarrow \Delta V_o = I_{L\max} r_C \Rightarrow r_C = \frac{0.02 * 8}{3.6} \Rightarrow r_C = 44 \text{ m}\Omega$$



$\Delta I_C = I_{L\max}$.

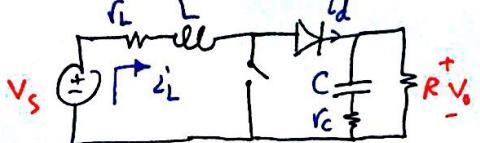

r_L in boost converter effect on the relation between V_s & V_o unlike buck converter.

Average: $P_{in} = P_{out} + P_{loss}$ $\rightarrow P_{loss} \text{ in Buck converter} = 0$
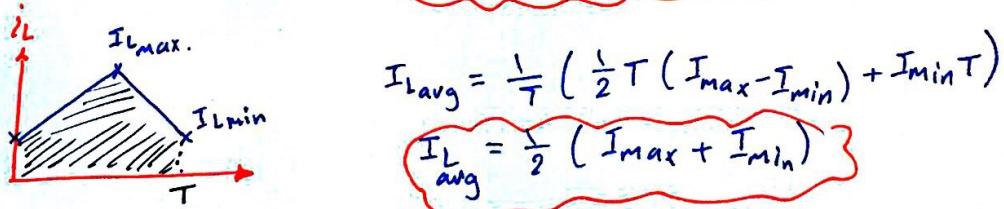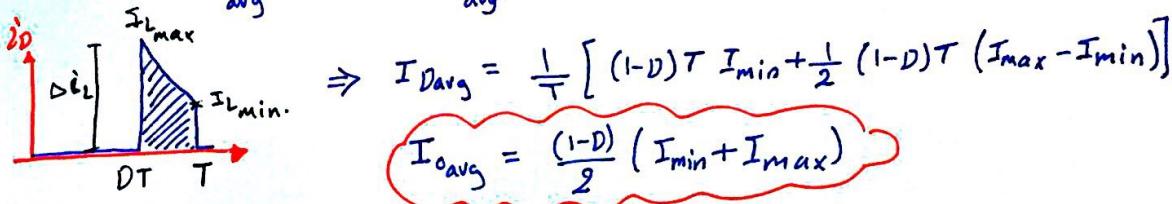
$$V_s I_{L\text{avg}} = V_o I_o + r_L I_{L\text{avg}}^2 \quad I_{o\text{avg}} = I_{D\text{avg}} - I_{C\text{avg}}$$



So, $I_{o\text{avg}} = (1-D) I_{L\text{avg}}$, $P_{in} = V_s I_{L\text{avg}} = V_o (1-D) I_{L\text{avg}} + r_L I_{L\text{avg}}^2$

$$V_o = \frac{V_s}{1-D} ; \text{ without } r_L$$


$$V_o = \frac{V_s}{1-D} \left[\frac{1}{1 + \frac{r_L}{R_o(1-D)^2}} \right] ; \text{ with } r_L$$

inductor resistance. Load resistance.

$$\frac{V_o}{P_o} \downarrow = \frac{V_o^2}{R} = I^2 R$$




$I_o \downarrow$
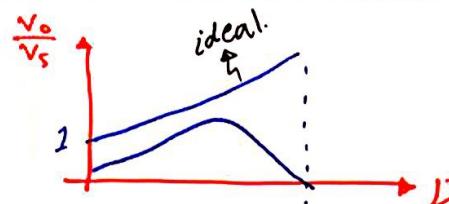
$$\frac{V_o}{V_s} = \frac{1}{1-D} \left(\frac{1}{1 + \frac{r_L}{R(1-D)^2}} \right)$$



* Efficiency: $\eta = \frac{P_o}{P_{in}} = \frac{V_o^2/R = P_o}{P_o + P_{loss}} \rightarrow I_L^2 r_L \Rightarrow \eta = \frac{1}{1 + \frac{r_L}{R(1-D)^2}}$

* Discontinuous Current Mode:

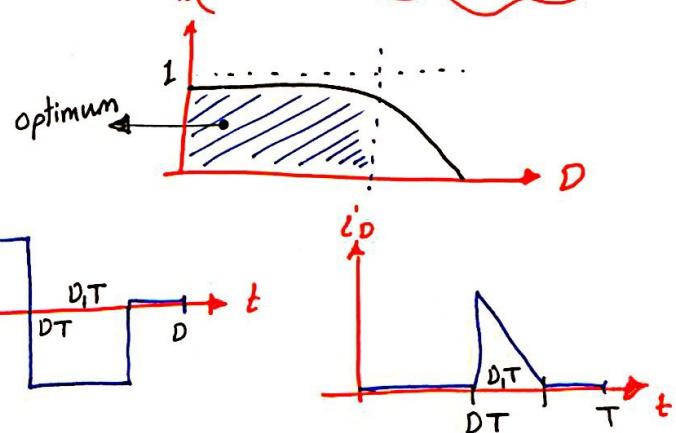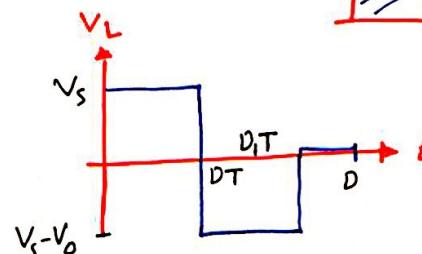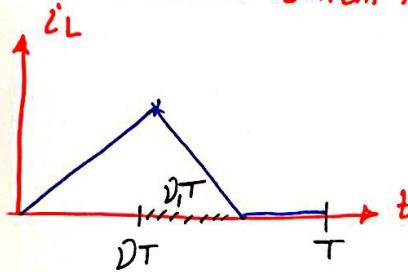

@ S.S: $V_{Lavg} = 0 \Rightarrow \frac{1}{T} [V_s D T + (V_s - V_o) D_1 T] = 0$

$$\Rightarrow V_s D + V_s D_1 - V_o D_1 = 0 \Rightarrow V_o = \frac{V_s}{D_1} (D + D_1) \dots ①$$

$$i_{Davg} = I_{oavg} = \frac{V_o}{R} \Rightarrow \frac{V_o}{R} = \frac{1}{T} \left[\frac{1}{2} D_1 T I_{Lmax} \right]$$

$$\frac{di}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{I_{max} - 0}{DT} = \frac{V_s}{L} \Rightarrow I_{max} = \frac{V_s D T}{L}$$

$$\Rightarrow D_1 = \frac{2 V_o L}{R V_s D T} \quad ②$$

Substitute ② in ①: (solve the equation)

$$\frac{V_o}{V_s} = \frac{1}{2} \left(1 + \sqrt{2 D^2 R T + 1} \right) \rightarrow \text{Discontinuous.}$$

$$\frac{V_o}{V_s} = \frac{1}{1-D} \rightarrow \text{Continuous.}$$

Example: A Boost converter $V_s = 20V$, $C = 100\mu F$, $D = 0.6$, $L = 100\mu H$, $R = 50$, $f = 15KHz$.

1) Verify that the inductor is in D.C.M ? 2) find V_o ? 3) find I_{Lmax} ?

Solution: C.C.M D.C.M

1) $I_{Lmin} = 0 \text{ or } < 0 \Rightarrow I_{Lmin} = \frac{V_s}{R(1-D)^2} - \frac{V_s D T}{2L} = \underline{-1.5A}$.



2) $V_o = \underline{60 \text{ volt.}}$

3) $I_{Lmax} = \frac{V_s D T}{L} = \underline{8A}$.

Buck-Boost Converter:

@ S.S, C.C.M:

$$I_{L\min} \geq 0$$

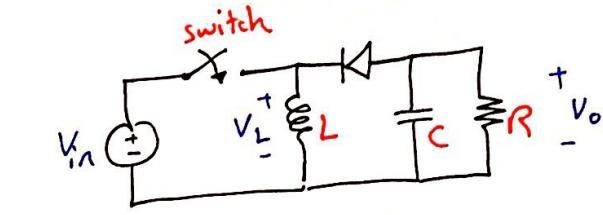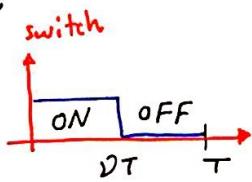

$$f = \frac{1}{T}$$

case(1): switch close: Diode O.C.

$$V_{in} = V_L = L \frac{di}{dt} \Rightarrow \frac{\Delta i}{DT} = \frac{V_{in}}{L} \Rightarrow (\Delta i)_{close} = V_{in} \frac{DT}{L}$$

case(2): switch open (off): Diode S/C.

$$V_L = V_o = L \frac{di_L}{dt} \Rightarrow (\Delta i_L)_{open} = V_o \frac{(1-D)T}{L}$$

→ DC Machines

As we know: $(\Delta i)_{close} + (\Delta i)_{open} = 0 \Rightarrow V_{in} \frac{DT}{L} + V_o \frac{(1-D)T}{L} = 0 \Rightarrow V_o = -\frac{V_{in} D}{1-D}$



if $\frac{D}{1-D} > 1$ it will work as Boost.

$$\Rightarrow D > 1-D \Rightarrow D > 0.5 \rightarrow \text{work as Boost.}$$


$$D < 0.5 \rightarrow \text{work as Buck.}$$

for Average Values:
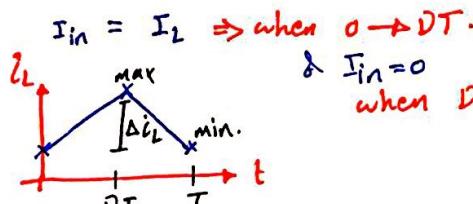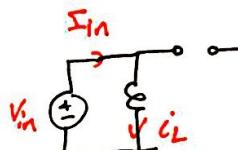
$$P_{in} = P_{out} \rightarrow V_{in} (I_{in})_{av} = \frac{V_o^2}{R}$$



& $I_{in} = 0$ when $DT \rightarrow T$

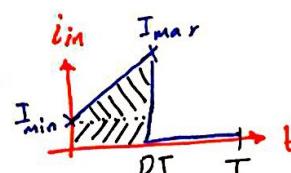

$$\text{so } (I_{in})_{av} = \frac{1}{T} [DT I_{L\min} + \frac{1}{2} DT (I_{max} - I_{min})] = \frac{D}{2} [I_{max} + I_{L\min}]$$

$$(I_L)_{av} = \frac{1}{T} [T I_{L\min} + \frac{1}{2} T (I_{max} - I_{min})] = \frac{I_{max} + I_{min}}{2}$$

$$\text{so } I_{in\ avg} = D I_{L\ avg}$$

$$\text{Now: } V_{in} I_{in\ avg} = \frac{V_o^2}{R} \rightarrow V_{in} D I_{L\ avg} = \left(\frac{V_{in} D}{1-D}\right)^2 * \frac{1}{R} \rightarrow I_{L\ avg} = \frac{V_{in} D}{(1-D)^2 R}$$

$$\Rightarrow I_{L\ min} = I_{L\ avg} - \frac{\Delta i_L}{2} \Rightarrow \Delta i_L = \frac{DT V_{in}}{L}$$


⇒ continue .

Now $I_{L\min}$ becomes:

$$I_{L\min} = \frac{V_{in}D}{(1-D)^2 R} - \frac{1}{2L} DT V_{in} \quad \text{remember @ C.C.M} \quad I_{L\min} > 0 \rightarrow \text{we found } L_{\min}.$$

$$V_{in}D \left(\frac{1}{R(1-D)^2} - \frac{1}{2L} \right) > 0 \Rightarrow L_{\min} = \frac{1}{2} R (1-D)^2$$

Now for C: from the Ripple.

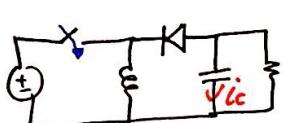


$$i_c = C \frac{dV_o}{dt} = C \frac{\Delta V_o}{\Delta t}$$

when switch on (Diode o/c).

$$i_c = -\frac{V_o}{R}$$

when switch off (Diode s/c).

$$i_c = I_L - \frac{V_o}{R}$$

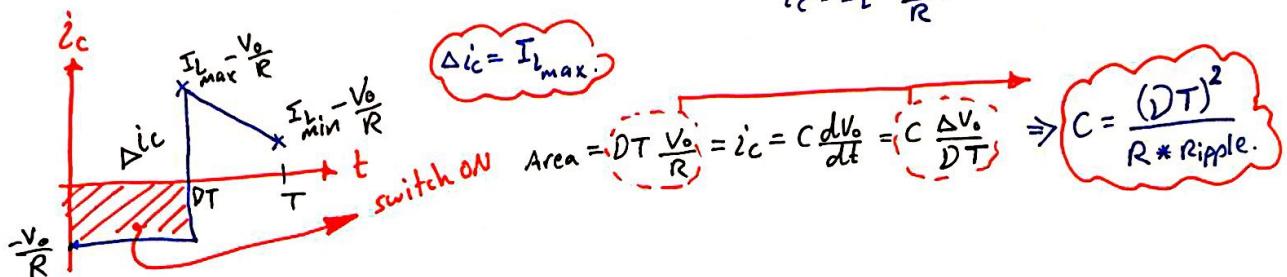

*if there is r_L There is NO effect.

*if there is r_C as we took in Buck: $\Delta V_o = \Delta i_C r_C$ & $\Delta i_C = I_{L\max}$.

Example: Buck-Boost Converter has the following: $V_{in} = 24V$, $D = 0.4$, $R_L = 5\Omega$, $L = 20\mu H$, $C = 80\mu F$, $f = 100\text{KHz}$.

Find: V_o , I_{avg} , $I_{L\min}$ & $I_{L\max}$, Ripple?

Solution: since $D = 0.4$ here it is Buck.

$$V_o = -V_{in} \frac{D}{1-D} \Rightarrow V_o = -16V, \quad I_{L\avg} = \frac{V_{in}D}{R(1-D)^2} = 5.33A, \quad \Delta i_L = \frac{DT V_{in}}{L} = 4.8A.$$

$$I_{L\min} = 5.33 - \frac{4.8}{2} \quad \text{To be sure } I_{L\min} \text{ must be } > 0. \quad \text{Ripple} = \frac{\Delta V_o}{V_o} = \frac{(DT)^2}{RC}$$

Example: A Buck Converter has a switch that open & close @ 20Hz. and remains close. for 3ms per cycle. if the avg Load current is 70A.



Find: Avg inductor current & Avg source Current?

Solution: $t_{on} = 3\text{msec}$


$$T = \frac{1}{20}$$


$$\Rightarrow DT = t_{on}$$

$$\text{so } D = 0.06$$

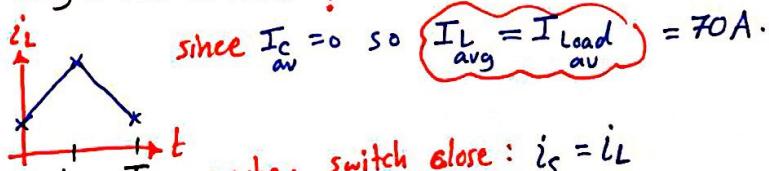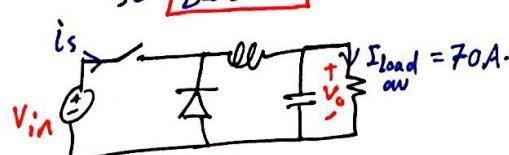

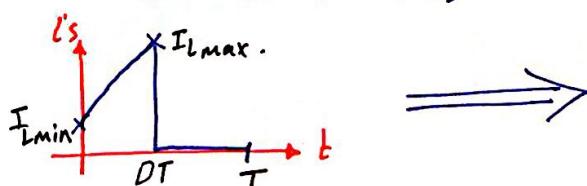
*when switch close: $i_S = i_L$
- - - - - open: $i_S = 0$



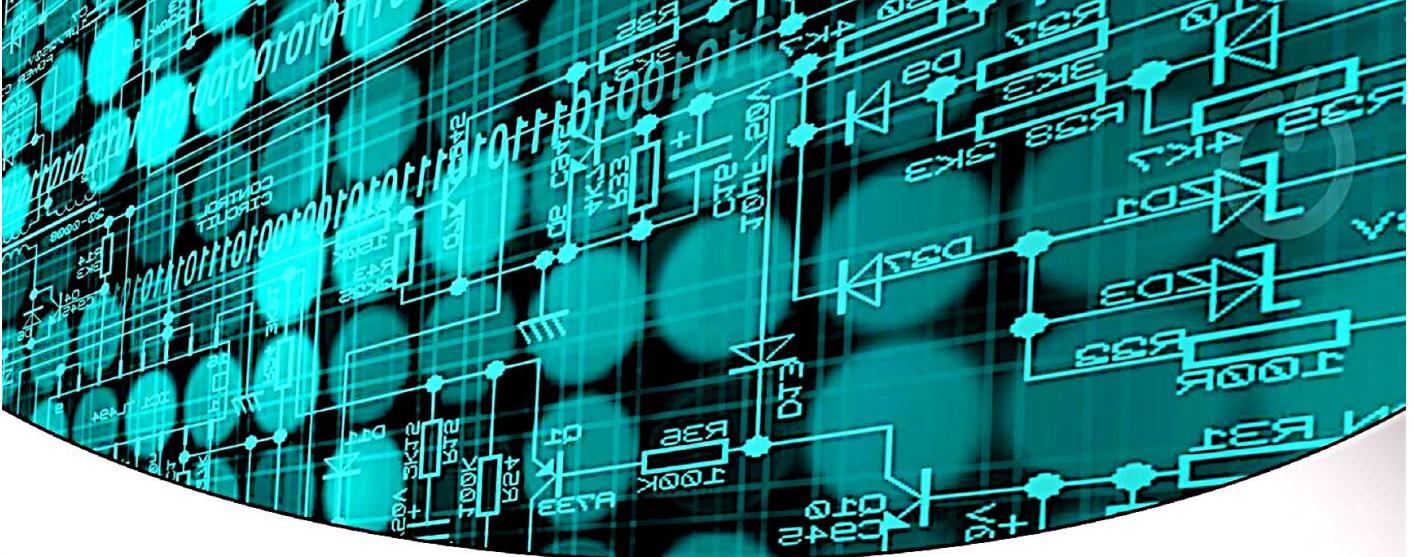


Power Electronics

Fall017

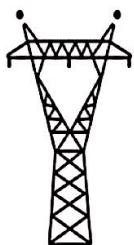

Dr. Sereen Althaher

By: Mhmd Abuhashya

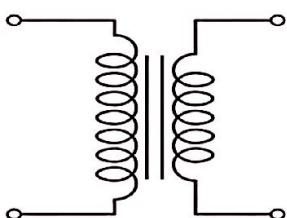

Powerunit-ju.com

$$(i_s)_{avg} = \frac{1}{T} [DT I_{Lmin} + \frac{1}{2} DT (I_{Lmax} - I_{Lmin})] = \frac{D}{2} [I_{Lmax} + I_{Lmin}] \quad \text{I}_{Lavg}$$



$$\text{so } (i_s)_{avg} = D * I_{Lavg} = (0.06) * (70) = \underline{\underline{4.2A}}$$

Example: We wish to charge a **120V** battery from **600V** DC source using a DC chopper. The avg. battery current should be **20A** with peak to peak ripple current **2A** if the chopper freq is **200 Hz**. $\Delta i = 2A$.

- Find:**
- 1) DC current drawn from the source.
 - 2) DC current in the diode.
 - 3) Duty cycle + t_{on}
 - 4) Inductance.

Solution: ① @ Avg. $P_{in} = P_{out} \rightarrow V_{in} (I_{in})_{avg} = V_0 I_{avg}$
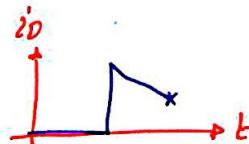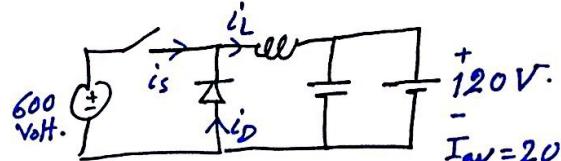
$$I_{in\ avg} = \frac{120 * 20}{600} \Rightarrow \boxed{I_{in\ avg} = 4A}$$



$$\textcircled{2} \quad i_s + i_d = i_L \Rightarrow i_d = i_L - i_s \quad ; \quad i_{avg}^L = i_{load\ avg} \quad \text{so} \quad i_{avg}^d = 20 - 4 \Rightarrow \boxed{i_{avg}^d = 16A}$$

$$\textcircled{3} \quad (I_D)_{avg} = \frac{1}{T} [(1-D)T I_{Lmin} + \frac{1}{2} (1-D) (I_{Lmax} - I_{Lmin})] = \boxed{(1-D) I_{Lavg} = I_{Davg}}$$

$$\text{so } 16 = (1-D) * 20 \Rightarrow \boxed{D = 0.2} \quad \text{OR By using } (I_s)_{avg} = D I_{Lavg}$$


$$\frac{t_{on}}{T} = D \Rightarrow \boxed{t_{on} = 1 \text{ msec.}} \quad \Rightarrow \boxed{D = 0.2}$$

$$\textcircled{4} \quad \begin{array}{c} \text{Graph of } i_L \text{ vs } t \\ \text{At } t=0, i_L = 20A \\ \text{At } t=t_{on}, i_L = 4A \\ \text{At } t=T, i_L = 20A \end{array} \quad \Delta i_L = \frac{V_0 (1-D) T}{L} \quad \text{so} \quad \boxed{L = 0.24H}$$


* first end of material

DC-DC: Buck $\left. \begin{matrix} \text{Boost} \\ \text{Buck-Boost} \end{matrix} \right\}$ same polarity of voltage. $\left. \begin{matrix} \text{powerflow in unidirection.} \\ \text{source} \rightarrow \text{load.} \end{matrix} \right\}$


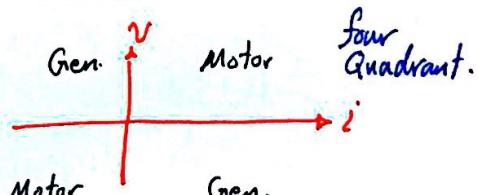
Application: wind turbine $\rightarrow \left. \begin{matrix} \text{change polarity} \\ \text{powerflow} \end{matrix} \right\}$



* 2-Quadrant Converter:


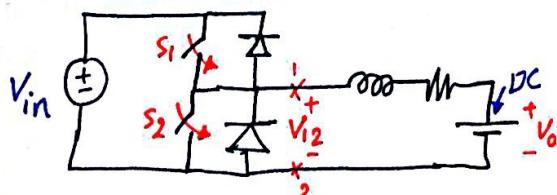


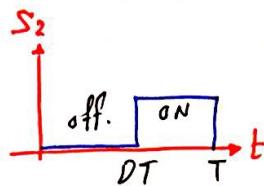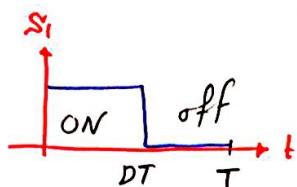* $S_1 \& S_2$ Can't be closed at the same time. But can be opened together for a short time, this called Dead Zone $\Rightarrow S_1 \& S_2$ off.



@ Av. inductor $V_L = 0$

Case(1):

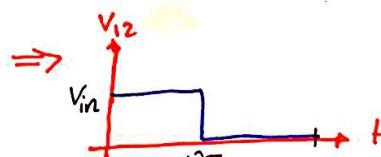
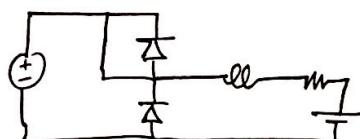


$$(V_{12})_{av} = \frac{1}{T} [DT V_{in}]$$

$$V_{12} = DV_{in}$$

$$\Rightarrow i_L = \frac{V_{12} - V_o}{R} \Rightarrow i_L = \frac{DV_{in} - V_o}{R}$$

Case(2):

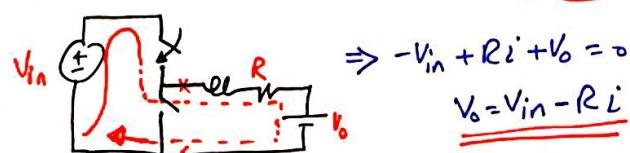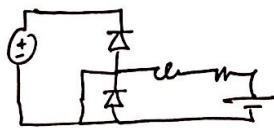


*when S_2 closed & S_1 opened \Rightarrow it will make V_o feed the cct & reverse the direction of power flow.

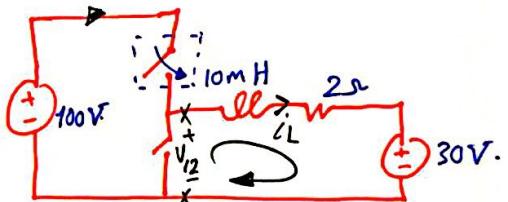Example: For the shown figure:

$$D_{S_1} = 0.2, f = 20\text{KHZ}.$$

- ① Find the value & the direction of DC current i_L ?
- ② find Δi_L ?
- ③ if D increased to 0.45 repeat ① & ②?




Solution:

$$\textcircled{1} \quad S_1 \text{ closed } \Rightarrow V_{12} = DV_{in} \Rightarrow 2i_L + 30 - (0.2)(100) = 0 \Rightarrow i_L = -5\text{A}$$


$$\textcircled{2} \quad L \frac{di_L}{dt} = V_L \Rightarrow \frac{\Delta i_L}{\Delta t} = \frac{\Delta V_L}{L}, \text{ when } S_2 \text{ closed: } \begin{array}{c} \Delta V_L \\ \text{---} \\ 2\Omega \\ \text{---} \\ 30\text{V} \end{array} \Rightarrow \Delta V_L = 30 - 2 * 5 = 20\text{volt}. \quad \Delta t = (1-D)T$$

$$\textcircled{3} \quad V_{12} = 0.45 * 100 = 45\text{volt}. \quad \Rightarrow i_L = \frac{45-30}{2} = 7.5\text{A} \quad (\text{so changing } D \text{ cause to reverse the direction of } i_L).$$

4-Quadrant Converter:

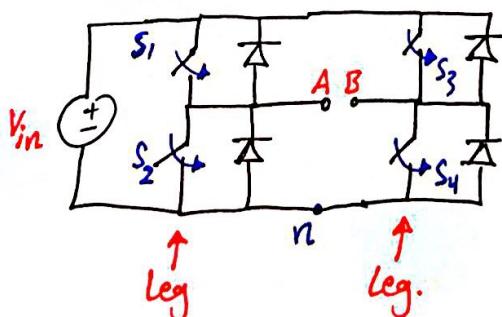

S_1, S_4 ON, OR S_2, S_3 ON

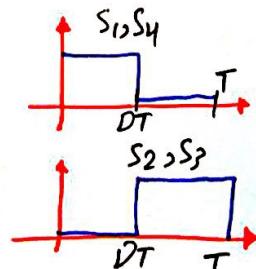

ALL S_1, S_2, S_3, S_4 off
"Dead Zone".


Case(1): S_1, S_4 closed.

$$V_{An} = V_{in}$$

$$V_{Bn} = \text{Zero}$$

$$\Rightarrow V_{An} - V_{Bn} = V_{AB}$$


\Rightarrow

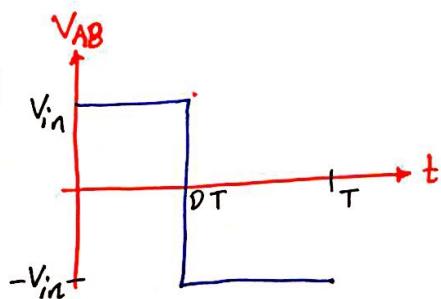

Case(2): S_2, S_3 closed.

$$V_{An} = 0$$

$$V_{Bn} = V_{in}$$

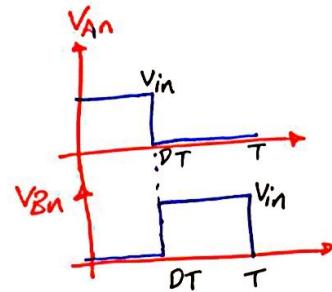


$$[V_{AB}]_{av} = \frac{1}{T} [DT V_{in} - V_{in} T(1-D)] = DV_{in} - V_{in} + V_{in}D \Rightarrow V_{AB} = V_{in} [2D-1]$$

$$2D-1=0 \Rightarrow D=\frac{1}{2}$$

$$2D-1=1 \Rightarrow D=1$$


\ominus \oplus
0.5

* 2-quadrant DC/DC:

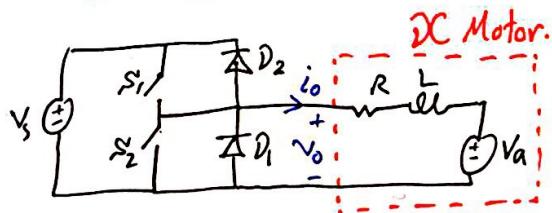


$S_1, D_1 \Rightarrow$ chopper 1.

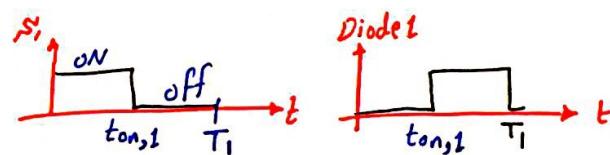$S_2, D_2 \Rightarrow$ chopper 2 (turned off).




* when S_2, D_2 ON:

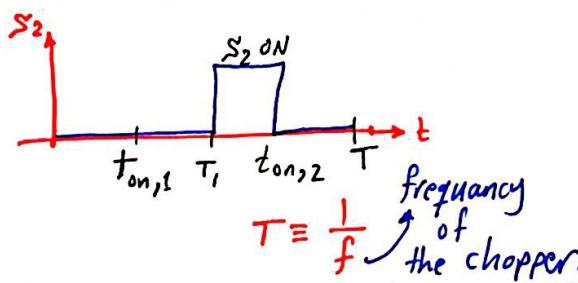






* Cases:

- S_1, D_1 (turned on).

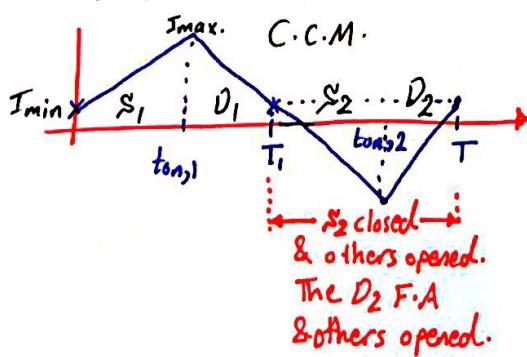

case(1): S_1, D_1 are ON.

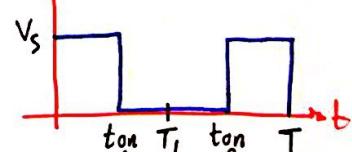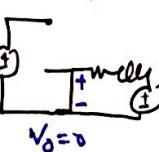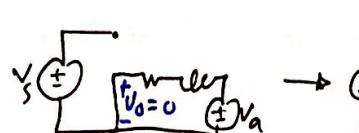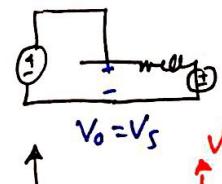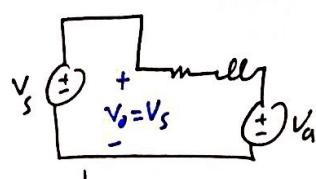$I_{max} > 0 \rightarrow (I_o)_{avg} > 0$ so $P > 0$ (source \rightarrow load) Q1



Case(2): $I_{min} < 0 \Rightarrow I_o > 0 \Rightarrow Q_1$
 $I_{max} > 0 \Rightarrow I_o < 0 \Rightarrow Q_2$

case(3):

S_1, D_1 turned off:

$$t_{on,1} = 0, T_1 = 0 \quad I_{min} < 0 \Rightarrow I_o < 0 \Rightarrow Q_2$$

S_2, D_2 are ON. $I_{max} < 0$





case(4):

S_1, D_1 turned off:

$$t_{on,1} = 0, T_1 = 0 \quad I_{min} < 0 \Rightarrow I_o < 0 \Rightarrow Q_2$$

Note that:
Before we deal in case $L \gg 1$
(gives i_o Linear Relation).

* Take D_1 (ON).

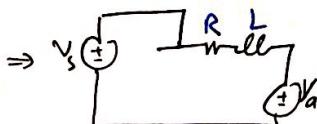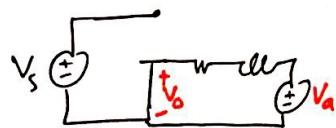

$$v_o = R i_o + L \frac{di_o}{dt} + V_a \quad \text{differential equation.}$$


↓ if we solve for i_o :

$$i_o(t) = \frac{v_o - V_a}{R} \left(1 - e^{-\frac{t}{T}} \right) + I_{min} e^{-\frac{t}{T}}$$

$$\Rightarrow \text{for } 0 < t \leq t_{on,1} \text{ where: } T = L/R$$

* Take D_1 (ON).
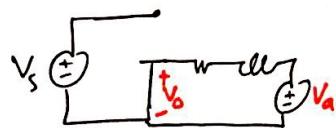
$$v_o = \text{Zero} = R i_o + L \frac{di_o}{dt} + V_a \Rightarrow \text{for } t_{on,1} < t < T_1$$




$$i_o(t) = -\frac{V_a}{R} \left(1 - e^{-\frac{t}{T}} \right) + I_{max} e^{-\frac{t}{T}} \dots \{2\}$$

* From {1} & {2} you can obtain I_{min} & I_{max} :

$$I_{max} = \frac{V_s}{R} \left(\frac{1 - e^{-\frac{T_1}{T}}}{1 - e^{\frac{T_1}{T}}} \right) - \frac{V_a}{R}$$


$$I_{min} = \frac{V_s}{R} \left(\frac{e^{\frac{T_1}{T}} - 1}{e^{\frac{T_1}{T}} - 1} \right) - \frac{V_a}{R}$$
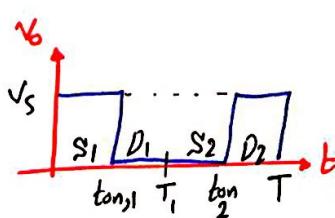
$$\text{Ripple} = \Delta I = I_{max} - I_{min}$$



$$(I_o)_{avg} = \frac{(V_o)_{avg} - V_a}{R}$$

* for easier calculations:
Duty Cycle:

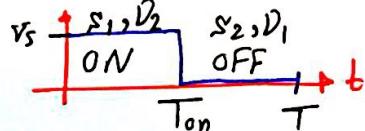

$$D = \frac{t_{on}}{T} \equiv \text{Duty Cycle.}$$

$$\text{so Now find } (V_o)_{avg}: \bar{V}_o = \frac{1}{T} \int_0^{T_1} v_s dt$$


$$\Rightarrow \bar{V}_o = V_s \frac{T_{on}}{T} \Rightarrow (V_o)_{avg} = DV_s \dots \{4\}$$

substitute {4} in {3}:

$$(I_o)_{avg} = \frac{DV_s - V_a}{R}$$

$$\text{RMS for } V_o: V_{o,\text{rms}} = \sqrt{\frac{1}{T_1} \int_0^{T_1} V_s^2 dt} = \sqrt{\frac{T_1}{T} V_s^2}$$
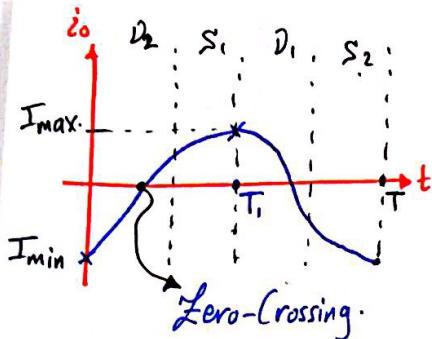
$$\Rightarrow V_{o,\text{rms}} = \sqrt{D} V_s$$



* When we do Control: we avoid this zero-crossing to occur, because S/C happen @ the Machine.

29

$$I_o = \frac{DV_s - V_a}{R} \neq 0$$

Example: 2Q-DC/DC converter Feeds an inductive load with $R=10\Omega$, $L=50mH$. & back emf $= 100V DC$ from a source of $340V DC$. if the chopper is operate at $200Hz$. with 25% on-state duty cycle. Find:

1) $(V_o)_{avg}$, $(V_o)_{rms}$. 2) $(I_o)_{max, min}$, ΔI_o = Ripple. 3) $(I_o)_{avg}$. 4) $i_o(t)$.

5) Zero-crossing point of $i_o(t)$. 6) Plot V_o , i_o , I_s .

7) Find the value of D if $(I_o)_{avg}=0$.

8) Find the value of V_a if $D=0.25$, $I_o=0$

Solution: $D=0.25$

① $V_o_{avg} = DV_s \Rightarrow V_o_{avg} = 85V$

$V_o_{rms} = \sqrt{D} V_s \Rightarrow V_o_{rms} = 170V$

④ $i_o = 24 - 28.3 e^{-t/5m}$; $0 \leq t \leq 1.25m$
 $i_o = -10 + 11.9 e^{-t/5m}$, $t < T - T_1$
 $\Rightarrow t \leq 3.75m$

⑤ $i_o = 0 \Rightarrow 24 = 28.3 e^{-t/5m}$
 $10 = 11.9 e^{-t/5m} \Rightarrow t = 0.83msec.$
 $t = 0.87msec.$

② $I_{max} = \frac{V_s}{R} \left(\frac{1 - e^{-T/T_1}}{1 - e^{-T/T}} \right) - \frac{V_a}{R}$

$\Rightarrow I_{min} = 4.38A$
 $I_{max} = 1.9A$.

$D = \frac{T_{on}}{T} = 0.25$
 $T_1 = 1.25msec.$

$T = \frac{1}{200} = 5msec$


$T = L/R$

③ $\bar{I}_o = \frac{V_o - V_a}{R} = \frac{85 - 100}{10} = -1.5A$ $\therefore Q_{II}$
 $\Delta I_o = I_{max} - I_{min} = 1.9 - (-4.38) = 6.28A$

* Four Quadrant DC/DC Converter:

• Application: DC Motor.

• Configuration:


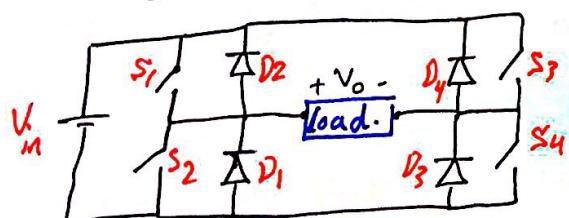


All of them work of freq.
of the chopper, $f = \frac{1}{T}$.


Case (1): T_1, T_4 (ON), D_1, D_4 (OFF) Then D_1, D_4 (ON)
 T_1, T_4 (off).

Case (2): T_2, T_3 (ON) Then D_2, D_3 (ON).


* for case (1): S_1, S_4 S.C.

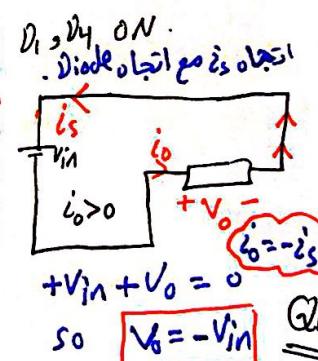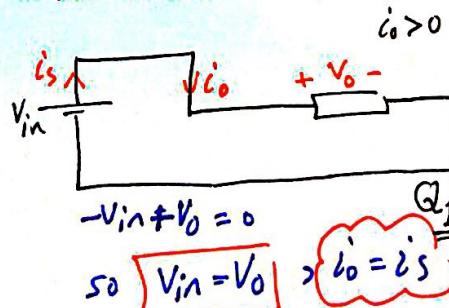

* for Case (2):

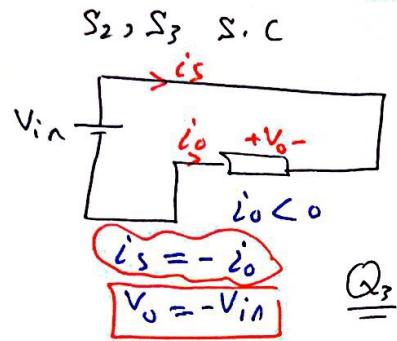

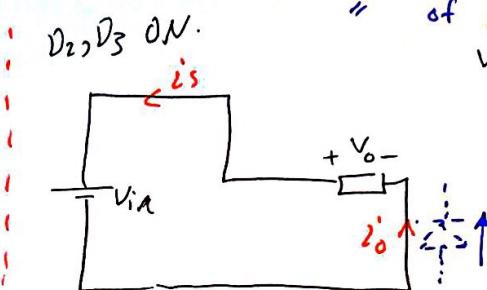* Always by convention direction of i_o " of i_s







30

$$i_o < 0$$

$$-i_o = -i_s$$

$$\Rightarrow i_o = i_s$$

$$V_{in} = V_o$$

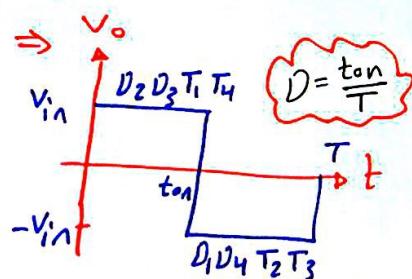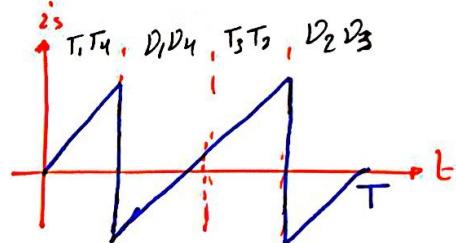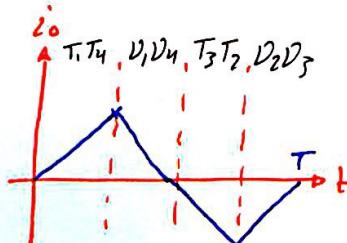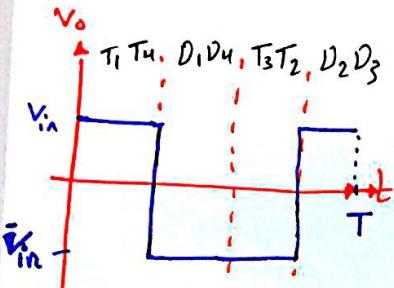

$$\Rightarrow V_o_{\text{av.}} = \frac{1}{T} \left[\int_0^{t_{on}} V_{in} dt + \int_{t_{on}}^T -V_{in} dt \right] = \frac{V_{in}}{T} [t_{on} - [T - t_{on}]]$$

$$\Rightarrow V_o_{\text{av.}} = \frac{V_{in}}{T} [2t_{on} - T] \Rightarrow \overline{V_o} = V_{in} [2D - 1]$$

$$\overline{I_o} = \frac{\overline{V_o} - V_a}{R}$$

• when $D=0$ (T_1, T_4 off)

$$\underline{V_o = -V_{in}}$$

• $D=1$ (T_1, T_4 ON)


$$\underline{V_o = V_{in}}$$

• Worst Case: $V_o = 0$

$$\begin{cases} 2D-1=0 \\ D=0.5 \end{cases}$$

$D > 0.5 \rightarrow V_o > 0$

$D < 0.5 \rightarrow V_o < 0$

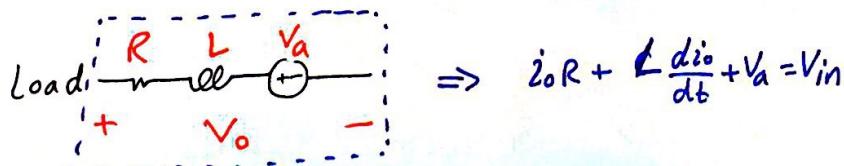

$$\Rightarrow i_o R + \frac{d i_o}{dt} + V_a = V_{in}$$

* You Can Observe the following Relations:

$$\textcircled{1} \cdot i_o(t) = \frac{V_s - V_a}{R} (1 - e^{-t/\tau}) + I_{\min} e^{-t/\tau}, \quad 0 \leq t \leq t_{on} \quad (D \geq 0.5).$$

$$\textcircled{2} \cdot i_o(t) = -\frac{(V_s + V_a)}{R} (1 - e^{-t/\tau}) + I_{\max} e^{-t/\tau}, \quad 0 \leq t \leq T - t_{on} \quad (D \leq 0.5)$$

$$\textcircled{3} \cdot \begin{cases} 0 \leq t \leq t_{on}, D \leq 0.5 \\ 0 \leq t \leq T - t_{on}, D \geq 0.5 \end{cases} \quad \begin{cases} i_o = -\frac{V_a}{R} (1 - e^{-t/\tau}) + I_{\max} e^{-t/\tau} \\ I_{\max} = \frac{V_s}{R} \left(\frac{1 - e^{-t_{on}/\tau}}{1 - e^{-T/\tau}} \right) - \frac{V_a}{R} \\ I_{\min} = \frac{V_s}{R} \left(\frac{e^{-t_{on}/\tau} - 1}{e^{-T/\tau} - 1} \right) - \frac{V_a}{R} \end{cases}$$

$$\tau = \frac{L}{R}$$

Example: 4-quadrant DC chopper feeds an inductive load. $R=10\Omega$, $L=50mH$, $D=0.25$, backemf = 55V, $V_s=340V$, $f_c=200Hz$. Find:
 (i) \bar{V}_o ? (ii) \bar{I}_o , Determine quadrant of operation? (iii) if \bar{I}_o is halved, find: a) Duty Cycle.? b) \bar{V}_o ?

31

Solution:

$$(i) \bar{V}_o = V_s(2D-1) \Rightarrow \bar{V}_o = -170V$$

$$(ii) \bar{I}_o = \frac{\bar{V}_o - V_a}{R} \Rightarrow \bar{I}_o = -22.5A$$


since \bar{I}_o & \bar{V}_o are both -ve
 $\Rightarrow Q_3$ "Motor".

$$(iii) \bar{I}_o = \frac{-22.5}{2} = \frac{V_o - 55}{10} \Rightarrow \bar{V}_o = -57.5V ; \bar{V}_o = (2D-1)V_s \Rightarrow D = 0.415$$


if we asked to find $i_o(t)$ \Rightarrow Apply the relation with $D \leq 0.5$.

* Single Phase Inverter:

• Configuration:

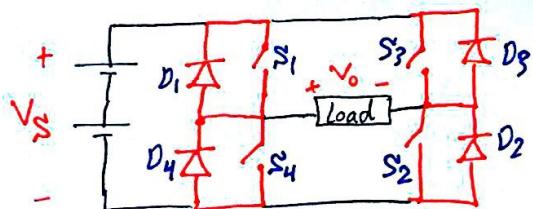

* Load : (inductive load)

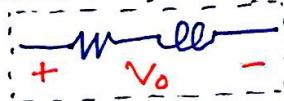

* Now any that both diode on the same leg work together (D_1 will be ON with D_2 , and D_3 ON with D_4).


* here we will work on $D=0.5$ which will give a zero DC value.

$$* \text{Fourier transform: } V_o(t) = \frac{4}{\pi} V_s \sum_{n=\text{odd}} \frac{1}{n} \sin(n\omega t), \quad \omega_0 = \frac{2\pi}{T} = 2\pi f_c$$

$$\Rightarrow \text{RMS value: } V_{o1} = \frac{V_{o1}}{\sqrt{2}} = \frac{4}{\pi} \frac{V_s}{\sqrt{2}} \Rightarrow V_{o1} = 0.9 V_s$$

$(n=1)$
fundamental freq.

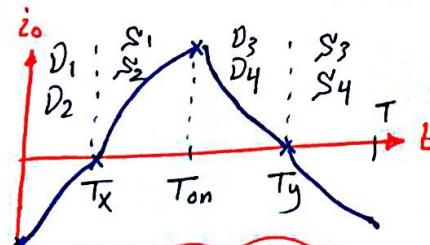- D_1, D_2 ($i_o < 0$)
- S_1, S_2 ($i_o > 0$)



$T_x, T_y \equiv$ time when zero crossing occurs.

To find them put $i_o(t) = 0$

$$\begin{aligned} \cdot t \leq \frac{T}{2} : \quad i_o(t) &= \frac{V_s}{R} - \left(\frac{V_s}{R} - I_{\min} \right) e^{-\frac{t-T_x}{T}} \\ \cdot t \geq \frac{T}{2} : \quad i_o(t) &= -\frac{V_s}{R} + \left(\frac{V_s}{R} + I_{\max} \right) e^{-\frac{(t-T_y)}{T}} \end{aligned}$$

$$* \text{Fourier transform: } i_o(t) = \frac{4}{\pi} \sum_{n=\text{odd}} \frac{V_s}{n Z_n} \sin(n\omega_0 t - \phi_n)$$

@ $n=1$:

$$i_{o1} = \frac{4}{\pi} \frac{V_s}{Z_1 \sqrt{2}} \Rightarrow i_{o1} = \frac{0.9 V_s}{Z_1}$$

$$P_i = V_{rms} I_{rms}$$

$$Z_n = \sqrt{R^2 + (n\omega L)^2}$$

$$\phi_n = \tan^{-1} \left(\frac{n\omega L}{R} \right)$$

Example: A single-phase inverter supplies $10\Omega + 50mH$ from 340V DC

$f = 50\text{Hz}$. Find:

- (i) $i_o(t)$? (ii) $V_{o,\text{rms}}$? (iii) Zero-crossing points on i_o ?

Solution:

$$I_{\max} = -I_{\min} = \frac{V_s}{R} \left(\frac{1 - e^{-\frac{T}{2}}}{1 + e^{-\frac{T}{2}}} \right) \Rightarrow \text{for single phase converter.}$$

(i) $C = \frac{L}{R} \Rightarrow T = \frac{1}{f} \Rightarrow I_{\max} = 25.9\text{A} \Rightarrow I_{\min} = -25.9\text{A}$.

Substitute these values in both relations of $i_o(t)$ $t \leq \frac{T}{2}$ & $t \geq \frac{T}{2}$: $\frac{-(t-10m)}{5m}$

for $t \leq \frac{T}{2}$: $i_o(t) = 34 - 59.9 e^{\frac{-t}{5m}} \text{A}$. for $t \geq \frac{T}{2}$: $i_o(t) = 34 + 59.9 e^{\frac{-(t-10m)}{5m}} \text{A}$

(ii) $V_{o,\text{rms}} = 0.9 V_s \Rightarrow V_{o,\text{rms}} = 306 \text{ volt.}$

(iii) find T_x & T_y :

$$0 = 34 - 59.9 e^{\frac{-T_x}{5m}}$$

solving: $T_x = 2.83 \text{ msec}$

$$0 = 34 + 59.9 e^{\frac{-(T_y-10m)}{5m}}$$

$$T_y = 12.83 \text{ msec}$$

Example: A single phase inverter supplies a load with $R=10\Omega$, $L=50mH$ & fed from 340V DC source. if the bridge is operating @ 50Hz. "Half Bridge Inverter"

Find: a) V_o ? b) $V_{o,\text{rms}}$? c) $I_{o,\text{max}}$? d) $i(t)$?

Solution:

• in case Copper, S_2 (ON):

$$i_o < 0 \Rightarrow -V_o - \frac{V_s}{2} = 0 \Rightarrow V_o = -\frac{V_s}{2}$$

• in case Copper, D_3 (ON):


$$i_o > 0 \Rightarrow +\frac{V_s}{2} + V_o = 0 \Rightarrow V_o = \frac{V_s}{2}$$

• in case Lower, S_2 (ON):

$$i_o > 0 \Rightarrow +V_o - \frac{V_s}{2} = 0 \Rightarrow V_o = \frac{V_s}{2}$$

• in case Lower, D_2 (ON):


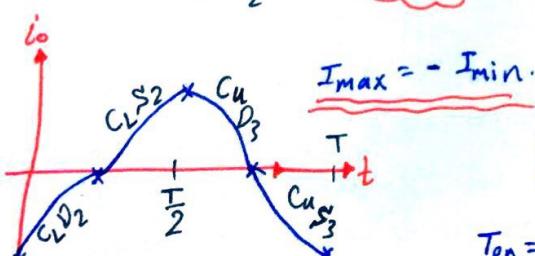
$$i_o < 0 \Rightarrow -V_o + \frac{V_s}{2} = 0 \Rightarrow V_o = \frac{V_s}{2}$$



$$T_{on} = \frac{T}{2} = 10 \text{ msec.}$$

$$C = \frac{L}{R} = 5 \text{ msec.}$$
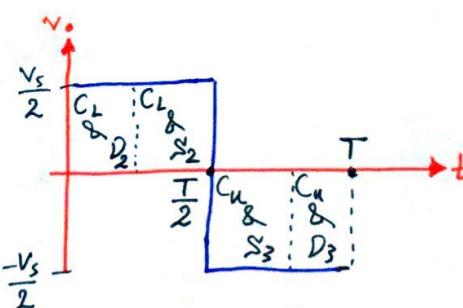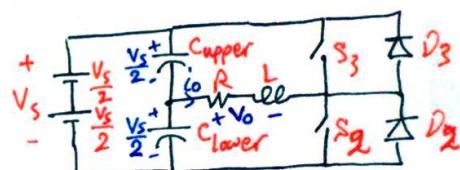
$$i(t) = \frac{V_s/2}{R} - \left(\frac{V_s/2}{R} - I_{\min} \right) e^{-t/C} ; 0 < t \leq 10 \text{ msec.}$$



$$V_{o,\text{rms}} = \sqrt{\frac{1}{T} \int_0^{T/2} \left(\frac{V_s}{2}\right)^2 dt + \int_{T/2}^T \left(\frac{V_s}{2}\right)^2 dt} \Rightarrow V_{o,\text{rms}} = \frac{V_s}{2}$$

$$\Rightarrow V_{o,\text{rms}} = 170 \text{ volt.}$$

$$I_{o,\text{max}} = \frac{V_s/2}{R} \left(\frac{1 - e^{-\frac{T_{on}}{C}}}{1 + e^{-\frac{T_{on}}{C}}} \right)$$



$$\Rightarrow I_{o,\text{max}} = 12.95 \text{ A}$$

$$I_{o,\text{min}} = -12.95 \text{ A.}$$

$I_{o,\text{max}}$ & $I_{o,\text{min}}$
same previous relation
just replace V_s by $V_s/2$.

* Pulse Width Modulation:

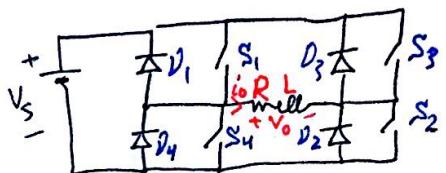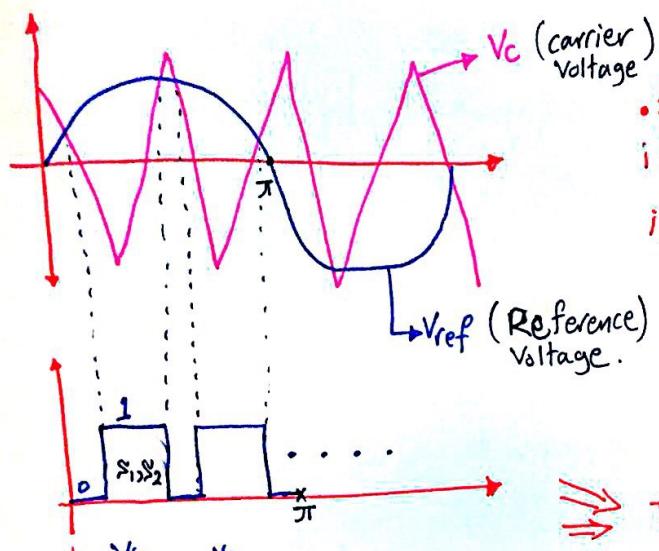inverter (DC \rightarrow AC) \Rightarrow sinusoidal.






[33]

- first assumption:
if $V_{ref} > V_c \Rightarrow 1$
- if $V_{ref} < V_c \Rightarrow 0$


- second assumption:
 $S_1, S_2 \text{ ON } (0 \rightarrow \pi)$
 $S_3, S_4 \text{ ON } (\pi \rightarrow 2\pi)$

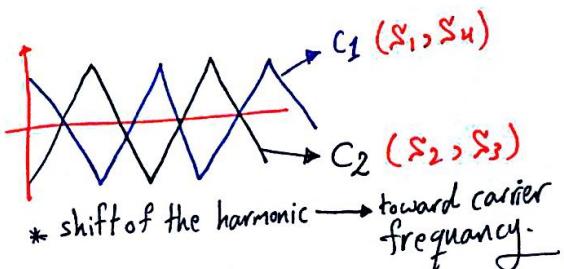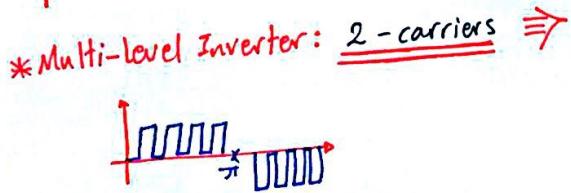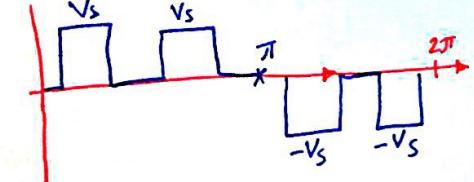\Rightarrow This is called: "Bipolar Inverter".




* shift of the harmonic \rightarrow toward carrier frequency.

* 3-phase Inverter (DC/AC):


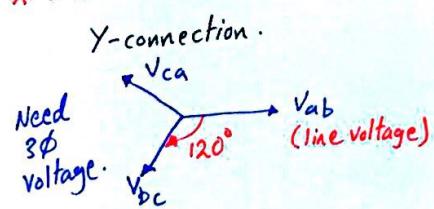


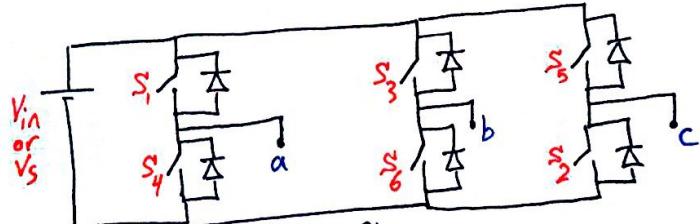\Rightarrow Configuration: will be with 3 legs {6 switches}.



* Control switches:

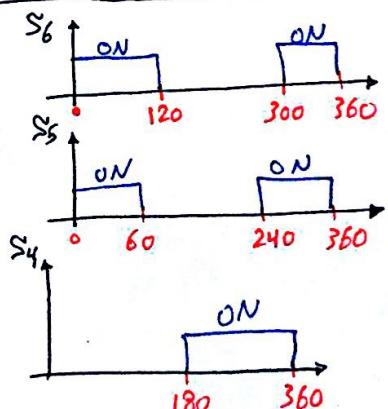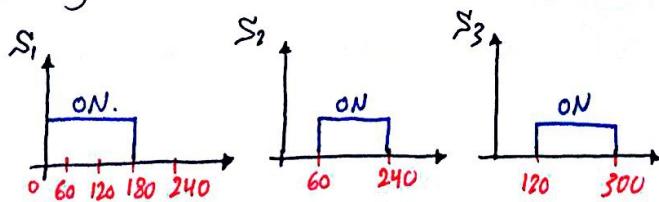- each leg has one switch ON @ each time segment.
- Time Domain \Rightarrow 6 time segments (60°).
- Each switch will operate for 3 time segments (180°).
- Sequentially each switch will be delayed by (60°).




*for 3φ inverter: (6-cases)

34

- ① $0 \rightarrow 60^\circ$ (s_1, s_5, s_6)
- ② $60^\circ \rightarrow 120^\circ$ (s_1, s_2, s_6)
- ③ $120^\circ \rightarrow 180^\circ$ (s_1, s_2, s_3)
- ④ $180^\circ \rightarrow 240^\circ$ (s_2, s_3, s_4)
- ⑤ $240^\circ \rightarrow 300^\circ$ (s_3, s_4, s_5)
- ⑥ $300^\circ \rightarrow 360^\circ$ (s_4, s_5, s_6)

Case ①: find V_{ab}, V_{bc}, V_{ca} (it will be like a load connected between the needed phases).

for V_{ab} :

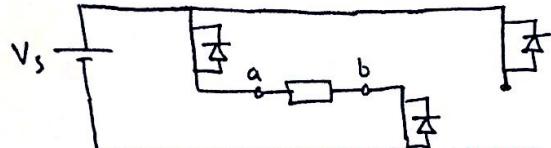

$$-V_s + V_{ab} = 0 \Rightarrow V_{ab} = V_s$$

the same will be done for V_{bc} & V_{ca} :
you will find that:

$$V_{bc} = -V_s$$

$$V_{ca} = 0$$

Note: $V_{ab} + V_{bc} + V_{ca} = 0$ for all 6-cases.

** Do the same for the other 5-cases, the results will be as follows:


case ②: $V_{ab} = V_s, V_{bc} = 0, V_{ca} = -V_s$

case ③: $V_{ab} = 0, V_{bc} = V_s, V_{ca} = -V_s$

case ④: $V_{ab} = -V_s, V_{bc} = V_s, V_{ca} = 0$

case ⑤: $V_{ab} = -V_s, V_{bc} = 0, V_{ca} = V_s$

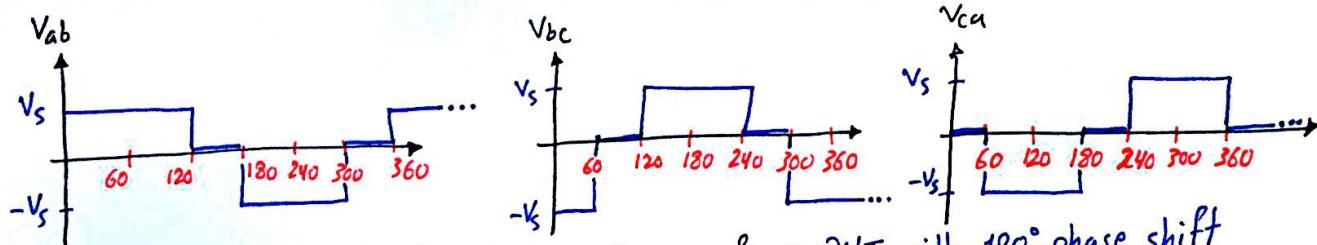
case ⑥: $V_{ab} = 0, V_{bc} = -V_s, V_{ca} = V_s$



Note: All of V_{ab}, V_{bc}, V_{ca} have the same figure BUT with 120° phase shift between each one of them with the other one.


*Phase to Neutral Voltages:

case ①:

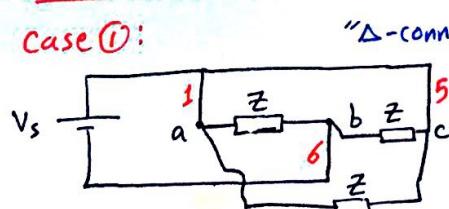

"Δ-connection"

we convert
to Y-connection

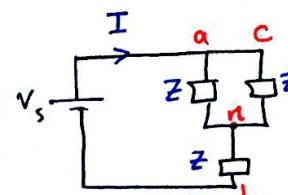


$$I = \frac{V_s}{\frac{3}{2}Z}$$

$$V_{an} = V_{cn} = \frac{V_s}{\frac{3}{2}Z} \cdot \frac{Z}{2}$$


$$\Rightarrow V_{an} = V_{cn} = \frac{V_s}{3}$$

$$V_{bn} = -\frac{2V_s}{3}$$

case ②:

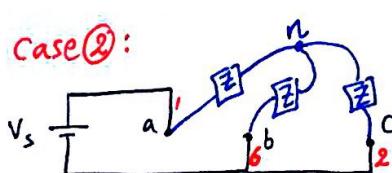

\Rightarrow

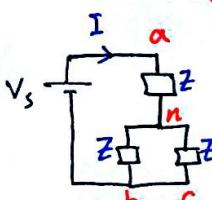

$$I = \frac{V_s}{\frac{3}{2}Z}$$

$$V_{an} = \frac{2}{3}V_s$$

$$V_{bn} = V_{cn} = -\frac{V_s}{3}$$

** Do the same for the other 4-cases.

* Fourier transform for the Line & phase voltages:

V_{ab} : will have No DC value. ($DC=0$) , it will NOT have third harmonic (which is an advantage).

, it will have odd freq. $1, 5, \dots$ → any factor of 3^n doesn't exist. ($3, 9, 27, \dots$)

V_{an} : will have odd freq. $1, 3, 5, \dots$

The expressions are given as follows:

$$V_{an} = \frac{2V_s}{\pi} \left[\sin(\omega t) + \frac{1}{3} \sin(3\omega t) + \frac{1}{5} \sin(5\omega t) + \dots \right]$$

$$V_{bn} = \frac{2V_s}{\pi} \left[\sin(\omega t - 120^\circ) + \frac{1}{3} \sin(3\omega t - 120^\circ) + \dots \right]$$


$$V_{cn} = \frac{2V_s}{\pi} \left[\sin(\omega t + 120^\circ) + \frac{1}{3} \sin(3\omega t + 120^\circ) + \dots \right]$$

$$V_{ab} = \sqrt{3} \frac{2V_s}{\pi} \left[\sin(\omega t + 30^\circ) - \frac{1}{5} \sin(5\omega t + 30^\circ) + \dots \right]$$

$$V_{bc} = \sqrt{3} \frac{2V_s}{\pi} \left[\sin(\omega t - 90^\circ) - \frac{1}{5} \sin(5\omega t - 90^\circ) + \dots \right]$$

$$V_{ca} = \sqrt{3} \frac{2V_s}{\pi} \left[\sin(\omega t + 150^\circ) - \frac{1}{5} \sin(5\omega t + 150^\circ) + \dots \right]$$

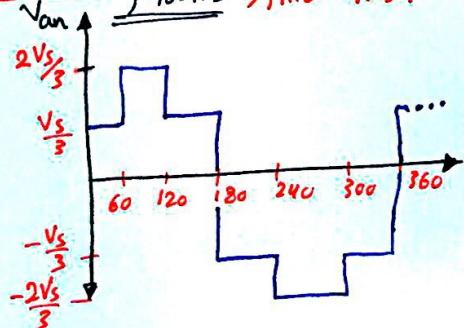Example: $f=100\text{Hz}$. , find V_{rms} ?




$$\Rightarrow T = 0.01 \text{ sec.} \Rightarrow \frac{I}{6} = \frac{0.01}{6} \text{ sec.}$$

$$V_{rms}^2 = \frac{2}{0.01} \left[\int_0^{0.01} \left(\frac{Vs}{3}\right)^2 dt + \int_{0.01}^{0.02} \left(\frac{2Vs}{3}\right)^2 dt + \int_{0.02}^{0.03} \left(\frac{Vs}{3}\right)^2 dt \right]$$

$$\text{Solving: } V_{rms} = 0.47Vs$$






Example: 3ϕ inverter is used to supply a 3ϕ load using a DC voltage source if the desired freq at the load side 500Hz .

Find the conduction period for each switch?

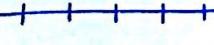Solution: 

$$\Rightarrow \text{conduction period} = 3 * \frac{1}{6} = \frac{1}{2} \text{ msec.} \Rightarrow \text{conduction} = 3 * \frac{1}{2} = 1 \text{ msec.}$$

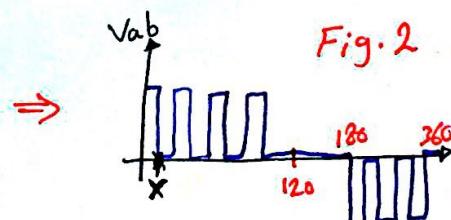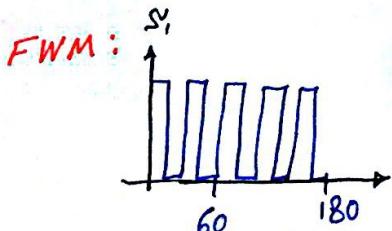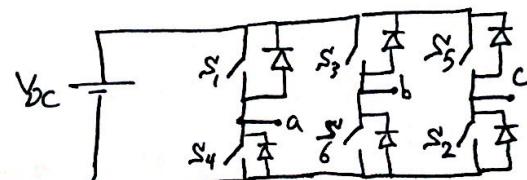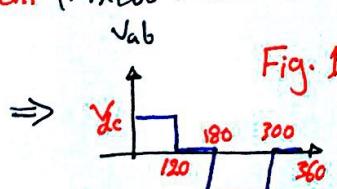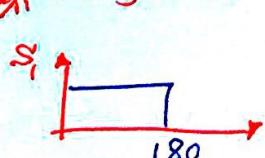* Voltage adjustment (Fixed Width Modulation [FWM]):



• objective: Reduction for V_{ab} .

→ continue.

for Fig 1: $V_{ab\text{rms}} \Big|_{\text{without FWM}} = \sqrt{\frac{1}{T} \int_0^{T/2} V_{dc}^2 dt + \int_{T/2}^{T+300/360} V_{dc}^2 dt} = \sqrt{\frac{2}{T} \int_0^{T/2} V_{dc}^2 dt}$

 $= V_{dc} \sqrt{\frac{2}{T} \left(\frac{2T}{3}\right)}$

• without FWM: $V_{ab\text{rms}} = \sqrt{\frac{2}{3}} V_{dc}$... ①

for Fig 2: $d \triangleq \text{Duty Cycle.} = \frac{\sum \text{on time}}{\frac{120}{360} T} \rightarrow \text{conduction period.}$

$V_{ab\text{rms}} = \sqrt{\frac{2N}{T} \int_0^X V_{dc}^2 dt} ; \text{ where } N = \# \text{ of conduction time.}$

$= \sqrt{\frac{2 \cdot N(dT)}{T} * V_{dc}} = V_{dc} \sqrt{\frac{2}{3} d}$

• with FWM:

$V_{ab\text{rms}} = \sqrt{\frac{2}{3}} V_{dc} \sqrt{d} = V_{ab\text{rms}} \Big|_{\text{without FWM}}$... ②

Divide ② by ① gives:

* Voltage reduction $\equiv \sqrt{d}$ *

$X = \frac{dT}{3N}$

$d = \frac{N}{\text{conduction period}}$
 $\Rightarrow d = \frac{N}{2I/6}$

$d = \frac{XN}{2I/6}$

* Summarize:

$\therefore V_{ab}$

without FWM: $V_{ab} = \sqrt{\frac{2}{3}} V_{dc}$

with FWM: $V_{ab} = \sqrt{\frac{2}{3}} V_{dc} / \sqrt{d}$

Example: FWM 3φ inverter with duty ratio equals 25% is used to reduce the voltage if $V_s = V_{dc} = 150$ volt. Calculate RMS with & without FWM?


Solution: $V_{ab\text{rms}} \Big|_{\text{without}} = \sqrt{\frac{2}{3}} V_{dc} = 122.48 \text{ volt.}$

$V_{ab\text{rms}} \Big|_{\text{with}} = \sqrt{\frac{2}{3}} V_{dc} / \sqrt{d} = 61.24 \text{ volt.}$

* Sequence Adjustment Using 3φ inverter acb:

A swap for s_1 with s_5 .
& s_2 with s_4


Do the same thing to find the voltages.

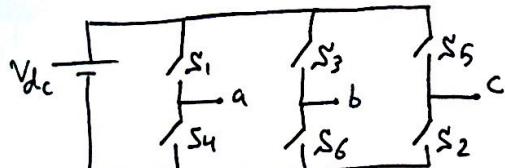

* Sinusoidal Pulse Width Modulation [SPWM]: * 3φ *

To control f, Mag., phase \Rightarrow To reduce the harmonics.

for leg (1):

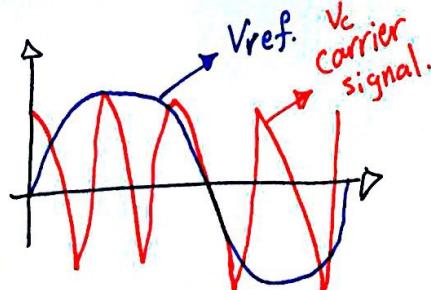


if $V_{ref} > V_c \Rightarrow \text{ON} \Rightarrow \text{upper switch.}$
if $V_{ref} < V_c \Rightarrow \text{ON} \Rightarrow \text{lower switch.}$




Power Electronics

Fall017

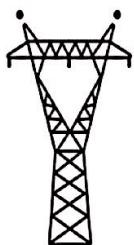

Dr. Sereen Althaher

By: Mhmd Abuhashya

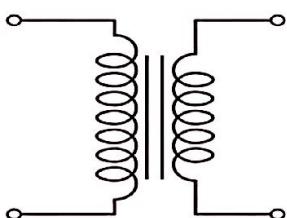

Powerunit-ju.com


* Rectifier *

- Why we use it? To control the voltage.
- Application: Induction Motor (No load).
- from PIZ model: if we want to decrease $V \Rightarrow$ decrease the current.
 $\downarrow = Z \downarrow I \downarrow$ $\Rightarrow P = IV$ (also decreased).
- H.W \equiv Half-Wave. • F.W \equiv Full-Wave.

* We will study the following subjects:

- \Rightarrow Resistive 1φ-H.W.
- \Rightarrow Inductive 1φ F.W.
- \Rightarrow Capacitive 3φ.

* Single-phase Half-Wave:

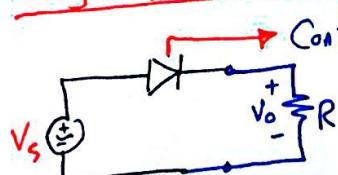


Control cct SCR "silicon Controlled Rectifier".

we will deal with the diode in ideal case. ($P=0$)

* Triggering Signal:
 $\alpha \equiv$ triggering point.

$$V_s = V_{max} \sin \omega t$$

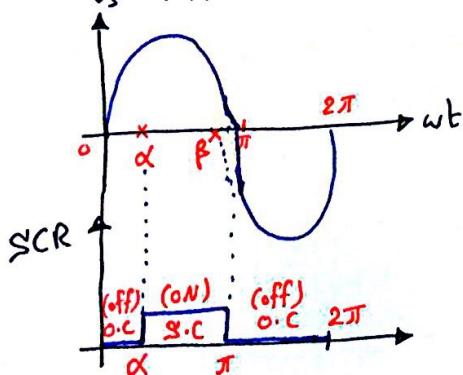

$$* I_{avg} = \frac{V_{avg}}{R} *$$

$$\text{case (I): } \beta < \pi \Rightarrow V_{avg} = \frac{1}{T} \int_{\alpha}^{\beta} V_{max} \sin \omega t dt$$


$$\text{case (II): } \beta > \pi \Rightarrow V_{avg} = \frac{1}{T} \int_{\alpha}^{\pi} V_{max} \sin \omega t dt$$

we will take case (II):

$$V_{avg} = \frac{V_{max}}{2\pi} [\cos \alpha - \cos \pi]$$

$$* \Rightarrow V_{avg} = \frac{V_m}{2\pi} [\cos \alpha + 1] *$$

. Draw V_{avg} :

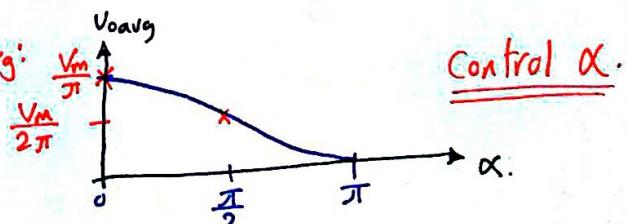

Control α .



Example: 1Ø-H.W rectifier is used to reduce the avg. voltage across a Resistive Load $R = 0.2 V_{o,\text{avg}}^2 + 5$ if $V_s = 110 \text{ rms}$ @ $\alpha = 90^\circ$.

Find: a) $I_o, \text{avg.}$? b) Plot the voltage across the SCR?

Solution:

$$\text{a) } I_{o,\text{avg}} = \frac{V_{o,\text{avg}}}{R} \Rightarrow V_{o,\text{avg}} = \frac{V_m}{2\pi} [1 + \cos \alpha] = \frac{110\sqrt{2}}{2\pi} = 24.76 \text{ volt.}$$
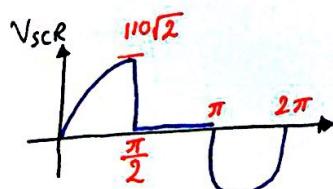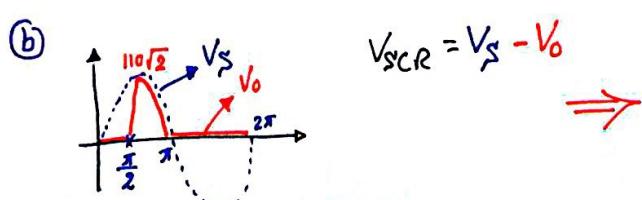
$$\Rightarrow R = 0.2 V_{o,\text{avg}}^2 + 5 \Rightarrow R = 127.6 \Omega \quad \boxed{I_{o,\text{avg}} = 0.194 \text{ A.}}$$



* Output voltage (RMS):

$$V_{o,\text{rms}} = \sqrt{\frac{1}{T} \int_0^T (V_o \sin \omega t)^2 dt} = \sqrt{\frac{V_m^2}{2\pi} \int_0^{\pi} \sin^2 \omega t dt} \quad \sin^2 \omega t = \frac{1}{2} [1 - \cos 2\omega t]$$

$$= \frac{V_m}{\sqrt{2} \cdot \sqrt{2}} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}} \Rightarrow \boxed{V_{o,\text{rms}} = \frac{V_{s,\text{rms}}, \text{source}}{\sqrt{2}} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}}}$$

@ $\alpha = 0$:


$$V_{o,\text{rms}} = \frac{V_{s,\text{rms}}}{\sqrt{2}}$$

@ $\alpha = \frac{\pi}{2}$:

$$V_{o,\text{rms}} = \frac{V_{s,\text{rms}}}{2}$$

@ $\alpha = \pi$:

$$V_{o,\text{rms}} = 0$$

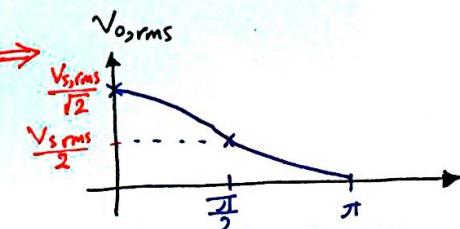

Example: AC source of 110 V rms is connected to a resistive element 2Ω through a H.W, 1Ø rectifier. for $\alpha = \frac{\pi}{4}$ & $\alpha = \frac{\pi}{2}$ find the following:

a) $V_{o,\text{rms}}$. b) $I_{o,\text{rms}}$. c) $V_{o,\text{avg}}$ drop across SCR.

Solution: a) $V_{o,\text{rms}} = 74.13 \text{ volt.}$ b) $I_{o,\text{rms}} = 37.07 \text{ A.}$

$$@ \alpha = \frac{\pi}{4}$$

$$V_{o,\text{rms}} = 55 \text{ volt.}$$

$$@ \alpha = \frac{\pi}{2}$$

$$I_{o,\text{rms}} = 27.5 \text{ A.}$$

$$@ \alpha = \frac{\pi}{2}$$

$$\boxed{c) V_{o,SCR} = V_{s,\text{avg}} - V_{o,\text{avg}}}$$

$$V_{o,SCR} = 0 - V_{o,\text{avg}}$$

$$\Rightarrow V_{o,SCR} = -42.27 \text{ volt.} \quad @ \alpha = \frac{\pi}{4}$$

$$\Rightarrow V_{o,SCR} = -24.76 \text{ volt.} \quad @ \alpha = \frac{\pi}{2}$$

Example: Design Rectifier to have a given V_s & a desired $V_{o,\text{avg}}$?

Design \Rightarrow find α by iterations.

\rightarrow to find $V_{o,\text{avg}}$ \Rightarrow find α from:

$$V_{o,\text{avg}} = \frac{V_m}{2\pi} [1 + \cos \alpha]$$

Take $V_{s,\text{rms}} = 110 \text{ volt}$, $V_{o,\text{rms}} = 80 \text{ volt.}$, Take $\alpha = 0, \frac{\pi}{2}, \pi$.

$$V_{o,\text{avg}} = \frac{V_{s,\text{rms}}}{\sqrt{2}} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}}$$

α by iterations

* Average Power:


$$P_{avg} = V_{0,rms} I_{0,rms} = \frac{V_{0,rms}^2}{R} = I_{0,rms}^2 R$$

$$\Rightarrow P_{avg} = \frac{V_m^2}{8\pi R} [2(\pi - \alpha) + \sin 2\alpha]$$

$$@ \alpha = \frac{\pi}{2}: P_{avg} = \frac{V_m^2}{8R}$$

$$@ \alpha = \pi: P_{avg} = \text{Zero.}$$

in rad.

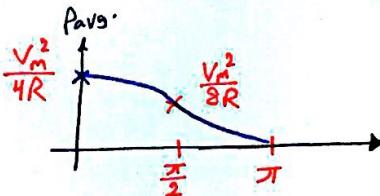

$$P_{avg, max} = \frac{V_m^2}{4R}$$

α = firing angle.

* Power Factor:

$$PF = \frac{|P|}{|SI|} \Rightarrow |SI| = V_{rms} I_{rms}$$

$$P = V_{rms} I_{rms} \cos \phi$$

this for i_s \Rightarrow Not sinusoidal.

\rightarrow harmonics.
 \rightarrow fundamental.

* Fourier Transform for $i_s(t)$:

$$\hookrightarrow i_s(t) = C \sin(\omega t + \phi)$$

$i_s(t)$ has the same figure of $v_s(t)$ divided by R .

$$I_{s,rms} = C_1 = \sqrt{a_1^2 + b_1^2}$$


$$a_1 = \frac{I_{s,max}}{2\pi} [\cos(2\alpha) - 1]$$

$$\hookrightarrow I_{s,max} = \frac{V_{s,max}}{R}$$

$$b_1 = \frac{I_{s,max}}{2\pi} [\sin 2\alpha + 2(\pi - \alpha)]$$

$$\phi_1 = \tan^{-1} \left[\frac{a_1}{b_1} \right]$$

$$\cos \phi_1 = \frac{b_1}{C_1}$$

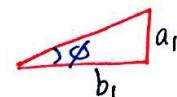

$$\Rightarrow PF = \frac{I_{s,rms}}{I_{rms}} \cos \phi$$

Example: 1Ø H.W.R is connected to 10Ω Resistor. $V_s = 110$ rms & $\alpha = 60^\circ$.

Find: P_{load} & PF ?

$$\text{Solution: } P_{load} = \frac{V_m^2}{8\pi R} [2\pi - 2\alpha + \sin 2\alpha] \Rightarrow P_{load} = 486.7 \text{ W.}$$

$$PF \Rightarrow I_{0,rms} = \frac{V_{rms}}{R} = \frac{V_{s,rms}}{\sqrt{2} R} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}}$$

$$\Rightarrow PF = \frac{I_{rms}}{I_{0,rms}} \cos \phi$$

$$I_{s,rms} \rightarrow \begin{cases} a_1 = -3.71 \\ b_1 = 6.24 \end{cases}$$

$$\Rightarrow PF = 0.447$$

$$\phi = \tan^{-1} \left(\frac{a_1}{b_1} \right)$$


lagging.

* Single-Phase - Full-Wave-Rectifier: "Resistive Load"

[40]

• Configuration: $V_S = V_m \sin \omega t$

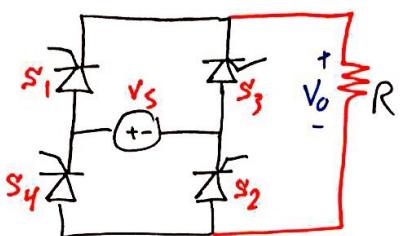
• Case ($V_S > 0$): S_1, S_2 (ON). from $\alpha \rightarrow \pi$.



$$\text{By KVL: } -V_S + V_O = 0 \Rightarrow V_O = V_S$$

• Case ($V_S < 0$): S_3, S_4 (ON).
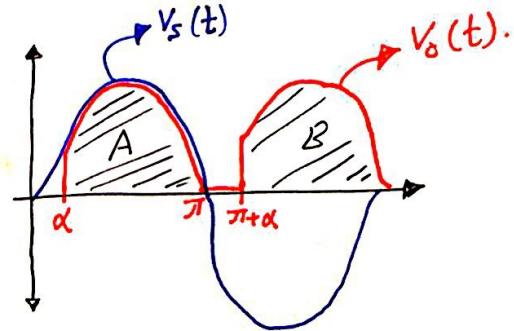
$$\text{By KVL: } +V_O + V_S = 0 \Rightarrow V_O = -V_S$$



$$V_{avg, FW} = 2V_{avg, HW}$$

$$P_{FW} = 2P_{HW}$$

$$V_{rms, FW} = \sqrt{2} V_{rms, HW}$$

$$\begin{aligned} a_{FW} &= 2a_{HW} \\ b_{FW} &= 2b_{HW} \\ C_{FW} &= 2C_{HW} \end{aligned}$$


$$PF_{HW} = PF_{FW}$$

A & B are symmetrical.

Example: F.W.R $R = 5 \Omega$, $V_S = 110V_{rms}$ $\Rightarrow V_{rms} = 55 V_{rms}$ Find α ?

$$\text{Solution: } V_{rms} = V_{S,rms} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}} \Rightarrow 55 = 110 \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}}$$



• By Try & Error:

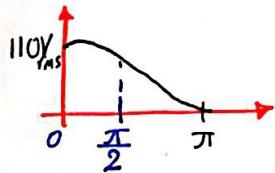

$$\begin{aligned} \text{Try } \alpha &= 0 \\ \text{Try } \alpha &= \frac{\pi}{2} \\ \text{Try } \alpha &= \pi \end{aligned}$$

$$\alpha = 112^\circ$$

* 1-Φ H.W.R : "Inductive Load"

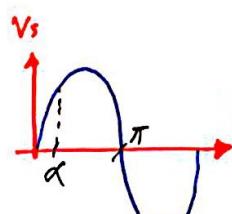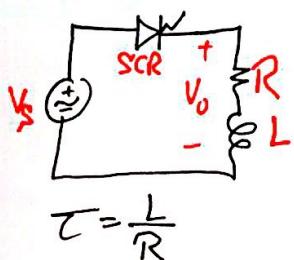

$$T = \frac{L}{R}$$

$$\begin{aligned} V_L(t) &= V_{max} \cos(\omega t - \frac{\pi}{2}) \\ I_L(t) &= -I_{max} \cos(\omega t) \\ P_L(t) &= -\frac{V_{max} I_{max}}{2} \sin(2\omega t) \end{aligned}$$

Assume Purely inductive Load: ($R=0$).

$$V_L(t) = V_{max} \sin(\omega t) = V_{max} \cos(\omega t - \frac{\pi}{2})$$

$$I_L(t) = I_{max} \cos(\omega t - \frac{\pi}{2} - \frac{\pi}{2})$$

$$\Rightarrow I_L(t) = I_{max} \cos(\omega t - \pi)$$


$$= -I_{max} \cos(\omega t).$$

$$P_L(t) = V(t) I(t)$$


$$= -V_{max} I_{max} \sin \omega t \cos \omega t$$

$$= -\frac{V_{max} I_{max}}{2} \sin 2\omega t$$

41

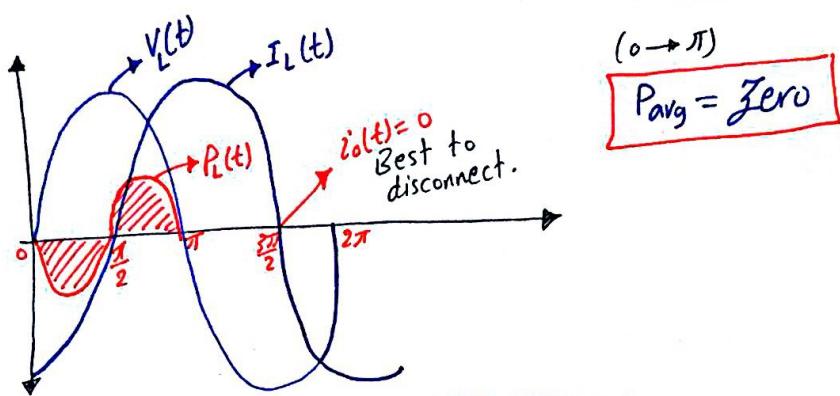

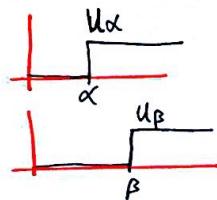
$$V_o(t) = V_s \quad (\alpha \rightarrow \beta) \Rightarrow V_o = V_s [U_\alpha - U_\beta] \quad i(t) = \frac{V_o(t)}{Z}$$



Laplace
 $i(t)$

$$i(t) = \frac{V_{max}}{|Z|} \left[(U_\alpha - U_\beta) \sin(\omega t - \phi) + U_\alpha \sin(\phi - \alpha) e^{-\frac{(wt-\alpha)}{\omega C}} \right]$$
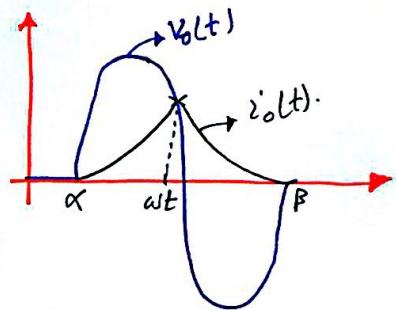
$$\begin{aligned} T &= \frac{1}{R} \\ Z &= \sqrt{R^2 + (\omega L)^2} \\ \phi &= \tan^{-1} \left(\frac{\omega L}{R} \right) \end{aligned}$$





$$V_{avg} = \frac{1}{2\pi} \int_{\alpha}^{\beta} V_{s,max} \sin \omega t \, d\omega t = \frac{V_{s,max}}{2\pi} [\cos \alpha - \cos \beta]$$

$$\Rightarrow I_{avg} = \frac{I_{avg,L}}{R} + I_{avg,R} = \text{Zero} + \frac{V_{avg}}{R} \Rightarrow I_{avg} = \frac{V_{s,max}}{2\pi R} [\cos \alpha - \cos \beta]$$

$$V_{avg} = V_{avg,L} + V_{avg,R} = \text{Zero} + I_{avg} R \Rightarrow \frac{V_o}{avg} = I_{avg} R \Rightarrow \text{Find } V_{rms} ?!$$

* 1φ-H.W.R with inductive load + Free wheeling diode:

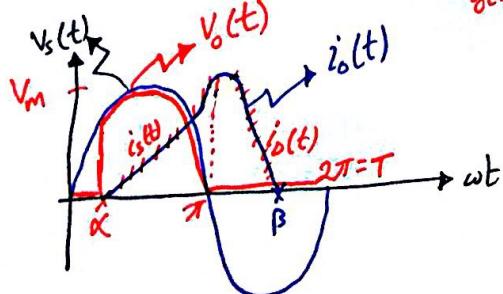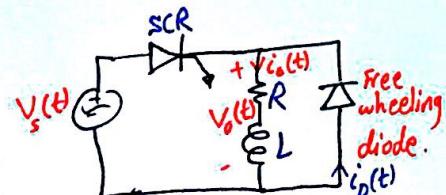we want to find $\langle V_o \rangle$, $V_o(t)$ & $i_o(t)$!?



$$i(t) = \begin{cases} \cdot \alpha \rightarrow \pi: \\ \quad i_s(t) = \frac{V_m}{|Z|} \left[\sin(\omega t - \phi) + \sin(\phi - \alpha) e^{-\frac{(wt-\alpha)}{\omega C}} \right] \dots \textcircled{1} \\ \cdot \pi \rightarrow \beta: \\ \quad i_D(t) = i_s(\pi) e^{-\frac{(wt-\pi)}{\omega C}} u(\omega t - \pi) \dots \textcircled{2} \end{cases}$$

$$V_{avg} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) \, d\omega t = \frac{V_m}{2\pi} [\cos \alpha + 1]$$

$$i_{avg} = I_{R,avg} = \frac{V_{avg}}{R}$$

Example: 1 ϕ -H.W.R connected to inductive load $R=10\Omega$, $L=20mH$.

[42]

$V_s = 110 \text{ volt}$ connected with F.W diode $\alpha = 60^\circ$, $f = 60 \text{ Hz}$.

Find: ① Conduction period $\gamma = \beta - \alpha$? ② i_{\max} ? ③ i_{avg} ?

Solution:

① Here we make assumptions: $< 10\%$ $\Rightarrow i_d(\beta) = 0.05 i_s(\pi)$

$$\text{so } 0.05 i_s(\pi) = i(\pi) e^{-\frac{(\beta-\pi)}{\omega T}}, \quad T = 2 \text{ msec.} \quad \Rightarrow \ln(0.05) = -\frac{(\beta-\pi)}{\omega T}$$


solving: $\beta = 309^\circ$

$$\therefore \gamma = \beta - \alpha = 309^\circ - 60^\circ \Rightarrow \gamma = 249^\circ$$

② The max value will occur @ $wt = \pi$: use equation ① in the previous page to find $i_{\max} = i_s(\pi)$. $\Rightarrow I_{\max} = 7.478 \text{ A}$.

$$③ i_{\text{avg}} = \frac{V_{\text{avg}}}{R} = \frac{\sqrt{2} V_{\text{rms}}}{2\pi R} [\cos \alpha + 1] \Rightarrow I_{\text{avg}} = 3.714 \text{ A}$$

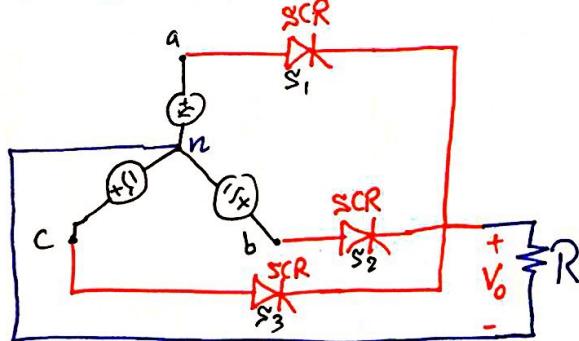* 3 ϕ H.W.R with Resistive Load: assume abc sequence "Balanced"



$$V_{an} = V_m \sin \omega t$$


$$V_{bn} = V_m \sin(\omega t - 120^\circ)$$

$$V_{cn} = V_m \sin(\omega t + 120^\circ)$$


$$S_1 \text{ ON} \Rightarrow V_{an} > V_{bn}, V_{cn}$$

$$S_2 \text{ ON} \Rightarrow V_{bn} > V_{an}, V_{cn}$$
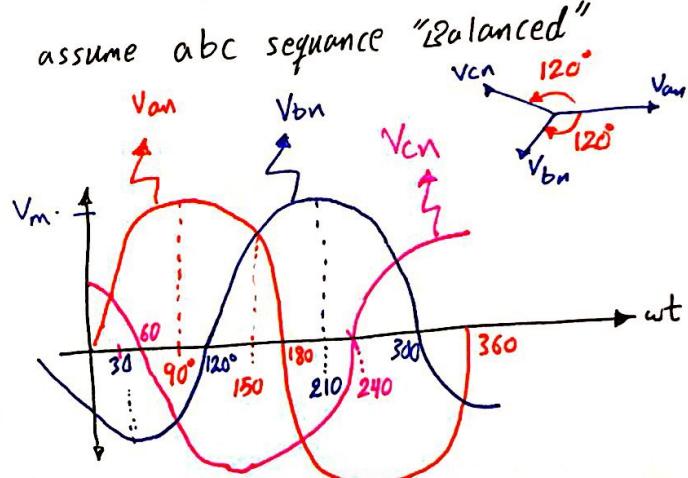
$$S_3 \text{ ON} \Rightarrow V_{cn} > V_{an}, V_{bn}$$




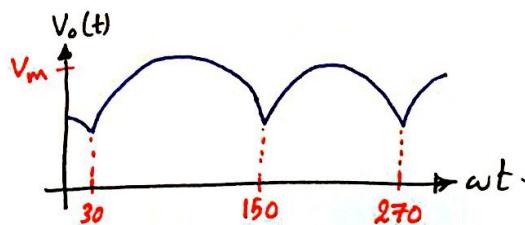- $0 \rightarrow 30^\circ \Rightarrow S_3 \text{ ON. } V_o = V_{cn}$
- $30 \rightarrow 150^\circ \Rightarrow S_1 \text{ ON. } V_o = V_{an}$
- $150 \rightarrow 270^\circ \Rightarrow S_2 \text{ ON } V_o = V_{bn}$



\Rightarrow All previous analysis for 3 ϕ done using $\alpha = 0$.

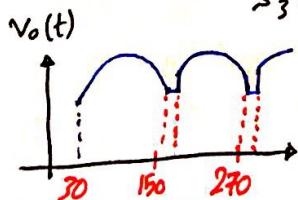if $\alpha = 30^\circ \Rightarrow S_1 \rightarrow \alpha$.
 $S_2 \rightarrow \alpha + 120^\circ$
 $S_3 \rightarrow \alpha + 240^\circ$



$$* V_{\text{avg}}: V_{\text{avg}}(3\phi) = 3 V_{\text{avg}}(1\phi)$$

$$* P_{\text{avg}}: P_{\text{avg}}_{3\phi} = 3 P_{\text{avg}}_{1\phi}$$

$$* I_{\text{avg}}: I_{\text{avg}} = \frac{V_{\text{avg}}}{R}$$

$$V_{o\ avg} = \frac{3V_m}{2\pi} [\cos\alpha - \cos\beta], \quad P_{avg} = \frac{3V_m^2}{8\pi R} [2(\beta-\alpha) + \sin 2\alpha - \sin 2\beta] \quad [43]$$

Example: 3ϕ - H.W.R $V_{ab} = 208 V_{rms}$, $R = 10\Omega$, $\alpha = 80^\circ, 30^\circ$ find P_{avg} ?


Solution: $V_m = \frac{208}{\sqrt{3}} * \sqrt{2}$ volt. for $\alpha = 80^\circ \Rightarrow \beta = \alpha + 120 = 200^\circ \Rightarrow 180^\circ$
for $\alpha = 30^\circ \Rightarrow \beta = 150^\circ$

$$\frac{P_{\alpha=80^\circ}}{3\Phi} = 1.32 kW, \quad \frac{P_{\alpha=30^\circ}}{3\Phi} = 2.042 kW$$


Note: MAX P_{avg} @ $\alpha = 0$.

* 3ϕ F.W.R :


• Configuration:

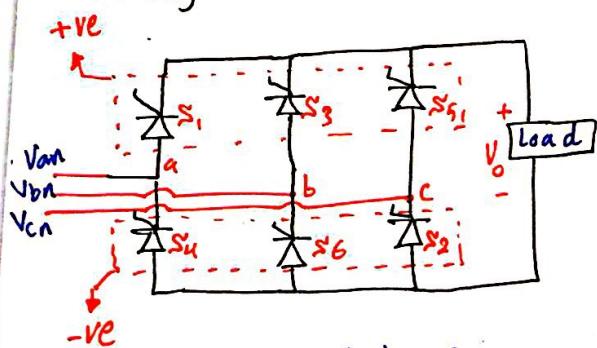


\Rightarrow Y-connection (Balanced)
abc

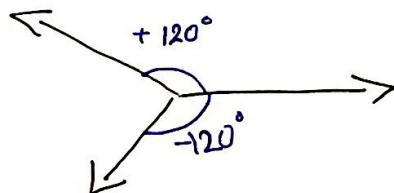

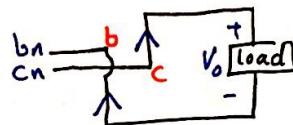* $0 \rightarrow 30^\circ$: $\begin{matrix} \text{upper} & \text{lower} \\ \text{S}_5 & \text{S}_6 \end{matrix}$ $\Rightarrow V_o = V_{an} - V_{bn}$



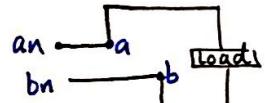By KVL: $+V_o + V_{bn} - V_{cn} = 0 \Rightarrow V_o = V_{cn} - V_{bn} \Rightarrow V_o = V_{CB}$



* $30^\circ \rightarrow 60^\circ$: $\begin{matrix} \text{upper} & \text{lower} \\ \text{S}_1 & \text{S}_6 \end{matrix} \Rightarrow V_o = V_{AB}$

* $60^\circ \rightarrow 90^\circ$: $\begin{matrix} \text{upper} & \text{lower} \\ \text{S}_1 & \text{S}_6 \end{matrix} \Rightarrow V_o = V_{AB}$

* $90^\circ \rightarrow 120^\circ$: $\begin{matrix} \text{upper} & \text{lower} \\ \text{S}_1 & \text{S}_2 \end{matrix} \Rightarrow V_o = V_{AC}$

* $120^\circ \rightarrow 150^\circ$: $\begin{matrix} \text{upper} & \text{lower} \\ \text{S}_1 & \text{S}_2 \end{matrix} \Rightarrow V_o = V_{AC}$

* $150^\circ \rightarrow 180^\circ$: $\begin{matrix} \text{upper} & \text{lower} \\ \text{S}_3 & \text{S}_2 \end{matrix} \Rightarrow V_o = V_{DC}$

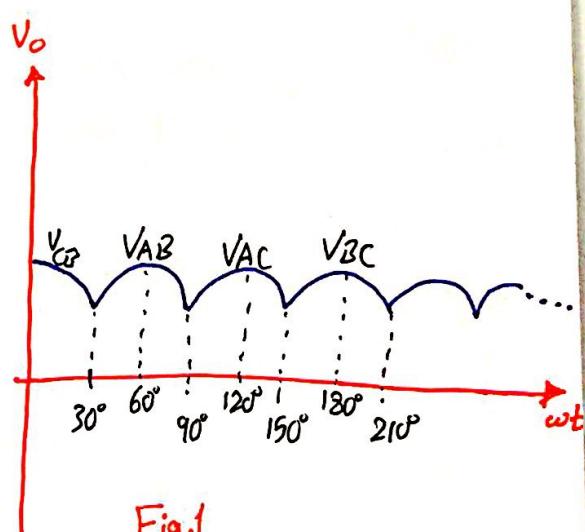


Fig.1



• Average for previous Fig.1: $V_{avg} = \frac{6}{2\pi} \int_{30}^{90} V_{AB} dt$ [44]

$$V_{an} = |V_{an}| \sin \omega t$$

$$V_{ab} = \sqrt{3} |V_{an}| \sin(\omega t + 30^\circ)$$

$$= \sqrt{3} |V_{an}| \sin(\omega t + 30^\circ)$$

$$\Rightarrow V_{avg} = \frac{3}{\pi} \int_{30}^{90} \sqrt{3} |V_{an}| \sin(\omega t + 30^\circ) dt$$

$$= \frac{3\sqrt{3} |V_{an}|}{\pi} [\cos 60 - \cos 120]$$

$$\Rightarrow V_{avg} = \frac{3\sqrt{3} |V_{an}|}{\pi} \xrightarrow{\text{peak value}}$$

• for the current:

$$I_{avg} = \frac{V_{avg}}{R}$$

$$\begin{array}{l} 0 \rightarrow 30 \quad S_5, S_6 \\ 30 \rightarrow 60 \quad S_1, S_6 \\ 60 \rightarrow 90 \quad S_1, S_5 \\ 90 \rightarrow 120 \quad S_1, S_2 \\ 120 \rightarrow 150 \quad S_1, S_2 \\ 150 \rightarrow 210 \quad S_3, S_2 \end{array}$$

$\alpha = 30^\circ$ Conduction Period $S_i \Rightarrow 120^\circ$

$$\begin{array}{ll} S_5: & 30^\circ \\ S_1: & 60 \rightarrow 180^\circ \\ S_2: & 90 \rightarrow 210 \end{array}$$

$$S_1, S_6 \Rightarrow V_{AB} (60 \rightarrow 90)$$

the same figure would be observed just shifted by 30° .

$$\text{For } V_{avg}: V_{avg} = \frac{6}{2\pi} \int_{30+\alpha}^{90+\alpha} |V_{an}| \sqrt{3} \sin(\omega t + 30^\circ) dt \Rightarrow \frac{3|V_{an}| \sqrt{3}}{\pi} [\cos(60 + \alpha) - \cos(120 + \alpha)]$$

$$= \frac{3\sqrt{3} |V_{an}|}{\pi} [\cos 60 \cos \alpha - \sin 60 \sin \alpha - \cos 120 \cos \alpha + \sin 120 \sin \alpha]$$

$$\Rightarrow V_{avg} = \frac{3\sqrt{3} |V_{an}|}{\pi} \cos \alpha \quad \text{for } \alpha = 0 \rightarrow 60$$

in case $\alpha = 60^\circ$

$$S_1, S_6 \Rightarrow V_{AB} (90 \rightarrow 120)$$

$$V_{AB} (120 \rightarrow 150)$$

$$S_5, S_6 \Rightarrow V_{CB} (60 \rightarrow 90)$$

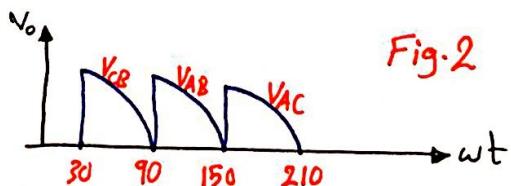


Fig. 2

in case $\alpha = 90^\circ$

$$S_1, S_6 \Rightarrow V_{AB} (120 \rightarrow 150)$$

$$V_{AB} (150 \rightarrow 180)$$

$$S_1, S_2 \Rightarrow V_{AC} (180 \rightarrow 210)$$

$$V_{AC} (210 \rightarrow 240)$$

$$\text{For Fig. 3: } V_{avg} = \frac{6}{2\pi} \int_{30+\alpha}^{150} |V_{an}| \sqrt{3} \sin(\omega t + 30^\circ) dt$$

$$= \frac{3\sqrt{3} |V_{an}|}{\pi} [\cos(60 + \alpha) - \cos(180)]$$

$$\Rightarrow V_{avg} = \frac{3\sqrt{3} |V_{an}|}{\pi} [\cos(60 + \alpha) + 1] \quad \text{for } \alpha = 90 \rightarrow 120$$



Fig. 3

$$\text{for } \alpha = 60^\circ \rightarrow 90^\circ : V_{avg} = \frac{6}{2\pi} \int_{30^\circ + \alpha}^{60^\circ + \alpha} |V_{an}| \sqrt{3} \sin(\omega t + 30^\circ) d\omega t \Rightarrow V_{avg} = \frac{3\sqrt{3} |V_{an}|}{\pi} \cos \alpha$$

* The Average Voltage given by:

$$V_{avg} = \begin{cases} \frac{3\sqrt{3} |V_{an}|}{\pi} \cos \alpha & , 0^\circ \leq \alpha < 90^\circ \\ \frac{3\sqrt{3} |V_{an}|}{\pi} [\cos(60^\circ + \alpha) + 1] & , 90^\circ \leq \alpha < 120^\circ \\ \text{Zero} & , \alpha \geq 120^\circ \end{cases}$$


Example: 3φ F.W.R, $V_{rms} = 208$ volt.

Find: i) Max. V_{avg} ? ii) α @ which $V_{avg} = V_{phase}$? iii) V_o , $\alpha = 30^\circ$?

Solution: i) Max @ $\alpha = 0^\circ \Rightarrow V_{avg} = \frac{3\sqrt{3} |V_{an}|}{\pi} \cos 0^\circ$, $V_{an} = \frac{\sqrt{2}}{\sqrt{3}} (208)$

assume $0^\circ \leq \alpha < 90^\circ$:

ii) $V_{avg} = \frac{3\sqrt{3} |V_{an}|}{\pi} \cos \alpha \Rightarrow V_{an} = V_{avg} \Rightarrow \cos \alpha = \frac{\pi}{3\sqrt{3}} \Rightarrow \alpha = 52.8^\circ$ if α wasn't $0^\circ \leq \alpha < 90^\circ$

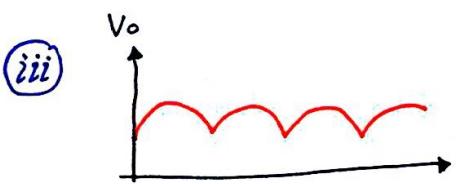

same Fig. 1 shifted By 30° .

Try other intervals.

* AC/AC Converter:

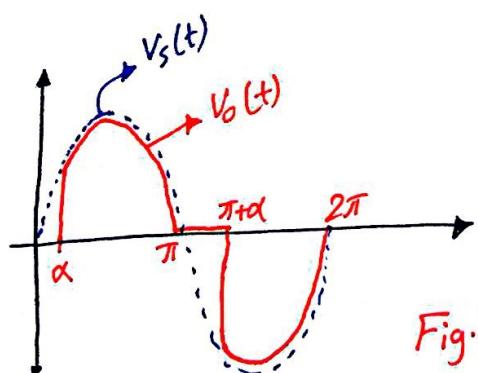
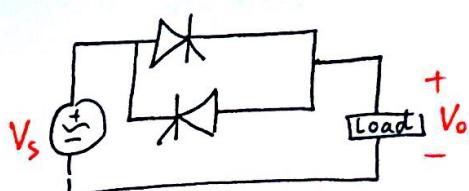


Fig. 4.

* for Fig. 4:

• Avg: $V_{avg} = \text{Zero.}$

• RMS: $V_{rms} = \sqrt{\frac{2}{2\pi} \int_{\alpha}^{\pi} (V_m \sin \omega t)^2 d\omega t}$

solving:

$$V_{rms} = \frac{V_m}{\sqrt{2\pi}} \sqrt{(\pi - \alpha) + \frac{\sin 2\alpha}{2}}$$

* * * End of Material * * *
Best of Luck * * *

