

* Harmonics:

• $f(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t)$

• $f(t) = a_0 + \sum_{n=1}^{\infty} C_n \cos(n\omega t + \theta_n)$

• $f(t) = a_0 + \sum_{n=1}^{\infty} C_n \sin(n\omega t + \theta_n) \rightarrow \theta_n = \tan^{-1}\left(\frac{a_n}{b_n}\right)$

$a_0 = \frac{1}{T} \int f(t) dt$
 $a_n = \frac{2}{T} \int f(t) \cos(n\omega t) dt$
 $b_n = \frac{2}{T} \int f(t) \sin(n\omega t) dt$

$C_n = \sqrt{a_n^2 + b_n^2}$, $\theta_n = \tan^{-1}\left(\frac{-b_n}{a_n}\right)$

• RMS: $F_{rms} = \sqrt{a_0^2 + \sum_{n=1}^{\infty} \left(\frac{C_n}{\sqrt{2}}\right)^2}$

* For Non linear $v(t)$ & $I(t)$: $P_{avg} = V_0 I_0 + \sum_{n=1}^{\infty} V_{rms,n} I_{rms,n} \cos(\theta_n - \phi_n)$

* For Linear $V_s(t)$ & Non linear $I(t)$:

$P_{avg} = V_{s,rms} I_{1,rms} \cos(\theta_s - \phi_1)$

$PF = \frac{I_{1,rms}}{I_{rms}} \cos(\theta_s - \phi_1)$

$DF = \frac{I_{1,rms}}{I_{rms}}$

$I_{rms} = \sqrt{I_0^2 + \sum_{n=1}^{\infty} \left(\frac{I_n}{\sqrt{2}}\right)^2}$

• THD: $THD = \sqrt{\frac{I_{rms}^2 - I_{1,rms}^2}{I_{1,rms}^2}}$, $DF = \frac{1}{\sqrt{1 + (THD)^2}}$

* Complex Power:

$S = \sqrt{P^2 + Q^2 + D^2}$

$D = V_{s,rms} \sqrt{\sum_{n \neq 1}^{\infty} I_{n,rms}^2}$

@ Fundamental.

* Switch: $T_{on} = DT \Rightarrow D = \frac{T_{on}}{T}$, $T = T_{on} + T_{off}$


• Assumptions:

@ steady state: $I_{C,avg} = 0$ & $V_{L,avg} = 0$

@ C.C.M: $I_{L,min} > 0$

• RMS for Sawtooth Signal:
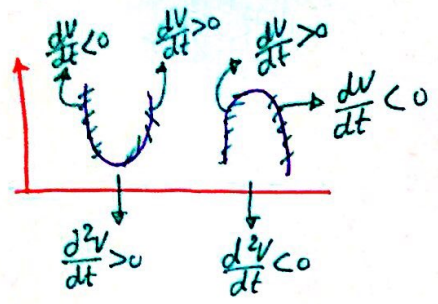
$$RMS = \sqrt{DC^2 + \left(\frac{\Delta i_L}{2\sqrt{3}}\right)^2}$$



✳ Buck :

• cct: $V_{in} \xrightarrow{D} L \rightarrow C \rightarrow R$

• C.C.M : $(\Delta i_L)_{close} = \frac{DT}{L} (V_{in} - V_o)$
 $(\Delta i_L)_{open} = \frac{-V_o T (1-D)}{L}$

$$V_o = DV_{in}$$

$$I_{L \max} = \frac{V_o}{R} + \frac{V_o T (1-D)}{2L}$$

$$\Rightarrow \underline{I_L = I_{o \text{ avg}}} \text{ , } \underline{I_S = D I_{L \text{ avg}}} \text{ , } \underline{I_D = (1-D) I_{L \text{ avg}}}$$

$$L_{min} = \frac{RT(1-D)}{2}$$

↳ $L = 1.25 L_{min}$

$$C = \frac{(1-D)}{8Lf^2 * \text{Ripple}}$$

↳ $\text{Ripple} = \frac{\Delta V_o}{V_o}$

$$I_{C \max} = \frac{+}{-} \frac{TV_o(1-D)}{2L}$$

* if there is r_c :

$$\Delta V_o = \Delta i_c r_c \Rightarrow \Delta i_c = \frac{V_o(1-D)}{Lf} \Rightarrow \text{Ripple} = \frac{\Delta V_o}{V_o}$$

• D.C.M :

$P_{in} = P_{out}$ (ideally).

* To find D_1 : Take Av. for i_L .

$$I_{L \min} = 0$$

$$I_{L \max} = \frac{DT(V_{in} - V_o)}{L}$$

** { @ D.C.M: $D_1 < 1-D$
 @ C.C.M: $D_1 > 1-D$

$$V_o = V_{in} \frac{D}{D+D_1}$$

$$D_1 = \frac{-D + \sqrt{D^2 + \frac{8L}{RT}}}{2}$$

* Boost: cct: $V_{in} \xrightarrow{L} S \xrightarrow{D} C \xrightarrow{R}$

C.C.M:

$(\Delta i_L)_{close} = \frac{V_{in} D}{Lf}$
 $(\Delta i_L)_{open} = \frac{(1-D)}{Lf} (V_{in} - V_o)$

$V_o = \frac{V_{in}}{1-D}$, $I_{L_{avg}} = \frac{V_{in}}{R(1-D)^2}$

$\Delta i_c = I_{L_{max}}$

$I_{L_{max}} = \frac{V_{in}}{R(1-D)^2} \pm \frac{V_{in} D}{2Lf}$

$L_{min} = \frac{RD}{2f(1-D)^2} \rightarrow L = 1.25 L_{min}$

$C = \frac{DT}{R * Ripple}$

* if there is r_c : same as Buck.

* if there is r_L :

$P_{in} = P_o + P_{loss}$
 $P_{loss} = r_L I_{L_{avg}}^2$

$I_{L_{avg}} = \frac{I_{L_{max}} + I_{L_{min}}}{2}$

$I_o = I_D = (1-D) I_{L_{avg}}$

$V_o = \frac{V_s}{1-D} \left[\frac{1}{1 + \frac{r_L}{R_o(1-D)^2}} \right]$

efficiency:

$\eta = \frac{1}{1 + \frac{r_L}{R(1-D)^2}}$

D.C.M:

$V_o = \frac{V_s}{D_1} (D+D_1)$

$D_1 = \frac{2V_o L}{R V_s D T}$

$V_o = \frac{V_s}{2} \left[1 + \sqrt{\frac{2D^2 RT}{L} + 1} \right]$

** { @ C.C.M: $I_{L_{min}} \geq 0$
 @ D.C.M: $I_{L_{min}} < 0$

* Buck-Boost:

** { Boost ; $D > 0.5$
 Buck ; $D < 0.5$

$P_{in} = P_{out}$

$D = \frac{|V_o|}{V_s + |V_o|}$

$V_o = \frac{-V_{in} D}{1-D}$

cct: $V_s \xrightarrow{S} L \xrightarrow{D} C \xrightarrow{R}$

$I_{L_{max}} = I_{L_{avg}} \pm \frac{\Delta i_L}{2}$

$I_{L_{avg}} = \frac{V_{in} D}{R(1-D)^2}$

$\Delta i_c = (\Delta i_L)_{close}$

$I_{in_{avg}} = D I_{L_{avg}}$

$(\Delta i_L)_{close} = \frac{V_o D}{Lf}$
 $(\Delta i_L)_{open} = \frac{V_o(1-D)}{Lf}$

* with r_c :
 $\Delta V_o = \Delta i_c r_c$; $\Delta i_c = I_{L_{max}}$

$L_{min} = \frac{I R (1-D)^2}{2}$

$C = \frac{(DT)^2}{R * Ripple}$

2-Quadrant Converter:

• when S_1 closed: $V_{i2} = DV_{in}$.

$$i_L = \frac{V_{i2} - V_o}{R}$$

• when S_2 closed:

→ find ΔV_L (when $V_{i2} = 0$, By KVL)

then find $\Delta i_L = T(1-D) \frac{\Delta V_L}{L}$

• For the First Case:

• Switch ON: $V_o = -R i_o + L \frac{di_o}{dt} + V_a$ $0 < t \leq T_1$

• Diode ON: $V_o = 0 = V_a + R i_o + L \frac{di_o}{dt}$ $0 < t \leq T - T_1$

$$\Rightarrow i_o(t) = \begin{cases} i_o(t) = \frac{V_s - V_a}{R} (1 - e^{-t/\tau}) + I_{min} e^{-t/\tau}, & 0 < t \leq T_1 \\ i_o(t) = -\frac{V_a}{R} (1 - e^{-t/\tau}) + I_{max} e^{-t/\tau}, & 0 < t \leq T - T_1 \end{cases}$$

• MAX & MIN:

$$I_{max} = \frac{V_s}{R} \left[\frac{1 - e^{-T_1/\tau}}{1 - e^{-T/\tau}} \right] - \frac{V_a}{R}$$

$$I_{min} = \frac{V_s}{R} \left[\frac{e^{T_1/\tau} - 1}{e^{T/\tau} - 1} \right] - \frac{V_a}{R}$$

$$D = \frac{T_{on}}{T}$$

$$\tau = L/R$$

*Ripple:

$$\Delta I = I_{max} - I_{min}$$

$$V_{o_{avg}} = DV_s$$

$$I_{o_{avg}} = \frac{DV_s - V_a}{R}$$

$$V_{o_{RMS}} = \sqrt{D} V_s$$

4-Quadrant Converter:

$$* i_o(t) = \frac{V_s - V_a}{R} [1 - e^{-t/\tau}] + I_{min} e^{-t/\tau} \quad \text{for } 0 < t \leq T_{on}; D \geq 0.5$$

$$* i_o(t) = -\left(\frac{V_s + V_a}{R}\right) [1 - e^{-t/\tau}] + I_{max} e^{-t/\tau} \quad \text{for } 0 < t \leq T - T_{on}; D \leq 0.5$$

$$* i_o(t) = \frac{-V_a}{R} [1 - e^{-t/\tau}] + I_{max} e^{-t/\tau} \quad \text{for } \begin{cases} 0 < t \leq T_{on}; D < 0.5 \\ 0 < t \leq T - T_{on}; D \geq 0.5 \end{cases}$$

• MAX & MIN:

$$I_{max} = \frac{V_s}{R} \left[\frac{1 - e^{-T_{on}/\tau}}{1 - e^{-T/\tau}} \right] - \frac{V_a}{R}$$

$$I_{min} = \frac{V_s}{R} \left[\frac{e^{T_{on}/\tau} - 1}{e^{T/\tau} - 1} \right] - \frac{V_a}{R}$$

* Ripple:

$$\Delta I = I_{max} - I_{min}$$

$$V_{o_{avg}} = V_s [2D - 1]$$

$$I_{o_{avg}} = \frac{V_{o_{avg}} - V_a}{R}$$

* Single Phase Inverter:

⇒ $D = 0.5$ $\omega = 2\pi f_c$ $V_{o_{rms}} = V_s$

• Fourier Transform:

* $V_o(t) = \frac{4}{\pi} V_s \sum_{n=odd} \frac{1}{n} \sin(n\omega t)$ ⇒ @ fund. freq. (n=1): $V_{o_{rms,1}} = 0.9 V_s$

* $i_o(t) = \frac{4}{\pi} \sum_{n=odd} \frac{V_s}{n Z_n} \sin(n\omega t - \phi_n)$ ⇒ @ fund. freq. (n=1): $I_{o_{rms,1}} = \frac{0.9 V_s}{|Z_1|}$

↳ $Z_n = \sqrt{R^2 + (n\omega L)^2}$
 $\phi_n = \tan^{-1} \left[\frac{n\omega L}{R} \right]$

* for $i_o(t)$:
 $i_o(t) = \frac{V_s}{R} - \left[\frac{V_s}{R} - I_{min} \right] e^{-t/\tau}$ for $t \leq T/2$
 $i_o(t) = -\frac{V_s}{R} + \left[\frac{V_s}{R} + I_{max} \right] e^{-(t-T/2)/\tau}$ for $t \geq T/2$

* Power:

$P_1 = I_{o_{rms,1}} * V_{o_{rms,1}}$ • MAX & MIN: $I_{max} = -I_{min} = \frac{V_s}{R} \left[\frac{1 - e^{-T/2\tau}}{1 + e^{-T/2\tau}} \right]$

* Single Phase Inverter with Capacitors on the first leg:

$V_{o_{rms}} = V_s/2$, $I_{max} = -I_{min} = \frac{V_s/2}{R} \left[\frac{1 - e^{-T/2\tau}}{1 + e^{-T/2\tau}} \right]$

* for $i_o(t)$:

$i_o(t) = \frac{V_s/2}{R} - \left[\frac{V_s/2}{R} - I_{min} \right] e^{-t/\tau}$ for $t \leq T/2$
 $i_o(t) = -\frac{V_s/2}{R} + \left[\frac{V_s/2}{R} + I_{max} \right] e^{-(t-T/2)/\tau}$ for $t \geq T/2$

Three Phase Inverter:

S_1, S_3, S_5
 S_4, S_6, S_2

case(1): S_1, S_6, S_5 .

case(2): S_1, S_6, S_2 .

case(3): S_1, S_3, S_2 .

case(4): S_4, S_3, S_2 .

case(5): S_4, S_3, S_5 .

case(6): S_4, S_6, S_5 .

Line Voltages:

case(1): $V_{ab} = V_s$
 $V_{bc} = -V_s$
 $V_{ca} = 0$

case(2): $V_{ab} = V_s$
 $V_{bc} = 0$
 $V_{ca} = -V_s$

case(3): $V_{ab} = 0$
 $V_{bc} = V_s$
 $V_{ca} = -V_s$

case(4): $V_{ab} = -V_s$
 $V_{bc} = V_s$
 $V_{ca} = 0$

case(5): $V_{ab} = -V_s$
 $V_{bc} = 0$
 $V_{ca} = V_s$

case(6): $V_{ab} = 0$
 $V_{bc} = -V_s$
 $V_{ca} = V_s$

Phase to Neutral Voltages:

case(1): $V_{an} = V_{cn} = \frac{V_s}{3}$
 $V_{bn} = -\frac{2V_s}{3}$

case(2): $V_{an} = \frac{2V_s}{3}$
 $V_{bn} = V_{cn} = -\frac{V_s}{3}$

The same for other cases. (prove it).

Fourier Transform:

$V_{an} = \frac{2V_s}{\pi} \left[\sin \omega t + \frac{1}{3} \sin 3\omega t + \frac{1}{5} \sin 5\omega t + \dots \right]$

$V_{bn} = \frac{2V_s}{\pi} \left[\sin(\omega t - 120) + \frac{1}{3} \sin 3(\omega t - 120) + \dots \right]$

$V_{cn} = \frac{2V_s}{\pi} \left[\sin(\omega t + 120) + \frac{1}{3} \sin 3(\omega t + 120) + \dots \right]$

$V_{ab} = \sqrt{3} \frac{2V_s}{\pi} \left[\sin(\omega t + 30) - \frac{1}{5} \sin 5(\omega t + 30) + \dots \right]$

$V_{bc} = \sqrt{3} \frac{2V_s}{\pi} \left[\sin(\omega t - 90) - \frac{1}{5} \sin 5(\omega t - 90) + \dots \right]$

$V_{ca} = \sqrt{3} \frac{2V_s}{\pi} \left[\sin(\omega t + 150) - \frac{1}{5} \sin 5(\omega t + 150) + \dots \right]$

Conduction Period:

cond. Period = $3 * \frac{T}{6}$; depending on # of switches

Without FWM: $V_{ab_{rms}} = \sqrt{\frac{2}{3}} V_s$

With FWM: $V_{ab_{rms}} = \sqrt{\frac{2}{3}} V_s \sqrt{d}$

$d = \frac{3N}{T}$


$x = \frac{dT}{3N}$

$V_{an_{rms}} = 0.47 V_s$

* For -ve Seq.:

Swap: S_1 with S_5
 S_2 with S_4

* Single Phase H.W.R with R-load:

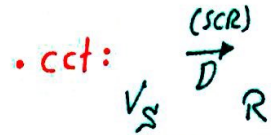

• Average Output Voltage:
 in case $\beta > \pi$: $V_{o\text{avg}} = \frac{V_m}{2\pi} [1 + \cos\alpha]$

in case $\beta < \pi$: $V_{o\text{avg}} = \frac{V_m}{2\pi} [\cos\alpha - \cos\beta]$

• Average Output Current: $I_{o\text{avg}} = \frac{V_{o\text{avg}}}{R}$

• RMS Output Voltage:
 in case $\beta > \pi$: $V_{o\text{rms}} = \frac{V_{s\text{rms}}}{\sqrt{2}} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}}$

in case $\beta < \pi$: $V_{o\text{rms}} = \frac{V_{s\text{rms}}}{\sqrt{2}} \sqrt{\frac{\beta - \alpha}{\pi} - \left(\frac{\sin 2\beta - \sin 2\alpha}{2\pi}\right)}$


• Voltage across the SCR: $V_{s\text{SCR}} = V_s - V_o$

• Average Power:
 in case $\beta > \pi$: $P_{\text{avg}} = \frac{V_m^2}{8\pi R} [2(\pi - \alpha) + \sin 2\alpha]$

in case $\beta < \pi$: $P_{\text{avg}} = \frac{V_m^2}{8\pi R} [2(\beta - \alpha) + \sin 2\alpha - \sin 2\beta]$

⇒ MAX Power @ $\alpha = 0$: $P_{\text{max}} = \frac{V_m^2}{4R}$

• Power Factor:

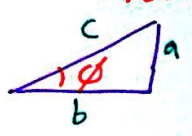

$I_{s1\text{max}} = \frac{V_{s1\text{max}}}{R}$... (1)

$a_1 = \frac{I_{s1\text{max}}}{2\pi} [-1 + \cos 2\alpha]$... (2)

$b_1 = \frac{I_{s1\text{max}}}{4\pi} [2(\pi - \alpha) + \sin 2\alpha]$... (3)

$I_{1\text{rms}} = \frac{C_1}{\sqrt{2}} = \frac{\sqrt{a_1^2 + b_1^2}}{\sqrt{2}}$... (4)


$V_{\text{rms}} = \frac{V_{s\text{rms}}}{\sqrt{2}} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}}$... (5)


$I_{\text{rms}} = \frac{V_{\text{rms}}}{R}$... (6)

$\phi_1 = \tan^{-1}\left(\frac{a_1}{b_1}\right)$... (7)
 $\cos \phi_1 = \frac{b_1}{c_1}$

$\text{Pf} = \frac{I_{1\text{rms}} \cos \phi_1}{I_{\text{rms}}}$... (8)

* Single Phase F.W.R with R-load :


• switch is a diode: 

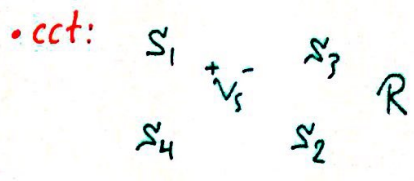

- case ($V_s > 0$): S_1, S_2 (ON). $\Rightarrow V_o = V_s$
- case ($V_s < 0$): S_3, S_4 (ON). $\Rightarrow V_o = -V_s$

$P_{F.H.W} = P_{F.F.W}$, $a_{i.F.W} = 2 a_{i.H.W}$, $b_{i.F.W} = 2 b_{i.H.W}$, $c_{i.F.W} = 2 c_{i.H.W}$, $V_{avg.F.W} = 2 V_{avg.H.W}$, $P_{F.W} = 2 P_{H.W}$, $V_{rms.F.W} = \sqrt{2} V_{rms.H.W}$

* Single Phase H.W.R with RL-load :

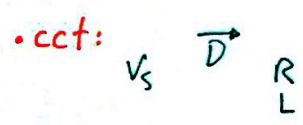


in case $R=0$:

$V_s(t) = V_m \sin \omega t$
 $V_L(t) = V_m \cos(\omega t - \frac{\pi}{2})$
 $I_L(t) = -I_m \cos(\omega t)$
 $P_L(t) = -\frac{V_m I_m}{2} \sin(2\omega t)$
 $P_{Lavg} = \text{Zero}$

• $\alpha \rightarrow \beta$:
 $V_o(t) = V_s [u_{\alpha} - u_{\beta}]$
 $i_o(t) = \frac{V_{max}}{|Z|} [(u_{\alpha} - u_{\beta}) \sin(\omega t - \phi) + u_{\alpha} e^{-\frac{-(\omega t - \alpha)}{\omega \tau}} \sin(\phi - \alpha)]$
 $\tau = L/R$; $Z = \sqrt{R^2 + (\omega L)^2}$; $\phi = \tan^{-1}(\frac{\omega L}{R})$
 $V_{avg} = \frac{V_{smax}}{2\pi} [\cos \alpha - \cos \beta]$; $I_{oavg} = \frac{V_{oavg}}{R}$

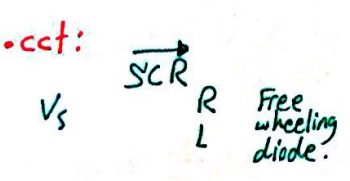* Single Phase H.W.R with RL-load + Free Wheeling Diode :



- Output Voltage: $(\alpha \rightarrow \pi)$: $V_o = V_s$
 $(\pi \rightarrow \beta)$: $V_o = 0$
- Output Current: $(\alpha \rightarrow \pi)$: $i_o(t) = i_s(t)$
 $(\pi \rightarrow \beta)$: $i_o(t) = i_D(t)$

for $i_o(t)$:

$i_o(t) = \begin{cases} i_s(t) = \frac{V_m}{|Z|} [\sin(\omega t - \phi) + e^{-\frac{-(\omega t - \alpha)}{\omega \tau}} \sin(\phi - \alpha)] ; \alpha \rightarrow \pi \\ i_D(t) = i_s(\pi) e^{-\frac{-(\omega t - \alpha)}{\omega \tau}} u(\omega t - \pi) ; \pi \rightarrow \beta \end{cases}$
 $i_{max} = i_s(\pi)$

$\Rightarrow V_o \text{ avg} = \frac{V_m}{2\pi} [1 + \cos \alpha]$, $I_o \text{ avg} = \frac{V_o \text{ avg}}{R}$

* Conduction Period $\equiv \delta = \alpha - \beta$

\Rightarrow finding β : *if No assumptions given assume $< 10\%$ & $i_o(\beta) = 0.05 i_o(\pi)$

\Rightarrow find β from: $0.05 = e^{-\frac{(\beta - \pi)}{\omega \tau}}$; $\omega = 2\pi f$
 $\tau = L/R$

* Three Phase H.W.R with R-load :

$V_{an} = V_m \sin \omega t$
 $V_{bn} = V_m \sin(\omega t - 120^\circ)$
 $V_{cn} = V_m \sin(\omega t + 120^\circ)$

a $\rightarrow S_1$ if $S_1(\text{ON}) \Rightarrow V_{an} > V_{bn}, V_{cn}$
b $\rightarrow S_2$ if $S_2(\text{ON}) \Rightarrow V_{bn} > V_{an}, V_{cn}$
c $\rightarrow S_3$ if $S_3(\text{ON}) \Rightarrow V_{cn} > V_{an}, V_{bn}$

(0 \rightarrow 30 $^\circ$) $\Rightarrow S_3$ ON $V_o = V_{cn}$

(30 $^\circ$ \rightarrow 150 $^\circ$) $\Rightarrow S_1$ ON $V_o = V_{an}$

(150 \rightarrow 270 $^\circ$) $\Rightarrow S_2$ ON $V_o = V_{bn}$

$V_o \text{ avg} (3\phi) = 3 V_o \text{ avg} (1\phi)$

$P_{\text{avg}} (3\phi) = 3 P_{\text{avg}} (1\phi)$

$I_{\text{avg}} (3\phi) = \frac{V_o \text{ avg} (3\phi)}{R}$

$V_o \text{ avg} (3\phi) = \frac{3V_m}{2\pi} [\cos \alpha - \cos \beta]$

$P_{\text{avg}} (3\phi) = \frac{3V_m^2}{8\pi R} [2(\beta - \alpha) + \sin 2\alpha - \sin 2\beta]$

$P_{\text{max}} @ \alpha = 0.$


\hookrightarrow if line voltage is given \Rightarrow convert to phase.

α
 $\alpha + 120$
 $\alpha + 240$

$\beta = \alpha + 120^\circ$

* Three Phase F.W.R : $\alpha = 0$:

. cct :

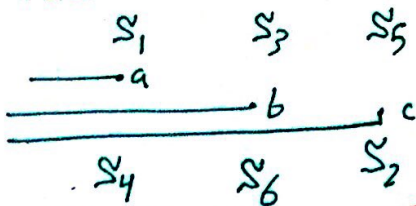

Case	0 \rightarrow 30	30 \rightarrow 60	60 \rightarrow 90	90 \rightarrow 120	120 \rightarrow 150	150 \rightarrow 180
upper switch	C S_5	A S_1	A S_1	A S_1	A S_1	B S_3
lower switch	B S_6	B S_6	B S_6	C S_2	C S_2	C S_2
V_o	V_{CB}	V_{AB}	V_{AB}	V_{AC}	V_{AC}	V_{BC}

$V_o \text{ avg} = \frac{3\sqrt{3} |V_{an}|}{\pi}$

$I_o \text{ avg} = \frac{V_o \text{ avg}}{R}$

$\alpha = 30$: \Rightarrow add 30° for all cases.
 $\Rightarrow V_o$ is the same shifted by 30° .

$\Rightarrow V_{o_{avg}} = \frac{3\sqrt{3}|V_{an}|}{\pi} \cos\alpha \rightarrow$ same for $\alpha = 60$.

$\alpha = 90$: $\Rightarrow V_{o_{avg}} = \frac{3\sqrt{3}|V_{an}|}{\pi} [1 + \cos(\alpha + 60^\circ)]$

Summarize $V_{o_{avg}}$:

$$V_{o_{avg}} = \begin{cases} \frac{3\sqrt{3}|V_{an}|}{\pi} \cos\alpha & ; 0 \leq \alpha < 90^\circ \\ \frac{3\sqrt{3}|V_{an}|}{\pi} [1 + \cos(\alpha + 60^\circ)] & ; 90^\circ \leq \alpha < 120^\circ \\ \text{Zero} & ; \alpha \geq 120^\circ \end{cases}$$

* AC/AC Converter:

cct:



$V_{o_{avg}} = \text{Zero}$

$$V_{o_{rms}} = \frac{V_m}{\sqrt{2\pi}} \sqrt{(\pi - \alpha) + \frac{\sin 2\alpha}{2}}$$

