

4marks

1. Answer the following:
(i) What is the difference between latching current and holding current?

Latching current is current required to trigger the thyristor

holding current is the minimum current for the thyristor until it switches off

Latching > Holding

- (ii) Give 2 advantages of GTO over SCR

① No Electromagnetic harmonics

② higher voltage capabilities

- (iii) Give 2 disadvantages of GTO compared to SCR

① higher overshoot current X

② higher $\frac{di}{dt}$ X

1.5


- (iv) Give 2 advantages of GTO over power transistor

① higher $\frac{dV(t)}{dt}$

② It needs more width of pulse X to turn on.

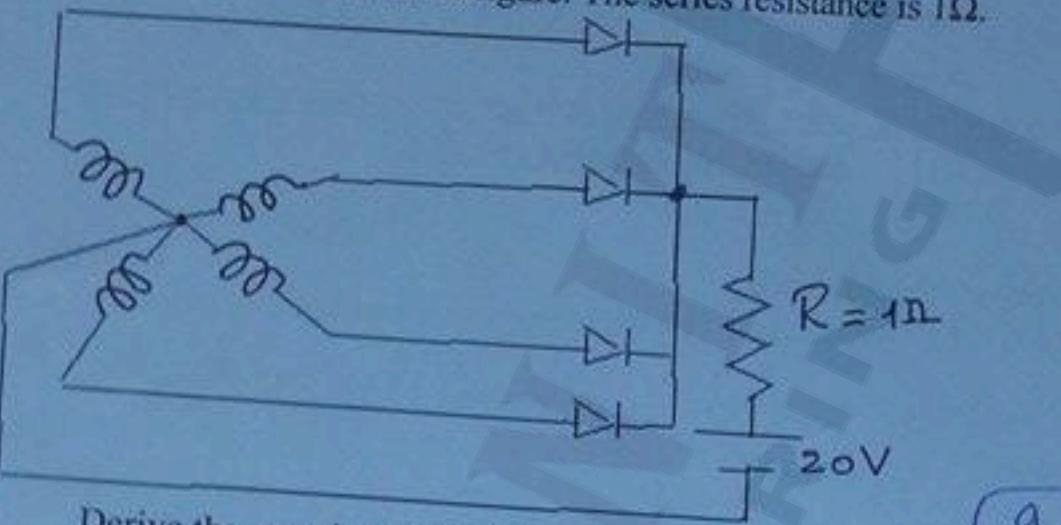2. ABET Problem for evaluating Students Outcome E:

It is required to supply a 100W to the 20V battery using a 4-phase star connected transformer secondary winding as shown in the figure. The series resistance is 1Ω . 10marks



6.5

- (i) Derive the equation for the dc and the rms output voltage.

$$V_{dc} = \frac{2}{2\pi} \int_0^{\frac{\pi}{4}} V_m \cos(\omega t) d\omega t = \frac{4}{\pi} \frac{4}{\pi} \int_0^{\frac{\pi}{4}} V_m \cos(\omega t) d\omega t$$

$$= \frac{4V_m}{\pi} \left[\sin(\omega t) \right]_0^{\frac{\pi}{4}} = \frac{4V_m}{\pi} \frac{\sqrt{2}}{2} = \left(\frac{2\sqrt{2}V_m}{\pi} = V_{dc} \right)$$

$$V_{rms} = \sqrt{\frac{1}{\frac{\pi}{4}} \int_0^{\frac{\pi}{4}} V_m^2 \cos^2(\omega t) d\omega t} = V_m \sqrt{\frac{4}{\pi} \int_0^{\frac{\pi}{4}} \cos^2(\omega t) d\omega t}$$

$$V_{rms} = V_m \sqrt{\frac{4}{\pi} \int_0^{\frac{\pi}{4}} \left[\frac{1}{2} + \frac{1}{2} \cos(2\omega t) \right] d\omega t} = V_m \sqrt{\frac{4}{\pi} \left(\frac{\pi}{8} + \frac{1}{4} \sin\left(\frac{\pi}{2}\right) \right)}$$

Find:

- (ii) The maximum supply voltage

$$V_{dc} = \frac{20 + \left(\frac{100}{20} \times 1 \right)}{\sqrt{battery}} \rightarrow I_{oR} \Rightarrow V_{dc} = 25\sqrt{ } \quad \boxed{V_{dc} = 25\sqrt{ }}$$

$$\therefore \frac{2\sqrt{2}V_m}{\pi} = V_{dc} \Rightarrow \frac{2\sqrt{2}V_m}{\pi} = 25 \Rightarrow \boxed{V_m = 27.768V}$$

- (iii) The rms value of the output voltage

$$\therefore V_{rms} = V_m \sqrt{\frac{4}{\pi} \left(\frac{\pi}{8} + \frac{1}{4} \right)} \Rightarrow \boxed{V_{rms} = 25.119V}$$

- (iv) The ac component of the output voltage

$$V_o(wt) = 27.768 \sin(wt)$$

X

ANSWER

- (v) The ac component and the rms of the current in the resistor

$$\text{day component } R \quad I_{r.m.s} = \frac{25.119}{R} = 25.119 A = \frac{V_{r.m.s}}{R}$$

$$I_o(wt) = \frac{27.768}{\sqrt{2}} \sin(wt)$$

X

- (vi) The dc value of each diode current

$$I_{dc} = \frac{100}{20} = 5 \Rightarrow I_{dc \text{ diode}} = \frac{5}{4} = \frac{5}{4} = 1.25 A$$

✓

- (vii) The transformer utilization factor



$$TUF = \frac{P_{dc}}{4V_s I_s} = \frac{(5)(25)}{(4)(25.119) \left(\frac{25.119}{\sqrt{2}}\right)} = 9.91\% \quad !$$

X

- (viii) The peak inverse voltage for each diode


$$PIV = \sqrt{q} V_m = \sqrt{4} \times 27.768 \quad \checkmark$$

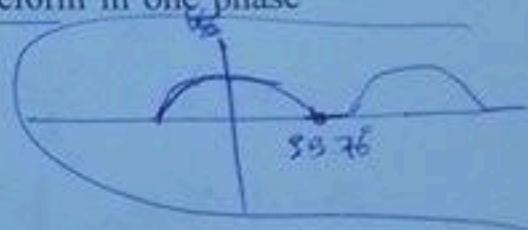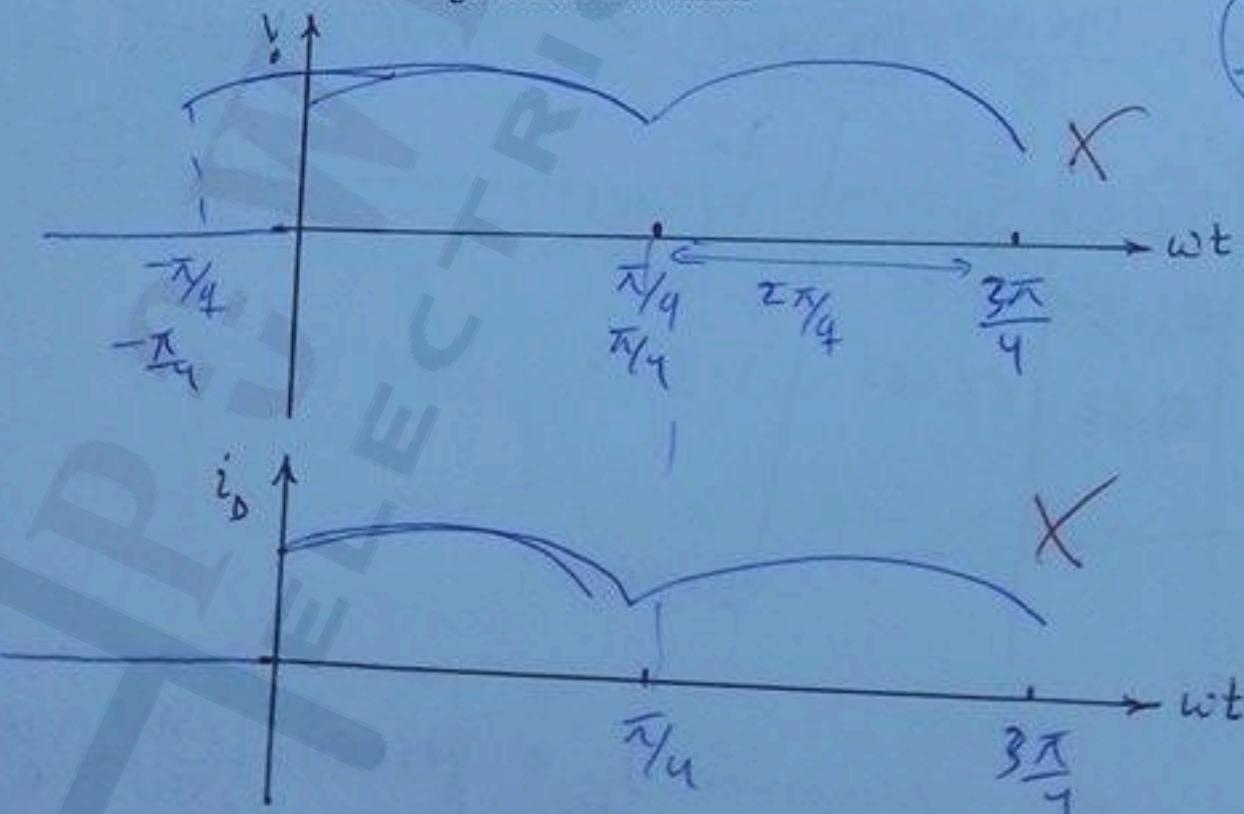- (ix) Sketch the output voltage waveform and the current waveform in one phase showing the time axis limits



(i) Draw the circuit diagram

10marks

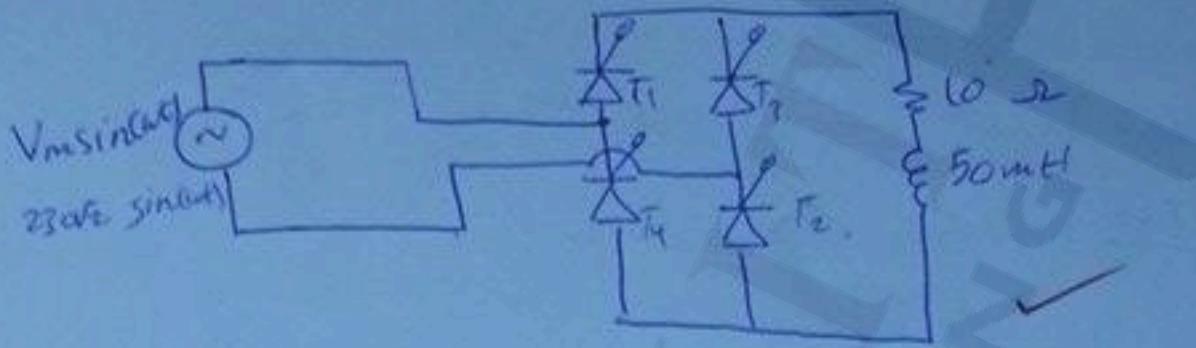

8.5

(ii) Is the output current continuous or discontinuous? Why?

$$\theta = \tan^{-1} \left(\frac{\omega L}{R} \right) = \tan^{-1} \left(\frac{2\pi \times 50 \times 50 \times 10^{-3}}{10} \right) = 57.52^\circ$$

$$\alpha = 45^\circ$$

$\alpha < \theta \Rightarrow$ ~~discontinuous~~ continuous

Continuous because α is smaller than θ

(iii) Find the rms value of the output current.

$$V_o = \frac{2V_m}{\pi} \cos(\alpha) \Rightarrow V_o = \frac{2(230)(\sqrt{2})}{\pi} \cos(45^\circ) = 146.423V$$

$$\Rightarrow I_o = \frac{V_o}{R} = \frac{146.423}{10} = 14.6423A$$

Finding I_o from graph

n	Vn/Vm	Vn	Zf	In
0	-	146.423	10	14.6423
2	0.65	211.425	32.97	6.413
4	0.25	81.32	63.623	1.278
6	-	-	-	negligible

$$Z_f = \sqrt{10^2 + (2(2\pi)50 \times 10)^2}$$

$$\therefore I_{rms} = \sqrt{(14.6423)^2 + (6.413)^2} \\ = 15.355A$$

- (iv) Find the rms value of the current in each thyristor

$$I_{\text{rms, thyristor}} = \frac{\bar{I}_{\text{rms}}}{\sqrt{2}} = 10.857 \text{ A}$$

15.355
 $\sqrt{2}$

- (v) Find the rms value of the supply current

$$\bar{I}_{\text{rms, Supply}} = \bar{I}_{\text{rms, load}} = 15.355 \text{ A}$$

- (vi) Find the average current in each thyristor

$$\bar{I}_{\text{dc, thyristor}} = \frac{\bar{I}_{\text{dc}}}{2} = \frac{14.6432}{2} = 7.3216 \text{ A}$$


- (vii) Find the efficiency of the converter

$$\eta = \frac{P_{\text{ac}}}{P_{\text{dc}}} = \frac{(14.6432)^2 (10)}{(15.355)^2 (230)} = 42.93\% \times$$


- (viii) Find the power factor

$$\text{P.f.} = \frac{P_{\text{ac}}}{V_s I_s} = \frac{(15.355)^2 (10)}{(230)(15.355)} = 0.472$$

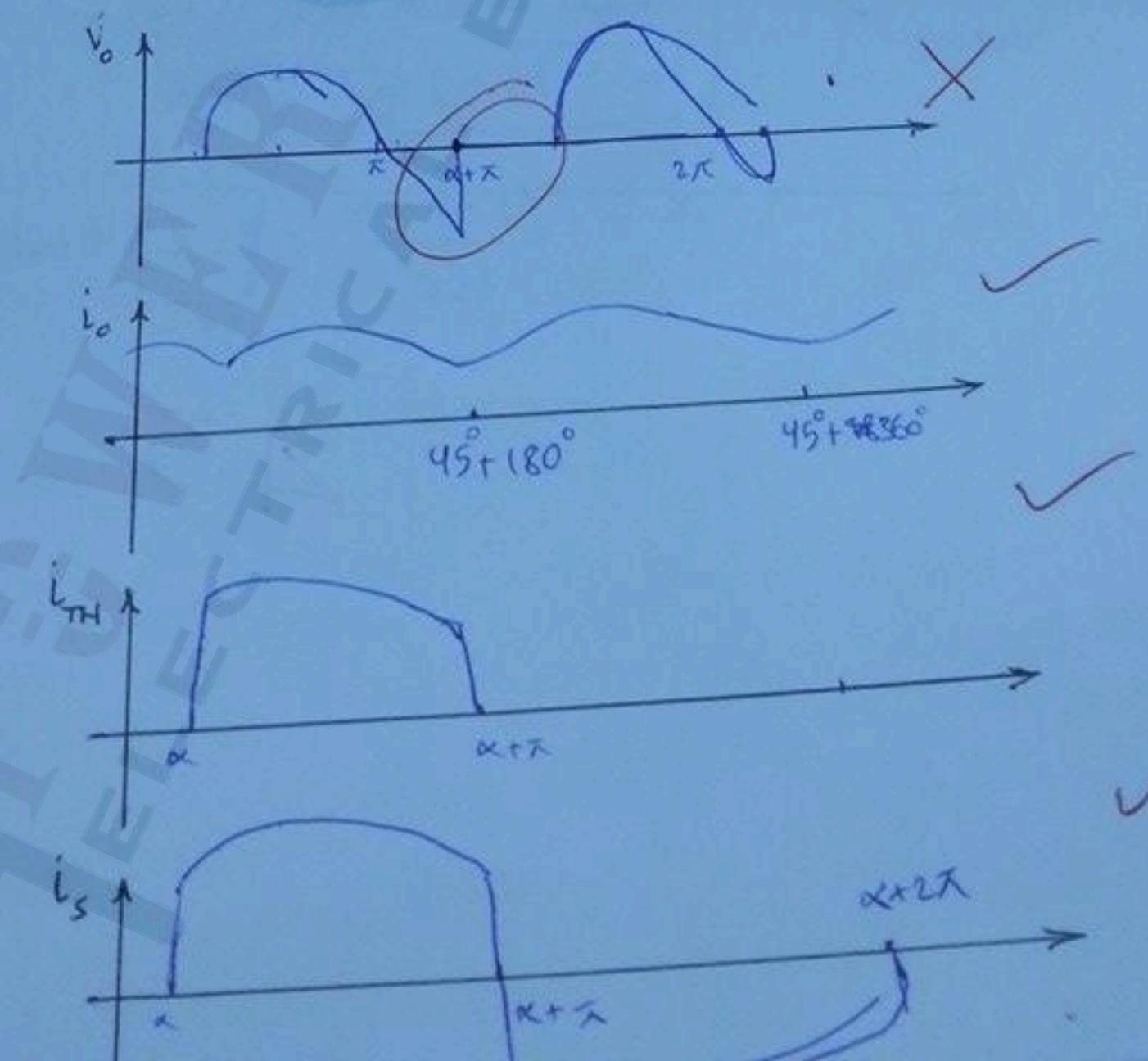- (ix) Sketch the waveforms of the output voltage, the output current, the current in one of the thyristors and the supply current.



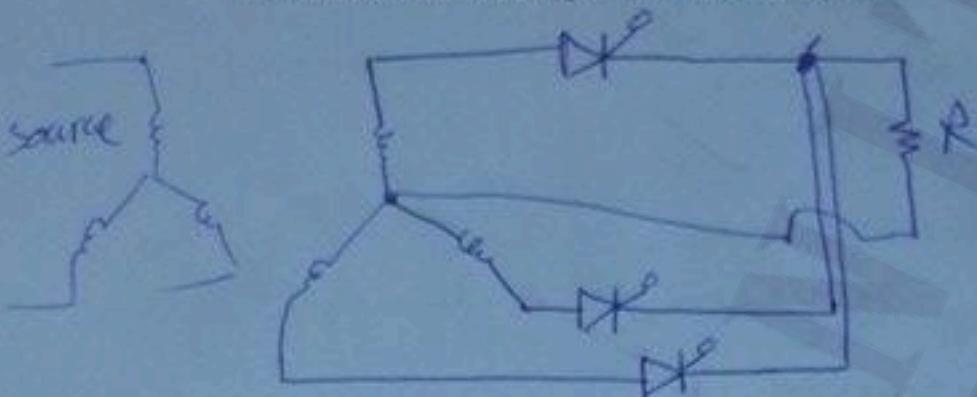4. A line to line voltage of 400V, 3-phase, half wave converter supplying an average voltage of 200V dc to a pure resistive load. 6marks
 (i) Sketch the circuit diagram for this converter.



- (ii) Find the firing angle of each thyristor. (Hint: check whether the current is continuous or discontinuous)

assume $\alpha < 30^\circ$

$$V_0 = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{\pi/6} V_m \sin(\omega t) dt = \frac{3\sqrt{3} V_m}{2\pi} \cos(\alpha)$$

$$\therefore 200 = \frac{3\sqrt{3} \left(\frac{400}{\sqrt{3}} \sqrt{2} \right)}{2\pi} \cos(\alpha)$$

$$\cos(\alpha) = 0.7404 \Rightarrow \alpha = 42.227^\circ \text{ Wrong}$$

α is continuous

$$V_0 = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{\pi/6} V_m \sin(\omega t) dt = \frac{3V_m}{2\pi} [1 + \cos(\pi/6 + \alpha)]$$

$$200 = \frac{3 \left(\frac{400}{\sqrt{3}} \sqrt{2} \right)}{2\pi} [1 + \cos(\pi/6 + \alpha)]$$

$$1.283 = 1 + \cos(\pi/6 + \alpha) \quad \checkmark$$

$$\alpha = 73.59^\circ \quad \times$$

$$\alpha = \frac{73.59 \times \pi}{180^\circ} = 1.284 \text{ radian}$$

4.5

(iii) Find the rms value of the output voltage

$$V_{rms} = \sqrt{\frac{5}{2\pi}} \int_{R/6\pi}^{\pi} V_m^2 \cos^2(\omega t) dt = \sqrt{3} V_m \left[\frac{5}{24} - \frac{\alpha}{4\pi} + \frac{1}{8\pi} \sin(2\alpha) \right]^{1/2}$$
$$= 167.765 \text{ V } X$$

(v) Find the rms value of the current in each thyristor

$$\sum_{\text{thyristor}} V_{rms} = \frac{I_{rms}}{\sqrt{3}} = \frac{V_{rms}}{R\sqrt{3}} = \frac{167.765}{R\sqrt{3}}$$
$$= \frac{167.765}{10\sqrt{3}} = 9.686 \text{ A } X$$

(vi) Sketch the waveform of the output voltage and current in one thyristor.

