
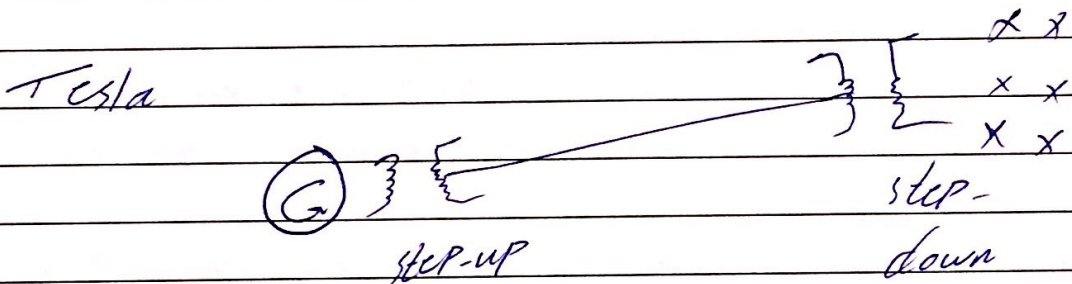


Power Electronics

Power Electronics: is about how to convert & monitor electric Power from one form to another


⇒ War of currents

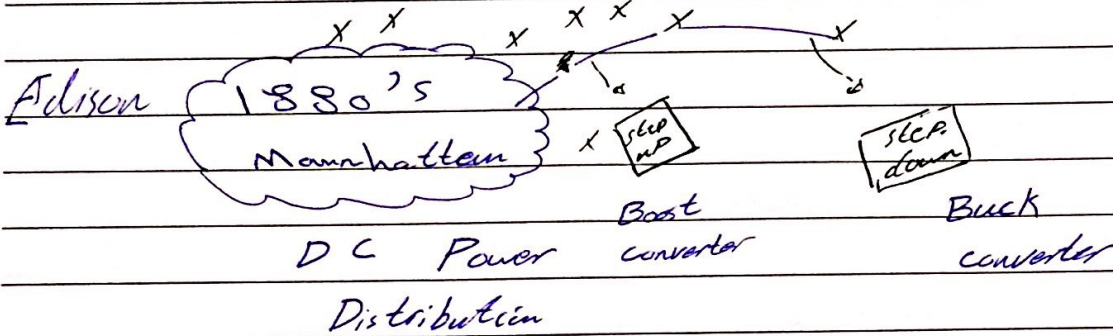

Power conversion types:


① DC/DC

Conversion: [converter]

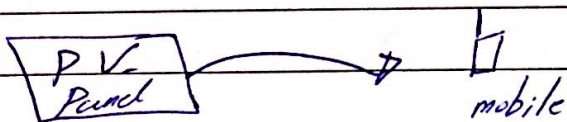

② DC/AC


Inversion [Inverters]

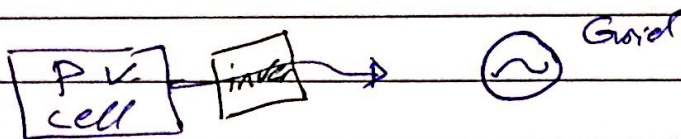

③ AC / DC Rectification [Rectifiers]




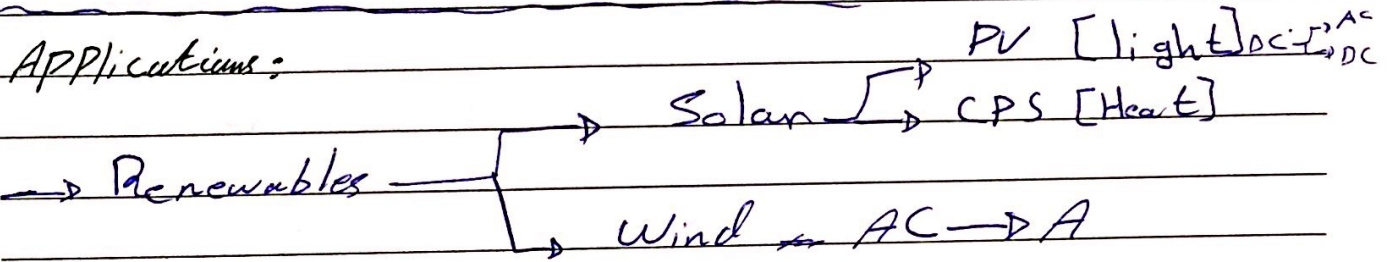④ AC/AC controllers [for low power applications]




Tafiteh \Rightarrow 100 MVA


Madun \Rightarrow 50 MVA

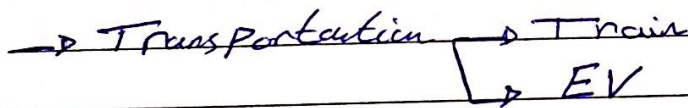

→ Electronic Devices

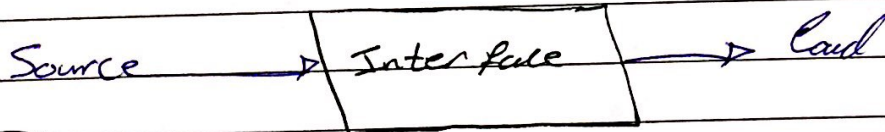

Example: wind Generator

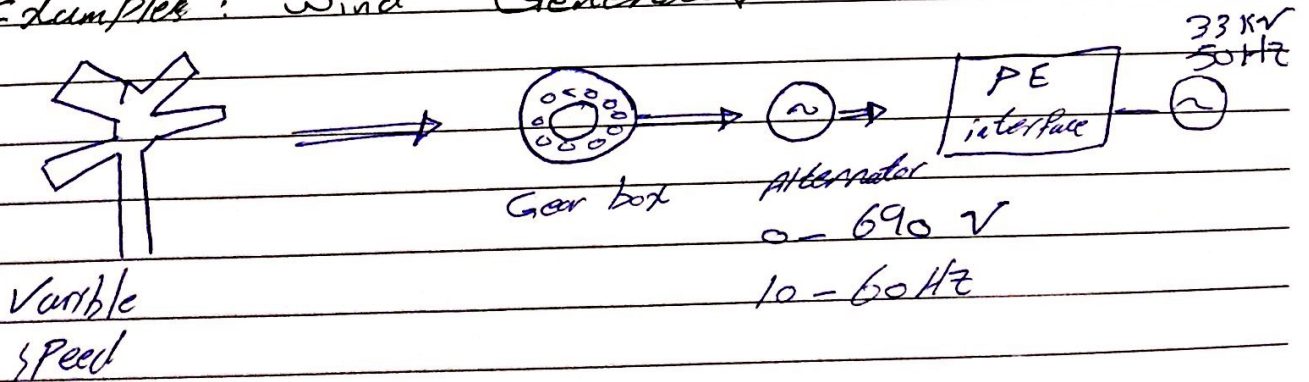

Example: PV- Panels



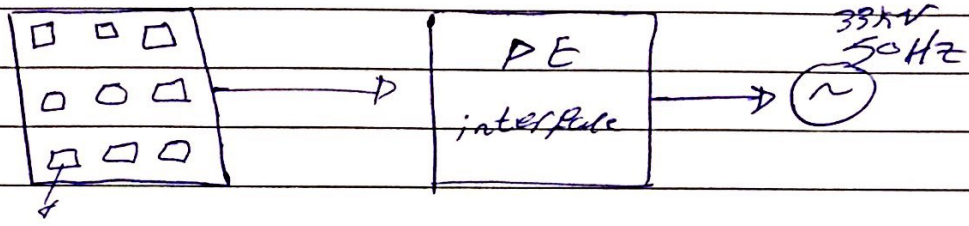
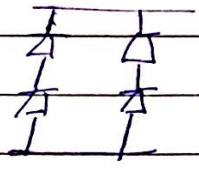


Photo-diode
 DC-voltage
 DC-current




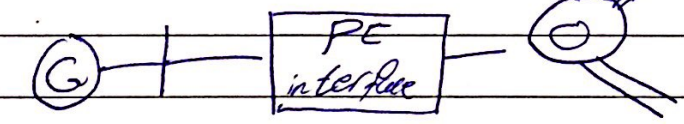


Example: Efficiency improvement


Motors [Drive] :-

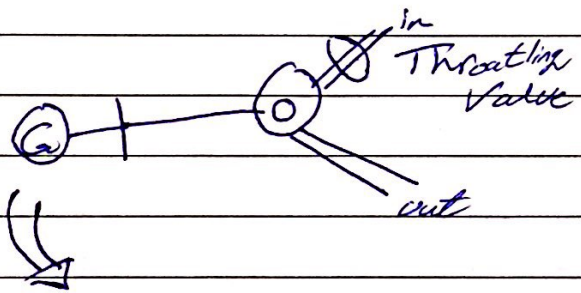


Lighting :-

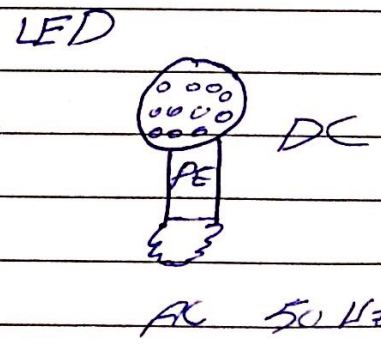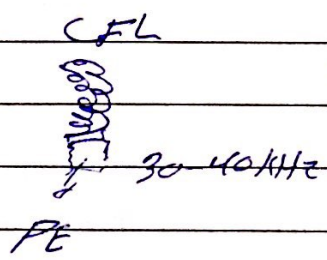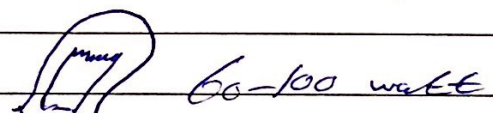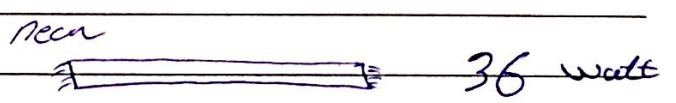

Example: Utility applications

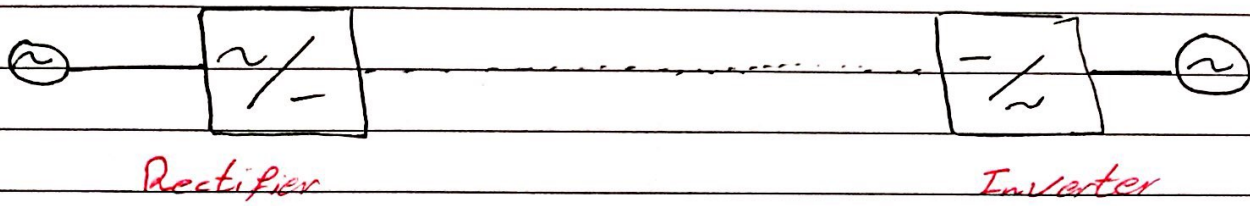


HVDC

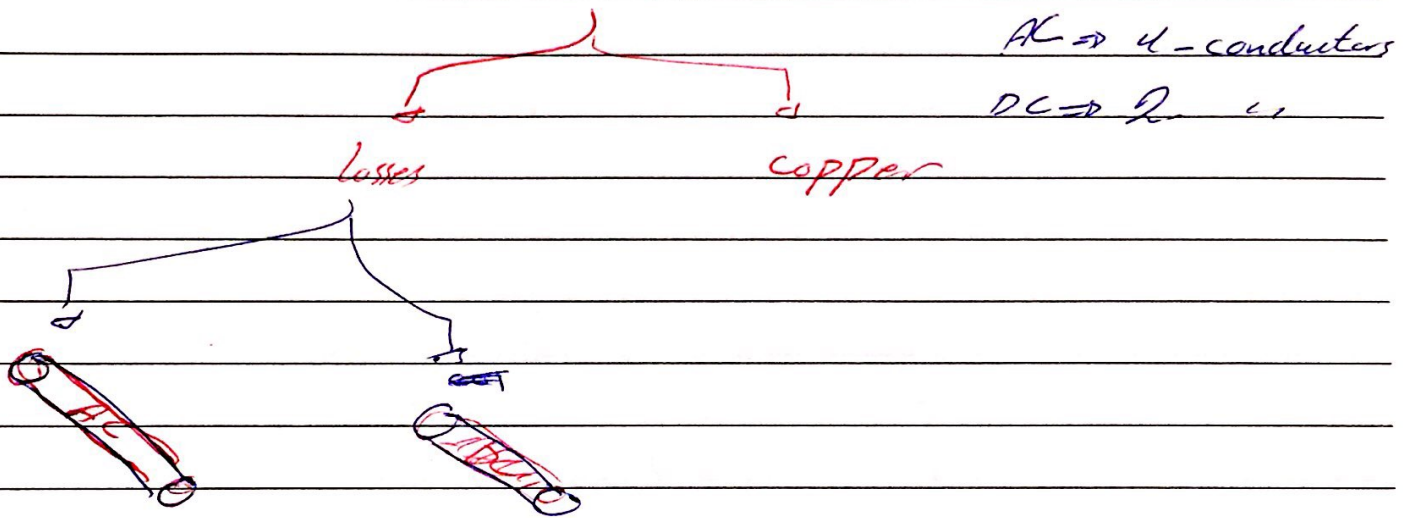

$$R_{AC} = \frac{PL}{A} \Rightarrow R_{AC} > R_{DC}$$

What is the essence of Power Electronics!

\rightarrow Switching

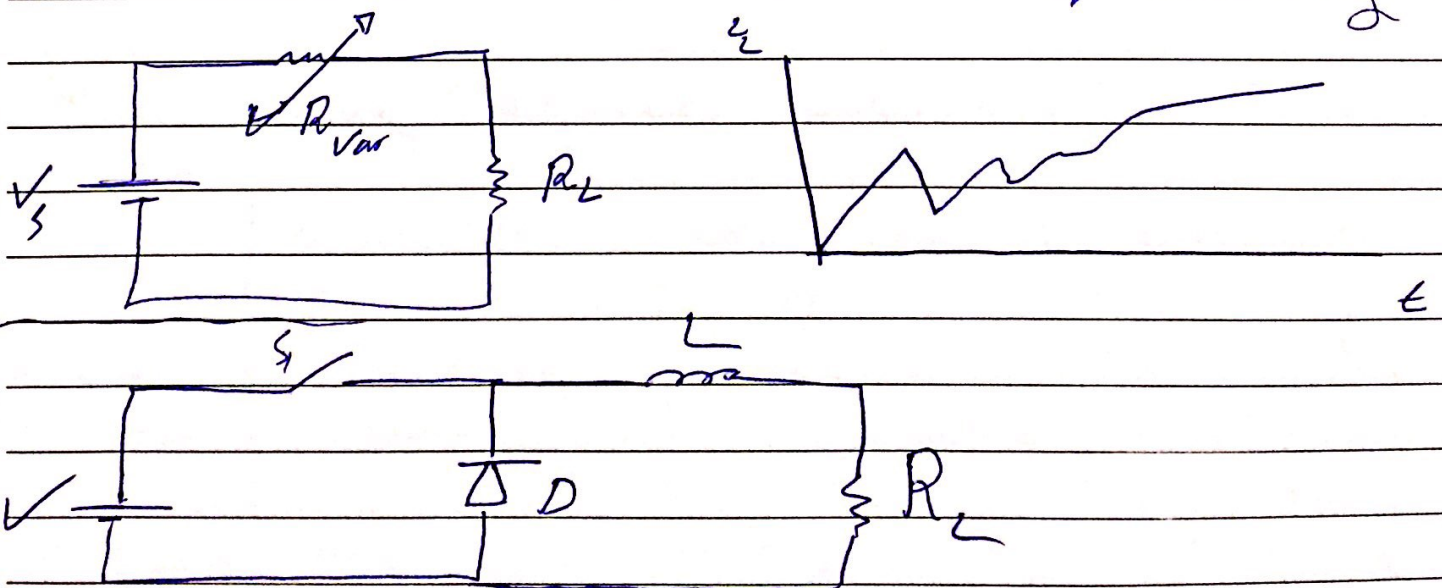

S_1 : off

Power


Zero

0% chmic cut off

S_1 : on


100% of Power

S_1 : on & off

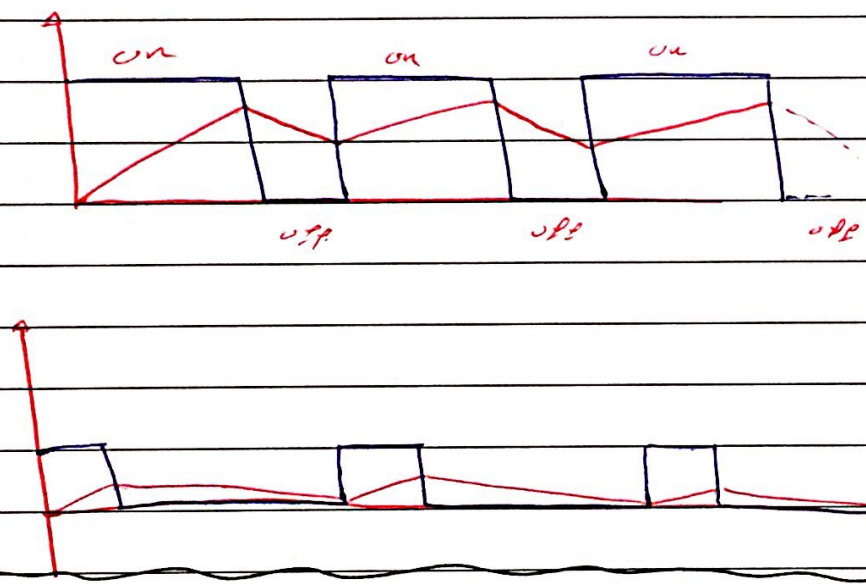


Switching Devices : controllability & Direction



	Uncontrollable	controllable on	controllable
Uni-Directional	Diode 	Thyristor (SCR) 	BJT - K_c MOSFET - E_g IGBT - K_c GTO
Bi-Directional	Diac 	Triac 	Modules Five Apple

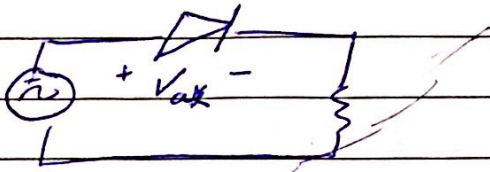


Switching Devices: Frequency & VA Rating

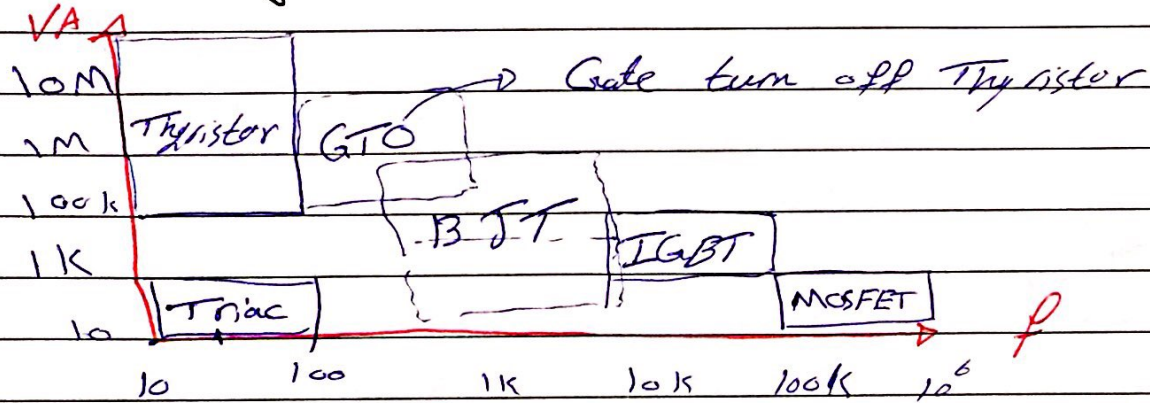


① Principle of AC-DC (Rectifier)

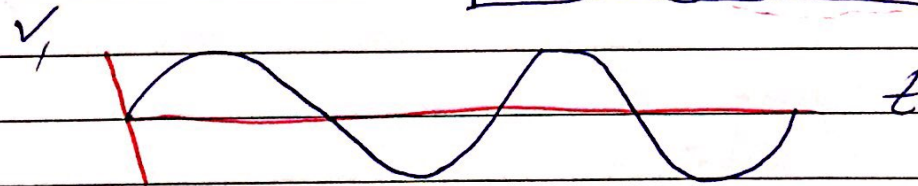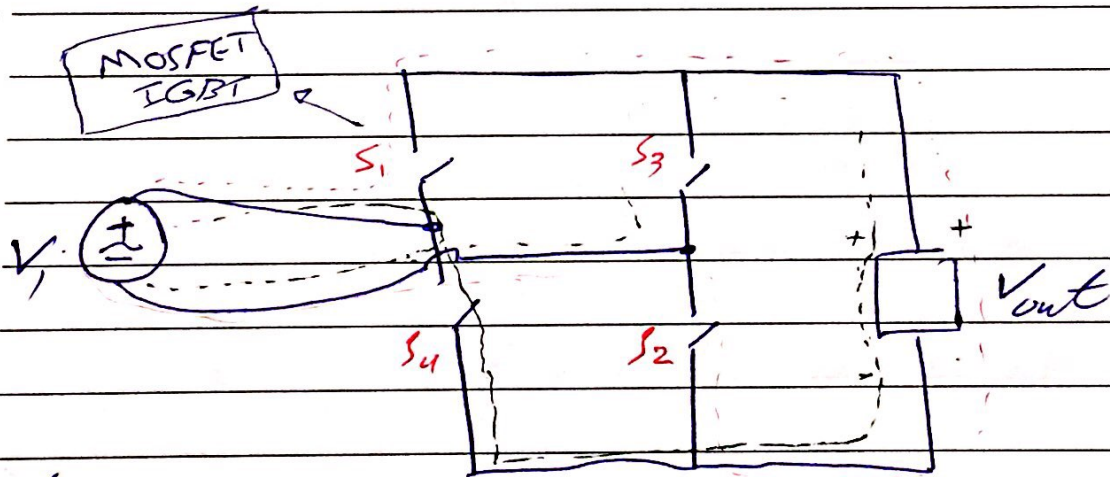


S_1, S_2

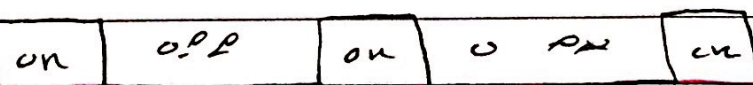

S_2 Set

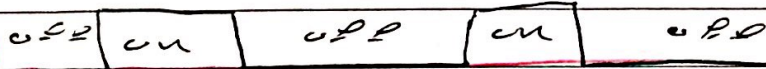


V_{out}

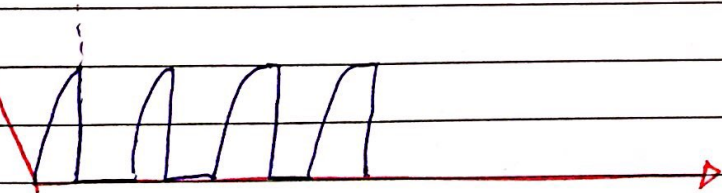

DC + ripple

+ve \Rightarrow DC signal
AVG \leftarrow
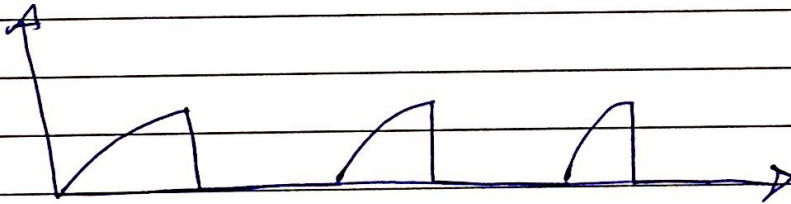
$$v(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} a_n \sin(n\omega t) + \sum_{n=1}^{\infty} b_n \cos(n\omega t)$$




$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt \neq 0 \Rightarrow DC$$

Fourier Series:


a_0
 \equiv
DC

$$c_n = \sqrt{b_n^2 + a_n^2}$$

\equiv
AC





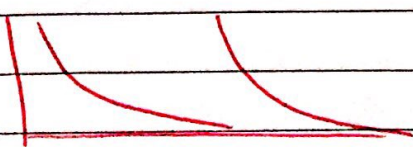


DC with ripple

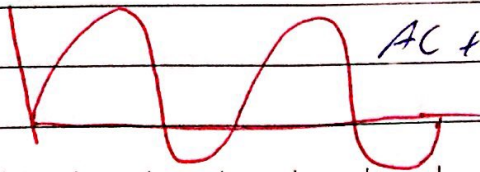


AC + DC offset

AC - DC Rectification

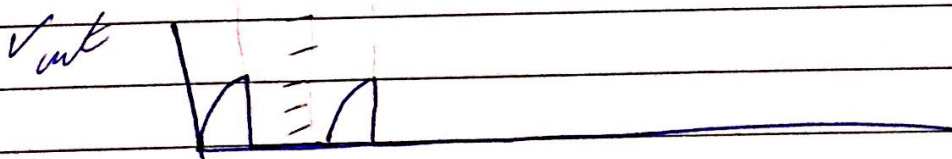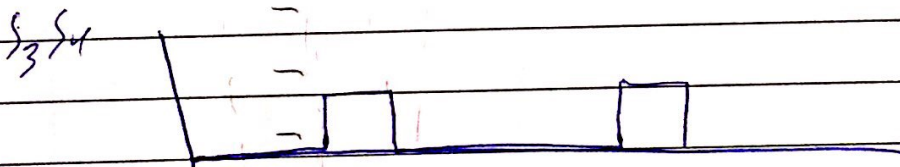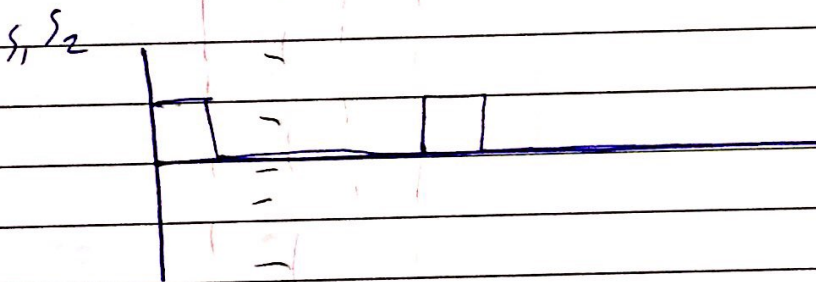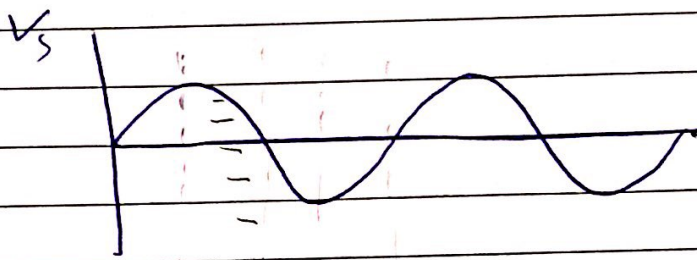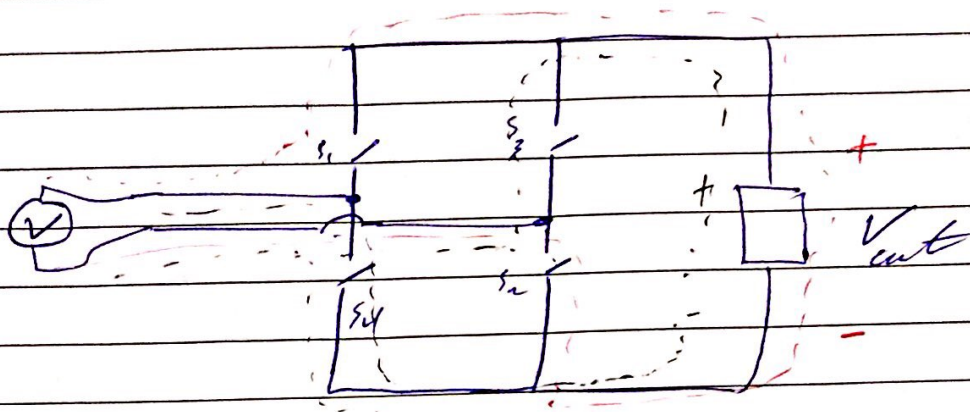


when S_1 & S_4 are on

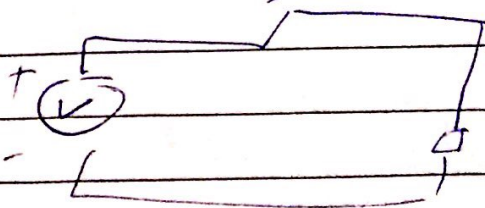

$$V_{Load} = V_s$$

when S_2 & S_3 are on

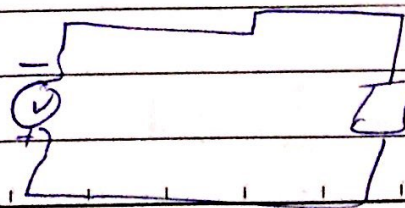

$$V_{Load} = V_s$$

$$V_o = (S_1 - S_3) V_s$$



S_1 : 1 on
 0 off



S_3 : 1 on
 0 off

or S_2 or S_4

S_1	S_3	V_{out}
1	1	///
0	0	0
1	0	V_s
0	1	$-V_s \Rightarrow -(-) = +ve$



DC-AC Inversion

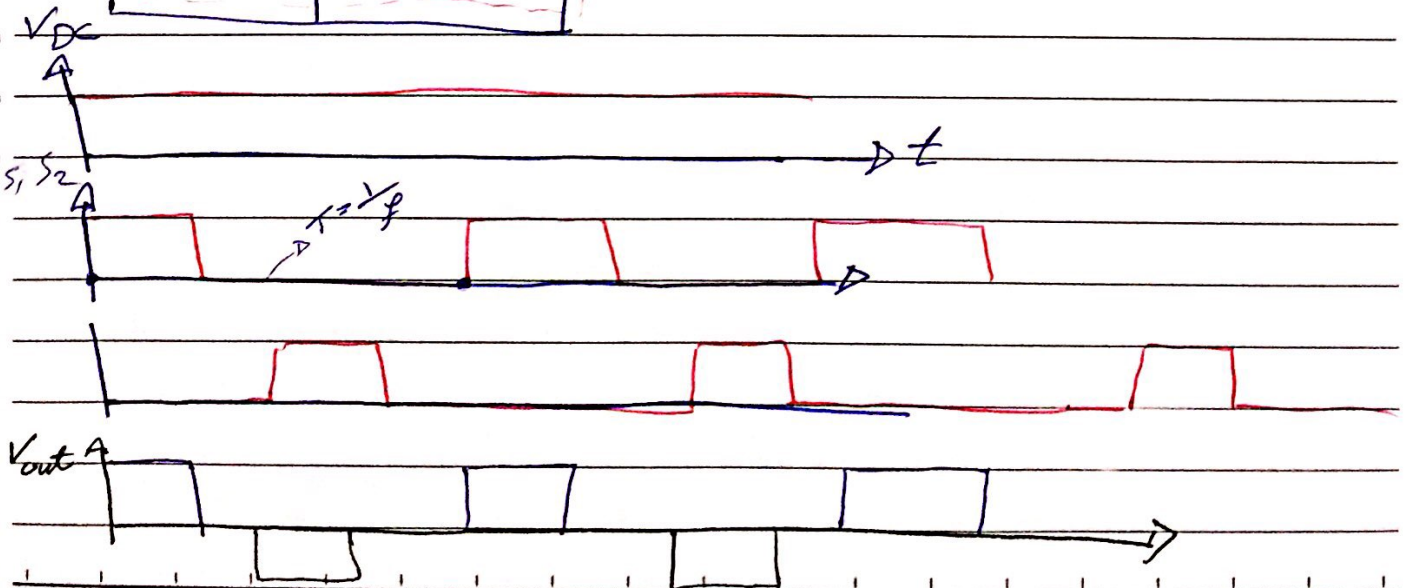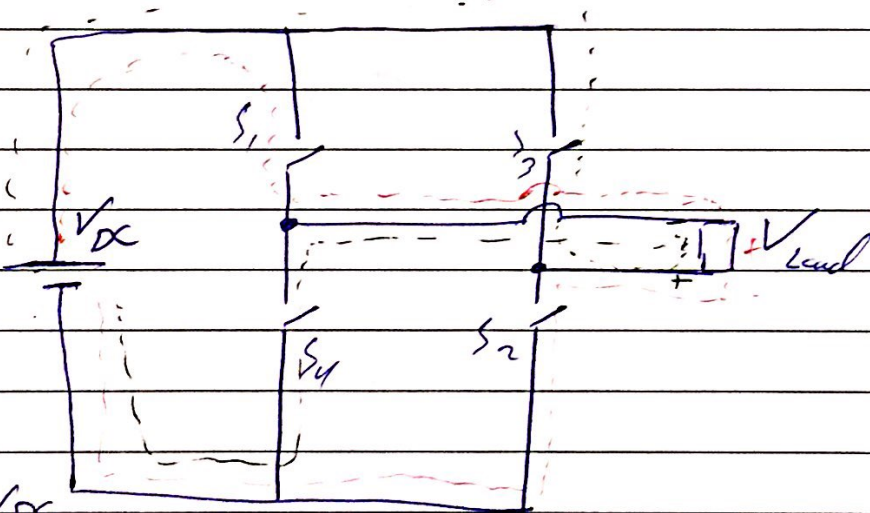



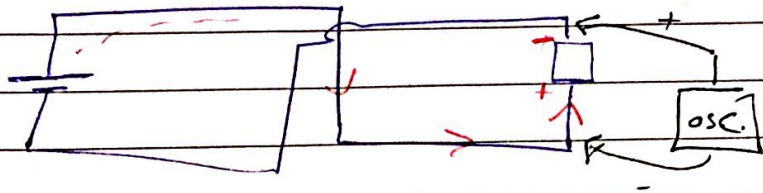
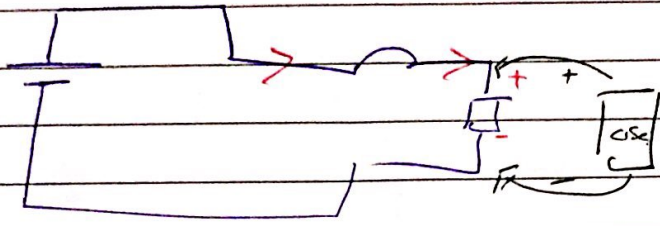



$$V_{AC} = (S_1 - S_3) V_{DC}$$

AC-AC controllers :-

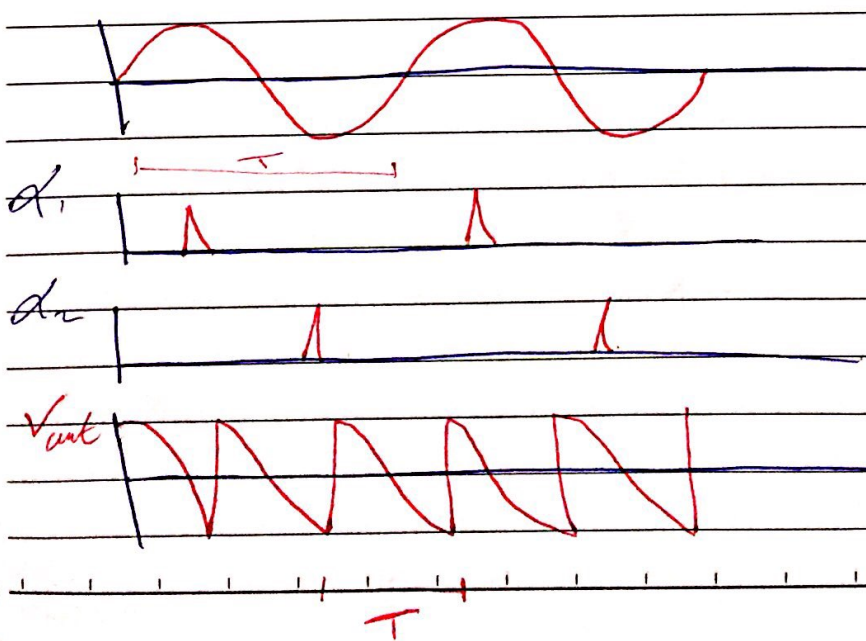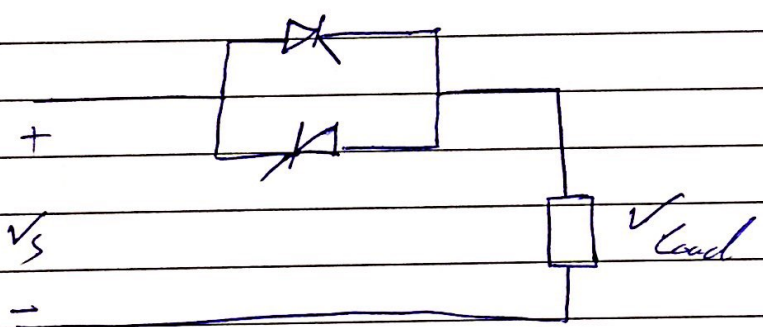


Principle of DC-DC converter.

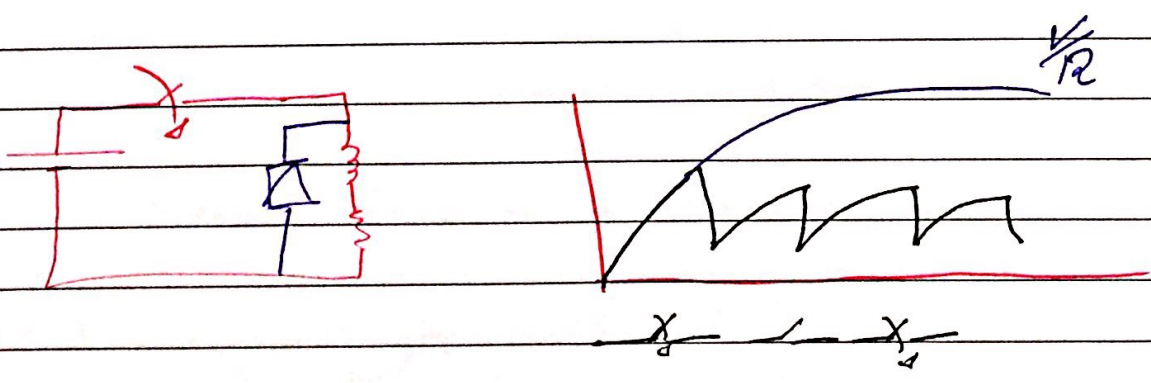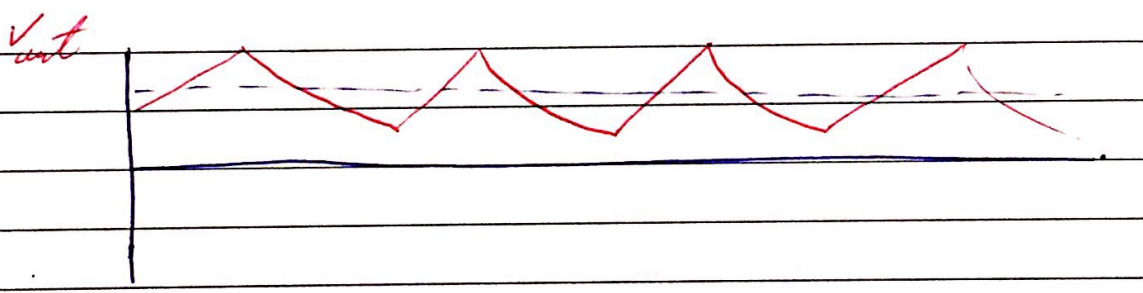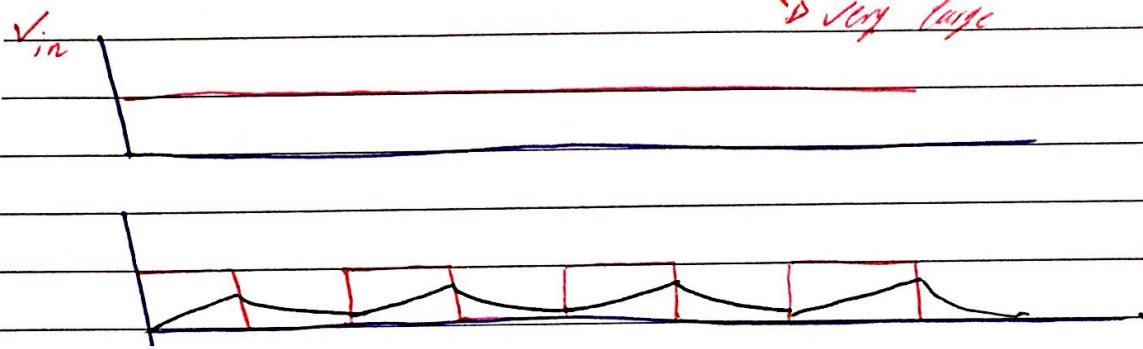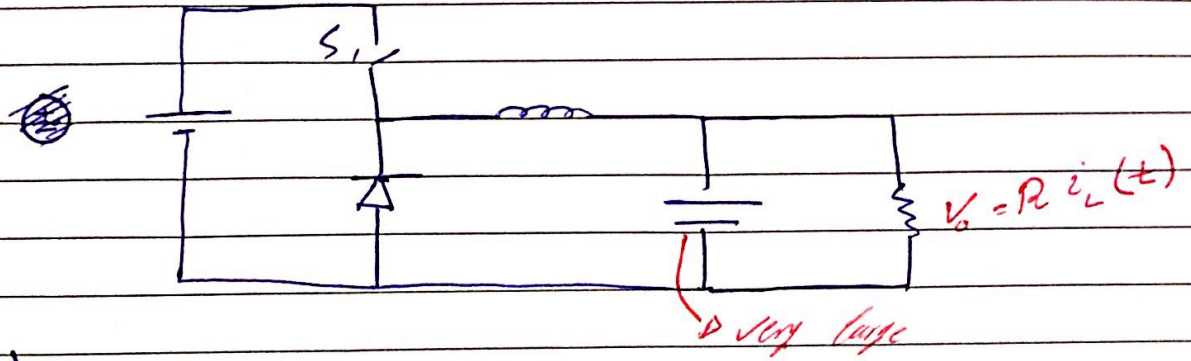

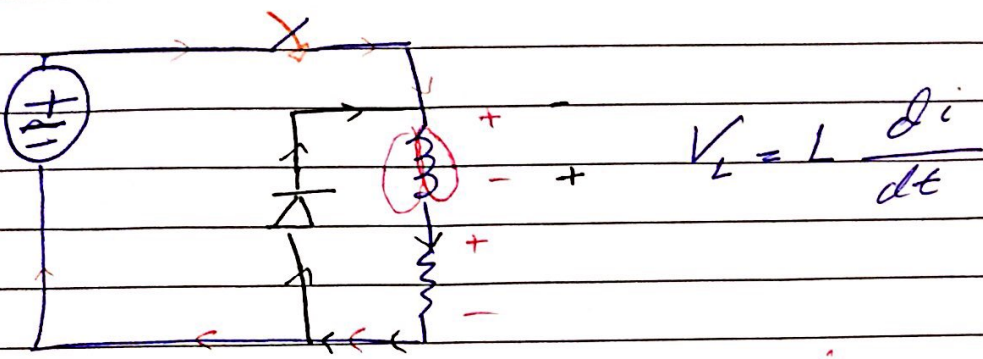


$$i_c = C \frac{dv_c}{dt}$$

Buck DC/DC converter

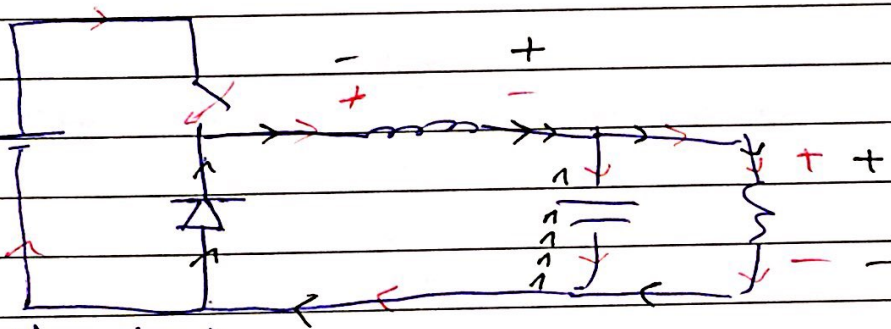



$$i_L(t) \approx i_R(t)$$

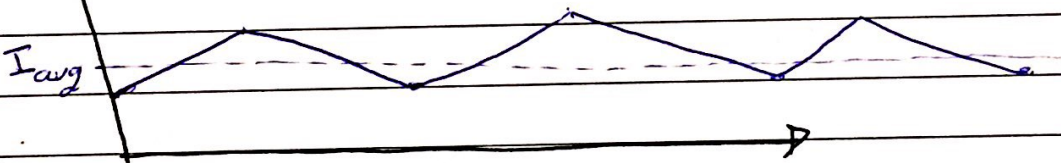

$$V_{out} = R I_{avg} \approx \text{DC Value}$$

PE biggest Problem is harmonics

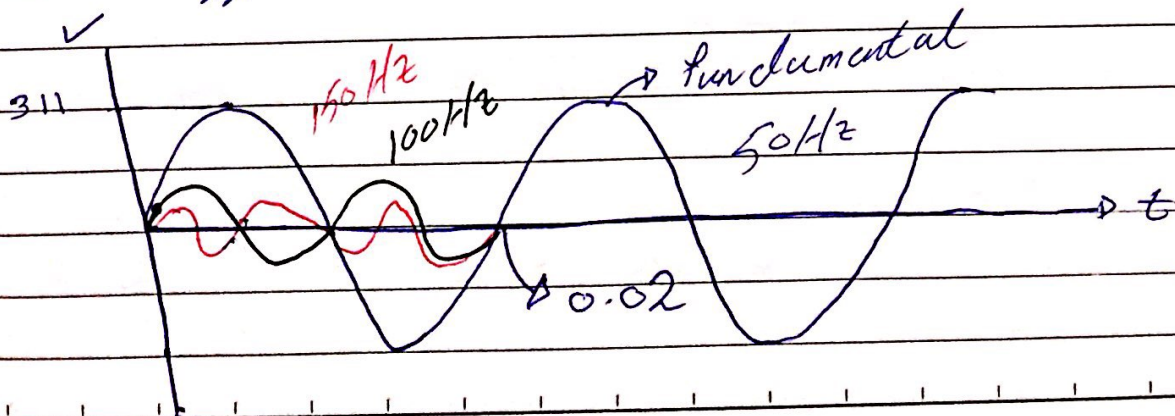


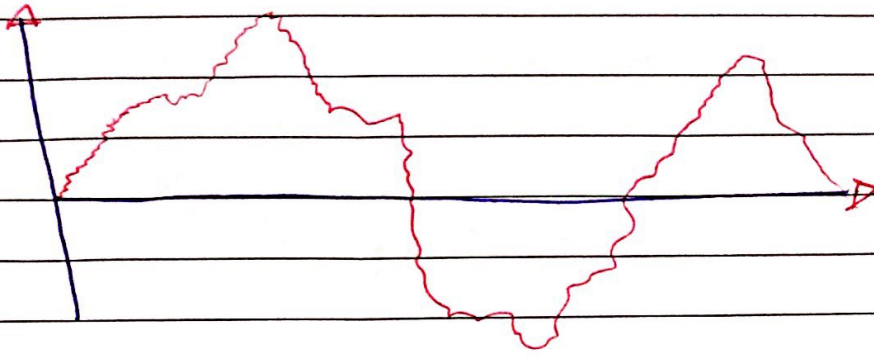

→ We need to characterize the harmonics using the Fourier Series

$$V = -N \frac{d\phi}{dt} = -N \omega \phi_m$$
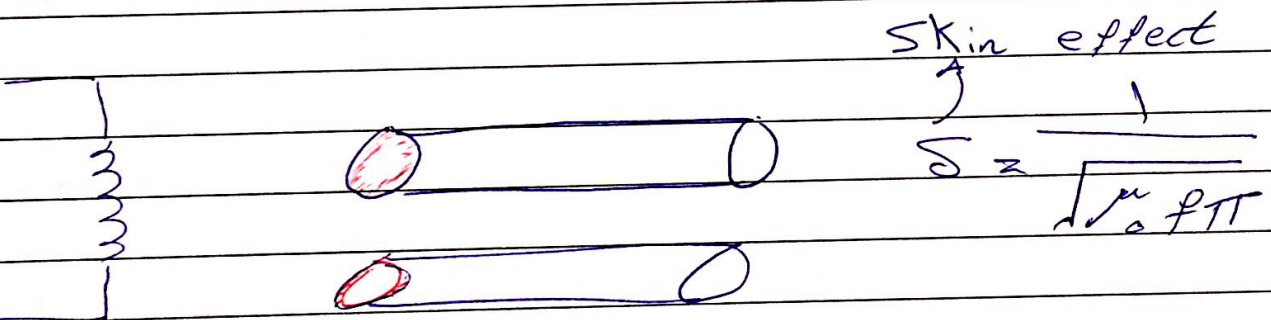
$$V = \sqrt{V_1^2 + V_2^2 + V_3^2 + \dots}$$



$$v(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t)$$

$$= \frac{a_0}{2} + \sum_{n=1}^{\infty} C_n \cos(n\omega t + \phi_n)$$


$$a_0 = \frac{2}{T} \int_0^T v_0(t) dt = \frac{1}{\pi} \int_0^{2\pi} v_0(\omega t) d\omega t$$

$$a_n = \frac{2}{T} \int_0^T V_0(t) \cos n\omega t dt = \frac{1}{\pi} \int_0^{2\pi} V_0(\omega t) \cos n\omega t d\omega t$$

$$b_n = \frac{2}{T} \int_0^T V_0(t) \sin n\omega t dt = \frac{1}{\pi} \int_0^{2\pi} V_0(\omega t) \sin n\omega t d\omega t$$

$$C_n = \sqrt{a_n^2 + b_n^2}, \quad \phi_n = \tan^{-1} \left(\frac{b_n}{a_n} \right)$$

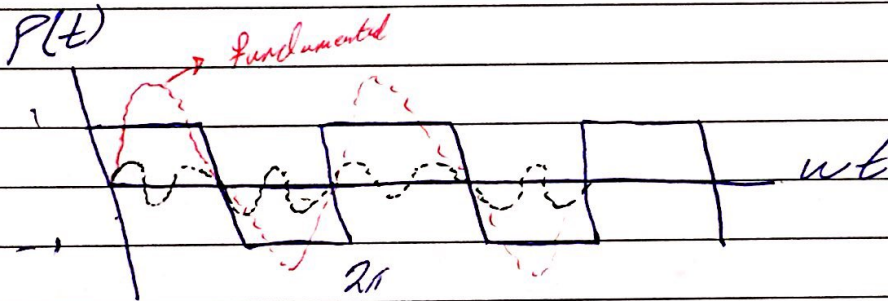Example: Find the first & 3rd harmonics for:



So we find C_1 & C_3

$$a_0 = \frac{2}{2\pi} \int_0^{2\pi} P(t) d\omega t$$

$$= \frac{2}{2\pi} \left[\int_0^{\pi} 1 d\omega t + \int_{\pi}^{2\pi} -1 d\omega t \right] = 0$$

$$a_n = \frac{2}{2\pi} \int_0^{2\pi} P(t) \cos n\omega t d\omega t$$

$$= \frac{1}{\pi} \left[\int_0^{\pi} \cos n\omega t d\omega t + \int_{\pi}^{2\pi} -\cos n\omega t d\omega t \right]$$

$$= 0$$

$$b_n = \frac{1}{\pi} \int_0^{2\pi} f(t) \sin nt \, dt$$

$$= \frac{1}{\pi} \left[\int_0^{\pi} \sin nt \, dt + \int_{\pi}^{2\pi} -\sin nt \, dt \right]$$

$$= \frac{1}{n\pi} \cos nt \Big|_0^{\pi} + \frac{1}{n\pi} \cos nt \Big|_{\pi}^{2\pi}$$

$$= \frac{2}{n\pi} - \frac{2}{n\pi} \cos n\pi$$

$$C_n = b_n$$

$$C_1 = C_n \Big|_{n=1} = b_1 = \frac{4}{\pi}$$


$$C_3 = C_n \Big|_{n=3} = b_3 = \frac{4}{3\pi}$$

$$b_n = \begin{cases} 0, & n \text{ even} \\ \frac{4}{n\pi}, & n \text{ odd} \end{cases}$$

$$v(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} A_n \cos(n\omega t)$$


$$= A_0 + A_1 \cos(\omega t) + A_2 \cos(2\omega t) + A_3 \cos(3\omega t) + \dots$$

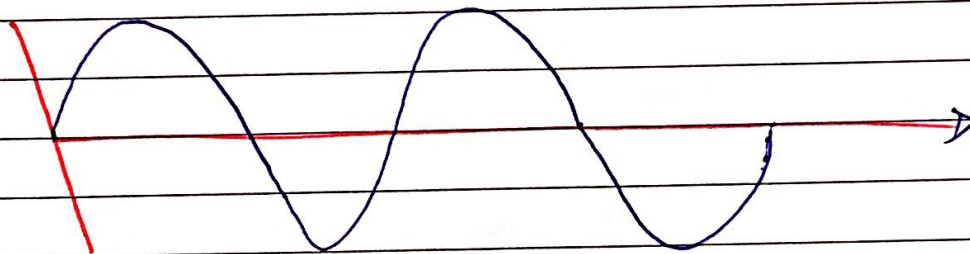Total Harmonic Distortion: (THD) : it is a measure of the closeness in shape between a wave form & its fundamental frequency




$$T.H.D = \frac{\sqrt{\sum_{n=2}^{\infty} (I_n)^2}}{I_1}$$

Ex: Find the THD for the signal :-

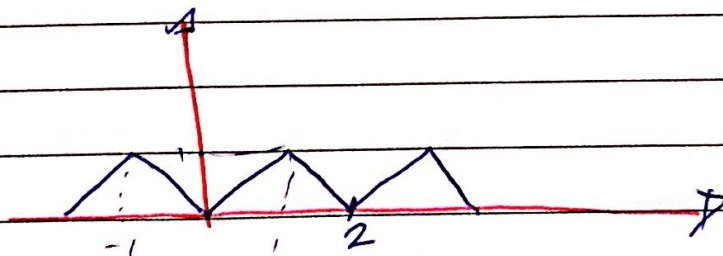

$$T = 2$$

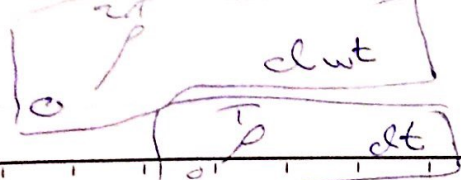

$$\frac{a_0}{2} \stackrel{?!}{=} \frac{1}{2}$$

$$a_n = \frac{2}{T} \int_0^T v(t) \cos(n\omega t) dt$$

$$= \frac{2}{T} \int_0^1 v(t) \cos(n\omega t) dt$$

$$= 2 \int_0^1 t \cos(n\omega t) dt$$

$$v(t) = \begin{cases} t & 0 \leq t \leq 1 \\ 0 & 1 < t \leq 2 \end{cases}$$

$$u = t \quad dv = \cos(n\omega t) dt$$

$$du = dt \quad v = \frac{1}{n\omega} \sin(n\omega t)$$

$$= 2 \left[\frac{t}{n\omega} \sin(n\omega t) \right]_0^1 - \int_0^1 \frac{1}{n\omega} \sin(n\omega t) dt$$

$$\omega = 2\pi f = \frac{2\pi}{T} = \pi$$

$$= \frac{2}{n^2 \omega^2} \cos(n\omega t) \Big|_0^1 = \frac{2}{n^2} (\cos(n\pi) - 1)$$

$$= \begin{cases} 0, & n \text{ even} \\ \frac{-4}{n^2} & n \text{ odd} \end{cases}$$

$$a_n = \frac{1}{n\pi}, \quad b_n = \frac{1}{n^2}$$

Find 3rd harmonic; $C_n = \sqrt{a_n^2 + b_n^2}$

$$C_3 = \sqrt{\left(\frac{1}{3\pi}\right)^2 + \left(\frac{1}{9}\right)^2}$$

⇒ For even functions

$$b_n = 0$$

⇒ For odd functions

$$a_n = 0$$

$$c_n = |a_n|$$

$$a_1 = \frac{-4}{\pi^2}$$

$$a_2 = 0$$

$$a_3 = \frac{-4}{9\pi^2}$$

$$a_4 = 0$$

$$a_5 = \frac{-4}{25\pi^2}$$

$$a_7 = \frac{-4}{49\pi^2}$$

$$a_9 = \frac{-4}{81\pi^2}$$

⇒ Find THD (consider the first 4 non zero harmonics)

$$THD = \sqrt{\sum_{n=2}^9 (I_n)^2}$$

I,

$$= \sqrt{\left(\frac{-4}{9\pi^2}\right)^2 + \left(\frac{-4}{25\pi^2}\right)^2 + \left(\frac{-4}{49\pi^2}\right)^2 + \left(\frac{-4}{81\pi^2}\right)^2}$$

$$\frac{21}{\pi^2}$$



$$\cong 20.2\% = 12\%$$

Part 1: DC/DC converters:-


Applications:

- ① PV Systems [DC load]
- ② DC Power Supplies
- ③ E.V.


Classification of DC/DC converters

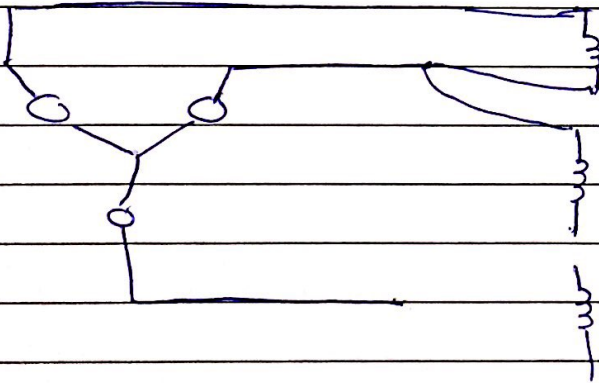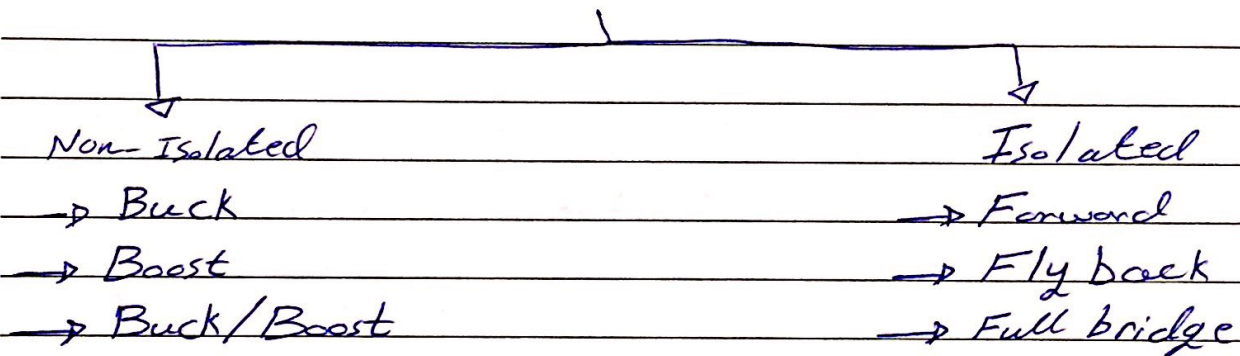


$$\Delta - \frac{V_1}{V_2}$$

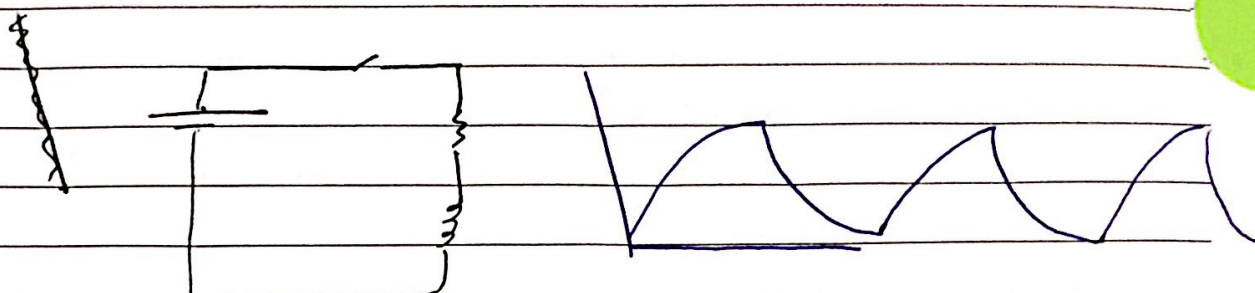




step up

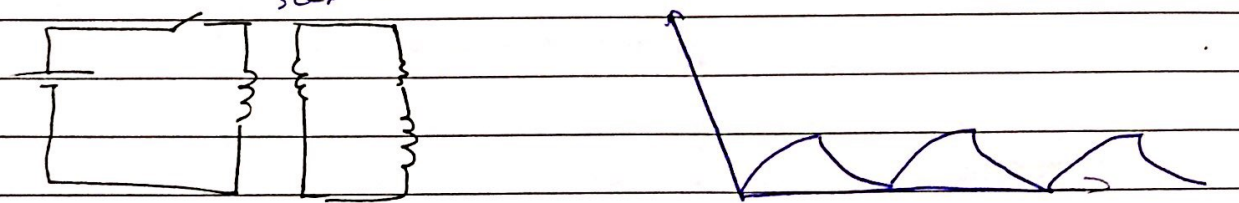

① Buck converter origin
"step down converter"

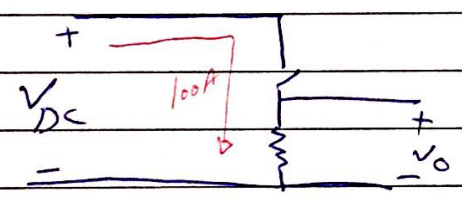

Trial II

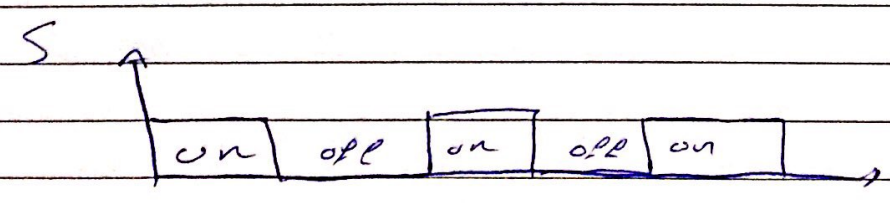
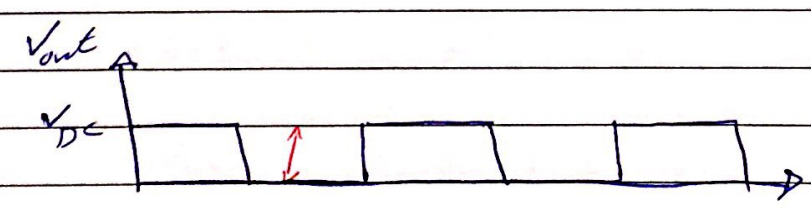
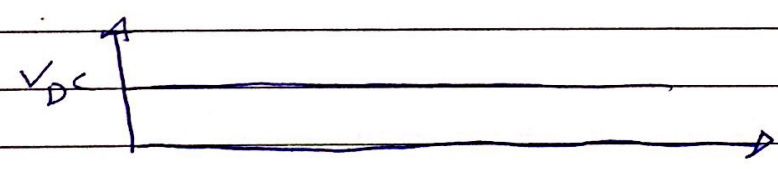


$$\text{Duty ratio (D)} = \frac{T_{on}}{T_{on} + T_{off}} = \frac{T_{on}}{T}$$

$$T = T_{on} + T_{off}$$

Trick (2)

$$V_L = L \frac{di}{dt}$$

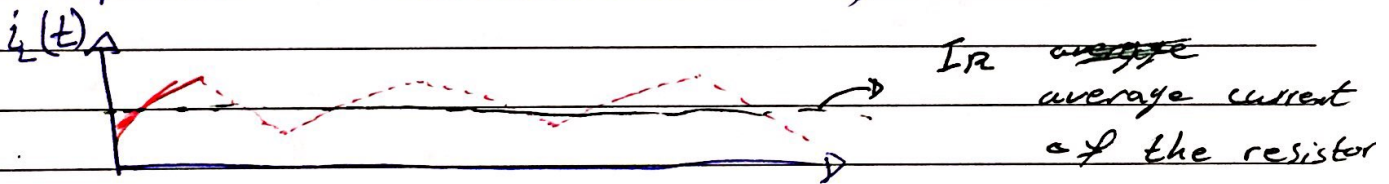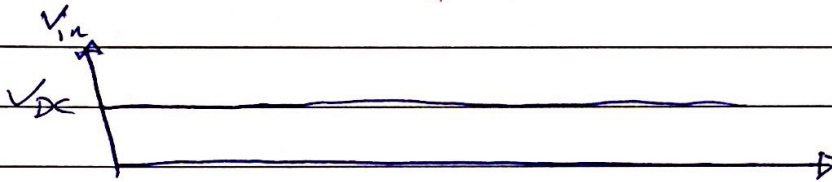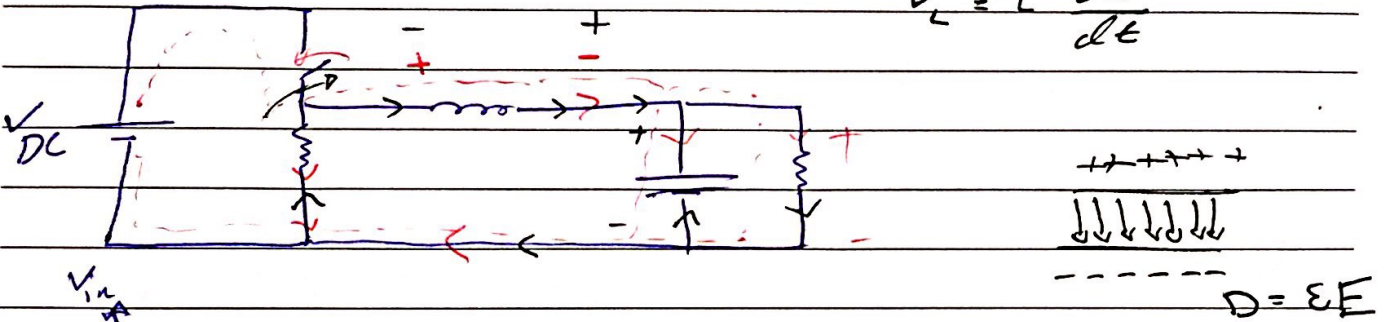

I_R average current of the resistor




→ In steady state and if L is very large

on state : $i_L(t) = i_L(t) + i_R'(t)$


off state : $i_L(t) + i_L(t) = i_R'(t)$

$$i_L(t) \cong 0$$

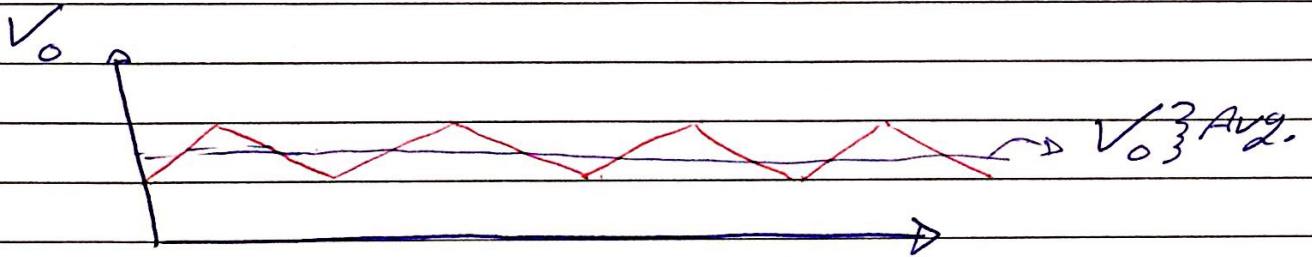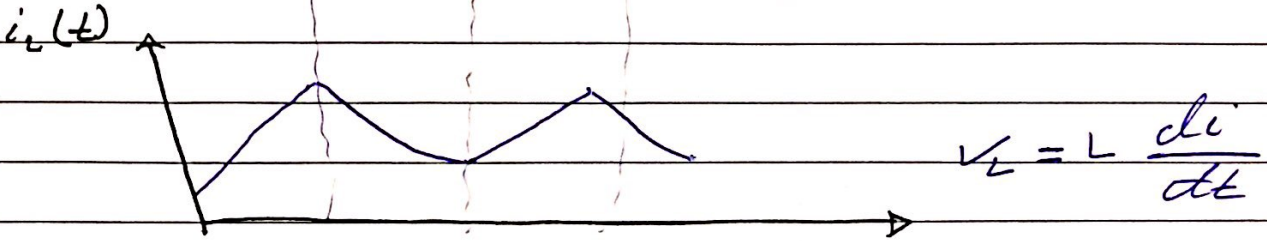
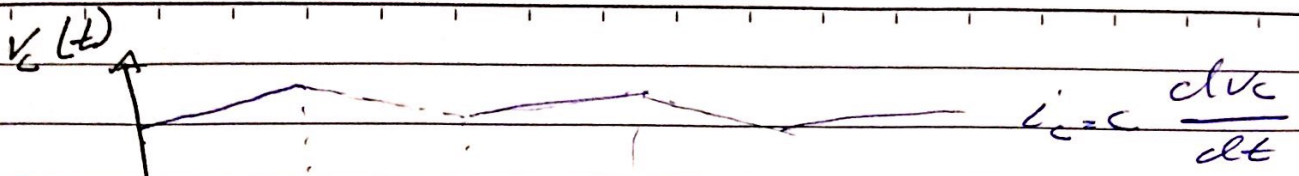
$$i_L(t) \cong i_R'(t) \Rightarrow I_R = \frac{1}{T} \int_0^T i_R(t) dt$$



Final version:

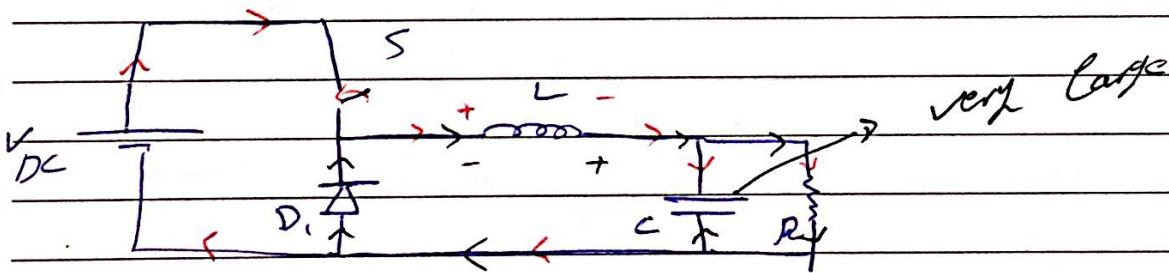


→ more efficient

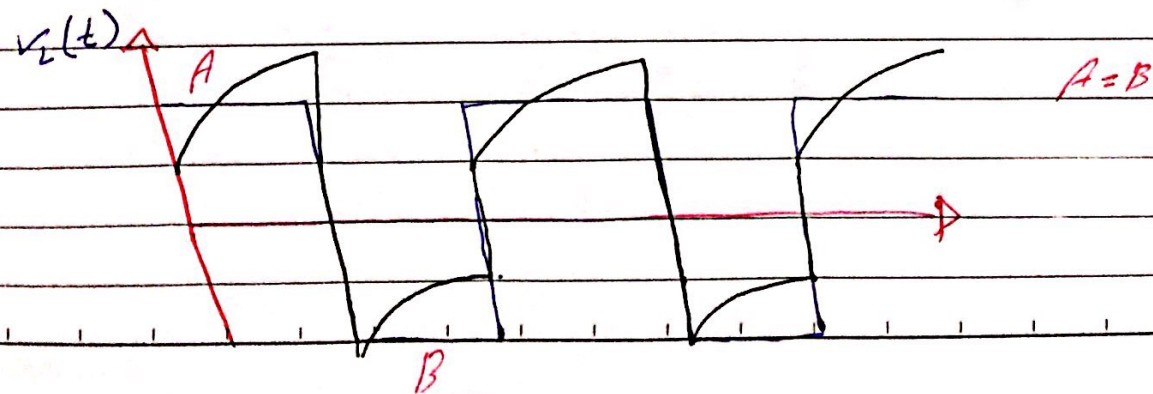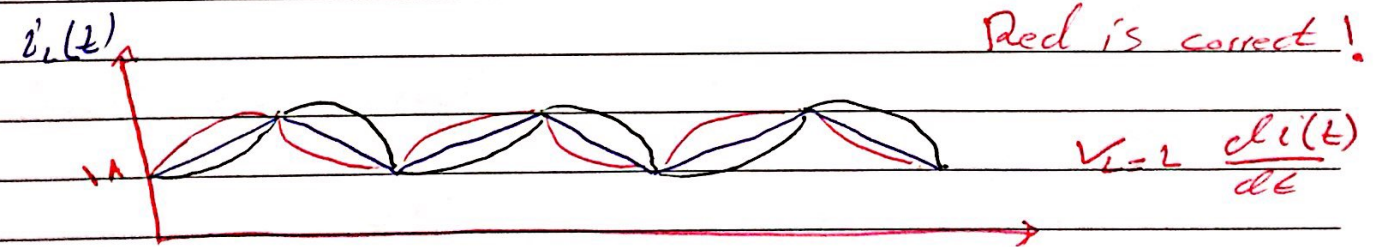

In steady state & considering the charge reservation Principle

$$i(t=0) = i(t=T_s)$$

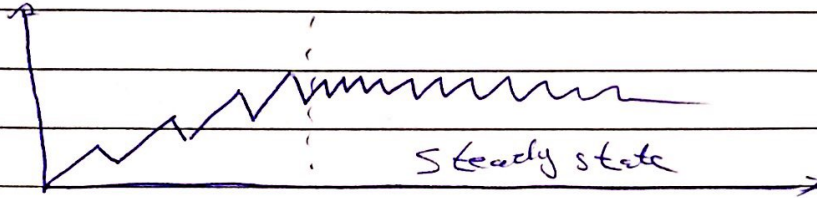

$$V_L = L \frac{di}{dt}$$


$$di(t) = \frac{1}{L} V_L dt$$

$$\int_{i(0)}^{i(T_s)} di(t) = \frac{1}{L} \int_0^{T_s} V_L dt$$


$$i(T_s) - i(0) = \frac{1}{L} \int_0^{T_s} V_L(t) dt$$

$\therefore A = B$ (Area A = Area B)

Buck converter

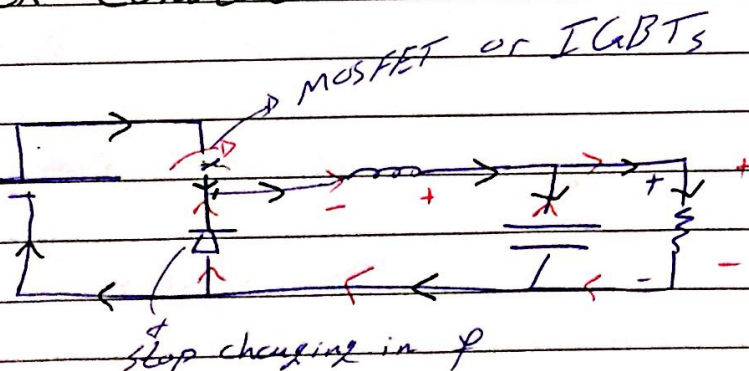


step down

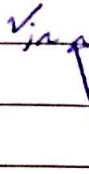

S





$$I_L(t) \approx i_L(t)$$

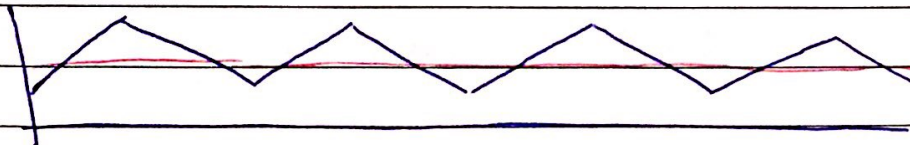

I_{avg}
 $V_o = R I_o$

$v_L(t)$

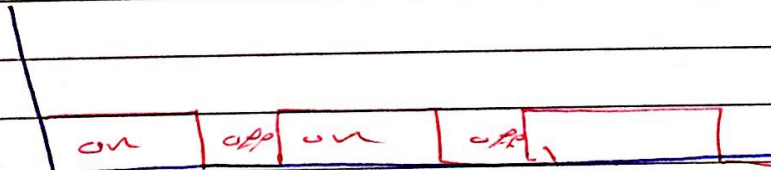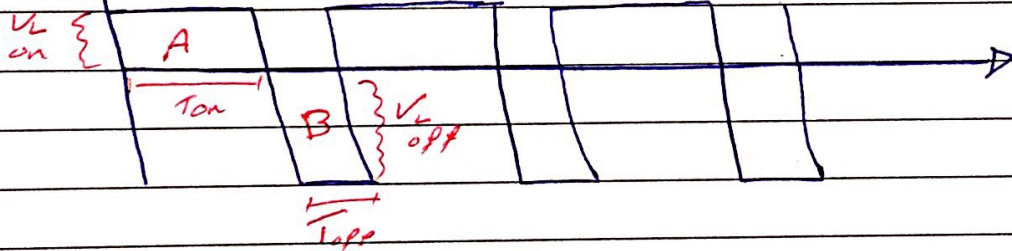

$$\text{Area A} = \text{Area B}$$

$$V_{L\text{on}} * T_{\text{on}} = V_{L\text{off}} * T_{\text{off}}$$

$$V_{L\text{on}} = V_{in} - V_o$$

$$V_{L\text{off}} = V_o \quad \text{[talking about areas]}$$

$$L \frac{di}{dt} = -V_o$$

$$\therefore (V_{in} - V_o) * T_{on} = V_o * T_{off}$$

$$D = \frac{t_{on}}{T} \Rightarrow t_{on} = DT$$

$$t_{off} = T - DT = (1-D)T$$

$$\Rightarrow (V_{in} - V_o)DT = V_o(1-D)T$$

$$DV_{in} - DV_o = V_o - DV_o$$

$$V_o = DV_{in}$$

$$i V_{in} = DC$$

$$V_o = AV_o$$

$$V_o(t) = R i_o(t)$$




$$V_{in} I_{in} = V_o I_o \quad [\text{considering lossless converter}]$$



$$V_{in} I_{in} = (DV_{in}) I_o$$

$$I_{in} = DI_o$$

$$\Rightarrow I_o = \frac{I_{in}}{D}$$

* How to control Switch ~~CPWM~~ [CPWM]

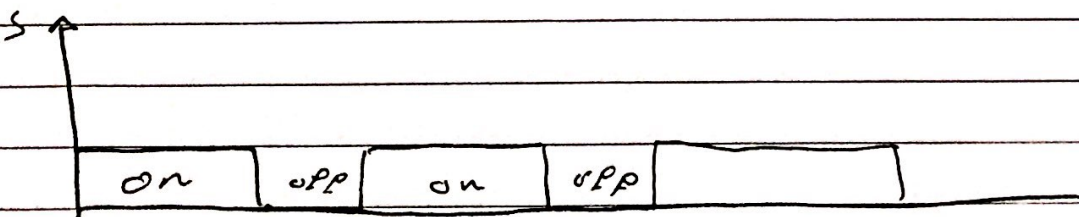


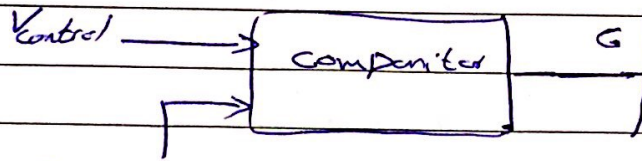
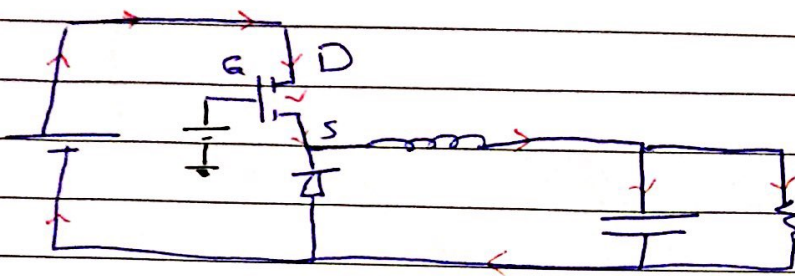


Repetitive wave form

[Sawtooth]


$$V_{\text{control}} > V_{\text{ST}} \Rightarrow 1$$
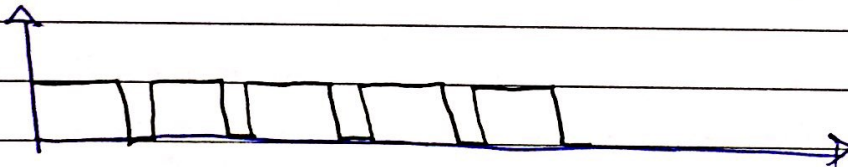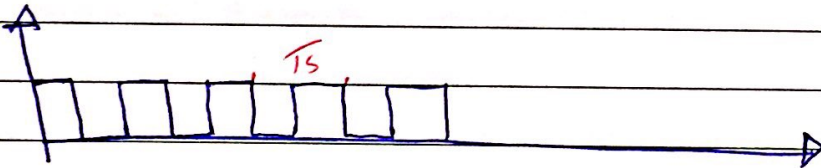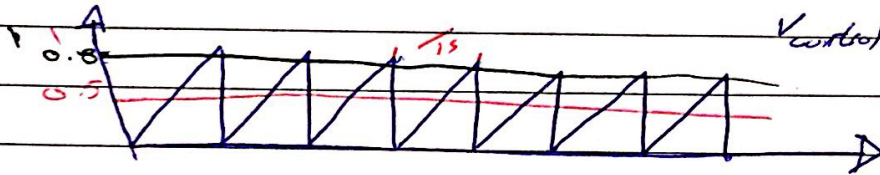
$$V_{\text{control}} < V_{\text{ST}} \Rightarrow 0$$




PWM = Pulse width modulation


Back to Buck converter

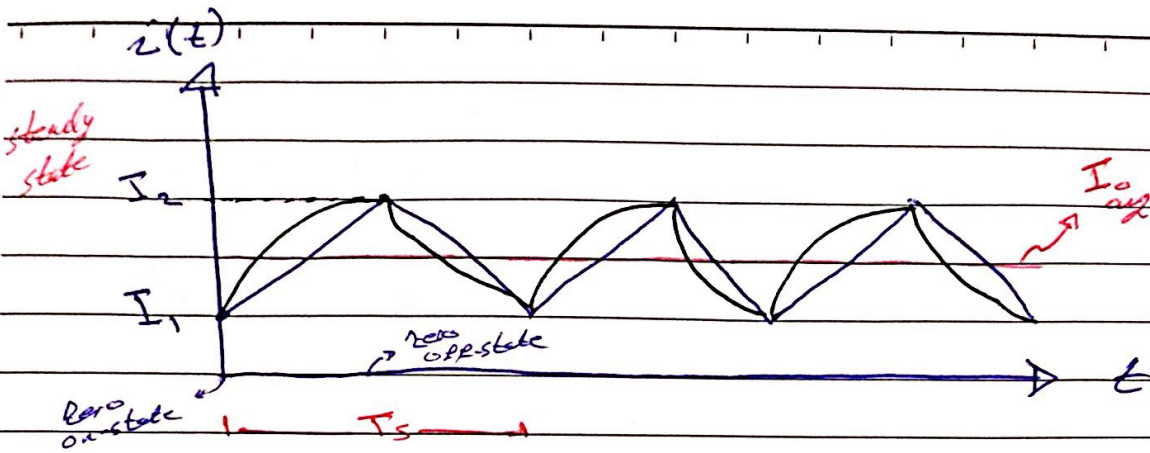

$$I_0 = \frac{I_1 + I_2}{2}$$

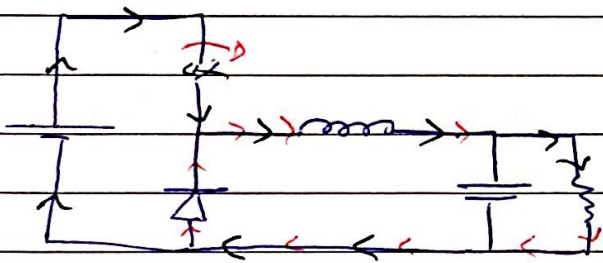

considering exact solution

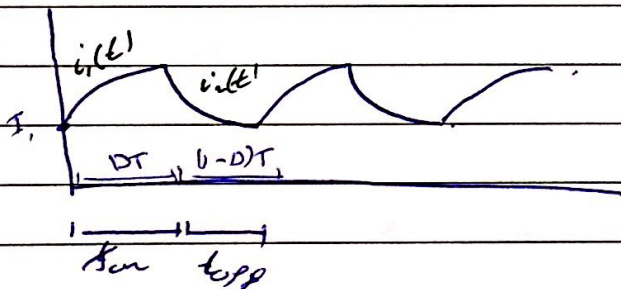

In the on-state

$$[i_L(0) = I_1]$$

$$-V_s + L \frac{di_L(t)}{dt} + R i_L(t) = 0$$

$$L \rightarrow V_s = R i_L(t) + L \frac{di_L(t)}{dt}$$

$$i_L(t) = I_1 e^{-\frac{tR}{L}} + \frac{V_s}{R} \left[1 - e^{-\frac{tR}{L}} \right]$$

natural

Forced

off-state

Apply KVL

$$i_2(0) = I_2$$

$$R_2 i_2(t) + L \frac{di_2(t)}{dt} = 0$$

$$i_2(t) = I_2 e^{-\frac{tR}{L}}$$

$$i_2(t = DT) = I_2 \dots \textcircled{1}$$


$$i_2(t = (1-D)T) = I_1 \dots \textcircled{2}$$

@ $t = DT$ sub. in $\textcircled{1}$

$$I_1 e^{-\frac{DTR}{L}} + \frac{V_s}{R} \left[1 - e^{-\frac{DTR}{L}} \right] = I_2$$

@ $t = (1-D)T$ sub. in $\textcircled{2}$

$$I_2 e^{-\frac{(1-D)TR}{L}} = I_1$$

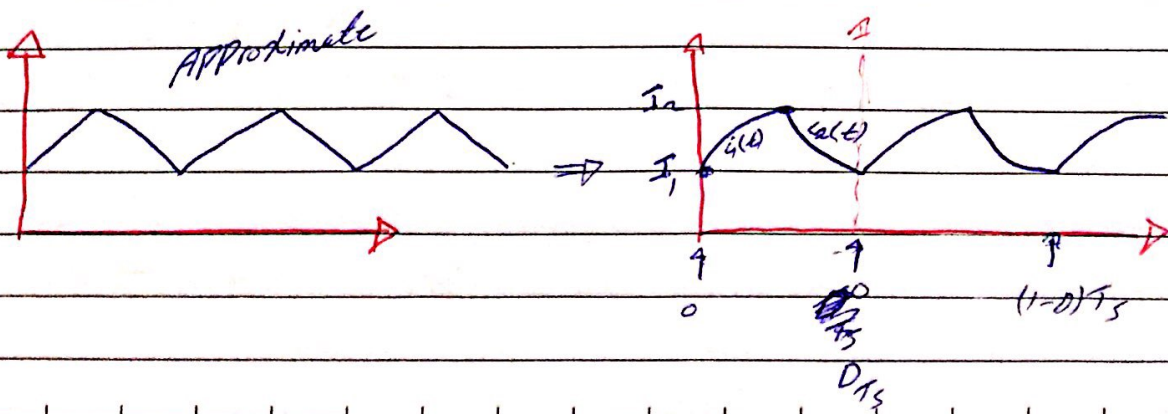


$$i_1(t = DT_s) = I_2$$

$$i_2(t = (1-D)T_s) = I_1$$

$$I_2 = I_1 e^{-\frac{DT_s R}{L}} + \frac{V_s}{R} \left[1 - e^{-\frac{DT_s R}{L}} \right] \dots \textcircled{1}$$
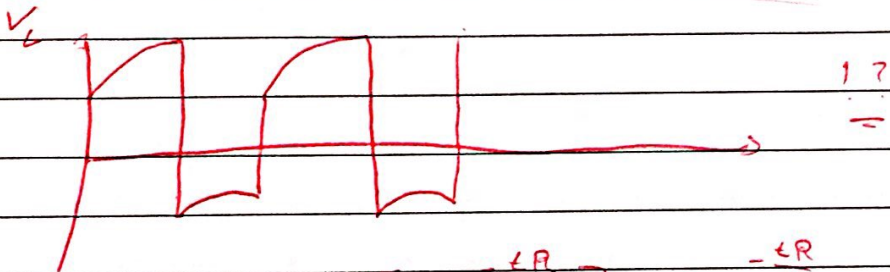
$$I_1 = I_2 e^{-\frac{(1-D)T_s R}{L}} \textcircled{2}$$



$$i_L(t) = \frac{V_s}{R} \left[1 - e^{-\frac{tR}{L}} \right] + I_1 e^{-\frac{tR}{L}}$$

Sub. (2) in (1)

$$I_2 = \left[I_2 e^{-\frac{(1-D)T_s R}{L}} \right] e^{-\frac{DT_s R}{L}} + \frac{V_s}{R} \left[1 - e^{-\frac{DT_s R}{L}} \right]$$

$$I_2 = \frac{V_s (1 - e^{-\frac{DT_s R}{L}})}{R (1 - e^{-\frac{T_s R}{L}})}$$

$$I_1 = \frac{V_s (e^{\frac{DT_s R}{L}} - 1)}{R (e^{\frac{T_s R}{L}} - 1)}$$

⇒ The Peak to Peak ripple

$$\Delta I = I_2 - I_1$$

$$= \frac{V_s}{R} \left[\frac{(1 - e^{-\frac{DT}{L}}) \left(+e^{\frac{TR}{L}} \right)}{(1 - e^{-\frac{TR}{L}}) \left(+e^{\frac{TR}{L}} \right)} - \frac{\left(\frac{DT}{L} - 1 \right)}{\left(\frac{TR}{L} - 1 \right)} \right]$$


$$= \frac{V_s}{R} \left[\frac{+(1-D)\frac{TR}{L} - e^{-\frac{TR}{L}} + e^{\frac{TR}{L}} - \frac{DT}{L} + 1}{e^{\frac{TR}{L}} - 1} \right]$$

When it is going to be maximum w.r.t D

→ Derive ΔI w.r.t. D & = 0

$$\frac{d\Delta I}{dD} = \frac{V_s}{R \left(e^{\frac{TR}{L}} - 1 \right)} \left[\frac{TR}{L} e^{-\frac{TR}{L}} + (1-D)\frac{TR}{L} - \frac{TR}{L} e^{\frac{DT}{L}} \right]$$
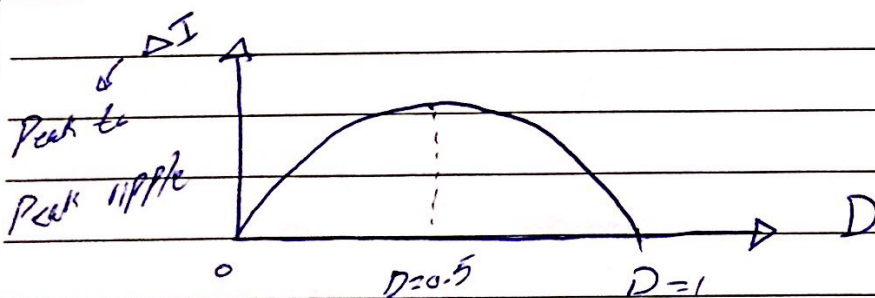
$$1 - D = D \Rightarrow D = \frac{1}{2} = 0.5$$



ΔI_{max} occurs when $D = 0.5$

$$\Delta I_{max} = \frac{V_s}{R} \left[\frac{-e^{-\frac{0.5TR}{L}} + e^{\frac{TR}{L}} - e^{\frac{0.5TR}{L}} + 1}{e^{\frac{TR}{L}} - 1} \right]$$

$$= \frac{V_s}{R} \left[\frac{(1 - e^{-\frac{0.5TR}{L}})^2}{(1 - e^{-\frac{0.5TR}{L}})(1 + e^{-\frac{0.5TR}{L}})} \right]$$

$$= \frac{V_s}{R} \left[\frac{e^{\frac{0.5TR}{L}} - 1}{e^{\frac{0.5TR}{L}} + 1} \right]$$

$$= \frac{V_s}{R} \tanh\left(\frac{TR}{4L}\right)$$

$$\rightarrow (x - y)^2 = x^2 - 2xy + y^2$$

$$\rightarrow \tanh(x) = \frac{e^{2x} - 1}{e^{2x} + 1}, \quad 2x = \frac{TR}{2L}$$


$$x = \frac{TR}{4L}$$

For very small θ


$$\tanh \theta = \theta$$

$$\therefore \Delta I_{\max} = \frac{V_s}{R} * \frac{TR}{4L}$$

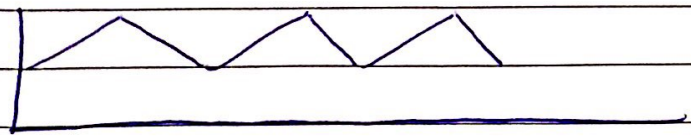
$$\Delta I_{\max} = \frac{V_s}{4fL} \quad \text{for a Buck converter}$$



steady state


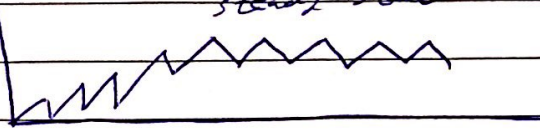


min. ripple
& wanted voltage

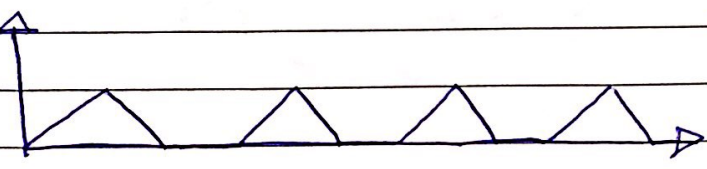

2 Modes of operation

continuous mode discontinuous mode

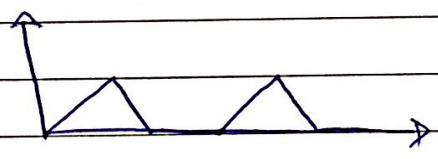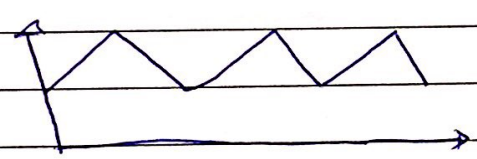


$$\frac{L}{R} = \tau \gg T$$

$$\frac{L}{R} = \tau \ll T$$

① Find which mode will be having higher output voltage [with the same duty ratio]

continuous mode $V_o = D V_{in}$

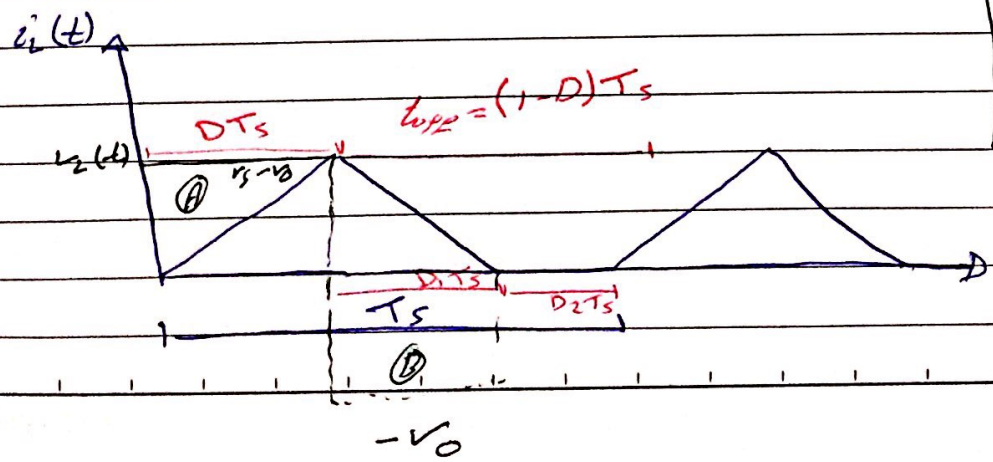

$$(V_s - V_o) D T_s = V_o (\Delta, T_s)$$

$$V_s D T_s - V_o D T_s = V_o \Delta, T_s$$

$$V_{out} = V_s \left[\frac{D}{D + \Delta_1} \right]$$

Discont.

$$V_{out} = V_s \left[\frac{D}{D + (1-D)} \right]$$

Cont.

V_{out} is greater in Discont. mode !!