

# Power Electronics

## NoteBook

Dr. Mohammad Z Khader

By: Mustafa Zahlan & Imtyaz Omar



- the devices in the Power electronics need solid state physics

- the

- Mercury arc rectifier act as a diode that use Mercury as conductor  
note that it can hold large current "The beginning of power electronics"

- after Mercury arc rectifier the metal tank rectifier appear.

- Grid controlled vacuum tube use bulbs & has multiple terminal  
note that old radio use five bulbs.

- transistor is semiconductor device can act as triode which has  
three terminal (bulbs).

- Ignitron, Phatron, Thyatron can hold large current but relatively  
it was small current.

\* all above pre history of power electronics. (-1957)

- first phase:

~~GEA~~ Application of fast-switching fully controlled semiconductor device  
which can make fast switching for large frequency.

- In thyristor can hold thousands of Amperes the large terminal is  
a diode & small one is gate act as a controller that allow ~~for~~  
specific amount of current to pass.



### \* Applications :-

#### (1) Motor drives :

from some kilo watts up to hundreds or thousands of kilo watts it can change the speed of the motors

#### (2) Electroplating: علاوة الطلاء

#### (3) Induction heating: علاوة التسخين

#### (4) Magnetic levitation: علاوة الرفع الكهرومغناطيسية

#### (5) High voltage dc transmission:

→ when DC power transmission it's more economical because the resistance of the DC is less than the AC because of skin effect in which AC current transmit on the outer surface of the conductor while DC current transmitted on all the cross-section area.

→ In large distance countries the conversion of AC voltage to DC & then transmit it through transmission lines & then convert it to AC is better than the transmission of AC directly because of the losses.

• we mean by good power quality is the pure sinusoidal wave voltage without harmonics & discontinuity & with constant peak to peak value & frequency.

• the process of electric power generation from solar energy use power electronics.

### Advantages :-

(1) Easy & flexible.

(2) Faster because it take millisecond, while the mechanical switch

take long time.

③ noise is less in power electronics:

as example: old telephony system use relays so when we move number nine for example nine relays will change it state so a large noise also it need maintenance because of sparks.

@ high efficiency

■ Disadvantages:


① it generates harmonics. because of the process of on/off switching

② Harmonics are injected into power

system lines the performance of

other load affected

→ illustration.

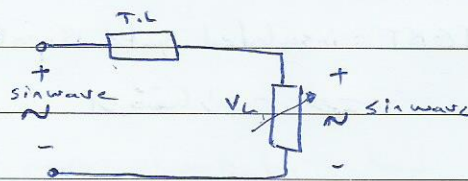

$$v = V_m \sin \omega t$$

$$i = \frac{V_m}{Z} \sin(\omega t + \theta) +$$

$$V_2 \sin(3\omega t)$$



\* the power factor is preferred to be near than 1 to make the generated power maximum.

### ■ Major issues in power electronics

reliable: موثوقة، وبسهولة صيانتها، وبسهولة إصلاحها، أو تبديلها

- less volume & weight for planes & spaceships & space stations
- less cost for large amount produced devices.

### ■ Power devices:

IGBT: insulated gate Bipolar transistor.

الاقفا، الت، زف

### ■ Slide 23:

thyristor will be studied in detailed in this course.

### ■ Slide 24:

• normal thyristor is used in low freq 50-60 Hz for rectification application also TRIAC can be used

• normal thyristor can be used for <sup>low frequency</sup> high frequency & high power.

• GTO: also thyristor & has property of stop of operation & can be used for larger frequencies & high power can be used in case

& UPS: ~~uninterrupted~~ <sup>power</sup> supply.  
uninterrupted

• MOSBIOP: works for larger frequency but with low power.

• when the frequency increase the power become less

- UPS = Uninterrupted power supply take the power from the (wall) and if the connector disconnect then it take the power from the battery.

Lecture no. 2 :

■ Slide 1 :

■ Slide 4 :

- AC : 230V & 60Hz

full wave rectifier using thyristor : we use switching on & off to control the average value.

• using triac we can control the amount of power absorbed by the load.

- Choppers used to convert the DC at one level to another level.

Choppers used to convert the DC level ~~from~~ by using transistor to cut the DC at specific intervals to change the average value.

- inverter change AC to AC.

• our concentration is in the power converter . but we use the filters to make the signal more smooth. also we use the feedback control switching



Slide 7:-

switched mode is the subject of power electronics.

Slide 8:-

we avoid the use of magnetics in power electronics.

Slide 9:-

we avoid the use of resistor because it generate loss in power.

why to avoid linear mode?

because of the DC component which represent a loss.

Slide 10:-

ideal switch consumes zero power since in either both cases either the voltage or current is zero.

Slide 11:-

the efficiency is 50% since we lost 500 watt at the transmission line.

Slide 13:-

we can use the amplifiers

Slide 14:-

the use of switch to brake the input signal such that


Slide 15:-

D  $\equiv$  Duty cycle  $\Rightarrow D = \frac{\text{Time on}}{\text{Total period}}$ 

Slide 16:-


since ~~we~~ we have some time on & some time off so this not desirable

so we can use low pass filter.

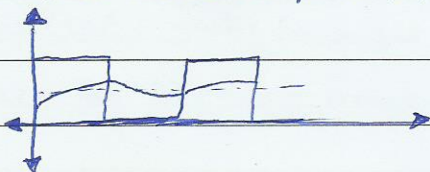

Slide 18 e-

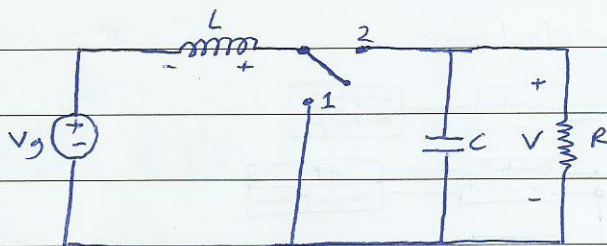the boost converter is used to store energy then to release it to obtain large voltage from low one example in car the available voltage is 12V & to start the engine we need 11,000 V so we use the boost converter to make this.



$$V_{dc} = L \frac{di}{dt}$$

$$di = \frac{V_{dc}}{L} \cdot dt$$


$$i = \frac{V_{dc}t}{L} + k$$

note that if the switching is instantaneously then the obtained voltage is infinite.

when the switch is moved to (2) then the voltage will be negative across the inductor since the change in current is negative so the output voltage will be the voltage across the inductor plus the  $V_g$ .

the new voltage depend on the period of switching that is  $\frac{1}{1-D}$

where  $D \equiv$  Duty cycle

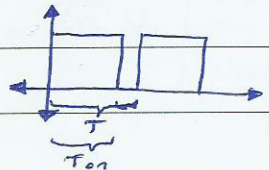


In this case voltage will be high since  $D \approx 1$

Slide 19 e-


\* single phase inverter.

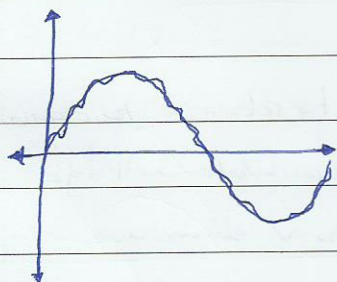the object of the capacitor & the inductor to make smoothing.





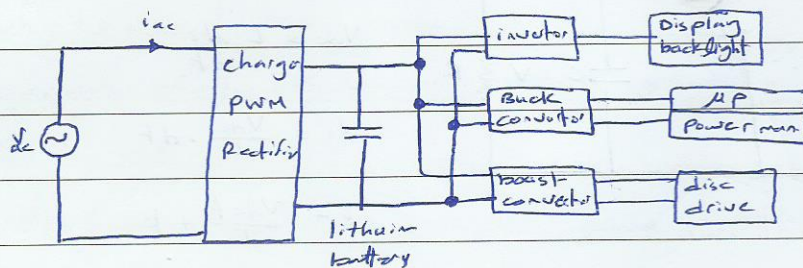- Slide 21: Example of power electronics.



- why inverter because screen need high frequency
- why battery to isolate the source  $V_{ac}$  from the rest items of the computer.
- why to use boost converter for disk drive because its run on higher voltage.
- Buck converter is a type of converter that converts DC to DC.

\* Power computation:

$p(t) = v(t) \cdot i(t)$   $\rightarrow$  the product of current & voltage.

$P = VI$


• note that for a resistive load:

$p(t) = R i^2(t)$

$P = RI^2$

$RI_{eff}^2 = \frac{R}{T} \int_0^T i^2(t) \cdot dt$  where  $I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2(t) \cdot dt}$

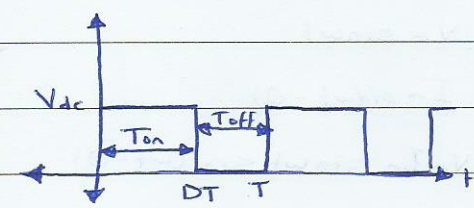• if  $D = \frac{T_{on}}{T_{on} + T_{off}}$



\* where  $T_{on}, T_{off}$  shown on the figure

\* note that  $T_{on} + T_{off} = T \equiv$  the period of the one cycle.

\*  $T_{off} = (1-D)T$

\*  $V_{av} = \frac{DT V_{dc}}{T} = DV_{dc}$


\*  $V_{rms} = \sqrt{\frac{DT V_{dc}^2}{T}} = \sqrt{D} V_{dc}$  the equivalent dc value that give the same energy of the shown AC voltage.

\* now let  $v(t) = V_m \sin \omega t$

$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2 \omega t \cdot d\omega t} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2 \omega t \cdot d\omega t}$


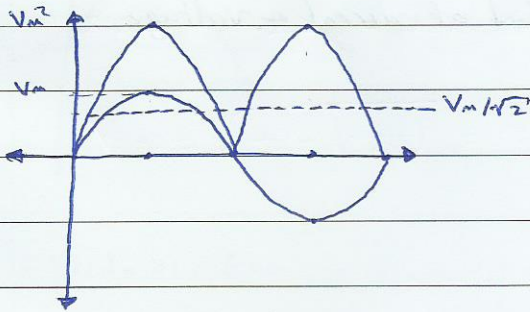
$$V_{rms} = \sqrt{\frac{V_m^2}{2\pi} \int_0^{2\pi} \frac{1}{2} (1 - \cos 2\omega t) d\omega t} = \sqrt{\frac{V_m^2}{2}} = \frac{V_m}{\sqrt{2}} = V_m / \sqrt{2}$$



• now for the power :-

let  $i$  lag  $v$  by certain angle  $\theta$

$$v(t) = V_m \sin \omega t$$

$$i(t) = I_m \sin(\omega t - \theta)$$

$$p(t) = V_m I_m \sin \omega t \sin(\omega t - \theta)$$

$$P_{avg} = \frac{V_m I_m \cos(\theta)}{2}$$


$$p(t) = \frac{V_m I_m \cos(\theta)}{2} + \frac{V_m I_m \cos(2\omega t - \theta)}{2}$$



\* for half-wave rectified :-



$$V_{rms} = \sqrt{\frac{V_m^2}{2\pi} \int_0^{\pi} \sin^2 \omega t \cdot d\omega t}$$
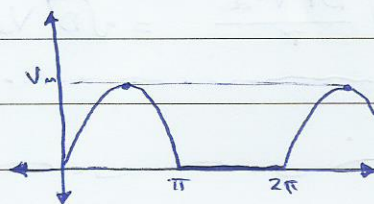
$$V_{rms} = \sqrt{\frac{V_m^2}{2\pi} \cdot \frac{\pi}{2}}$$




$$V_{rms} = V_m / 2$$

For single phase :-

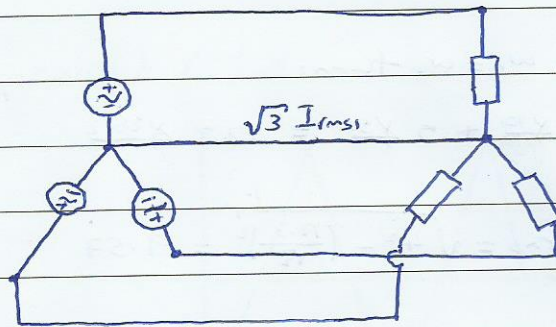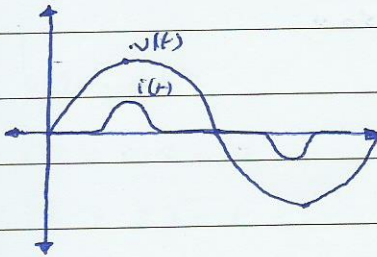

$$i_n = i_1(t) + i_2(t) + i_3(t)$$
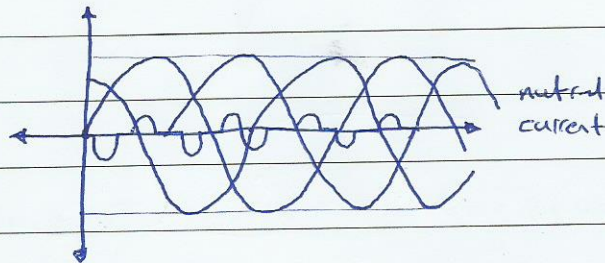
$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i_n^2(t) \cdot dt}$$



$$I_{rms} = \sqrt{3} I_{rms1}$$

\* now multiple frequencies :-

$$v(t) = V_1 \sin \omega_1 t + V_2 \sin \omega_2 t$$

$$v^2(t) = V_1^2 \sin^2 \omega_1 t + V_2^2 \sin^2 \omega_2 t + 2 V_1 V_2 \sin \omega_1 t \sin \omega_2 t$$

$$v^2(t) = V_1^2 \sin^2 \omega_1 t + V_2^2 \sin^2 \omega_2 t + \frac{2 V_1 V_2}{2} [\cos(\omega_1 - \omega_2)t + \cos(\omega_1 + \omega_2)t]$$

$$V_{rms} = \sqrt{V_{rms1}^2 + V_{rms2}^2}$$

Example :- let  $v(t) = 4 + 8 \sin(\omega_1 t + 10^\circ) + 5 \sin(\omega_2 t + 50^\circ)$

Find the rms value if ①  $\omega_1 = \omega_2$  ②  $\omega_1 = 2\omega_2$ ?

Answer :-

① if  $\omega_1 = 2\omega_2$  then  $\omega_1 \neq \omega_2$  so

$$V_{rms} = \sqrt{4^2 + \frac{8^2}{2} + \frac{5^2}{2}} = \sqrt{60.5} = 7.778$$



2) if  $\omega_1 = \omega_2$  then:

$$8 \angle 10^\circ + 5 \angle 50^\circ = 12.3 \angle 25.2^\circ$$

$$" 8 \cos 10^\circ + j 8 \sin 10^\circ + 5 \cos 50^\circ + j 5 \sin 50^\circ "$$

$$V_{rms} = \sqrt{4^2 + \left(\frac{12.3}{\sqrt{2}}\right)^2} = 9.57$$


\* Consider the following current find the rms value?

•  $0 \rightarrow t_1$

•  $y = mx + b$

$$i_1 = \frac{2I_m}{m} t - \frac{I_m}{b}$$

$$m = \frac{2I_m}{t_1} \quad b = -I_m$$

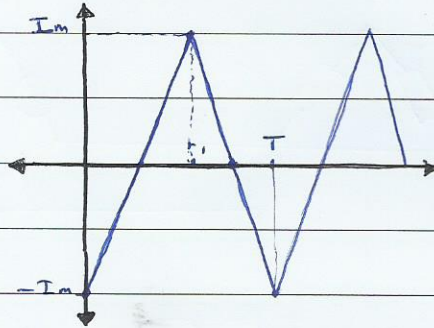

•  $I_m = mt_1 + b$  &  $-I_m = mT + b$  solve them to take the values of  $m$  &  $b$ .

•  $m(T - t_1)$



- Sinusoidal Source with non-linear load.

$$v(t) = V_1 \sin(\omega t + \theta)$$

$$\rightarrow V_{rms} = V_1 / \sqrt{2}$$

$$i(t) = I_0 + \sum I_n \sin(\omega t + \phi_n)$$

$$\rightarrow I_{rms} = \sqrt{I_0^2 + (I_1/\sqrt{2})^2 + \dots}$$

$$P = \frac{V_1}{\sqrt{2}} \cdot \frac{I_1}{\sqrt{2}} \cos(\theta_1 - \phi_1)$$

$$Q = (V_1/\sqrt{2}) (I_1/\sqrt{2}) \sin(\theta_1 - \phi_1)$$

$$|S| = I_{rms} \cdot V_{rms}$$

$$\boxed{P.F. = P / |S|}$$

$$P.F. = \frac{V_{rms} \cdot I_{rms} \cos(\theta_1 - \phi_1)}{V_{rms} \cdot I_{rms}} = \frac{I_{rms} \cos(\theta_1 - \phi_1)}{I_{rms}}$$

$$\boxed{P.F. = \text{Distortion factor} \times \text{displacement factor.}}$$

- note that:

$$\text{Displacement factor} \equiv \cos(\theta_1 - \phi_1)$$

$$\text{Displacement angle} \equiv \theta_1 - \phi_1$$

$$\text{Distortion factor} \equiv (I_{rms} / I_{rms})$$

$$\bullet \text{ Total harmonic distortion} \equiv \sqrt{\frac{\sum_{n=2}^{\infty} I_{n,rms}^2}{I_{1,rms}^2}} \rightarrow \text{review it}$$

$$\text{Total harmonic distortion} = \sqrt{\frac{I_{rms}^2 - I_{1,rms}^2}{I_{1,rms}^2}}$$

$$\text{Total harmonic distortion} = \sqrt{\frac{1}{(DF)^2} - 1} = \text{THD}$$

$$S^2 = P^2 + Q^2 + D^2$$

$$D = \sqrt{S^2 - P^2 - Q^2} = V_{rms} \sqrt{\sum_{n=1}^{\infty} I_n^2}$$

$$D.F = \frac{1}{\sqrt{1 + THD^2}}$$

■ Example:-  $v(t) = 100 \cos(377t)$

$$i(t) = 8 + 15 \cos(377t + 30) + 6 \cos(2 \times 377t + 45) + 2 \cos(3 \times 377t + 60)$$

$$\bullet P = \frac{100}{\sqrt{2}} \times \frac{15}{\sqrt{2}} \times \cos(-30) = 650 \text{ watt}$$

$$\bullet Q = \frac{100}{\sqrt{2}} \times \frac{15}{\sqrt{2}} \sin(-30) = -375 \text{ VAR "capacitive"}$$

$$\bullet I_{rms} = \sqrt{(8)^2 + (15/\sqrt{2})^2 + (6/\sqrt{2})^2 + (2/\sqrt{2})^2} = 14 \text{ A}$$

$$\bullet |S| = (100/\sqrt{2})(14) = 990 \text{ VA}$$

$$\bullet D = \sqrt{(990)^2 - (650)^2 - (-375)^2} = 648 \text{ VAD}$$

$$\bullet P.F = \frac{650}{990} = 0.66$$


$$\bullet D.F = \frac{15/\sqrt{2}}{14} = 0.76$$

$$\bullet THD = \sqrt{\left(\frac{1}{0.76}\right)^2 - 1} = 0.86$$

$$\begin{aligned} P.F &= D.F \times \text{displacement} \\ P.F &= 0.76 \times 0.866 \\ P.F &= 0.66 \end{aligned}$$



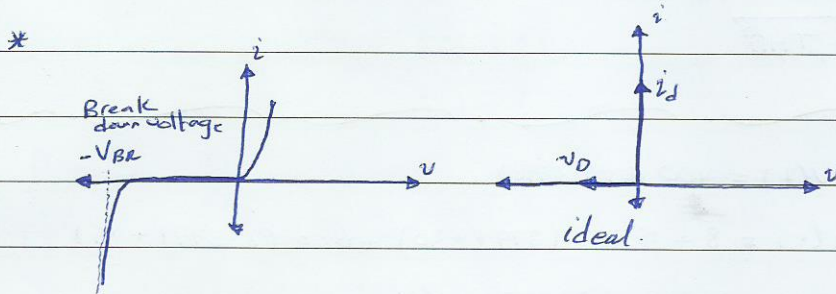\* note that the  $(I_{D1}, I_{D2})$  is very important because if we don't fix it this would generate sparks + vibrations that increase the resistance of the diode.



- Reverse break down voltage it's the maximum voltage we can apply to the diode with remain it to do its work. & we avoid it.

- $t_{rr} \equiv$  reverse recovery time.

- 6000 volt  $\rightarrow$  peak value not rms.

- the forward portion of the characteristics can be approximately describe by  $I_D = I_S (e^{v_D/nV_T} - 1)$

- if the temperature is high then the current is low.

- note that usually  $e^{v_D/nV_T} \gg 1$  then  $I_D = I_S e^{v_D/nV_T}$

- $I_D$  always much greater than  $I_S \rightarrow$  reverse current.


- now if  $v_D$  is negative then the current become

$$I_D = I_S (e^{v_D/nV_T} - 1)$$

↓  
less than 1

$$I_D = -I_S$$

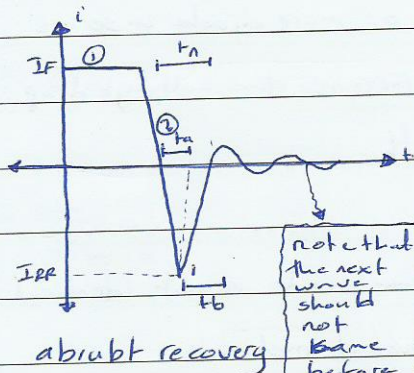• note that the reverse saturation current  $I_s$  is in range of nano or micro Amperes see example?



note that the next wave should not be same before reach this point

- ① when the current passes through the Diode
- ② at the instant of ~~cut~~ turn the current off
- note that the reverse recovery current can be greater than  $I_F$
- $t_b$  assumed to be 25% because at this time we will not enter the non linear region yet.

•  $t_{rr} = t_a + t_b$   
total recovery time

• we should not apply new current before the total recovery time apply.

• we should not apply high frequency to diode because high frequency means high low time between two waves so that  $t_{rr}$  not yet passed

•  $t_{rr}$  = the time need to remove the charge on the diode in the reverse direction.

• Soft recovery factor (SF) =  $t_b / t_a$ .

•  $I_{RR} = t_a \frac{di}{dt}$

$Q_{RR} \approx \frac{1}{2} I_{RR} t_a + \frac{1}{2} I_{RR} t_b$   
 ↳ charge of the reverse recovery

•  $t_{rr} t_a = \frac{2Q_{RR}}{di/dt}$  —  $t_b$  is negligible compared with  $t_a$  then because the moving up direction is faster than moving down.

$t_a = \sqrt{\frac{2Q_{RR}}{di/dt}} = \sqrt{2Q_{RR} \frac{di}{dt}}$




• why to use diode in series:-

if we have a certain requirement of voltage & one diode can't hold this voltage we can connect two or more diode in series this will not effect the voltage since it will increase the voltage drop. but same current will pass through both.

• note that if the characteristics of the two diode is not identical then the voltage will be divided in non-equivalent method.

• why this make problem:

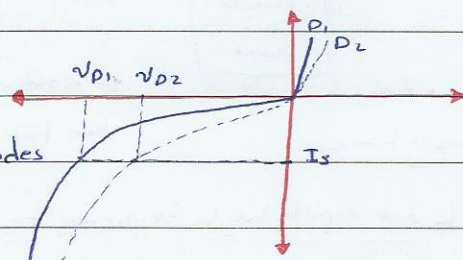because if we connect two diodes each one can hold 6000 volt in series with 10,000 volt source



one may take 7000 volt and another take 3,000 volt due to the non-identical characteristics so the first will burn.

• How we can solve this ?


by connecting parallel resistor in parallel with each diode.

■ Example:-  $V_D = 5KV$ ,  $I_{s1} = 30mA$ ,  $I_{s2} = 35mA$

$$\frac{V_{D1}}{100K} + 30mA = 35mA + \frac{V_{D2}}{100K}$$

$$V_{D1} + V_{D2} = 50KV$$

$$V_{D1} = 50KV - V_{D2}$$

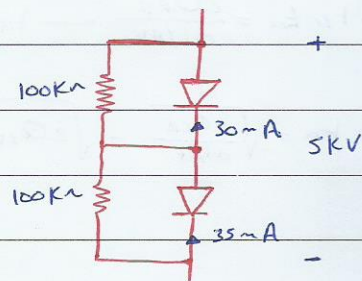

$$\frac{5K}{100K} + 30mA - \frac{V_{D2}}{100K} = \frac{V_{D2}}{100K} + 35mA$$

$$50mA - 5mA = \frac{V_{D2}}{50K}$$

$$V_{D2} = 45 * 50 = 2,25KV \quad + \quad V_{D1} = 2.75KV$$

• now we need  $V_{D1}$  &  $V_{D2}$  to be equal:

$$\frac{2.5K}{R_1} + 30mA = \frac{2.5K}{R_2} + 35mA$$

now let  $R_1 = 100K$   $\rightarrow$  we assume it such that it near the  $I_S$  value

$$25mA + 30mA = \frac{2.5K}{R_2} + 35mA \quad \rightarrow \quad R_2 = \frac{2.5K}{20mA}$$


$$R_2 = 50 * 2.5K = 125K\Omega$$

■ note that we put resistances in parallel to solve steady state problem "same voltage for both"

■ & we put RC circuit in parallel with diode to solve the transient problem "have same transient voltage characteristics"

■ Parallel connection:

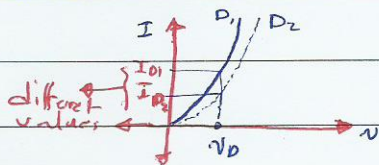
• note that in this case the diode is forward biased & it's used to limit the current but this make Problem since we not guarantee with the same current to pass through the two diodes so we add resistances in series but in this case they have very small value (m $\Omega$ ) range.




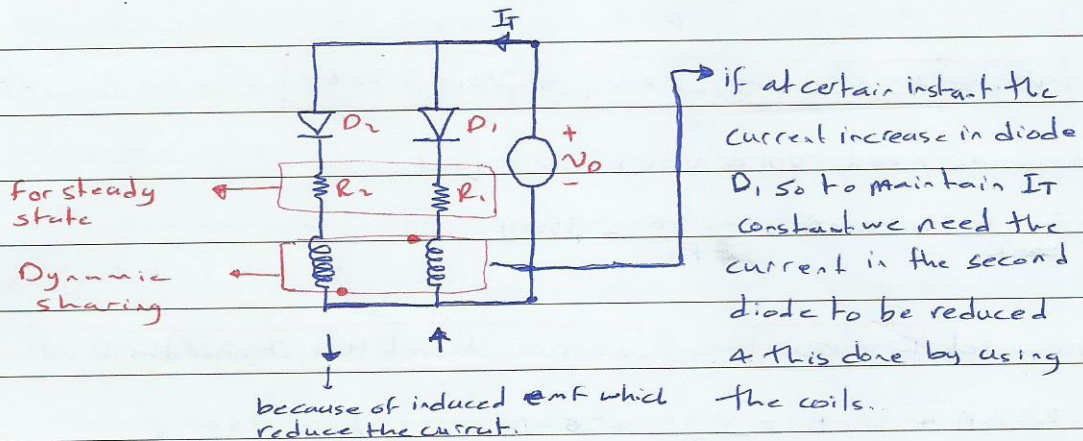
### ■ But how to solve the Dynamic problem?

by using coils with negative dot convention.




### ■ Recovery of trapped Energy with diode:

• note that when the switch closed then the voltage across the coil will increase since that  $i(t) = \frac{1}{L} \int v \cdot dt$  since the source is dc.

• when the switch open if the recovery of trapped energy not available then a spark will exist

~~write~~ when the recovery of trapped energy is supported then when the voltage is built & switch open the energy will transfer through the transformer in inverse polarity & diode is on so the energy will go to the battery.

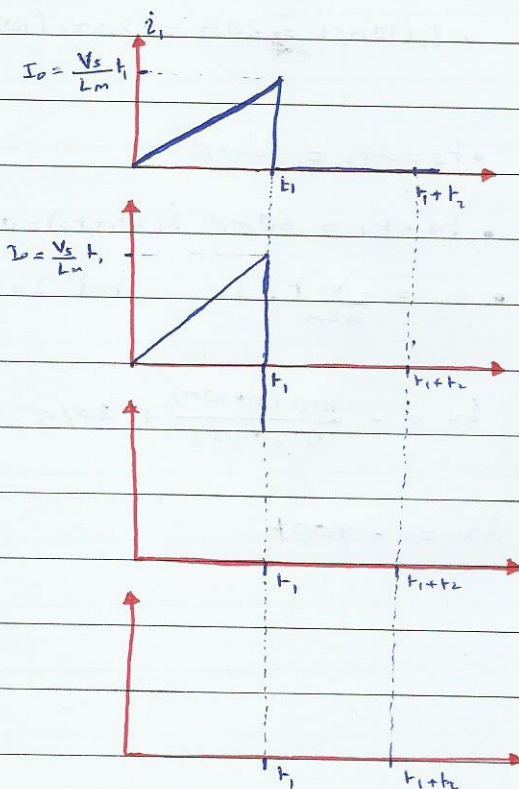- note that  $L_m$  is the inductance seen by the source current & the battery stored energy in it
- in mode 1 the current through the diode is zero since the polarity is reversed.
- in mode 2 the current  $i_s$  is zero due to opening the switch.






■ **Example:**  $V_s = 100$ ,  $L_m = 50 \text{ mH}$ ,  $a = 5$ , find all current & voltages?

• **Solution:**
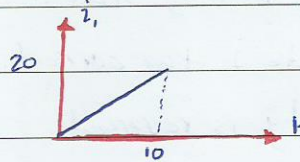
$$\bullet \dot{i}_1 = \frac{100}{0.05} t = 2000t$$




$$\bullet \dot{i}_1(10 \text{ ms}) = 20 \text{ A} = 2000(10 \text{ ms}) = 20 \text{ A}$$

$$\bullet t_2 = at_1 = 50 \text{ ms}$$

$$\bullet t_2 + t_1 = 60 \text{ ms} \quad \dot{i}_2(t_1 + t_2) = 0$$
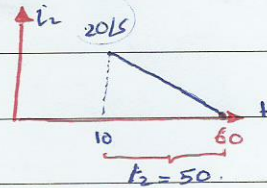
$$\bullet \dot{i}_2 = -\frac{V_s t}{aL_m} + I_0 \quad \text{but } I_0 = \dot{i}_1(t_1)/a = 20/5$$



$$\dot{i}_2 = -\frac{100(t+10\text{ms})}{5(0.05)} + 20/5$$

$$\dot{i}_2 = -400t$$




# Power Electronics Lecture (5)

Prof. Mohammed Zeki Khedher

Electrical Engineering Department of  
University of Jordan

## Diode Circuits or Uncontrolled Rectifier

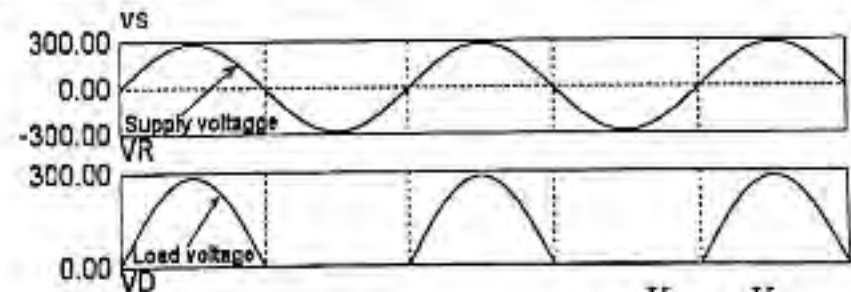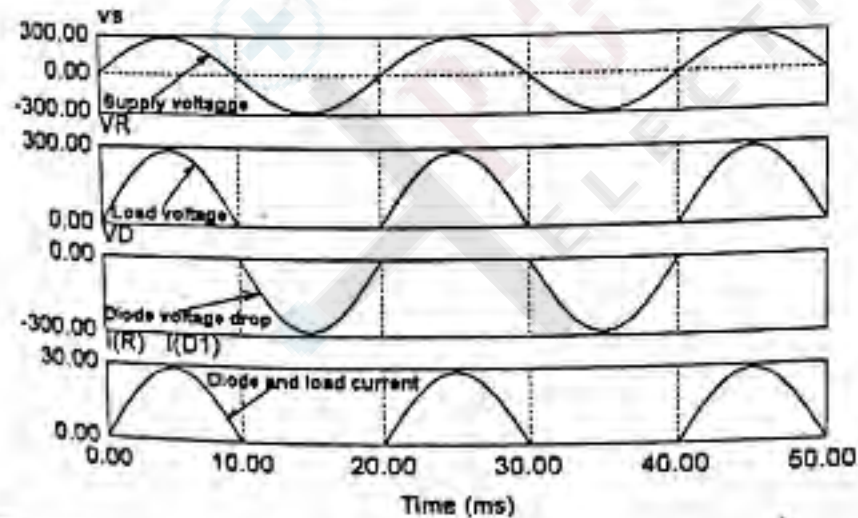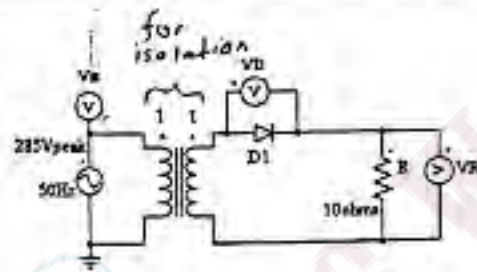**Rectification: The process of converting the alternating voltages and currents to direct currents**



$$V_{dc} = \frac{1}{2\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t = \frac{V_m}{\pi}$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{V_m}{\pi R}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t \, d\omega t} = \frac{V_m}{2}$$

$$I_{rms} = \frac{V_{rms}}{R} = \frac{V_m}{2R}$$

the load and diode currents  
supplied current

$$I_S = I_D = \frac{V_m}{2R}$$



$$P_{dc} = I_{dc}^2 R$$

$$P_{ac} = I_{rms}^2 R$$

$$V_{rms}^2 = V_{ac}^2 + V_{dc}^2$$



### Performance Parameters

$\eta = P_{dc} / P_{ac}$  rectification efficiency

$$V_{ac} = \sqrt{V_{rms}^2 - V_{dc}^2}$$

$FF = V_{rms} / V_{dc}$  form factor

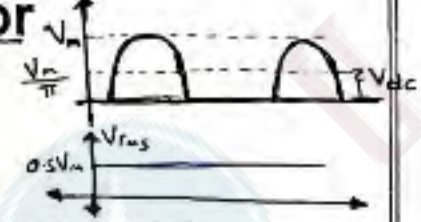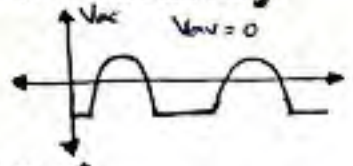$RF = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \sqrt{\frac{V_{rms}^2}{V_{dc}^2} - 1} = \sqrt{FF^2 - 1}$



wave form

voltage we supply is fundamental but harmonics appear in current doesn't add to power.

$$THD_i = \sqrt{\frac{I_S^2 - I_{S1}^2}{I_{S1}^2}} = \sqrt{\frac{I_S^2}{I_{S1}^2} - 1}$$

$$THD_v = \sqrt{\frac{V_S^2 - V_{S1}^2}{V_{S1}^2}} = \sqrt{\frac{V_S^2}{V_{S1}^2} - 1}$$

Load is not resistive

$$PF = \frac{P_{ac}}{V_S I_S} = \frac{V_S I_{S1} \cos \phi_1}{V_S I_S} = \frac{I_{S1}}{I_S} \cos \phi_1$$

= Distortion Factor \* Displacement

### Transformer Utilization Factor

$TUF = P_{dc} / N_s I_s$


the deviation of the utilization factor to the power factor give

$$\frac{PF}{TUF} = \frac{P_{ac}}{V_S I_S} = \frac{P_{ac}}{P_{dc}} \rightarrow \text{rectification factor efficiency.}$$

### Crest Factor

$$CF = I_{s-peak} / I_{s-rms}$$

↓  
Prac caused by the harmonics.

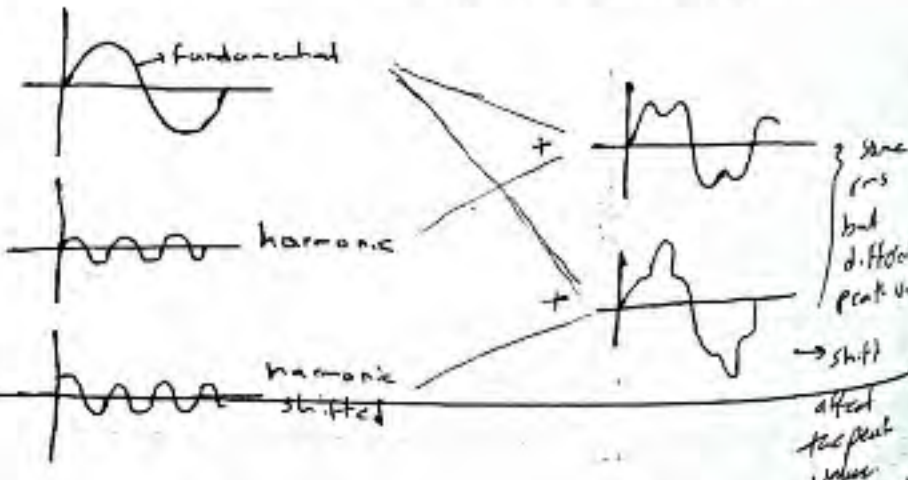

**EXAMPLE 1:** The rectifier shown in figure has a pure resistive load of  $R$ . Determine (a) The efficiency, (b) Form factor (c) Ripple factor (d) Peak inverse voltage (PIV) of diode  $D_1$ .

$$V_{dc} = \frac{1}{2\pi} \int_0^\pi V_m \sin(\omega t) d\omega t = \frac{V_m}{2\pi} (-\cos \pi - \cos(0)) = \frac{V_m}{\pi} \quad I_{dc} = \frac{V_{dc}}{R} = \frac{V_m}{\pi R}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^\pi (V_m \sin \omega t)^2 d\omega t} = \frac{V_m}{2} \quad I_{rms} = \frac{V_m}{2R}$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{V_{dc} \cdot I_{dc}}{V_{rms} \cdot I_{rms}} = \frac{\frac{V_m}{\pi} \cdot \frac{V_m}{\pi R}}{\frac{V_m}{2} \cdot \frac{V_m}{2R}} = 40.53\%$$

$$FF = \frac{V_{rms}}{V_{dc}} = \frac{2}{\frac{V_m}{\pi}} = \frac{\pi}{2} = 1.57$$

$$RF = \frac{V_{ac}}{V_{dc}} = \sqrt{FF^2 - 1} = \sqrt{1.57^2 - 1} = 1.211$$

It is clear from the Figure that the PIV is  $V_m$   
negative voltage

$$V_{dc} = V_m \times 0.5$$

$V_m \rightarrow$  rms value

- $VA = V_o I_o = 0.707 V_m \times 0.5 V_m / R$
- $TUF = P_{dc} / V_o I_o = (0.318)^2 / (0.707 \times 0.5) = 0.286$
- $CF = I_{s-peak} / I_s = 1 / 0.5 = 2$
- $PF = P_{ac} / VA = 0.5^2 / (0.707 \times 0.5) = 0.707$


The main disadvantages of half wave rectifier are:

- High ripple factor,
- Low rectification efficiency,
- Low transformer utilization factor, and,
- DC saturation of transformer secondary winding.



Half wave Rectifier with a Battery


↳ To charge a battery.

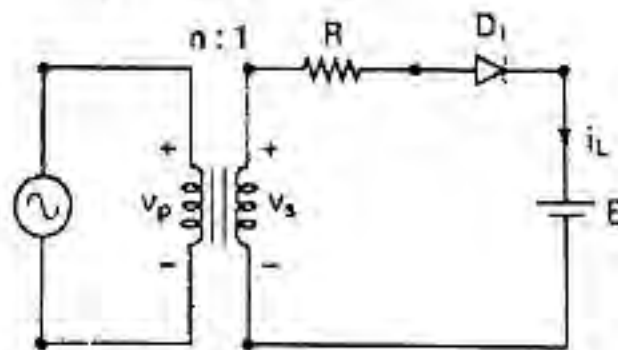

when  $V_s > E$   
 then the  $E$  will charge to reach  $V_s$

(a) Circuit



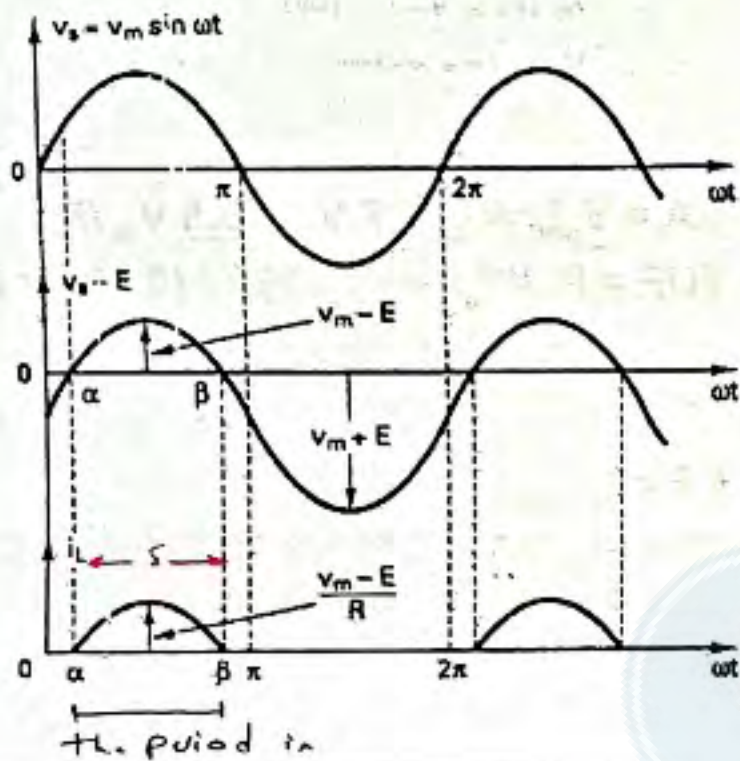

the period in which the battery is charged.

$$I_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\beta} \frac{V_m \sin \omega t - E}{R} \cdot dt$$

$$I_{dc} = \frac{1}{2\pi R} [2V_m \cos \alpha + 2E\alpha - \pi E]$$

↳  $\alpha$  in radians

③ what is the power rated for the resistor.

$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\beta} \left( \frac{V_m \sin \omega t - E}{R} \right)^2 \cdot dt}$$

$$I_{rms} = \sqrt{\frac{1}{2\pi R^2} \left[ \left[ \frac{V_m^2}{2} + E^2 \right] (\pi - 2\alpha) + \frac{V_m^2}{2} \sin 2\alpha - 4V_m E \cos \alpha \right]}$$

$$P_R = (I_{rms})^2 R$$

$$P_R = 8.2^2 \times 4.26$$

$$P_R = 286.4 \text{ W}$$

④ Power in battery

$$P_E = (I_{dc})^2 V_{dc}$$

why since harmonic not generate power

$$P_E = 12 \times 5 = 60 \text{ W}$$

→ period to charge

$$\frac{100}{60} = 1.66 \text{ Hz}$$

⑤ efficiency:

$$\eta = \frac{60}{60 + 286.4} = 17.32\%$$

$$V_m \sin \alpha = E$$

which gives

when the angle is  $> \alpha$  then we charge the battery

$$\alpha = \sin^{-1} \frac{E}{V_m}$$

Diode  $D_1$  will be turned off when  $v_s < E$  at

the period to charge the battery is

$$\alpha < \omega t < \pi - \alpha$$

$$\alpha < \omega t < \beta$$

$$\beta = \pi - \alpha$$

Example 2 A battery with  $E = 12 \text{ V}$  &  $100 \text{ WH}$   
 $I_{dc} = 5 \text{ A}$ ,  $V_{rms} = 120 \text{ V}$ ,  $60 \text{ Hz}$ ,  $\alpha = \frac{\pi}{6}$   
 what is the charge period  $S$ ?

$$\textcircled{1} V_m \sin \alpha = E$$

$$\sin \alpha = \frac{E}{V_m} \rightarrow \alpha = \sin^{-1} \left( \frac{12}{60\sqrt{2}} \right)$$

$$\alpha = 8.13^\circ = 0.1419 \text{ rad}$$

$$S = \pi - 2\alpha$$

$$S = 180 - 2 \times 8.13 = 163.74^\circ$$

$$V_m = \sqrt{2} \times 120 = 169.71$$

② what is the value of  $R$ ?

$$5 = \frac{1}{2\pi R} [2 \times 120 \times \cos(163.74) + 2 \times 12 \times 0.1419 - \pi \times 12]$$

$$R = 4.26 \Omega$$

$$PIV = V_m + E = 169.71 + 12 = 181.71 \text{ V}$$



# Power Electronics Lecture (6)

Prof. Mohammed Zeki Khedher  
Electrical Engineering Department of  
University of Jordan

note that at  $\omega t = 0$   $i$  full  $= 0$   
then:  $A = \frac{V_m}{Z} \sin \theta$

$$Z = \sqrt{R^2 + (\omega L)^2} \quad \tan \theta = \frac{\omega L}{R}$$

$$i(t) = \frac{V_m \sin(\omega t - \theta)}{Z} + A e^{-\frac{t}{L/R}}$$

$$i(\omega t) = \frac{V_m}{Z} \left( \frac{\sin(\omega t - \phi)}{\text{force response}} + \frac{\sin(\phi) e^{-\frac{\omega t}{\tau}}}{\text{natural response}} \right)$$

$$i(\beta) = \frac{V_m}{Z} \left( \sin(\beta - \phi) + \sin(\phi) e^{-\frac{\beta}{\tan \phi}} \right) = 0$$

↳ solve it using trial & error method.


$$V_{dc} = \frac{V_m}{2\pi} \int_0^\beta \sin \omega t \, d\omega t = \frac{V_m}{2\pi} (1 - \cos \beta)$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^\beta (V_m \sin \omega t)^2 \, d\omega t} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\beta + 0.5(-\sin(2\beta))}$$

$$I_{dc} = \frac{1}{2\pi} \int_0^\beta i(t) \, dt = \frac{1}{2\pi} \int_0^\beta \frac{V_m}{Z} (\sin(\omega t - \phi) + \sin(\phi) e^{-\frac{\omega t}{\tau}}) \, dt$$

note that at  $\beta$  point the voltage across the inductance equal to the voltage of the source so that  $i(\omega t) = 0$  |  $i(\beta) = 0$  |  $\beta$  distinguish angle.
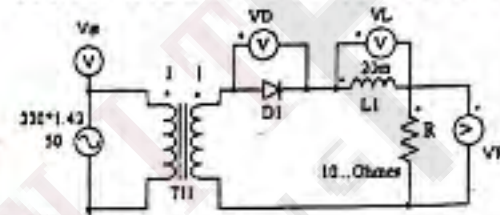
## Half Wave Diode Rectifier With R-L Load




\* current in the inductance  $\rightarrow$  lags after the voltage (lag)

↳ lag the  $V_s$  voltage

$V_L$  is the slope of the current

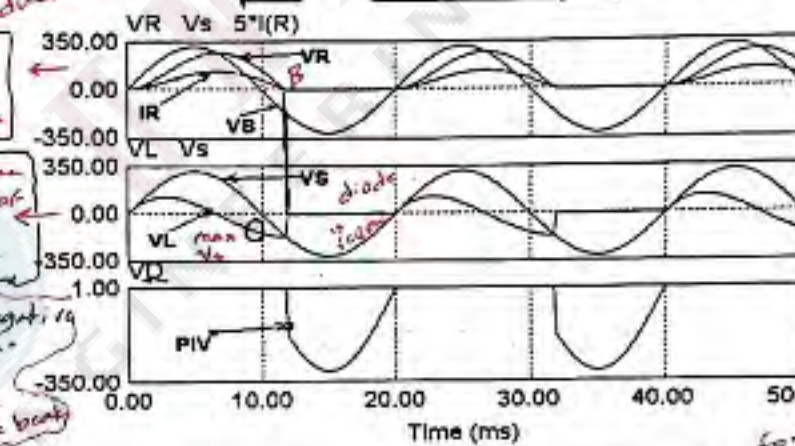it goes negative since the slope is negative after the beta




\* Diode off when current through it is zero.

$$* V_L = L \frac{di}{dt} + Ri$$

$$V_m \sin \omega t = Ri + L \frac{di}{dt}$$



$$i(t) = i_f(t) + i_n(t)$$

force response      natural response

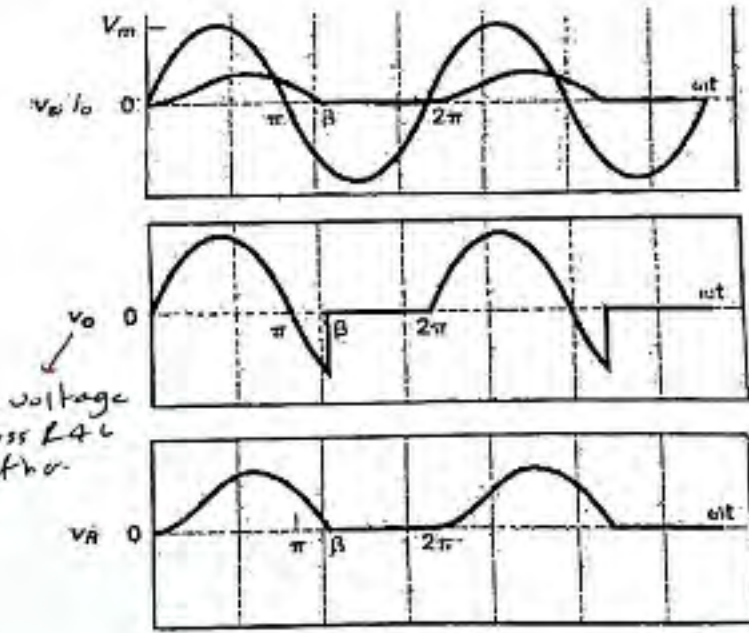

the voltage across R & L together.



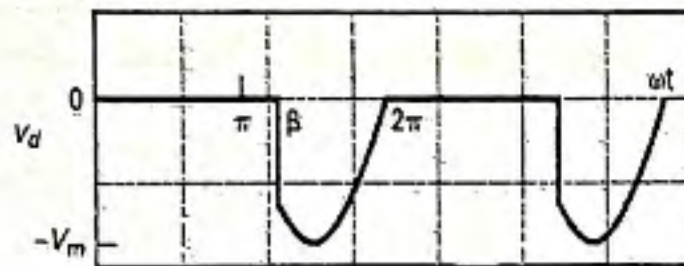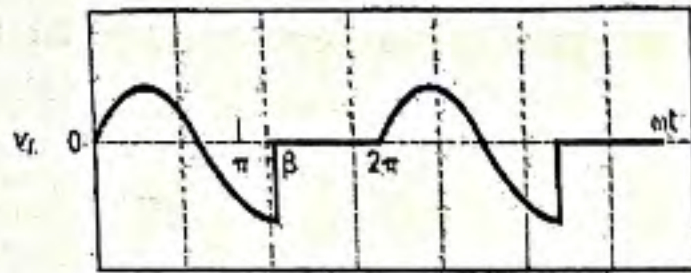

↳ note that  $v_o$  is the complement of the output voltage since it's in reverse period.

$$i(t) = i_f(t) + i_n(t).$$

$$i_f(t) = \left(\frac{V_m}{Z}\right) \sin(\omega t - \theta)$$

$$\text{where } Z = \sqrt{R^2 + (\omega L)^2} \text{ and } \theta = \tan^{-1}\left(\frac{\omega L}{R}\right).$$

$$Ri(t) + L \frac{di(t)}{dt} = 0.$$

For this first-order circuit, the natural response has the form

$$i_n(t) = Ae^{-t/\tau}$$

$$i(t) = i_f(t) + i_n(t) = \frac{V_m}{Z} \sin(\omega t - \theta) + Ae^{-t/\tau}$$

$$i(0) = \frac{V_m}{Z} \sin(0 - \theta) + Ae^0 = 0$$

$$A = -\frac{V_m}{Z} \sin(-\theta) = \frac{V_m}{Z} \sin(\theta).$$

Substituting for  $A$  in Eq. 3-9,

$$i(t) = \frac{V_m}{Z} \sin(\omega t - \theta) + \frac{V_m}{Z} \sin(\theta) e^{-t/\tau}$$

$$= \frac{V_m}{Z} \left[ \sin(\omega t - \theta) + \sin(\theta) e^{-t/\tau} \right].$$

$$\begin{aligned} i(\omega t) &= \frac{V_m}{Z} \sin(\omega t - \theta) + \frac{V_m}{Z} \sin(\theta) e^{-\omega t/\omega\tau} \\ &= \frac{V_m}{Z} \left[ \sin(\omega t - \theta) + \sin(\theta) e^{-\omega t/\omega\tau} \right]. \end{aligned}$$

$$i(\beta) = \frac{V_m}{Z} [\sin(\beta - \theta)] + \frac{V_m}{Z} \sin(\theta) e^{-\beta/\omega\tau} = 0$$

$$\sin(\beta - \theta) + \sin(\theta) e^{-\beta/\omega\tau} = 0$$

*→ solve it use upper curve in the lower slide.*

$$i(\omega t) = \begin{cases} \frac{V_m}{Z} \sin(\omega t - \theta) + \frac{V_m}{Z} \sin(\theta) e^{-\omega t/\omega\tau} & \text{for } 0 \leq \omega t \leq \beta \\ 0 & \text{for } \beta \leq \omega t \leq 2\pi \end{cases}$$

*→ diode is reverse current is zero.*

where  $Z = \sqrt{R^2 + (\omega L)^2}$ ,  $\theta = \tan^{-1} \left( \frac{\omega L}{R} \right)$ , and  $\tau = \frac{L}{R}$ .

$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i^2(\omega t) d(\omega t)} = \sqrt{\frac{1}{2\pi} \int_0^{\beta} i^2(\omega t) d(\omega t)}$$


more complex expression than that for voltage

$$I_{av} = \frac{1}{2\pi} \int_0^{\beta} i(\omega t) d(\omega t)$$

Half wave Single phase rectifier

Distinction angle against  $\frac{\omega t}{\pi}$


$$\frac{E}{V} = \sin \alpha$$

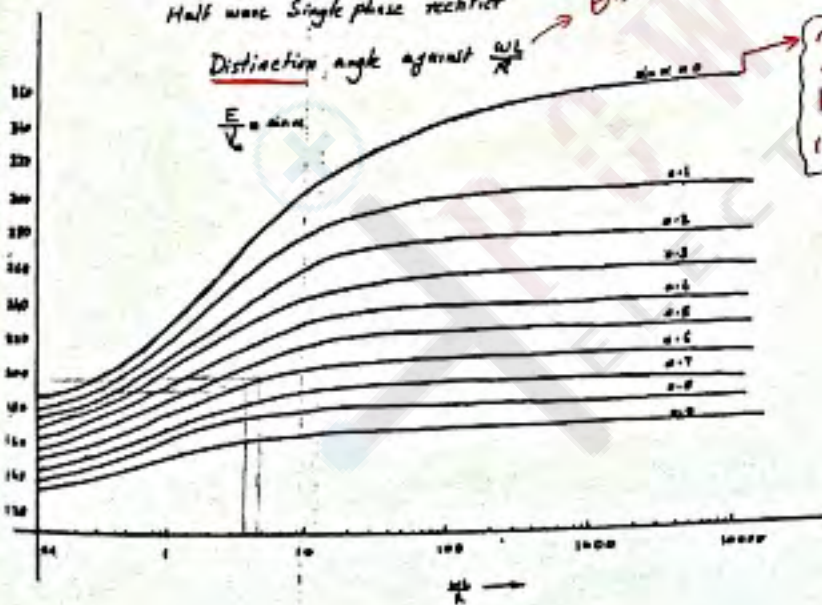


*note that we will use this to solve the  $i(\beta) = 0$*
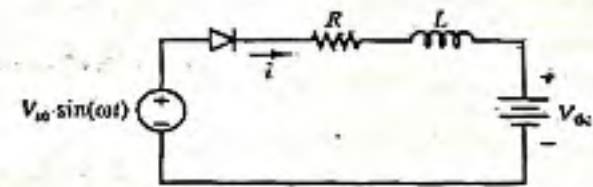
### Supplying Power to a dc Source from an ac Source


→ charging battery using RL rectifying circuit



(a)

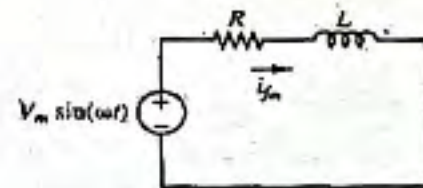

(b)

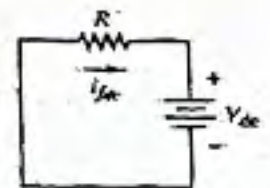

(c)




$i \neq 0$  at  $\omega t = \alpha$

$$V_m \sin \alpha = V_{dc}$$

$$0 = \frac{V_m}{Z} \sin(\alpha - \theta) - \frac{V_{dc}}{R} + Ae^{-\frac{\omega t}{\tau}}$$
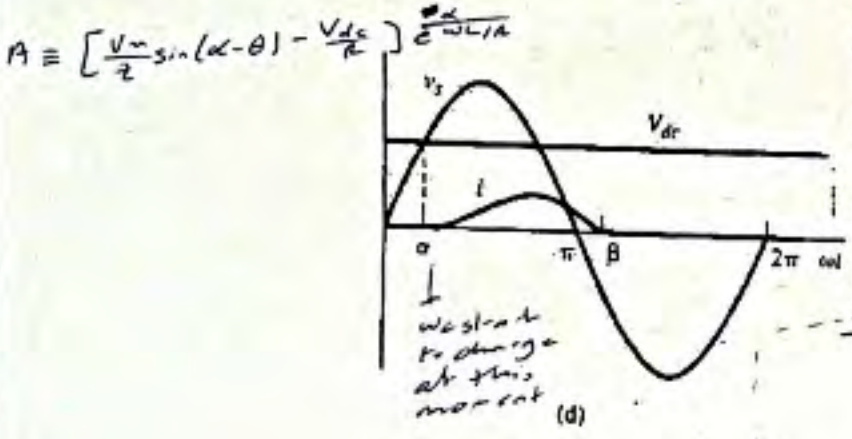
$$\alpha = \sin^{-1} \left( \frac{V_{dc}}{V_m} \right)$$



Example:  $R=2\Omega, L=20\text{mH}, V_{dc}=100\text{V}, V_s=120\sqrt{2}\text{V}$   
 $f=60\text{Hz}$

$$\sin \alpha = \frac{V_{dc}}{V_m} = \frac{100}{120\sqrt{2}} = \frac{100}{169.7} = 0.589$$

$$\alpha = 36.1^\circ = 0.63 \text{ rad/sec}$$

$$\frac{\omega L}{R} = \frac{2\pi \cdot 60 \cdot 20\text{m}}{2} = 3.77$$

$$\rightarrow \text{From graph } \beta = 193^\circ$$

$$i(\omega t) = 21.8 \sin(\omega t - 1.31) - 50 + 75.3 e^{-\frac{\omega t}{3.77}}$$

$$I_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\beta} i(\omega t) \cdot d\omega t$$

$$I_{dc} = 2.25 \text{ A}$$

$$\rightarrow I_{rms} = \frac{1}{2\pi} \int_{\alpha}^{\beta} i^2(\omega t) \cdot d\omega t = 3.98 \text{ A}$$

$$V_m \sin(\omega t) = Ri(t) + L \frac{di(t)}{dt} + V_{dc}$$

$$i(t) = i_p(t) + i_h(t)$$

$$i_p(t) = \frac{V_m}{Z} \sin(\omega t - \theta) - \frac{V_{dc}}{R}$$

$$i_h(t) = Ae^{-t/\tau}$$

$$i(\omega t) = \begin{cases} \frac{V_m}{Z} \sin(\omega t - \theta) - \frac{V_{dc}}{R} + Ae^{-\omega t/\tau} & \text{for } \alpha \leq \omega t \leq \beta \\ 0 & \text{otherwise} \end{cases}$$

$$P_E = (100)(2.25) = 225 \text{ watt}$$

$$P_R = (3.98)^2 \cdot 2 = 31.2 \text{ watt}$$

$P_L = 0 \rightarrow$  Inductor stores energy, takes it back when voltage changes.

$$I = \left( -\frac{V_m}{Z} \sin(\alpha - \theta) + \frac{V_{dc}}{R} \right) e^{\alpha/\omega\tau}$$

$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\beta} i^2(\omega t) d(\omega t)}$$

$$P_{dc} = IV_{dc}$$

$$\eta = \frac{225}{225 + 31.2} = \dots$$

$$P.F. = \frac{256.2}{(3.98)(120)} = 0.54$$


$$TUF = \frac{225}{(3.98)(120)}$$

where  $I$  is the average current, that is,


$$I = \frac{1}{2\pi} \int_{\alpha}^{\beta} i(\omega t) d(\omega t)$$

without free wheeling diode then the previous sketches are considered.




with free wheeling diode:

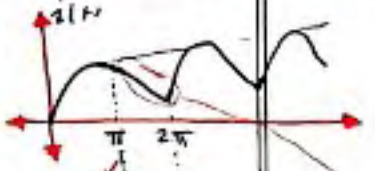

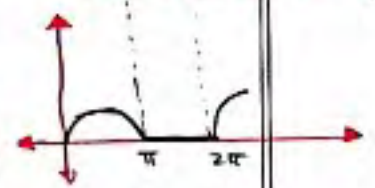$V_s$  negative & diode 2 is on now so the current is exponential.




## FREEWHEELING DIODE

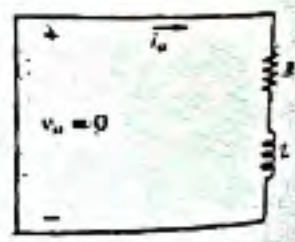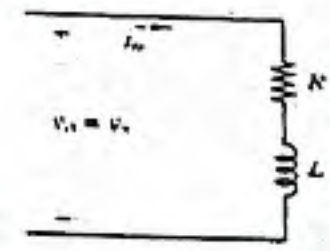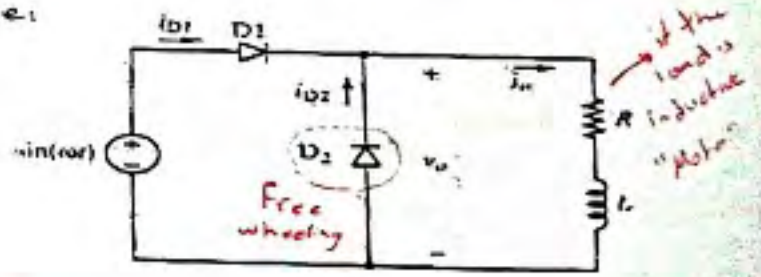



note that the main component in the total current is the fundamental & the harmonic is reduced due to two reason → (1) because we divided into  $x_n$  which depend on the frequency which doubled with harmonics
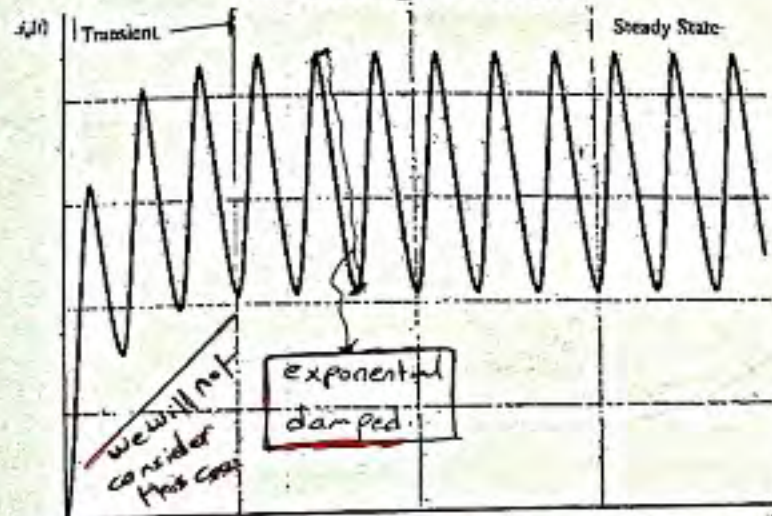
## Load Current transient to steady state



$$a_0 = \frac{1}{2\pi} \int_0^{2\pi} V_m \sin(\omega t) dt$$

$$a_0 = \frac{V_m}{\pi}$$



$$a_n = \frac{1}{\pi} \int_0^{\pi} V_m \sin(\omega t) \cos(n\omega t) dt$$

$$a_n = \frac{V_m}{2\pi} \int_0^{\pi} \sin(2n\omega t) dt$$


Result

$$i(t) = \frac{V_m}{R} + \frac{V_m}{2} \sin(\omega t) - \sum_{n=2,4,6} \frac{2V_m}{(n^2-1)\pi} \cos(n\omega t)$$

Find Fourier Series

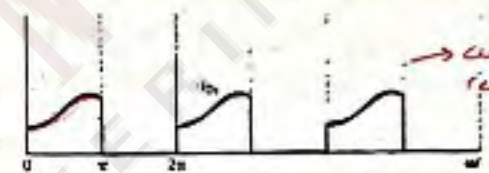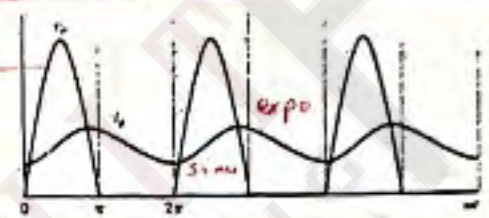

current in the rectification diode

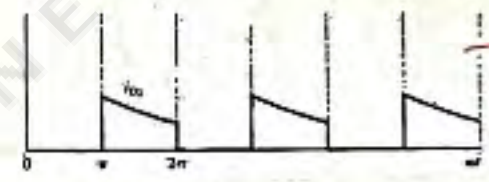

current in the freewheeling diode

we want to reduce the fluctuation by increasing L

## Reducing Load Current Harmonics

$$i_n(t) \approx I_n = \frac{V_n}{R} = \frac{V_m}{\pi R} \left( \frac{L}{R} \rightarrow \infty \right)$$

Example 2-

$R = 2\Omega$ ,  $L = 25mH$ ,  $V_m = 100$   
 $f = 60Hz$  find

$$V_{dc} = \frac{V_m}{\pi} = \frac{100}{\pi} = 31.8V$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{31.8}{2} = 15.9A$$

f	$V_n$	$X_n$	$Z_n$	$I_n$
0	31.8	0	2	15.9
60	50	$2\pi(0.025)$ 60	9.63	5.19
120	21.2	$2\pi(0.025)$ (120)	18.96	1.12
240	4.24	$2\pi(0.025)$ (240)	37.35	0.11

$$i(t) = 15.9 + 5.19 \sin(\omega t + \theta_1) + 1.12 \sin(\omega t + \theta_2) + 0.11 \sin(\omega t + \theta_3)$$

$$I_{rms} = \sqrt{(15.9)^2 + (5.19)^2 + (1.12)^2 + (0.11)^2}$$

$$I_{rms} = 16.34A$$

## Example Half wave with freewheeling diode

source is 240 V rms at 60 Hz and  $R = 8\Omega$ . (a) Assume  $L$  is infinite for practical purposes. Determine the power absorbed by the load and the power factor as seen by the source. State  $V_m$ ,  $I_{dc}$ , and  $I_{rms}$ . (b) Determine the average current in each diode. (c) Determine  $L$  such that the peak-to-peak current is no more than 10% of the average current.

$$\frac{V_m}{2} \rightarrow L = 0.57H$$

$$i_0(\omega) = I_0 = \frac{V_0}{R} = \frac{V_m/\pi}{R} = \frac{240\sqrt{2}/\pi}{8} = 13.5A = I_{rms}$$

Power in the resistor is

$$P = (I_{rms})^2 R = (13.5)^2 \cdot 8 = 1459W$$

Source rms current is computed from

$$I_{s,rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (13.5)^2 d(\omega t)} = 9.55A$$

The power factor is

$$PF = \frac{P}{V_{s,rms} I_{s,rms}} = \frac{1459}{(240)(9.55)} = 0.637$$

Each diode conducts for one-half of the time. Average current for each diode is  $I_0/2 = 13.5/2 = 6.75A$ .

$$\Delta I_0 = 2I_1$$

$$I_{01} = I_{02} = \frac{16.34}{\sqrt{2}}$$

$$I_{rms} = 11.55A$$

$$P = I^2 R$$


$$P = 16.34^2 (2)$$

$$P = 534W$$



# Half wave rectifier with capacitor filter


①  $\alpha \rightarrow \pi/2$

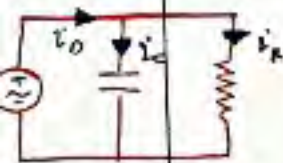


②  $\pi \rightarrow \theta$



③  $\theta \rightarrow \alpha + 2\pi$

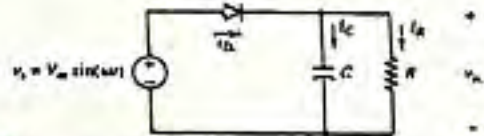

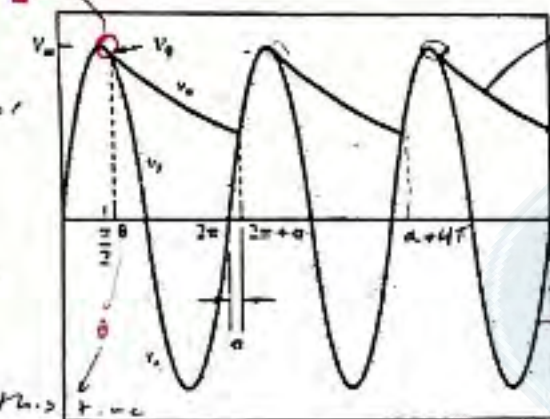at this region the current in the capacitor is  $-i_C$  so the  $i_C = i_C + i_D$  in this region at the peak  $i_C = 0$



when  $v_o > v_s$  so the diode is off  $\Delta v_o$  hence the voltage in the capacitor is dropped in the resistor & then recharge when  $v_s > v_o$

at this time the current in diode = 0

$$v_o(\omega t) = \begin{cases} V_m \sin \omega t & \text{diode on} \\ V_c e^{-(\omega t - \theta)/\omega RC} & \text{diode off} \end{cases}$$

$$\frac{d}{d(\omega t)} (V_m \sin \omega t) = V_m \cos \omega t$$

and


$$\frac{d}{d(\omega t)} (V_m \sin \theta e^{-(\omega t - \theta)/\omega RC}) = V_m \sin \theta \left( -\frac{1}{\omega RC} \right) e^{-(\omega t - \theta)/\omega RC}$$

At  $\omega t = \theta$ , the slopes of the voltage functions are equal:

$$V_m \cos \theta = \frac{V_m \sin \theta}{-\omega RC} e^{-(\theta - \theta)/\omega RC} = \frac{V_m \sin \theta}{-\omega RC}$$

$$\frac{V_m \cos \theta}{V_m \sin \theta} = \frac{1}{-\omega RC}$$
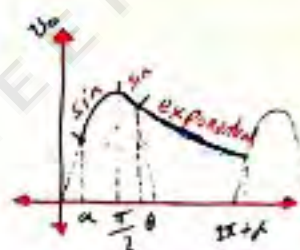
$$\frac{1}{\tan \theta} = \frac{1}{-\omega RC}$$



Solving for  $\theta$  and expressing  $\theta$  so it is in the proper quadrant.

$$\theta = \tan^{-1}(-\omega RC) = -\tan^{-1}(\omega RC) + \pi$$

In practical circuits where the time constant is large,

$$\theta \approx \frac{\pi}{2} \quad \text{and} \quad V_m \sin \theta \approx V_m$$

$$V_m \sin(2\pi + \alpha) = (V_m \sin \theta) e^{-(2\pi + \alpha - \theta)/\omega RC}$$

$$\sin(\alpha) - (\sin \theta) e^{-(2\pi + \alpha - \theta)/\omega RC} = 0$$

→ solve by graph

$$i_C(\omega t) = \omega C \frac{dv_o(\omega t)}{d(\omega t)}$$

$$i_C(\omega t) = \begin{cases} \frac{V_m \sin \theta}{R} e^{-(\omega t - \theta)/\omega RC} & \text{for } \theta \leq \omega t \leq 2\pi + \alpha \\ & \text{(diode off)} \\ \omega C V_m \cos(\omega t) & \text{for } 2\pi + \alpha \leq \omega t \leq 2\pi \\ & \text{(diode on)} \end{cases}$$

$$i_s = i_D = i_R + i_C$$



$$i_{C, \text{peak}} = \omega C V_m \cos(2\pi + \alpha) = \omega C V_m \cos \alpha.$$

Resistor current at  $\omega t = 2\pi + \alpha$  is obtained from Eq. 3-37:

$$i_R(2\omega t + \alpha) = \frac{V_m \sin(2\omega t + \alpha)}{R} = \frac{V_m \sin \alpha}{R}.$$

Peak diode current is

$$I_{D, \text{peak}} = \omega C V_m \cos \alpha + \frac{V_m \sin \alpha}{R} = V_m \left( \omega C \cos \alpha + \frac{\sin \alpha}{R} \right).$$

$$\Delta V_o = V_m - V_m \sin \alpha = V_m (1 - \sin \alpha).$$

$$\text{If } V_o \approx V_m$$


$\theta \approx \pi/2$ , then

at  $\alpha = \pi/2$  is

$$v_o(2\pi + \alpha) \approx V_m e^{-(2\pi + \pi/2 - \pi/2)/\omega RC} = V_m e^{-2\pi/\omega RC}.$$

The ripple voltage can then be approximated as
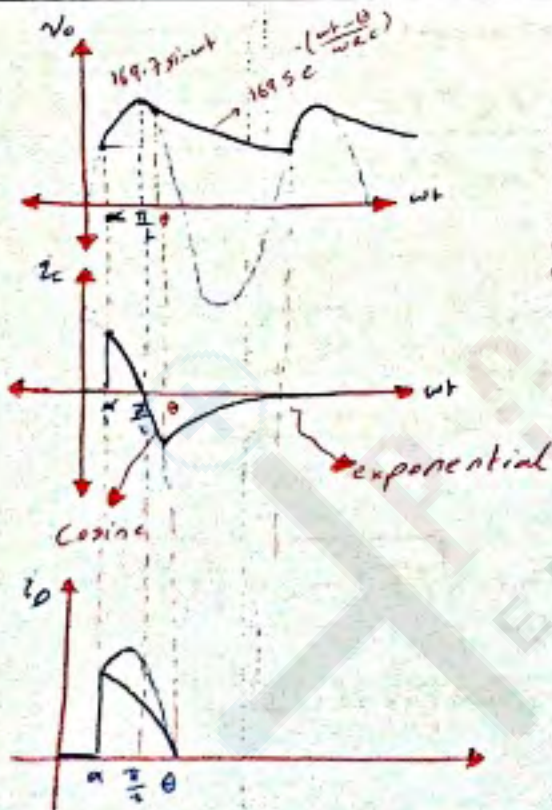
$$\Delta V_o \approx V_m - V_m e^{-2\pi/\omega RC} = V_m (1 - e^{-2\pi/\omega RC}).$$



• Example :

$$120 \text{ Vrms}, R = 500 \Omega, f = 60 \text{ Hz}, C = 100 \mu\text{F}$$

$$V_m = 120 \sqrt{2} = 169.7 \text{ V}$$

$$\theta = \tan^{-1}(\omega RC) = \tan^{-1}(2\pi(60)(100 \mu)(500))$$

$$\theta = 93^\circ$$

• from graph:  $\alpha = 48^\circ$

$$V_o \sin(\theta) = 169.7 \sin(93) = 169.5$$

$$\Delta V = V_m (1 - \sin \alpha)$$

$$\Delta V = 43 \text{ V}$$

$$i_{D, \text{peak}} = 169.7 (2\pi \cdot 60 + 100 \mu) = \cos 48 + \frac{51 \cdot 48}{500}$$

$$= 24.5 \text{ A}$$

• want ripple  $< 10\% V_m$  then find C

$$\alpha \approx \sin^{-1} \left( 1 - \frac{\Delta V}{V_m} \right) \longrightarrow C = 3333 \mu\text{F}$$

$$\Delta V / V_m \approx \frac{1}{fRC} \text{ with } 8\% \text{ error}$$



# Power Electronics Lecture (7)

Prof. Mohammed Zeki Khedher  
Electrical Engineering Department of  
University of Jordan

Handwritten notes and calculations:

$$P_{avg} = \frac{V_m}{\pi} \times \frac{V_m}{\pi} = \frac{V_m^2}{\pi^2}$$


$$I_{avg} = \frac{V_m}{\pi R}$$

$$P_{avg} = I_{avg}^2 R = \left(\frac{V_m}{\pi R}\right)^2 R = \frac{V_m^2}{\pi^2}$$



## Single-Phase Full-Wave Diode Rectifier

Center-Tap Diode Rectifier two half wave

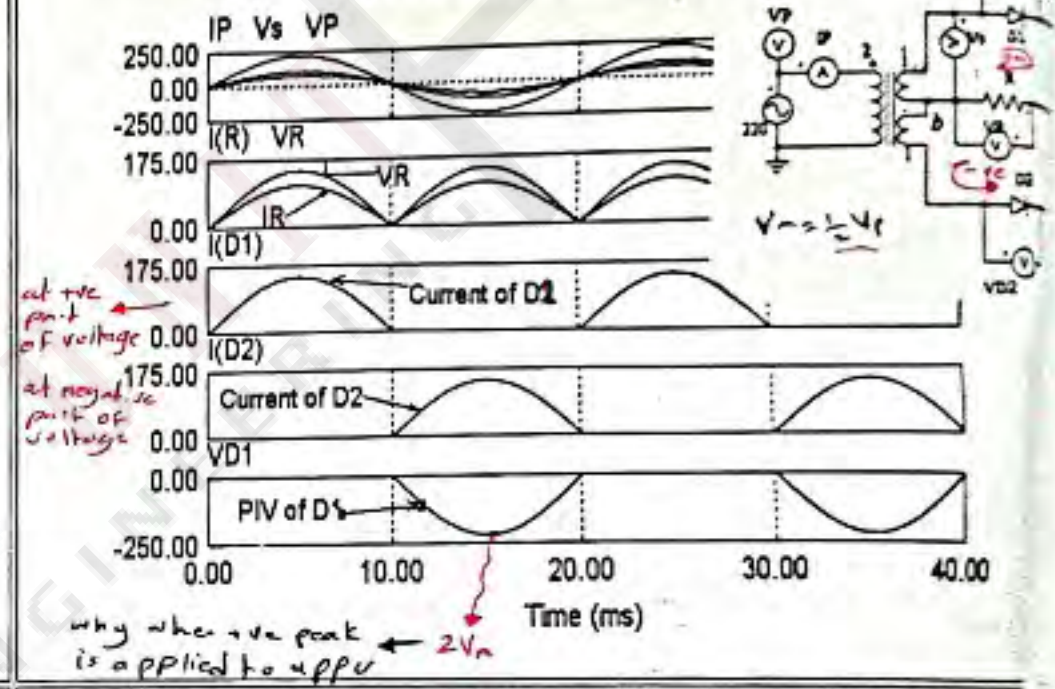

$$V_{dc} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t = \frac{2V_m}{\pi}$$

$$I_{dc} = \frac{2V_m}{\pi R}$$

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} (V_m \sin \omega t)^2 \, d\omega t} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{V_m}{\sqrt{2} R}$$

PIV of each diode =  $\frac{2V_m}{\pi}$  since the square of it as the square of the sine.

$$I_S = I_D = \frac{V_m}{2R}$$

**Example 3.** The rectifier in Fig.2.8 has a purely resistive load of  $R$ . Determine (a) The efficiency, (b) Form factor (c) Ripple factor (d) TUF (e) Peak inverse voltage (PIV) of diode D1 and (f) Crest factor of transformer secondary current.

diode then the voltage at the right most node is  $+V_m$  & at the left node to second diode is  $-ve V_m$

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{V_{dc} * I_{dc}}{V_{rms} * I_{rms}} = \frac{\frac{2V_m}{\pi} * \frac{2V_m}{\pi R}}{\frac{V_m}{\sqrt{2}} * \frac{V_m}{\sqrt{2} R}} = 81.0\%$$

increased with respect to half wave

$$FF = \frac{V_{rms}}{V_{dc}} = \frac{\frac{V_m}{\sqrt{2}}}{\frac{2V_m}{\pi}} = \frac{\pi}{2\sqrt{2}} = 1.11$$


$$RF = \frac{V_{ac}}{V_{dc}} = \sqrt{FF^2 - 1} = \sqrt{1.11^2 - 1} = 0.48$$

The PIV is  $2V_m$



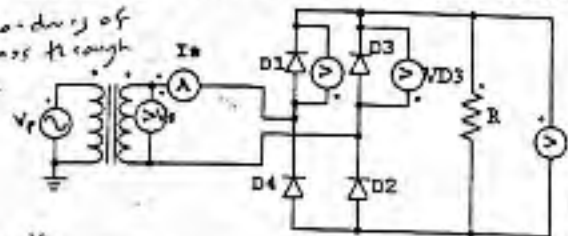
### Single-Phase Full Bridge Diode Rectifier With Resistive Load

in this the secondary of transformer will pass through it the +ve & -ve current



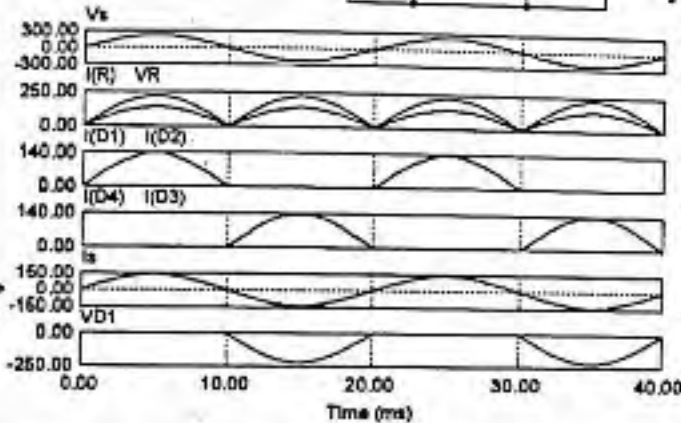- $V_m$  here equal to  $V_p$
- the voltage applied to one diode is  $V_m$  & for two diode is  $2V_m$
- volta- per for this case is same for primary & secondary while not for the previous



current in transformer

Example:  $V_m = 100V, 60Hz, R_s = 10\Omega, L = 10mH, \text{ Bridge}$

with 1- $\phi$  unideal bridge

$$V_{dr} = \frac{2 \times 100}{\pi} = 63.7V \quad I_{dc} = \frac{63.7}{10} = 6.37$$

$\frac{1}{2}$	$\frac{V_m}{\pi}$	$\frac{X_m}{2 \times 2\pi \times 60 \times 10^{-3}}$	$\frac{Z_s}{49.2 \times 10^{-3}}$	$\frac{I_s}{7.34}$
4	8.44	15.1	0.47	

$$V_L(t) = V_{dc} + \sum_{n=2,4,\dots} (a_n \cos n\omega t + b_n \sin n\omega t)$$

$$I_{rms} = \sqrt{(6.37)^2 + \left(\frac{8.44}{\sqrt{2}}\right)^2 + \left(\frac{15.1}{\sqrt{2}}\right)^2 + \dots}$$

$$V_{dc} = \frac{1}{2\pi} \int_0^{2\pi} v_L(t) d(\omega t) = \frac{2}{2\pi} \int_0^{\pi} V_m \sin \omega t d(\omega t) = \frac{2V_m}{\pi}$$

$$P.F. = 0.96 = \frac{P_{ac}}{V_L I_{rms}}$$





$$I_{o,dc} = \frac{6.37}{2}$$

$$I_{pac} = \frac{I_{rms}}{\sqrt{2}}$$

$$a_n = \frac{4V_m}{\pi} \sum_{n=1,3,5,\dots} \frac{-1}{(n-1)(n+1)}$$

$$b_n = \frac{1}{\pi} \int_0^{2\pi} v_L \sin n\omega t d(\omega t) = \frac{2}{\pi} \int_0^{\pi} V_m \sin \omega t \sin n\omega t d(\omega t) = 0$$

Substituting the values of  $a_n$  and  $b_n$ , the expression for the output voltage is
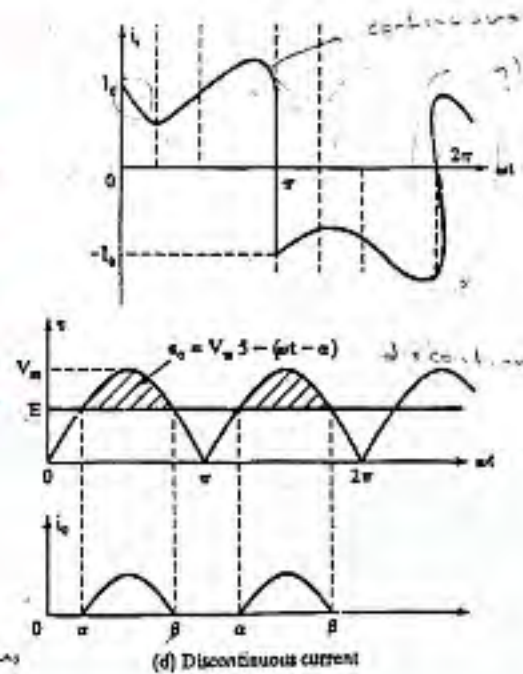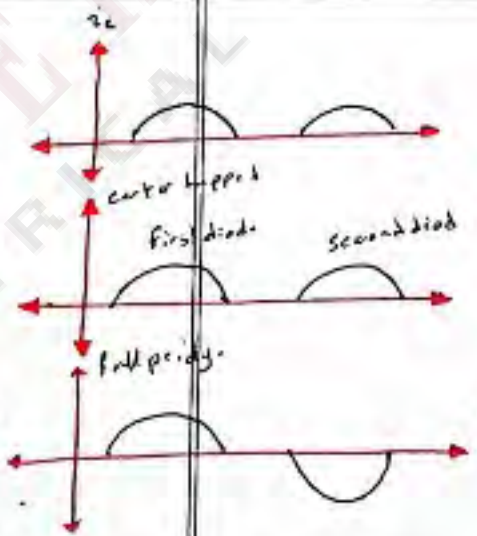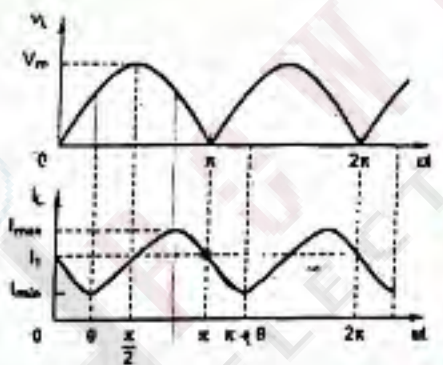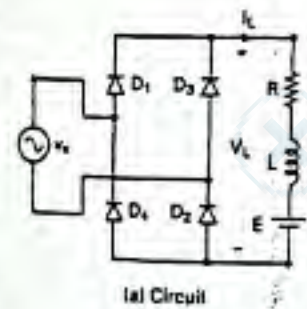
$$v_L(t) = \frac{2V_m}{\pi} - \frac{4V_m}{3\pi} \cos 2\omega t - \frac{4V_m}{15\pi} \cos 4\omega t - \frac{4V_m}{15\pi} \cos 6\omega t - \dots$$


Continuous if there is battery &  $\beta > \alpha + \pi$   
discontinuous if  $\beta < \alpha + \pi$

$$i_D = \frac{\sqrt{2} V_s}{Z} \sin(\omega t - \theta) + A_1 e^{-(R/L)t} - \frac{E}{R}$$

• note that if we have an inductor & resistor without battery then the current is continuous

(d) Discontinuous current





\* Example 1

$V_{rms} = 120V$   
 $R = 2\Omega$   
 $L = 10mH$   
 $V_{dc} = 80V$

$\alpha = \sin^{-1}\left(\frac{80}{\sqrt{2} \cdot 120}\right)$   
 $\alpha = 28^\circ$



$\beta = 190^\circ$

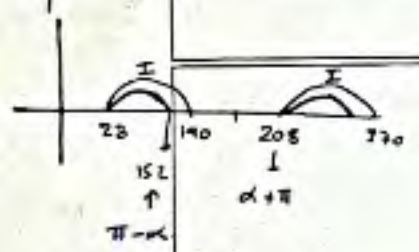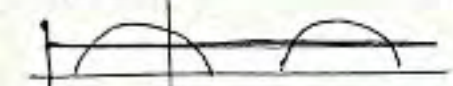

→ discontinuous.  
 note that we can solve the continuous by fourier series for the new voltage

**Case 1: continuous load current.**

at  $\omega t = \pi$ ,  $i_L = I_1$ .

$A_1 = \left(I_0 + \frac{E}{R} - \frac{\sqrt{2} V_s}{Z} \sin \theta\right) e^{jR/L \cdot \pi / \omega}$

$i_0 = \frac{\sqrt{2} V_s}{Z} \sin(\omega t - \theta) + \left(I_0 + \frac{E}{R} - \frac{\sqrt{2} V_s}{Z} \sin \theta\right) e^{jR/L \cdot \omega t} - \frac{E}{R}$

$\frac{(V_m)^2}{R}$   
 $\frac{V_m}{\sqrt{2}} \frac{V_m}{R}$

$i_0(\omega t = 0) = i_0(\omega t = \pi)$ . That is,  $i_0(\omega t = 0) = I_0$

$I_0 = \frac{\sqrt{2} V_s}{Z} \sin \theta \frac{1 + e^{-jR/L \cdot \pi / \omega}}{1 - e^{-jR/L \cdot \pi / \omega}} - \frac{E}{R}$  for  $I_0 \geq 0$

for ratio tapped the power factor is  $\frac{1}{\sqrt{2}}$

$i_0 = \frac{\sqrt{2} V_s}{Z} \left[ \sin(\omega t - \theta) + \frac{2}{1 - e^{-jR/L \cdot \pi / \omega}} \sin \theta e^{-j2k\omega t} \right] - \frac{E}{R}$

for  $0 \leq \omega t \leq \pi$  and  $I_0 \geq 0$

$I_r = \left[ \frac{1}{2\pi} \int_0^\pi i_0^2 d(\omega t) \right]^{1/2}$

$I_{rms} = (I_r^2 + I_0^2)^{1/2} = \sqrt{2} \cdot I_r$

$I_d = \frac{1}{2\pi} \int_0^\pi i_0 d(\omega t)$

**Case 2: discontinuous load current.**

$\alpha = \sin^{-1} \frac{E}{V_m}$

At  $\omega t = \alpha$ ,  $i_L(\omega t) = 0$  and Eq. (3-65) gives

$A_1 = \left[ \frac{E}{R} - \frac{\sqrt{2} V_s}{Z} \sin(\alpha - \theta) \right] e^{jR/L \cdot \alpha / \omega}$

which, after substituting in Eq. (3-65), yields the load current

$i_0 = \frac{\sqrt{2} V_s}{Z} \sin(\omega t - \theta) + \left[ \frac{E}{R} - \frac{\sqrt{2} V_s}{Z} \sin(\alpha - \theta) \right] e^{jR/L \cdot \omega t - \alpha}$

At  $\omega t = \beta$ , the current falls to zero, and  $i_0(\omega t = \beta) = 0$ . That is,

$\frac{\sqrt{2} V_s}{Z} \sin(\beta - \theta) + \left[ \frac{E}{R} - \frac{\sqrt{2} V_s}{Z} \sin(\alpha - \theta) \right] e^{jR/L \cdot \beta - \alpha} = 0$   
 $-E/R$

**Example 4** single-phase diode bridge rectifier has a purely resistive load of  $R=15$  ohms and,  $V_S=300 \sin 314 t$  and unity transform ratio. Determine (a) The efficiency, (b) Form factor, (c) Ripple factor, (d) The peak inverse voltage, (PIV) of each diode, and, (e) power factor.

$V_{dc} = \frac{1}{\pi} \int_0^\pi V_m \sin \alpha x dx = \frac{2V_m}{\pi} = 190.956 V$        $I_{dc} = \frac{2V_m}{\pi R} = 12.73 A$

$V_{rms} = \left[ \frac{1}{\pi} \int_0^\pi (V_m \sin \alpha x)^2 dx \right]^{1/2} = \frac{V_m}{\sqrt{2}} = 212.132 V$



$\eta = \frac{P_{dc}}{P_{ac}} = \frac{V_{dc} I_{dc}}{V_{rms} I_{rms}} = 81.06 \%$        $FF = \frac{V_{rms}}{V_{dc}} = 1.11$

$RF = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \sqrt{\frac{V_{rms}^2}{V_{dc}^2} - 1} = \sqrt{FF^2 - 1} = 0.482$       The PIV = 300V

**Input power factor**  $\frac{\text{Real Power}}{\text{Apperant Power}} = \frac{V_S I_S \cos \theta}{V_S I_S}$

→  $V_{dc}$   
 Diode V  
 source V



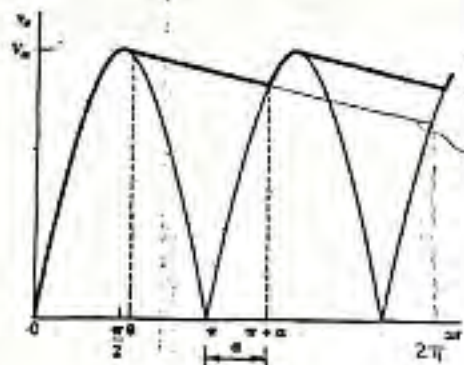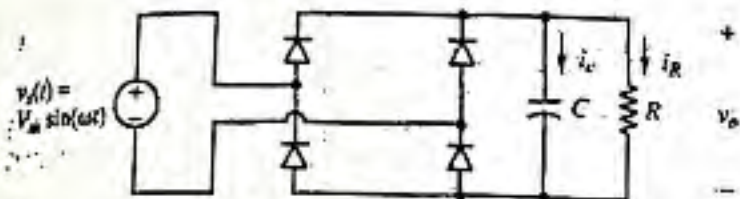

same equations for half wave but with replace  $2\pi$  by  $\pi$ .  
is half wave rectifier


Example:

$R = 500 \Omega$ ,  $C = 100 \mu F$   
 $V = 160 V$ ,  $f = 60 Hz$

$$v_o(\omega t) = \begin{cases} |V_m \sin \omega t| & \text{one diode pair on} \\ (V_m \sin \theta) e^{-(\pi + \alpha - \theta)/\omega RC} & \text{diodes off} \end{cases}$$

$$\theta = \tan^{-1}(-\omega RC) = -\tan^{-1}(\omega RC) + \pi$$

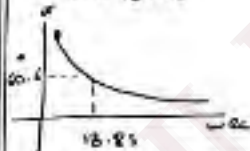$\omega RC = 2\pi(60)(500)(100 \mu)$   
 $\omega RC = 18.85$



$$(V_m \sin \theta) e^{-(\pi + \alpha - \theta)/\omega RC} = -V_m \sin(\pi + \alpha)$$

$$(\sin \theta) e^{-(\pi + \alpha - \theta)/\omega RC} - \sin(\alpha) = 0$$

- $\alpha = 60.6^\circ$  from graph
- $\theta = \pi - \tan^{-1}(\omega RC)$
- $\theta = 93^\circ$

$$\Delta V_o = V_m(1 - \sin \alpha)$$

$$\Delta V_o = 169.7(1 - \sin(60.6^\circ))$$

$$\Delta V_o = 22V$$

$$\Delta V_o = V_m - |V_m \sin(\pi + \alpha)| = V_m(1 - \sin \alpha)$$

the capacitor needed to make  $\Delta V_o = 0.1 V_m$

$$\Delta V_o = 0.1 = \frac{V_m}{2fRC} \Rightarrow C = 1670 \mu F$$

half the value of half wave.

where  $\omega RC \gg \pi$ ,

$$\theta \approx \pi/2$$

$$\alpha \approx \pi/2$$

$$v_o(\pi + \alpha) = V_m e^{-(\pi + \pi/2 - \pi/2)/\omega RC} = V_m e^{-\pi/\omega RC}$$

$$\Delta V_o \approx V_m(1 - e^{-\pi/\omega RC})$$

$$e^{-\pi/\omega RC} \approx 1 - \frac{\pi}{\omega RC}$$

$$\Delta V_o \approx \frac{V_m \pi}{\omega RC} = \frac{V_m}{2fRC}$$

ripple voltage.

$$I_{rms} = \frac{V_m}{2f}$$

center tapped

bridge

## Comparison between Single Phase Rectifiers

maximum voltage can apply in reverse case of diode without breakdown

	Fullwave	Half wave	Full wave
			center-tap    bridge
Peak repetitive reverse voltage VRRM	1.57 Vdc	3.14 Vdc	3.14 Vdc
Rms input voltage per transformer leg $V_s$	1.11 Vdc	2.22 Vdc	1.11 Vdc
Diode average current IF,AV.	1.00 Idc	0.50 Idc	0.50 Idc
Diode rms current IF,RMS.	1.57 Idc	0.785 Idc	0.785 Idc
Form factor of diode current IF,RMS.	1.57	1.57	1.57
Rectification ratio	0.405	0.81	0.81
Form factor	1.57	1.11	1.11
Ripple factor	1.21	0.482	0.482
Transformer rating primary VA Pdc	2.69 Pdc	1.23 Pdc	1.23
Transformer rating secondary VA Pdc	3.49 Pdc	1.76 Pdc	1.23
Output ripple frequency fr	1 fl	2 fl	2 fl

$$V_{dc} = \frac{V_m}{\pi}$$

$$V_{dc} = \frac{2V_m}{\pi}$$

in full wave is half the value  
increase with full wave


$I_{rms}$  is differ for both so transformer rating differ



Tuesday 25<sup>th</sup> / Mar / 2014

lecture 16

Multi-phase Rectifier

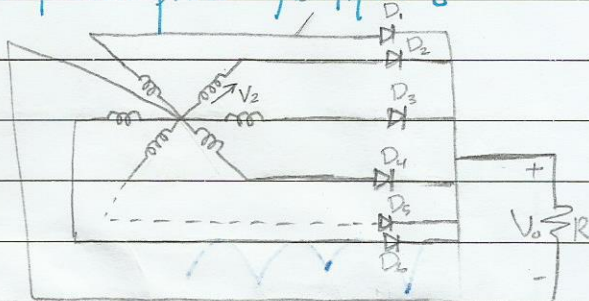

phase =  $q \cdot 2\pi/q$  (لقد في  $2\pi/q$ )

∴ period =  $2\pi/q$


$$V_{dc} = \frac{2}{2\pi/q} \int_0^{\pi/q} V_m \cos \omega t \, d\omega t = V_m \frac{q}{\pi} \sin \frac{\pi}{q}$$

لو جاب في  $(\cos \text{ و } \sin)$  لحد  $\pi/q$

$$\frac{2\pi}{q} \rightarrow \frac{4\pi}{q}$$

$$\frac{2\pi}{q} \rightarrow \frac{4\pi}{q}$$

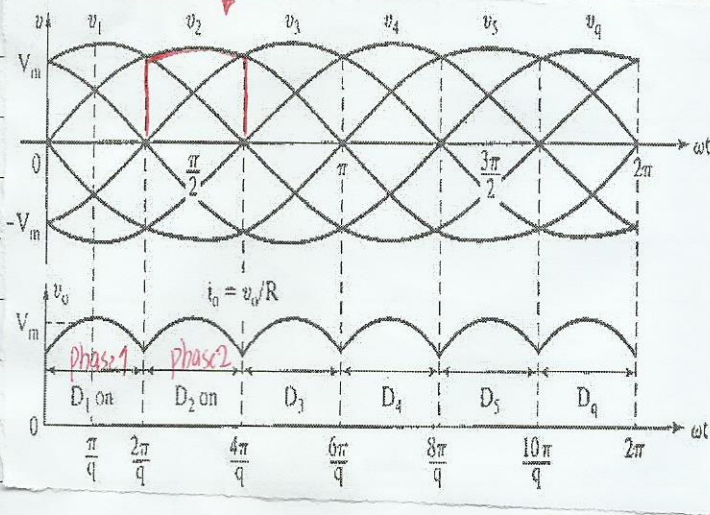في  $\pi/q$  لحد  $\pi/q$  و  $\cos$  و  $\sin$  لحد  $\pi/q$



$$V_{rms} = \sqrt{\frac{2}{2\pi/q} \int_0^{\pi/q} V_m^2 \cos^2 \omega t \, d\omega t} = V_m \left[ \frac{q}{2\pi} \left( \frac{\pi}{q} + \frac{1}{2} \sin \frac{2\pi}{q} \right) \right]^{1/2}$$

if fullwave  $\Rightarrow q=2$

$$\Rightarrow \therefore V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} \text{ "For single diode"} = \sqrt{\frac{2}{2\pi} \int_0^{\pi/2} I_m^2 \cos^2 \omega t \, d\omega t} = \frac{V_{rms}}{R\sqrt{q}}$$

$$= \frac{V_{rms}}{R\sqrt{q}}$$


$\rightarrow$  if  $q=2 \Rightarrow$

$$I_{rms} = \frac{V_m}{\sqrt{2}R}$$


التي كذا قبل



# Three phase Half-wave Rectifier

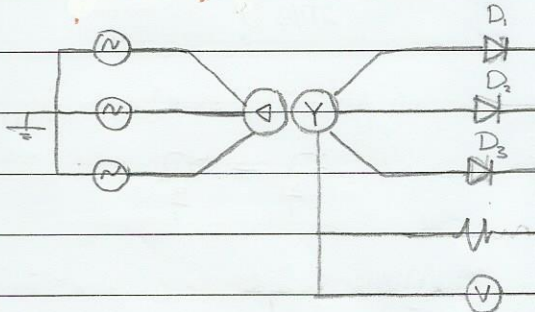

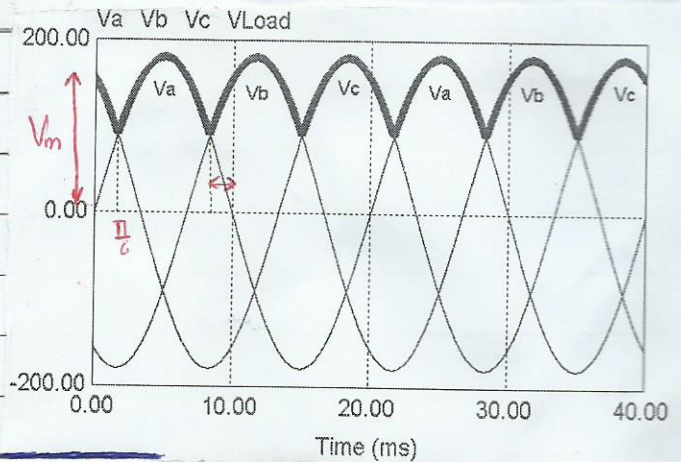each phase is half-wave rectifier  
 → each wave is 120°



$$V_{dc} = \frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} V_m \sin \omega t \, d\omega t = \frac{3\sqrt{3} V_m}{2\pi}$$

$$I_{dc} = \frac{3\sqrt{3} V_m}{2 * 2\pi R}$$

$$V_{rms} = \sqrt{\frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} (V_m \sin \omega t)^2 \, d\omega t} = \sqrt{\frac{1}{2} + \frac{3\sqrt{3}}{8\pi} V_m} = 0.8407 V_m$$

$$I_{rms} = \frac{0.8407 V_m}{R}$$

$$I_r = I_s = \frac{0.8407 V_m}{\sqrt{3} R}$$

current in single diode.

$$PIV \Rightarrow \sqrt{2} V_{L1} = \sqrt{3} V_m$$

Example: 3 phase star rectifier is operated from 460V, 50Hz supply at the 2<sup>nd</sup> ary side and the load R = 20Ω, Determine:

Rectifier efficiency, Form Factor, Ripple Factor, Peak inverse voltage,

$$V_s = \frac{460}{\sqrt{3}} = 265.58$$

$$V_{m, peak} = 265.58 * \sqrt{2} = 375.59$$

phase voltage

$$\Rightarrow V_{dc} = \frac{3\sqrt{3} V_m}{2\pi}$$

$$I_{dc} = \frac{V_{dc}}{R}$$

$$V_{rms} = 0.8407 V_m$$

$$I_{rms} = \frac{V_{rms}}{R}$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{V_{dc} I_{dc}}{V_{rms} I_{rms}} = 96.767\%$$

$$FF = \frac{V_{rms}}{V_{dc}} = 101.657\%$$



$$RF = \sqrt{1 - FF^2} = 18.28\%$$


$$PIV = \sqrt{3} V_m = 650.54$$

$$\rightarrow PF = \frac{(0.8407 V_m)^2 / R}{3 \times \frac{V_m}{\sqrt{2}} \times \frac{0.8407 V_m}{\sqrt{3} R}} = 0.6844$$

$$TUF = \frac{(0.8407 V_m)^2 / R}{3 \times \frac{V_m}{\sqrt{2}} \times \frac{0.8407 V_m}{\sqrt{3} R}} = 0.6643$$


$\eta = \frac{TUF}{PF} = 97.7\%$   
 rms phase voltage =  $\frac{\text{peak voltage}}{\sqrt{2}}$   
 rms phase current =  $\frac{\text{rms total}}{\sqrt{3}}$
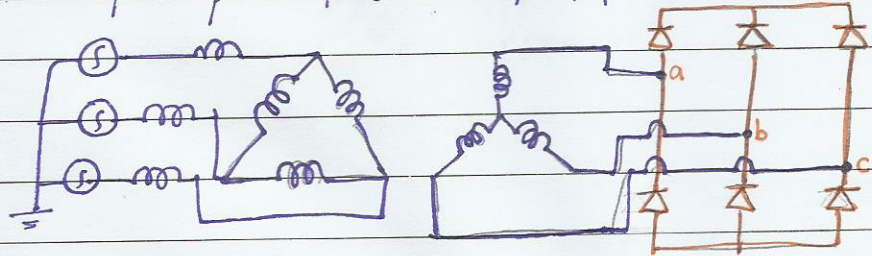
### Three phase Full wave Rectifier with Rload :



- voltage that is given to the load is line to line.
- in each moment [ 2 phase ON the 3<sup>rd</sup> OFF

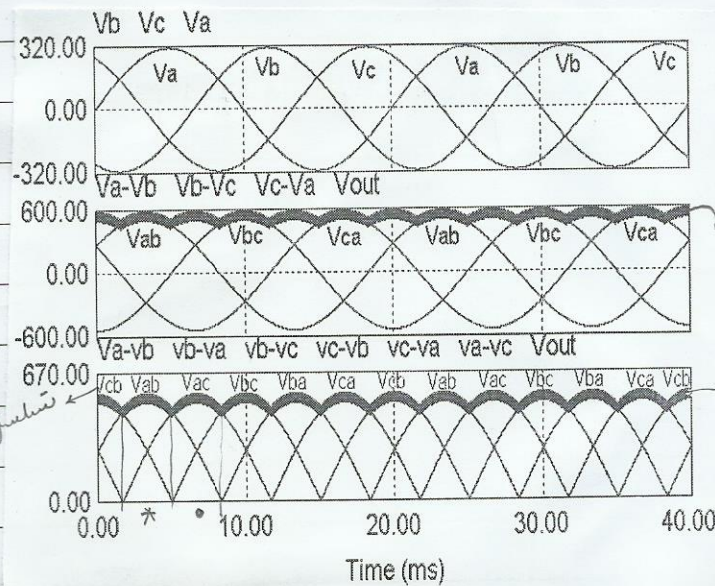→ phase angle  $120^\circ$   $\leftarrow$   $\frac{360^\circ}{3}$   
 $\leftarrow$   $120^\circ$  OFF  $60^\circ$   $\leftarrow$   $\frac{120^\circ}{2}$




$V_a$   $\leftarrow$   $60^\circ$   $\leftarrow$   $\frac{360^\circ}{6}$   
 $V_{ab} = V_b - V_a$   
 $V_{bc} = V_c - V_b$   
 fundamental  $\leftarrow$   $360^\circ$   $\leftarrow$   $\frac{360^\circ}{6}$   
 peak cosine line to line  $\leftarrow$   $360^\circ$   $\leftarrow$   $\frac{360^\circ}{6}$

دیاگرام

is divided into 6 sections



Lecture 17

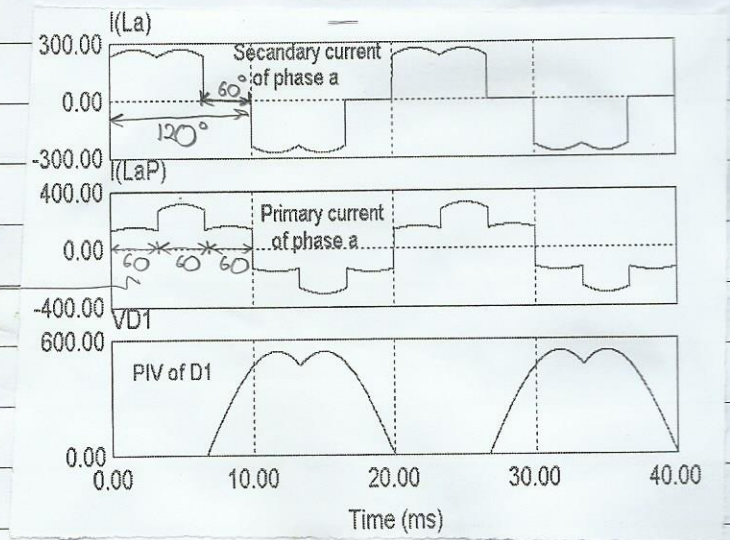

# through it the voltage is doubled

2<sup>nd</sup> ary:

120 +ve → 60 OFF → 120 -ve

$$\Rightarrow V_{rms} = \left[ \frac{2}{2\pi/6} \int_0^{\pi/6} 3 V_m^2 \cos^2 \omega t \, d\omega t \right]^{1/2} = \left( \frac{2}{3} + \frac{9\sqrt{3}}{4\pi} \right)^{1/2} V_m = \underline{1.6554 V_m}$$

$$I_r = \left[ \frac{4}{2\pi} \int_0^{\pi/6} I_m^2 \cos^2 \omega t \, d\omega t \right]^{1/2} = \underline{0.55/8 I_m} \text{ "For one diode"} \quad \left[ \sqrt{2} \times I_{one diode} \right]$$

$$\Rightarrow \text{the transformer 2<sup>nd</sup> ary current} = \frac{8}{2\pi} \int_0^{\pi/6} I_m^2 \cos^2 \omega t \, d\omega t = \underline{0.7804 I_m}$$

• For a three phase rectifier ⇒  $\eta = 6$  :

$$V_o(t) = 0.9549 V_m \left( 1 + \frac{2}{35} \cos(6\omega t) - \frac{2}{143} \cos(12\omega t) + \dots \right)$$



# Note:

## # Slide Performance Comparison between Single & 3-phase Rectifier

• Example: the 3-phase bridge rectifier is operated from 460V, 50Hz supply and the load resistance is  $R = 20 \Omega$ . Determine:  $\eta$ , FF, RF, PIV, PF,

$V_{dc} = \frac{3\sqrt{3} V_m}{\pi} = 1.654 V_m = 621.226$

$I_{dc} = \frac{V_{dc}}{R} = 31.0613 A$

$V_{rms} = \sqrt{\frac{3}{2} + \frac{9\sqrt{3}}{4\pi}} V_m = 621.752$

$I_{rms} = \frac{V_{rms}}{R} = 31.0876$

الفولتية في الريبل 0.5V


$\eta = \frac{P_{dc}}{P_{ac}} = 99.83\%$

$FF = \frac{V_{rms}}{V_{dc}} = 100.08\%$

$RF = \sqrt{1 - FF^2} = 4\%$

$PIV = \sqrt{3} V_m = 650.54 V$
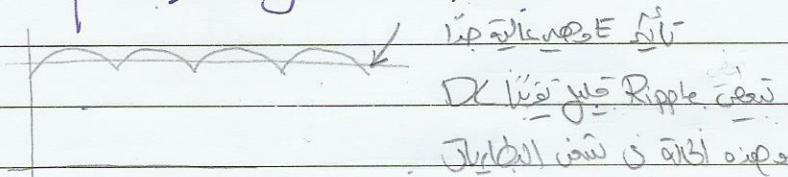
## • 3-phase Bridge Rectifier with RL loads



"If E very close to the peak" "Discard the ripple"

$V_{ab}(t) = \sqrt{2} V_{ab} \sin(\omega t) \quad \frac{\pi}{3} \leq \omega t \leq \frac{2\pi}{3}$

$i_o(t) = \frac{\sqrt{2} V_{ab} \sin(\omega t - \theta)}{\sqrt{R^2 + \omega^2 L^2}} - \frac{E}{R} + A e^{-\frac{R}{L}t}$

$\tan^{-1} \omega L / R$


⇒ under a steady state:  $i_o(\omega t = \pi/3) = i_o(\omega t = 2\pi/3) = I_o$

$\therefore I_o = \frac{\sqrt{2} V_{ab} \sin(2\pi/3 - \theta) - \sin(\pi/3 - \theta) e^{-(R/L)(\pi/3\omega)}}{1 - e^{-(R/L)(\pi/3\omega)}} - \frac{E}{R}$

initial value

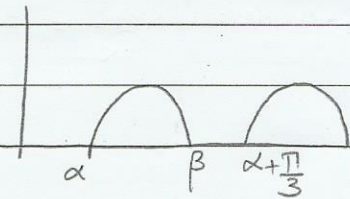1) Conditions for Continuous load Current:

$$\left( \frac{E}{\sqrt{2} V_{ab} / \text{critical}} \right) = \left[ \frac{\sin(\frac{2\pi}{3} - \theta) - \sin(\frac{\pi}{3} - \theta) e^{-\pi/3 \tan \theta}}{1 - e^{-\pi/3 \tan \theta}} \right] \cos \theta$$





two case  
→  $\beta > (\alpha + \pi/3) \Rightarrow$  Continuous  
→  $\beta < (\alpha + \pi/3) \Rightarrow$  Dis. cont.


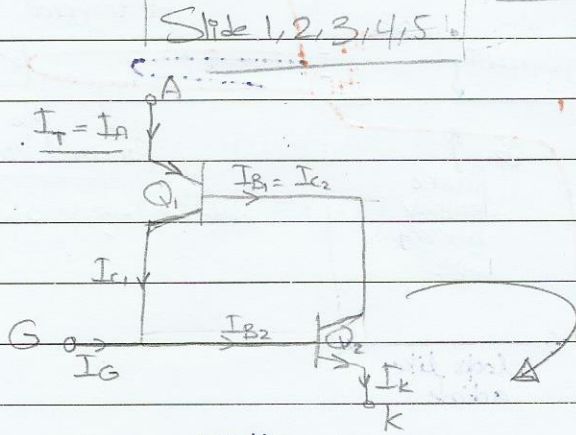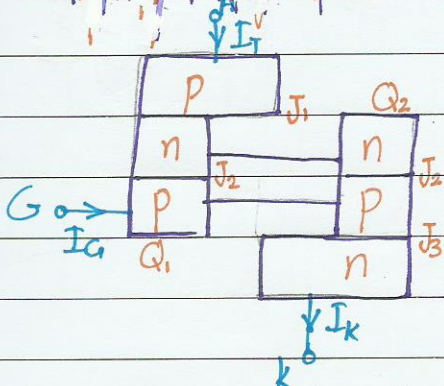
# THYRISTOR

the purpose of a thyristor is to be able to control diode.



3 junction  $\Rightarrow$  looks like 2 transistor  
 $\begin{matrix} \text{npn} & \text{pnp} \end{matrix}$

if there's no gate current, it won't work  $\Rightarrow$   $I_g$  is needed


Operation mode: forward bias.  $I_{B2}$  &  $I_{C1}$  are normally equal

$\Rightarrow I_c = \beta I_B + (1 + \beta) I_{CBO} \Rightarrow$  dc value of the collector to base current

$I_c = \alpha I_E + I_{CBO}$

$I_E = I_c + I_B$

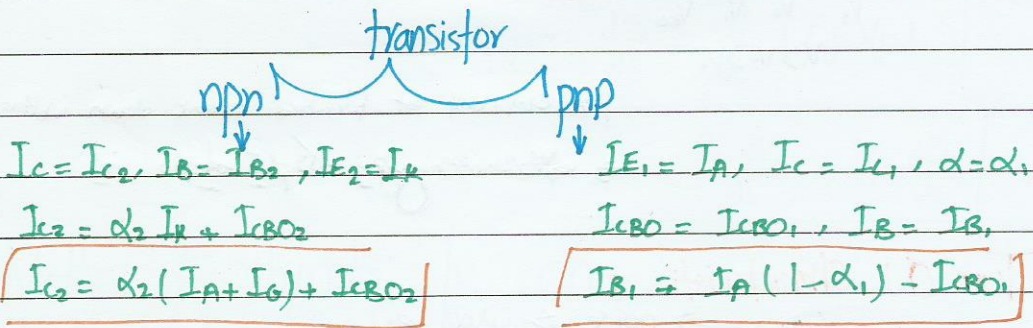$\Rightarrow I_B = I_E (1 - \alpha) - I_{CBO}$



from the equivalent ckt, we see that:

$I_{E2} = I_{B1}$

$\Rightarrow I_A = \frac{\alpha_2 I_g + I_{CBO1} + I_{CBO2}}{1 - (\alpha_1 + \alpha_2)}$

case 1

$I_g = 0$

$I_A = \frac{I_{CBO1} + I_{CBO2}}{1 - (\alpha_1 + \alpha_2)}$

case 2

$I_g \neq 0$


$I_A = \frac{\alpha_2 I_g + I_{CBO1} + I_{CBO2}}{1 - (\alpha_1 + \alpha_2)}$








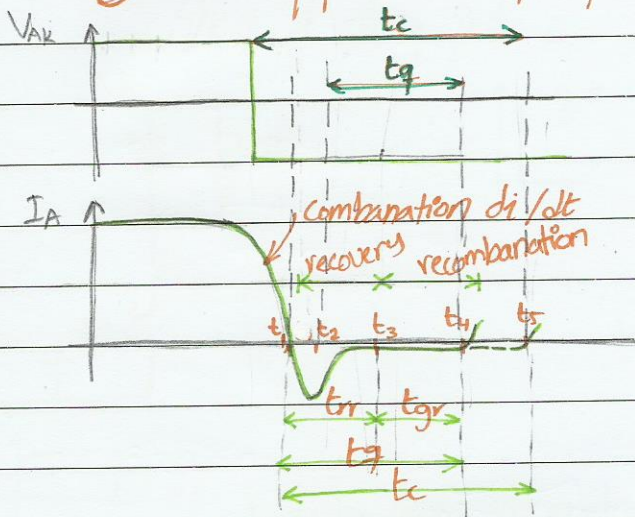↳ Switch OFF Characteristic is the same as switch off for diode  $\Rightarrow$  when  $I_A = 0$ .



(إزالة التيار)  
 $t_c$ : circuit off time  
 $t_q$ : device off time

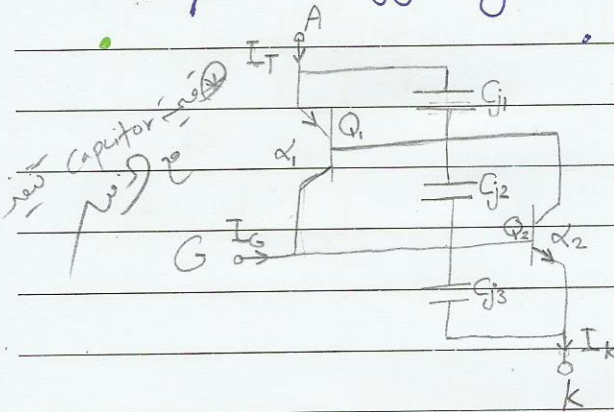•  $dV/dt$  triggering is concern about rate of change of voltage.  
 • the three junctions have a charges between them  $\rightarrow$  the charges [between p & n] will work as capacitor.  $\Rightarrow$  between junctions



$\Rightarrow$  because of the capacitors [ $t_{on}$ ] increases exponentially, if there's no capacitor it'll be sharp increasing.

$$i_{j2} = \frac{dq_2}{dt} = \frac{d}{dt} (C_{j2} V_{j2})$$

$$i_{j2} = \frac{C_{j2} dV_{j2}}{dt} + V_{j2} \frac{dC_{j2}}{dt}$$


### ↳ Method of Thyristor Turn on is

1. Thermal turn on  $\Rightarrow$  ليس في كل مرة (switch-on) في كل مرة
2. Light
3. High Voltage
4. Gate Current
5.  $dV/dt \Rightarrow$  a low amount of voltage but there's spark (إتفاح) this will cause switching due to capacitor where  $dV/dt$  will produce current.




lecture 22

Short & long pulse :

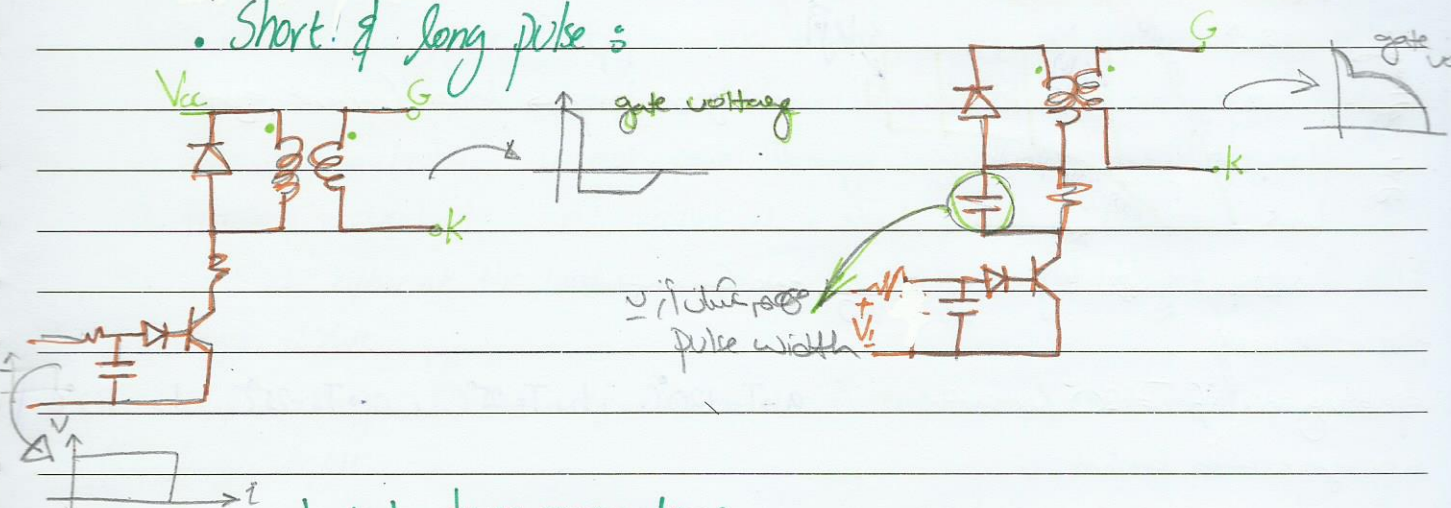

↳ pulse train generator :

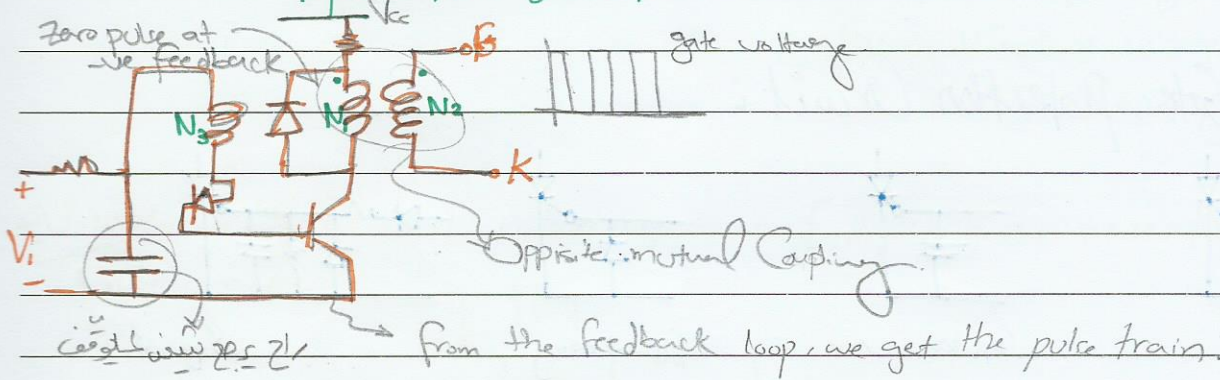


↳ pulse train with timer and AND gate :

Why is required

For Comparison between AC & DC


↳ R-triggering :

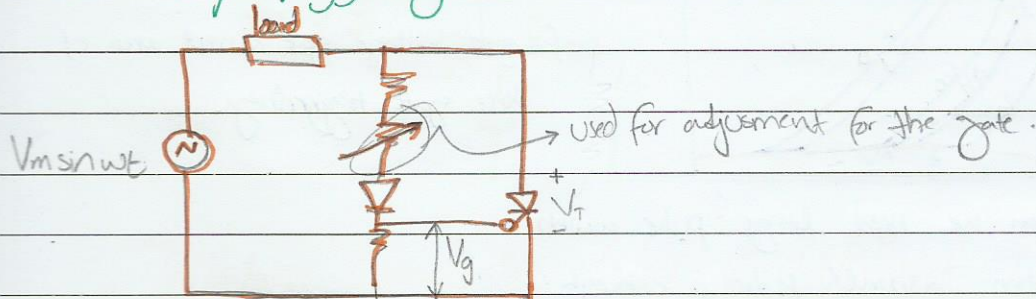

and there's RC triggering ; check out the slides



## Gate Triggering Characteristics

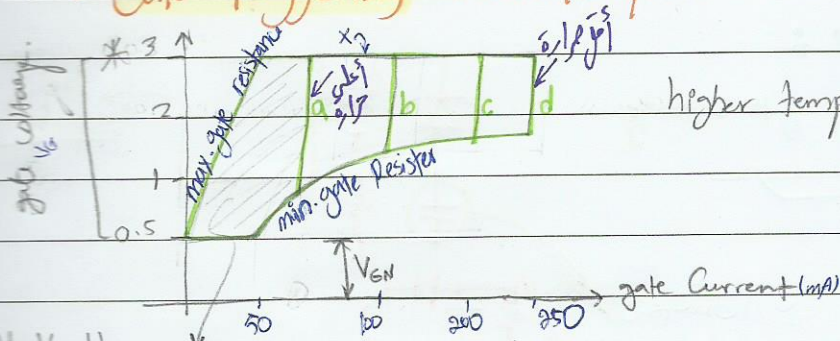


that's the range

operating in. if  $T=120^\circ$  we can't supply it with current or voltage higher than \*

a →  $T=120^\circ\text{C}$ , b →  $T=25^\circ\text{C}$ , c →  $T=-25^\circ\text{C}$ , d →  $T=-50^\circ\text{C}$


## Gate Protection Circuits

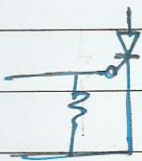


Resistor



Capacitor in case of transient

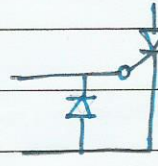


free wheeling diode

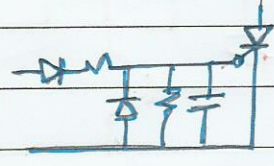

size of diode to protect the gate
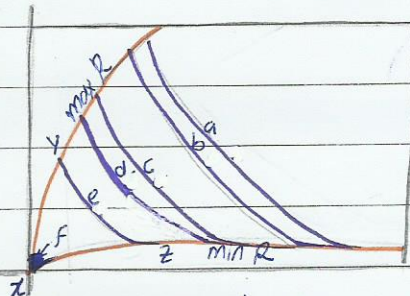
## Gate Input Characteristics

پولس (pulse) کی شکل میں (پولس) کی شکل میں (پولس) کی شکل میں  
 triggering کی شکل میں



a, b, c, d, e → pulse duration

$a < b, \dots < e$

∴ gate voltage gate current area of sure gate triggering.

if V & I are low then we need large pulse width.  
 if V & I are high then a small pulse is enough.




**High Temperature due to :**


↳ this cause a low power quality

← since thyristor works at a proper temp. it's different due to these reasons

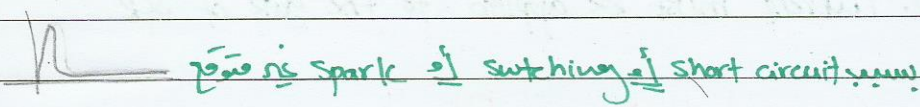
1. sustained overload: current passes through higher than rated current
2. transient overload: O.L occurs at a short period of time.
3. short ckt either at the load or in one of the device.
4. large  $di/dt$
5. surge voltage
6. large  $dV/dt$
7. excessive gate power in case of SCRs
8. insufficient gate drive in case of SCRs




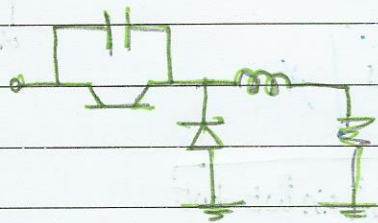
**Snubber :** to protect any device [protecting thyristor or transistor]



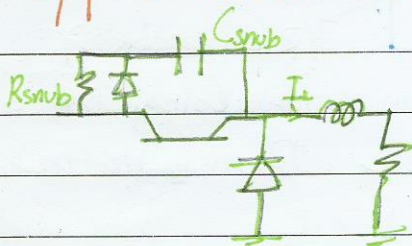**Turn off Snubber circuit :** works as the snubber



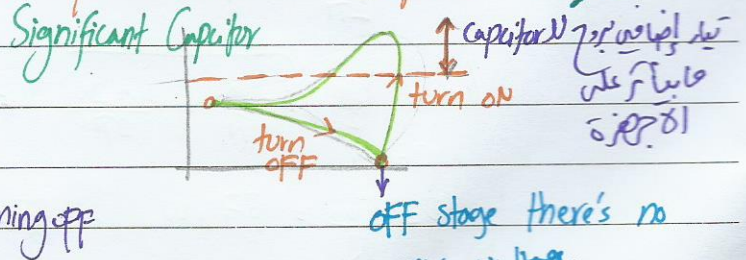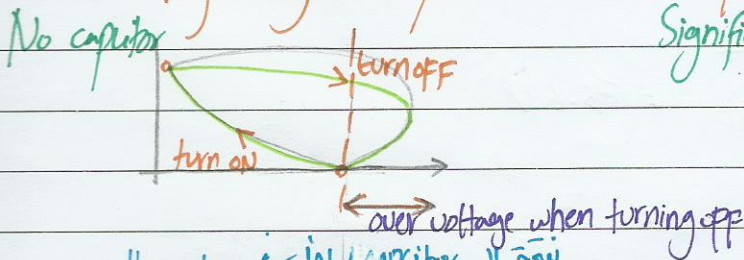**Trajectory Comparison With & Without Capacitor :**



Using Snubber

↓ capacitor ↓  
↓ voltage ↓  
↓ over voltage ↓




# Controlled Rectifier: «التيار قال كله بلين أخذاه قبل كان عقبات!!»

Normal Rectifier are considered as uncontrolled rectifier  
 away to control the output is to use SCR instead of diode, two Condition must  
 be met before SCR can conduct:

1.  $V_{AK}$  must be forward
2. current must be applied to the gate of SCR
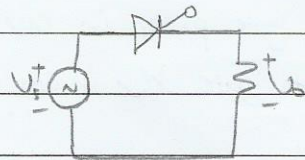
## Controlled Halfwave RL load:


$$V_o = V_{avg} = V_{DC} = \int_{\alpha}^{\pi} V_m \sin \omega t \, d\omega t$$



$$V_o = \frac{V_m}{2\pi} (1 + \cos \alpha) \quad *$$

avg. DC output voltage.      firing angle
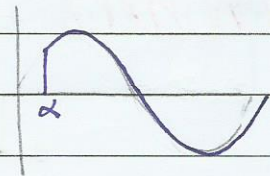
$$P = I_{rms}^2 R = \frac{V_{rms}^2}{R} \quad *$$



$$\Rightarrow V_{rms} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d\omega t}$$

$$V_{rms} = \frac{V_m}{2} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}} \quad *$$

if  $\alpha = 0 \Rightarrow V_{rms} = V_m/2$   
 (Rad  $> 180^\circ < \pi$ )

- Example: Design a circuit to produce an average voltage of 40V across 100Ω from 120V<sub>rms</sub>, 60Hz ac source. Determine the power absorbed by R & PF?

$$V_o = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$40 = \frac{120\sqrt{2}}{2\pi} (1 + \cos \alpha) \Rightarrow \alpha = 61.2^\circ = 1.07 \text{ rad.}$$

$$V_{rms} = \frac{V_m}{2} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}} = 75.6 \text{ V}$$

$$P = \frac{V_{rms}^2}{R} = 57.1 \text{ W}$$

$$PF = \frac{57.1}{(120)(75.6)} = 0.63$$




lecture 23

- Note: if an uncontrolled diode is used ( $\alpha=0$ )  $\Rightarrow V_o = \frac{V_m}{\pi} = \frac{120\sqrt{2}}{\pi} = 54V$
- R in series  $\Rightarrow$  simply voltage divider

Controlled Half wave RL load:
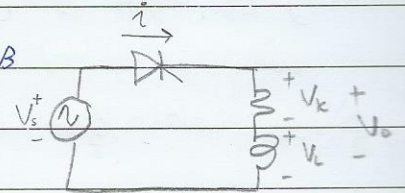
$$i(\omega t) = \begin{cases} \frac{V_m}{Z} [\sin(\omega t - \theta) - \sin(\alpha - \theta) e^{(\alpha - \omega t)/\omega\tau}] & \alpha < \omega t < \beta \\ 0 & \text{otherwise} \end{cases}$$




$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\beta} i^2(\omega t) d\omega t}$$

$$I_{avg} = \frac{1}{2\pi} \int_{\alpha}^{\beta} i(\omega t) d\omega t$$

$$V_{avg} = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$$

$$P = I_{rms}^2 R$$

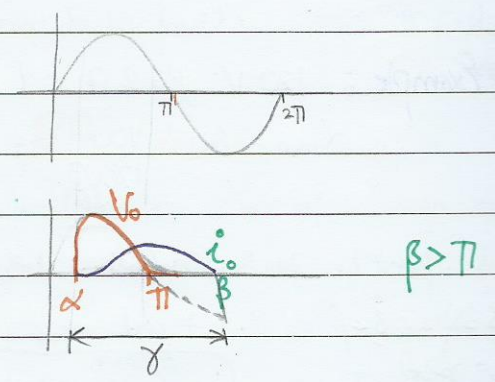

$\gamma \equiv$  conduction angle  $= \beta - \alpha$   
 distinction Firing

$\tan(\alpha - \theta) = \frac{\sin \gamma}{e^{-\gamma/\omega L/R} - \cos \gamma}$  to find  $\alpha$

$\theta = \tan^{-1} \frac{\omega L}{R}$

$\beta$  &  $\gamma$  have to be known. we can find them from graph.

- Examples if  $V = 120V$ ,  $R = 20\Omega$ ,  $L = 0.04H$ ,  $\alpha = 45^\circ$ ,  $f = 60Hz$

$V_m = 120\sqrt{2} = 169.7V$

$Z = \sqrt{20^2 + 0.04 \times 2\pi \times 60} = 25\Omega$

$\theta = \tan^{-1} \omega L/R = 0.646$

$\omega L/R = 0.754$

from the graph  $\Rightarrow \alpha = 45^\circ$

$i(\omega t) = \frac{V_m}{Z} [\sin(\omega t - \theta) - e^{\omega t / 0.754}]$   $\alpha < \omega t < \beta \rightarrow 172 + 4 = 217$

$I_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\beta} i(\omega t) d\omega t = 2.19V$


$I_{rms} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\beta} i^2(\omega t) d\omega t} = 3.26A$

PF =  $\frac{213}{120 \times 0.26} = 0.54$



→ if there's a source [ controlled half wave RL load with source ]

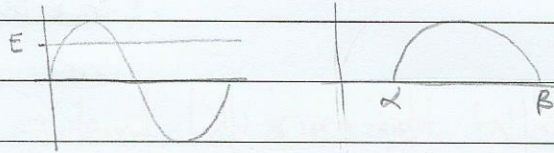$\sin \alpha = \frac{E}{V_m}$   
 Firing angle  $\alpha = \sin^{-1} (E/V_m)$



$i(\omega t) = \frac{V_m}{Z} \sin(\omega t - \theta) - \frac{E}{R} + A e^{-\omega t / (\omega L/R)}$   
 $\downarrow \left[ -\frac{V_m}{Z} \sin(\alpha - \theta) + \frac{E}{R} \right] e^{\alpha / (\omega L/R)}$

• Example : 120 V,  $R = 2 \Omega$ ,  $L = 20 \text{ mH}$ ,  $E = 100 \text{ V}$ ,  $f = 60 \text{ Hz}$ ;  $\alpha = 45^\circ$   
 $\alpha_{\min} = \sin^{-1} \frac{100}{120\sqrt{2}} = 36^\circ$

$i(\omega t) = 21.8 \sin(\omega t - 1.312) - 50 + 75 e^{-\omega t / 3.77}$

graph  $\alpha = 45^\circ$  and  $\beta = 3.37 \text{ rad}$


$I_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_{\alpha=45}^{\beta=3.37} i^2(\omega t) d\omega t} =$

$I_{\text{dc}} = \frac{1}{2\pi} \int_{\alpha}^{\beta} i(\omega t) d\omega t = 2.19 \text{ A}$


$P_E = 2.19 \times 100 = 219 \text{ W}$

$P_R = I_{\text{rms}}^2 \times R = 3.9^2 \times 2$

→ Controlled Full-wave Rectifier :

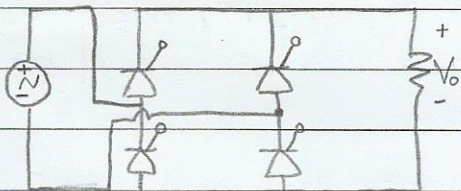

bridge Rectifier

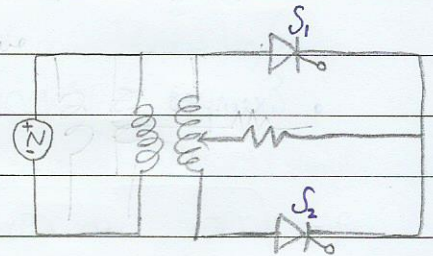


Centre tapped

→ current is half-wave

$I_{\text{rms}}$  in R is what we calculate

$I_{\text{rms}}$  in  $S_1$  &  $S_2 \rightarrow \frac{I_{\text{out}}}{\sqrt{2}}$

output for resistive load →

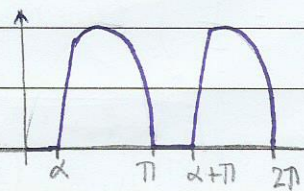



lecture 24

⇒ For resistive load: 
$$V_o = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) d\omega t = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$I_o = V_o / R$$


$$I_{rms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} \left(\frac{V_m \sin \omega t}{R}\right)^2 d\omega t}$$

$$I_{rms} = \frac{V_m}{R} \sqrt{\frac{1-\alpha}{2} + \frac{\sin 2\alpha}{2\pi}}$$
 if  $\alpha=0$ ,  $I_{rms} = \frac{V_m}{\sqrt{2}R}$

$$P = I_{rms}^2 R$$
 (power delivered to the load)


as full wave Rectifier

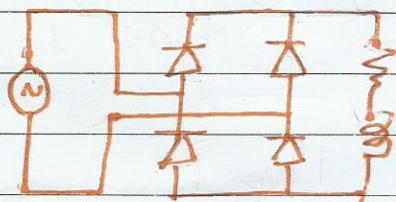⇒ Full-wave Controlled Rectifier with RL load:



in this case current always +ve while voltage [+ve or -ve] depends on  $\alpha$

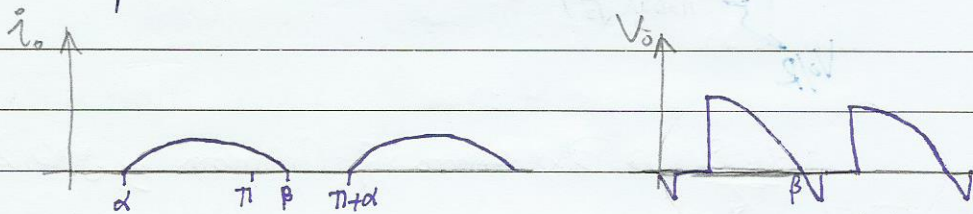
→ Discontinuous Mode: it's like half wave Rectifier except that period for the output is  $\pi$ .  $\beta < \alpha + \pi$



$$i_o(\omega t) = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \left[ \sin(\omega t - \theta) - \sin(\alpha - \theta) e^{-(\omega t - \alpha)/\omega L} \right]$$
  
 where  $\theta = \tan^{-1}(\omega L/R)$

→ Continuous Mode

$\beta > \pi + \alpha$

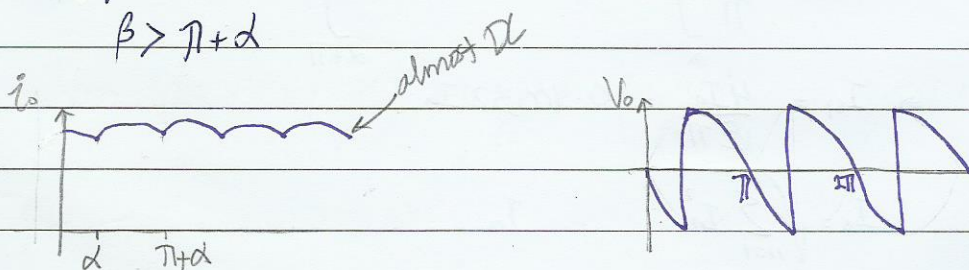



Largest Harmonic at  $\alpha = 90^\circ$

$\Rightarrow \omega t = \pi + \alpha$


- Fourier Series:  $V_0(\omega t) = V_0 + \sum_{n=1}^{\infty} V_n \cos(n\omega t + \theta_n)$

$\sqrt{a_n^2 + b_n^2}$

harmonics from the graph;

$V_0 = \frac{1}{\pi} \int_{\alpha}^{\pi + \alpha} V_m \sin \omega t \, d\omega t = \frac{2V_m}{\pi} \cos \alpha$

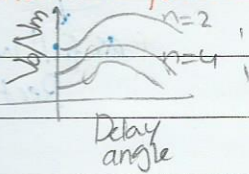there's no odd harmonic since the fundamental = 2



$a_n = \frac{2V_m}{\pi} \left[ \frac{\cos(n+1)\alpha}{n+1} - \frac{\cos(n-1)\alpha}{n-1} \right]$

$b_n = \frac{2V_m}{\pi} \left[ \frac{\sin(n+1)\alpha}{n+1} - \frac{\sin(n-1)\alpha}{n-1} \right]$

depends on  $\alpha$  values

$\theta = \tan^{-1}(-b_n/a_n)$

$I_n = \frac{V_n}{Z}$

$I_{rms} = \sqrt{I_0^2 + \sum_{n=2,4}^{\infty} \left(\frac{I_n}{\sqrt{2}}\right)^2}$

$V_0/R$

$\alpha = 0$  Discontinuous & Continuous

$\frac{\omega t}{R}$  delay firing delay

High inductor; Fourier series for  $i_s$ :

$I_{dc} = 0$   
 $a_n = \frac{1}{\pi} \int_{\alpha}^{\alpha + \pi} I_n \cos(n\omega t) \, d\omega t = \int_{\alpha + \pi}^{\alpha + 2\pi} I_n \cos(n\omega t) \, d\omega t$

$\Rightarrow I_{s1} = \frac{4I_a}{\sqrt{2}\pi} = 0.90032 I_a$

$I_s = \sqrt{\sum_{n=1}^{\infty} I_n^2} = I_a$

HF =  $\sqrt{\left(\frac{I_s}{I_a}\right)^2 - 1} = 0.483$        $\alpha = 60^\circ = \pi/3$

• Example:  $V_s = 120 \text{ V}$ ,  $R = 10 \Omega$ ,  $f = 60 \text{ Hz}$ ,  $\alpha = 60^\circ$ ,  $L = 20 \text{ mH}$  ?!

$$\theta = \tan^{-1} \frac{\omega L}{R} = \tan^{-1} \left( \frac{2\pi \times 60 \times 0.02}{10} \right) = 0.646 \text{ rad} \approx 37^\circ$$

$$\alpha = 60^\circ = 1.047 \text{ rad}$$

$\Rightarrow \alpha > \theta \therefore$  discontinuous

From the graph,  $\gamma = 156$ .

$$\beta = \gamma + \alpha = 216$$

$$\Rightarrow I_o = \frac{1}{\pi} \int_{\alpha}^{\beta} i(\omega t) d\omega t = 7.05 \text{ A}$$

• Example: single phase, full wave controlled rectifier with RL load where  $V_s = 120 \text{ V}$ ,  $f = 60 \text{ Hz}$

$\alpha = 60^\circ$ ,  $R = 10 \Omega$ ,  $L = 100 \text{ mH}$  ?!

$$\theta = \tan^{-1} \left( \frac{2\pi \times 60 \times 0.1}{20} \right) = 75^\circ$$

$\alpha < \theta \Rightarrow$  Continuous.

$$V_o = \frac{2V_m}{\pi} \cos \alpha = \frac{2 \times 120\sqrt{2}}{\pi} \cos 60 = 54 \text{ V}$$

From graph 4-12:  $\frac{V_o}{V_m} = 0.76$

F	$V_o/V_m$	$V_o$	Z	$I_o$
60	0.76	54	10	5.4
2x60	0.76	129.8	76	1.71
4x60	0.3	50.4	151	0.33
6x60	0.18	32.2	226	0.14


$$I_{\text{rms}} = \sqrt{(5.4)^2 + \left(\frac{1.71}{\sqrt{2}}\right)^2 + \left(\frac{0.33}{\sqrt{2}}\right)^2 + \left(\frac{0.14}{\sqrt{2}}\right)^2} = 5.54 \text{ A}$$

$$P = 5.54^2 \times 10 = 307 \text{ W}$$



Lecture 25

→ RL Source Load:

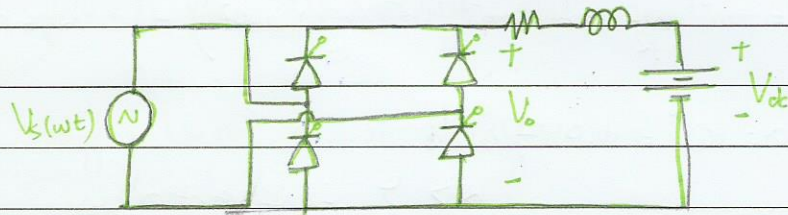

if  $\alpha < 90^\circ \Rightarrow$  +ve output

if  $\alpha > 90^\circ \Rightarrow$  -ve output, we can't connect it to a positive battery, we have to flip it [works as inverter DC  $\rightarrow$  AC return power to the source].

$\Rightarrow \alpha \geq \sin^{-1}(V_{dc}/V_m)$


For Continuous Current:

$V_o = \frac{2V_m}{\pi} \cos \alpha$

$I_o = \frac{V_o - V_{dc}}{R}$


$P_{dc} = I_o V_{dc}$

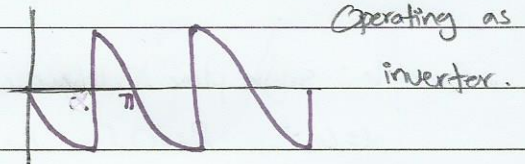$P = I_{rms}^2 R = I_o^2 R$  if L is high.



→ Average DC Output Voltage:

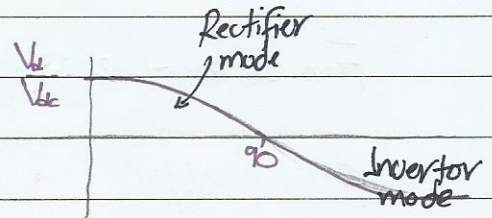$V_o = \frac{2\sqrt{2} V_s \cos \alpha}{\pi}$



assuming AC side inductance is zero

Note that Output can go -ve for  $\alpha > 90$  [this mean -ve power flow  $\Rightarrow$  inversion].

• Example:  $V = 120$  V,  $E = -110$  V,  $R = 0.5 \Omega$ ,  $L$  is large,  $f = 60$  Hz,  $P_k = 1000$  W?

$$I = \frac{1000}{110} = 9.09 \text{ A}$$

$$V = 9.09 \times 0.5 - 110 = -105.5 \text{ V}$$

$$-105.5 = \frac{2V_m \cos \alpha}{\pi} \Rightarrow \alpha = 165.5$$

$$P_s = 1000 - 9.09^2 (0.5) = 959 \text{ W}$$

$$P_R = 9.09^2 \times 0.5 = 41 \text{ W}$$

if thyristor not ideal  $\Rightarrow V_{th} = 1$  V  $\therefore V_{th} = 2$  V since each time 2 thyrs are operating

$$V_s = -105.5 - 2 = -107.5$$

$$I_E = I_R = \frac{110 - 107.5}{0.5} = 5 \text{ A}$$

we can change it value by changing  $\alpha$ .

$$P_E = 5 \times 110 = 550 \text{ W}$$

$$P_{TH} = 5 \times 1 = 5 \text{ W}$$

$$P_{TH(\text{total})} = 2.5 \times 5 = 10 \text{ W}$$

$$\therefore P_s = 550 - 10 - 5^2 \times 0.5 = 557.5 \text{ W}$$



• Example:  $240 \text{ V}_{\text{rms}}$ ,  $60 \text{ Hz}$ ,  $V_{\text{dc}} = 100 \text{ V}$ ,  $R = 5 \Omega$ ,  $L$  is very large, Continuous  
 $P_{\text{dc}} = 1000 \text{ W}$ ,  $\alpha = ?!$

$\alpha$  is less than  $90^\circ$  because it's working as rectifier

$\rightarrow$  if  $\alpha > 90^\circ$  it's inverter

$$I_0 = \frac{1000}{100} = 10 \text{ A}$$

$$V_0 = 10 \times 5 + 100 = 150$$

$$= \frac{2V_m \cos \alpha}{\pi}$$


$$150 = \frac{2 \times 240\sqrt{2}}{\pi} \cos \alpha \Rightarrow \alpha = 46^\circ$$

Find  $(L)$  that will limit peak to peak load current to  $2 \text{ A}$ ?

$L$  is large but not very large [not dc but there's a small ripple].

$$I_{\text{rms}} = \frac{2}{2\sqrt{2}} = 0.707$$

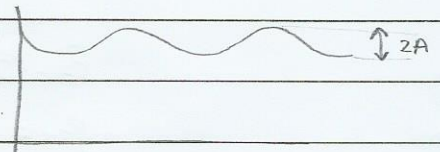harmonic  
 "fundamental"  
 neglect the rest.





$$\rightarrow \text{From the graph (11-12)} \Rightarrow \frac{V_2}{V_{\text{rms}}} = 0.68 = \frac{V_2}{240\sqrt{2}} \Rightarrow \underset{\text{Peak}}{V_2} = 230 \text{ V}$$

$$\Rightarrow \frac{230}{I_{\text{peak}}} = 230 = 2\pi \times 60 \times 2 \times L$$


$$\Rightarrow L = 0.31 \text{ H}$$

Lecture 26

# Three Phase Controlled Rectifier

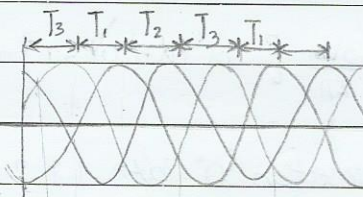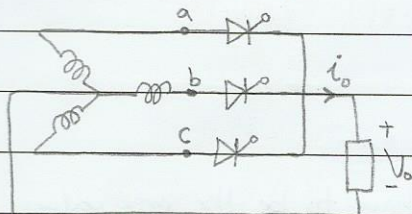

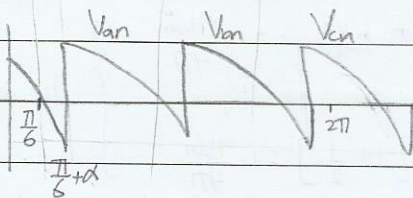α مابنا ذها من المبر بناذها من 30° من أول نقطة تقاطع.




كل فترة واحد راج يتغير (بما في) كله متوقف

all of them are shifted by α

يعني بنأخر Firing بكم قبل α

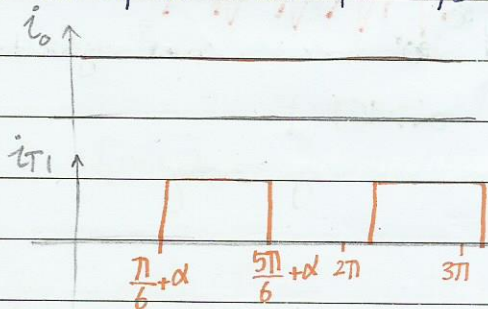⇒ each thyristor conducts for  $2\pi/3 = 120^\circ \Rightarrow$  Constant load Current.



Note:

$$V_{en} = v_{an} = V_m \sin(\omega t)$$

$$V_{bn} = v_{bn} = V_m \sin(\omega t - 120^\circ)$$

$$V_{cn} = v_{cn} = V_m \sin(\omega t - 240^\circ)$$

T<sub>1</sub> triggered at  $\omega t = \frac{\pi}{6} + \alpha = 30 + \alpha$

T<sub>2</sub> " "  $\omega t = 150 + \alpha$

T<sub>3</sub> " "  $\omega t = 270 + \alpha$

if the reference voltage is  $V_{en} = v_{an} = V_m \sin(\omega t)$

$$V_{dc} = \frac{3}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m \sin \omega t \, d\omega t = \frac{3\sqrt{3}}{2\pi} V_m \cos \alpha = \frac{3V_m}{2\pi} \cos \alpha$$

max dc output voltage at  $\alpha=0 \Rightarrow V_{dc \max} = \frac{3\sqrt{3}}{2\pi} V_m$

$$V_{rms} = \left( \frac{3}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m^2 \sin^2 \omega t \, d\omega t \right)^{1/2}$$

$$= \sqrt{3} V_m \left( \frac{1 + \sqrt{3} \cos 2\alpha}{8\pi} \right)^{1/2}$$



### → 3phase Half-wave Controlled Rectifier For RL load:

$$\text{For } \alpha < 30 \Rightarrow V_{dc} = \frac{3\sqrt{3}}{2\pi} V_m \cos \alpha \quad \dots 1$$

$$\text{For } \alpha > 30 \Rightarrow V_{dc} = \frac{3V_m}{2\pi} \left[ \cos(\alpha + 30) + 1 \right] \quad \dots 2$$

at point of intersection  $30^\circ$  both 1 & 2 must have to be the same value.



$$1 \dots \frac{3\sqrt{3}}{2\pi} V_m \times \frac{\sqrt{3}}{2} = \frac{9V_m}{4\pi}$$

$$2 \dots \frac{3V_m}{2\pi} \left[ 1 + \frac{1}{2} \right] = \frac{9V_m}{4\pi}$$

} the same value at  $\alpha = 30^\circ$ .

$\alpha = 30^\circ$

$\alpha = 60^\circ$

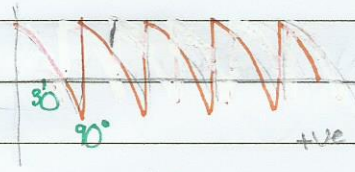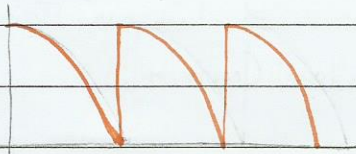


the avg. voltage

$\alpha = 90^\circ$

the avg. voltage

$\alpha > 90^\circ$

-ve avg. voltage

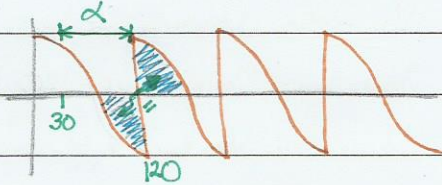

zero avg. voltage

• Example: 3phase, 208V, 60Hz,  $R = 10\Omega$  a. 90% of max  $V_{dc}$ , b. 50% of max  $I_{rms}$

$$a. \quad V_m = \frac{208}{\sqrt{3}} \sqrt{2} = 169.83$$

$$\cos \alpha = 0.9 \Rightarrow \alpha = 25.84^\circ$$

$$\text{since } \alpha < 30, \text{ then } V_{dc} = \frac{3\sqrt{3}}{2\pi} V_m \cos \alpha = 126.4 \text{ V}$$

$$I_{dc} = 126.4 / 10 = 12.64 \text{ A}$$

$$I_{rms} = \frac{\sqrt{3}}{R} V_m \left[ \frac{1}{6} + \frac{\sqrt{3}}{8} \cos 2\alpha \right]^{1/2} = 13.6 \text{ A}$$

$$\eta = \frac{12.64^2 \times 10}{13.6 \times 10} = 88.1\%$$

$$TUF = \frac{12.64^2 \times 10}{3 \times \frac{208}{\sqrt{3}} \times 13.6} = 0.564$$

$$b. \quad V_{dc} = \frac{3V_m}{2\pi} (1 + \cos(\alpha + 30)) = \frac{3\sqrt{3} V_m}{2\pi} \cos \alpha$$

$$\frac{3 \times 169.83}{2\pi} (1 + \cos(\alpha + 30)) = \frac{3\sqrt{3} \times 169.83 \times 0.5}{2\pi}$$

$$\Rightarrow \alpha = 67.7$$

$$\Rightarrow V_{rms} = \sqrt{3} V_m \left[ \frac{5}{24} - \frac{\alpha}{4\pi} + \frac{1}{8\pi} \sin\left(\frac{\pi}{3} + 2\alpha\right) \right]^{1/2} = 94.74 \text{ V}$$

$$V_{dc} = \frac{3 \times 169.83}{2\pi} (1 + \cos(\alpha + 30)) = 70.23$$

$$I_{dc} = \frac{70.23}{10} = 7.023$$

$$I_{dTH} = \frac{7.023}{3} = 2.34$$

$$I_{rms} = 94.74 / 10 = 9.474$$

$$I_{rmsTH} = 9.474 / \sqrt{3} = 5.47$$

$$\eta = \frac{7.023^2 \times 10}{9.474^2 \times 10} = 54.95\%$$





$$TUF = \frac{7.023^2 \times 10}{3 \times \frac{208}{\sqrt{3}} \times 5.47} = 25\%$$

$$PF = \frac{9.474^2 \times 10}{3 \times \frac{208}{\sqrt{3}} \times 5.47} = 0.455$$



lecture 26

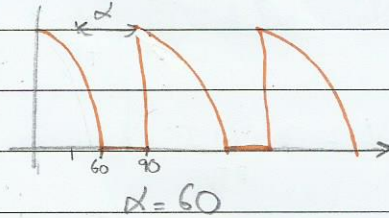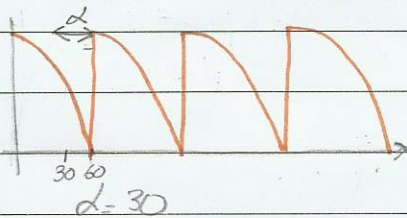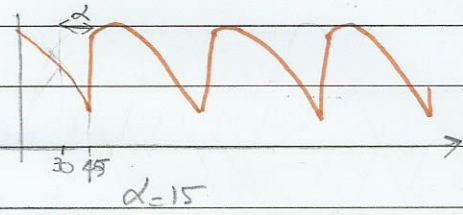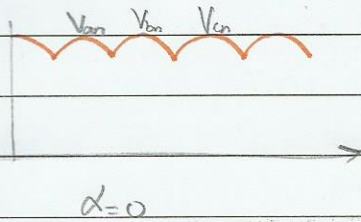→ 3 phase Half wave Controlled with R-L & FWD: no -ve parts.



→ more than 30° there's no -ve parts "it's zero" because it's resistive & after 30° there's no current & no current from the other thyristor until 90°..

⇒ BUT, at free wheeling it won't be like this because after the 1<sup>st</sup> thyristor stop working "after 30°" the free wheeling diode will work.

T<sub>1</sub> conducts from  $(30 + \alpha)$  to 180 ⇒  $V_o = U_m \sin(\omega t) = V_{an}$


T<sub>2</sub> " "  $(150 + \alpha)$  to 300 ⇒  $V_o = U_m \sin(\omega t - 120) = V_{bn}$

T<sub>3</sub> " "  $(270 + \alpha)$  to 420 ⇒  $V_o = U_m \sin(\omega t - 240) = V_{cn}$

$$\Rightarrow V_{dc} = \frac{3}{2\pi} \int_{30+\alpha}^{180} V_o \, d\omega t = \frac{3U_m}{2\pi} [1 + \cos(\alpha + 30)]$$

→ Three phase Semi-Converter ≡ half Controlled bridge converter.

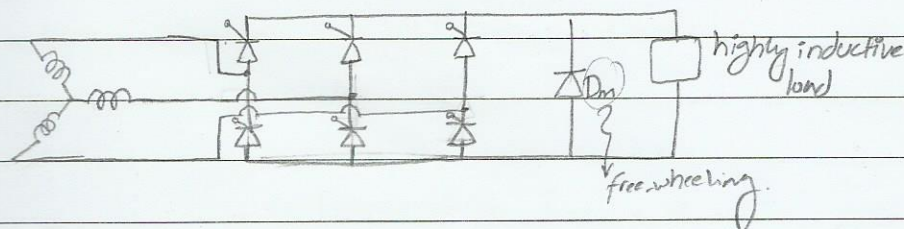each period one of the diode is on ⇒ which will prevent the -ve.





power factor decrease as the delay angle increase.

power factor is better than that of 3 phase half-wave Converter..

if  $\alpha < 60^\circ \Rightarrow$  Continuous  
 if  $\alpha > 60^\circ \Rightarrow$  Zero because there's no  $(-ve)$

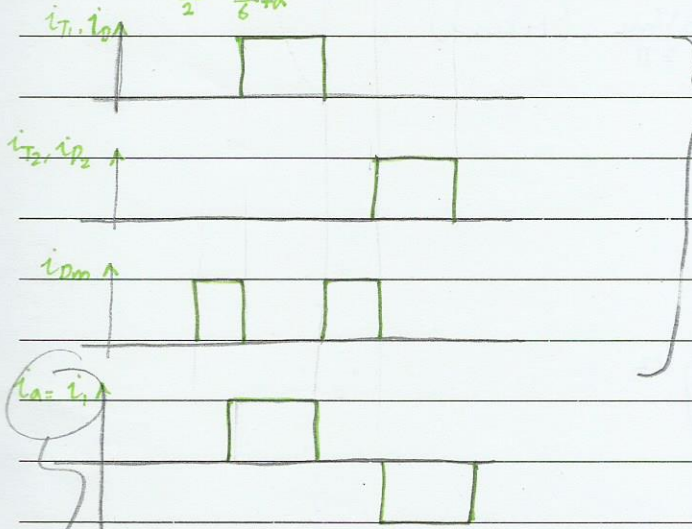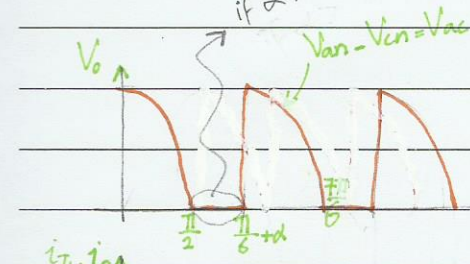Note that load voltage is line to line Not phase volt.




if the load is highly inductive, then the output is almost DC  $\Rightarrow$  the DC is separated between  $D_1$  &  $D_3$  while  $D_m$  complete the parts that there's no direct operating

التيار في الحمل فيكون شبه مستمر

doubled current (in +ve & -ve), to calculate it  $\Rightarrow \sqrt{2} I_L$

for  $\alpha < 60^\circ$

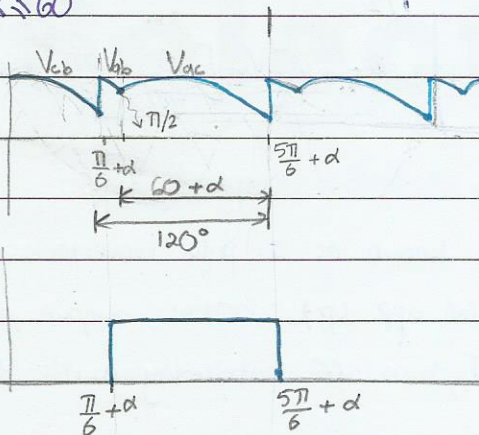

if

$D_2$  from  $\frac{7\pi}{6}$  to  $\frac{11\pi}{6}$ ;  $T_2$  from  $\frac{5\pi}{6} + \alpha$  to  $\frac{9\pi}{6} + \alpha$

$D_3$  from 0 to  $\frac{\pi}{2}$ ;  $T_3$  from  $\frac{9\pi}{6} + \alpha$  to  $2\pi + \alpha$

$D_1$  from  $\frac{\pi}{2}$  to  $\frac{7\pi}{6}$ ,  $T_1$



for  $\alpha > 60^\circ \rightarrow$  Discontinuous Output :

$$V_{dc} = \frac{3}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{7\pi}{6}} \sqrt{3} V_m \sin(\omega t - \frac{\pi}{6}) d\omega t$$

$$\Rightarrow V_{dc} = \frac{3\sqrt{3}}{2\pi} V_m (1 + \cos \alpha) = \frac{3V_{rms}}{2\pi} (1 + \cos \alpha)$$

max DC output at  $\alpha = 0 \Rightarrow V_{dc} = \frac{3\sqrt{3}}{\pi} V_m$

$$\Rightarrow V_{rms} = \left[ \frac{3}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{7\pi}{6}} V_{ac}^2 d\omega t \right]^{1/2}$$

$$= \sqrt{3} V_m \left[ \frac{3}{4\pi} (\pi - \alpha + \frac{\sin 2\alpha}{2}) \right]^{1/2}$$

for  $\alpha < 60^\circ \rightarrow$  Continuous :

$$V_{dc} = \frac{3}{2\pi} \left[ \int_{\frac{\pi}{6} + \alpha}^{\pi/2} V_{ab} d\omega t + \int_{\pi/2}^{\frac{5\pi}{6} + \alpha} V_{ac} d\omega t \right] = \frac{3\sqrt{3}}{2\pi} V_m (1 + \cos \alpha)$$


$$V_{rms} = \left[ \frac{3}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\pi/2} V_{ac}^2 d\omega t + \int_{\pi/2}^{\frac{5\pi}{6} + \alpha} V_{ac}^2 d\omega t \right]^{1/2} = \sqrt{3} V_m \left[ \frac{3}{4\pi} \left( \frac{2\pi}{3} + \sqrt{3} \cos^2 \alpha \right) \right]^{1/2}$$

$\rightarrow$  Three phase Full Converter is known as six pulse converter, used in industrial app. up to 120kW output power.

$\Rightarrow T_2$  triggered at  $\frac{\pi}{2} + \alpha$ ,  $T_6$  turn off naturally as it's RB as soon as  $T_2$  is triggered.

Thyristor Sequence of triggering:

12, 23, 34, 45, 56, 61, 12, 23, ...

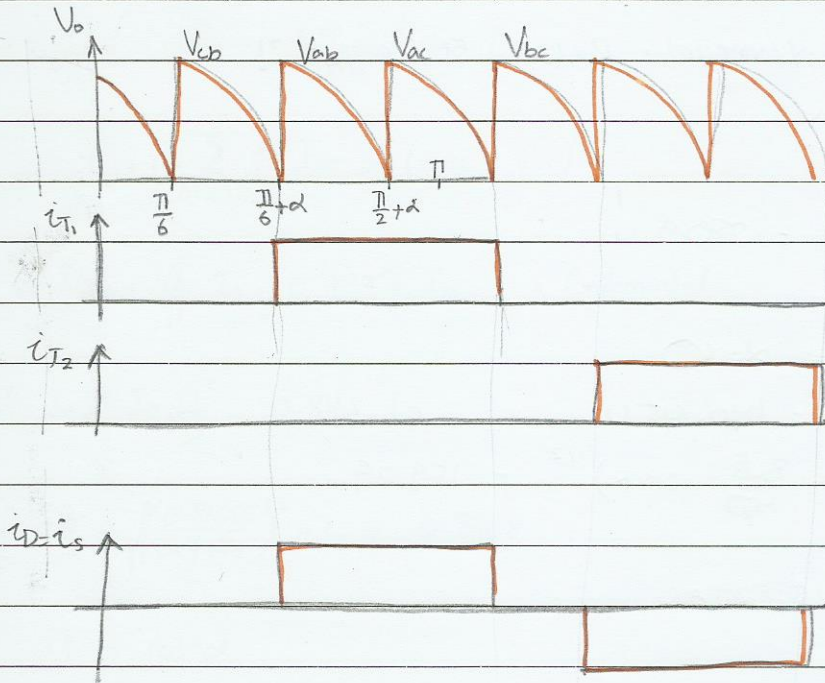

$i_o$  is constant.

• Thyristor are triggered at interval of  $\pi/3$

• the frequency of output ripple voltage is  $6f_s$


$$V_{dc} = \frac{6}{2\pi} \int_{\pi/6 + \alpha}^{\pi/2 + \alpha} V_o \, d\omega t$$

$\rightarrow v_o = v_{ab} = \sqrt{3} V_m \sin(\omega t + \frac{\pi}{6})$


$$\Rightarrow V_{dc} = \frac{3\sqrt{3}}{\pi} V_m \cos \alpha = \frac{3V_{mL}}{\pi} \cos \alpha$$

$\alpha > 90 \rightarrow -ve$  inverter  
 $\alpha < 90 \rightarrow +ve$  OR  
 $\alpha = 0 \rightarrow$  diode. converter
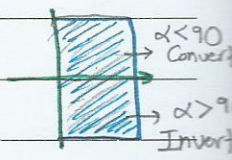
$$V_{rms} = \left( \frac{6}{2\pi} \int_{\pi/6 + \alpha}^{\pi/2 + \alpha} v_o^2 \, d\omega t \right)^{1/2} = \sqrt{3} V_m \left( \frac{1}{2} + \frac{3\sqrt{3}}{4\pi} \cos 2\alpha \right)^{1/2}$$



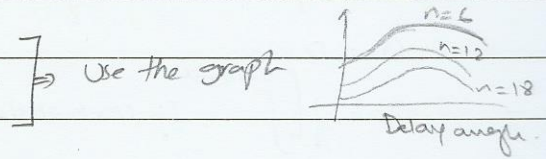• Note: increasing  $\alpha$  will increase harmonic  
 $\rightarrow$  min  $\alpha$  is 6<sup>th</sup> harmonic  
 max  $\alpha$  is 18<sup>th</sup> harmonic





Thursday 24<sup>th</sup>/Apr/2014

Lecture 27

• Example:  $V = 208 \text{ V}$ ,  $60 \text{ Hz}$ ,  $\gamma$  connected,  $R = 10 \Omega$ , 50% output ?!

$$V_m = \frac{208\sqrt{2}}{\sqrt{3}} = 169.83 \text{ V}$$

$$V_{dc(\max)} = \frac{3\sqrt{3}}{\pi} \frac{169.83}{\pi} = 280.9 \text{ V}$$

$$\cos \alpha = 0.5 \Rightarrow \alpha = 60^\circ$$

$$V_{dc} = 280.9 \times 0.5 = 140.45 \text{ V}$$

$$V_{rms} = \sqrt{3} V_m \left( \frac{1}{2} + \frac{3\sqrt{3}}{4\pi} \cos \alpha \right)^{1/2} = 159.29$$

$$I_{rms} = 159.29 / 10 = 15.929 \text{ A}$$

each thyristor:  $I_{dc} / \sqrt{3}$

$$I_{TDC} = \frac{14.045}{3} = 4.68 \text{ A}$$

$$I_{T(RMS)} = \frac{15.929}{\sqrt{3}} = 9.2 \text{ A}$$

$$I_s = 9.2\sqrt{2} = 13 \text{ A}$$

$$\eta = \frac{14.045^2 \times 10}{15.929^2 \times 10} = 77\%$$

$$TUF = \frac{14.045^2 \times 10}{\sqrt{3} \times 208 \times 9.2} = 0.421$$

$$PF = \frac{15.929^2 \times 10}{\sqrt{3} \times 208 \times 9.2} = 0.542 \text{ lags}$$

• Now in the case of highly Inductance :

$$a_0 = 0$$

$$a_n = \frac{1}{\pi} \left[ \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} I_a \cos n\omega t d\omega t - \int_{\frac{7\pi}{6} + \alpha}^{\frac{11\pi}{6} + \alpha} I_a \cos n\omega t d\omega t \right]$$

$$= \begin{cases} -4 I_a \frac{\sin n\pi}{3} \sin n\alpha & n = 1, 3, 5, \dots \\ 0 & n = 2, 4, 6, \dots \end{cases} \quad *$$

$$b_n = \frac{1}{\pi} \left[ \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} I_a \sin n\omega t d\omega t - \int_{\frac{7\pi}{6} + \alpha}^{\frac{11\pi}{6} + \alpha} I_a \sin n\omega t d\omega t \right]$$

$$= 4 \frac{I_a}{n\pi} \frac{\sin n\pi}{3} \cos n\alpha \rightarrow *$$

$$I_{sn} = \frac{1}{\sqrt{2}} \sqrt{a_n^2 + b_n^2} = \frac{2\sqrt{2} I_a}{n\pi} \sin \frac{n\pi}{3}$$

$$\therefore i_s(t) = \sum_{n=1,5,7,\dots} \sqrt{2} I_{sn} \sin(n\omega t + \phi_n)$$

$$\Rightarrow I_{s1} = \frac{\sqrt{6}}{\pi} I_a = 0.7797 I_a \quad \text{"fundamental"}$$

$$I_s = I_a \sqrt{\frac{2}{3}} = 0.8165 I_a$$

$$\Rightarrow HF = \sqrt{\left(\frac{0.81655}{0.7797}\right)^2 - 1} = 0.3108$$

$$DF = \cos \alpha$$

$$PF = \frac{0.7797}{0.8165} \times \cos \alpha \quad \#$$










# Power Factor Improvement:

- Extinction angle control
- Symmetrical angle Control
- pulse width modulation (PWM).

↳ Extinction angle Control:  $\equiv$  Semi-converter, Single phase.

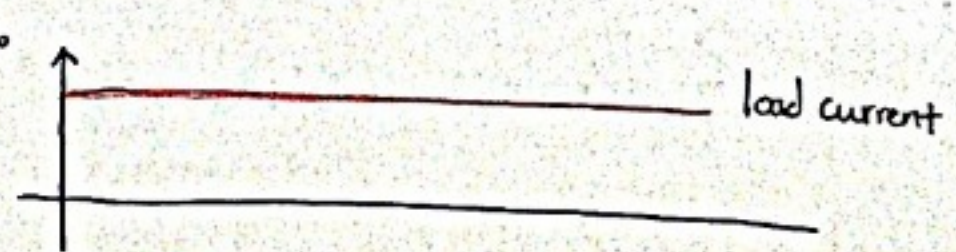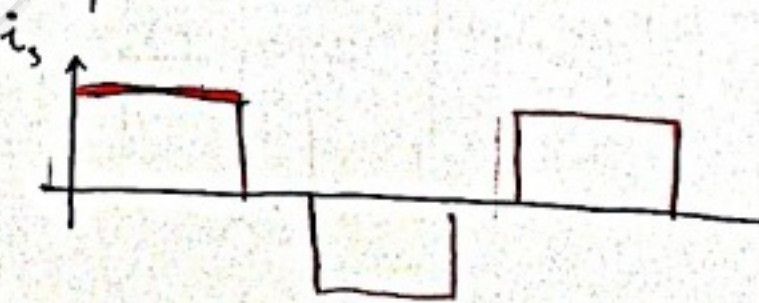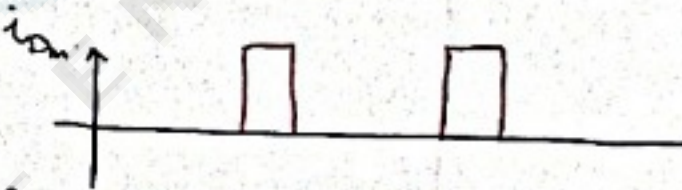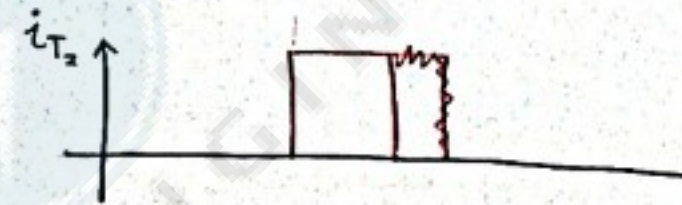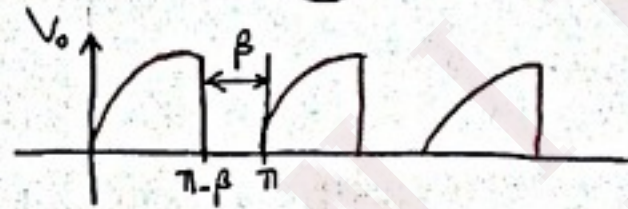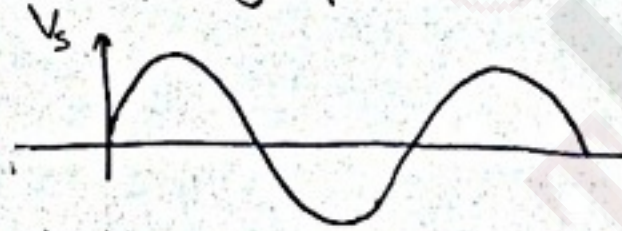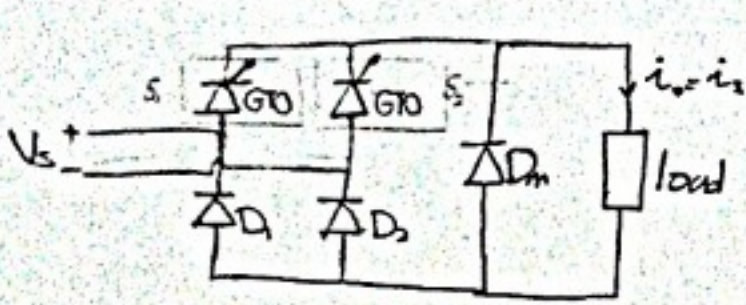$S_1, S_2 \Rightarrow$  Forced-commutated switches.



$$V_{dc} = \frac{2}{2\pi} \int_0^{\pi-\beta} V_m \sin \omega t \, d\omega t = \frac{V_m}{\pi} (1 + \cos \beta)$$


$$V_{rms} = \left[ \frac{2}{2\pi} \int_0^{\pi-\beta} V_m^2 \sin^2 \omega t \, d\omega t \right]^{1/2}$$

$$= \frac{V_m}{\sqrt{2}} \left[ \frac{1}{\pi} \left( \pi - \beta + \frac{\sin 2\beta}{2} \right) \right]^{1/2}$$

the switching <sup>action</sup> of  $S_1$  &  $S_2$  can be performed by GTO [gate turn-off thyristor], the characteristic of GTOs can be turned on by applying short positive pulse to its gate as in case of normal thyristor, & turned off by applying short negative impulse to its gate.

$\Rightarrow$  the extinction angle control,  $S_1$  &  $S_2$  :  
 $S_1$  : turned on at  $\omega t = 0$ , turned off at  $\omega t = \pi - \beta$   
 $S_2$  : turned on at  $\omega t = \pi$ , turned off at  $\omega t = 2\pi - \beta$

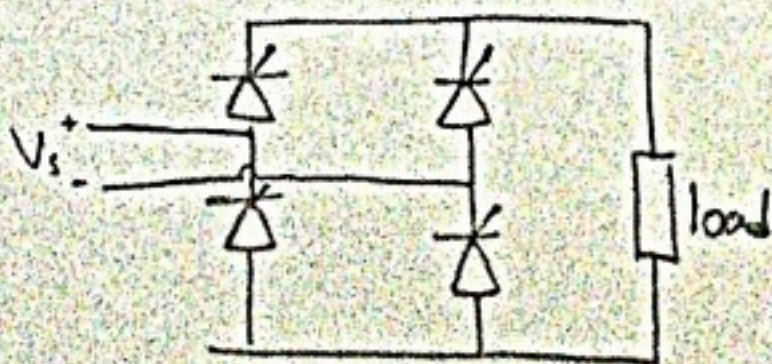Full converter  $\Rightarrow$  4 GTO's [we get rid of the FWD 'Dm'].





$\Rightarrow$  2 GTO's works at a time.

\* Notes  
 check out the slide  
 for sketches



↳ Symmetrical Angle Control:  $\equiv$  semi-converter with free-wheeling diode:

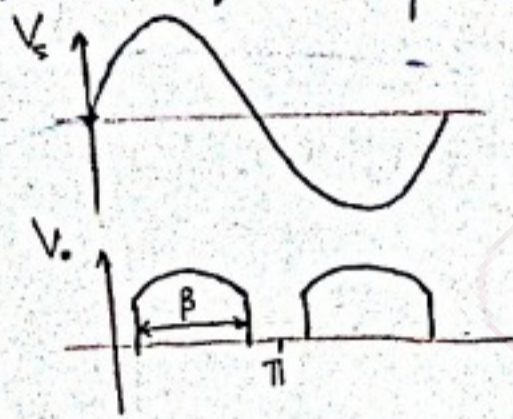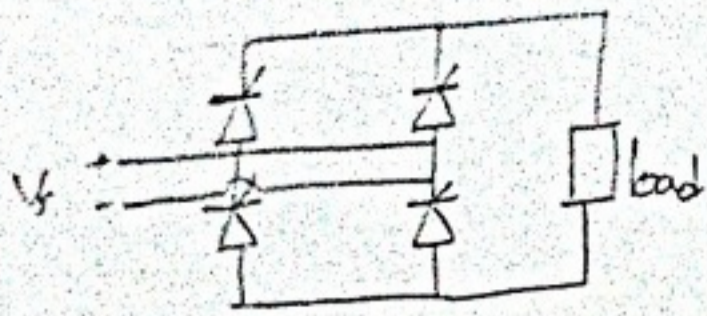The symmetrical angle control allows one quadrant operation



$$V_{dc} = \frac{2}{2\pi} \int_{\frac{\pi-\beta}{2}}^{\frac{\pi+\beta}{2}} V_m \sin \omega t \, d\omega t = \frac{2V_m}{\pi} \sin \frac{\beta}{2}$$

$$V_{rms} = \frac{2}{2\pi} \int_{\frac{\pi-\beta}{2}}^{\frac{\pi+\beta}{2}} V_m^2 \sin^2 \omega t \, d\omega t = \frac{V_m}{\sqrt{2}} \left[ \frac{1}{\pi} (\beta + \sin \beta) \right]^{1/2}$$

→ Express the input current in Fourier series;

$$i_s(t) = I_a + \sum_{n=1,2,\dots}^{\infty} a_n \cos n\omega t + b_n \sin n\omega t$$

$$a_0 = \frac{1}{2\pi} \int_{\frac{\pi-\beta}{2}}^{\frac{\pi+\beta}{2}} I_a \, d\omega t - \frac{1}{2\pi} \int_{\frac{3\pi-\beta}{2}}^{\frac{3\pi+\beta}{2}} I_a \, d\omega t = 0$$

$$a_n = \frac{1}{\pi} \int_0^{2\pi} i_s(t) \cos n\omega t \, d\omega t = 0$$

$$b_n = \frac{1}{\pi} \int_0^{2\pi} i_s(t) \sin n\omega t \, d\omega t = \frac{4I_a}{n\pi} \sin \frac{n\beta}{2} \quad \text{For } n \text{ odd}$$

$$= 0 \quad \text{For } n \text{ even}$$

$$\Rightarrow i_s(t) = \sum_{n=1,3,\dots}^{\infty} \sqrt{2} I_n \sin(n\omega t + \phi_n) \rightarrow \tan^{-1} \frac{a_n}{b_n} = 0$$

The rms value of the  $n^{\text{th}}$  harmonic input:  $I_n = \frac{1}{\sqrt{2}} (a_n^2 + b_n^2)^{1/2} = \frac{2\sqrt{2}}{n\pi} I_a \sin \frac{n\beta}{2}$

The rms value of the fundamental:  $I_{s1} = \frac{2\sqrt{2}}{\pi} I_a \sin \frac{\beta}{2}$

The rms input current:  $I_s = I_a \sqrt{\frac{\beta}{\pi}}$

$$HF = \left[ \left( \frac{I_s}{I_{s1}} \right)^2 - 1 \right]^{1/2}$$

$$DF = \cos \phi_1 = 1$$

$$PF = \left( \frac{I_{s1}}{I_s} \right) DF$$



→ if  $\beta = \frac{\pi}{3}$ ,  $DF = 1$ : Find  $V_{rms}$ ,  $I_{s1}$ ,  $I_s$ , HF, PF?  $V_m = 169.83$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \left[ \frac{1}{\pi} (\beta + \sin \beta) \right]^{1/2} = \frac{169.83}{\sqrt{2}} \left[ \frac{1}{\pi} \left( \frac{\pi}{3} + \sin 60 \right) \right]^{1/2} = 93.72 \text{ V}$$

$$V_{dc} = \frac{2V_m}{\pi} \sin \frac{\beta}{2} = \frac{2 \times 169.83}{\pi} \sin 30 = 54.06 \text{ V}$$

$$I_s = I_a \sqrt{\frac{\beta}{\pi}} = 0.5774 I_a$$



$$I_{s1} = \frac{2\sqrt{2}}{n\pi} I_a \sin \frac{n\beta}{2} = \frac{2\sqrt{2}}{\pi} I_a \sin \frac{\beta}{2} = 0.4502 I_a$$

$$\Rightarrow HF = \left[ \left( \frac{I_s}{I_{s1}} \right)^2 - 1 \right]^{1/2} = 0.803$$

$$PF = \left( \frac{I_{s1}}{I_s} \right) DF = 0.797 \text{ lagging} \quad \#$$

→ Pulse Width Modulation

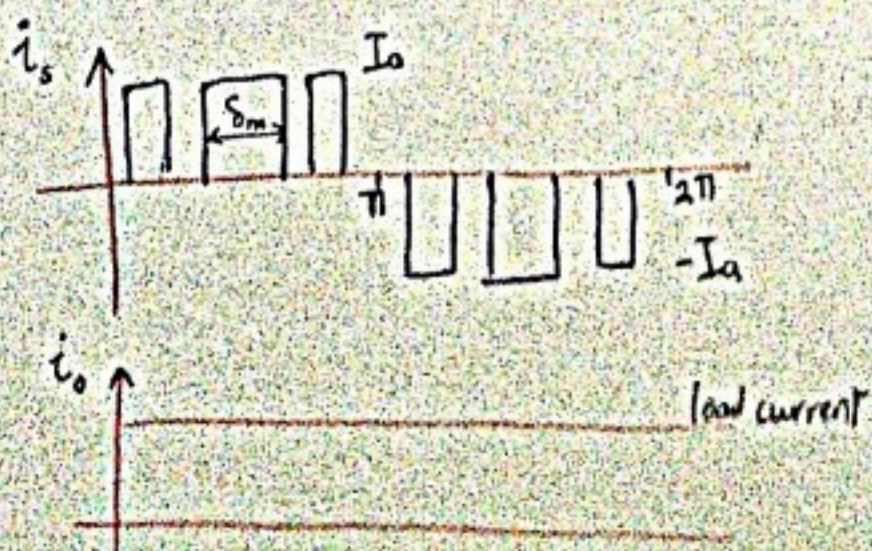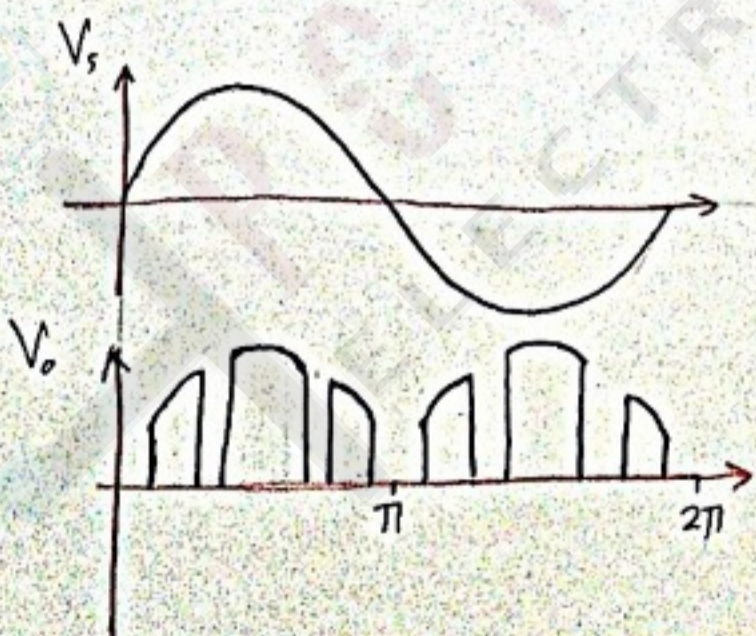If the output voltage of a single phase semi- or full converters is controlled by varying the delay angle, extinction angle or symmetrical angle, there's only one pulse per half cycle and as a result the lowest order harmonic is the third. In pulse width modulation, the converter switches are turned on and off several times during a half-cycle.



$$V_{dc} = \sum_{m=1}^p \frac{2}{2\pi} \int_{\alpha_m}^{\alpha_m + \delta_m} V_m \sin \omega t \, d\omega t$$

$$= \frac{V_m}{\pi} \sum_{m=1}^p [\cos \alpha_m - \cos(\alpha_m + \delta_m)]$$

$$i_s(t) = \frac{V_m}{\pi} \left( A_0 + \sum_{n=1,3,\dots}^{\infty} \frac{A_n}{\text{zero}} \cos n\omega t + \frac{B_n}{\text{zero}} \sin n\omega t \right)$$

$$= \frac{1}{\pi} \int_{\alpha_m}^{\alpha_m + \delta_m} i_s(t) \sin n\omega t \, d\omega t$$

$$\text{For odd } n \Rightarrow \frac{4I_a}{n\pi} \sum \sin\left(\frac{2\delta_m}{4}\right) \left[ \sin\left(n\left(\alpha_m + \frac{3\delta_m}{4}\right)\right) - \sin\left[n\left(\alpha_m + \frac{\delta_m}{4} + \pi\right)\right] \right]$$

For even  $n \Rightarrow$  zero

$$\Rightarrow i_s(t) = \sum_{n=1,3,\dots}^{\infty} \sqrt{2} \frac{I_n}{n} \sin(n\omega t + \phi_n)$$

$\frac{1}{\sqrt{2}} (A_n^2 + B_n^2)^{1/2} = \frac{R_n}{\sqrt{2}}$



Sinusoidal Pulse Width Modulation: the same as pulse width modulation, but instead of comparing it with DC, compare it with a Full wave rectifier sinusoidal.

بأنه هنا قطع قطب في الجهد  
 يكون في البداية، أيضاً قليل  
 في الوسط كبير.

In a sinusoidal PWM control, the DF is unity & PF is improved, the lower order harmonics are eliminated or reduced, for example with four pulses per half cycle the lowest order harmonic is the fifth; and with six pulses per half cycle the lowest order harmonic is the seventh.

\* Modulation Index  $\equiv M = \frac{A_c}{A_r}$

$0 < M < 1$

carrier voltage  
 reference voltage





# DC Chopper: [DC → DC] converter

• two types of choppers:


1. step-up:

$$V_{out} \gg V_{in}$$

2. step-down:

$$V_{out} < V_{in}$$


→ principle of step-down chopper:

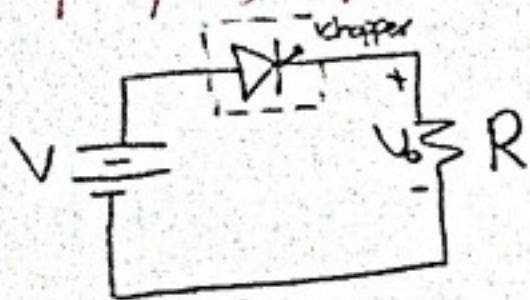

• the thyristor acts as a switch

→ when thyristor is ON  $\Rightarrow V_o = V$

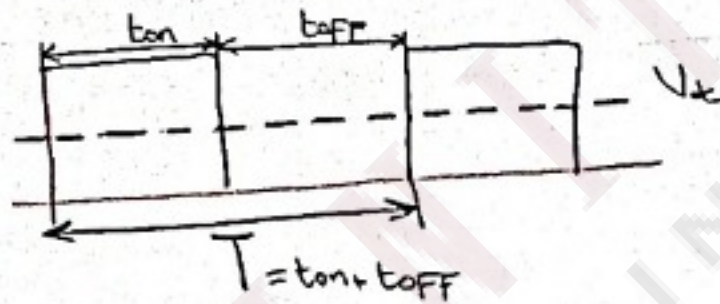→ when thyristor is OFF  $\Rightarrow V_o = 0$



$$V_{dc} = V \left( \frac{t_{on}}{t_{on} + t_{off}} \right) = V \left( \frac{t_{on}}{T} \right) = VD$$

Duty cycle  $\equiv D$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^{t_{on}} V_o^2 dt} = \sqrt{D} V$$


$$P_{output} = \frac{DV^2}{R}$$

the effective input resistance of chopper:  $R_i = \frac{R}{D}$


Note:   
 \* The output voltage can be varied by the duty cycle.

• Basic DC to DC converter:


1. Buck Converter:

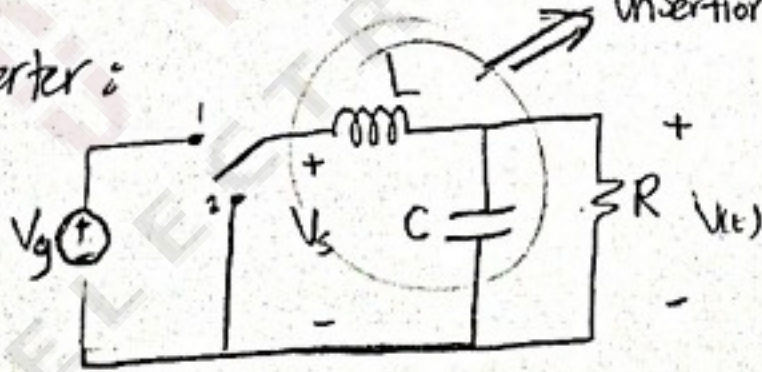

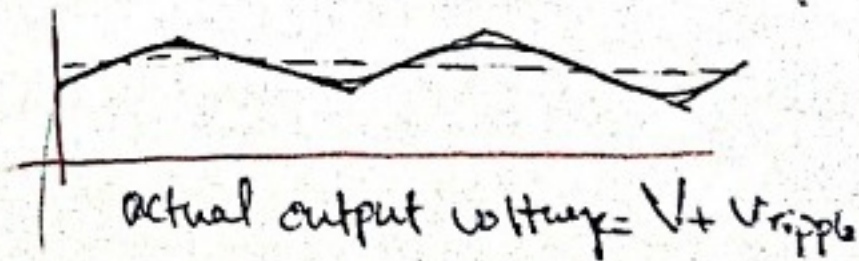insertion of low pass filter  $\Rightarrow$  to remove switching harmonic & pass only DC component



→ Buck converter analysis:

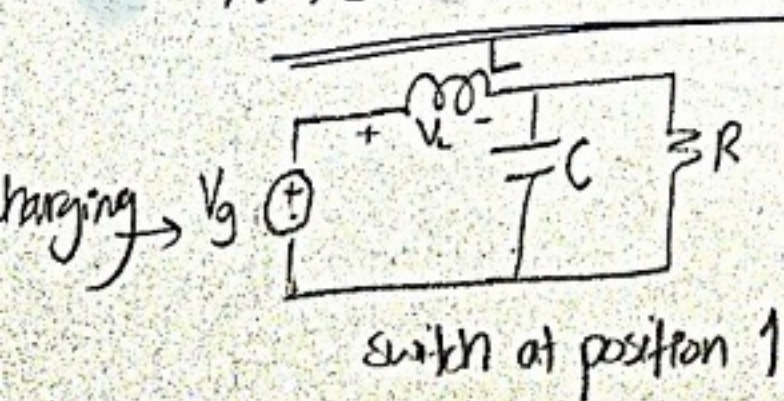


switch at position 1

$$V_L = V_g - V(t)$$

small ripple approximation:  $V_L = V_g - V$

$$\Rightarrow V_L(t) = L \frac{di(t)}{dt}$$
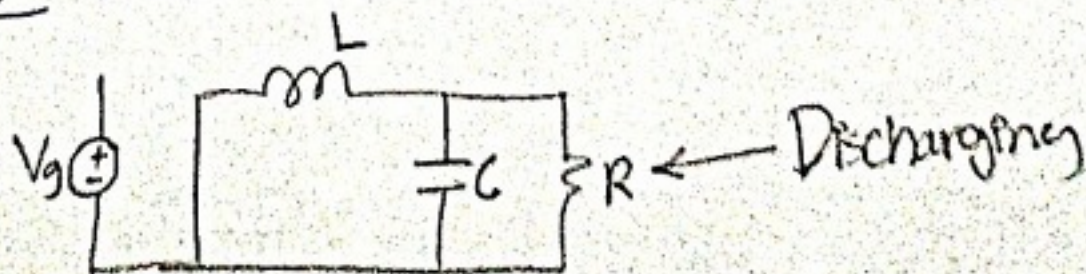
$$\Rightarrow di/dt = V_L(t)/L = (V_g - V)/L$$




switch at position 2

$$V_L = -V(t)$$

small ripple approximation:  $\Delta V$
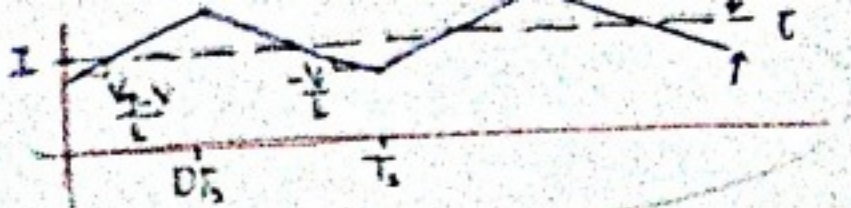
$$\Rightarrow \frac{di}{dt} = -\frac{V}{L}$$





transient


$$2C = \left(\frac{V_g - V}{L}\right) (DT_s)$$

$$\Rightarrow C = \frac{V_g - V}{2L} (DT_s)$$

$$\Rightarrow L = \frac{V_g - V}{2C} DT_s$$

the inductance if we want a fixed ripple

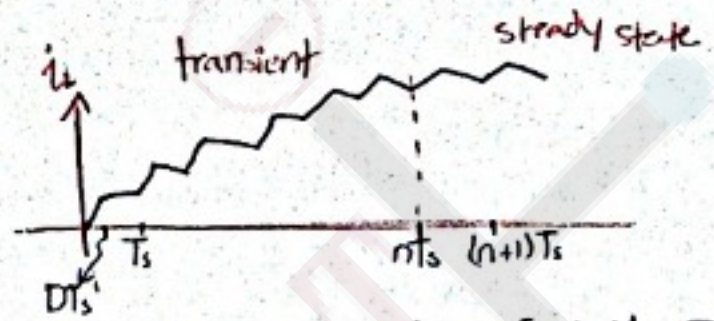
→ when converter operates in equilibrium:  
 $i_L(n+1)T_s = i_L(nT_s) \Rightarrow$  steady state




المساحة تحت منحنى "DQ" هي (في حالة التوازن) متساوية  
 المتوسطة في المحور

whenever the converter operates in steady state  
 → total area (volt/sec) under the inductor voltage waveform is zero.

## 2. Boost Converter:

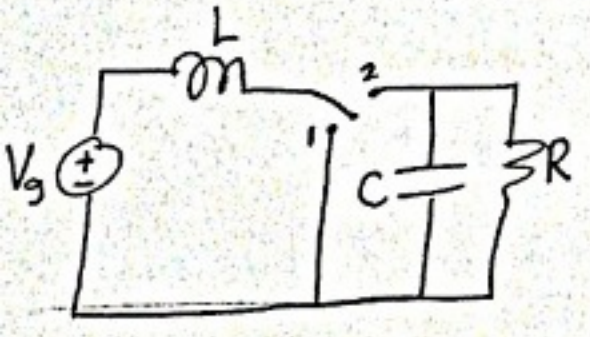


→ Boost Converter analysis:

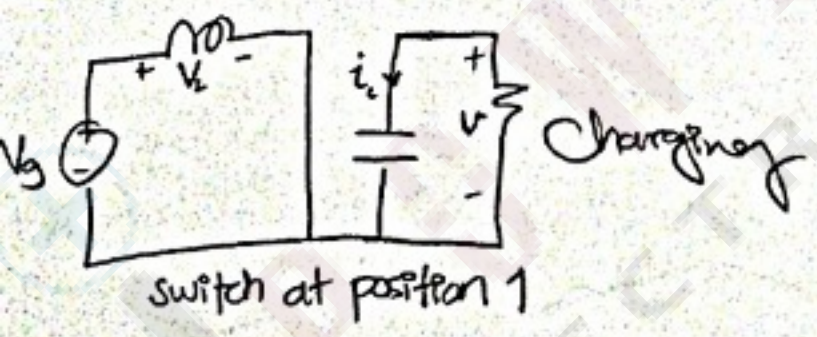

$$V_L = V_g$$

$$i_C = -\frac{V}{R}$$

small ripple approximation:  $V_L = V_g$

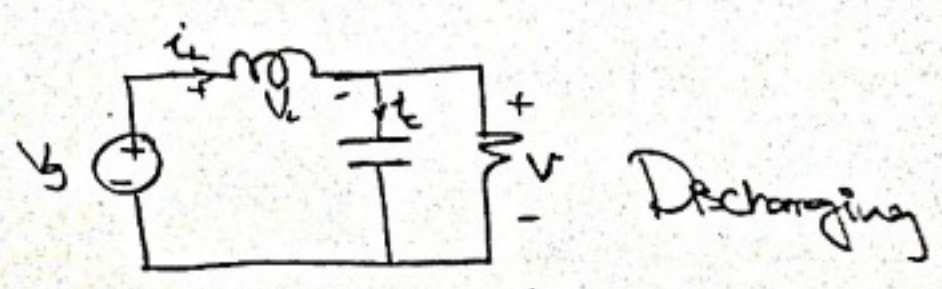


$$V_L = V_g - V$$

$$i_C = i_L - \frac{V}{R}$$

$V_g$ : avg. value (const)  
 $V$ : function of time

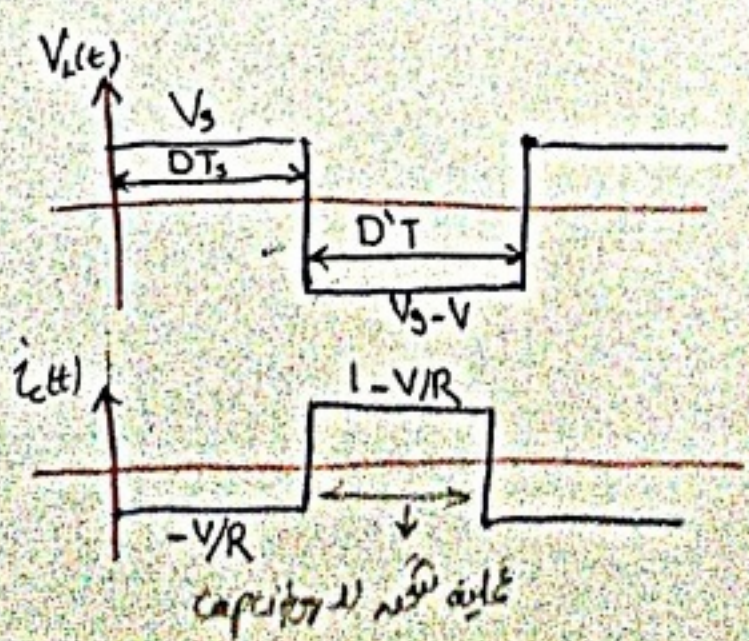small ripple approximation:  $V_L = V_g - V$



inductor volt/sec:  $\int_0^{T_s} V_L(t) dt = V_g DT_s + (V_g - V) D'T_s = 0$


$$\Rightarrow V = \frac{V_g}{D'} = \frac{V_g}{1-D}$$

the voltage conversion ratio

$$M = \frac{V}{V_g} = \frac{1}{D'} = \frac{1}{1-D}$$



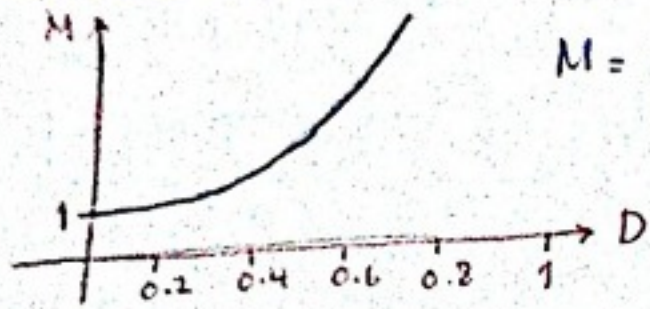→ Conversion ratio  $M(D)$  of the boost converter:



$$M = \frac{1}{D} = \frac{1}{1-D}$$

"starts from zero  $\rightarrow \infty$ "

• practically  $D \neq 0$  &  $D \neq 1 \Rightarrow$  so  $M$  will never reach 1 or  $\infty$ , since the switch isn't ideal.

→ ~~Continuous Conduction Mode (CCM) and Discontinuous Conduction Mode (DCM)~~

↳ Methods of Control:

the output DC voltage can be varied by:

1. PWM control or constant frequency operation
2. Variable frequency control.


↳ 1. PWM: Output voltage is varied by varying the ON time.

↳ 2. Variable Frequency Control: chopping freq. is varied keeping  $t_{on}$  or  $t_{off}$  constant.

• to obtain full output voltage range  $\Rightarrow$  freq. has to be varied over a wide range.

• this method produces harmonic in the output & for large  $t_{off}$  load current  $\Rightarrow$  it may be discontinuous.

→ principle of Step Up Chopper:

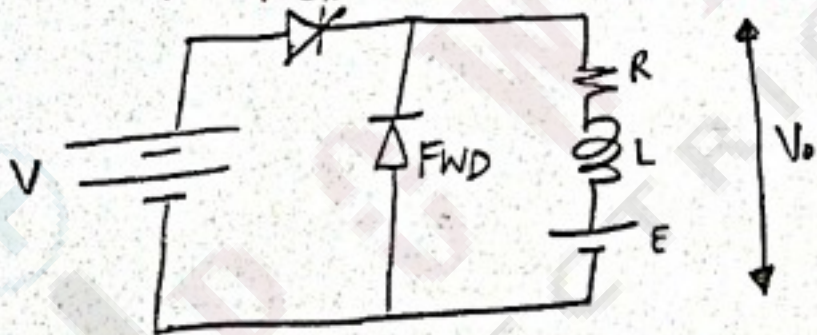


• when chopper is ON  $\Rightarrow$  supply is connected across the load current flows from supply  $\rightarrow$  load.

• when chopper is off  $\Rightarrow$  load current continues flow in the same direction through FWD

• load current can be continuous or discontinuous depends on: value of  $L$  & Duty cycle.


• For continuous current operation, load current varies between  $I_{max}$  &  $I_{min}$

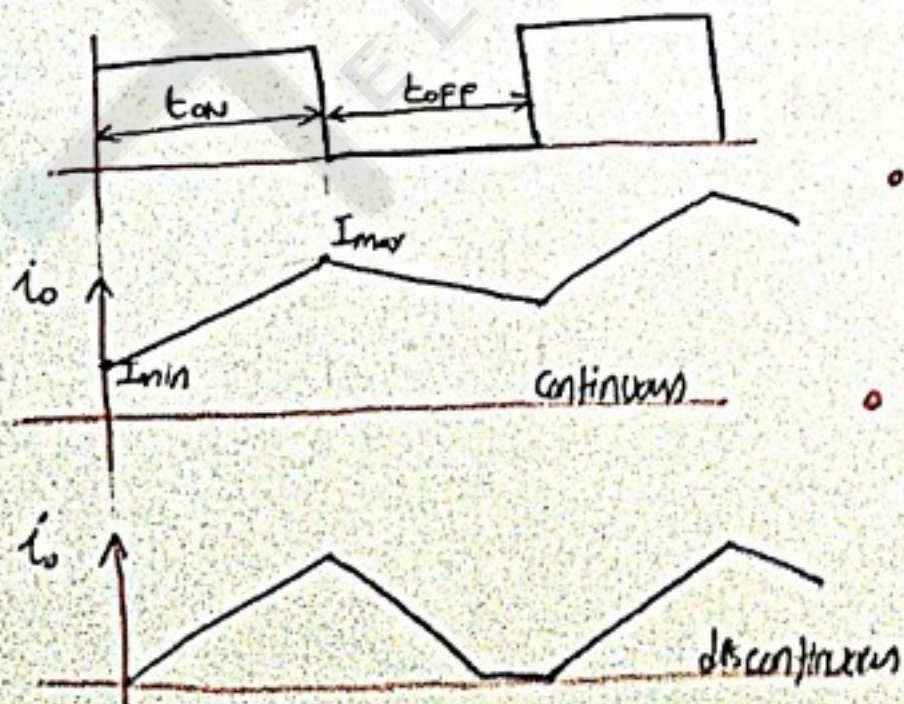• when  $I = I_{max} \Rightarrow$  the chopper turned off  
when  $I$  reduces to  $I_{min} \Rightarrow$  chopper is ON.





↳ when Chopper is ON:  $0 < t < t_{on}$

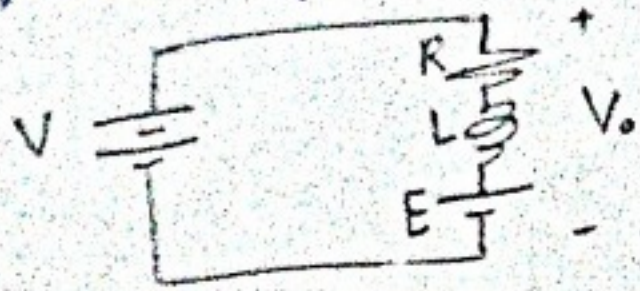

$$V = i_o R + L \frac{di_o}{dt} + E$$

$$\Rightarrow \text{taking Laplace transform: } \frac{V}{s} = R I_o(s) + L [s I_o(s) + i_o] + \frac{E}{s}$$

at  $t=0$ ,  $i_o(0^-) = I_{min}$ :

$$I_o(s) = \frac{V-E}{L(s + \frac{R}{L})} + \frac{I_{min}}{s + \frac{R}{L}}$$

↳ taking the Inverse:

$$i_o(t) = \frac{V-E}{R} [1 - e^{-t(\frac{R}{L})}] + I_{min} e^{-\frac{R}{L}t}$$

↳ when chopper is OFF:  $0 < t < t_{off}$

$$i_o(t) = I_{max} e^{-\frac{R}{L}t} - \frac{E}{R} [1 - e^{-\frac{R}{L}t}]$$

# Check out the derivation

to find  $I_{max}$  &  $I_{min}$ :

$$I_{max} = \frac{V}{R} \left[ \frac{1 - e^{-\frac{RDT}{L}}}{1 - e^{-\frac{RT}{L}}} \right] - \frac{E}{R}$$

$$I_{min} = \frac{V}{R} \left[ \frac{e^{-\frac{RDT}{L}} - 1}{e^{-\frac{RT}{L}} - 1} \right] - \frac{E}{R}$$

→  $(I_{max} - I_{min})$  known as steady state ripple.

$$V_{dc} = VD$$

$$I_{dc} = \frac{I_{max} + I_{min}}{2}$$


$$\Delta I = I_{max} - I_{min}$$



### Classification Of Choppers

- Choppers are classified as
  - Class A Chopper
  - Class B Chopper
  - Class C Chopper
  - Class D Chopper
  - Class E Chopper



### Class A Chopper

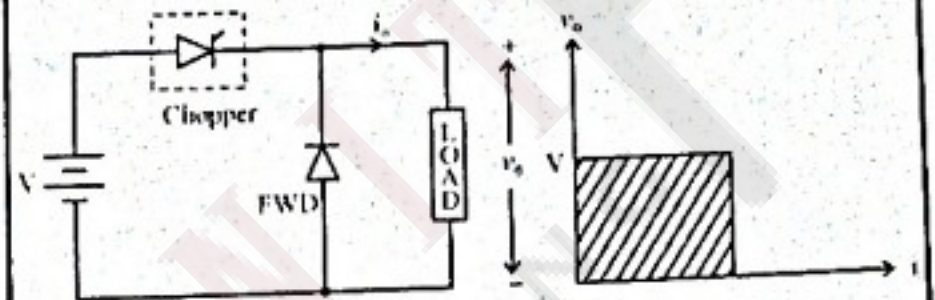

- When chopper is *ON*, supply voltage  $V$  is connected across the load.
- When chopper is *OFF*,  $v_o = 0$  and the load current continues to flow in the same direction through the FWD.
- The average values of output voltage and current are always positive.
- *Class A Chopper* is a first quadrant chopper.

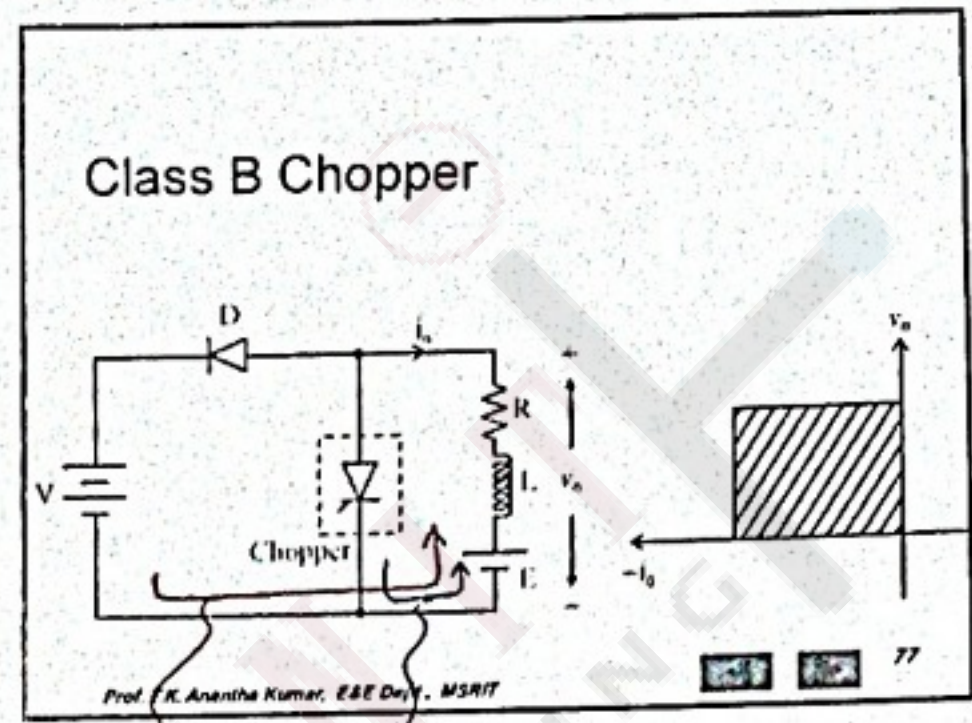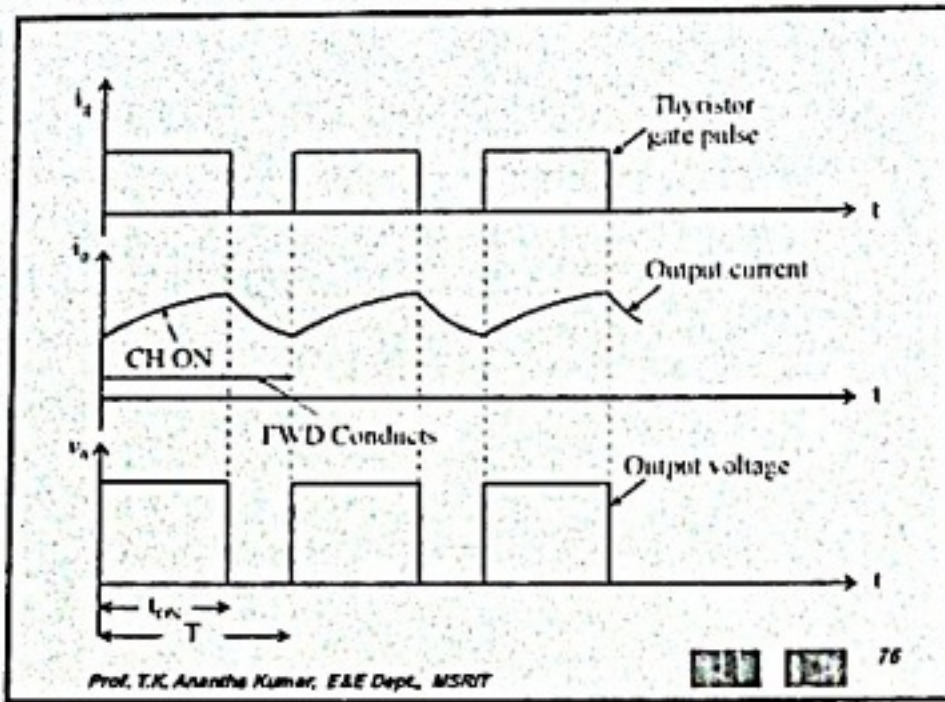- *Class A Chopper* is a step-down chopper in which power always flows from source to load.
- It is used to control the speed of dc motor.
- The output current equations obtained in step down chopper with  $R-L$  load can be used to study the performance of *Class A Chopper*.







if chopper is OFF, stored power in  $L$  will be discharged and return to the source.

if chopper is ON a current always  $-i_a$  of voltage  $+v_a$   
 $\rightarrow$  then  $E$  will work as generator and keep the generated power in  $L$

- When chopper is ON,  $E$  drives a current through  $L$  and  $R$  in a direction opposite to that shown in figure.
- During the ON period of the chopper, the inductance  $L$  stores energy.
- When Chopper is OFF, diode  $D$  conducts, and part of the energy stored in inductor  $L$  is returned to the supply.

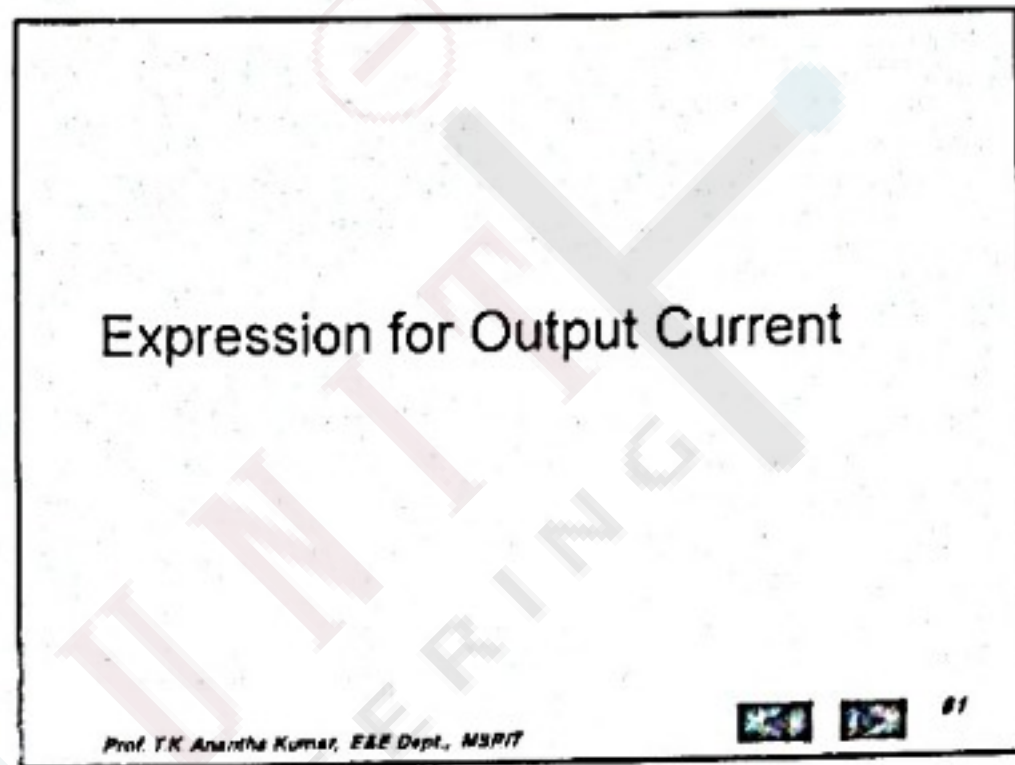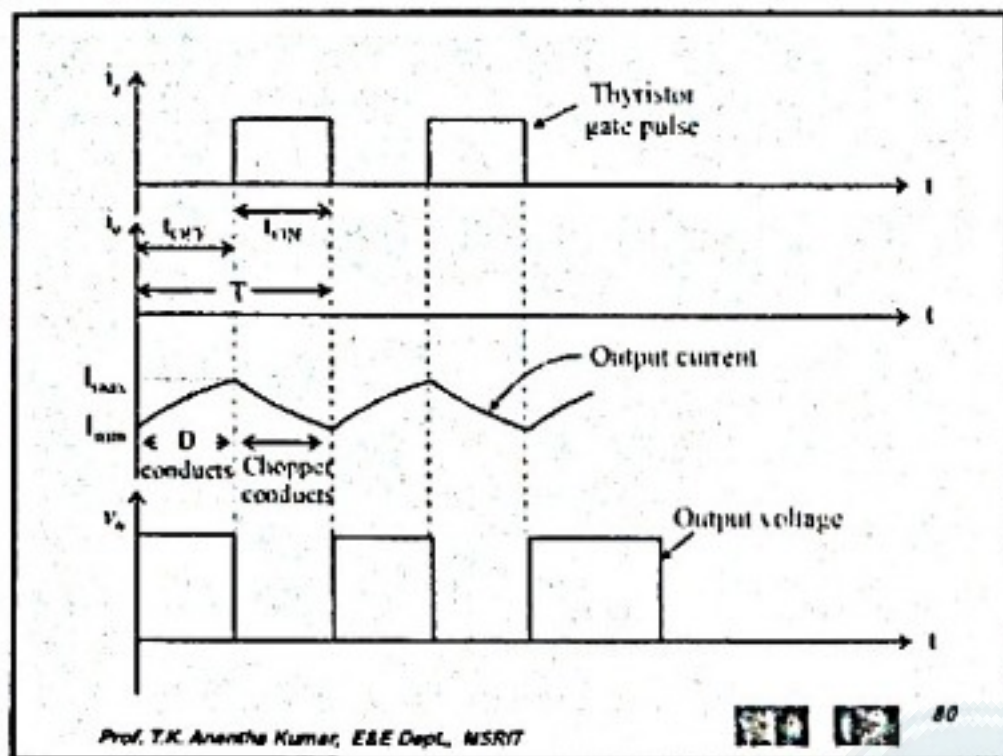- Average output voltage is positive.
- Average output current is negative.
- Therefore *Class B Chopper* operates in second quadrant.
- In this chopper, power flows from load to source.
- *Class B Chopper* is used for regenerative braking of dc motor. (محرمانی (4) تم یقیناً (source) الی)
- *Class B Chopper* is a step-up chopper.





During the interval diode 'D' conducts voltage equation is given by

$$V = \frac{L di_o}{dt} + Ri_o + E$$

For the initial condition i.e.,

$$i_o(t) = I_{min} \text{ at } t = 0$$

The solution of the above equation is obtained along similar lines as in step-down chopper with R-L load

$$\therefore i_o(t) = \frac{V-E}{R} \left( 1 - e^{-\frac{R}{L}t} \right) + I_{min} e^{-\frac{R}{L}t} \quad 0 < t < t_{OFF}$$

$$\text{At } t = t_{OFF} \quad i_o(t) = I_{max}$$

$$I_{max} = \frac{V-E}{R} \left( 1 - e^{-\frac{R}{L}t_{OFF}} \right) + I_{min} e^{-\frac{R}{L}t_{OFF}}$$

During the interval chopper is ON voltage equation is given by

$$0 = \frac{L di_o}{dt} + Ri_o + E$$



Redefining the time origin, at  $t = 0$   $i_o(t) = I_{max}$


The solution for the stated initial condition is

$$i_o(t) = I_{max} e^{-\frac{R}{L}t} - \frac{E}{R} \left( 1 - e^{-\frac{R}{L}t} \right) \quad 0 < t < t_{ON}$$

At  $t = t_{ON}$   $i_o(t) = I_{min}$

$$\therefore I_{min} = I_{max} e^{-\frac{R}{L}t_{ON}} - \frac{E}{R} \left( 1 - e^{-\frac{R}{L}t_{ON}} \right)$$

Class C Chopper = class A + class B

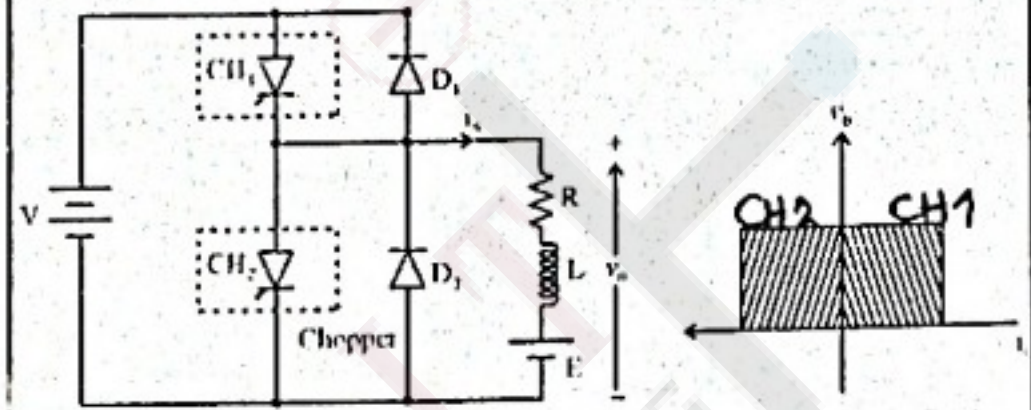

- Class C Chopper is a combination of Class A and Class B Choppers.
- For first quadrant operation, CH<sub>1</sub> is ON or D<sub>2</sub> conducts.
- For second quadrant operation, CH<sub>2</sub> is ON or D<sub>1</sub> conducts.
- When CH<sub>1</sub> is ON, the load current is positive.
- The output voltage is equal to 'V' & the load receives power from the source.
- When CH<sub>1</sub> is turned OFF, energy stored in inductance L forces current to flow through the diode D<sub>2</sub> and the output voltage is zero.

Free wheeling Diode


- Current continues to flow in positive direction.
- When CH<sub>2</sub> is triggered, the voltage E forces current to flow in opposite direction through L and CH<sub>2</sub>.
- The output voltage is zero.
- On turning OFF CH<sub>2</sub>, the energy stored in the inductance drives current through diode D<sub>1</sub> and the supply
- Output voltage is V, the input current becomes negative and power flows from load to source.

class C  $\Rightarrow$  class A: Motor  
class B: Regenerator



- Average output voltage is positive
- Average output current can take both positive and negative values.
- Choppers  $CH_1$  &  $CH_2$  should not be turned ON simultaneously as it would result in short circuiting the supply.
- *Class C Chopper* can be used both for dc motor control and regenerative braking of dc motor.
- *Class C Chopper* can be used as a step-up or step-down chopper.

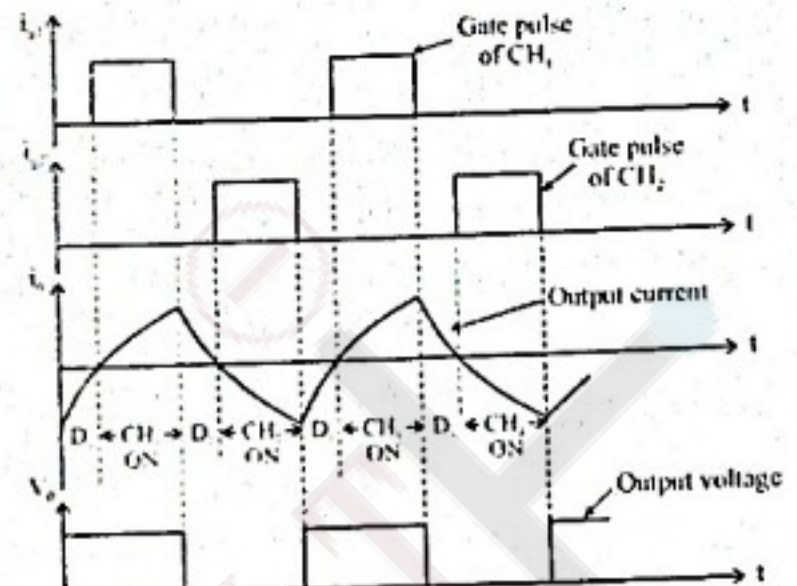
Prof. T.K. Anantha Kumar, E&E Dept., MSRIT




Prof. T.K. Anantha Kumar, E&E Dept., MSRIT



### Class D Chopper

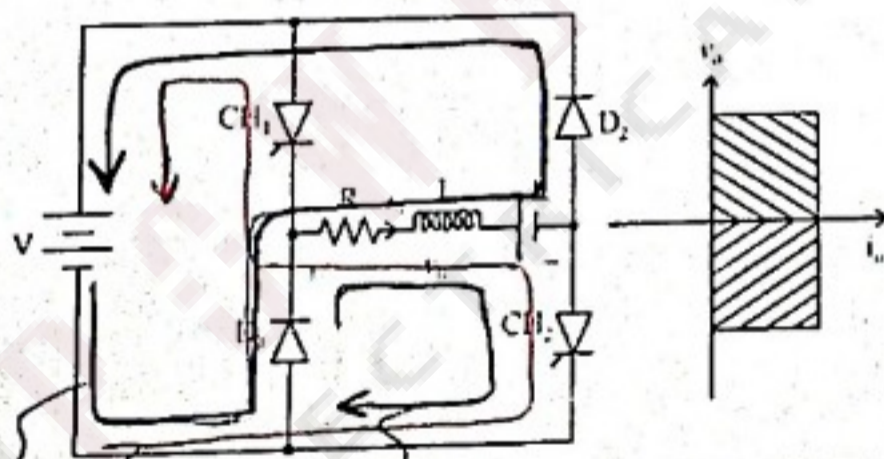

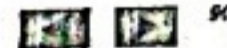Prof. T.K. Anantha Kumar, E&E Dept., MSRIT



- Class D is a two quadrant chopper.
- When both  $CH_1$  and  $CH_2$  are triggered simultaneously, the output voltage  $v_o = V$  and output current flows through the load.
- When  $CH_1$  and  $CH_2$  are turned OFF, the load current continues to flow in the same direction through load,  $D_1$  and  $D_2$ , due to the energy stored in the inductor  $L$ .
- Output voltage  $v_o = -V$ .

Prof. T.K. Anantha Kumar, E&E Dept., MSRIT





IF CH1 is OFF

if CH1 & CH2 works at the same time


if CH1 & CH2 are OFF, voltage will be negative, current flows in the same direction as before.



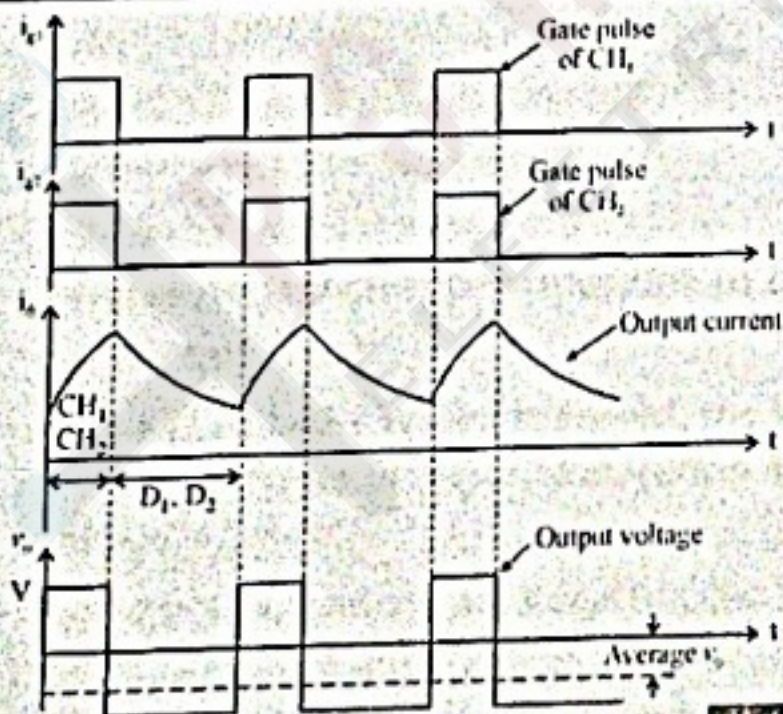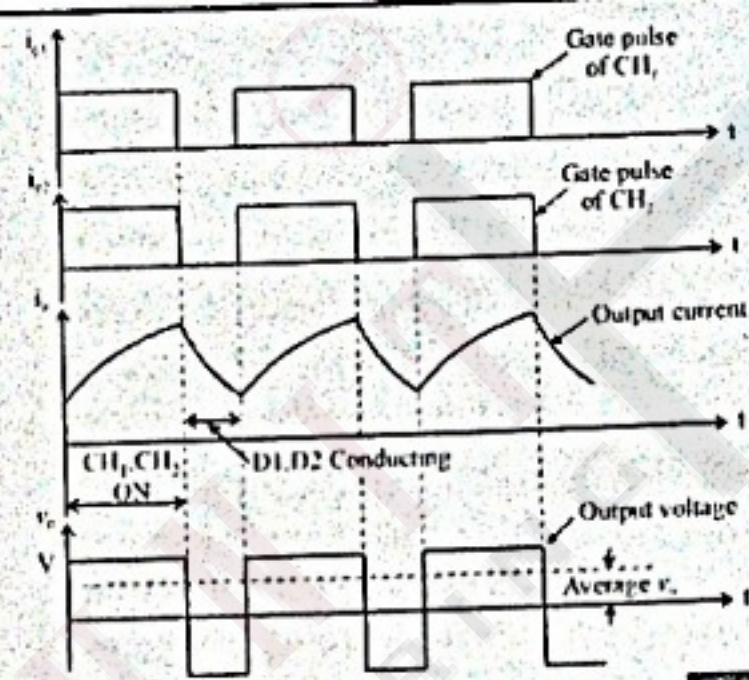- Average load voltage is positive if chopper ON time is more than the OFF time
- Average output voltage becomes negative if  $t_{ON} < t_{OFF}$ .
- Hence the direction of load current is always positive but load voltage can be positive or negative.


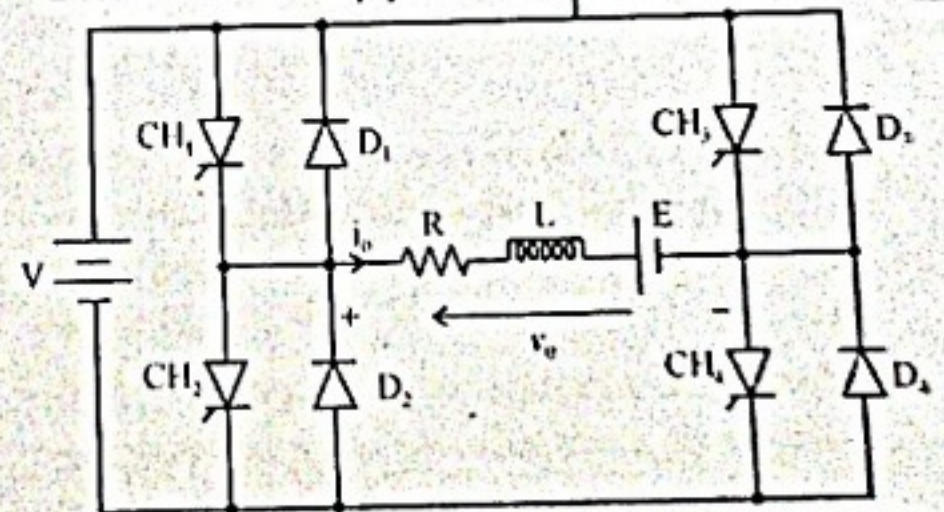
### Class E Chopper comparison of class D & E






for each quadrant there are two equivalent cks

→ ∴ we have 8 equivalent

### Four Quadrant Operation

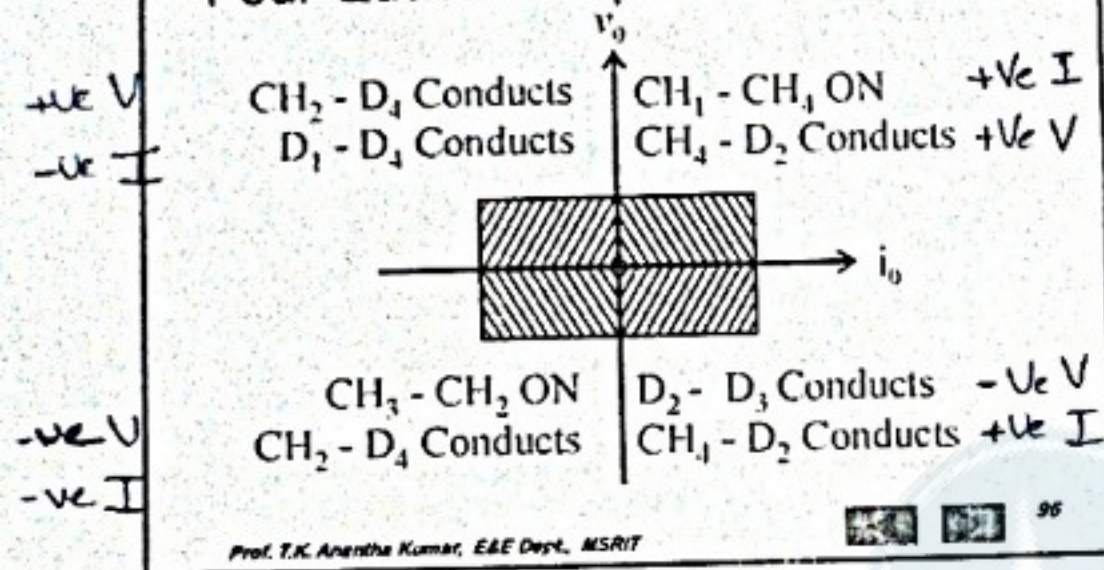

- Class E is a four quadrant chopper
- When  $CH_1$  and  $CH_4$  are triggered, output current  $i_o$  flows in positive direction through  $CH_1$  and  $CH_4$ , and with output voltage  $v_o = V$ .
- This gives the first quadrant operation.
- When both  $CH_1$  and  $CH_4$  are OFF, the energy stored in the inductor  $L$  drives  $i_o$  through  $D_2$  and  $D_3$  in the same direction, but output voltage  $v_o = -V$ .

Prof. T.K. Anantha Kumar, E&E Dept., MSRIT

- Therefore the chopper operates in the fourth quadrant.
- When  $CH_2$  and  $CH_3$  are triggered, the load current  $i_o$  flows in opposite direction & output voltage  $v_o = -V$ .
- Since both  $i_o$  and  $v_o$  are negative, the chopper operates in third quadrant.

Prof. T.K. Anantha Kumar, E&E Dept., MSRIT


- When both  $CH_2$  and  $CH_3$  are OFF, the load current  $i_o$  continues to flow in the same direction  $D_1$  and  $D_4$  and the output voltage  $v_o = V$ .
- Therefore the chopper operates in second quadrant as  $v_o$  is positive but  $i_o$  is negative.

Prof. T.K. Anantha Kumar, E&E Dept., MSRIT



# Impulse Commutated Chopper

→ away to force the thyristor to stop.

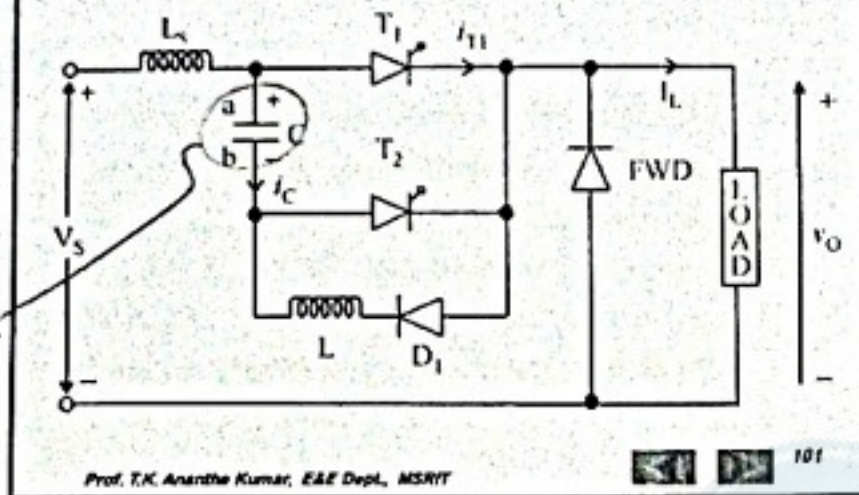


یولڈ ہینڈ لڈی  
زیدہ کاتھاب  
thyristor

- To start the circuit, capacitor 'C' is initially charged with polarity (with plate 'a' positive) by triggering the thyristor  $T_2$ .
- Capacitor 'C' gets charged through  $V_s$ ,  $C$ ,  $T_2$  and load.
- As the charging current decays to zero thyristor  $T_2$  will be turned-off.
- With capacitor charged with plate 'a' positive the circuit is ready for operation.
- Assume that the load current remains constant during the commutation process.

• For convenience the chopper operation is divided into five modes.

- Mode-1
- Mode-2
- Mode-3
- Mode-4
- Mode-5

## Mode-1 Operation

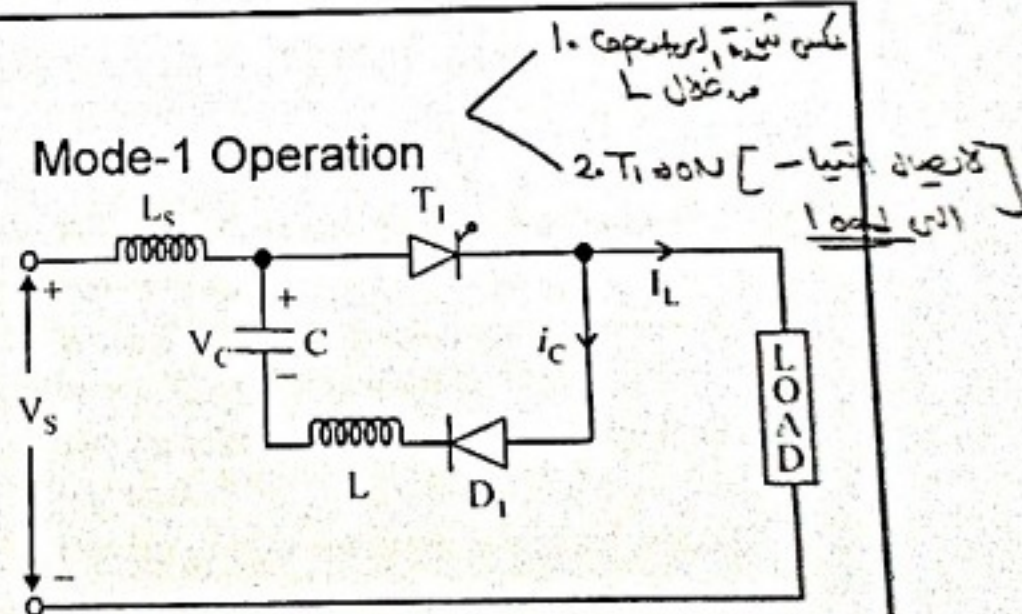



- Thyristor  $T_1$  is fired at  $t = 0$ .
- The supply voltage comes across the load.
- Load current  $I_L$  flows through  $T_1$  and load.
- At the same time capacitor discharges through  $T_1$ ,  $D_1$ ,  $L_1$ , & 'C' and the capacitor reverses its voltage.
- This reverse voltage on capacitor is held constant by diode  $D_1$ .

## Capacitor Discharge Current


$$i_c(t) = V \sqrt{\frac{C}{L}} \sin \omega t$$

Where  $\omega = \frac{1}{\sqrt{LC}}$

& Capacitor Voltage

$$V_c(t) = V \cos \omega t$$

## Mode-2 Operation

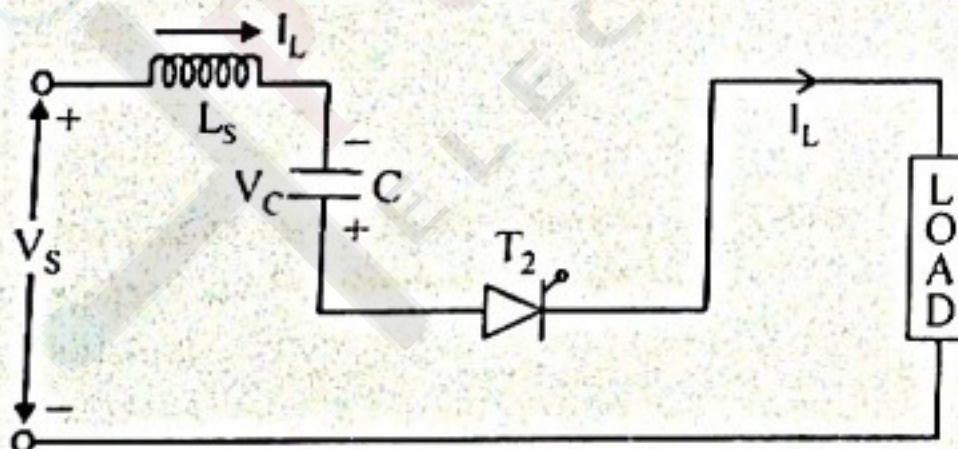

$T_1 \rightarrow \text{OFF}$   
 $T_2 \rightarrow \text{ON}$

mode 1  $\rightarrow$  ON  
mode 2 }  
mode 3 }  $\rightarrow$   $\left. \begin{array}{l} \text{مفتاح انتقالية (تحتوي)} \\ \text{OFF} \end{array} \right\}$   
mode 4 }  
mode 5  $\rightarrow$  OFF

- Thyristor  $T_2$  is now fired to commutate thyristor  $T_1$ .
- When  $T_2$  is ON capacitor voltage reverse biases  $T_1$  and turns it off.
- The capacitor discharges through the load from  $-V$  to  $0$ .
- Discharge time is known as circuit turn-off time.



Circuit turn-off time is given by

$$t_c = \frac{\overset{\text{max}}{V_c} \times C}{\underset{\text{max}}{I_L}} \rightarrow \text{gives min time for this mode.}$$

Where  $I_L$  is load current.

$t_c$  depends on load current, it must be designed for the worst case condition which occur at the maximum value of load current and minimum value of capacitor voltage.

- Capacitor recharges back to the supply voltage (with plate 'a' positive).
- This time is called the recharging time and is given by


$$t_d = \frac{V_s \times C}{I_L}$$

- The total time required for the capacitor to discharge and recharge is called the commutation time and it is given by  $t_r = t_c + t_d$

- At the end of Mode-2 capacitor has recharged to  $V_s$  and the free wheeling diode starts conducting.

Mode-3 Operation

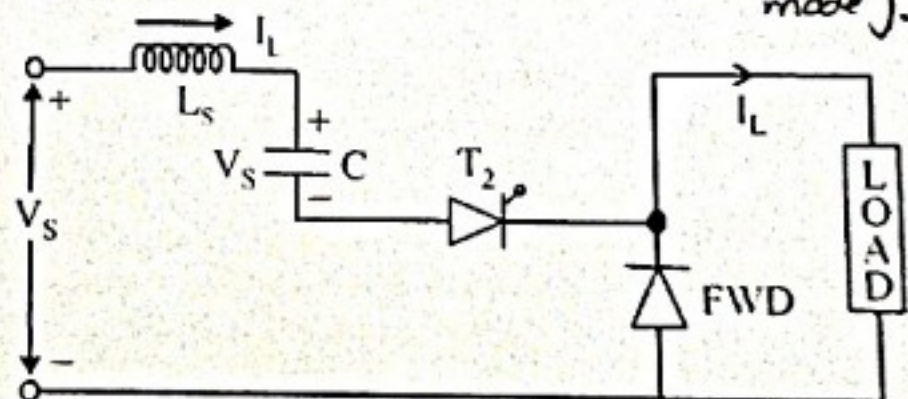FWD  $\Rightarrow$  ON (فرد بنفیس کتب یفیر)   
  $T_2 \Rightarrow$  OFF [at the end of this mode].





- *FWD* starts conducting and the load current decays.
- The energy stored in source inductance  $L_S$  is transferred to capacitor.
- Hence capacitor charges to a voltage higher than supply voltage,  $T_2$  naturally turns off.


The instantaneous capacitor voltage is

$$V_C(t) = V_S + I_L \sqrt{\frac{L_S}{C}} \sin \omega_S t$$

Where

$$\omega_S = \frac{1}{\sqrt{L_S C}}$$


### Mode-4 Operation

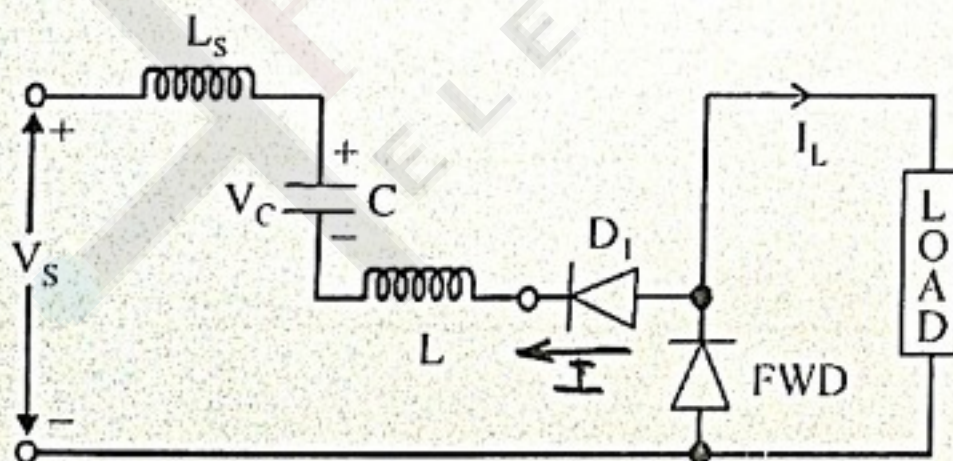

- Capacitor has been overcharged i.e. its voltage is above supply voltage.
- Capacitor starts discharging in reverse direction.
- Hence capacitor current becomes negative.
- The capacitor discharges through  $L_S$ ,  $V_S$ , *FWD*,  $D_1$  and  $L$ .
- When this current reduces to zero  $D_1$  will stop conducting and the capacitor voltage will be same as the supply voltage





## Mode-5 Operation

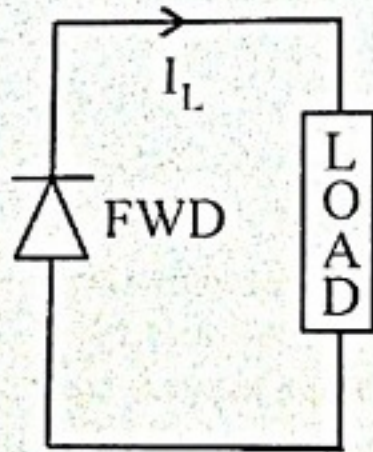


- Both thyristors are off and the load current flows through the FWD.
- This mode will end once thyristor  $T_1$  is fired.

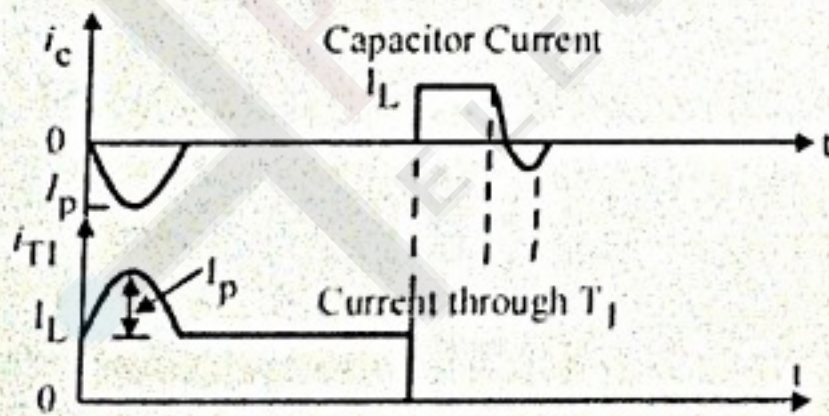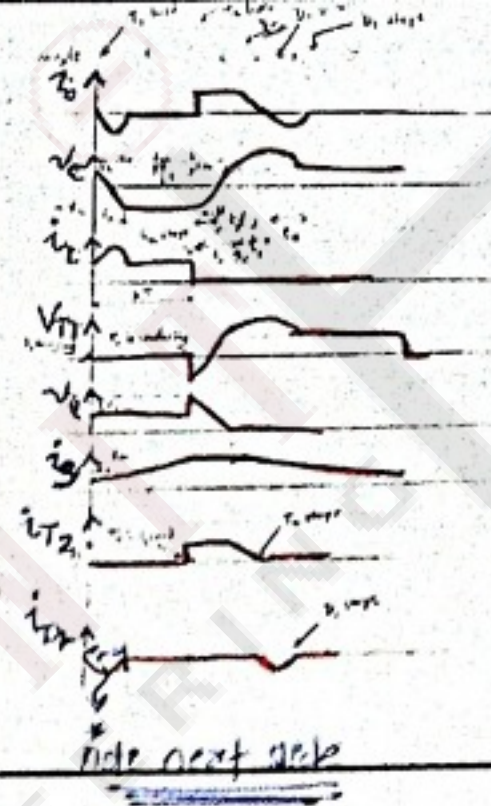Prof. T.K. Anantha Kumar, E&E Dept., MSRIT



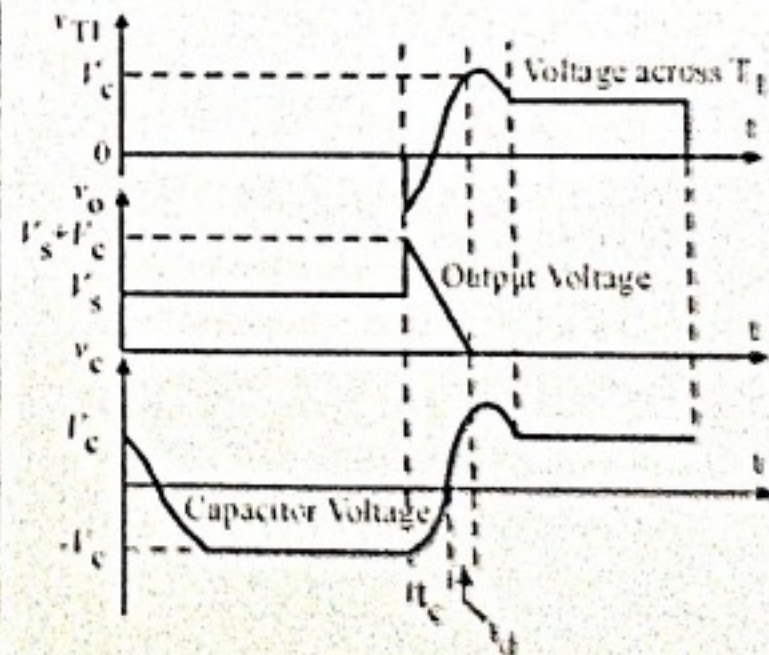Prof. T.K. Anantha Kumar, E&E Dept., MSRIT



Prof. T.K. Anantha Kumar, E&E Dept., MSRIT





## Disadvantages

- A starting circuit is required and the starting circuit should be such that it triggers thyristor  $T_2$  first.
- Load voltage jumps to almost twice the supply voltage when the commutation is initiated.
- The discharging and charging time of commutation capacitor are dependent on the load current and this limits high frequency operation, especially at low load current.

- Chopper cannot be tested without connecting load.
- Thyristor  $T_1$  has to carry load current as well as resonant current resulting in increasing its peak current rating.

$t_{on} \Rightarrow$  time for mode 1  $\Rightarrow t_{on\ min} =$  time of mode 1

$t_{off} \Rightarrow$  time for mode 2, 3, 4, 5  $\Rightarrow t_{off\ min} =$  time for 3+2+4

} so duty cycle can't be less than 5%, if  $\ast$  in graph ( $i_a$ ) is 5%.



# Chapter 4 AC to AC Converters

## Outline


4.1 AC voltage controllers

4.2 Other AC controllers

input : AC fixed

output : AC variable

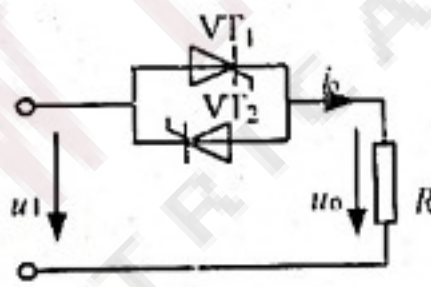
### 4.1.1 Single-phase AC voltage controller



The phase shift range (operation range of phase delay angle):

$$0 \leq \alpha \leq \pi$$

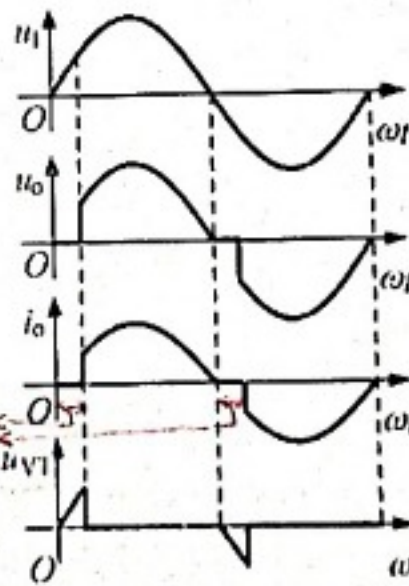*الزاوية التي يمتنع بها thyristor*  
*التي يمتنع بها thyristor*




Firing for thyristor

output current the same as output voltage

Voltage across the thyristor

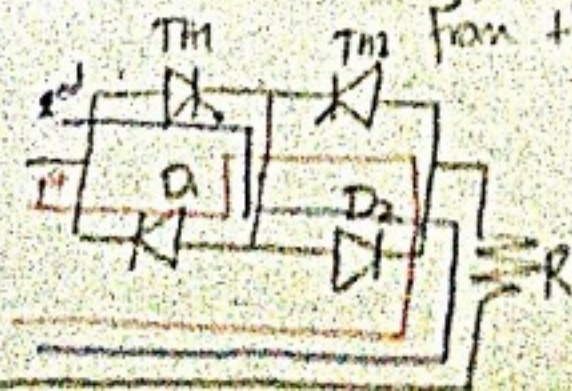• a problem occurs for this type of ckt's cathode for the 1<sup>st</sup> thyristor is connected to one end of the 2<sup>nd</sup> [when firing happens will give current for the gate (cathode)]  
 ⇒ so the problem is that we can't give current for two thyristor from the same source [different source, different earth each].





■ Resistive load, quantitative analysis

RMS value of output voltage

$$U_o = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} (\sqrt{2}U_1 \sin \omega t)^2 d(\omega t)} = U_1 \sqrt{\frac{1}{2\pi} \sin 2\alpha + \frac{\pi - \alpha}{\pi}} \quad (4-1)$$

same as Full wave rectifier just that 2<sup>nd</sup> thyristor is  $(-\sin)$

RMS value of output current

$$I_o = \frac{U_o}{R} \quad (4-2)$$

RMS value of thyristor current


$$I_T = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} \left( \frac{\sqrt{2}U_1 \sin \omega t}{R} \right)^2 d(\omega t)} = \frac{U_1}{R} \sqrt{\frac{1}{2} \left( 1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi} \right)} \quad (4-3)$$

Power factor of the circuit


$$\lambda = \frac{P}{S} = \frac{U_o I_o}{U_1 I_o} = \frac{U_o}{U_1} = \sqrt{\frac{1}{2\pi} \sin 2\alpha + \frac{\pi - \alpha}{\pi}} \quad (4-4)$$

Inductive (Inductor-resistor) load, operation principle

so delay occurs

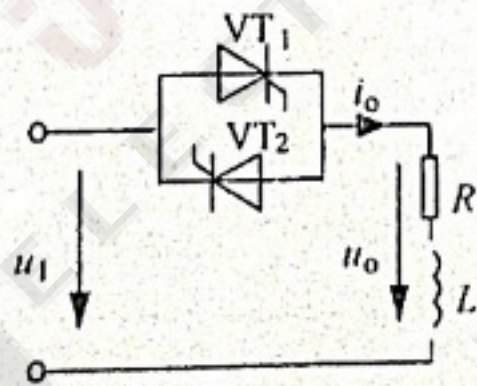

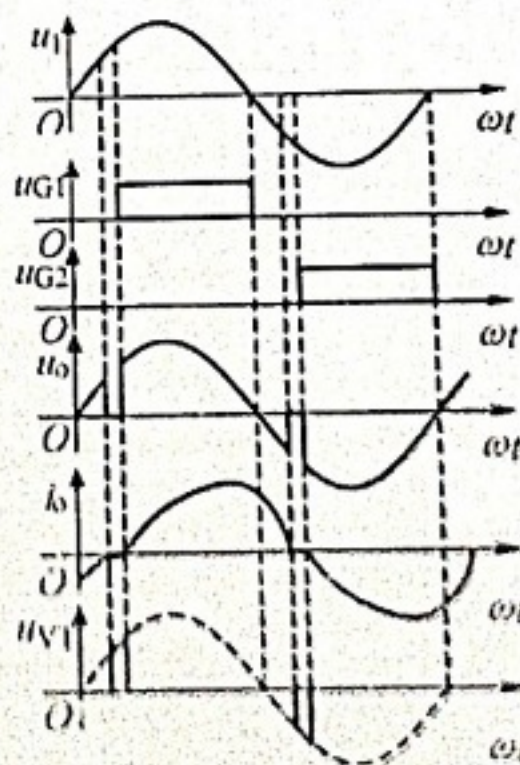The phase shift range:  
 $\varphi \leq \alpha \leq \pi$



if  $\theta$  large &  $X$  small  $\Rightarrow$  Continuous Output



**Inductive load, quantitative analysis**  
 Differential equation

$$L \frac{di_o}{dt} + Ri_o = \sqrt{2}U_1 \sin \omega t$$

$$i_o|_{\omega t = \alpha} = 0 \quad (4-5)$$


Solution

$$i_o = \frac{\sqrt{2}U_1}{Z} \left[ \sin(\omega t - \varphi) - \sin(\alpha - \varphi)e^{-\frac{R}{L}(\omega t - \alpha)} \right] \quad \alpha \leq \omega t \leq \alpha + \theta \quad (4-6)$$

Considering  $i_o = 0$  when  $\omega t = \alpha + \theta$

$$\text{We have} \quad \sin(\alpha + \theta - \varphi) = \sin(\alpha - \varphi)e^{-\frac{R}{L}\theta} \quad (4-7)$$

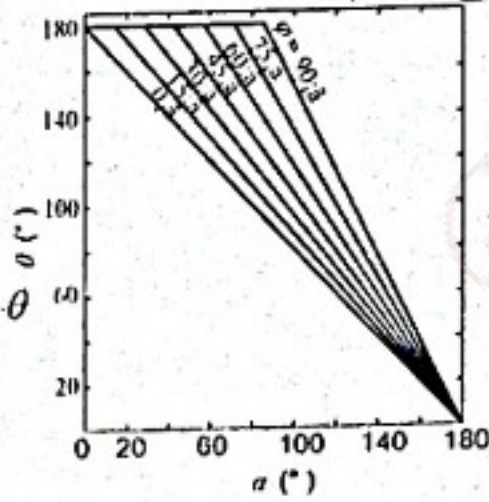
same as Full wave but here there's a +ve part & a -ve part [in full wave it's always +ve]




The RMS value of output voltage, output current, and thyristor current can then be calculated.

**4.1.2 Three-phase AC voltage controller**


Classification of three-phase circuits

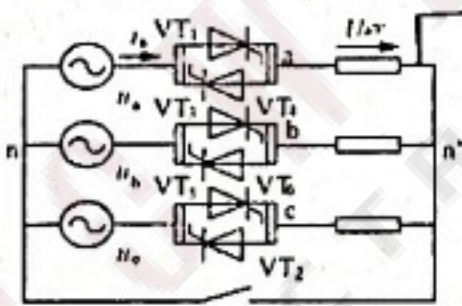


Y connection

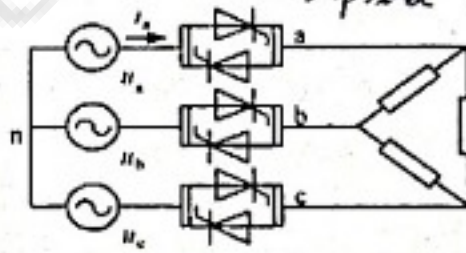

Line-controlled  $\Delta$  connection

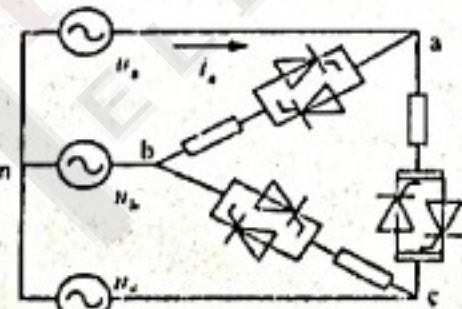


Branch-controlled  $\Delta$  connection

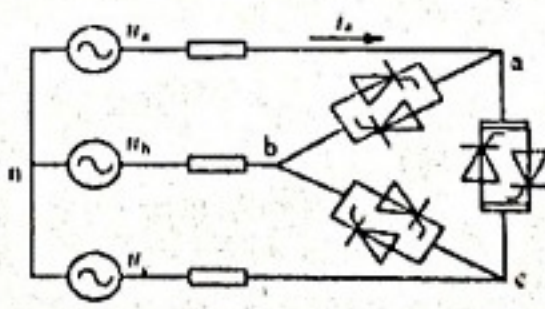

Neutral-point controlled  $\Delta$  connection

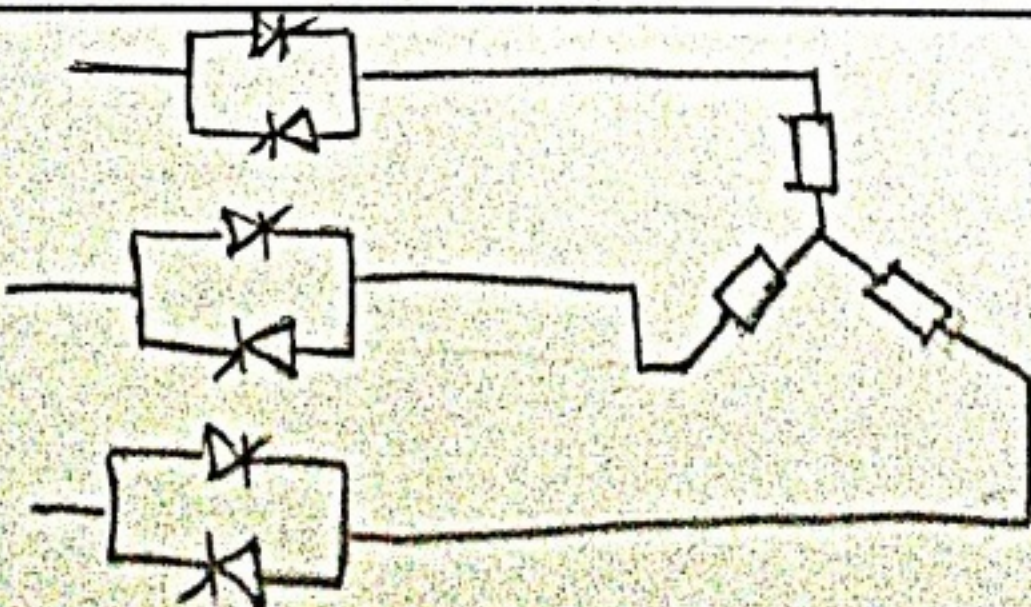یہ تینوں تھائریسٹروں کو 2 phase connected line to line




If one thyristor doesn't work it won't be three phase anymore,  $\Rightarrow$  it will be two phase connected line to line.

3ON  $\Rightarrow$  3P  $\Rightarrow$   $V_p = V_c$

2ON  $\Rightarrow$  line to line / 2  $\Rightarrow$   $V_p = V_c / 2$



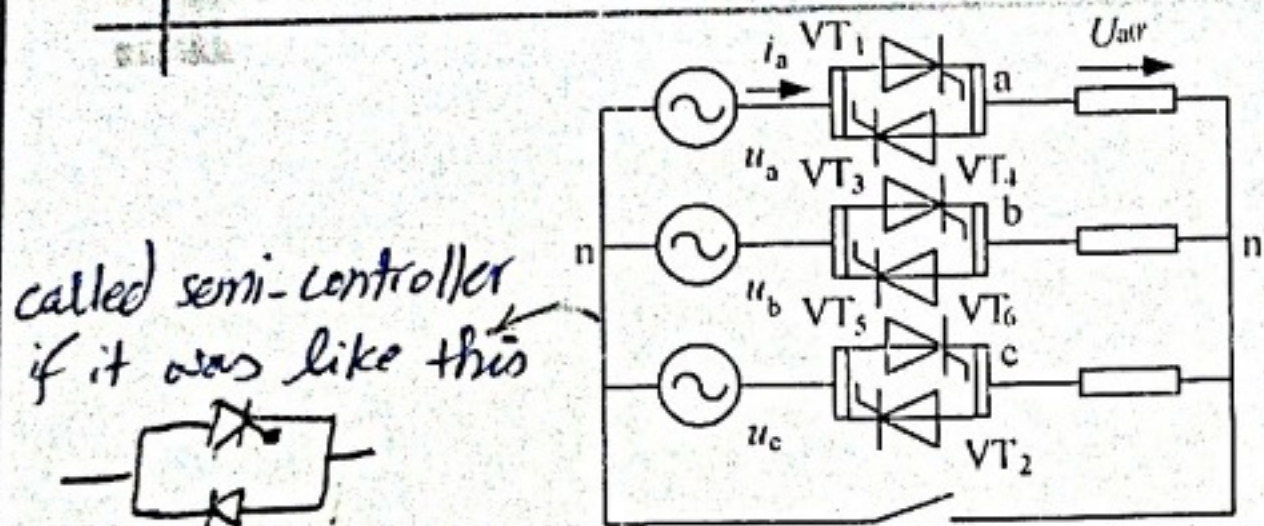▪ 3- phase 3- wire Y connection AC voltage controller




For a time instant, there are 2 possible conduction states:

- Each phase has a thyristor conducting. Load voltages are the same as the source voltages.
- There are only 2 thyristors conducting, each from a phase. The load voltages of the two conducting phases are half of the corresponding line to line voltage, while the load voltage of the other phase is 0.

## 4.2 Other AC controllers
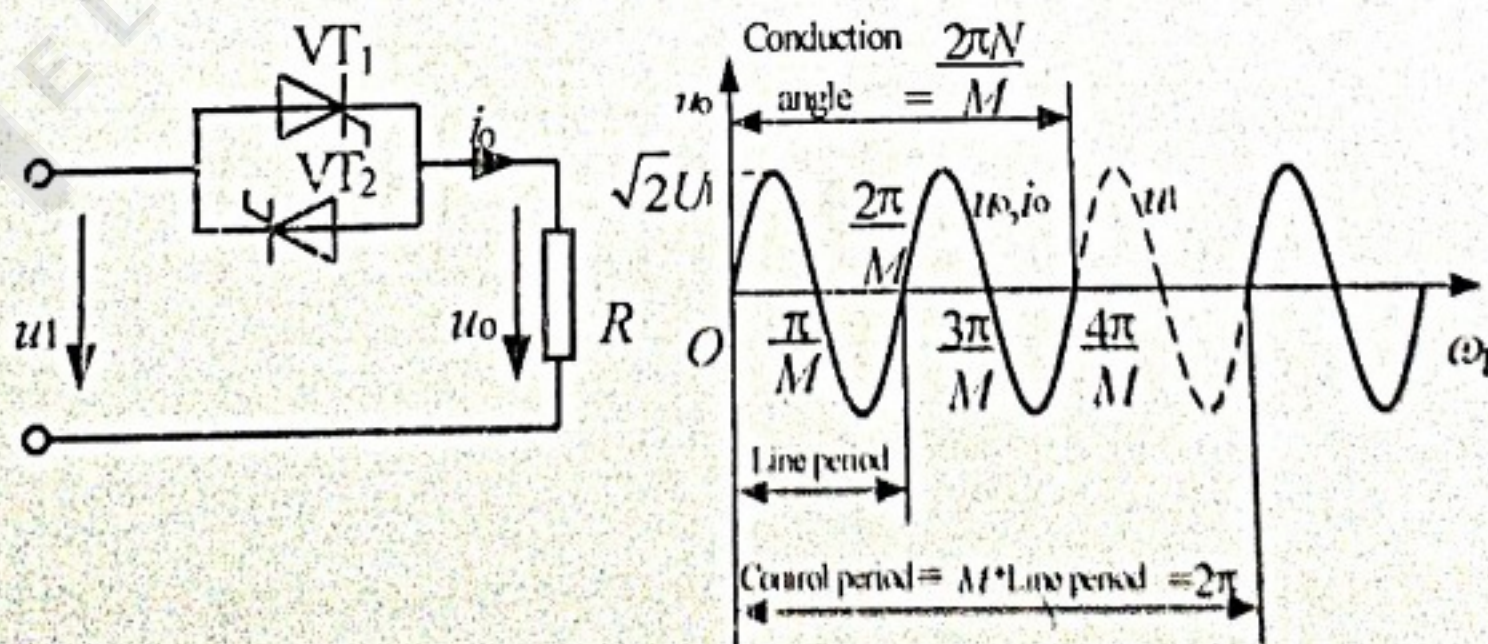
### 4.2.1 Integral cycle control—AC power controller



Circuit topologies are the same as AC voltage controllers.

Only the control method is different.


Load voltage and current are both sinusoidal when thyristors are conducting.



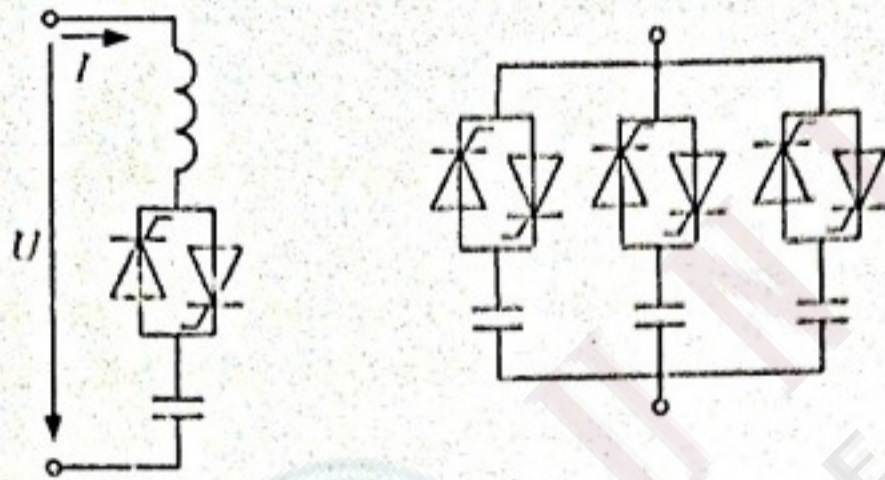
## 4.2.2 Electronic AC switch

Circuit topologies are the same as AC voltage controllers. But the back-to-back thyristors are just used like a switch to turn the equipment on or off.

Application—Thyristor-switched capacitor (TSC)


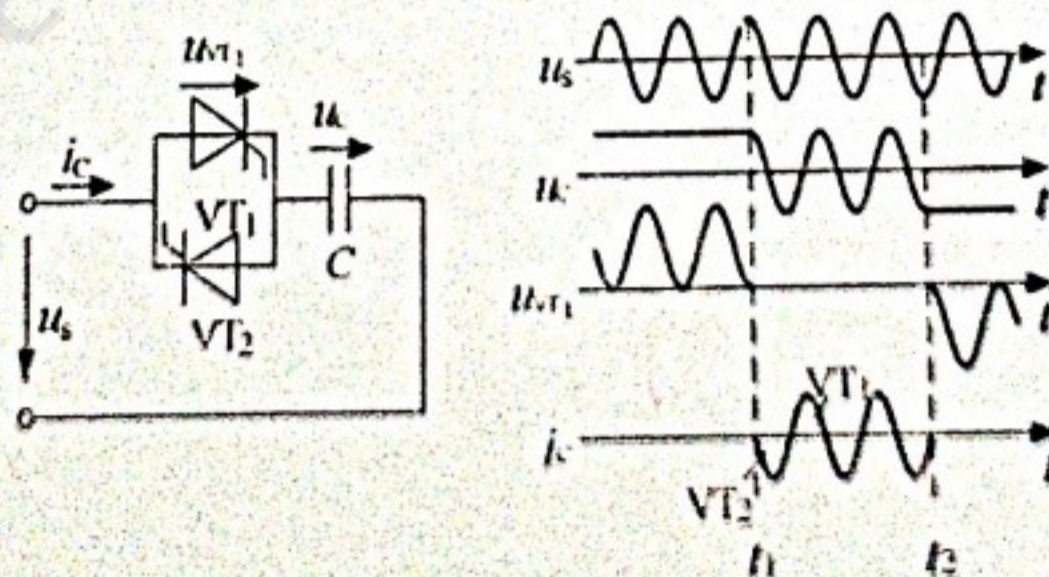
### TSC waveforms when the capacitor is switched in/out



The voltage across the thyristor must be nearly zero when switching in the capacitor, and the current of the thyristor must be zero when switching out the capacitor.

$V_{VT} \rightarrow$  zero switch on  
 $i_c \rightarrow$  zero switch off







## ECE 8830 - Electric Drives

---

### Topic 10: Cycloconverters

↓  
AC Fixed Frequency → AC variable Frequency

## Introduction

---

Cycloconverters directly convert ac signals of one frequency (usually line frequency) to ac signals of variable frequency. These variable frequency ac signals can then be used to directly control the speed of ac motors.

Thyristor-based cycloconverters are typically used in low speed, high power (multi-MW) applications for driving induction and wound field synchronous motors.



## Phase-Controlled Cycloconverters

The basic principle of cycloconversion is illustrated by the single phase-to-single phase converter shown below.

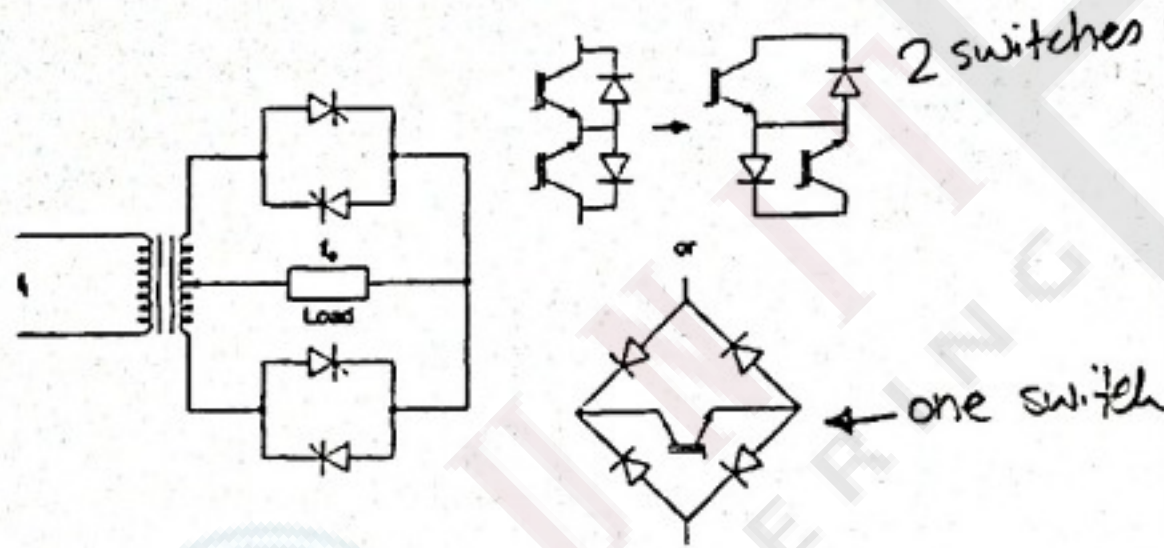


Figure 4.3 Single-phase-to-single-phase cycloconverter circuit showing ac switch configurations


## Phase-Controlled Cycloconverters (cont'd)

A positive center-tap thyristor converter is connected in anti-parallel with a negative converter of the same type. This allows current/voltage of either polarity to be controlled in the load.

The waveforms are shown on the next slide.



## Phase-Controlled Cycloconverters (cont'd)

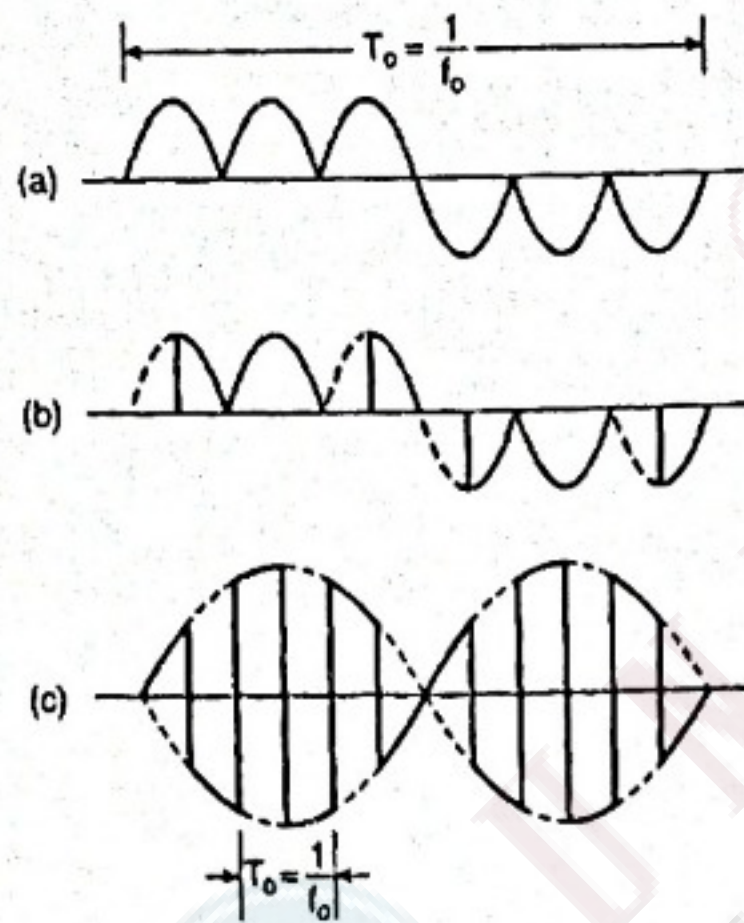

**Figure 4.4** Fabricated waveforms for Figure 4.3 (a) Integral half-cycle control, (b) Waveform with firing angle modulation, (c) Waveform with step-up cycloconversion

## Phase-Controlled Cycloconverters (cont'd)

An integral half-cycle output wave is created which has a fundamental frequency  $f_o = (1/n) f_i$ , where  $n$  is the number of input half-cycles per half-cycle of the output. The thyristor firing angle can be set to control the fundamental component of the output signal. Step-up frequency conversion can be achieved by alternately switching high frequency switching devices (e.g. IGBTs, instead of thyristors) between positive and negative limits at high frequency to generate carrier-frequency modulated output.



## Phase-Controlled Cycloconverters (cont'd)

3 $\Phi$  to single phase conversion can be achieved using either of the dual converter circuit topologies shown below:

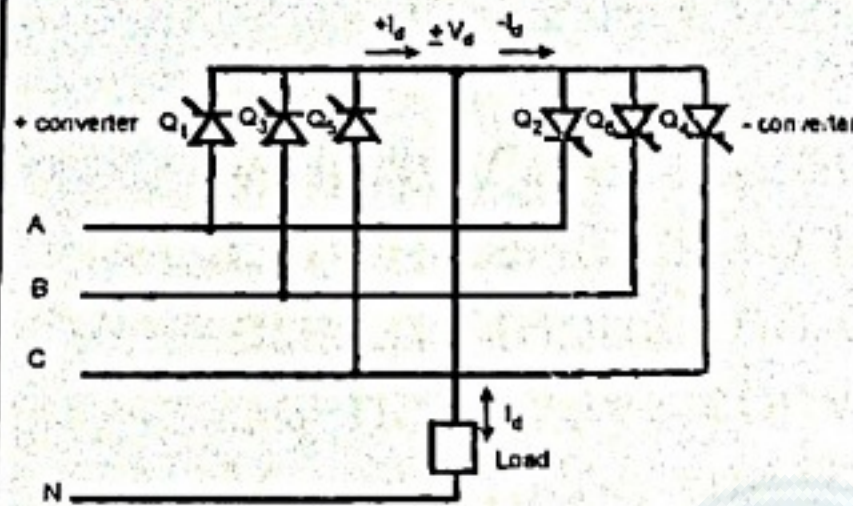


Figure 4.5 Three-phase, half-wave dual converter

$$V_o = 0.675 V_L$$

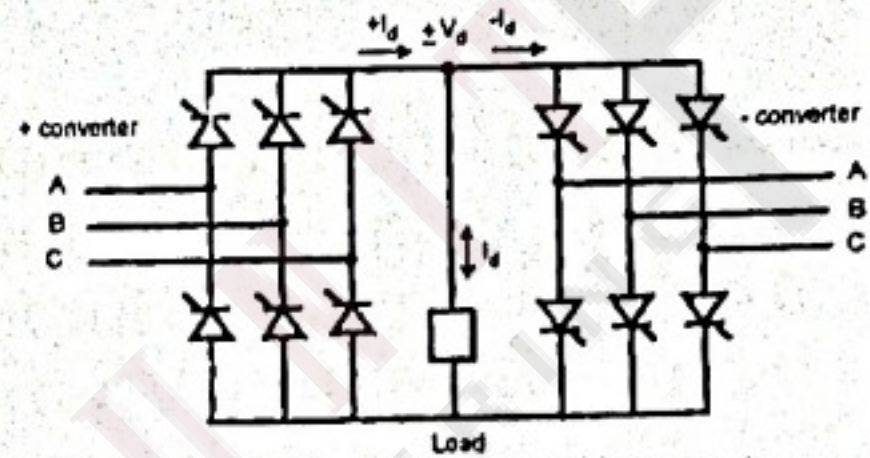


Figure 4.6 Three-phase, dual-bridge converter

$$V_o = 1.35 V_L$$

where  $V_L \equiv$  the rms line voltage

## Phase-Controlled Cycloconverters (cont'd)

A Thevenin equivalent circuit for the dual converter is shown below:

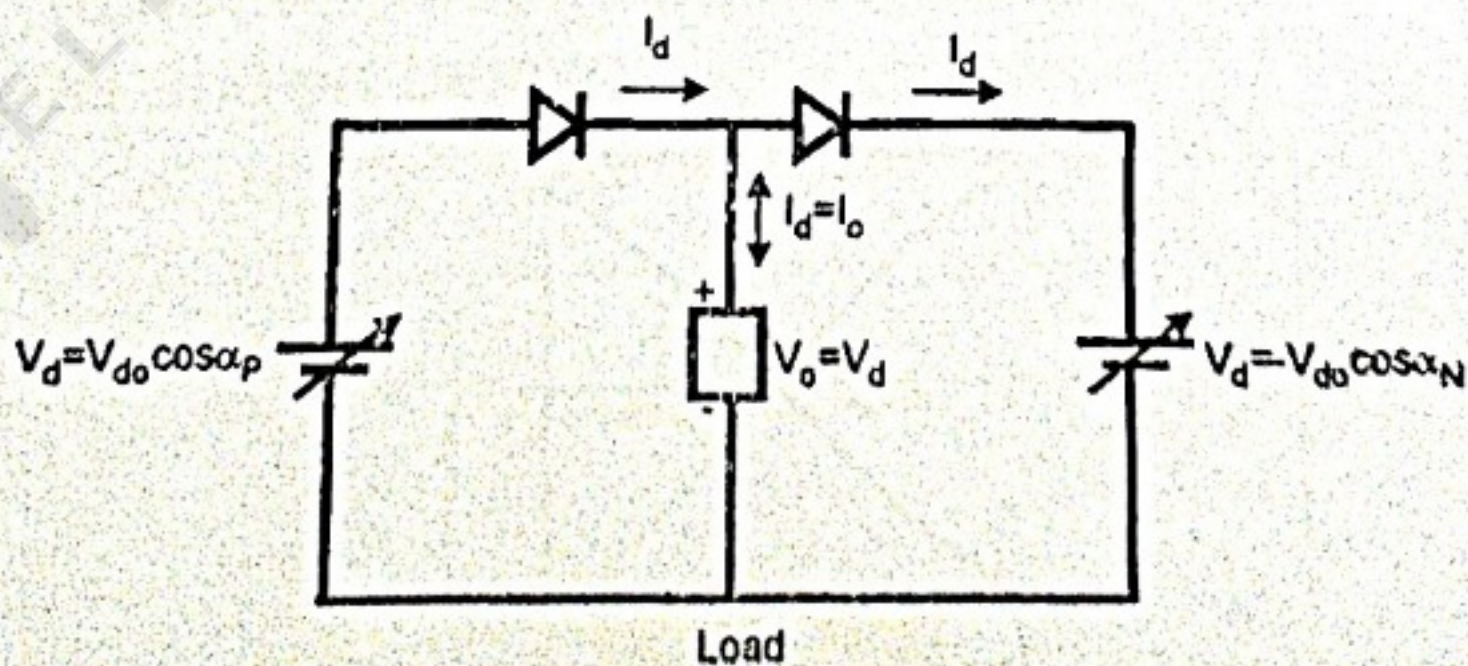


Figure 4.8 Thevenin-equivalent circuit of dual converter



## Phase-Controlled Cycloconverters (cont'd)


The input and output voltages are adjusted to be equal and the load current can flow in either direction. Thus,

$$V_0 = V_d = V_{d0} \cos \alpha_p = -V_{d0} \cos \alpha_n$$

where  $V_{d0}$  is the dc output voltage of each converter at zero firing angle and  $\alpha_p$  and  $\alpha_n$  are the input and output firing angles. For a  $3\Phi$  half-wave converter  $V_{d0} = 0.675V_L$  and  $V_{d0} = 1.35V_L$  for the bridge converter ( $V_L$  is the rms line voltage).
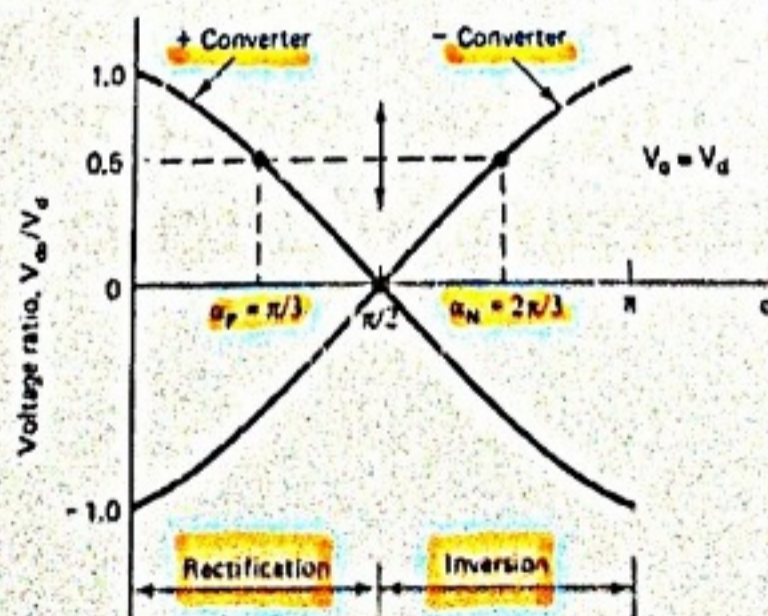
## Phase-Controlled Cycloconverters (cont'd)

Voltage-tracking between the input and output voltages is achieved by setting the sum of the firing angles to  $\pi$ . Positive or negative voltage polarity can be achieved as shown below:



$$\alpha_n + \alpha_p = \pi$$

Figure 4.9 Voltage-tracking control in dual converter showing firing angle relations







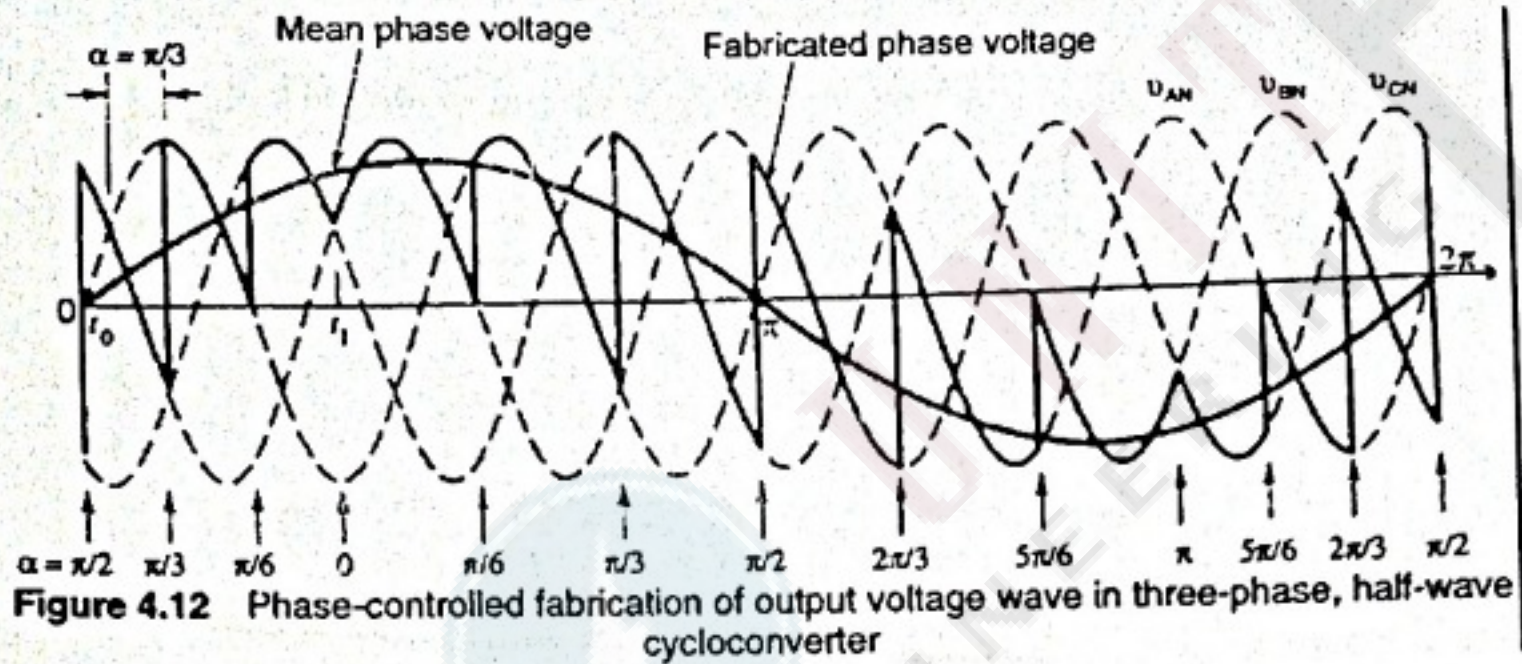
## Phase-Controlled Cycloconverters (cont'd)

An output phase wave is achieved by sinusoidal modulation of the thyristor firing angles.






## Chapter 4 DC to AC Conversion (INVERTER)

- General concept
- Single-phase inverter
- Harmonics
- Modulation
- Three-phase inverter
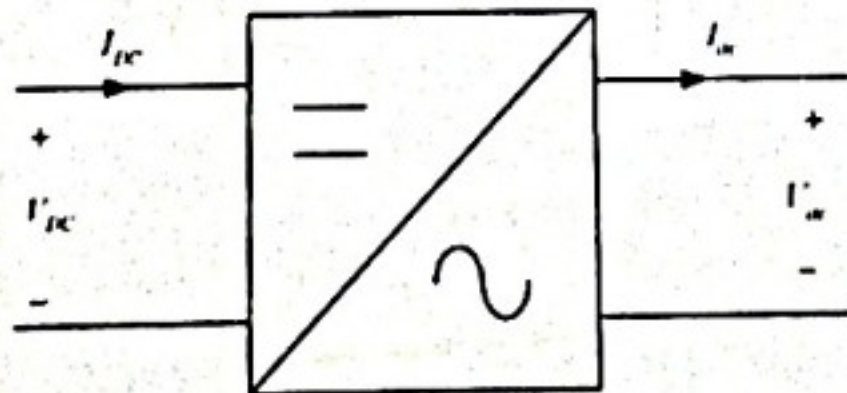
### DC to AC Converter (Inverter)

- DEFINITION: Converts DC to AC power by switching the *DC input voltage (or current)* in a pre-determined sequence so as to generate *AC voltage (or current) output*.
- General block diagram





- TYPICAL APPLICATIONS:
  - Un-interruptible power supply (UPS), Industrial (induction motor) drives, Traction, HVDC




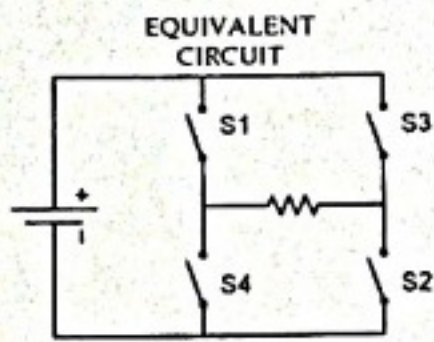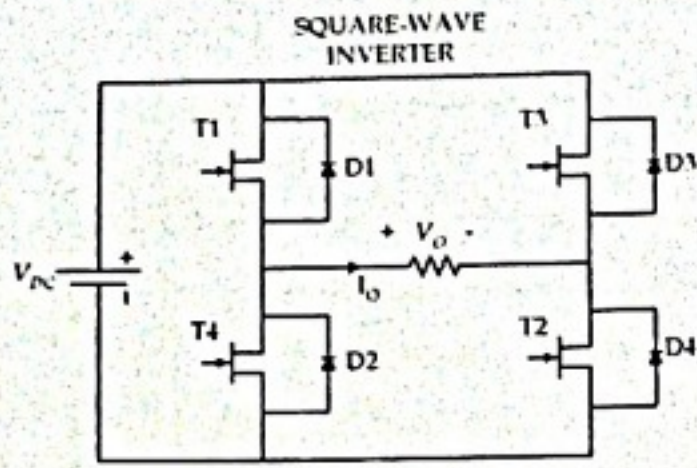
## Simple square-wave inverter (1)

- To illustrate the concept of AC waveform generation




## AC Waveform Generation

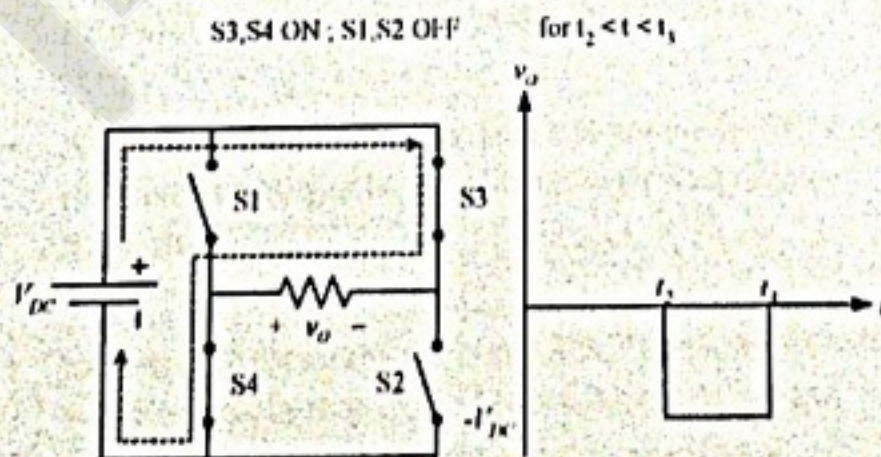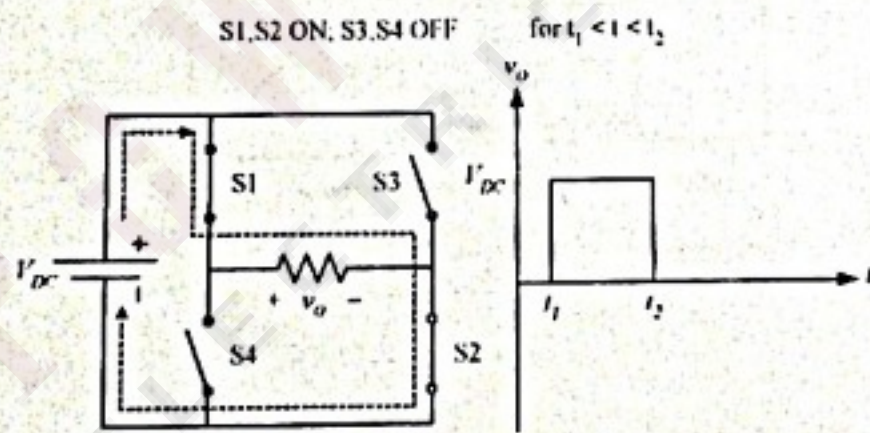


if  $t_2$  both at the same moment  
it'll produce square wave.



## AC Waveforms

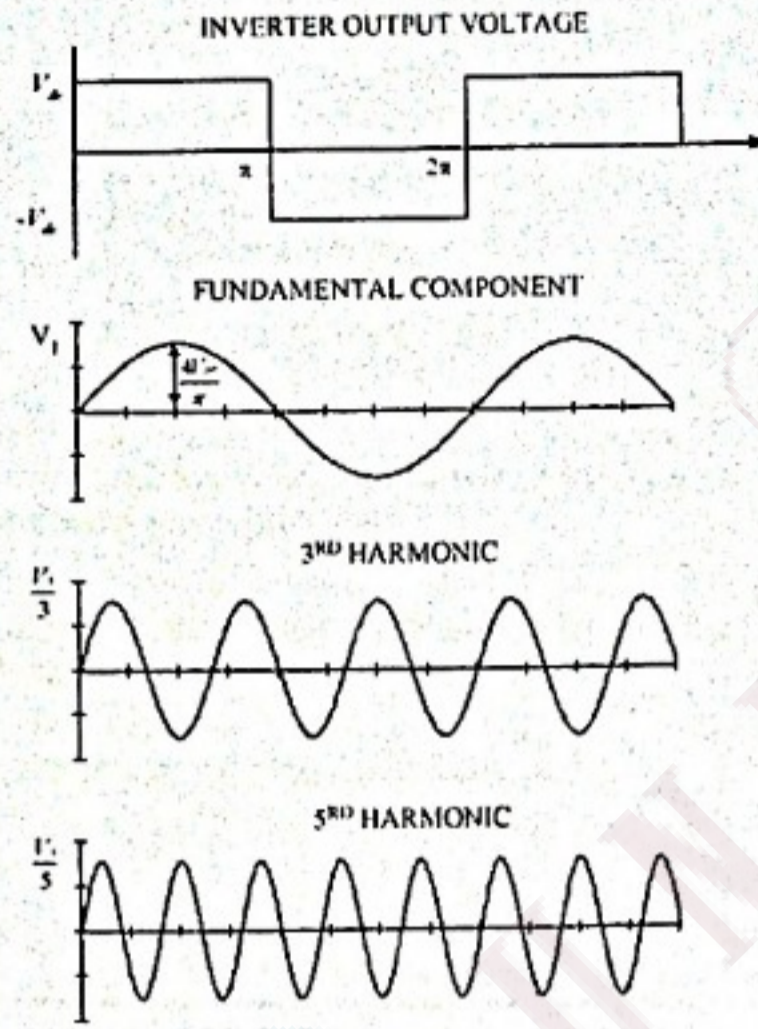


## Harmonics Filtering

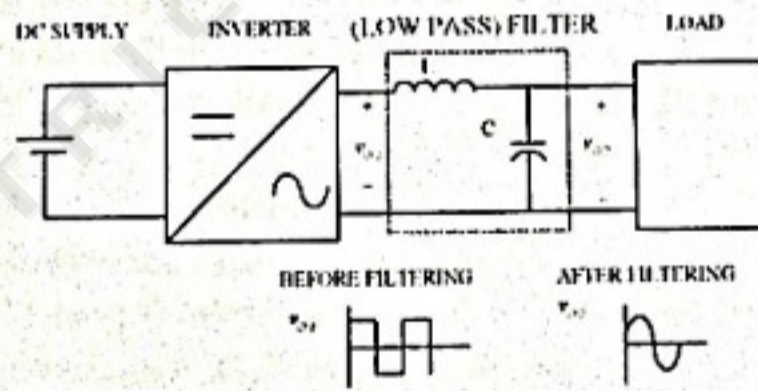

- Output of the inverter is "chopped AC voltage with zero DC component". It contains harmonics.
- An LC section low-pass filter is normally fitted at the inverter output to reduce the high frequency harmonics.
- In some applications such as UPS, "high purity" sine wave output is required. Good filtering is a must.
- In some applications such as AC motor drive, filtering is not required.


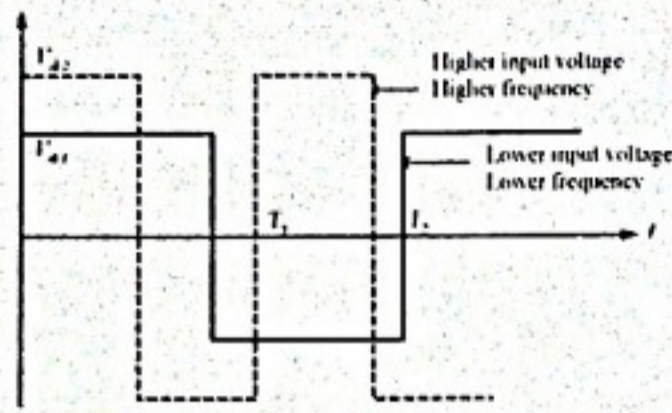
## Variable Voltage Variable Frequency Capability



- Output voltage frequency can be varied by “period” of the square-wave pulse.
- Output voltage amplitude can be varied by varying the “magnitude” of the DC input voltage.
- Very useful: e.g. variable speed induction motor drive

## Output voltage harmonics/ distortion

- Harmonics cause distortion on the output voltage.
- Lower order harmonics (3<sup>rd</sup>, 5<sup>th</sup> etc) are very difficult to filter, due to the filter size and high filter order. They can cause serious voltage distortion.
- Why need to consider harmonics?
  - Sinusoidal waveform quality.
  - “Power Quality” issue.
  - Harmonics may cause degradation of equipment. Equipment need to be “de-rated”.
- Total Harmonic Distortion (THD) is a measure to determine the “quality” of a given waveform.



## Fourier Series

- Study of harmonics requires understanding of wave shapes. Fourier Series is a tool to analyse wave shapes.

### Fourier Series

$$a_0 = \frac{1}{\pi} \int_0^{2\pi} f(v) d\theta \quad (\text{"DC" term})$$

$$a_n = \frac{1}{\pi} \int_0^{2\pi} f(v) \cos(n\theta) d\theta \quad (\text{"cos" term})$$


$$b_n = \frac{1}{\pi} \int_0^{2\pi} f(v) \sin(n\theta) d\theta \quad (\text{"sin" term})$$

### Inverse Fourier

$$f(v) = \frac{1}{2} a_0 + \sum_{n=1}^{\infty} (a_n \cos n\theta + b_n \sin n\theta)$$

where  $\theta = \omega t$

## Harmonics of square-wave (1)

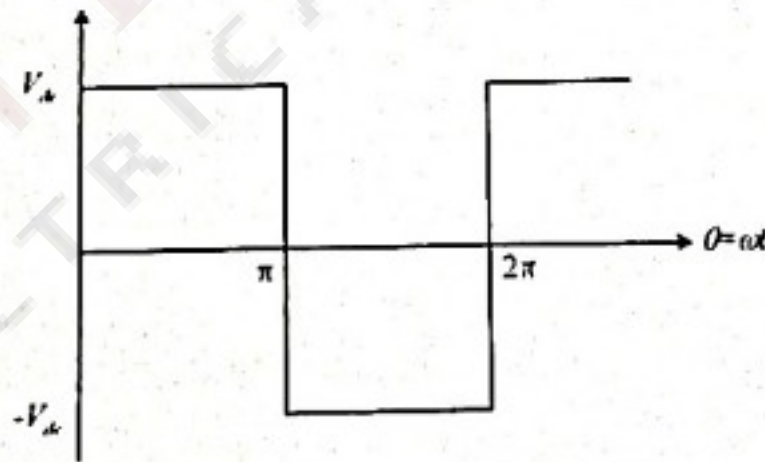

$$a_0 = \frac{1}{\pi} \left[ \int_0^{\pi} V_{dc} d\theta + \int_{\pi}^{2\pi} -V_{dc} d\theta \right] = 0$$

$$a_n = \frac{V_{dc}}{\pi} \left[ \int_0^{\pi} \cos(n\theta) d\theta - \int_{\pi}^{2\pi} \cos(n\theta) d\theta \right] = 0$$

$$b_n = \frac{V_{dc}}{\pi} \left[ \int_0^{\pi} \sin(n\theta) d\theta - \int_{\pi}^{2\pi} \sin(n\theta) d\theta \right]$$



## Harmonics of square wave (2)

Solving,

$$\begin{aligned}
 b_n &= \frac{V_{dc}}{n\pi} \left[ -\cos(n\theta) \Big|_0^\pi + \cos(n\theta) \Big|_\pi^{2\pi} \right] \\
 &= \frac{V_{dc}}{n\pi} \left[ (\cos 0 - \cos n\pi) + (\cos 2n\pi - \cos n\pi) \right] \\
 &= \frac{V_{dc}}{n\pi} \left[ (1 - \cos n\pi) + (1 - \cos n\pi) \right] \\
 &= \frac{2V_{dc}}{n\pi} (1 - \cos n\pi)
 \end{aligned}$$

When  $n$  is even,  $\cos n\pi = 1$


$$b_n = 0$$

(i.e. even harmonics do not exist)

When  $n$  is odd,  $\cos n\pi = -1$

$$b_n = \frac{4V_{dc}}{n\pi}$$

## Quasi-square wave (QSW)

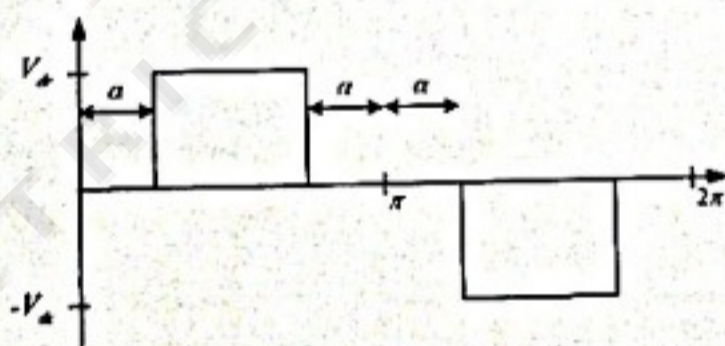

Note that  $a_n = 0$ . (due to half-wave symmetry)

$$\begin{aligned}
 b_n &= 2 \left[ \frac{1}{\pi} \int_\alpha^{\pi-\alpha} V_{dc} \sin(n\theta) d\theta \right] = \frac{2V_{dc}}{n\pi} \left[ -\cos n\theta \Big|_\alpha^{\pi-\alpha} \right] \\
 &= \frac{2V_{dc}}{n\pi} [\cos(n\alpha) - \cos n(\pi - \alpha)]
 \end{aligned}$$

Expanding:

$$\cos n(\pi - \alpha) = \cos(n\pi - n\alpha)$$

$$= \cos n\pi \cos n\alpha + \sin n\pi \sin n\alpha = \cos n\pi \cos n\alpha$$

$$\Rightarrow b_n = \frac{2V_{dc}}{n\pi} [\cos(n\alpha) - \cos n\pi \cos n\alpha]$$

$$= \frac{2V_{dc}}{n\pi} \cos(n\alpha) [1 - \cos n\pi]$$



## Harmonics control

If  $n$  is even,  $\Rightarrow b_n = 0$ ,

If  $n$  is odd,  $\Rightarrow b_n = \frac{4V_{dc}}{n\pi} \cos(n\alpha)$

In particular, amplitude of the fundamental is :

$$b_1 = \frac{4V_{dc}}{\pi} \cos(\alpha)$$

*Note:*

The fundamental,  $b_1$ , is controlled by varying  $\alpha$


Harmonics can also be controlled by adjusting  $\alpha$ ,

Harmonics Elimination :

For example if  $\alpha = 30^\circ$ , then  $b_3 = 0$ , or the third harmonic is eliminated from the waveform. In general, harmonic  $n$  will be eliminated if :

$$\alpha = \frac{90^\circ}{n}$$

## Half-bridge inverter (1)

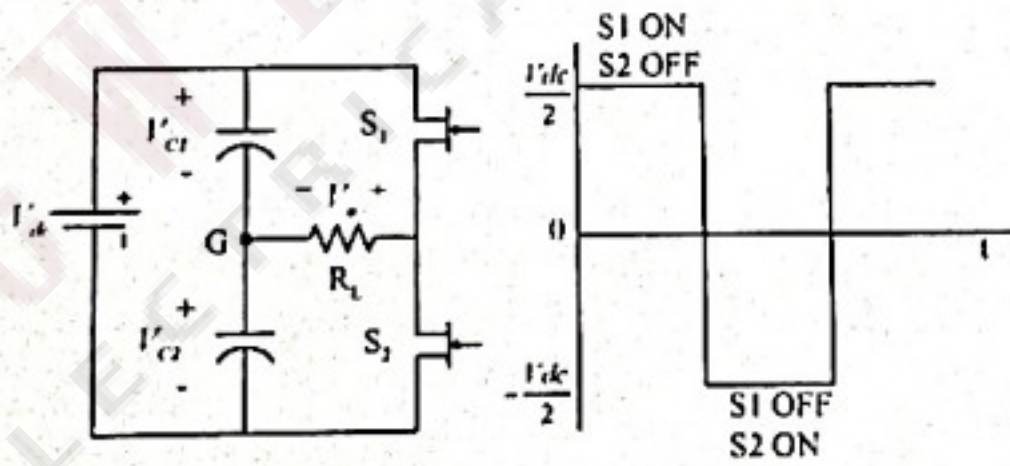


- Also known as the "inverter leg".
- Basic building block for full bridge, three phase and higher order inverters.
- G is the "centre point".
- Both capacitors have the same value. Thus the DC link is equally "split" into two.
- The top and bottom switch has to be "complementary", i.e. If the top switch is closed (on), the bottom must be off, and vice-versa.



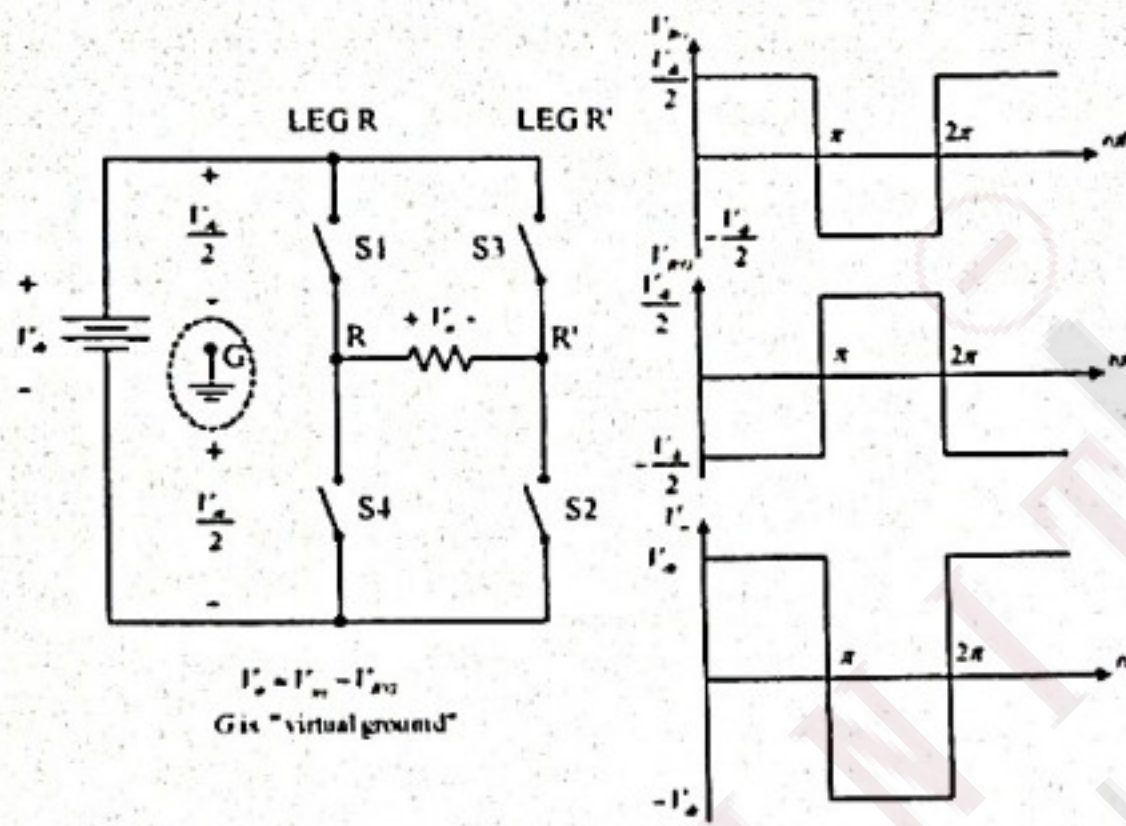
## Single-phase, full-bridge (1)

- Full bridge (single phase) is built from two half-bridge leg.
- The switching in the second leg is "delayed by 180 degrees" from the first leg.


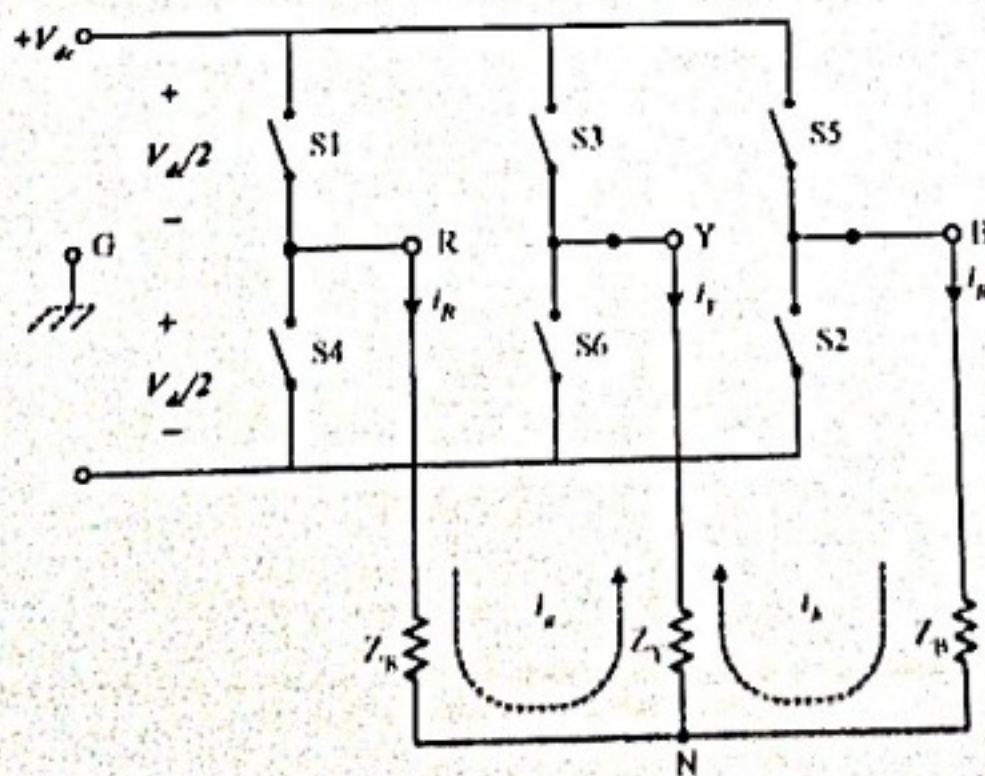
## Three-phase inverter

- Each leg (Red, Yellow, Blue) is delayed by 120 degrees.
- A three-phase inverter with star connected load is shown below





**I. Voltage Source Inverter (VSI)**  
**A. Six-Step VSI (1)**

➤ Six-Step three-phase Voltage Source Inverter

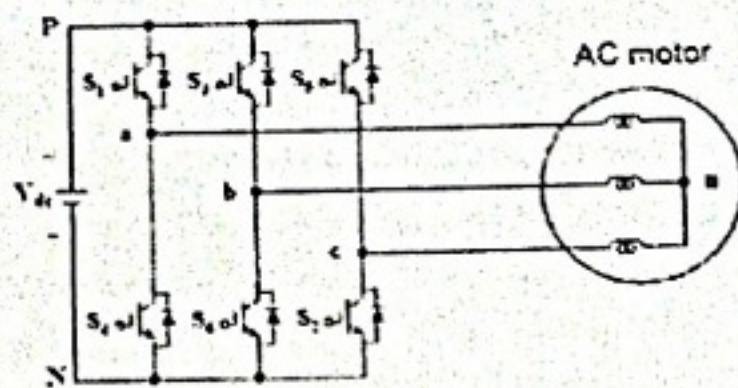


Fig. 1 Three-phase voltage source inverter.

1

**I. Voltage Source Inverter (VSI)**  
**A. Six-Step VSI (2)**

➤ Gating signals, switching sequence and line to negative voltages

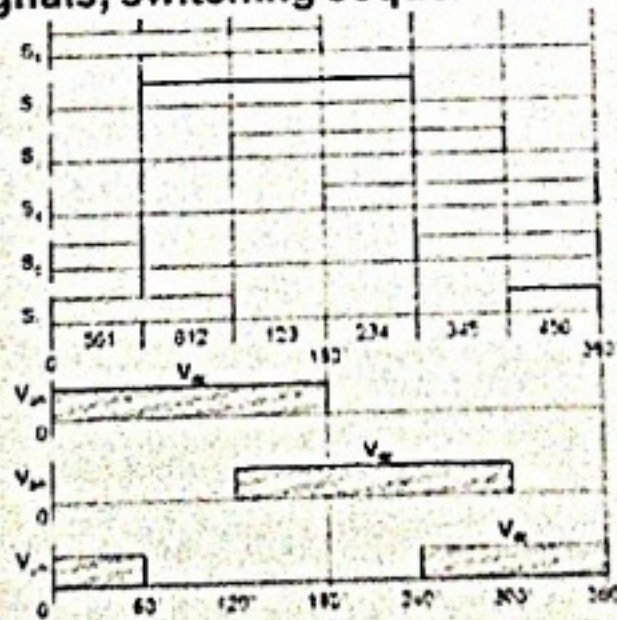


Fig. 2 Waveforms of gating signals, switching sequence, line to negative voltages for six-step voltage source inverter.

1



# I. Voltage Source Inverter (VSI)

## A. Six-Step VSI (3)

➤ Switching Sequence:

561 ( $V_1$ ) → 612 ( $V_2$ ) → 123 ( $V_3$ ) → 234 ( $V_4$ )  
 → 345 ( $V_5$ ) → 456 ( $V_6$ ) → 561 ( $V_1$ )

where, 561 means that  $S_5$ ,  $S_6$  and  $S_1$  are switched on

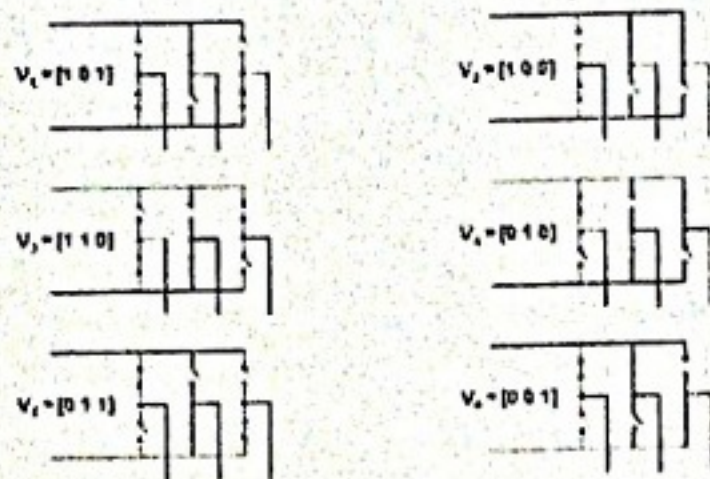


Fig. 3 Six inverter voltage vectors for six-step voltage source inverter.

# I. Voltage Source Inverter (VSI)

## A. Six-Step VSI (4)

➤ Line to line voltages ( $V_{ab}$ ,  $V_{bc}$ ,  $V_{ca}$ )  
 ➤ and line to neutral voltages ( $V_{an}$ ,  $V_{bn}$ ,  $V_{cn}$ )

• Line to line voltages

$$V_{ab} = V_{an} - V_{bn}$$

$$V_{bc} = V_{bn} - V_{cn}$$

$$V_{ca} = V_{cn} - V_{an}$$

• Phase voltages

$$V_{an} = 2/3V_{an} - 1/3V_{bn} - 1/3V_{cn}$$

$$V_{bn} = -1/3V_{an} + 2/3V_{bn} - 1/3V_{cn}$$

$$V_{cn} = -1/3V_{an} - 1/3V_{bn} + 2/3V_{cn}$$


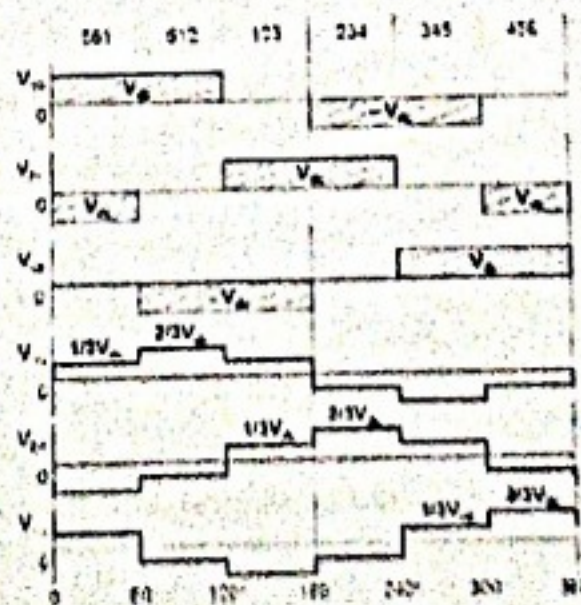


Fig. 4 Waveforms of line to neutral (phase) voltages and line to line voltages for six-step voltage source inverter.

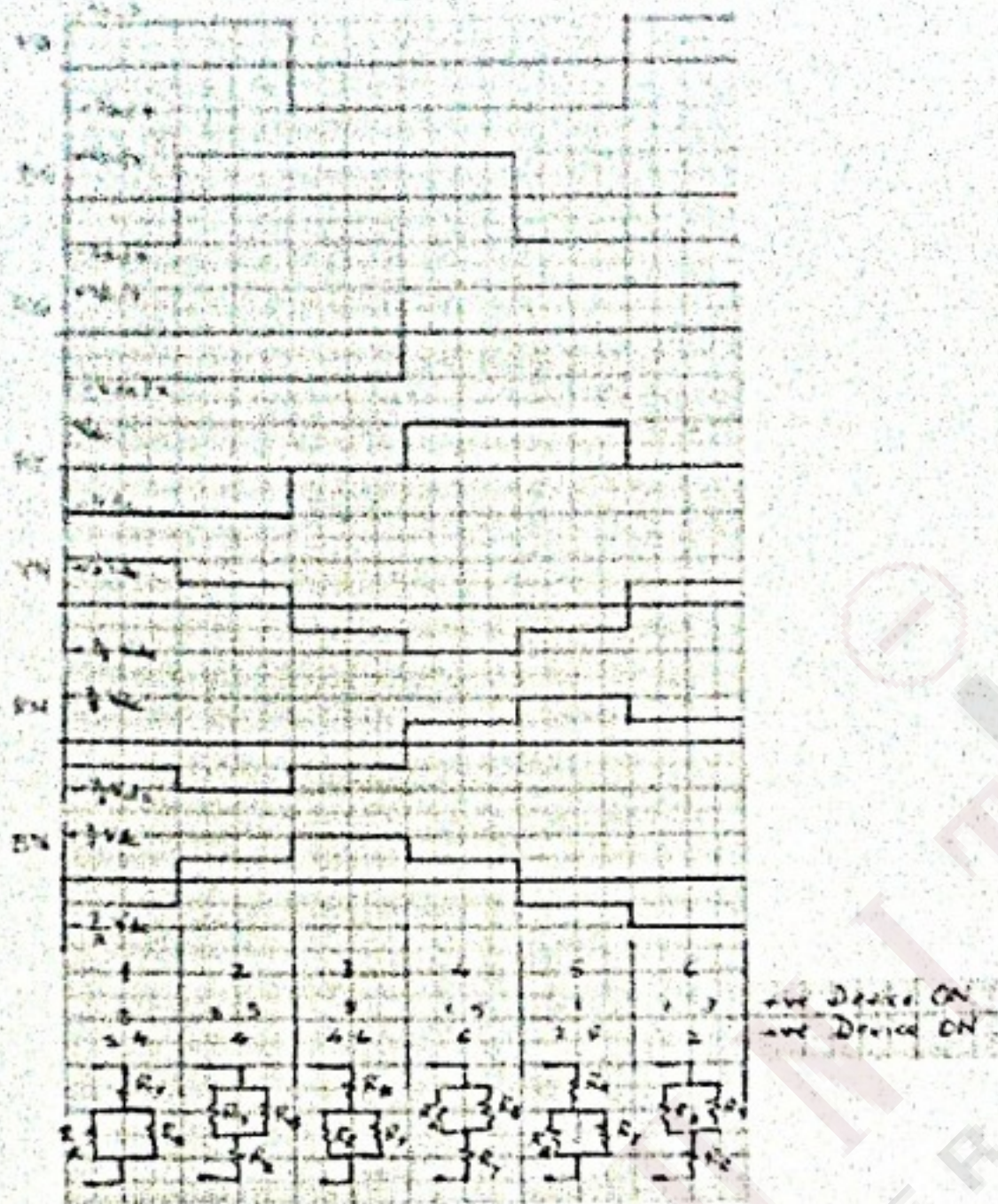

## Three phase inverter waveforms



### I. Voltage Source Inverter (VSI)

#### A. Six-Step VSI (5)

➤ Amplitude of line to line voltages ( $V_{ab}$ ,  $V_{bc}$ ,  $V_{ca}$ )

• Fundamental Frequency Component ( $V_{ab1}$ )

$$(V_{ab})_1(\text{rms}) = \frac{\sqrt{3}}{\sqrt{2}} \frac{4}{\pi} \frac{V_{dc}}{2} = \frac{\sqrt{6}}{\pi} V_{dc} \approx 0.78V_{dc}$$

• Harmonic Frequency Components ( $V_{abh}$ )

: amplitudes of harmonics decrease inversely proportional to their harmonic order

$$(V_{ab})_h(\text{rms}) = \frac{0.78}{h} V_{dc}$$

where,  $h = 6n \pm 1$  ( $n = 1, 2, 3, \dots$ )



## I. Voltage Source Inverter (VSI)

### A. Six-Step VSI (6)

#### ➤ Characteristics of Six-step VSI

- It is called "six-step inverter" because of the presence of six "steps" in the line to neutral (phase) voltage waveform
- Harmonics of order three and multiples of three are absent from both the line to line and the line to neutral voltages and consequently absent from the currents
- Output amplitude in a three-phase inverter can be controlled by only change of DC-link voltage ( $V_{dc}$ )

8

## I. Voltage Source Inverter (VSI)

### B. Pulse-Width Modulated VSI (1)

#### ➤ Objective of PWM

- Control of inverter output voltage
- Reduction of harmonics

#### ➤ Disadvantages of PWM

- Increase of switching losses due to high PWM frequency
- Reduction of available voltage
- EMI problems due to high-order harmonics

9



I. Voltage Source Inverter (VSI)  
 B. Pulse-Width Modulated VSI (2)

➤ Pulse-Width Modulation (PWM)

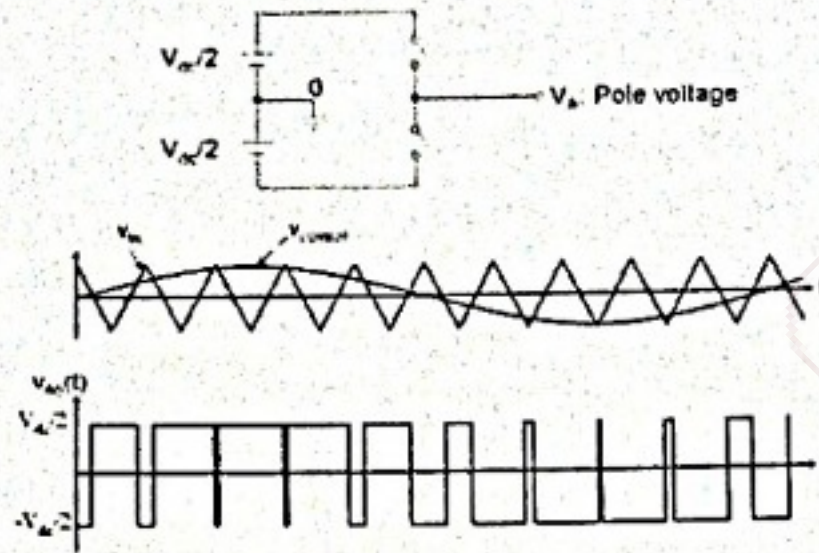


Fig. 5 Pulse-width modulation.  
 10

I. Voltage Source Inverter (VSI)  
 B. Pulse-Width Modulated VSI (3)

➤ Inverter output voltage

- When  $v_{control} > v_{tri}$ ,  $V_{Ao} = V_{dc}/2$
- When  $v_{control} < v_{tri}$ ,  $V_{Ao} = -V_{dc}/2$

➤ Control of inverter output voltage

- PWM frequency is the same as the frequency of  $v_{tri}$
- Amplitude is controlled by the peak value of  $v_{control}$
- Fundamental frequency is controlled by the frequency of  $v_{control}$

➤ Modulation Index (m)

$$\therefore m = \frac{v_{control}}{v_{tri}} = \frac{\text{peak of } (V_{Ao})_1}{V_{dc}/2}$$

where,  $(V_{Ao})_1$ : fundamental frequency component of  $V_{Ao}$



## II. PWM METHODS

### A. Sine PWM (1)

#### ➤ Three-phase inverter

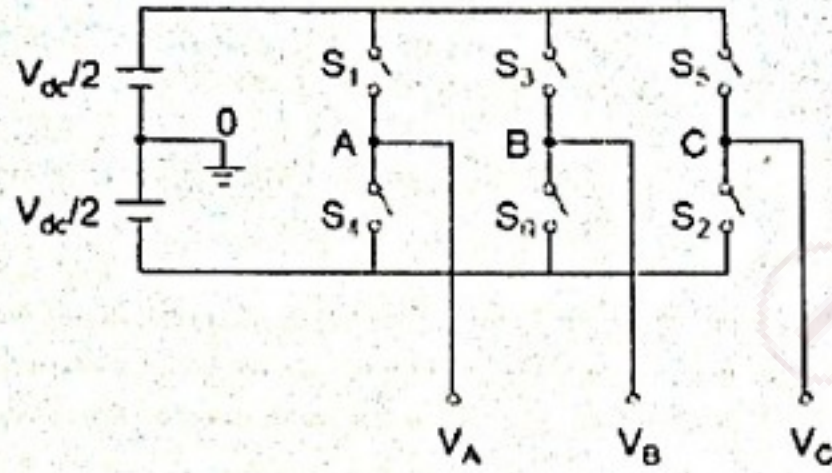


Fig. 6 Three-phase Sine PWM Inverter.

12

## II. PWM METHODS

### A. Sine PWM (2)

#### ➤ Three-phase sine PWM waveforms

- Frequency of  $v_{tri}$  and  $v_{control}$

⇒ Frequency of  $v_{tri} = f_c$

⇒ Frequency of  $v_{control} = f_1$

where,  $f_c =$  PWM frequency

$f_1 =$  Fundamental frequency

- Inverter output voltage

⇒ When  $v_{control} > v_{tri}$   $V_{AB} = V_{dc}/2$

⇒ When  $v_{control} < v_{tri}$   $V_{AB} = -V_{dc}/2$

where,  $V_{AB} = V_{AO} - V_{BO}$

$V_{BC} = V_{BO} - V_{CO}$

$V_{CA} = V_{CO} - V_{AO}$

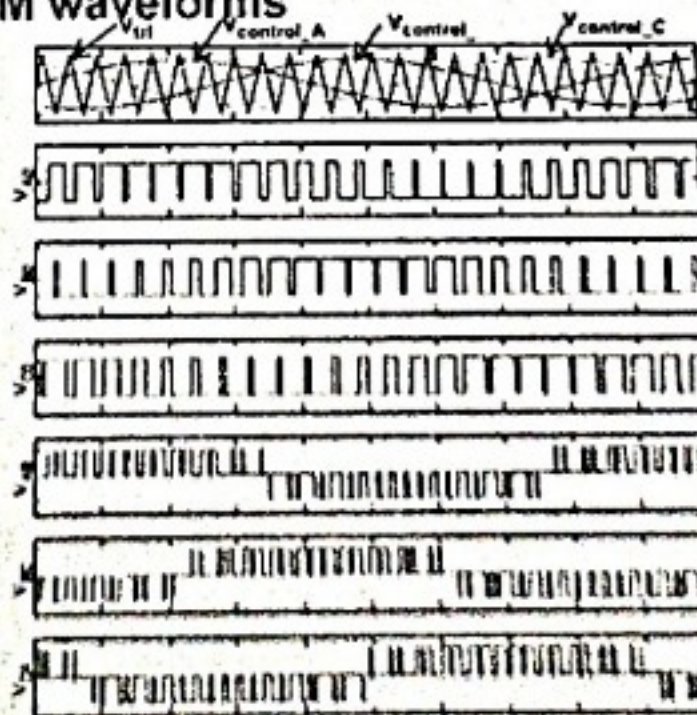


Fig. 7 Waveforms of three-phase sine PWM inverter.

13



## II. PWM METHODS

### A. Sine PWM (3)

#### ➤ Amplitude modulation ratio ( $m_a$ )

$$\therefore m_a = \frac{\text{peak amplitude of } v_{\text{control}} \text{ or peak value of } (V_m)_1}{\text{amplitude of } v_{\text{tri}}} = \frac{V_m}{V_{dc}/2}$$


where,  $(V_m)_1$ : fundamental frequency component of  $V_m$

#### ➤ Frequency modulation ratio ( $m_f$ )

$$m_f = \frac{f_c}{f_1} \text{ where, } f_c = \text{PWM frequency and } f_1 = \text{fundamental frequency}$$

- $m_f$  should be an odd integer
  - ⇒ If  $m_f$  is not an integer, there may exist subharmonics at output voltage
  - ⇒ If  $m_f$  is not odd, DC component may exist and even harmonics are present at output voltage
- $m_f$  should be a multiple of 3 for three-phase PWM inverter
  - ⇒ An odd multiple of 3 and even harmonics are suppressed

## Pulse Width Modulation (PWM)

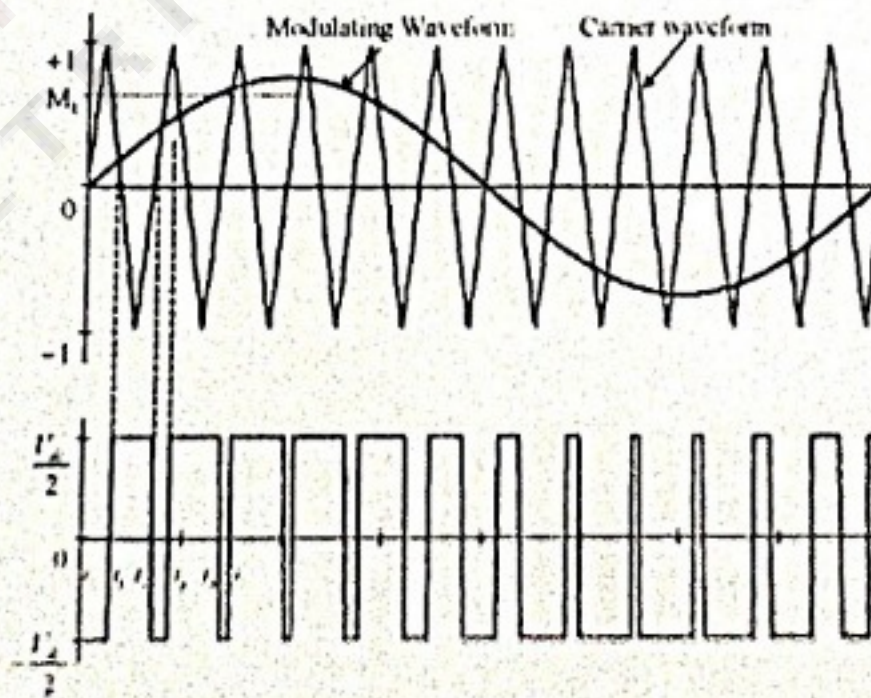


- Triangulation method (Natural sampling)
  - Amplitudes of the triangular wave (carrier) and sine wave (modulating) are compared to obtain PWM waveform. Simple analogue comparator can be used.
  - Basically an analogue method. Its digital version, known as REGULAR sampling is widely used in industry.



## PWM types

- Natural (sinusoidal) sampling (as shown on previous slide)
  - Problems with analogue circuitry, e.g. Drift, sensitivity etc.
- Regular sampling
  - simplified version of natural sampling that results in simple digital implementation
- Optimised PWM
  - PWM waveform are constructed based on certain performance criteria, e.g. THD.
- Harmonic elimination/minimisation PWM
  - PWM waveforms are constructed to eliminate some undesirable harmonics from the output waveform spectra.
  - Highly mathematical in nature
- Space-vector modulation (SVM)
  - A simple technique based on volt-second that is normally used with three-phase inverter motor-drive

## Modulation Index, Ratio

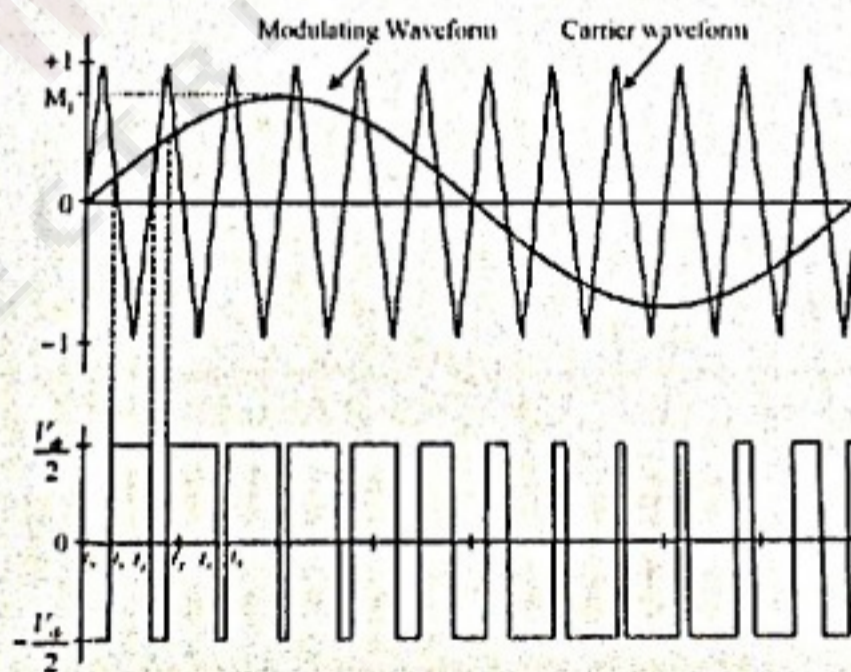

Modulation Index (Modulation Depth) =  $M_1$  :

$$M_1 = \frac{\text{Amplitude of the modulating waveform}}{\text{Amplitude of the carrier waveform}}$$

Modulation Ratio (Frequency Ratio) =  $M_R (= p)$

$$M_R = p = \frac{\text{Frequency of the carrier waveform}}{\text{Frequency of the modulating waveform}}$$



## Modulation Index, Ratio

Modulation Index determines the output voltage fundamental component

If  $0 < M_1 < 1$ ,

$$V_1 = M_1 V_m$$

where  $V_1, V_m$  are fundamental of the output voltage and input (DC) voltage, respectively.


Modulation ratio determines the incident (location) of harmonics in the spectra.

The harmonics are normally located at :

$$f = kM_R(f_m)$$


where  $f_m$  is the frequency of the modulating signal and  $k$  is an integer (1,2,3...)

## Regular sampling

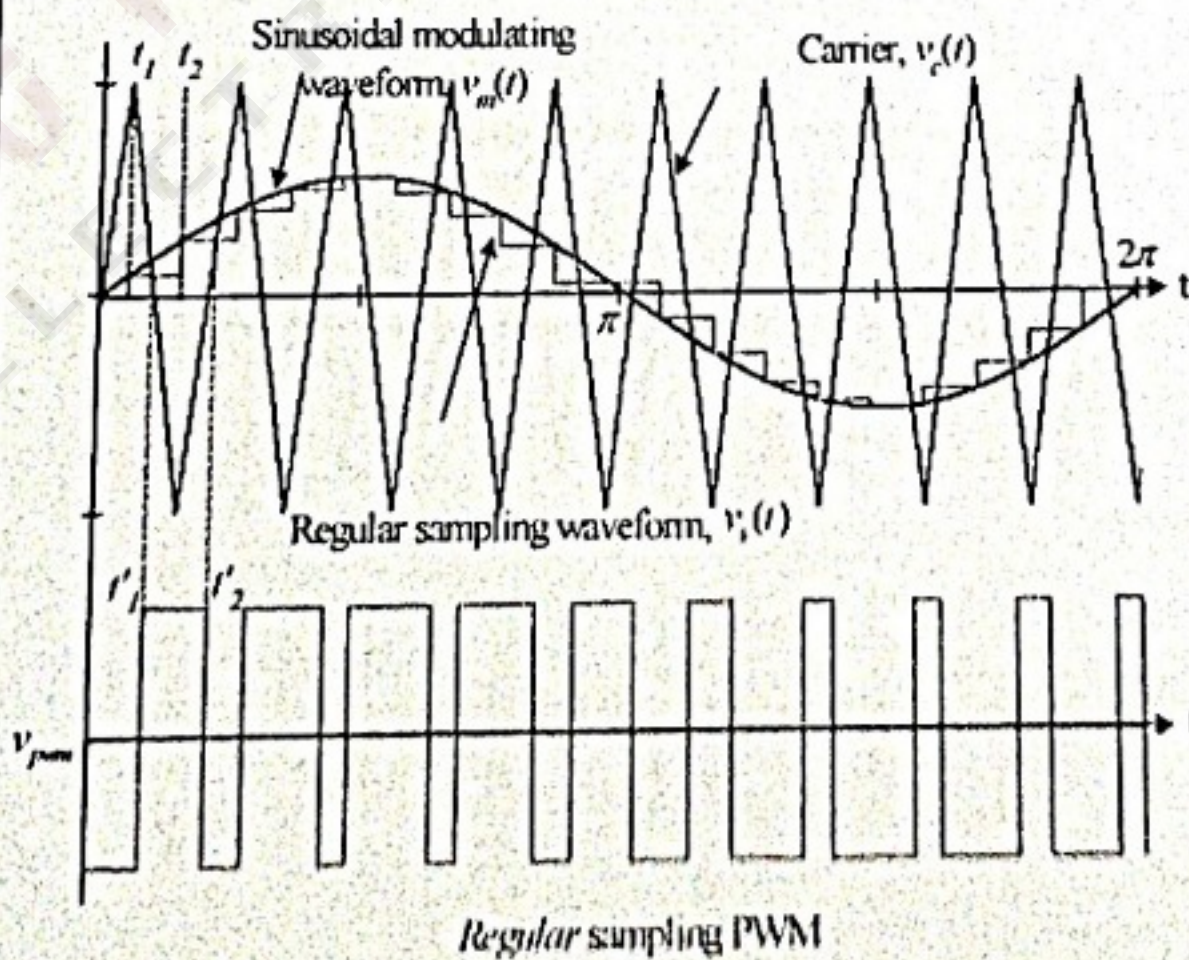



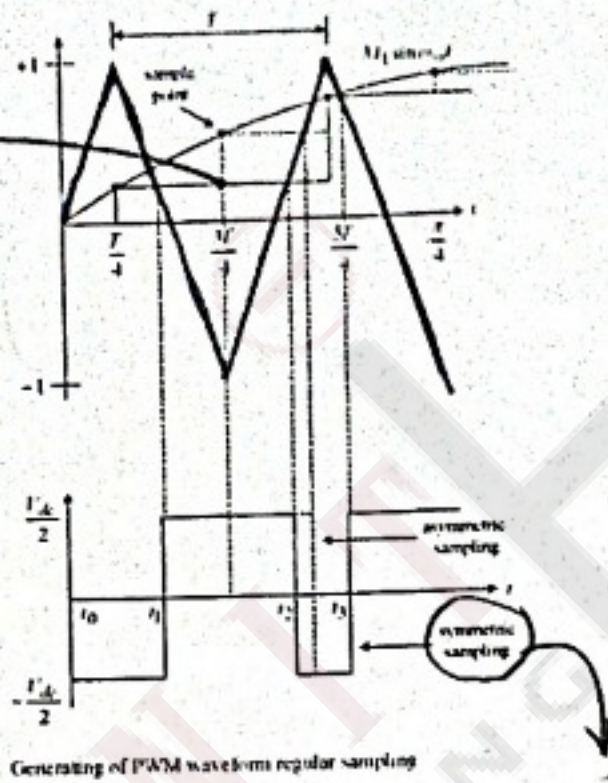
## Asymmetric and symmetric regular sampling



Intersection point between carrier & square wave

من صفة للموجة في كل لحظة في كل لحظة  
 على افتراض نقطة التقاطع (الامتداد الزمني)  
 فين يبتلع ال carrier ساعة ال  
 • Die Asymmetrical

## Bipolar Switching

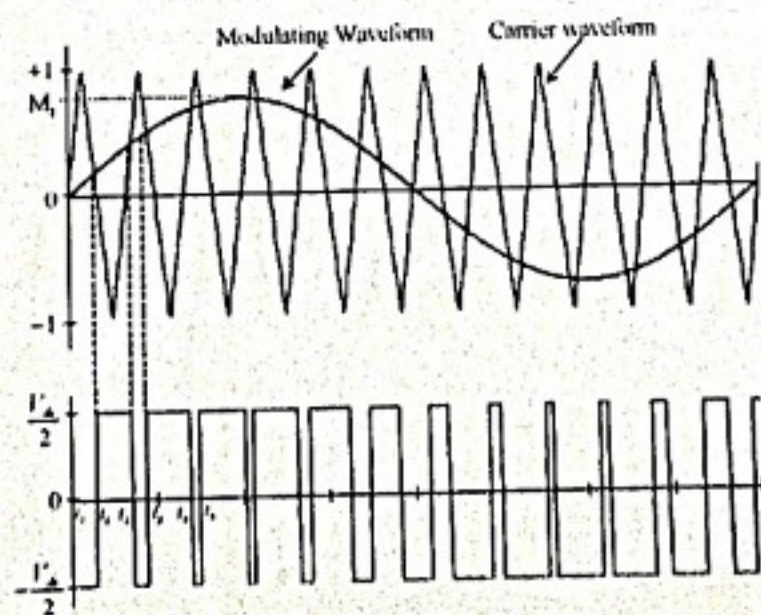







## Three-phase harmonics

- For three-phase inverters, there is significant advantage if  $M_R$  is chosen to be:
  - **Odd:** All even harmonic will be eliminated from the pole-switching waveform.
  - **triplens** (multiple of three (e.g. 3,9,15,21, 27..)): All triplens harmonics will be eliminated from the line-to-line output voltage.
- By observing the waveform, it can be seen that with odd  $M_R$ , the line-to-line voltage shape looks more "sinusoidal".
- As can be noted from the spectra, the phase voltage amplitude is 0.8 (normalised). This is because the modulation index is 0.8. The line voltage amplitude is square root three of phase voltage due to the three-phase relationship

## Effect of odd and "triplens"

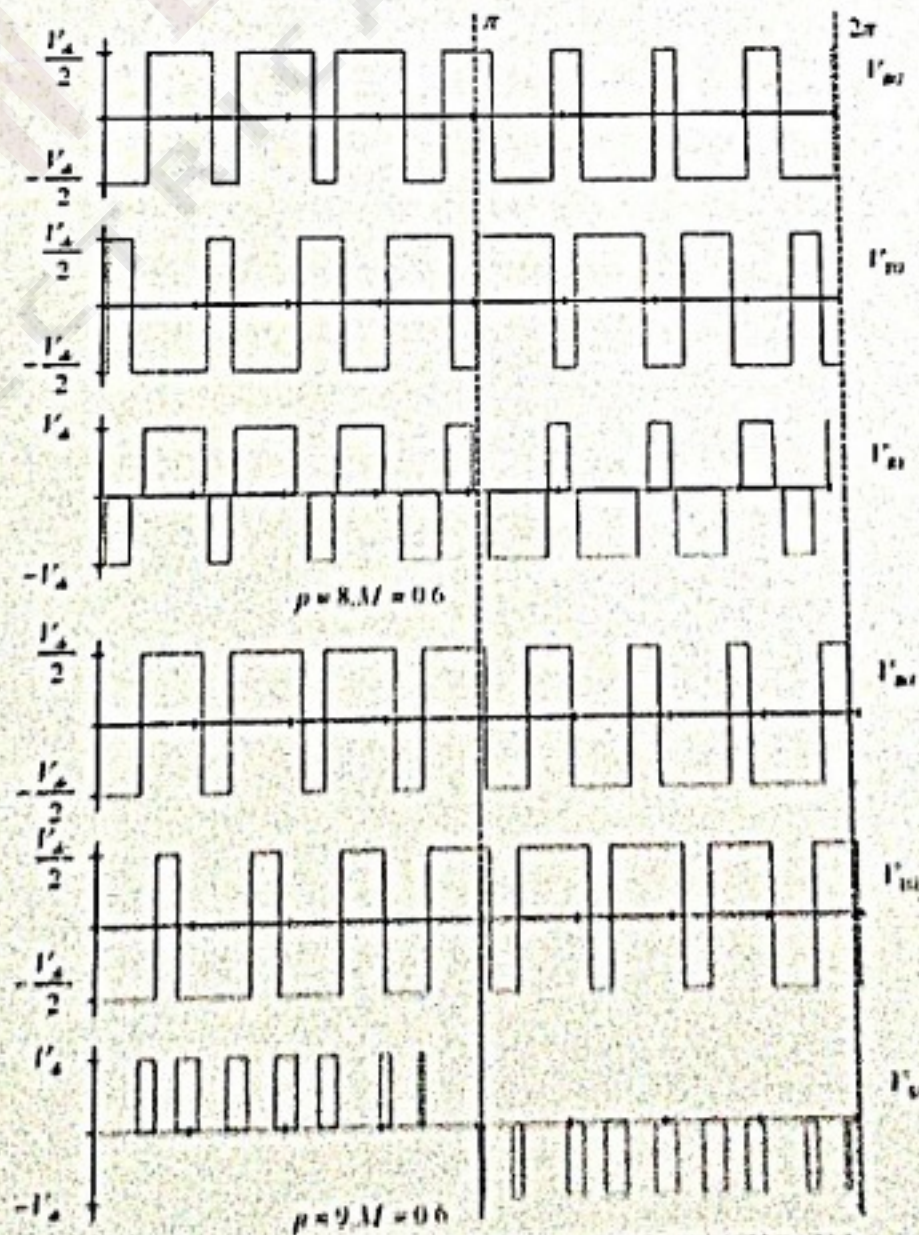


ILLUSTRATION OF BENEFITS OF USING A FREQUENCY RATIO THAT IS A MULTIPLE OF THREE IN A THREE PHASE INVERTER



# Three phase inverter with RL load

- It is desirable to have  $M_R$  as large as possible.
- This will push the harmonic at higher frequencies on the spectrum. Thus filtering requirement is reduced.
- Although the voltage THD improvement is not significant, but the current THD will improve greatly because the load normally has some current filtering effect.
- However, higher  $M_R$  has side effects:
  - Higher switching frequency: More losses.
  - Pulse width may be too small to be constructed. “Pulse dropping” may be required.

